

P1. (10 points) Use algebraic manipulation to show that for three input variables x_1 , x_2 , and x_3 the following is true:

$$\sum m(1, 2, 3, 4, 5, 6, 7) = x_1 + x_2 + x_3$$

P2. (10 points) For the following two expressions, draw the truth table and express each one of them as a sum of minterms and also as a product of maxterms:

$$(XY + Z)(Y + XZ)$$

$$(\bar{A} + B)(\bar{B} + C)$$

P3. (20 points) Find the simplest SOP circuit that implements the function:

$$f(x_1, x_2, x_3) = \sum m(3, 4, 6, 7)$$

Then draw the circuit diagram using only NAND gates.

P4. (20 points) Considering the truth table below, which has three inputs (X, Y, Z) and two outputs (M, N)

X	Y	Z	M	N
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Write the functions M and N in short hand notation using minterms and maxterms. (5 points)
- Write the functions M and N in canonical sum-of-products (SOP) and canonical product-of-sums (POS) forms. (5 points)
- Obtain the simplest SOP expressions for the functions M and N and draw their respective circuit diagrams. (10 points)

P5. (20 points) A circuit that checks for equality has one output f and four inputs x_1, x_2, y_1, y_2 . Let $X=x_1x_2$ and $Y=y_1y_2$ represent two 2-digit binary numbers. The output f should be 1 if the numbers represented by X and Y are equal. Otherwise, f should be 0. For example, if $x_1=1, x_2=0, y_1=0, y_2=1$, then the output should be zero because $X=2$ and $Y=1$ (in decimal). On the other hand, if $x_1=x_2=1$ and $y_1=y_2=1$, then the output should be 1 because the two numbers are equal.

- Show the truth table for f . (10 points)
- Write the canonical sum-of-products expression for the function f . (5 points)
- Write the canonical product-of-sums expression for the function f . (5 points)

P6. (10 points) Show how to implement a NOT gate using:

- 2-input NAND gate(s),
- 2-input NOR gate(s)
- 2-1 multiplexer(s).

For part (a) and part (b), you should use a different approach than simply connecting both terminals to the input signal. Note that you are allowed to connect constant voltages (i.e., logic values 0 or 1) to the gates.

P7. (10 points) Redraw the following circuit using only NAND gates:

