

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Fast Adders

CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev

Administrative Stuff

- **HW5 is out**
- **It is due on Monday Oct 5 @ 4pm.**
- **Please write clearly on the first page (in block capital letters) the following three things:**
 - **Your First and Last Name**
 - **Your Student ID Number**
 - **Your Lab Section Letter**

Administrative Stuff

- **Labs Next Week**
- **Mini-Project**
- **This one is worth 3% of your grade.**
- **Make sure to get all the points.**
- **http://www.ece.iastate.edu/~alexs/classes/2015_Fall_281/labs/Project-Mini/**

Quick Review

The problems in which row are easier to calculate?

$$\begin{array}{r} 82 \\ - 61 \\ \hline ?? \end{array}$$

$$\begin{array}{r} 48 \\ - 26 \\ \hline ?? \end{array}$$

$$\begin{array}{r} 32 \\ - 11 \\ \hline ?? \end{array}$$

$$\begin{array}{r} 82 \\ - 64 \\ \hline ?? \end{array}$$

$$\begin{array}{r} 48 \\ - 29 \\ \hline ?? \end{array}$$

$$\begin{array}{r} 32 \\ - 13 \\ \hline ?? \end{array}$$

The problems in which row are easier to calculate?

$$\begin{array}{r} 82 \\ - 61 \\ \hline 21 \end{array}$$

$$\begin{array}{r} 48 \\ - 26 \\ \hline 22 \end{array}$$

$$\begin{array}{r} 32 \\ - 11 \\ \hline 21 \end{array}$$

Why?

$$\begin{array}{r} 82 \\ - 64 \\ \hline 18 \end{array}$$

$$\begin{array}{r} 48 \\ - 29 \\ \hline 19 \end{array}$$

$$\begin{array}{r} 32 \\ - 13 \\ \hline 19 \end{array}$$

Another Way to Do Subtraction

$$82 - 64 = 82 + 100 - 100 - 64$$

Another Way to Do Subtraction

$$\begin{aligned}82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100\end{aligned}$$

Another Way to Do Subtraction

$$\begin{aligned}82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100 \\ &= 82 + (99 + 1 - 64) - 100\end{aligned}$$

Another Way to Do Subtraction

$$82 - 64 = 82 + 100 - 100 - 64$$

$$= 82 + (100 - 64) - 100$$

$$= 82 + (99 + 1 - 64) - 100$$

$$= 82 + (99 - 64) + 1 - 100$$

Another Way to Do Subtraction

$$82 - 64 = 82 + 100 - 100 - 64$$

$$= 82 + (100 - 64) - 100$$

$$= 82 + (99 + 1 - 64) - 100$$

Does not require borrows

$$= 82 + (99 - 64) + 1 - 100$$

9's Complement (subtract each digit from 9)

$$\begin{array}{r} 99 \\ - 64 \\ \hline 35 \end{array}$$

10's Complement

(subtract each digit from 9 and add 1 to the result)

$$\begin{array}{r} 99 \\ - 64 \\ \hline 35 + 1 = 36 \end{array}$$

Another Way to Do Subtraction

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

Another Way to Do Subtraction

9's complement

$$\begin{aligned} 82 - 64 &= 82 + (99 - 64) + 1 - 100 \\ &= 82 + 35 + 1 - 100 \end{aligned}$$

Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

$$= 82 + (35 + 1) - 100$$

10's complement

Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

$$= 82 + (35 + 1) - 100$$


10's complement

$$= 82 + 36 - 100 \quad // \text{ add the first two}$$


Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + \overset{\text{9's complement}}{(99 - 64)} + 1 - 100 \\ &= 82 + \overset{\text{10's complement}}{(35 + 1)} - 100 \\ &= 82 + 36 - 100 \quad // \text{ add the first two} \\ &= 118 - 100 \quad // \text{ delete the leading 1} \\ &= 18 \end{aligned}$$

Formats for representation of integers

 

(a) Unsigned number

 

(b) Signed number

Negative numbers can be represented in following ways

- Sign and magnitude
- 1' s complement
- 2' s complement

1' s complement

Let K be the negative equivalent of an n -bit positive number P .

Then, in 1' s complement representation K is obtained by subtracting P from $2^n - 1$, namely

$$K = (2^n - 1) - P$$

This means that K can be obtained by inverting all bits of P .

Find the 1' s complement of ...

0 1 0 1

0 0 1 0

0 0 1 1

0 1 1 1

Find the 1's complement of ...

0 1 0 1

1 0 1 0

0 0 1 0

1 1 0 1

0 0 1 1

1 1 0 0

0 1 1 1

1 0 0 0

Just flip 1's to 0's and vice versa.

Example of 1's complement addition

$$\begin{array}{r} (+5) \\ +(+2) \\ \hline (+7) \end{array} \quad \begin{array}{r} 0101 \\ +0010 \\ \hline 0111 \end{array}$$

Example of 1's complement addition

$$\begin{array}{r} (-5) \\ +(+2) \\ \hline (-3) \end{array} \quad \begin{array}{r} 1010 \\ +0010 \\ \hline 1100 \end{array}$$

[Figure 3.8 from the textbook]

Example of 1's complement addition

$$\begin{array}{r} (-5) \\ + (-2) \\ \hline (-7) \end{array} \quad \begin{array}{r} 1010 \\ + 1101 \\ \hline 10111 \\ \text{C} \rightarrow 1 \\ \hline 1000 \end{array}$$

2' s complement

Let K be the negative equivalent of an n -bit positive number P .

Then, in 2' s complement representation K is obtained by subtracting P from 2^n , namely

$$K = 2^n - P$$

Deriving 2' s complement

For a positive n-bit number P, let K_1 and K_2 denote its 1' s and 2' s complements, respectively.

$$K_1 = (2^n - 1) - P$$
$$K_2 = 2^n - P$$

Since $K_2 = K_1 + 1$, it is evident that in a logic circuit the 2' s complement can be computed by inverting all bits of P and then adding 1 to the resulting 1' s-complement number.

Find the 2' s complement of ...

0 1 0 1

0 0 1 0

0 0 1 1

0 1 1 1

Find the 2' s complement of ...

0 1 0 1

1 0 1 1

0 0 1 0

1 1 1 0

0 0 1 1

1 1 0 1

0 1 1 1

1 0 0 1

Quick Way to find 2's complement

- **Scan the binary number from right to left**
- **Copy all bits that are 0 from right to left**
- **Stop at the first 1**
- **Copy that 1 as well**
- **Invert all remaining bits**

Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

[Table 3.2 from the textbook]

Example of 2' s complement addition

$$\begin{array}{r} (+5) \\ + (+2) \\ \hline (+7) \end{array} \qquad \begin{array}{r} 0101 \\ + 0010 \\ \hline 0111 \end{array}$$

Example of 2' s complement addition

$$\begin{array}{r} (-5) \\ + (+2) \\ \hline (-3) \end{array} \qquad \begin{array}{r} 1011 \\ + 0010 \\ \hline 1101 \end{array}$$

Example of 2' s complement addition

$$\begin{array}{r} (+5) \quad \quad 0101 \\ + (-2) \quad \quad + 1110 \\ \hline (+3) \quad \quad 10011 \end{array}$$

↑
ignore

Example of 2's complement addition

$$\begin{array}{r} (-5) \\ + (-2) \\ \hline (-7) \end{array} \qquad \begin{array}{r} 1011 \\ + 1110 \\ \hline 11001 \end{array}$$

↑
ignore

Example of 2's complement subtraction

$$\begin{array}{r} (+5) \quad 0101 \\ - (+2) \quad \underline{0010} \\ \hline (+3) \end{array} \quad \Rightarrow \quad \begin{array}{r} 0101 \\ + 1110 \\ \hline 10011 \\ \uparrow \\ \text{ignore} \end{array}$$

Example of 2's complement subtraction

$$\begin{array}{r} (-5) \\ - (+2) \\ \hline (-7) \end{array} \quad \begin{array}{r} 1011 \\ - 0010 \\ \hline \end{array} \quad \Rightarrow \quad \begin{array}{r} 1011 \\ + 1110 \\ \hline 11001 \\ \uparrow \\ \text{ignore} \end{array}$$


Example of 2' s complement subtraction

$$\begin{array}{r} (+5) \quad 0101 \\ - (-2) \quad \underline{1110} \\ \hline (+7) \end{array} \quad \Rightarrow \quad \begin{array}{r} 0101 \\ + \underline{0010} \\ \hline 0111 \end{array}$$

 Example of 2's complement subtraction

$$\begin{array}{r} (-5) \\ - (-2) \\ \hline (-3) \end{array} \quad \begin{array}{r} 1011 \\ - 1110 \\ \hline \end{array} \quad \Rightarrow \quad \begin{array}{r} 1011 \\ + 0010 \\ \hline 1101 \end{array}$$

Graphical interpretation of four-bit 2's complement numbers




(a) The number circle

(b) Subtracting 2 by adding its 2's complement

Take Home Message

- **Subtraction can be performed by simply adding the 2's complement of the second number, regardless of the signs of the two numbers.**
- **Thus, the same adder circuit can be used to perform both addition and subtraction !!!**


Adder/subtractor unit

 

[Figure 3.12 from the textbook]


XOR Tricks

control	y	out
0	0	0
0	1	1
1	0	1
1	1	0

 


XOR as a repeater

control	y	out
0	0	0
0	1	1
1	0	1
1	1	0

 


XOR as an inverter

control	y	out
0	0	0
0	1	1
1	0	1
1	1	0

 


Addition: when control = 0

 


[Figure 3.12 from the textbook]

Addition: when control = 0

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 

[Figure 3.12 from the textbook]

Subtraction: when control = 1

 

[Figure 3.12 from the textbook]

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (+2) \quad +0010 \\
 \hline
 (+9) \quad 1001 \\
 c_4 = 0 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (+2) \quad +0010 \\
 \hline
 (-5) \quad 1011 \\
 c_4 = 0 \\
 c_3 = 0
 \end{array}$$

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (-2) \quad +1110 \\
 \hline
 (+5) \quad 10101 \\
 c_4 = 1 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (-2) \quad +1110 \\
 \hline
 (-9) \quad 10111 \\
 c_4 = 1 \\
 c_3 = 0
 \end{array}$$

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (+2) \quad +0010 \\
 \hline
 (+9) \quad 1001 \\
 c_4 = 0 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (+2) \quad +0010 \\
 \hline
 (-5) \quad 1011 \\
 c_4 = 0 \\
 c_3 = 0
 \end{array}$$

Overflow occurs only in these two cases.

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (-2) \quad +1110 \\
 \hline
 (+5) \quad 10101 \\
 c_4 = 1 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (-2) \quad +1110 \\
 \hline
 (-9) \quad 10111 \\
 c_4 = 1 \\
 c_3 = 0
 \end{array}$$

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (+2) \quad +0010 \\
 \hline
 (+9) \quad 1001 \\
 \\
 c_4 = 0 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (+2) \quad +0010 \\
 \hline
 (-5) \quad 1011 \\
 \\
 c_4 = 0 \\
 c_3 = 0
 \end{array}$$

Overflow occurs only in these two cases.

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (-2) \quad +1110 \\
 \hline
 (+5) \quad 10101 \\
 \\
 c_4 = 1 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (-2) \quad +1110 \\
 \hline
 (-9) \quad 10111 \\
 \\
 c_4 = 1 \\
 c_3 = 0
 \end{array}$$

$$\text{Overflow} = c_3 \bar{c}_4 + \bar{c}_3 c_4$$

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (+2) \quad +0010 \\
 \hline
 (+9) \quad 1001 \\
 \\
 c_4 = 0 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (+2) \quad +0010 \\
 \hline
 (-5) \quad 1011 \\
 \\
 c_4 = 0 \\
 c_3 = 0
 \end{array}$$

Overflow occurs only in these two cases.

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (-2) \quad +1110 \\
 \hline
 (+5) \quad 10101 \\
 \\
 c_4 = 1 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (-2) \quad +1110 \\
 \hline
 (-9) \quad 10111 \\
 \\
 c_4 = 1 \\
 c_3 = 0
 \end{array}$$

$$\text{Overflow} = \underbrace{c_3 \bar{c}_4 + \bar{c}_3 c_4}_{\text{XOR}}$$

Calculating overflow for 4-bit numbers with only three significant bits

$$\begin{aligned}\text{Overflow} &= c_3 \bar{c}_4 + \bar{c}_3 c_4 \\ &= c_3 \oplus c_4\end{aligned}$$

Calculating overflow for n-bit numbers with only n-1 significant bits

$$\text{Overflow} = c_{n-1} \oplus c_n$$

Another way to look at the overflow issue

$$X = x_3x_2x_1x_0$$

$$Y = y_3y_2y_1y_0$$

$$S = s_3s_2s_1s_0$$

Another way to look at the overflow issue

$$X = x_3x_2x_1x_0$$

$$Y = y_3y_2y_1y_0$$

$$S = s_3s_2s_1s_0$$


If both numbers that we are adding have the same sign but the sum does not, then we have an overflow.

$$\text{Overflow} = x_3y_3\bar{s}_3 + \bar{x}_3\bar{y}_3s_3$$

Can we perform addition even faster?


The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.

The Full-Adder Circuit

 

[Figure 3.3c from the textbook]

The Full-Adder Circuit

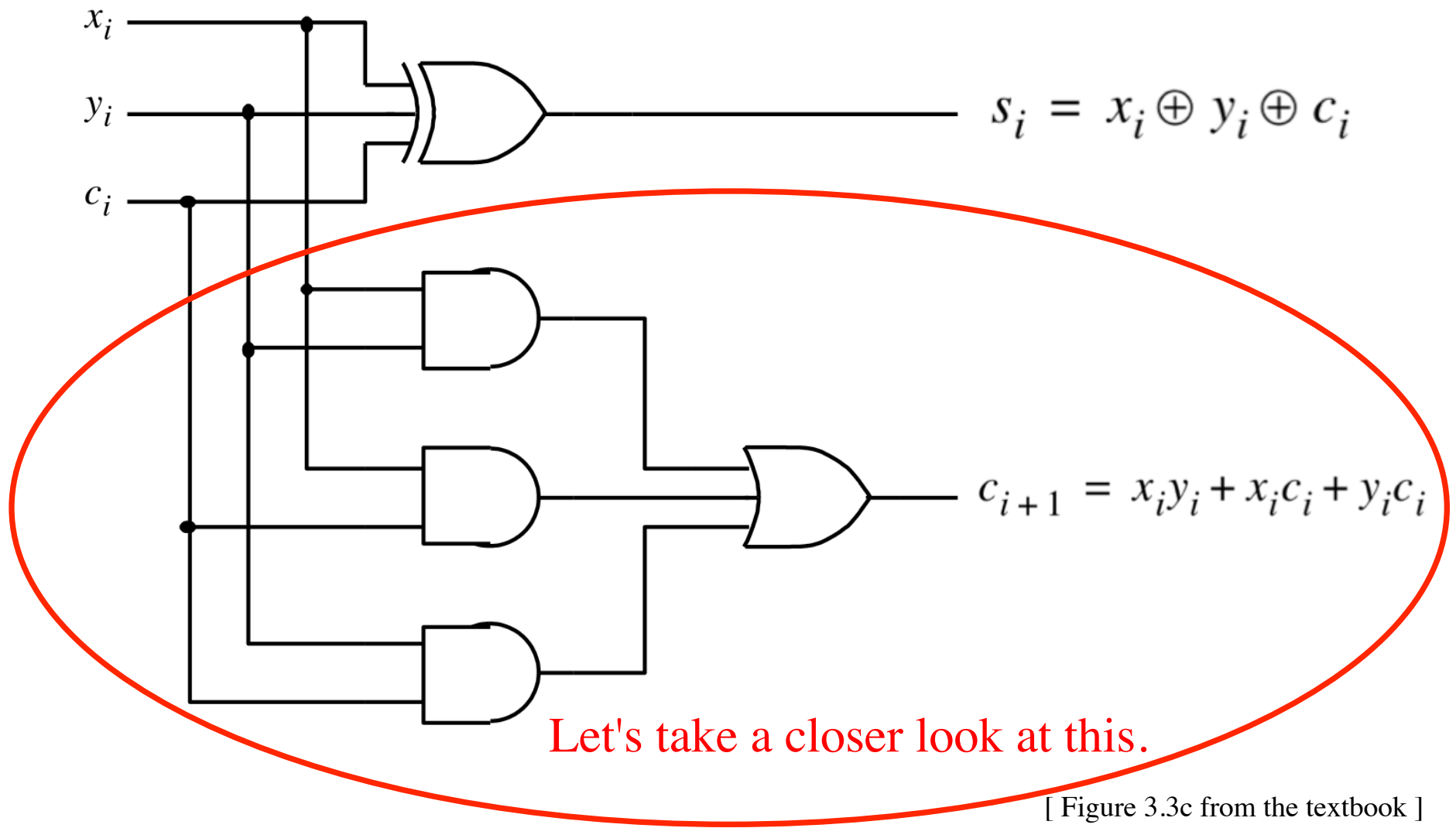

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Decomposing the Carry Expression


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i)c_i$$

Decomposing the Carry Expression

$$C_{i+1} = x_i y_i + x_i C_i + y_i C_i$$


$$C_{i+1} = x_i y_i + (x_i + y_i) C_i$$

 

Another Way to Draw the Full-Adder Circuit


$$C_{i+1} = x_i y_i + x_i C_i + y_i C_i$$

$$C_{i+1} = x_i y_i + (x_i + y_i)C_i$$

 


Another Way to Draw the Full-Adder Circuit

$$C_{i+1} = x_i y_i + (x_i + y_i)c_i$$

 

Another Way to Draw the Full-Adder Circuit
 
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$




Another Way to Draw the Full-Adder Circuit


g - generate

p - propagate

 
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} C_i$$



 Yet Another Way to Draw It (Just Rotate It)



Now we can Build a Ripple-Carry Adder

 


$$c_1 = g_0 + p_0c_0$$

$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$

[Figure 3.14 from the textbook]

Now we can Build a Ripple-Carry Adder

 


$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[Figure 3.14 from the textbook]

The delay is 5 gates (1+2+2)

 

 n-bit ripple-carry adder: $2n+1$ gate delays



Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$


$$= g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1}$$

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

 The first two stages of a carry-lookahead adder




$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[Figure 3.15 from the textbook]


It takes 3 gate delays to generate c_1

 

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$


It takes 3 gate delays to generate c_2

 


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

 The first two stages of a carry-lookahead adder



It takes 4 gate delays to generate s_2

 

N-bit Carry-Lookahead Adder

- **It takes 3 gate delays to generate all carry signals**
- **It takes 1 more gate delay to generate all sum bits**
- **Thus, the total delay through an n-bit carry-lookahead adder is only 4 gate delays!**

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$


Even this takes
only 3 gate delays

$$+ p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2$$

$$+ p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0$$


$$+ p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0$$

A hierarchical carry-lookahead adder with ripple-carry between blocks

 

[Figure 3.16 from the textbook]

A hierarchical carry-lookahead adder

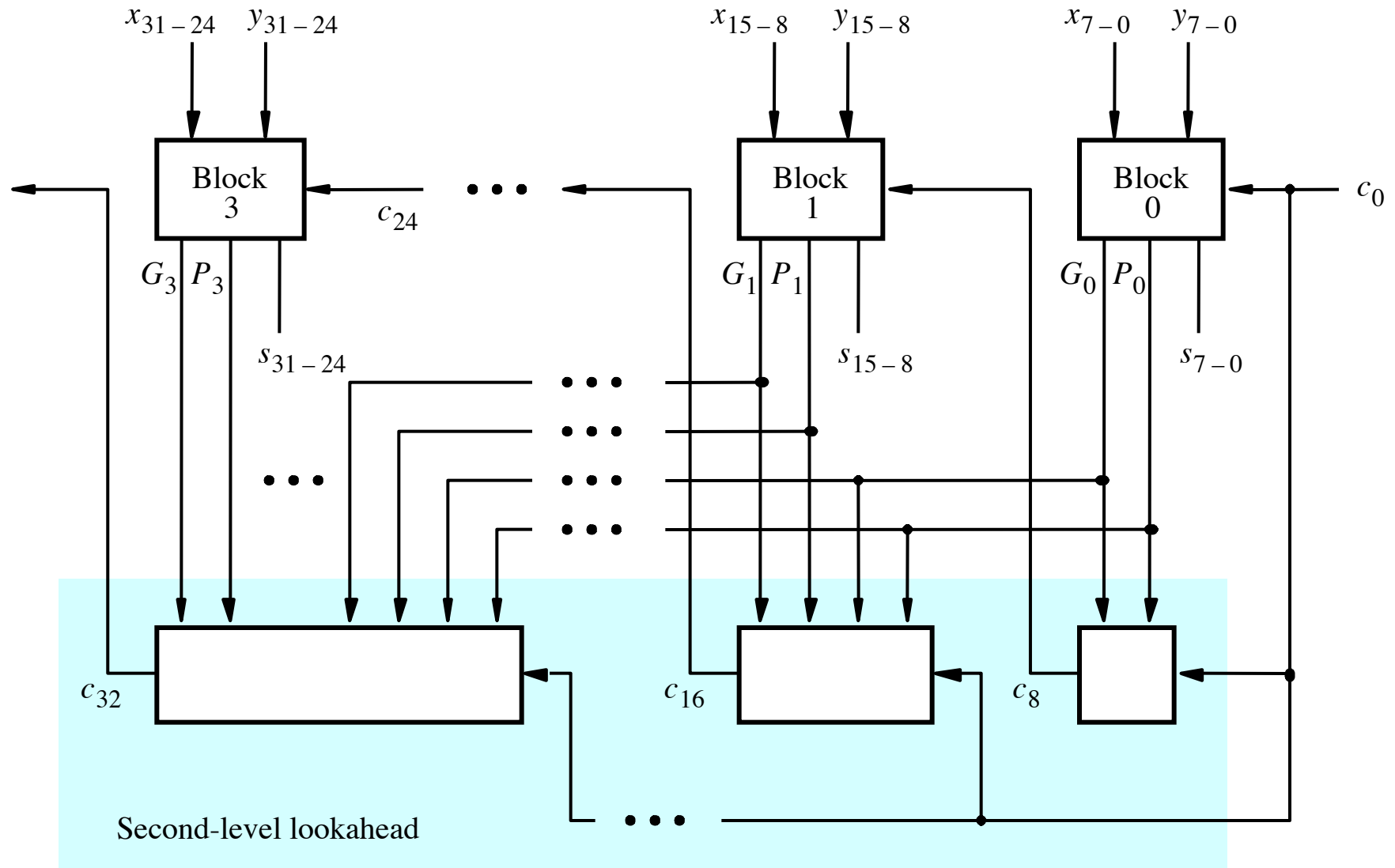

[Figure 3.17 from the textbook]

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned} c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 →

P_0 →

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 →

P_0 →

$$c_8 = G_0 + P_0c_0$$

The Hierarchical Carry Expression


$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

A hierarchical carry-lookahead adder


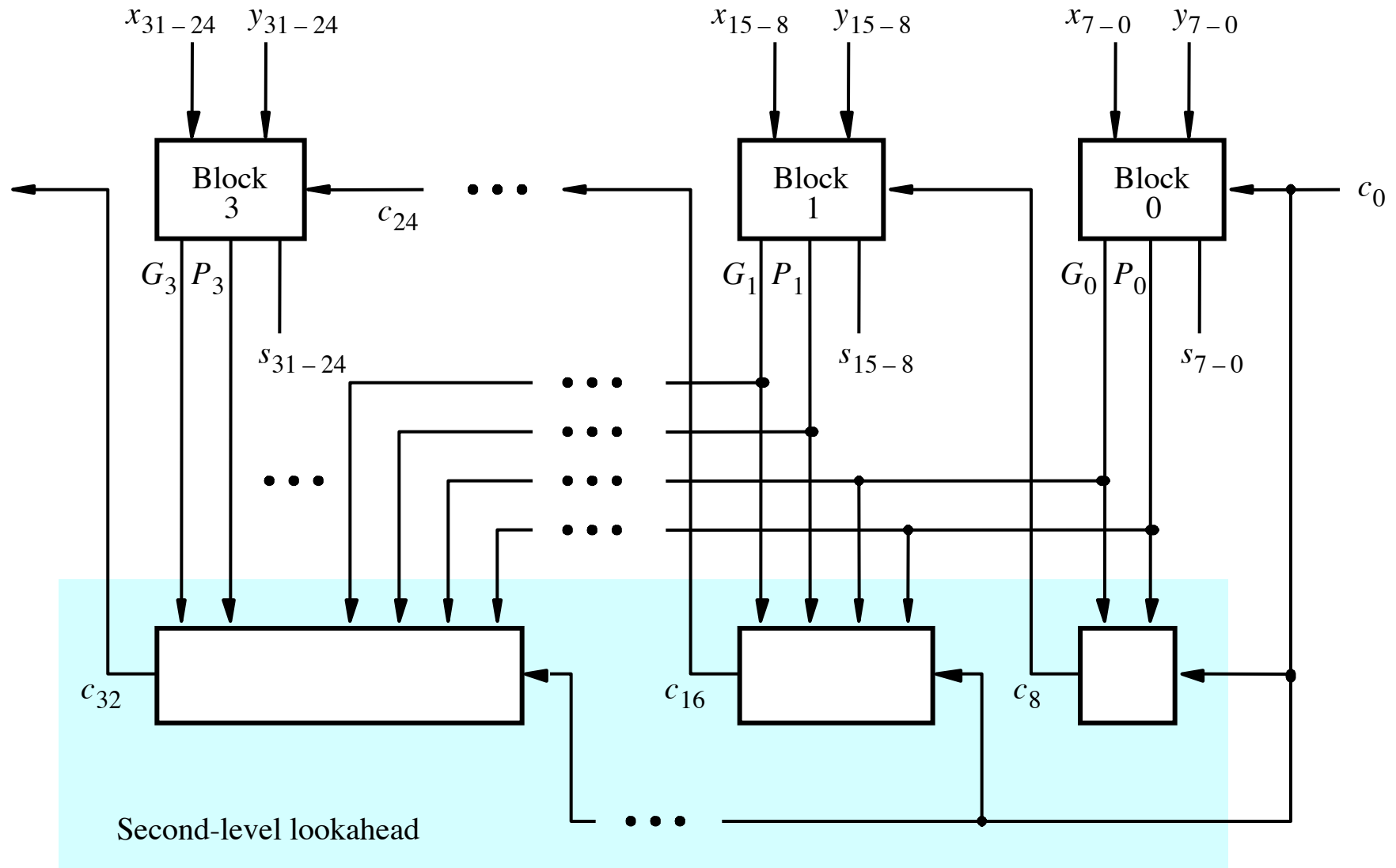


[Figure 3.17 from the textbook]

Hierarchical CLA Adder Carry Logic

- C8** – 5 gate delays
- C16** – 5 gate delays
- C24** – 5 Gate delays
- C32** – 5 Gate delays

SECOND
LEVEL
HIERARCHY

  

FIRST LEVEL HIERARCHY



Hierarchical CLA Critical Path

SECOND
LEVEL
HIERARCHY

C9 – 7 gate delays

C17 – 7 gate delays

C25 – 7 Gate delays

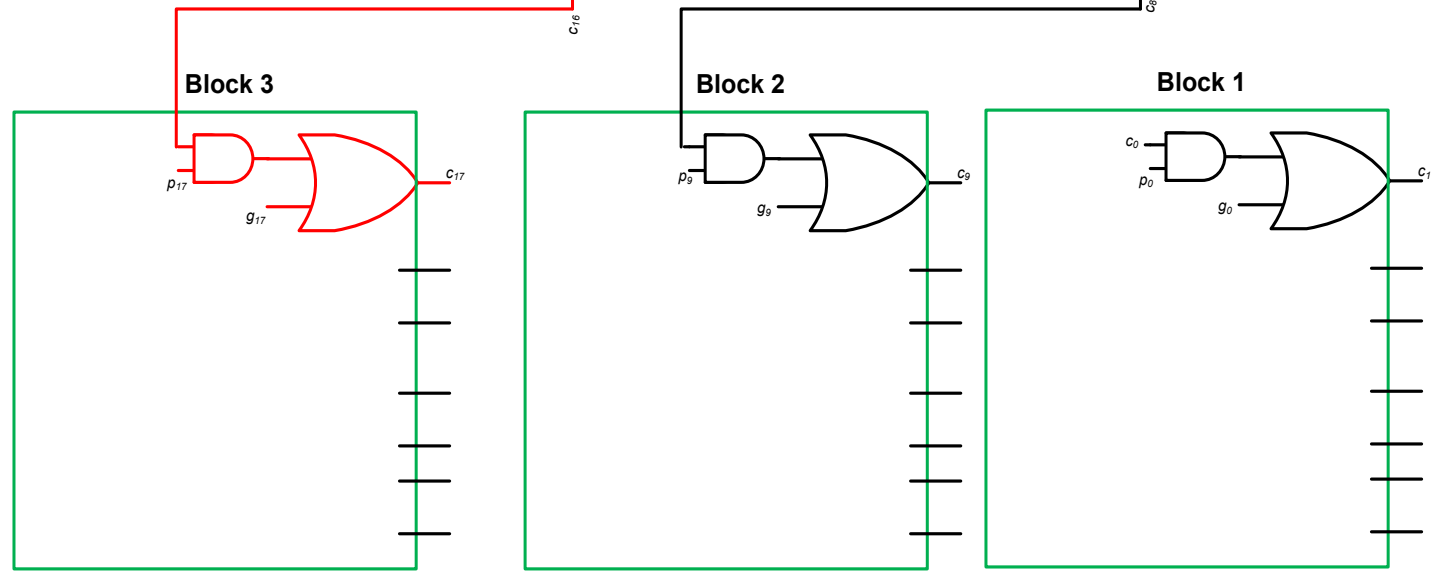 

FIRST LEVEL HIERARCHY

Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- Is 8 gates
 - 3 to generate all G_j and P_j
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)

Questions?

THE END