

# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**


**<http://www.ece.iastate.edu/~alexs/classes/>**

# D Flip-Flops

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*


# **Quick Review**

# A simple memory element with NOT Gates

 


[ Figure 5.2 from the textbook ]
 
# A simple memory element with NAND Gates




# A simple memory element with NOR Gates

 


# Basic Latch

# A simple memory element with NOR Gates

 





# A simple memory element with NOR Gates

 

# A simple memory element with NOR Gates


 


# A memory element with NOR gates

 


[ Figure 5.3 from the textbook ]

# Two Different Ways to Draw the Same Circuit

  

[ Figure 5.3 & 5.4 from the textbook ]
 
# Circuit and Characteristic Table for the Basic Latch




(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Truth table

 

Time

(c) Timing diagram

[ Figure 5.4 from the textbook ]


# **Gated SR Latch**

# Motivation

- **The basic latch changes its state when the input signals change**
- **It is hard to control when these input signals will change and thus it is hard to know when the latch may change its state.**
- **We want to have something like an Enable input**
- **In this case it is called the “Clock” input because it is desirable for the state changes to be synchronized**




# Circuit Diagram for the Gated SR Latch

 


[ Figure 5.5a from the textbook ]

# Circuit Diagram for the Gated SR Latch

 


This is the “gate”  
of the gated latch

# Circuit Diagram for the Gated SR Latch

 

Notice that these are complements of each other


 
# Circuit Diagram and Characteristic Table for the Gated SR Latch



Clk	S	R	$Q(t + 1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x


[ Figure 5.5a-b from the textbook ]

# Circuit Diagram and Graphical Symbol for the Gated SR Latch

  


[ Figure 5.5a,c from the textbook ]

# Timing Diagram for the Gated SR Latch

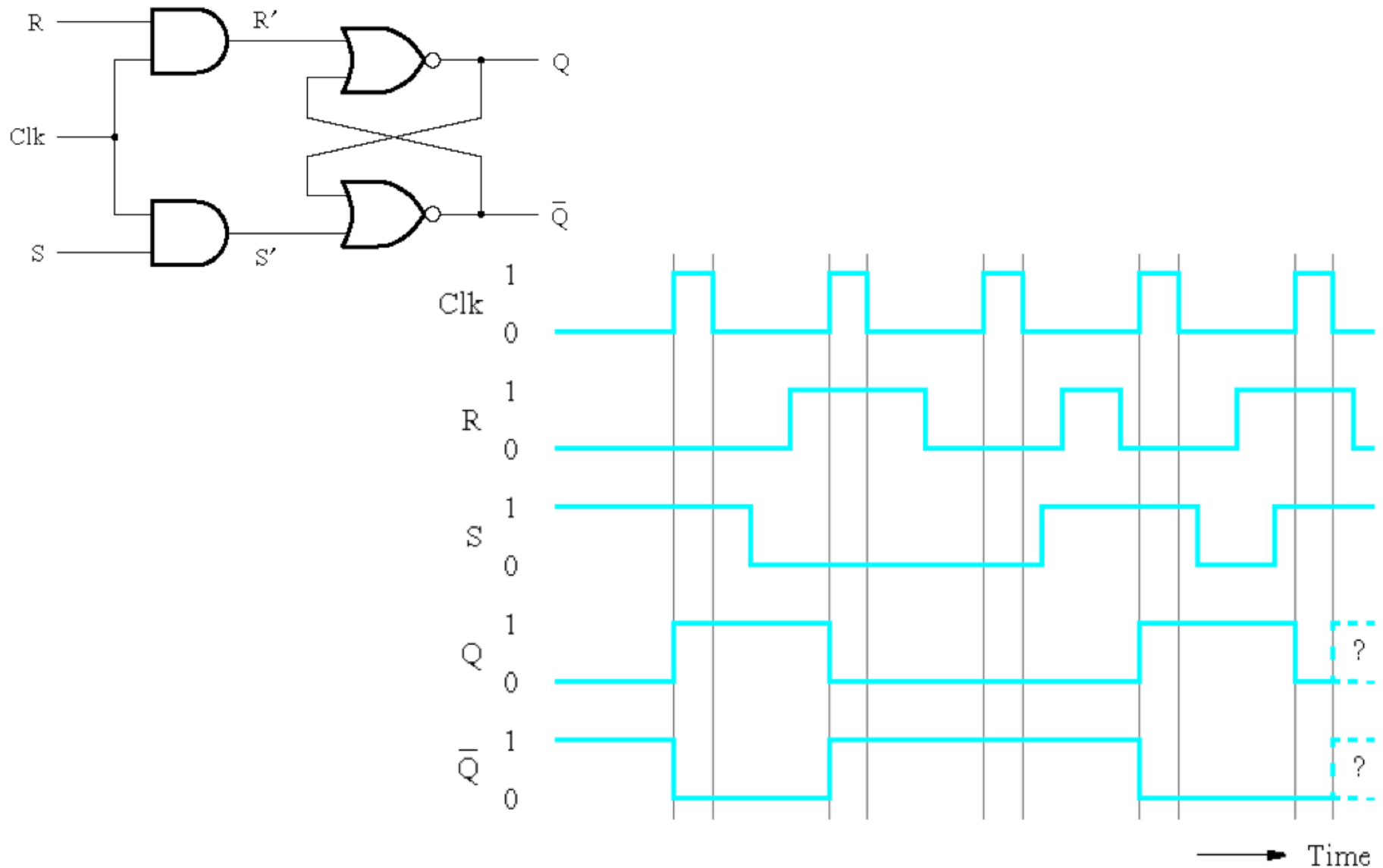


[ Figure 5.5c from the textbook ]

# Gated SR latch with NAND gates

 

[ Figure 5.6 from the textbook ]


# Gated SR latch with NAND gates

 

In this case the “gate” is constructed using NAND gates! Not AND gates.




# Gated SR latch with NAND gates

 


Also, notice that the positions of S and R are now swapped.

# Gated SR latch with NAND gates

 


Finally, notice that when  $\text{Clk}=1$  this turns into the basic latch with NAND gates, i.e., the  $\bar{S}\bar{R}$  Latch.


## Gated SR latch with NOR gates

 


## Gated SR latch with NAND gates

 

## Gated SR latch with NOR gates

 


## Gated SR latch with NAND gates

 


Graphical symbols are the same

# Gated SR latch with NOR gates

 

Clk	S	R	Q(t + 1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)

# Gated SR latch with NAND gates

 

Clk	S	R	Q(t + 1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)


Characteristic tables are the same

# **Gated D Latch**

# Motivation

- **Dealing with two inputs (S and R) could be messy. For example, we may have to reset the latch before some operations in order to store a specific value but the reset may not be necessary depending on the current state of the latch.**
- **Why not just have one input and call it D.**
- **The D latch can be constructed using a simple modification of the SR latch.**


# Circuit Diagram for the Gated D Latch

 

[ Figure 5.7a from the textbook ]




# Circuit Diagram for the Gated D Latch

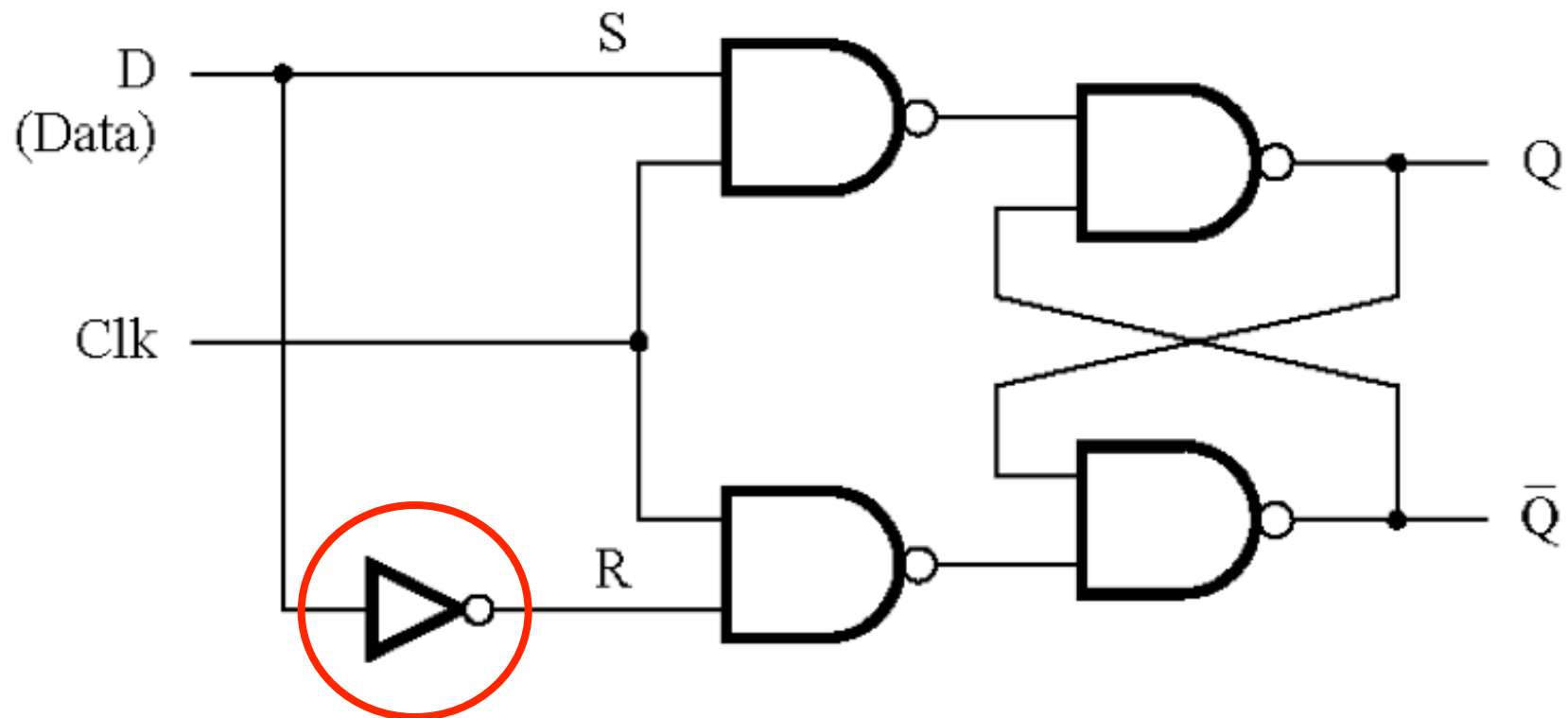

This is the only  
new thing here.

 
# Circuit Diagram and Characteristic Table for the Gated D Latch



Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

Note that it is now impossible to have  $S=R=1$ .


 
# Circuit Diagram and Characteristic Table for the Gated D Latch



Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1



When Clk=1 the output follows the D input.  
When Clk=0 the output cannot be changed.

# Circuit Diagram and Graphical Symbol for the Gated D Latch

  


[ Figure 5.7a,c from the textbook ]

# Timing Diagram for the Gated D Latch

  

[ Figure 5.7d from the textbook ]

# Setup and hold times

 


Setup time ( $t_{su}$ ) – the minimum time that the D signal must be stable prior to the the negative edge of the Clock signal

Hold time ( $t_h$ ) – the minimum time that the D signal must remain stable after the the negative edge of the Clock signal


# **Master-Slave D Flip-Flop**

# Constructing a Master-Slave D Flip-Flop From Two D Latches

Master

 

Slave

 




# Constructing a Master-Slave D Flip-Flop From Two D Latches

Master


Slave

 


# Constructing a Master-Slave D Flip-Flop From Two D Latches

Master

Slave

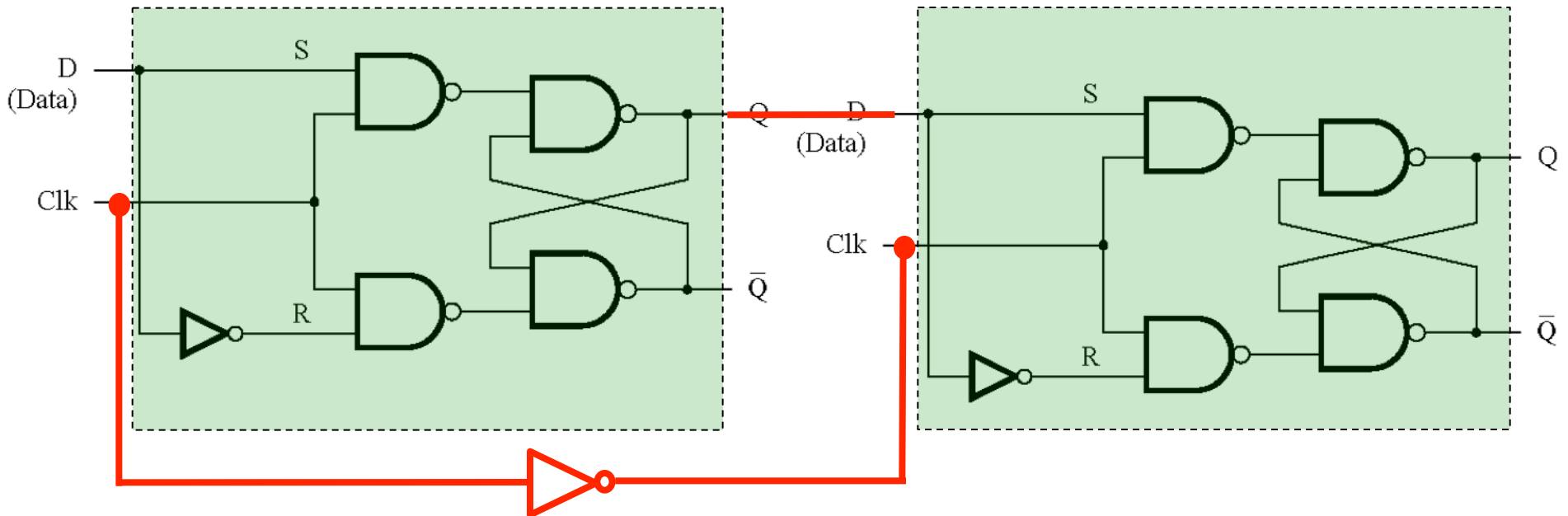

# Constructing a Master-Slave D Flip-Flop From Two D Latches

 


[ Figure 5.9a from the textbook ]


# Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

Master

 

Slave

 


# Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

Master

Slave

 


# **Edge-Triggered D Flip-Flops**

# Motivation

**In some cases we need to use a memory storage device that can change its state no more than once during each clock cycle.**



# Master-Slave D Flip-Flop

 

(a) Circuit




# Timing Diagram for the Master-Slave D Flip-Flop

  


[ Figure 5.9a,b from the textbook ]

# Graphical Symbol for the Master-Slave D Flip-Flop

 

[ Figure 5.9c from the textbook ]

 
# Graphical Symbol for the Master-Slave D Flip-Flop




The > means that this is edge-triggered

The small circle means that it is the negative edge

 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



 
# Positive-Edge-Triggered Master-Slave D Flip-Flop


 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



 
# Positive-Edge-Triggered Master-Slave D Flip-Flop




# **Other Types of Edge-Triggered D Flip-Flops**


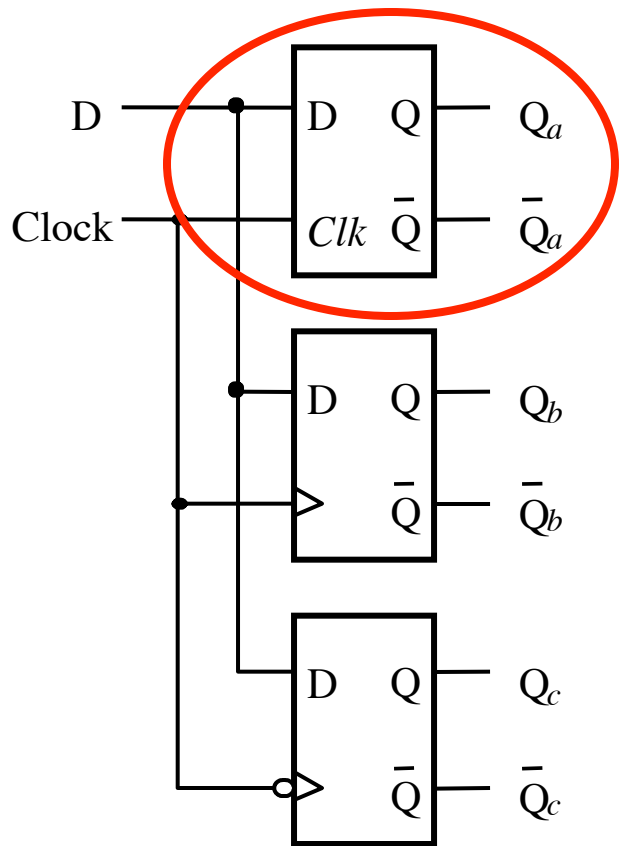
# Comparison of level-sensitive and edge-triggered D storage elements




 Level-sensitive  
(the output mirrors the D input when Clk=1)






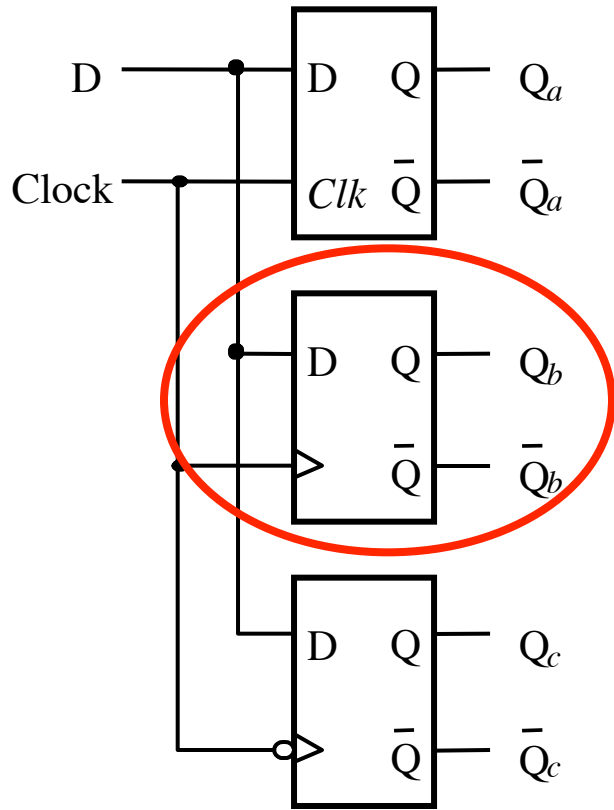
# Comparison of level-sensitive and edge-triggered D storage elements




Positive-edge-triggered

 

 
# Comparison of level-sensitive and edge-triggered D storage elements




Negative-edge-triggered

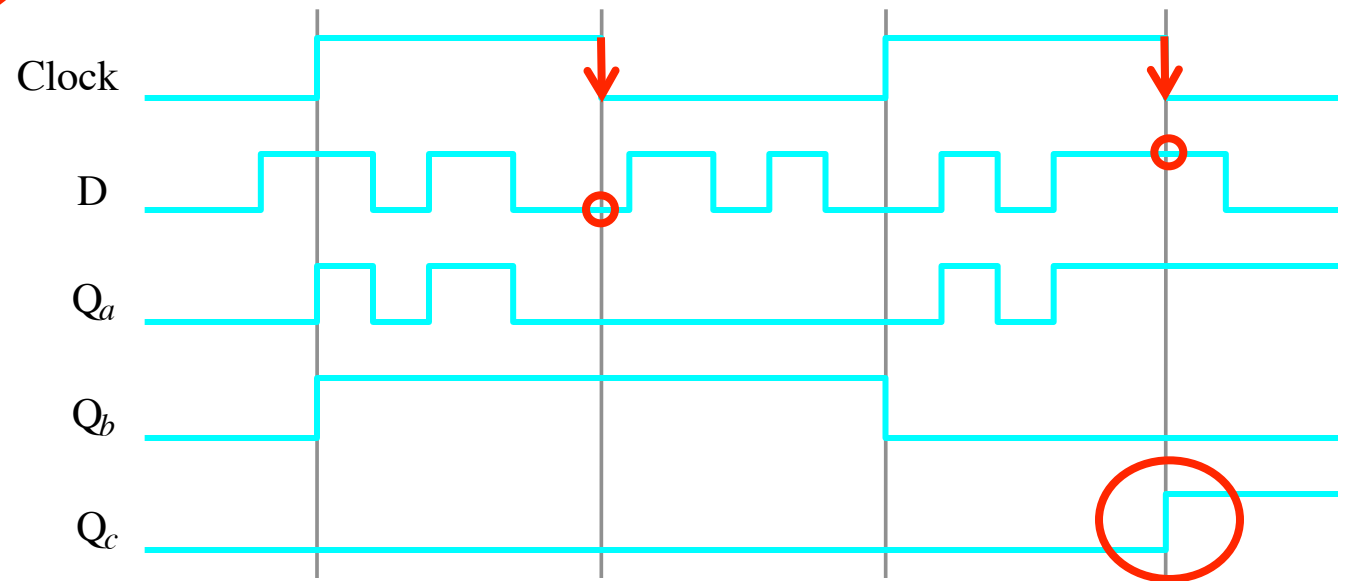

# A positive-edge-triggered D flip-flop

 

(a) Circuit

 


(b) Graphical symbol


[ Figure 5.11 from the textbook ]
 
# A positive-edge-triggered D flip-flop

This circuit behaves like a positive-edge-triggered D flip-flop, but it uses only 6 NAND gates. Thus, it can be implemented with fewer transistors than the master-slave D flip-flop.




(a) Circuit

 


(b) Graphical symbol
 
# Master-slave D flip-flop with Clear and Preset



(a) Circuit

 


(b) Graphical symbol

[ Figure 5.12 from the textbook ]


# **Positive-edge-triggered D flip-flop with Clear and Preset**

# Positive-edge-triggered D flip-flop with Clear and Preset

 


[ Figure 5.13a from the textbook ]
 
# Positive-edge-triggered D flip-flop with Clear and Preset




(b) Graphical symbol

 


(c) Adding a synchronous clear



# Flip-Flop Timing Parameters

 

(a) D flip-flop with asynchronous clear

 

[ Figure 5.14 from the textbook ]

(b) Timing diagram

# Terminology

- **Basic Latch** – is a feedback connection of two NOR gates or two NAND gates, which can store one bit of information. It can be set using the S input and reset to 0 using the R input.
- **Gated Latch** – is a basic latch that includes input gating and a control input signal. The latch retains its existing state when the control input is equal to 0. Its state may be changed when the control signal is equal to 1.

# Terminology

- **Two types of gated latches**  
**(the control input is the clock):**
- **Gated SR Latch** – uses the S and R inputs to set the latch to 1 or reset it to 0.
- **Gated D Latch** – uses the D input to force the latch into a state that has the same logic value as the D input.

# Terminology

- **Flip-Flop** – is a storage element that can have its output state changed only on the edge of the controlling clock signal.
- **Positive-edge triggered** – if the state changes when the clock signal goes from 0 to 1.
- **Negative-edge triggered** – if the state changes when the clock signal goes from 1 to 0.

# Terminology

The word ***latch*** is mainly used for storage elements, while clocked devices are described as ***flip-flops***.

A **latch** is level-sensitive, whereas a **flip-flop** is edge-sensitive. That is, when a latch is enabled it becomes transparent, while a flip flop's output only changes on a single type (positive going or negative going) of clock edge.

**Questions?**

**THE END**