

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

FSM as an Arbiter Circuit

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **Homework 11 is out**
- **It is due on Monday Nov 30 @ 4pm**

Administrative Stuff

- **Homework 12 is out**
- **It is due on Monday Dec 7 @ 4pm**

Administrative Stuff

- **Final Project (7% of your grade)**
- **Read the instructions in the e-mail that I sent you.**
- **Let me know if you did not get that e-mail.**
- **Also, posted on the class web page (Labs section)**
- **This is your lab for the last two weeks**
- **This is due during your last lab (dead week)**

Arbiter Circuit


Goal

- **Design a machine that controls access by several devices to a shared resource**
- **The resource can be used by only one device at a time**
- **Any changes can occur only on the positive edge of the clock signal**
- **Each device provides one input to the FSM, which is called a request**
- **The FSM produces one output for each device, which is called a grant**



Goal

- **The requests from the devices are prioritized**
- **If two requests are active at the same time, then only the device with the highest priority will be given access to the shared resource**
- **After a device is done with the shared resource, it must make its request signal equal to 0.**
- **If there are no outstanding requests, then the FSM stays in an Idle state**

Conceptual Diagram

 


Conceptual Diagram

  


[Figure 9.20 from the textbook]

State diagram for the arbiter

 


[Figure 6.72 from the textbook]

State diagram for the arbiter

 

Highest Priority Device


State diagram for the arbiter

 

Highest Priority Device


Lowest Priority Device

State diagram for the arbiter

 


State diagram for the arbiter

 Each device must release the resource after it is done using it




Alternative style of state diagram for the arbiter

 


[Figure 6.73 from the textbook]

**Let's look at a simpler example with
only two devices that need to use
the shared resource**

State diagram for the simpler arbiter

 

State diagram for the arbiter circuit

 

State Table

	$r_1 r_2 = 00$	01	10	11	Output
A	A	C	B	B	00
B	A	A	B	B	10
C	A	C	A	C	01

State-Assigned Table

		$Y_1, Y_2 = 00$	01	10	11		
Y_2, Y_1		Y_2, Y_1	Y_2, Y_1	Y_2, Y_1	Y_2, Y_1	g_1, g_2	
A	00	00	10	01	01	00	
B	01	00	00	01	01	10	
C	10	00	10	00	10	01	
	11	d d	d d	d d	d d	d d	

Output Expressions

Output expressions

$$g_1 = \gamma_1$$

$$g_2 = \gamma_2$$

Next State Expressions

Y_2

		$Y_2 Y_1$			
		00	01	11	10
$r_1 r_2$	00	0	0	d	0
	01	1	0	d	1
	11	0	0	d	1
	10	0	0	d	0


$$Y_2 = r_2 Y_2 + \bar{r}_1 r_2 \bar{Y}_1$$

Y_1

		$Y_2 Y_1$			
		00	01	11	10
$r_1 r_2$	00	0	0	d	0
	01	0	0	d	0
	11	1	1	d	0
	10	1	1	d	0

$$Y_1 = r_1 \bar{Y}_2$$

Circuit Diagram

 

Questions?

THE END