

Arithmetic Circuits and Combinational-
Circuit Building Blocks
Assigned Date: Seventh Week
Due Date: Monday, Oct. 10, 2016

P1. (20 points)

Consider the addition of the two ***n*-bit 2's complement** numbers:

$$X = x_{n-1}x_{n-2}\dots x_1x_0$$

$$Y = y_{n-1}y_{n-2}\dots y_1y_0$$

Suppose the sum is $S = s_{n-1}s_{n-2}\dots s_1s_0$ and the carry is $C_n = c_n c_{n-1} c_{n-2} \dots c_1 c_0$.

- (5 points) If X is positive, Y is negative, and $c_{n-1}=0$, what should be the values of c_n and s_{n-1} ? Will overflow occur?
- (5 points) If X is negative, Y is negative, and $c_{n-1}=0$, what should be the values of c_n and s_{n-1} ? Will overflow occur?
- (5 points) Following the idea in part (a) and (b), please construct a truth table for the values of c_n and s_{n-1} for all combinations of the sign of X , the sign of Y , and the value of c_{n-1} . For each combination, please also state if overflow occurs or not.
- (5 points) Based on the truth table in part (c), prove that $\text{Overflow} = c_n \oplus c_{n-1}$.

P2. (10 points)

In class we learned that a carry-lookahead adder is faster than a ripple-carry adder. Could you explain why sometimes a designer might still choose a ripple-carry adder instead of a carry-lookahead adder?

P3. (10 points)

Perform the following conversions.

- (5 points) Decimal number 5.375 to fixed-point number.
- (5 points) Fixed-point number 1101.0111 to decimal number.

P4. (10 points)

Convert the decimal number 15.625 to IEEE 754 single-precision floating number format.

P5. (10 points)

Convert the following IEEE 754 single-precision floating number to decimal number.

1 01111110 0110000 00000000 00000000


Arithmetic Circuits and Combinational- Circuit Building Blocks

Assigned Date: Seventh Week

Due Date: Monday, Oct. 10, 2016

P6. (20 points)

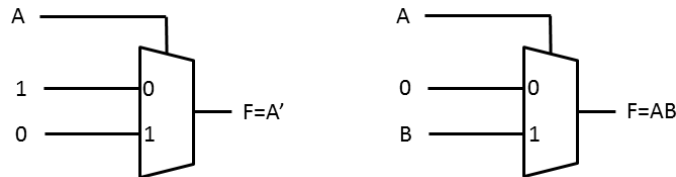The following two examples illustrate how to implement NOT and AND functions with 2-to-1 multiplexers.



Use only 2-to-1 multiplexer to implement each of the following functions:

- (5 points) $F(A, B) = A + B$ (OR)
- (5 points) $F(A, B) = A \oplus B$ (XOR)
- (5 points) $F(A, B) = \overline{A \cdot B}$ (NAND)
- (5 points) $F(A, B) = \overline{A + B}$ (NOR)

Assume the inverse of each input variable is available. (i.e., you can directly use the inverse of each input variable A or B in your answer.)

P7. (10 points)

Use only 2-to-1 multiplexers to implement the circuit for the following function:

$$F(A, B, C) = \prod M(1, 2, 4, 5)$$

Assume the inverse of each input variable is available. (i.e., you can directly use the inverse of each input variable A , B , or C , in your answer.)

P8. (10 points)

Repeat P7, but this time using only one 4-to-1 multiplexer.