

## Recitation #7 Solutions


1.  $10100$

$$\begin{array}{r} 1010 \\ + 1011 \\ \hline 0101 \end{array}$$

Overflow.


2. The truth table:

A	B	C	f	
0	0	0	1	c'
0	0	1	0	
0	1	0	0	
0	1	1	1	
1	0	0	0	c
1	0	1	1	
1	1	0	1	
1	1	1	1	

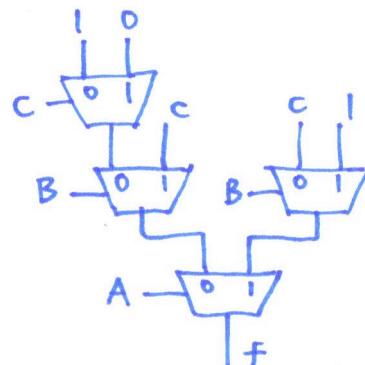


3. The truth table:


a	b	c	d	e	f	Index
0	0	0	0	0	0	0
0	0	0	0	1	0	
0	0	0	1	0	0	
0	0	0	1	1	1	
0	0	1	0	0	d	4
0	0	1	0	1	0	
0	0	1	1	0	1	
0	0	1	1	1	1	
0	1	0	0	0	1	8
0	1	0	0	1	0	
0	1	0	1	0	0	
0	1	0	1	1	0	
0	1	1	0	0	1	12
0	1	1	0	1	d	
0	1	1	1	0	d	
0	1	1	1	1	1	
1	0	0	0	0	0	16
1	0	0	0	1	0	
1	0	0	1	0	0	
1	0	0	1	1	0	
1	0	1	0	0	d	20
1	0	1	0	1	0	
1	0	1	1	0	d	
1	0	1	1	1	0	
1	1	0	0	0	1	24
1	1	0	0	1	d	
1	1	0	1	0	d	
1	1	0	1	1	1	
1	1	1	0	0	0	28
1	1	1	0	1	0	
1	1	1	1	0	1	
1	1	1	1	1	1	31

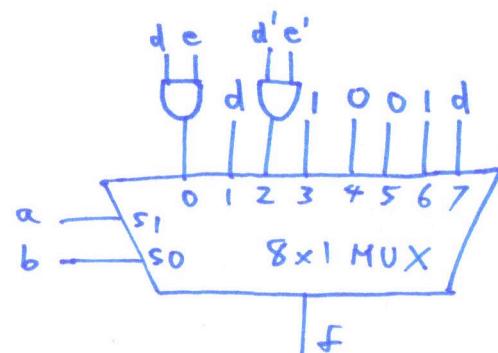

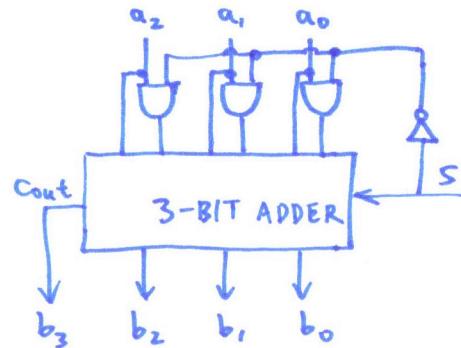4. a. When  $S=0$ ,  $B=A+A +S$   
 When  $S=1$ ,  $B=A+000 +S$



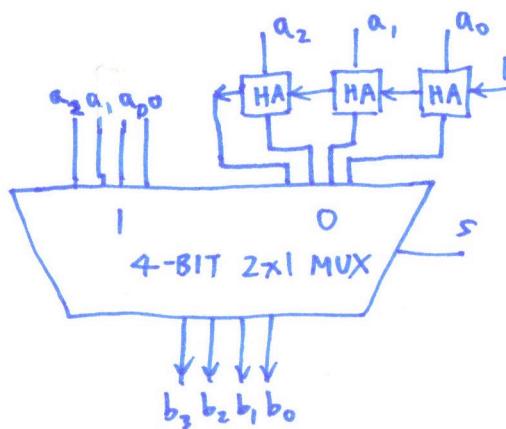
- b. Note that  $2A = a_2 a_1 a_0 0$  (i.e., shifting A to right by 1 bit).  
 Also, we can use 3 half adders to implement an add-one circuit.  
 Then we can use the MUX to select the correct output based on S.




5. a.

a	b	c	d	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

b.

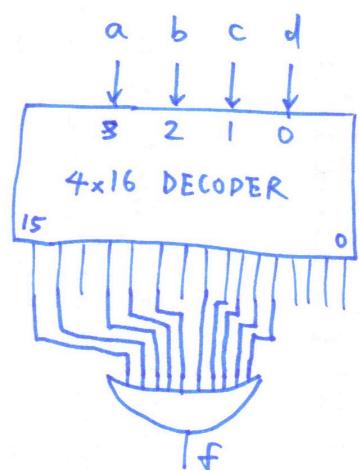

c.

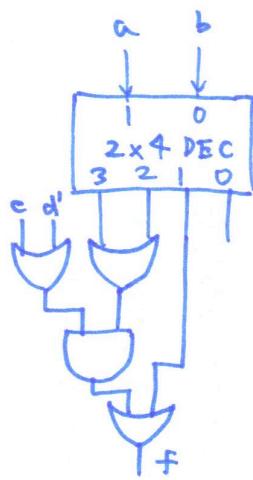

d.

