

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Multiplication


*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW 6 is out**
- **It is due on Monday Oct 10 @ 4pm**


Quick Review

The Full-Adder Circuit

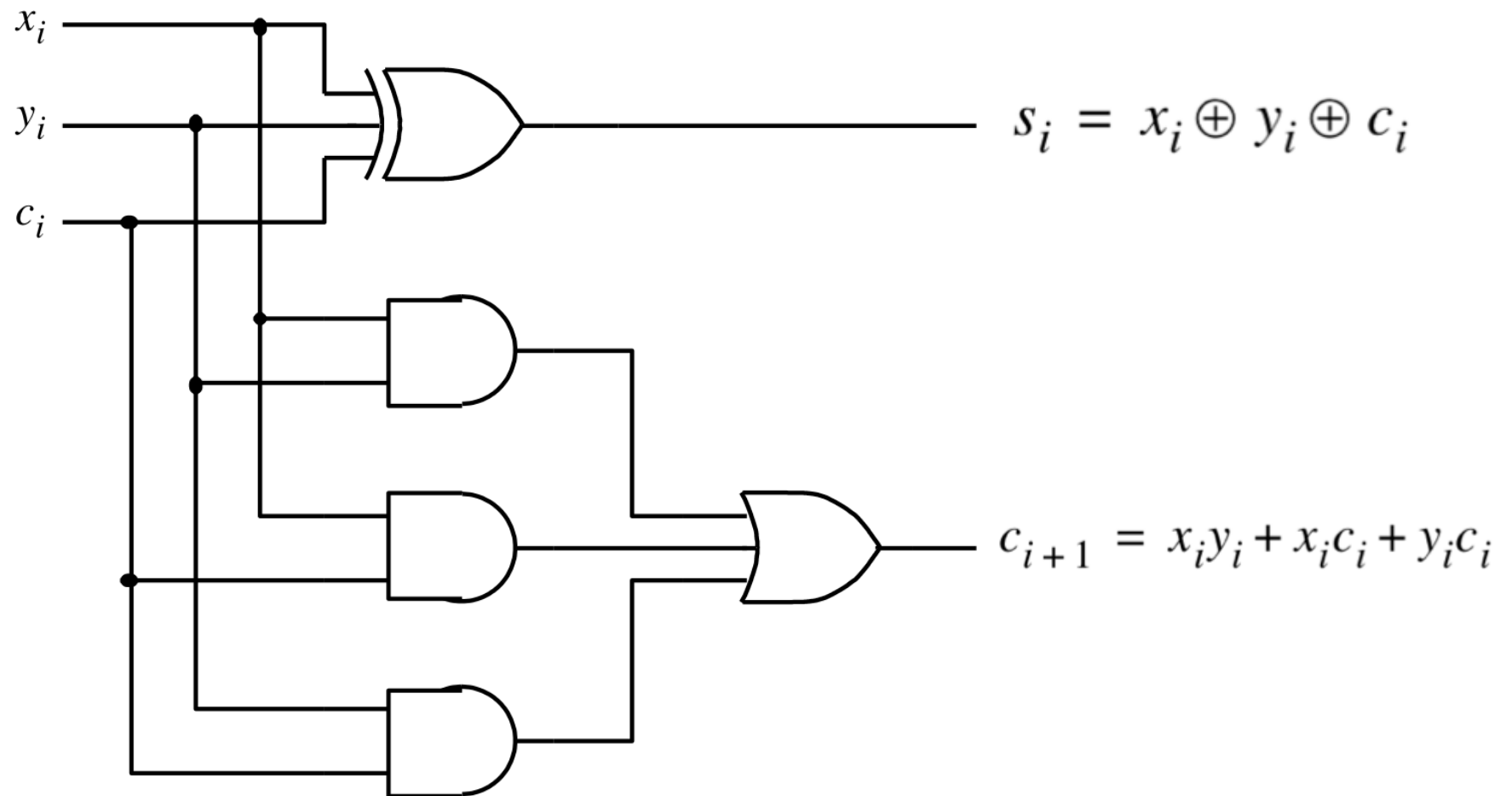


[Figure 3.3c from the textbook]

The Full-Adder Circuit

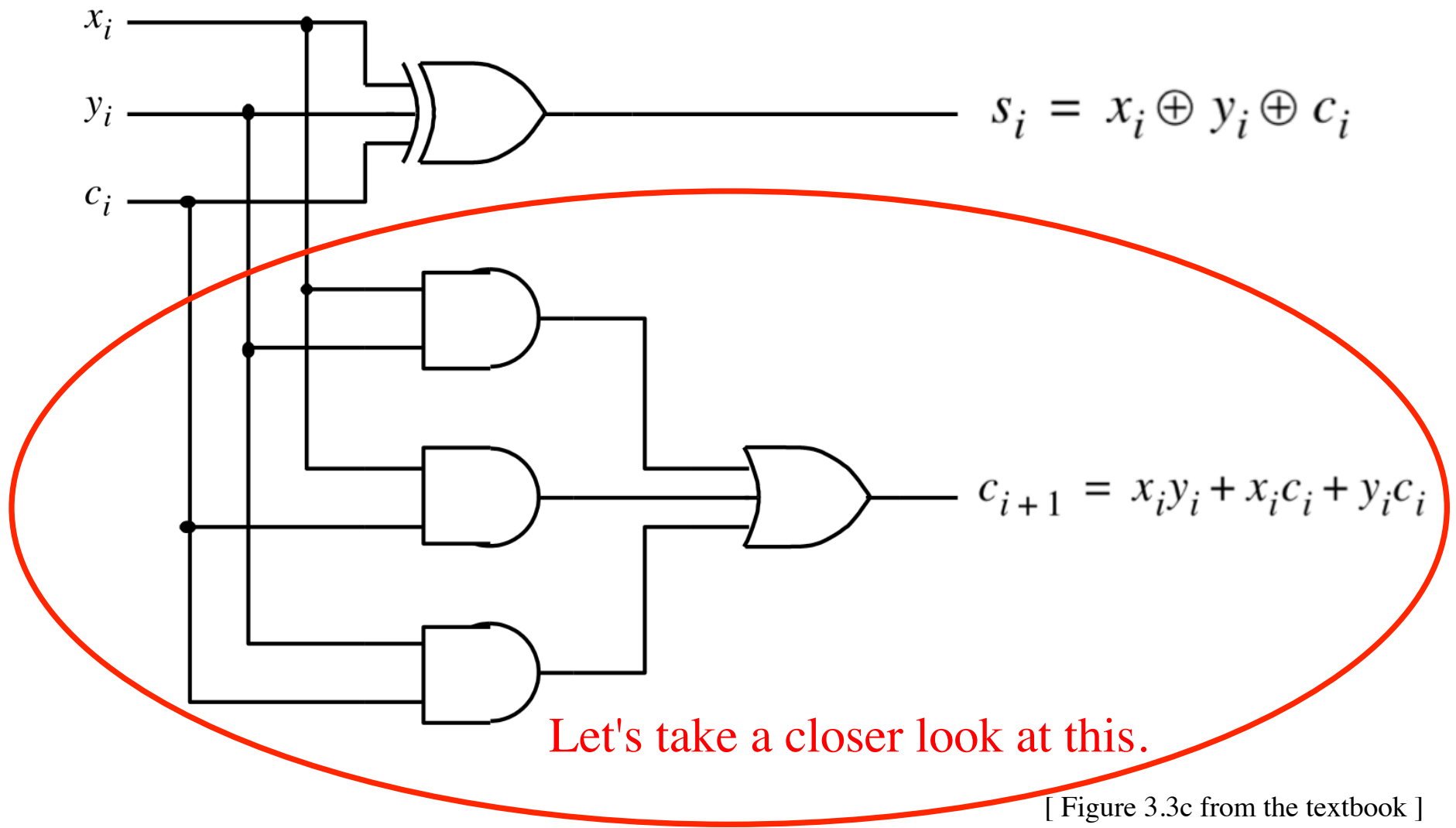

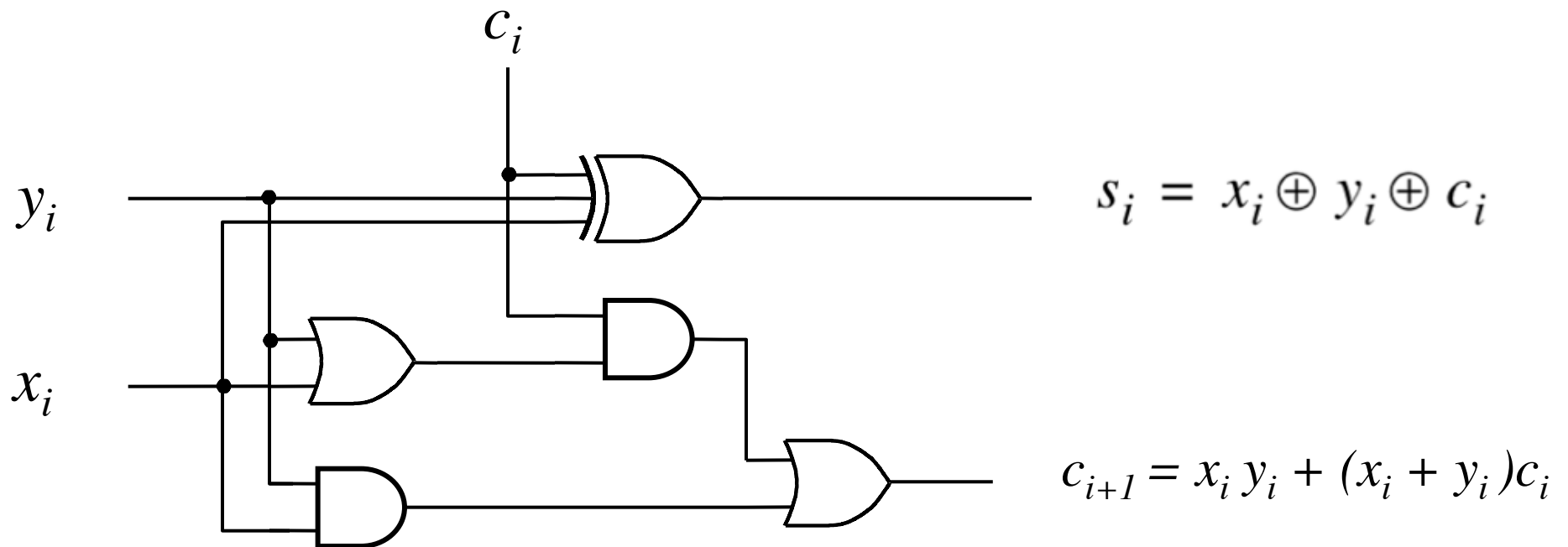Another Way to Draw the Full-Adder Circuit



Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Decomposing the Carry Expression


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

Decomposing the Carry Expression

$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$C_{i+1} = x_i y_i + (x_i + y_i) c_i$$

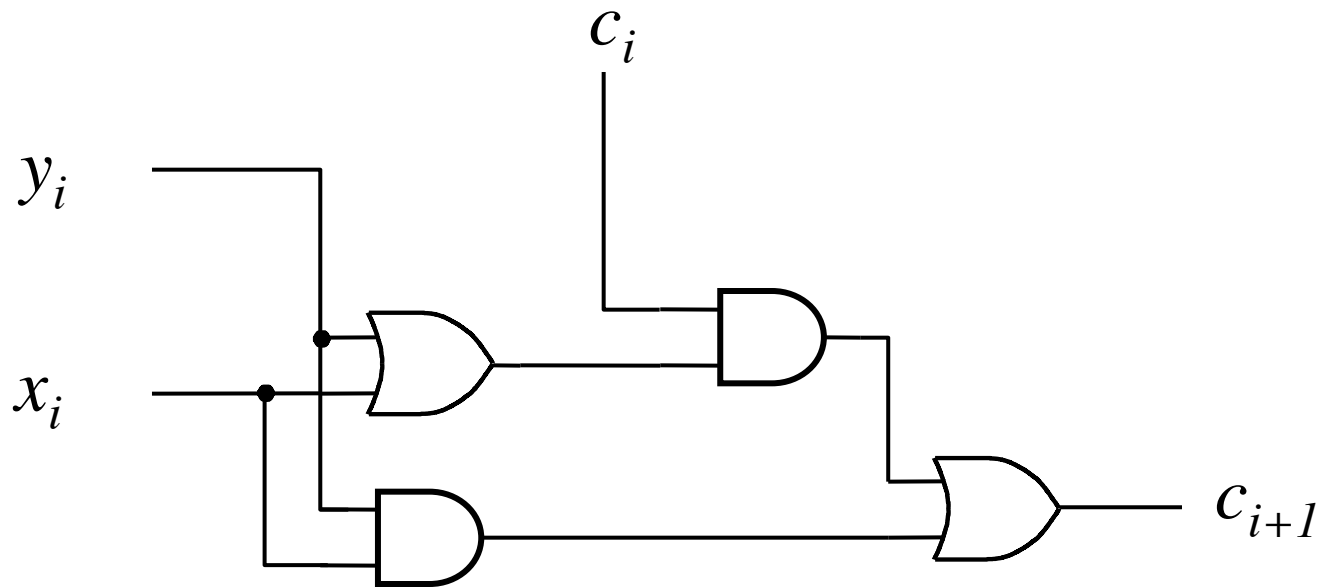

Another Way to Draw the Full-Adder Circuit


$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$C_{i+1} = x_i y_i + (x_i + y_i)c_i$$

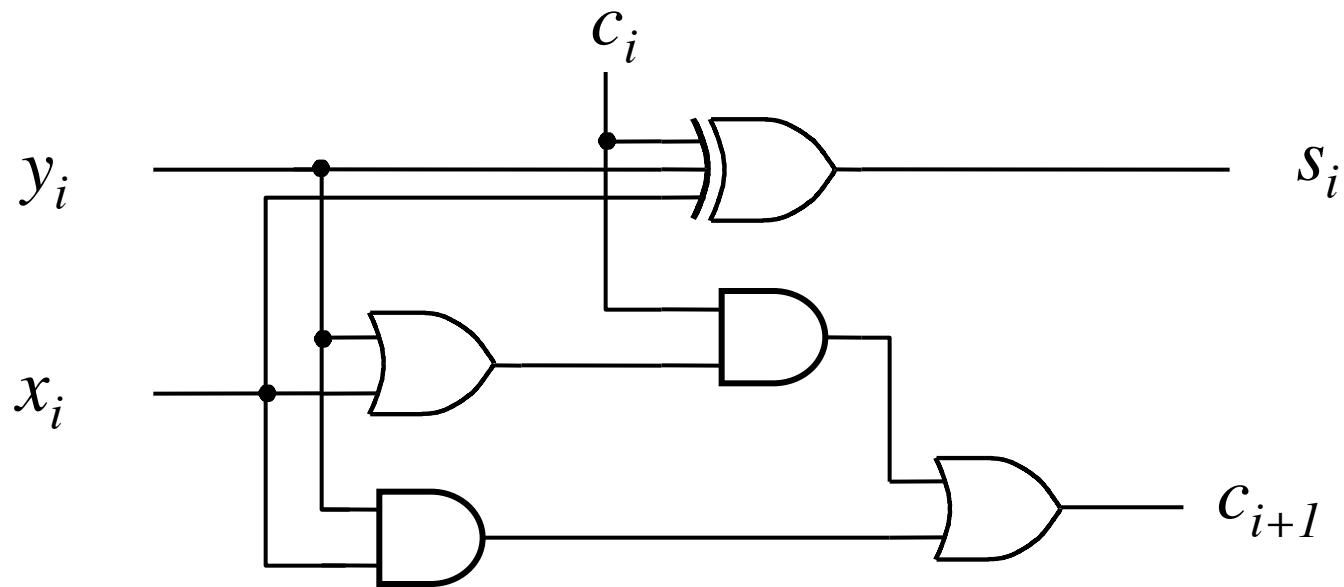


Another Way to Draw the Full-Adder Circuit

$$C_{i+1} = x_i y_i + (x_i + y_i)c_i$$

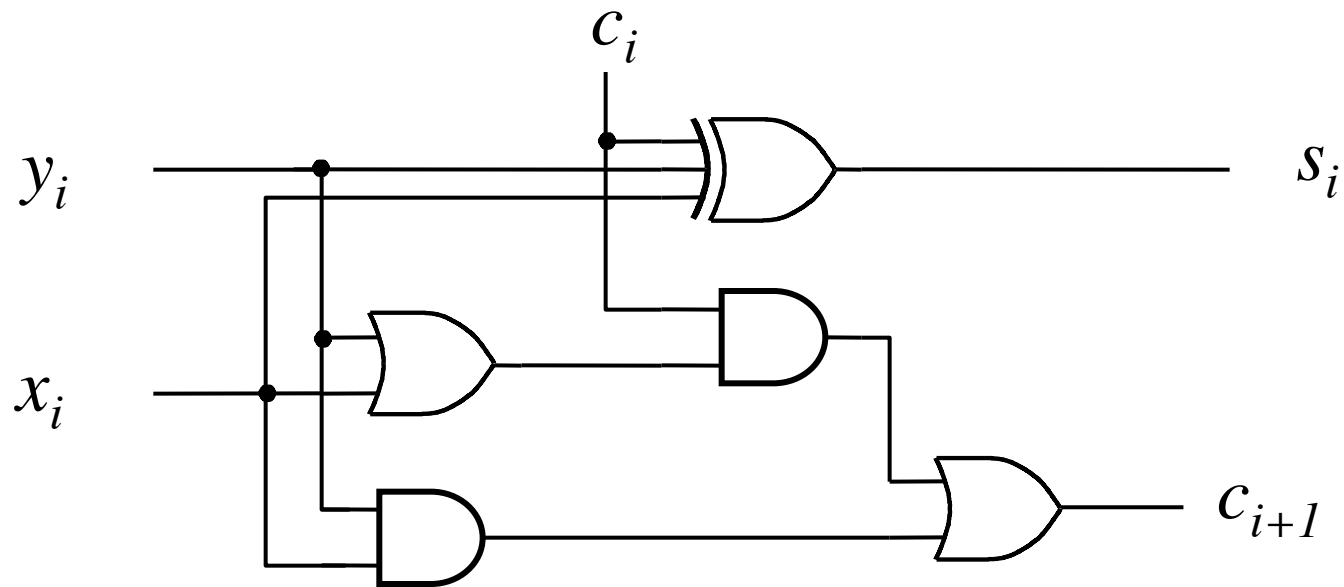


Another Way to Draw the Full-Adder Circuit
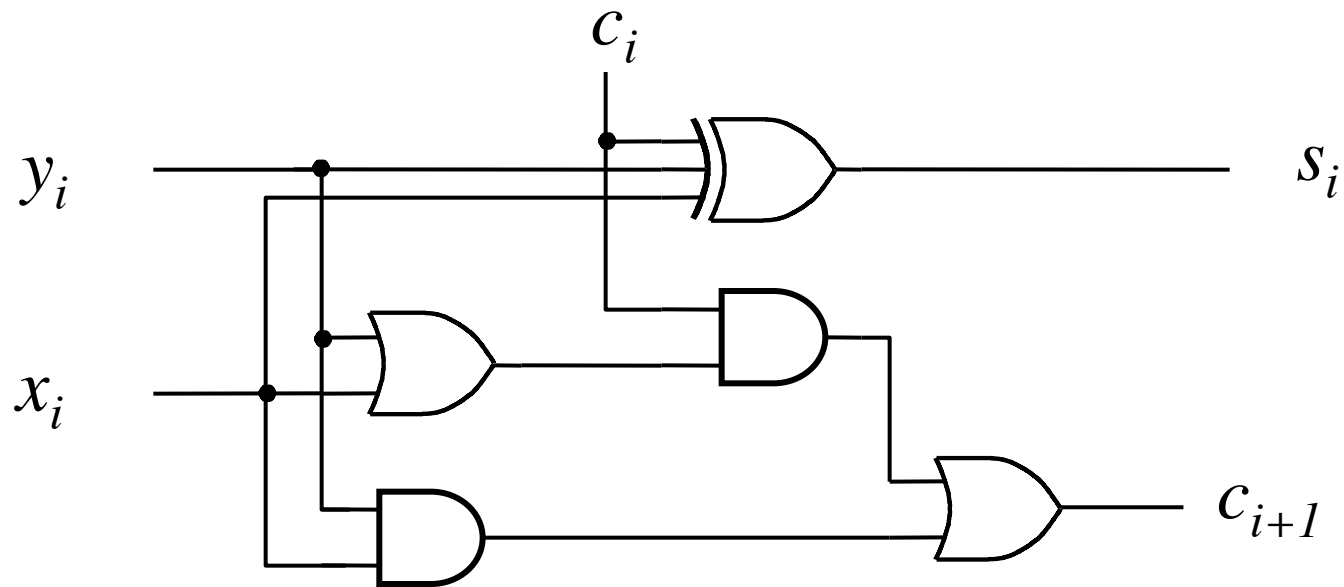
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$




Another Way to Draw the Full-Adder Circuit

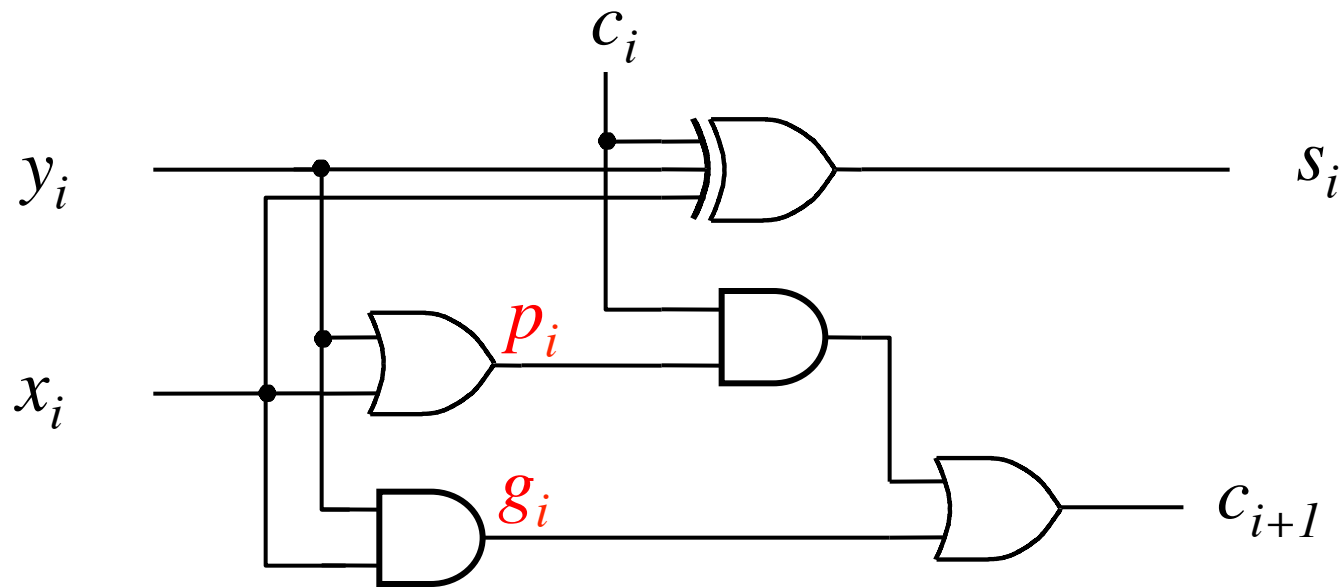
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} C_i$$



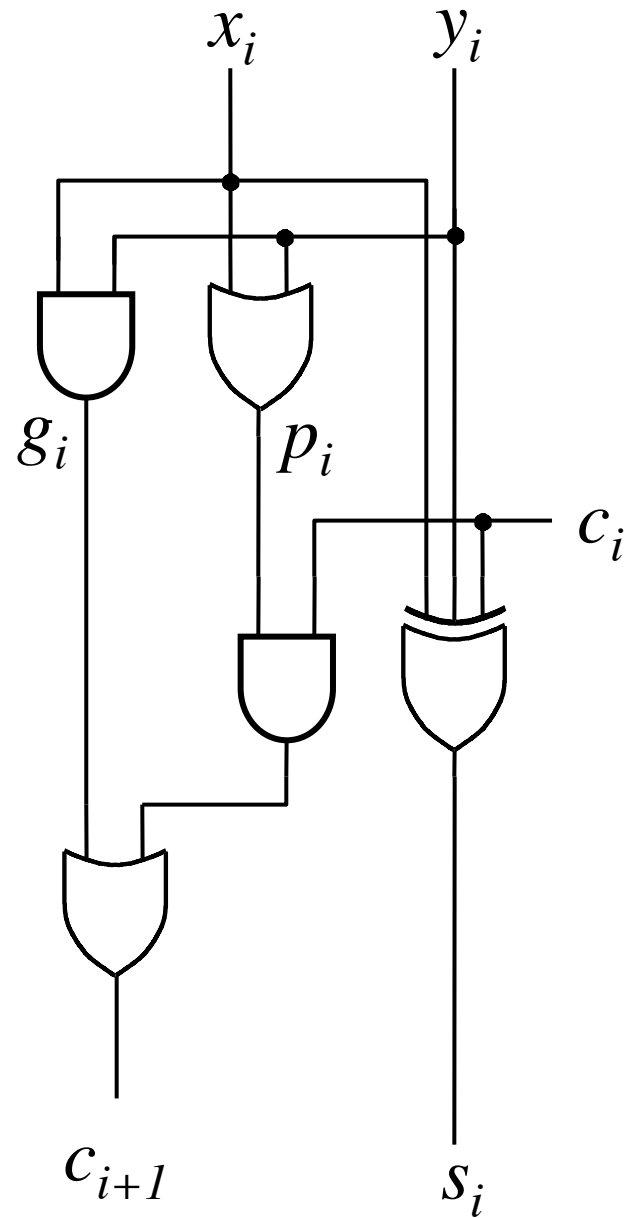Yet Another Way to Draw It (Just Rotate It)



Now we can Build a Ripple-Carry Adder

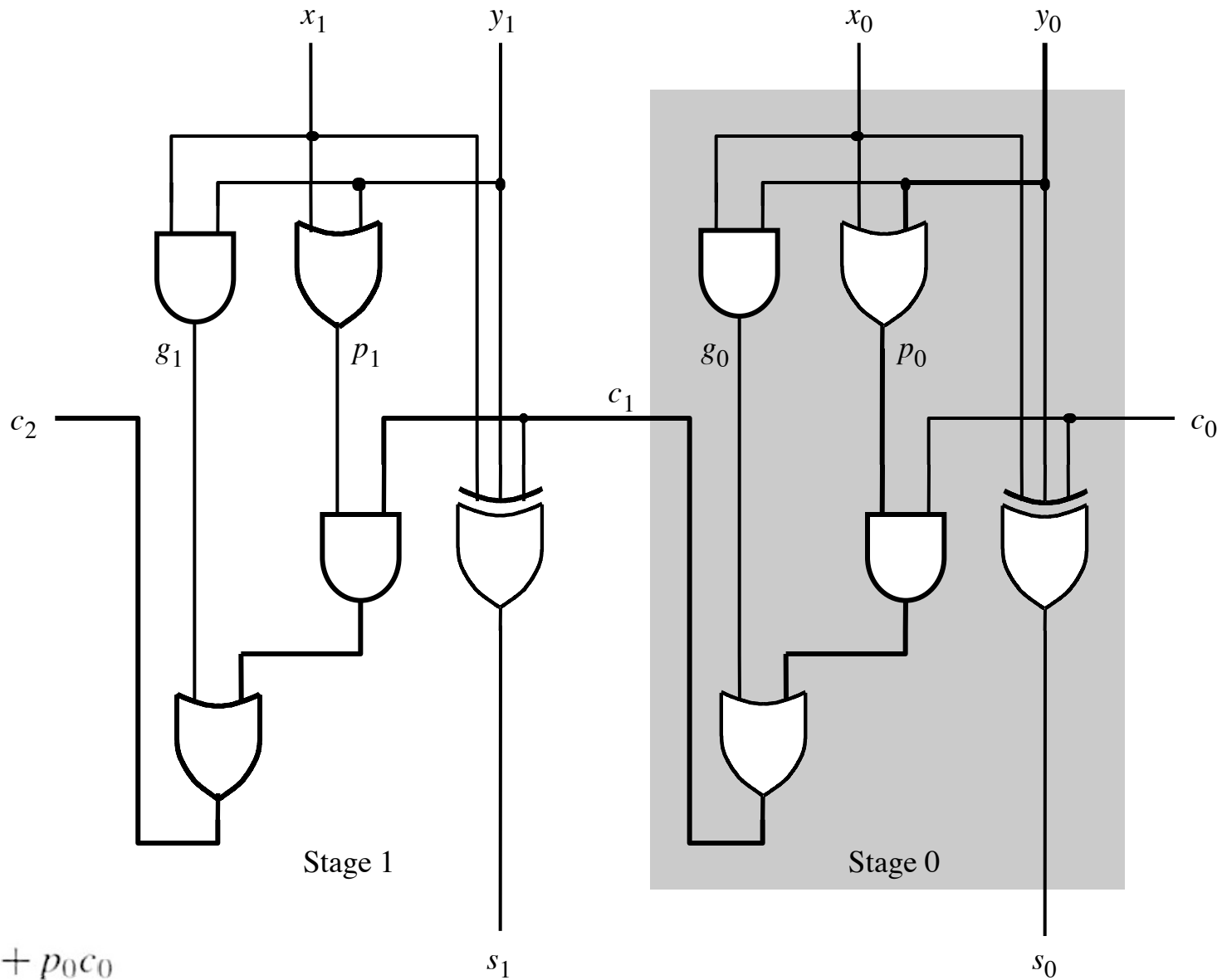


$$c_1 = g_0 + p_0c_0$$

$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$

[Figure 3.14 from the textbook]

Now we can Build a Ripple-Carry Adder

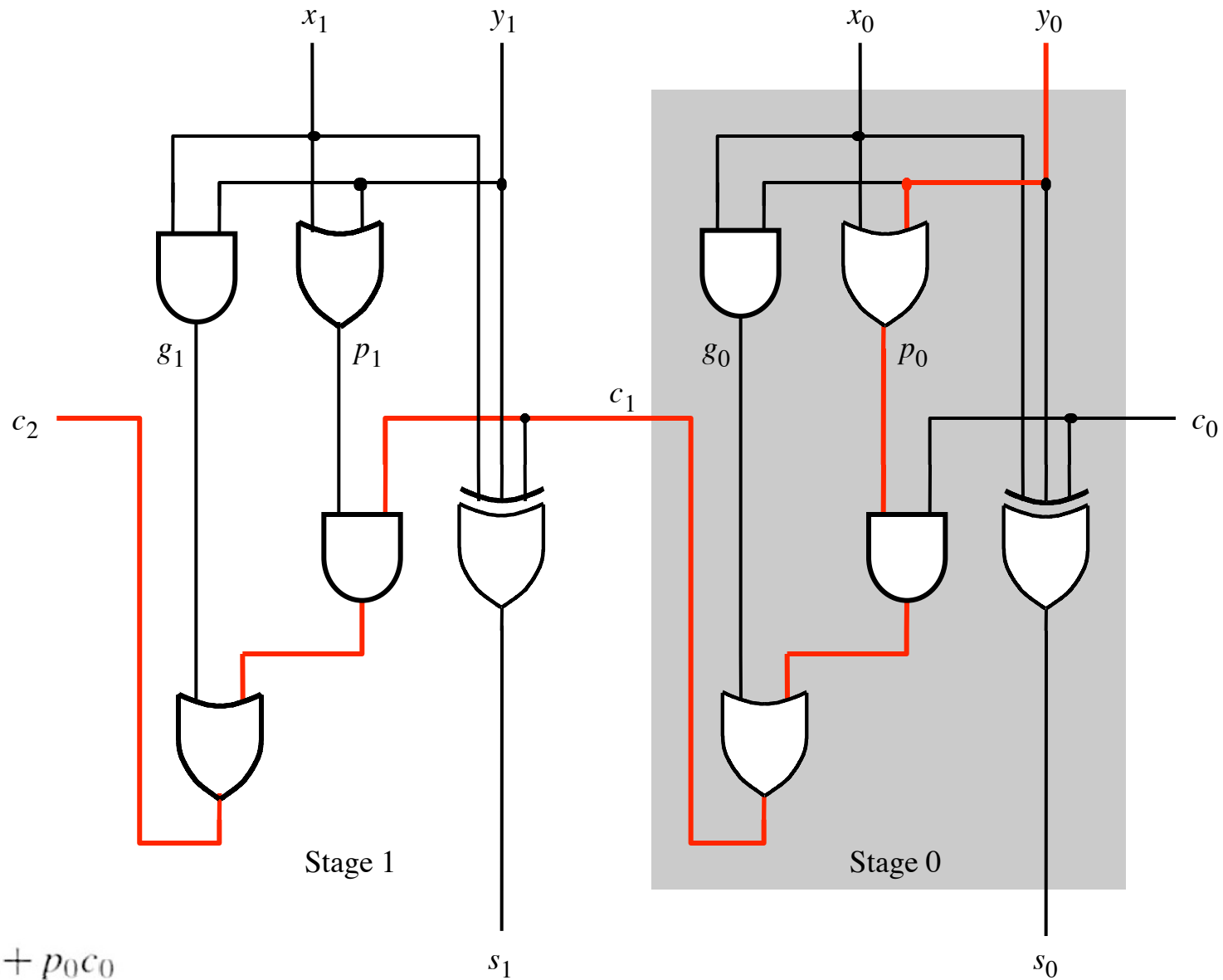


$$c_1 = g_0 + p_0c_0$$


$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$

[Figure 3.14 from the textbook]

The delay is 5 gates (1+2+2)

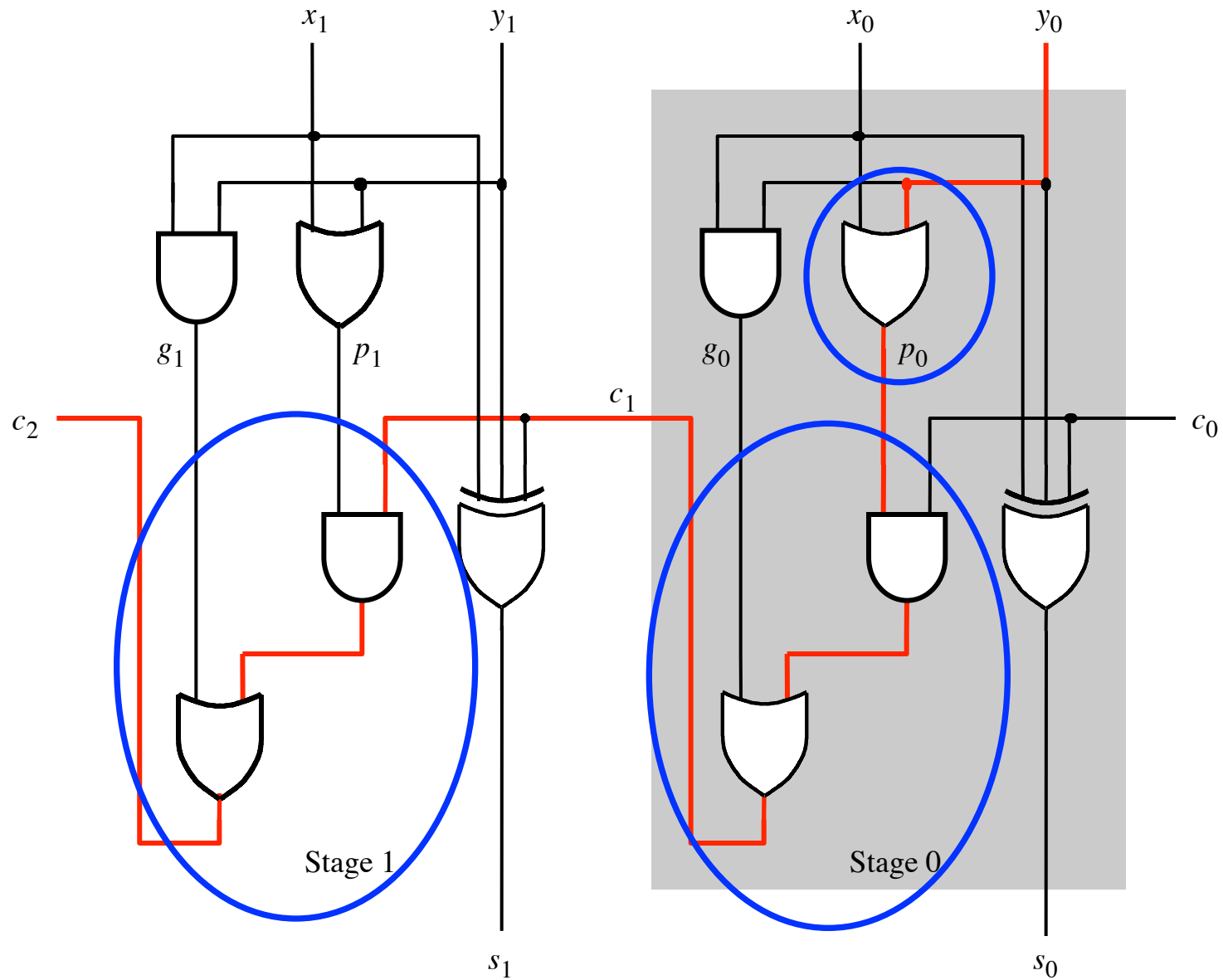

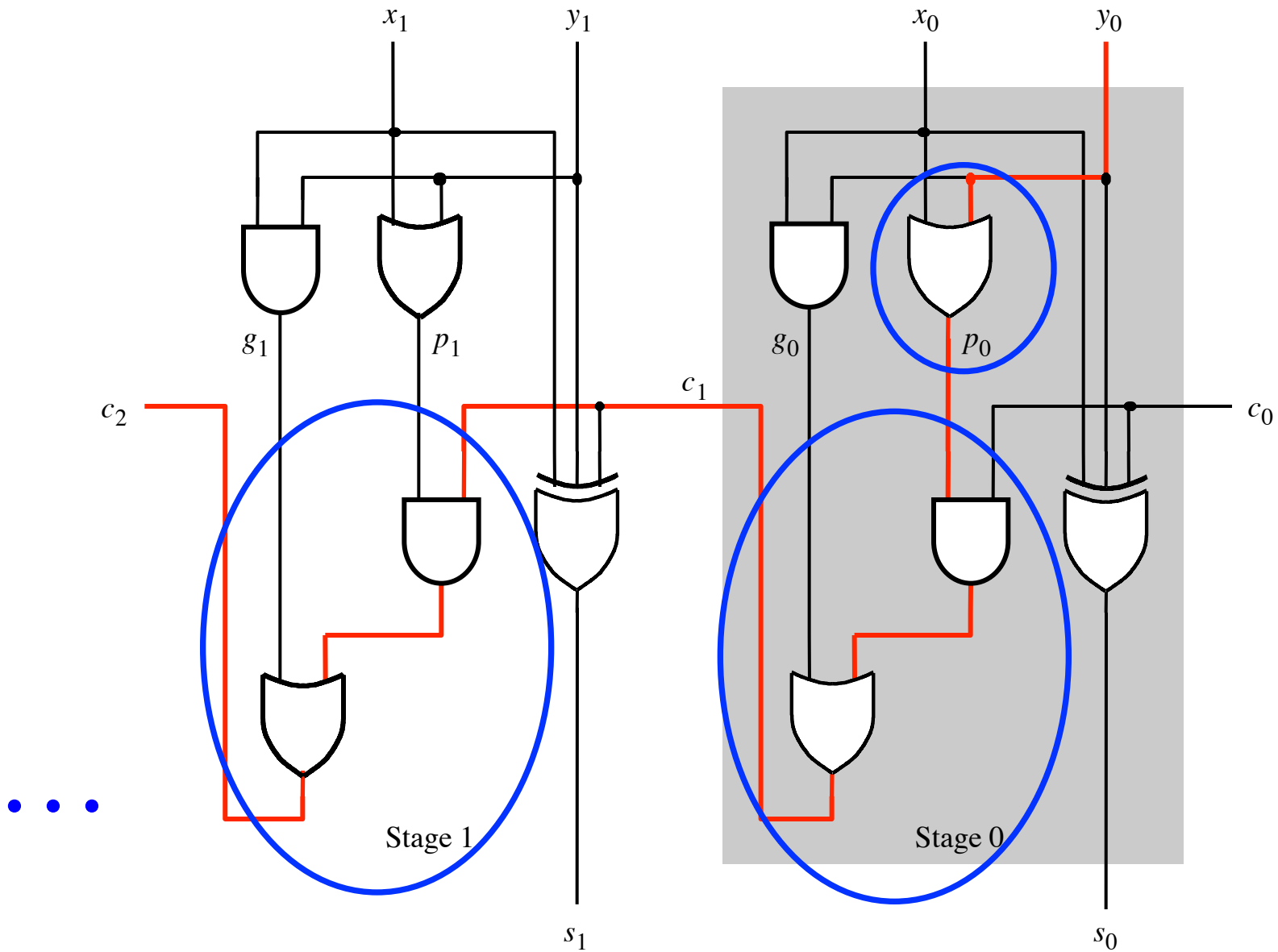n-bit ripple-carry adder: $2n+1$ gate delays



Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$


$$= g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1}$$

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

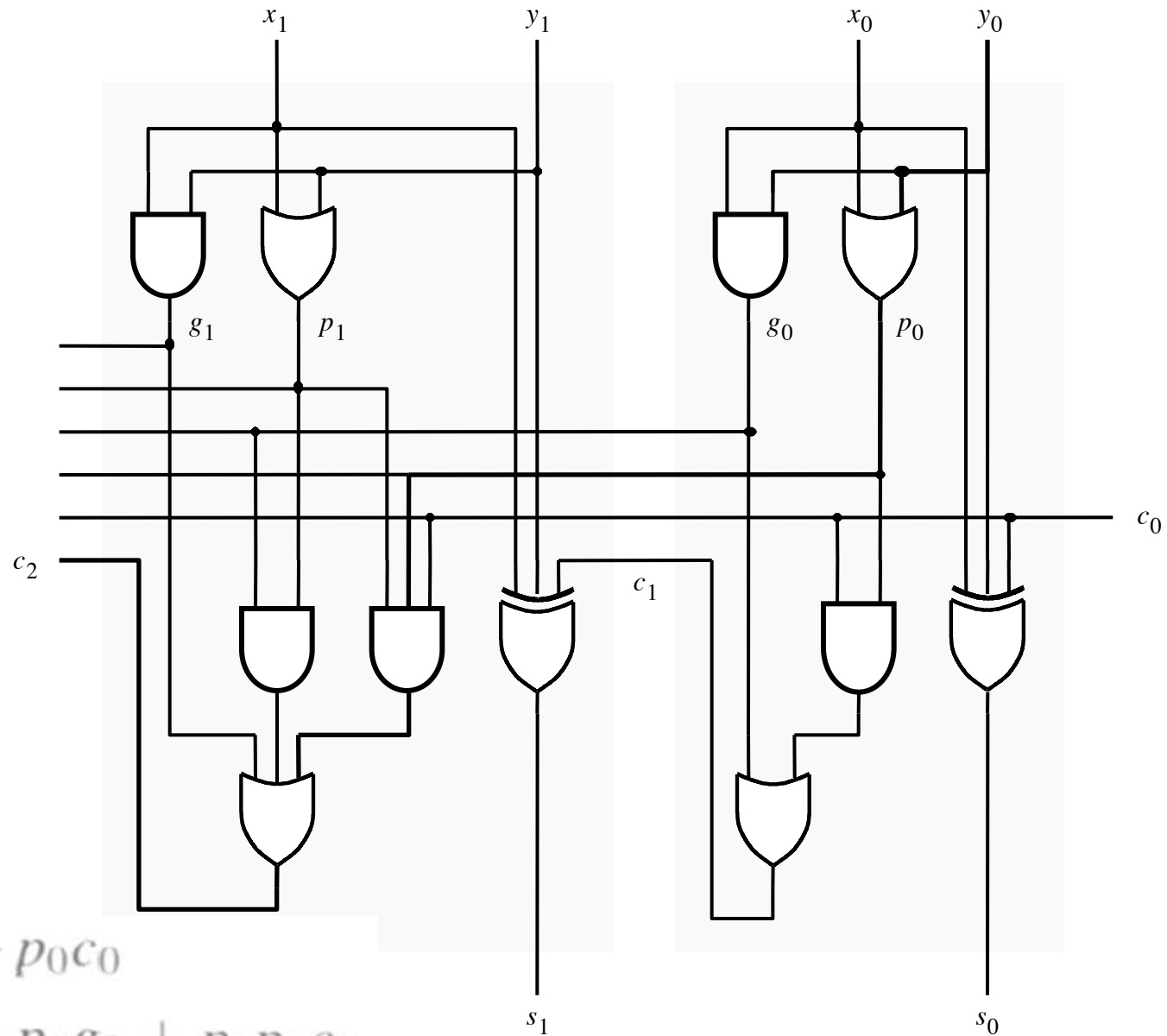The first two stages of a carry-lookahead adder




$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[Figure 3.15 from the textbook]


It takes 3 gate delays to generate c_1

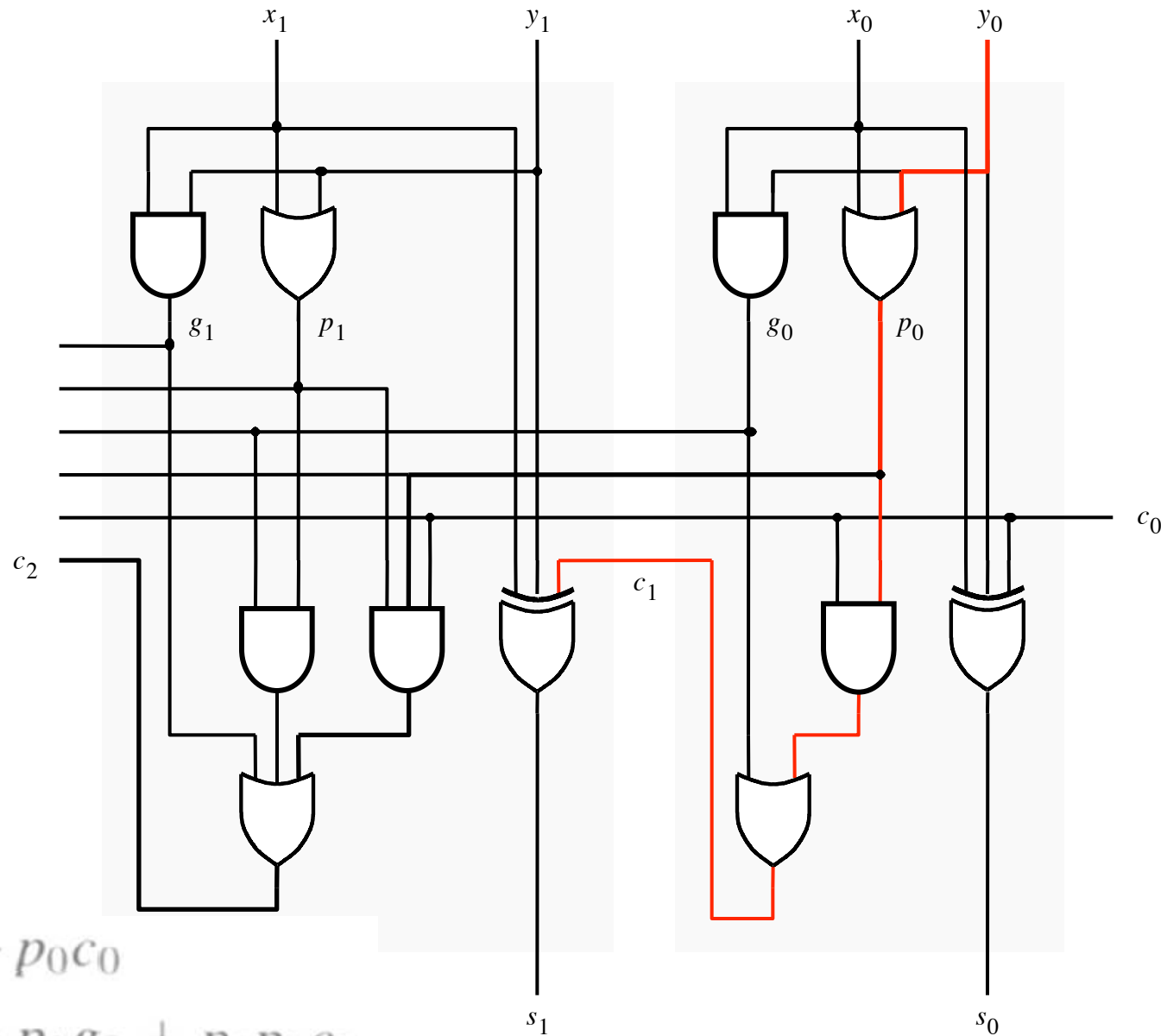

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$


It takes 3 gate delays to generate c_2

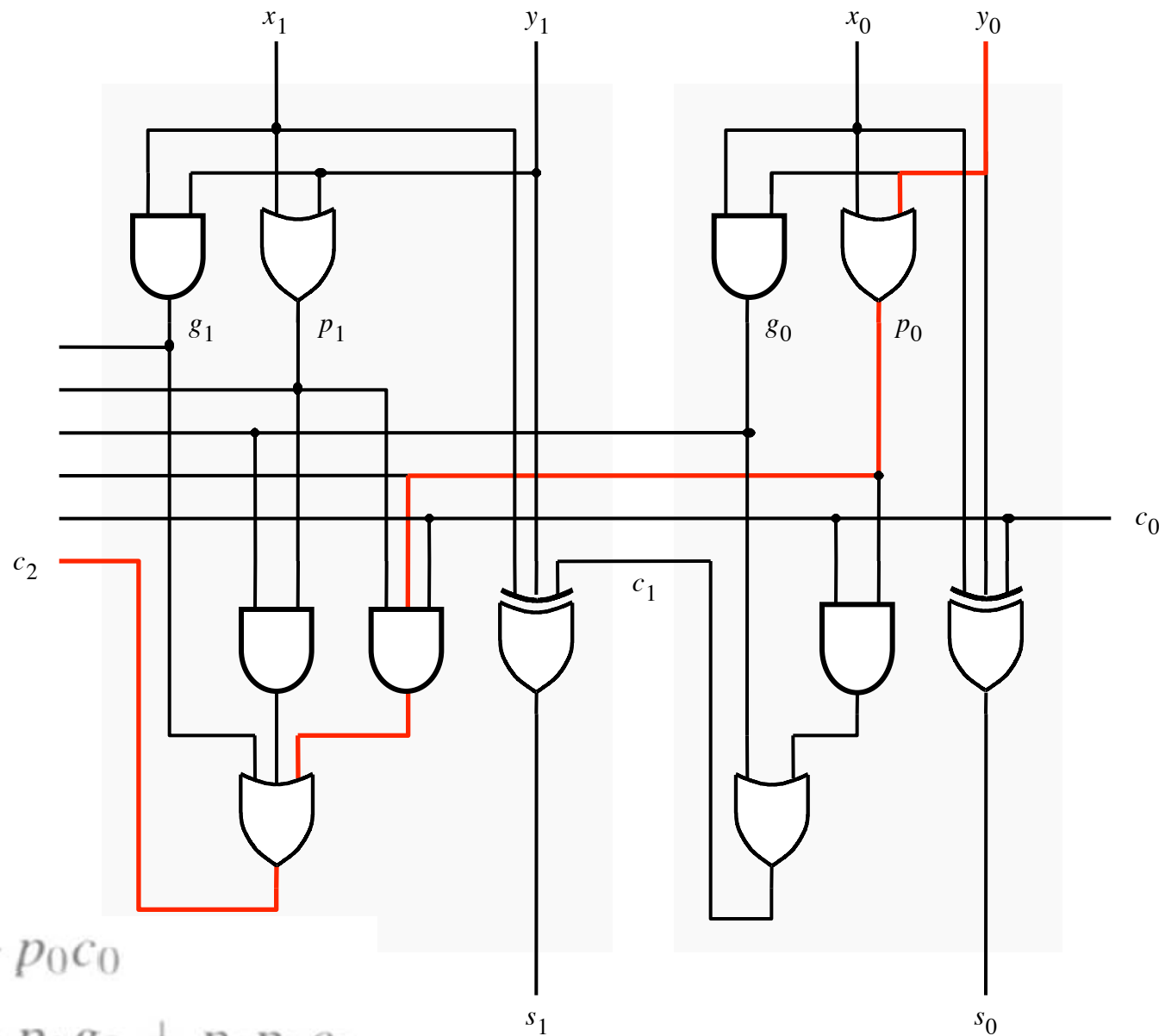


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

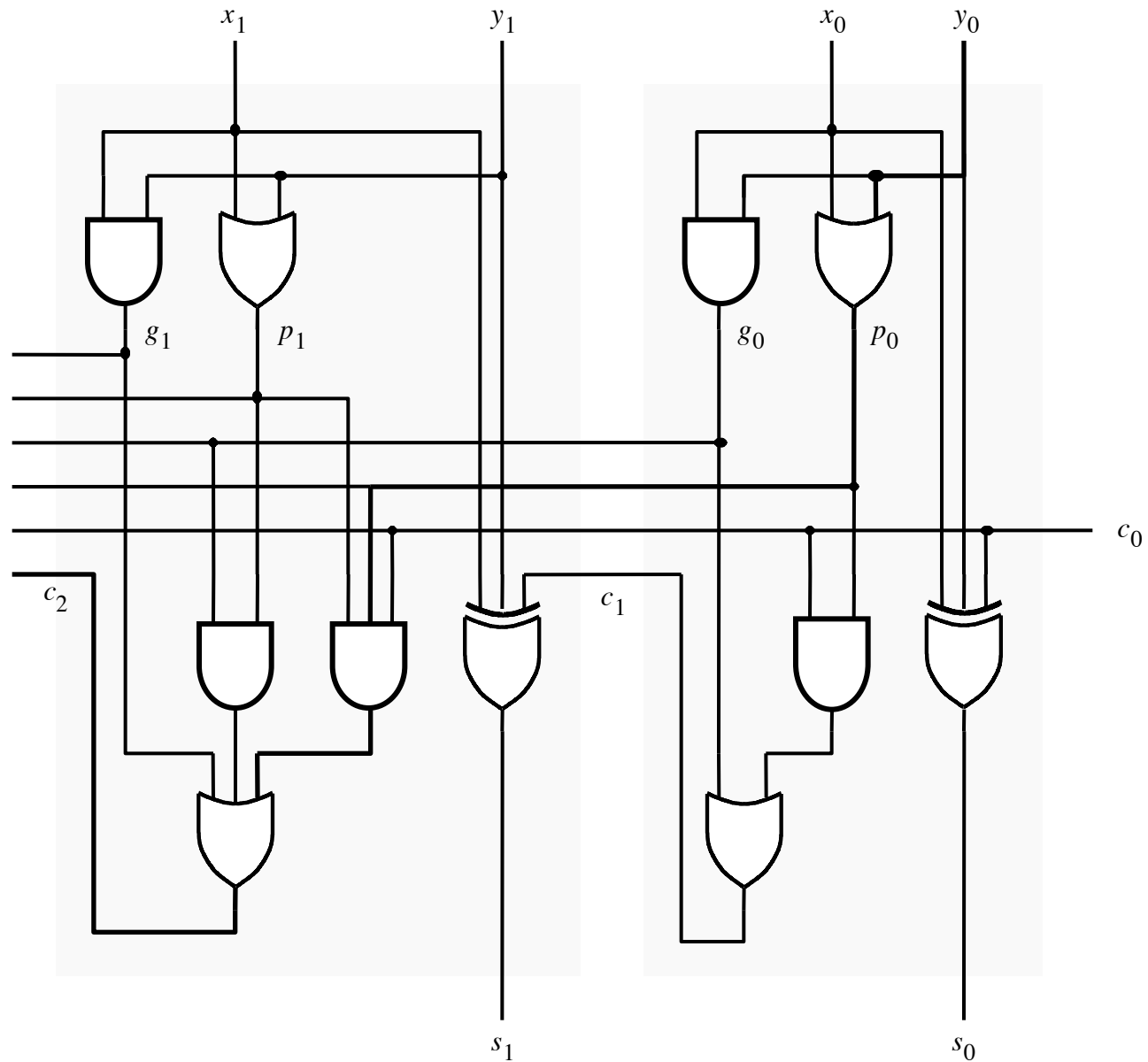The first two stages of a carry-lookahead adder



It takes 4 gate delays to generate s_2

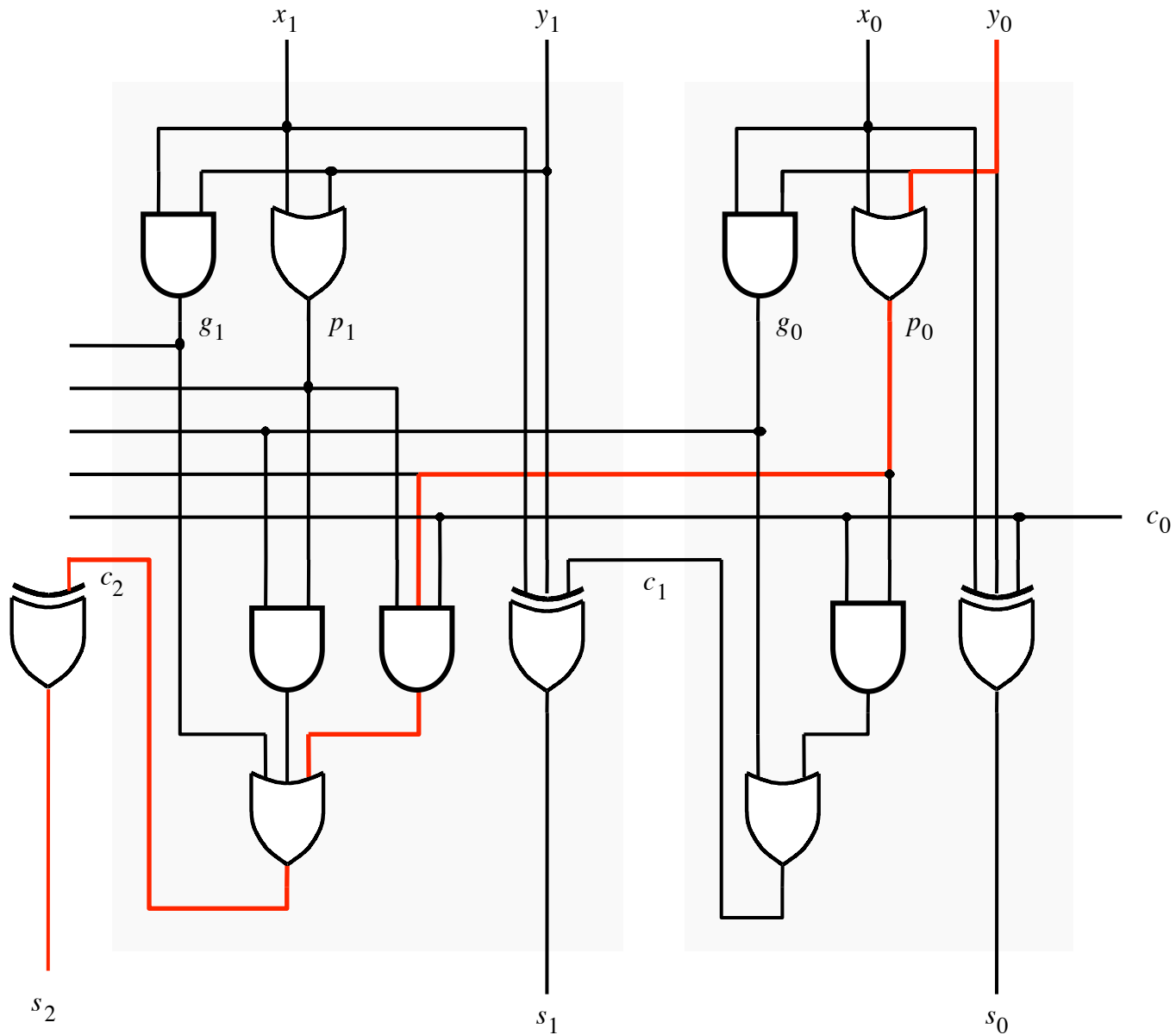

N-bit Carry-Lookahead Adder

- **It takes 3 gate delays to generate all carry signals**
- **It takes 1 more gate delay to generate all sum bits**
- **Thus, the total delay through an n-bit carry-lookahead adder is only 4 gate delays!**

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$


Even this takes
only 3 gate delays

$$+ p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2$$

$$+ p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0$$

$$+ p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0$$

A hierarchical carry-lookahead adder with ripple-carry between blocks

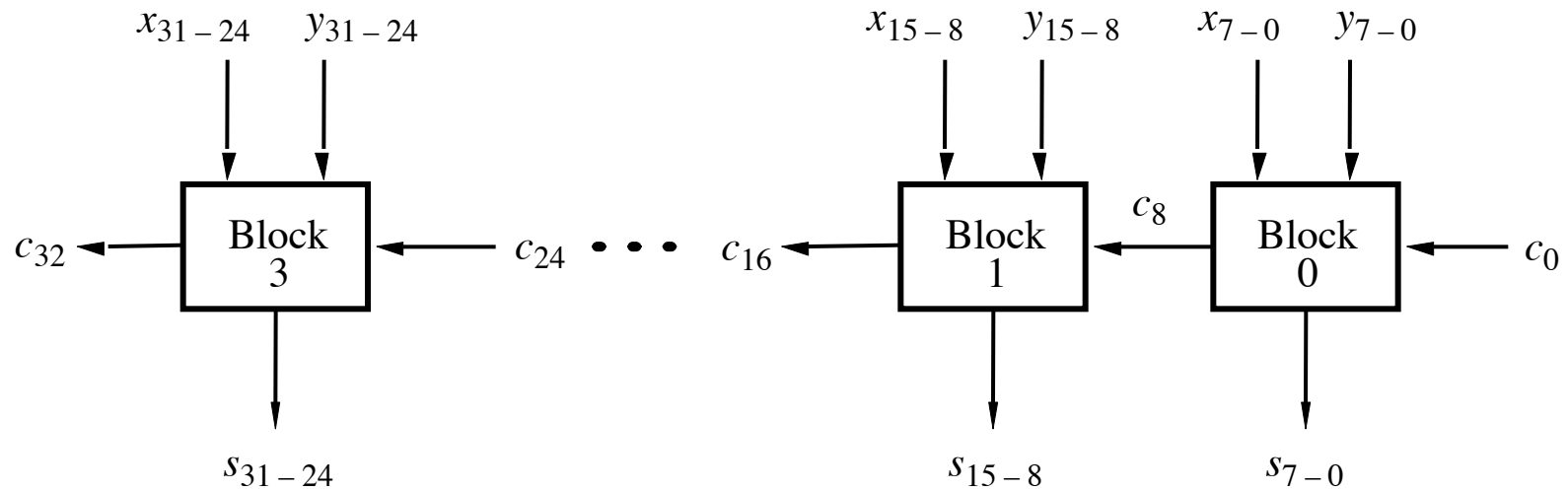

[Figure 3.16 from the textbook]

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned} c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 →

P_0 →

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 →

P_0 →

$$c_8 = G_0 + P_0c_0$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$



$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

Hierarchical CLA Adder Carry Logic

- C8** – 5 gate delays
- C16** – 5 gate delays
- C24** – 5 Gate delays
- C32** – 5 Gate delays

SECOND
LEVEL
HIERARCHY

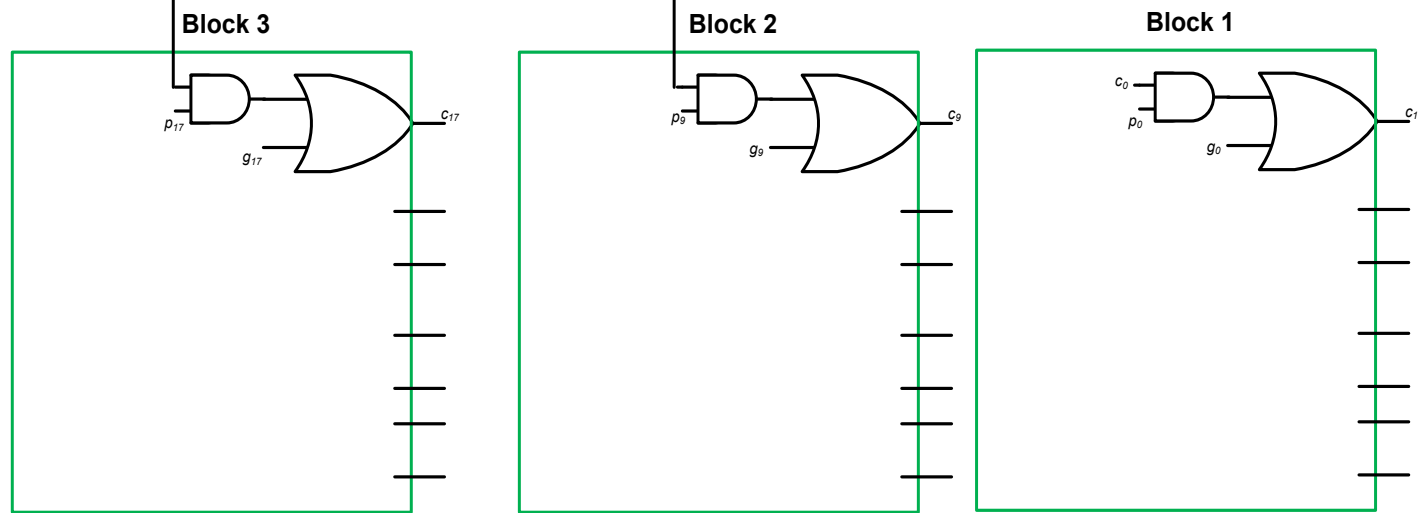
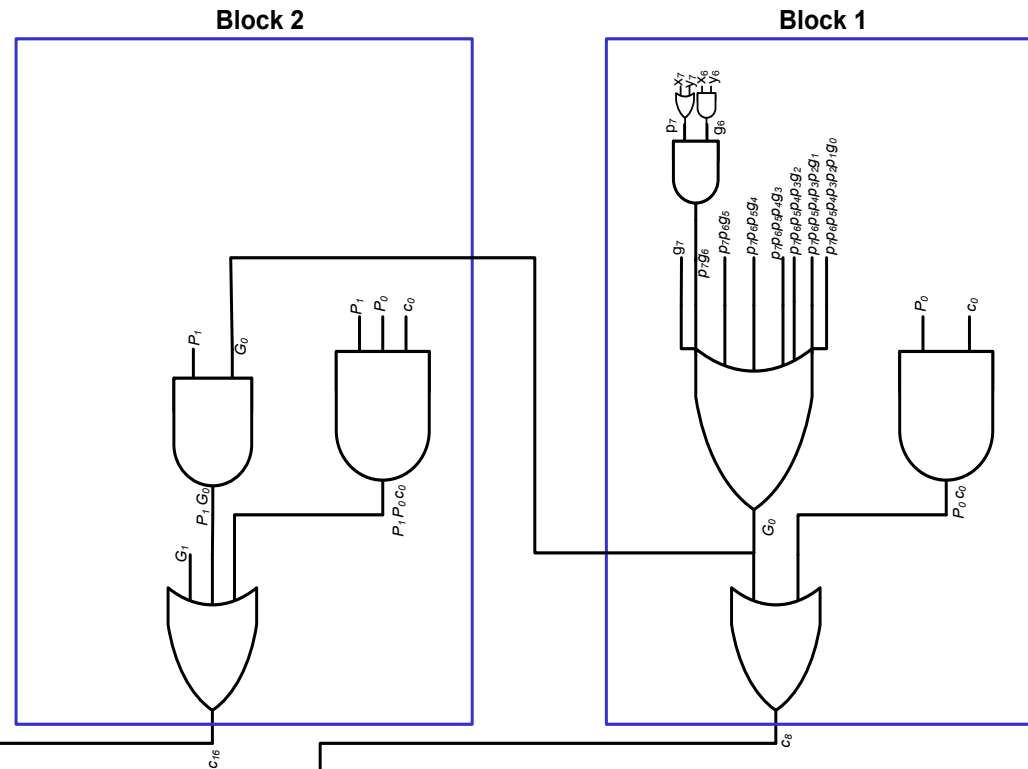


FIRST LEVEL HIERARCHY

Hierarchical CLA Critical Path

SECOND
LEVEL
HIERARCHY

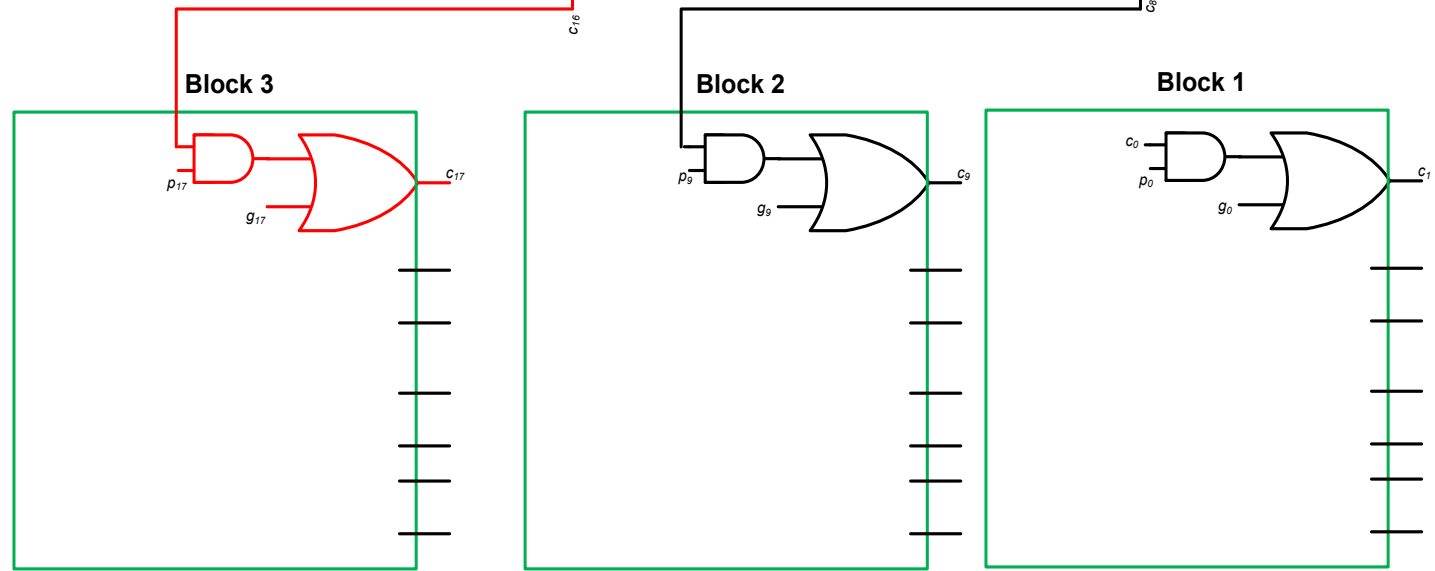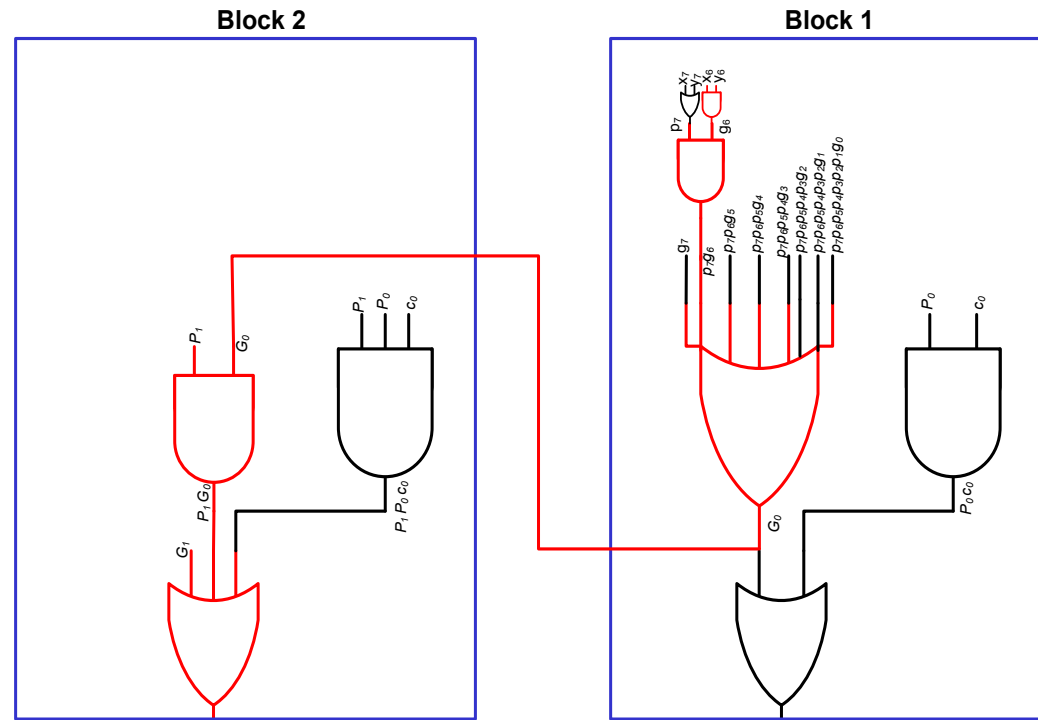- C9 – 7 gate delays
- C17 – 7 gate delays
- C25 – 7 Gate delays



FIRST LEVEL HIERARCHY

Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- Is 8 gates
 - 3 to generate all G_j and P_j
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)

Decimal Multiplication by 10

What happens when we multiply a number by 10?

$$4 \times 10 = ?$$

$$542 \times 10 = ?$$

$$1245 \times 10 = ?$$

Decimal Multiplication by 10

What happens when we multiply a number by 10?

$$4 \times 10 = 40$$

$$542 \times 10 = 5420$$

$$1245 \times 10 = 12450$$

Decimal Multiplication by 10

What happens when we multiply a number by 10?

$$4 \times 10 = 40$$

$$542 \times 10 = 5420$$

$$1245 \times 10 = 12450$$

You simply add a zero as the rightmost number

Decimal Division by 10

What happens when we divide a number by 10?

$$14 / 10 = ?$$

$$540 / 10 = ?$$

$$1240 \times 10 = ?$$

Decimal Division by 10

What happens when we divide a number by 10?

$$14 / 10 = 1 \quad //\text{integer division}$$

$$540 / 10 = 54$$

$$1240 / 10 = 124$$

You simply delete the rightmost number

Binary Multiplication by 2

What happens when we multiply a number by 2?

011 times 2 = ?

101 times 2 = ?

110011 times 2 = ?

Binary Multiplication by 2

What happens when we multiply a number by 2?

$$011 \text{ times } 2 = 0110$$

$$101 \text{ times } 2 = 1010$$

$$110011 \text{ times } 2 = 1100110$$

You simply add a zero as the rightmost number

Binary Multiplication by 4

What happens when we multiply a number by 4?

011 times 4 = ?

101 times 4 = ?

110011 times 4 = ?

Binary Multiplication by 4

What happens when we multiply a number by 4?

$$011 \text{ times } 4 = 01100$$

$$101 \text{ times } 4 = 10100$$

$$110011 \text{ times } 4 = 11001100$$

add two zeros in the last two bits and shift everything else to the left

Binary Multiplication by 2^N

What happens when we multiply a number by 2^N ?

011 times $2^N = 01100\dots0$ // add N zeros

101 times 4 = 10100...0 // add N zeros

110011 times 4 = 11001100...0 // add N zeros

Binary Division by 2

What happens when we divide a number by 2?

0110 divided by 2 = ?

1010 divides by 2 = ?

110011 divides by 2 = ?

Binary Division by 2

What happens when we divide a number by 2?

0110 divided by 2 = 011

1010 divides by 2 = 101

110011 divides by 2 = 11001

You simply delete the rightmost number

Decimal Multiplication By Hand

$$\begin{array}{r} 5127 \\ \times 4265 \\ \hline 25635 \\ 307620 \\ 1025400 \\ 20508000 \\ \hline 21866655 \end{array}$$

Binary Multiplication By Hand

| | | |
|----------------|-------|-----------------|
| Multiplicand M | (14) | 1 1 1 0 |
| Multiplier Q | (11) | x 1 0 1 1 |
| | | <hr/> |
| | | 1 1 1 0 |
| | | 1 1 1 0 |
| | | 0 0 0 0 |
| | | 1 1 1 0 |
| | | <hr/> |
| Product P | (154) | 1 0 0 1 1 0 1 0 |

Binary Multiplication By Hand

| | | |
|-------------------|-------|-----------------|
| Multiplicand M | (14) | 1 1 1 0 |
| Multiplier Q | (11) | × 1 0 1 1 |
| | | <hr/> |
| Partial product 0 | | 1 1 1 0 |
| | | + 1 1 1 0 |
| | | <hr/> |
| Partial product 1 | | 1 0 1 0 1 |
| | | + 0 0 0 0 |
| | | <hr/> |
| Partial product 2 | | 0 1 0 1 0 |
| | | + 1 1 1 0 |
| | | <hr/> |
| Product P | (154) | 1 0 0 1 1 0 1 0 |

The diagram illustrates the binary multiplication process. The multiplicand is 1110 (14) and the multiplier is 1011 (11). The partial products are 1110, 10101, and 01010. The final product is 10011010 (154). Blue arrows indicate the alignment of the partial products.

Binary Multiplication By Hand

| | | | | | | | | |
|-------------------|-------|-------|----------|----------|----------|----------|----------|--|
| | | | | m_3 | m_2 | m_1 | m_0 | |
| | | | \times | q_3 | q_2 | q_1 | q_0 | |
| | | | <hr/> | | | | | |
| Partial product 0 | | | | m_3q_0 | m_2q_0 | m_1q_0 | m_0q_0 | |
| | | | $+$ | m_3q_1 | m_2q_1 | m_1q_1 | m_0q_1 | |
| | | | <hr/> | | | | | |
| Partial product 1 | | | | $PP1_5$ | $PP1_4$ | $PP1_3$ | $PP1_2$ | |
| | | | $+$ | m_3q_2 | m_2q_2 | m_1q_2 | m_0q_2 | |
| | | | <hr/> | | | | | |
| Partial product 2 | | | | $PP2_6$ | $PP2_5$ | $PP2_4$ | $PP2_3$ | |
| | | | $+$ | m_3q_3 | m_2q_3 | m_1q_3 | m_0q_3 | |
| | | | <hr/> | | | | | |
| Product P | p_7 | p_6 | p_5 | p_4 | p_3 | p_2 | p_1 | |

[Figure 3.34c from the textbook]

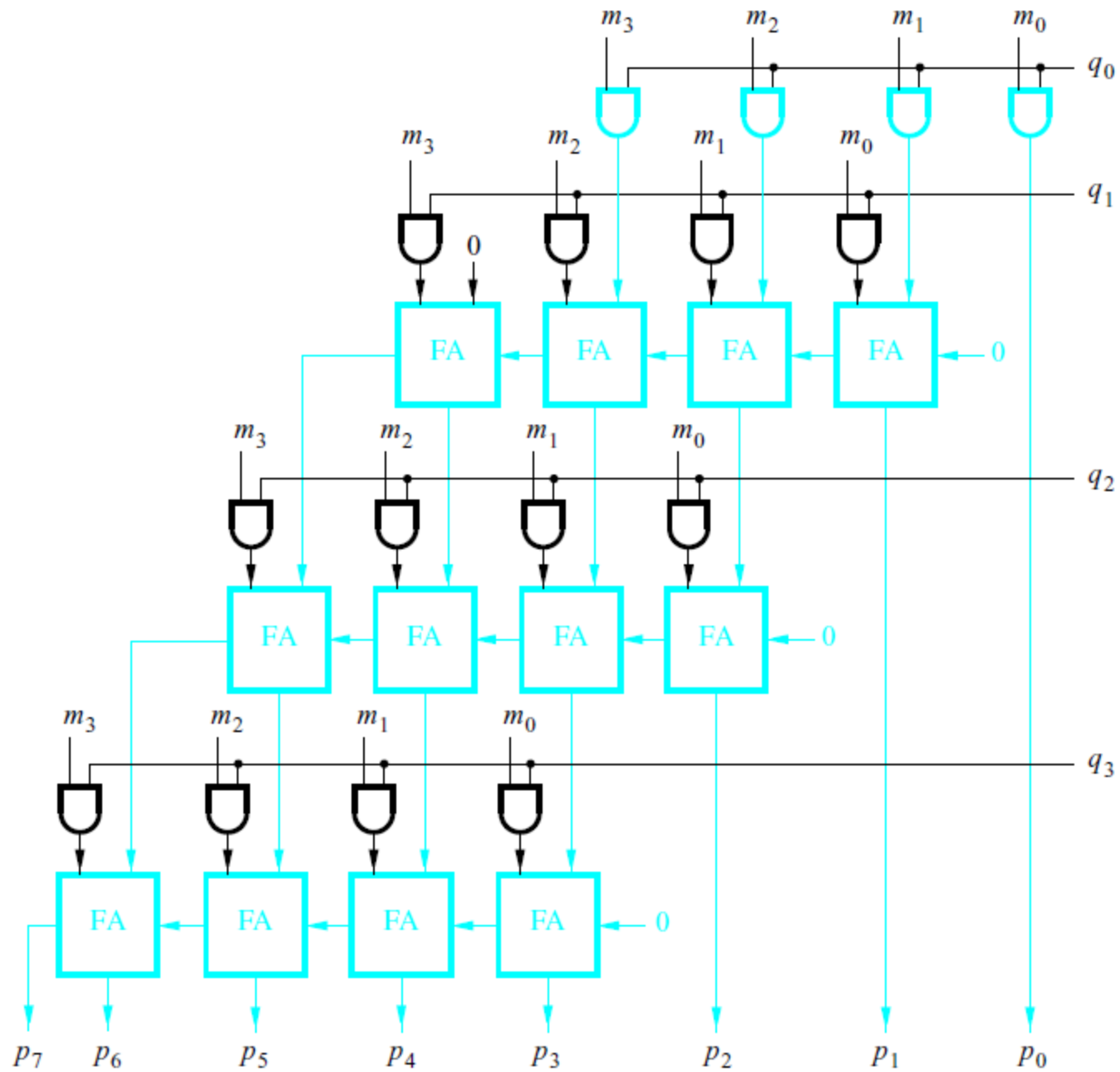


Figure 3.35. A 4x4 multiplier circuit.

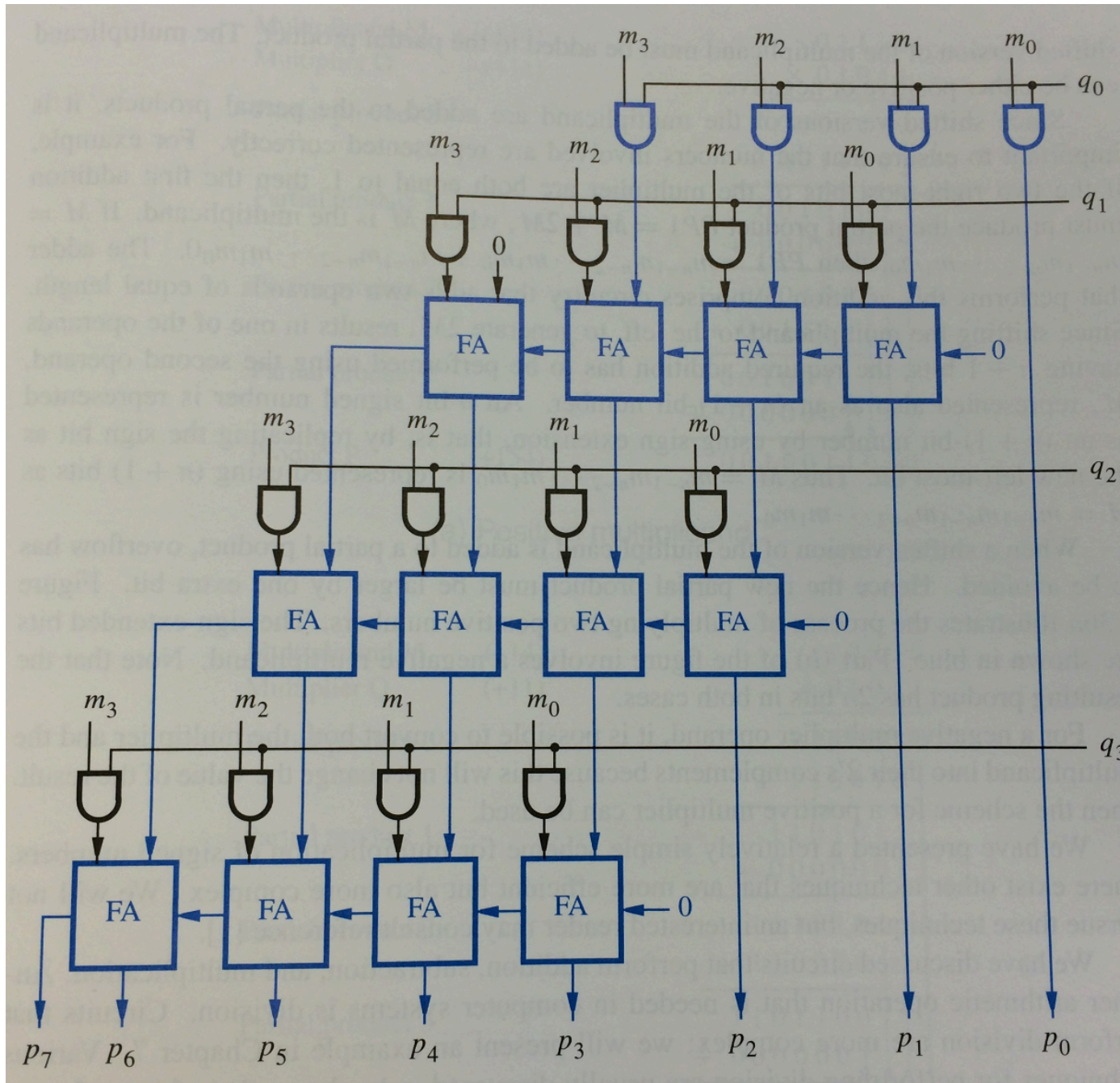


Figure 3.35. A 4x4 multiplier circuit.

Positive Multiplicand Example

Multiplicand M (+14)

Multiplier Q (+11)

Partial product 0

Partial product 1

Partial product 2

Partial product 3

Product P (+154)

$$\begin{array}{r}
 01110 \\
 \times 01011 \\
 \hline
 0001110 \\
 + 001110 \\
 \hline
 0010101 \\
 + 000000 \\
 \hline
 0001010 \\
 + 001110 \\
 \hline
 0010011 \\
 + 000000 \\
 \hline
 0010011010
 \end{array}$$

[Figure 3.36a in the textbook]

Positive Multiplicand Example

| | | |
|------------------------------------------|---------------------------------------|---------------------|
| Multiplicand M | (+14) | 0 1 1 1 0 |
| Multiplier Q | (+11) | x 0 1 0 1 1 |
| <hr style="border: 0.5px solid black;"/> | | |
| Partial product 0 | | 0 0 0 1 1 1 0 |
| | add an extra bit to avoid overflow | + 0 0 1 1 1 0 |
| <hr style="border: 0.5px solid black;"/> | | |
| Partial product 1 | | 0 0 1 0 1 0 1 |
| | | + 0 0 0 0 0 0 |
| <hr style="border: 0.5px solid black;"/> | | |
| Partial product 2 | | 0 0 0 1 0 1 0 |
| | | + 0 0 1 1 1 0 |
| <hr style="border: 0.5px solid black;"/> | | |
| Partial product 3 | | 0 0 1 0 0 1 1 |
| | | + 0 0 0 0 0 0 |
| <hr style="border: 0.5px solid black;"/> | | |
| Product P | (+154) | 0 0 1 0 0 1 1 0 1 0 |

[Figure 3.36a in the textbook]

Negative Multiplicand Example

Multiplicand M (-14)

Multiplier Q (+11)


Partial product 0

Partial product 1

Partial product 2

Partial product 3

Product P (-154)

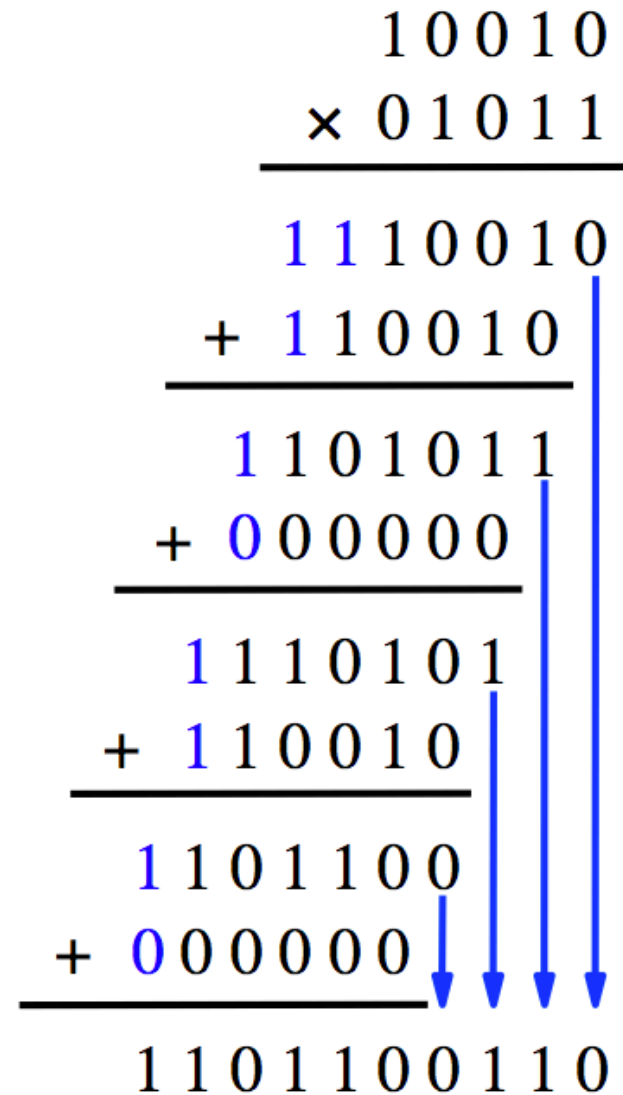

[Figure 3.36b in the textbook]

Negative Multiplicand Example

| | | |
|-------------------|----------------------------------------------------------|--------------------------------------------------------------|
| Multiplicand M | (-14) | 1 0 0 1 0 |
| Multiplier Q | (+11) | × 0 1 0 1 1 |
| Partial product 0 | add an extra bit to avoid overflow but now it is 1 | $\begin{array}{r} 1110010 \\ + 110010 \\ \hline \end{array}$ |
| Partial product 1 | | $\begin{array}{r} 1101011 \\ + 000000 \\ \hline \end{array}$ |
| Partial product 2 | | $\begin{array}{r} 1110101 \\ + 110010 \\ \hline \end{array}$ |
| Partial product 3 | | $\begin{array}{r} 1101100 \\ + 000000 \\ \hline \end{array}$ |
| Product P | (-154) | 1 1 0 1 1 0 0 1 1 0 |

[Figure 3.36b in the textbook]

What if the Multiplier is Negative?

- Convert both to their 2's complement version
- This will make the multiplier positive
- Then Proceed as normal
- This will not affect the result
- Example: $5 * (-4) = (-5) * (4) = -20$

Binary Coded Decimal

Table of Binary-Coded Decimal Digits

| Decimal digit | BCD code |
|---------------|----------|
| 0 | 0000 |
| 1 | 0001 |
| 2 | 0010 |
| 3 | 0011 |
| 4 | 0100 |
| 5 | 0101 |
| 6 | 0110 |
| 7 | 0111 |
| 8 | 1000 |
| 9 | 1001 |

Addition of BCD digits

| | | |
|-------|-----------|-------|
| X | 0 1 1 1 | 7 |
| + Y | + 0 1 0 1 | + 5 |
| <hr/> | <hr/> | <hr/> |
| Z | 1 1 0 0 | 12 |

Addition of BCD digits

$$\begin{array}{r} X \\ + Y \\ \hline Z \end{array} \quad \begin{array}{r} 0111 \\ + 0101 \\ \hline 1100 \end{array} \quad \begin{array}{r} 7 \\ + 5 \\ \hline 12 \end{array}$$

The result is greater than 9, which is not a valid BCD number

Addition of BCD digits

| | | |
|---------|-----------------------------|-----|
| X | 0 1 1 1 | 7 |
| + Y | + 0 1 0 1 | + 5 |
| <hr/> | | |
| Z | 1 1 0 0 | 12 |
| | + 0 1 1 0 | |
| | <hr/> | |
| carry → | 1 0 0 1 0 | |
| | $\underbrace{\hspace{2em}}$ | |
| | S = 2 | |

← add 6

[Figure 3.38a in the textbook]


Addition of BCD digits

| | | |
|-------|-----------|-------|
| X | 1 0 0 0 | 8 |
| + Y | + 1 0 0 1 | + 9 |
| <hr/> | <hr/> | <hr/> |
| Z | 1 0 0 0 1 | 17 |

[Figure 3.38b in the textbook]

Addition of BCD digits

| | | |
|-------|-----------|-----|
| X | 1 0 0 0 | 8 |
| + Y | + 1 0 0 1 | + 9 |
| <hr/> | | |
| Z | 1 0 0 0 1 | 17 |



The result is 1, but it should be 7

Addition of BCD digits

| | | |
|---------|-----------|-----|
| X | 1 0 0 0 | 8 |
| + Y | + 1 0 0 1 | + 9 |
| <hr/> | | |
| Z | 1 0 0 0 1 | 17 |
| | + 0 1 1 0 | |
| | <hr/> | |
| carry → | 1 0 1 1 1 | |
| | ⏟ | |
| | S = 7 | |

← add 6

Why add 6?

- **Think of BCD addition as a mod 16 operation**
- **Decimal addition is mod 10 operation**


BCD Arithmetic Rules

$$Z = X + Y$$

If $Z \leq 9$, then $S=Z$ and carry-out = 0

If $Z > 9$, then $S=Z+6$ and carry-out = 1

Block diagram for a one-digit BCD adder

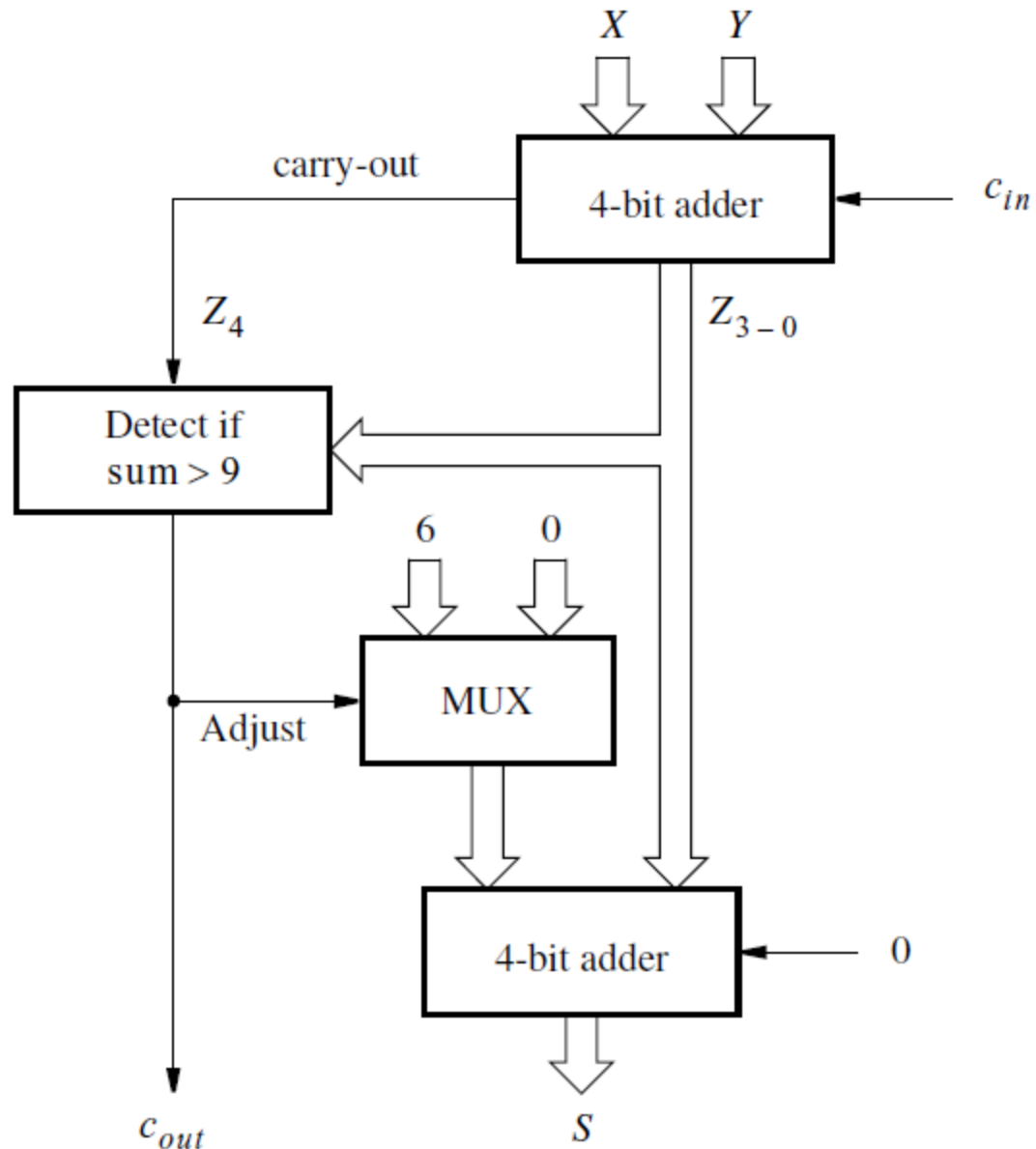

[Figure 3.39 in the textbook]

How to check if the number is > 9 ?

7 - 0111

8 - 1000

9 - 1001

10 - 1010

11 - 1011

12 - 1100


13 - 1101

14 - 1110

15 - 1111

A four-variable Karnaugh map

| x1 | x2 | x3 | x4 | |
|----|----|----|----|-----|
| 0 | 0 | 0 | 0 | m0 |
| 0 | 0 | 0 | 1 | m1 |
| 0 | 0 | 1 | 0 | m2 |
| 0 | 0 | 1 | 1 | m3 |
| 0 | 1 | 0 | 0 | m4 |
| 0 | 1 | 0 | 1 | m5 |
| 0 | 1 | 1 | 0 | m6 |
| 0 | 1 | 1 | 1 | m7 |
| 1 | 0 | 0 | 0 | m8 |
| 1 | 0 | 0 | 1 | m9 |
| 1 | 0 | 1 | 0 | m10 |
| 1 | 0 | 1 | 1 | m11 |
| 1 | 1 | 0 | 0 | m12 |
| 1 | 1 | 0 | 1 | m13 |
| 1 | 1 | 1 | 0 | m14 |
| 1 | 1 | 1 | 1 | m15 |

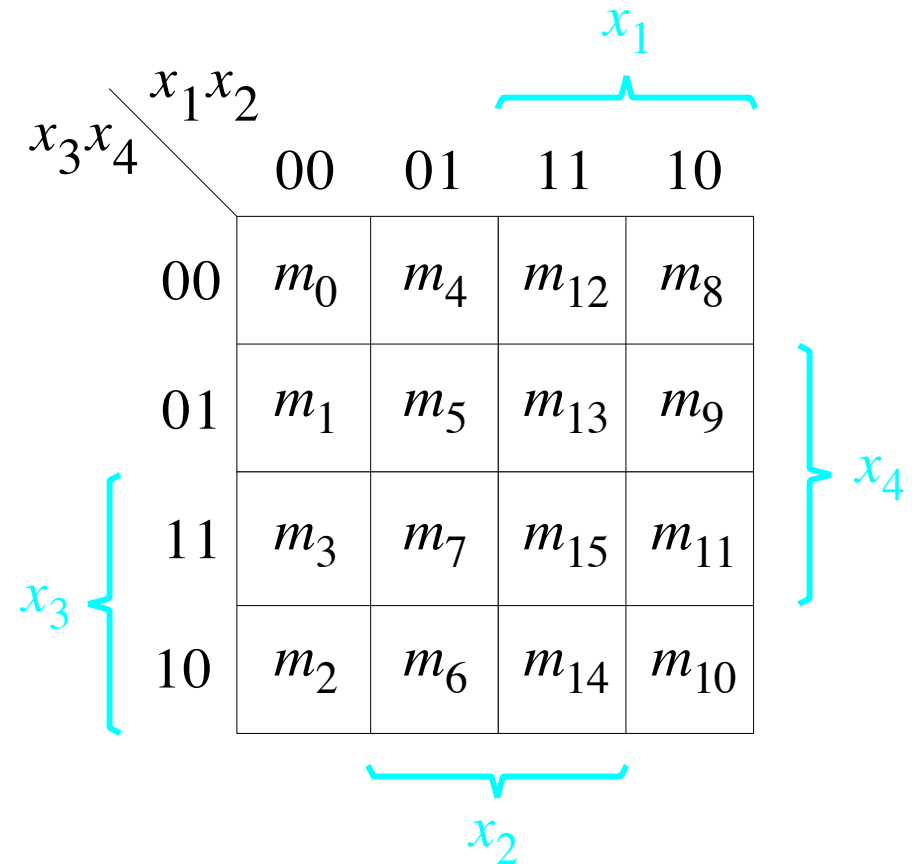

How to check if the number is > 9 ?

| z3 | z2 | z1 | z0 | |
|-------|----|----|----|-----|
| 0 | 0 | 0 | 0 | m0 |
| 0 | 0 | 0 | 1 | m1 |
| 0 | 0 | 1 | 0 | m2 |
| 0 | 0 | 1 | 1 | m3 |
| <hr/> | | | | |
| 0 | 1 | 0 | 0 | m4 |
| 0 | 1 | 0 | 1 | m5 |
| 0 | 1 | 1 | 0 | m6 |
| 0 | 1 | 1 | 1 | m7 |
| <hr/> | | | | |
| 1 | 0 | 0 | 0 | m8 |
| 1 | 0 | 0 | 1 | m9 |
| 1 | 0 | 1 | 0 | m10 |
| 1 | 0 | 1 | 1 | m11 |
| <hr/> | | | | |
| 1 | 1 | 0 | 0 | m12 |
| 1 | 1 | 0 | 1 | m13 |
| 1 | 1 | 1 | 0 | m14 |
| 1 | 1 | 1 | 1 | m15 |

| $z_3 z_2$ | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|
| 00 | 0 | 0 | 1 | 0 |
| 01 | 0 | 0 | 1 | 0 |
| 11 | 0 | 0 | 1 | 1 |
| 10 | 0 | 0 | 1 | 1 |

How to check if the number is > 9 ?

| z3 | z2 | z1 | z0 | |
|-------|----|----|----|-----|
| 0 | 0 | 0 | 0 | m0 |
| 0 | 0 | 0 | 1 | m1 |
| 0 | 0 | 1 | 0 | m2 |
| 0 | 0 | 1 | 1 | m3 |
| <hr/> | | | | |
| 0 | 1 | 0 | 0 | m4 |
| 0 | 1 | 0 | 1 | m5 |
| 0 | 1 | 1 | 0 | m6 |
| 0 | 1 | 1 | 1 | m7 |
| <hr/> | | | | |
| 1 | 0 | 0 | 0 | m8 |
| 1 | 0 | 0 | 1 | m9 |
| 1 | 0 | 1 | 0 | m10 |
| 1 | 0 | 1 | 1 | m11 |
| <hr/> | | | | |
| 1 | 1 | 0 | 0 | m12 |
| 1 | 1 | 0 | 1 | m13 |
| 1 | 1 | 1 | 0 | m14 |
| 1 | 1 | 1 | 1 | m15 |

| | | z_3z_2 | | z_1z_0 | |
|----------|----|----------|----|----------|----|
| | | 00 | 01 | 11 | 10 |
| z_1z_0 | 00 | 0 | 0 | 1 | 0 |
| | 01 | 0 | 0 | 1 | 0 |
| | 11 | 0 | 0 | 1 | 1 |
| | 10 | 0 | 0 | 1 | 1 |

$$f = z_3z_2 + z_3z_1$$

How to check if the number is > 9?

| z3 | z2 | z1 | z0 | |
|----|----|----|----|-----|
| 0 | 0 | 0 | 0 | m0 |
| 0 | 0 | 0 | 1 | m1 |
| 0 | 0 | 1 | 0 | m2 |
| 0 | 0 | 1 | 1 | m3 |
| 0 | 1 | 0 | 0 | m4 |
| 0 | 1 | 0 | 1 | m5 |
| 0 | 1 | 1 | 0 | m6 |
| 0 | 1 | 1 | 1 | m7 |
| 1 | 0 | 0 | 0 | m8 |
| 1 | 0 | 0 | 1 | m9 |
| 1 | 0 | 1 | 0 | m10 |
| 1 | 0 | 1 | 1 | m11 |
| 1 | 1 | 0 | 0 | m12 |
| 1 | 1 | 0 | 1 | m13 |
| 1 | 1 | 1 | 0 | m14 |
| 1 | 1 | 1 | 1 | m15 |

| $z_1z_0 \backslash z_3z_2$ | 00 | 01 | 11 | 10 |
|----------------------------|----|----|----|----|
| 00 | 0 | 0 | 1 | 0 |
| 01 | 0 | 0 | 1 | 0 |
| 11 | 0 | 0 | 1 | 1 |
| 10 | 0 | 0 | 1 | 1 |

$$f = z_3z_2 + z_3z_1$$

In addition, also check if there was a carry


$$f = \text{carry-out} + z_3z_2 + z_3z_1$$

Verilog code for a one-digit BCD adder

```
module bcdadd(Cin, X, Y, S, Cout);  
  input Cin;  
  input [3:0] X, Y;  
  output reg [3:0] S;  
  output reg Cout;  
  reg [4:0] Z;  
  
  always@ (X, Y, Cin)  
  begin  
    Z = X + Y + Cin;  
    if (Z < 10)  
      {Cout, S} = Z;  
    else  
      {Cout, S} = Z + 6;  
  end  
  
endmodule
```


[Figure 3.40 in the textbook]

Circuit for a one-digit BCD adder

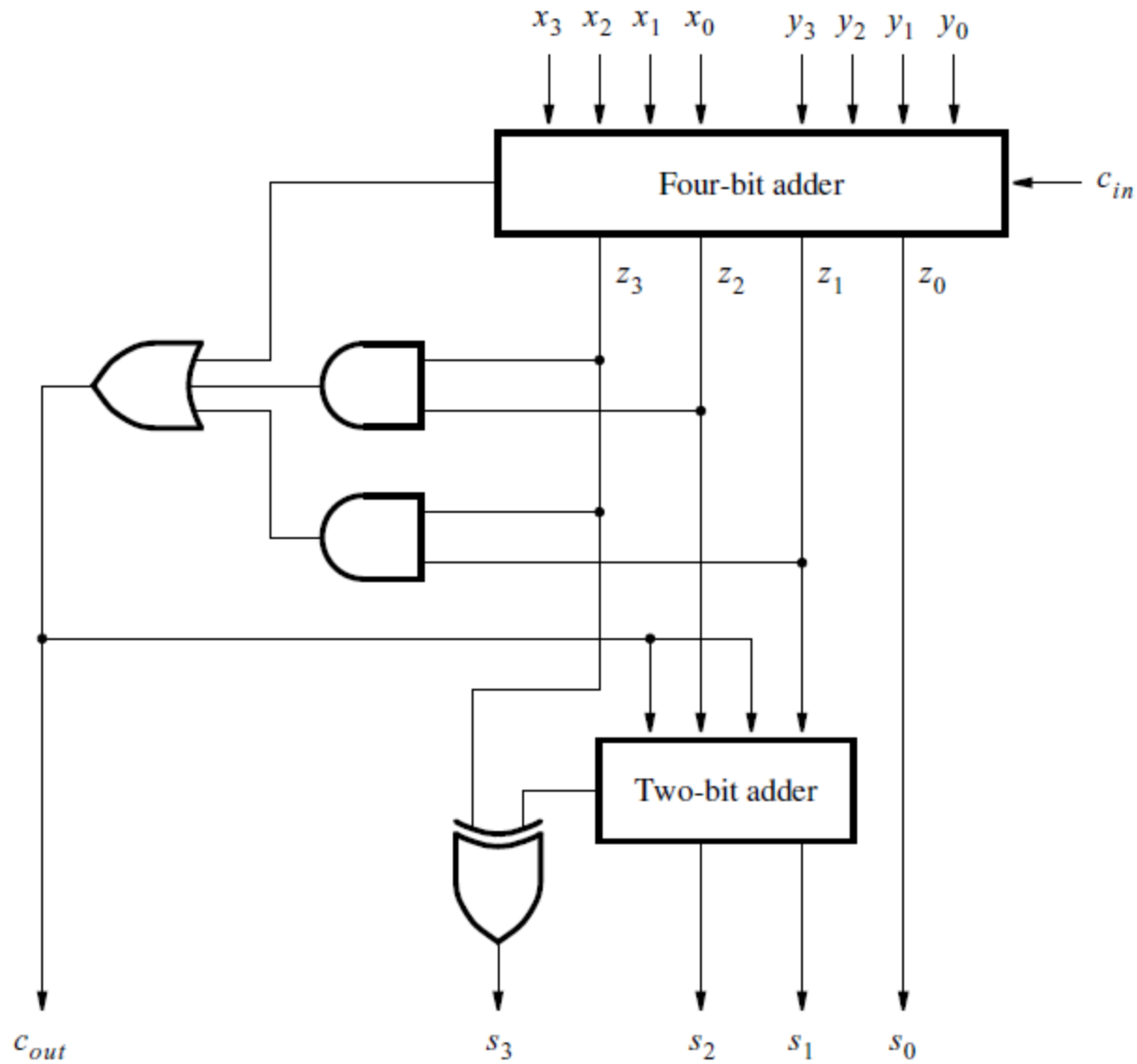


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

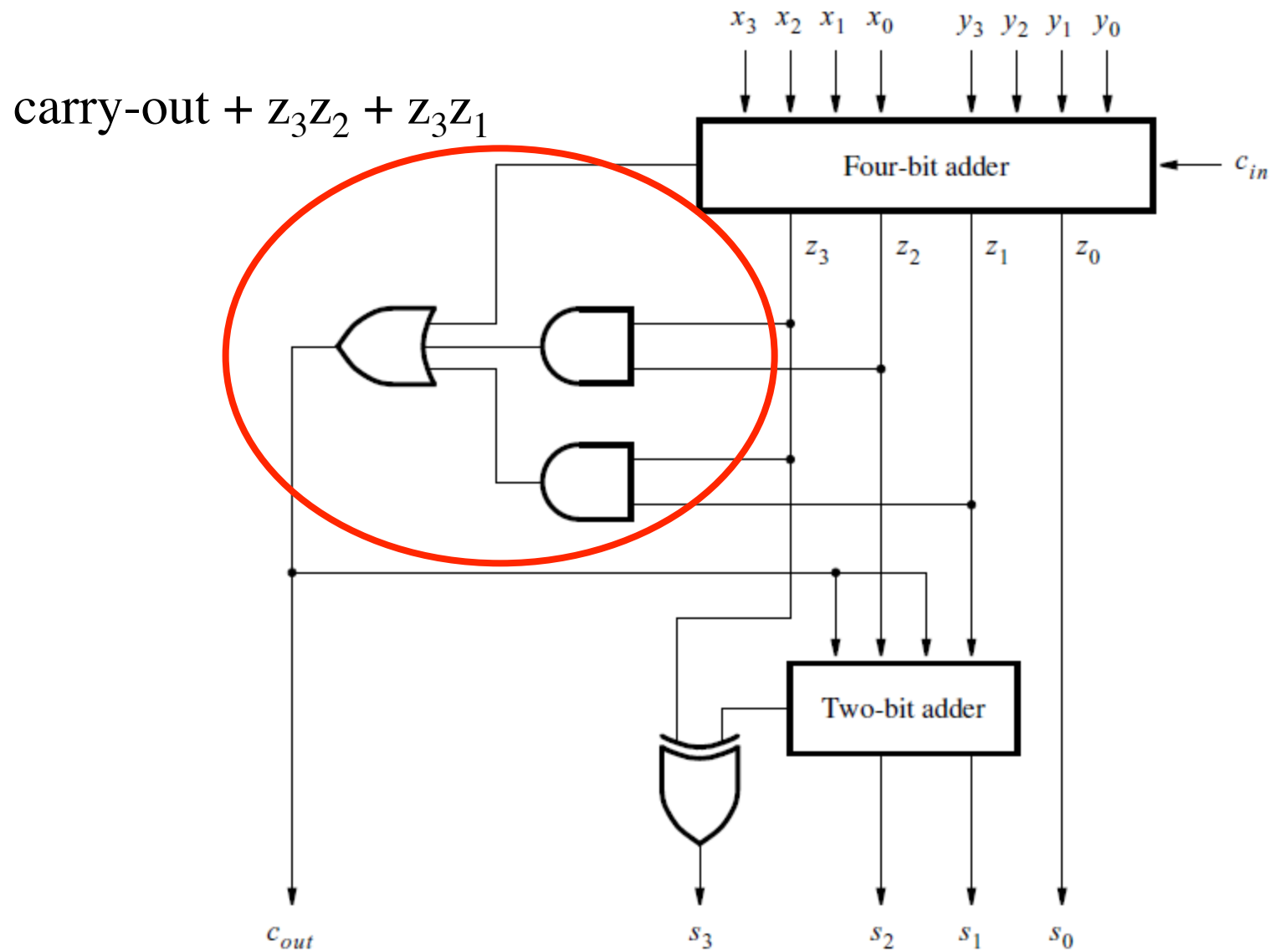


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

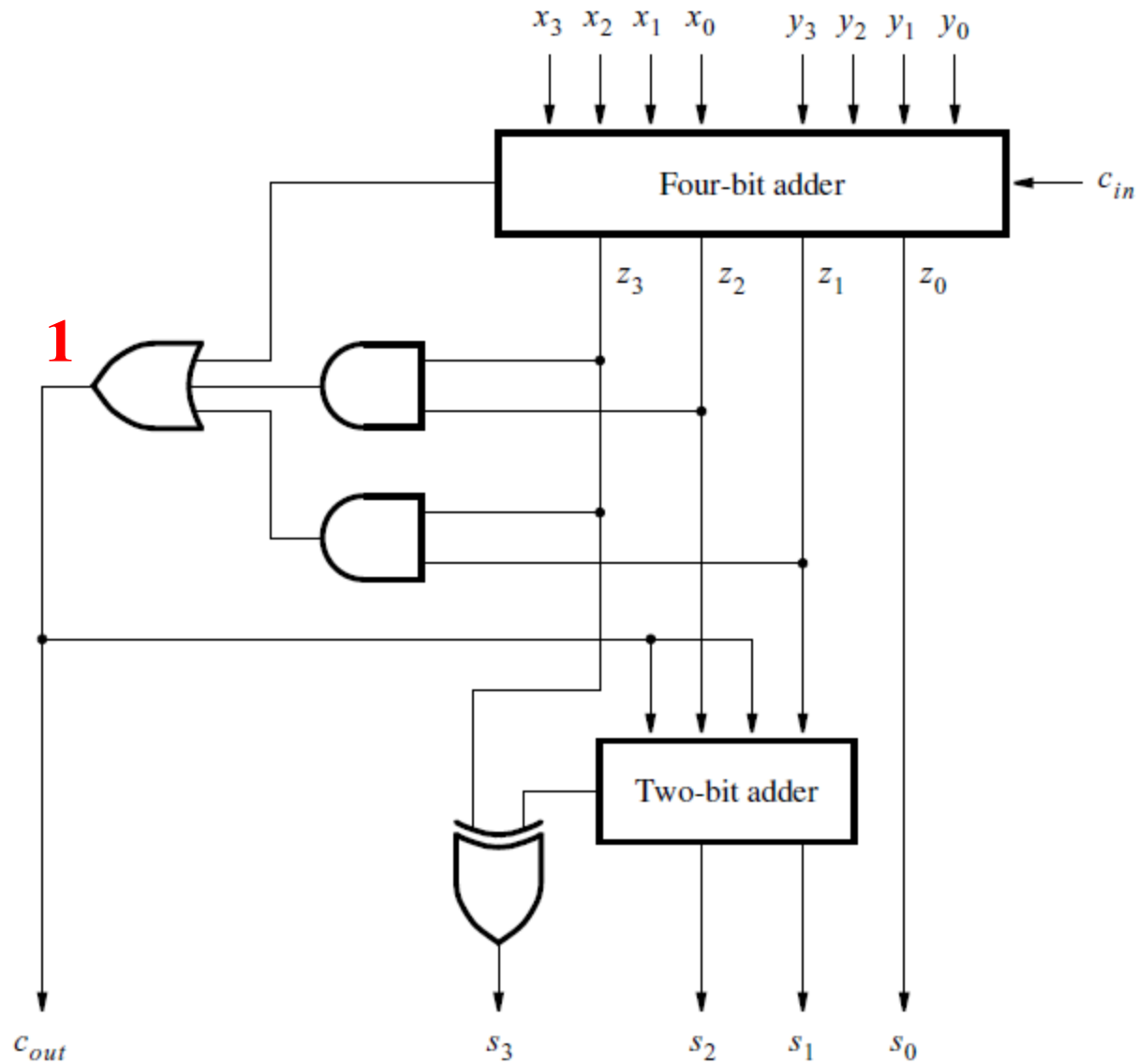


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

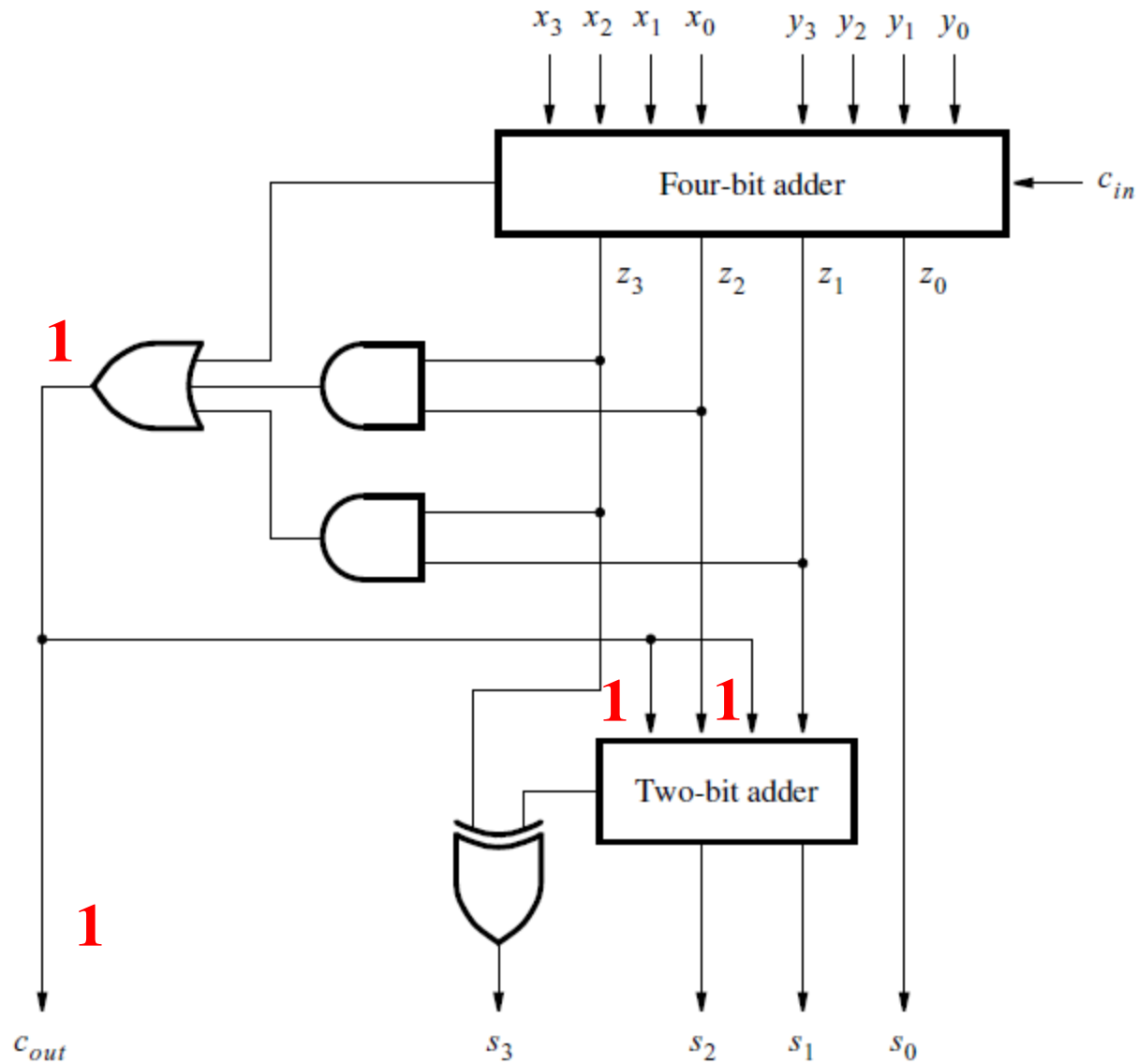


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

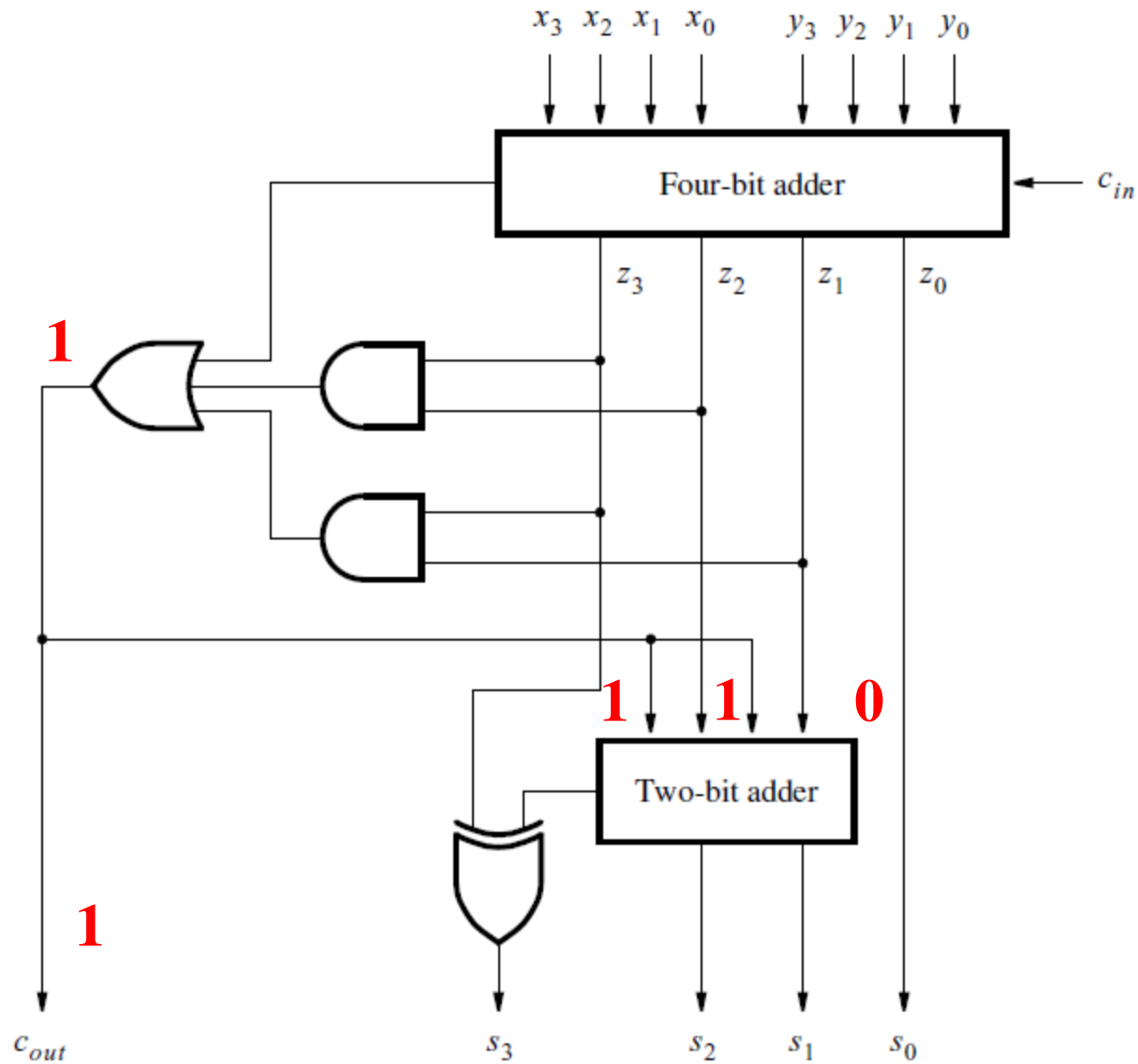

[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

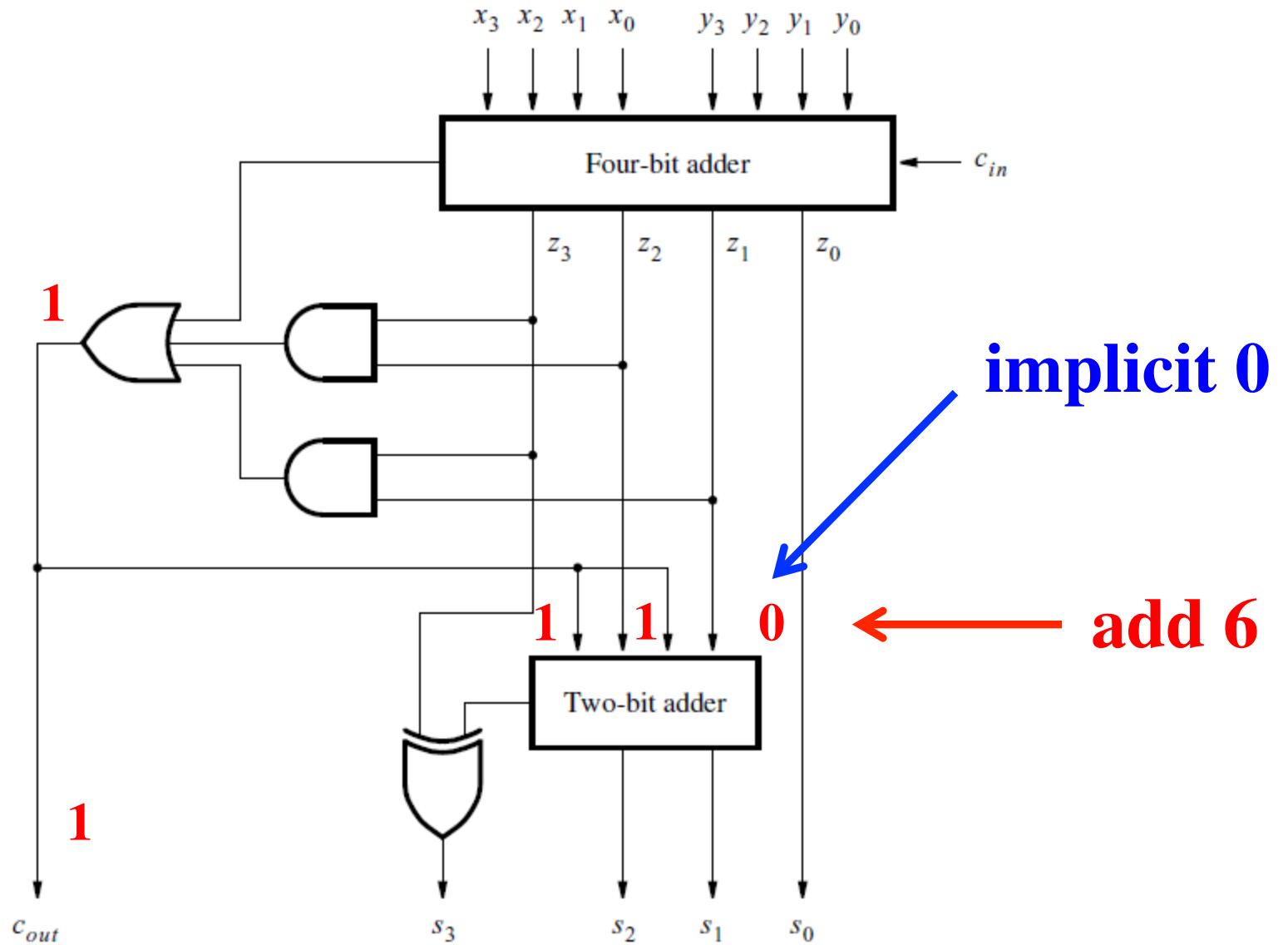

[Figure 3.41 in the textbook]

Questions?

THE END