



# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Registers

*CprE 281: Digital Logic*  
*Iowa State University, Ames, IA*  
*Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **The second midterm is next Friday.**
- **Homework 8 is due next Monday.**

# **Administrative Stuff**

- **Midterm Exam #2**
- **When: Friday October 28 @ 4pm.**
- **Where: This classroom**
- **What: Chapters 1, 2, 3, 4 and 5.1-5.8**
- **The exam will be open book and open notes (you can bring up to 3 pages of handwritten notes).**

# Midterm 2: Format

- The exam will be out of 130 points
- You need 95 points to get an A
- It will be great if you can score more than 100 points.
  - but you can't roll over your extra points ☹️

# Midterm 2: Topics

- **Binary Numbers and Hexadecimal Numbers**
- **1's complement and 2's complement representation**
- **Addition and subtraction of binary numbers**
- **Circuits for adders and fast adders**
  
- **Single and Double precision IEEE floating point formats**
- **Converting a real number to the IEEE format**
- **Converting a floating point number to base 10**
  
- **Multiplexers (circuits and function)**
- **Synthesis of logic functions using multiplexers**
- **Shannon's Expansion Theorem**


# Midterm 2: Topics

- **Decoders (circuits and function)**
- **Demultiplexers**
- **Encoders (binary and priority)**
- **Code Converters**
- **K-maps for 2, 3, and 4 variables**
  
- **Synthesis of logic circuits using adders, multiplexers, encoders, decoders, and basic logic gates**
- **Synthesis of logic circuits given constraints on the available building blocks that you can use**
  
- **Latches (circuits, behavior, timing diagrams)**
- **Flip-Flops (circuits, behavior, timing diagrams)**
- **Registers and Register Files**


# **Review of Flip-Flops**




# A simple memory element with NOT Gates

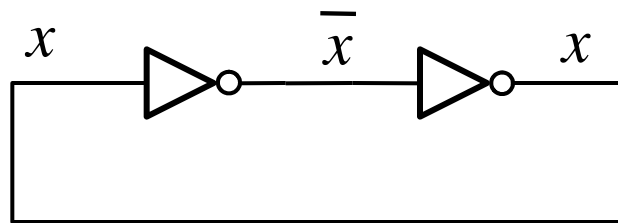
 
# A simple memory element with NAND Gates




# A simple memory element with NOR Gates

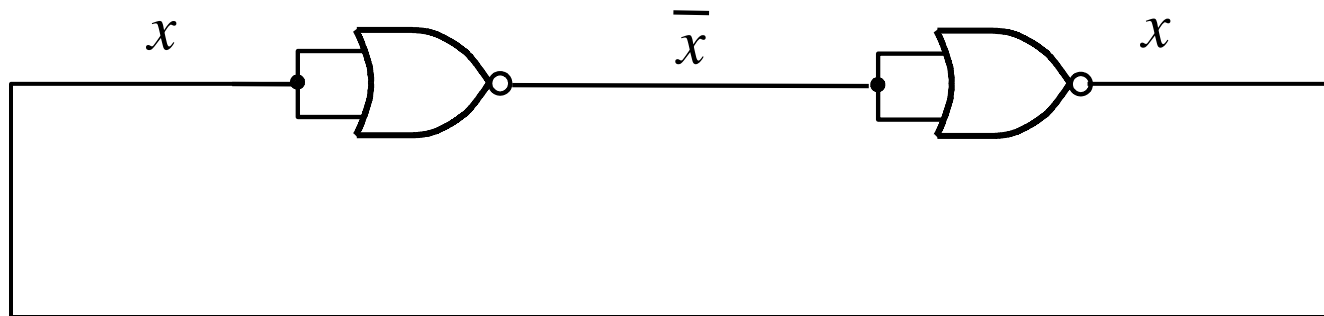


# Basic Latch


# A simple memory element with NOR Gates

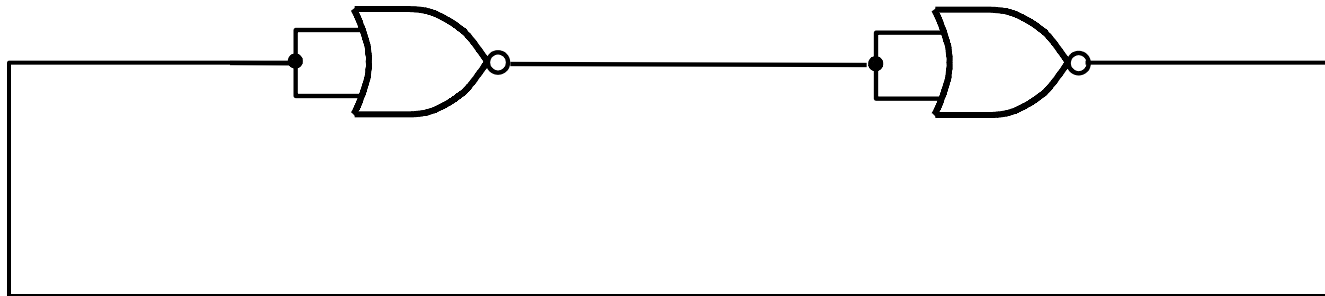


# A simple memory element with NOR Gates

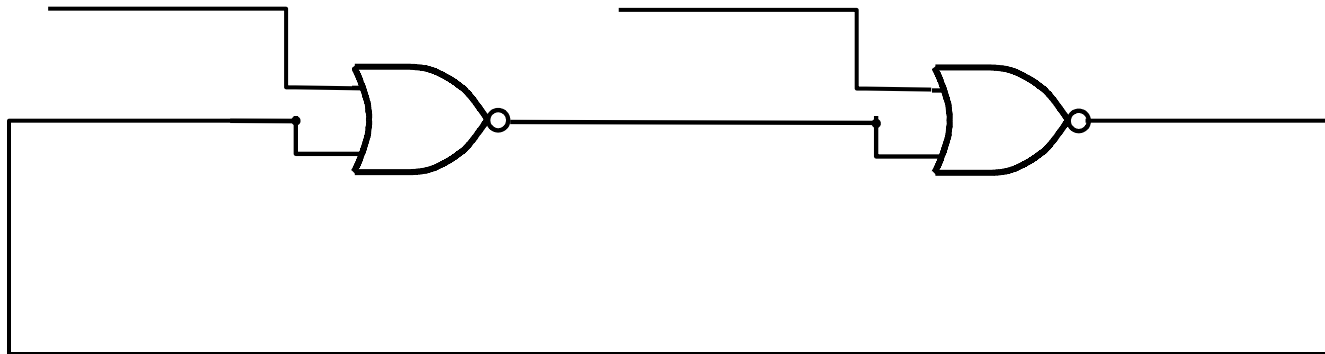

# A simple memory element with NOR Gates

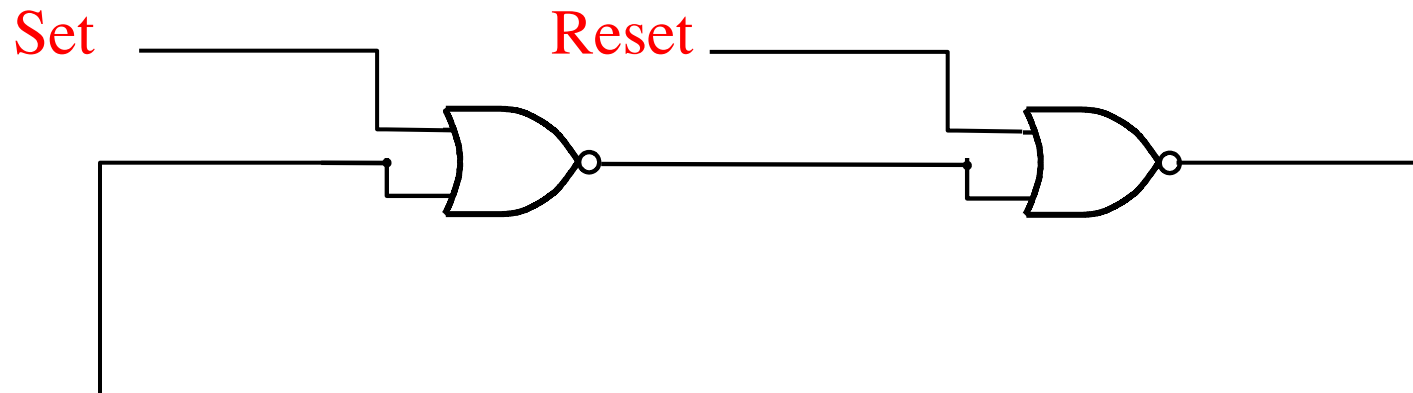



# A memory element with NOR gates

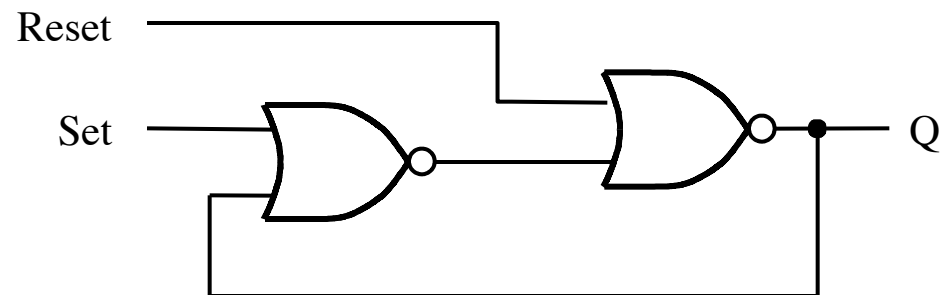

[ Figure 5.3 from the textbook ]




# Two Different Ways to Draw the Same Circuit

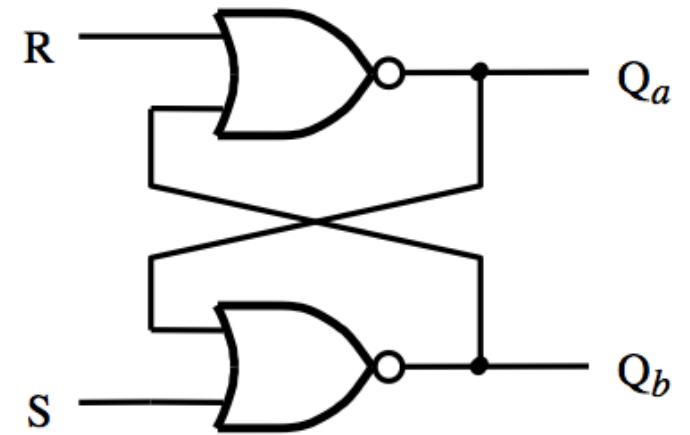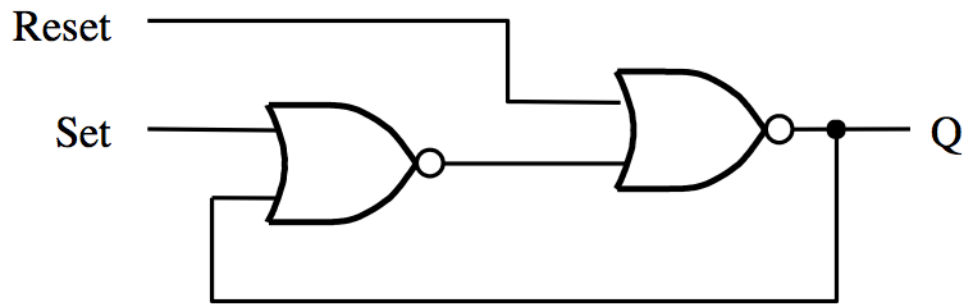

[ Figure 5.3 & 5.4 from the textbook ]

# SR Latch: Circuit and Truth Table

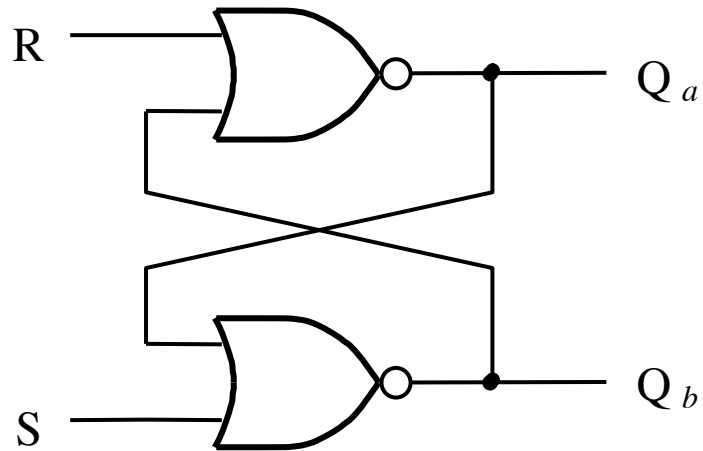


(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	<b>(Undesirable)</b>

(b) Truth table

[ Figure 5.4a,b from the textbook ]

## NOR Gate

 


## NOR Gate Truth table

$x_1$	$x_2$	f
0	0	1
0	1	0
1	0	0
1	1	0


# **Gated SR Latch**

# Circuit Diagram for the Gated SR Latch

 


[ Figure 5.5a from the textbook ]

# Circuit Diagram for the Gated SR Latch

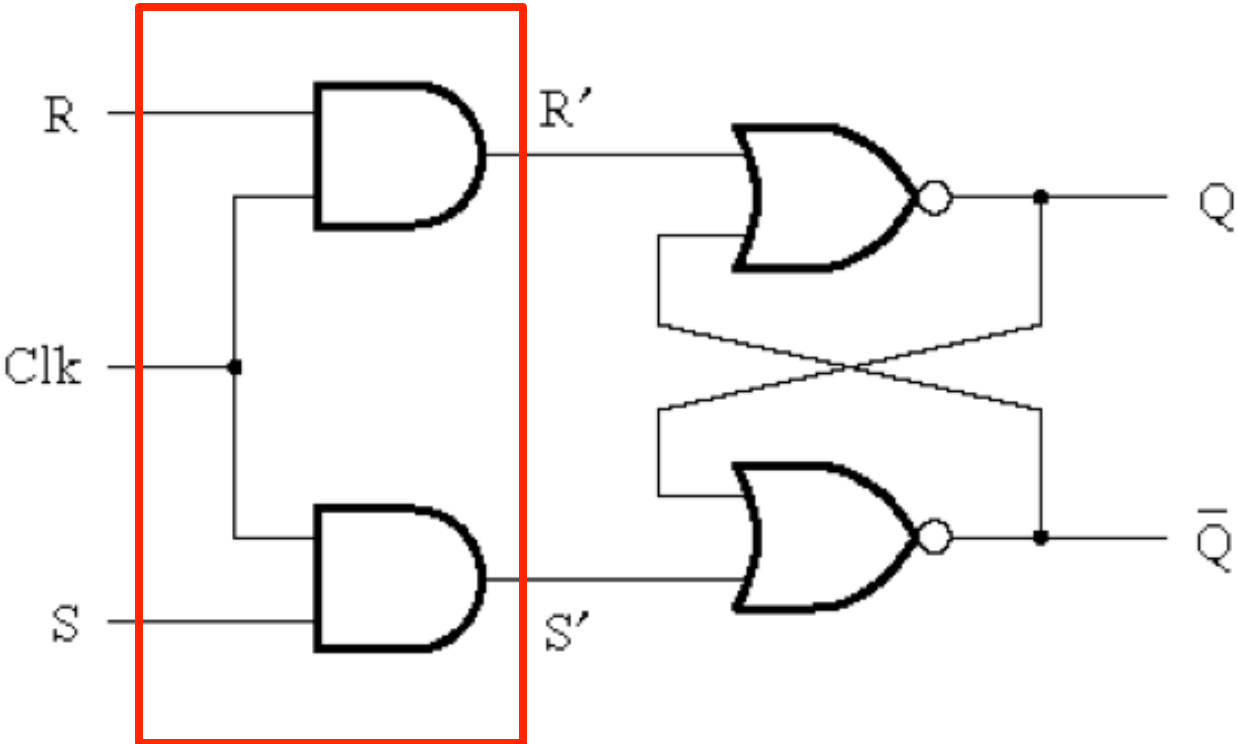


This is the “gate”  
of the gated latch

# Circuit Diagram for the Gated SR Latch

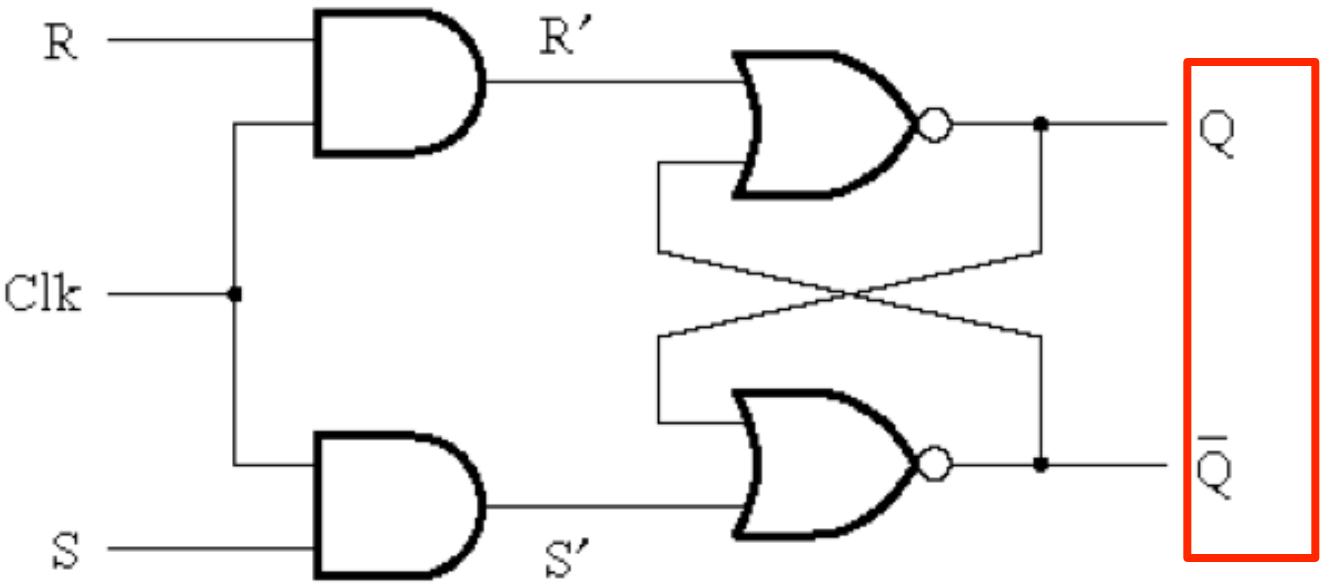


Notice that these are complements of each other
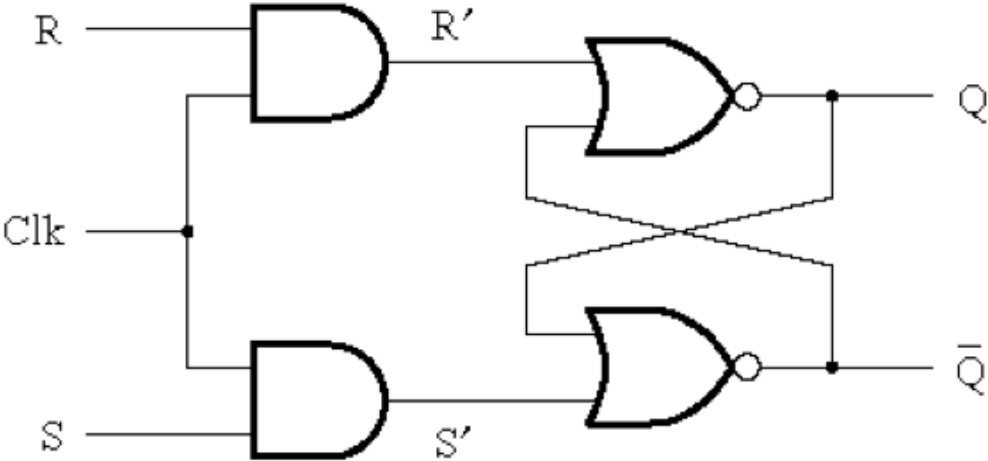
# Gated SR Latch: Circuit Diagram, Characteristic Table, and Graphical Symbol




Clk	S	R	$Q(t + 1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x (Undesirable)

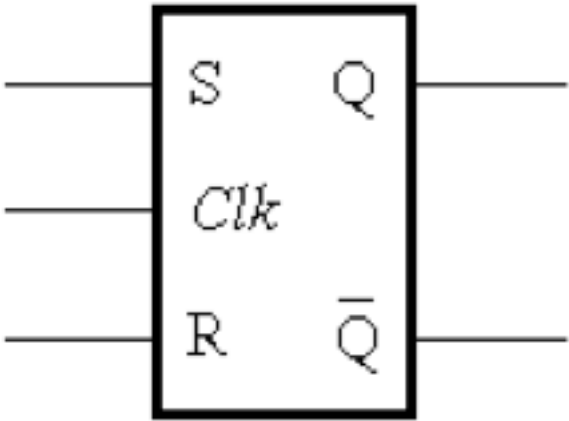

[ Figure 5.5 from the textbook ]


# Gated SR latch with NAND gates

 

[ Figure 5.6 from the textbook ]




# Gated SR latch with NAND gates

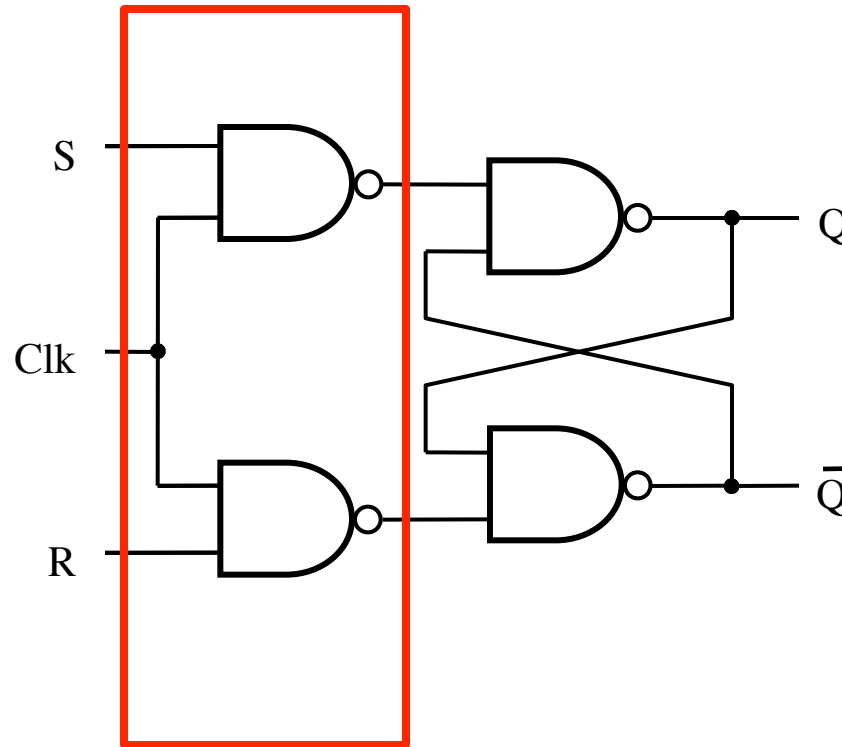


In this case the “gate” is constructed using NAND gates! Not AND gates.

# Gated SR latch with NAND gates

 


Also, notice that the positions of S and R are now swapped.

# Gated SR latch with NAND gates

 


Finally, notice that when  $\text{Clk}=1$  this turns into the basic latch with NAND gates, i.e., the  $\bar{S}\bar{R}$  Latch.


## Gated SR latch with NOR gates

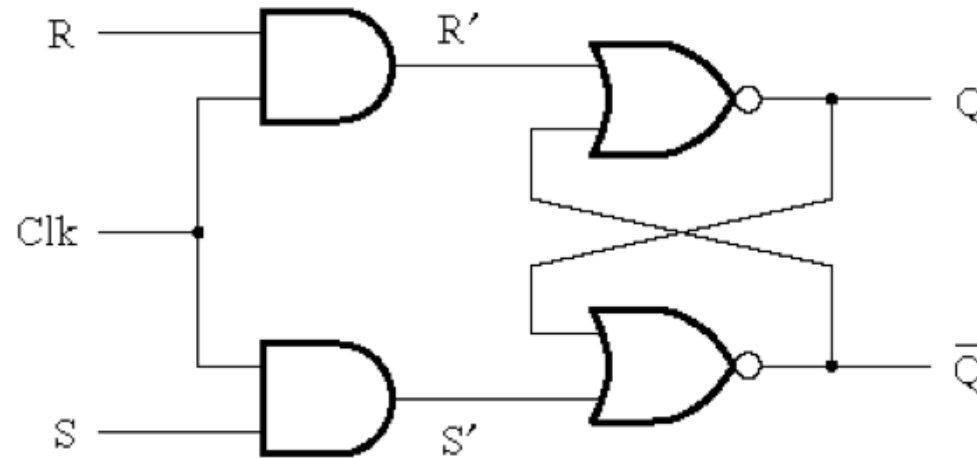


## Gated SR latch with NAND gates

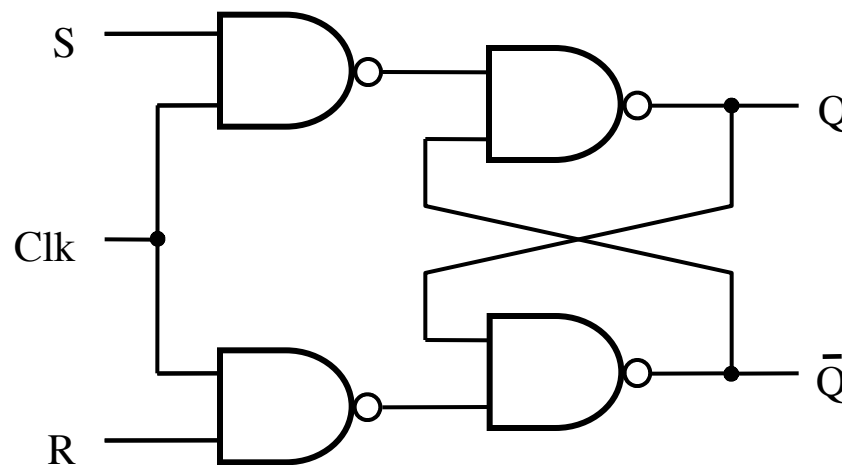

## Gated SR latch with NOR gates

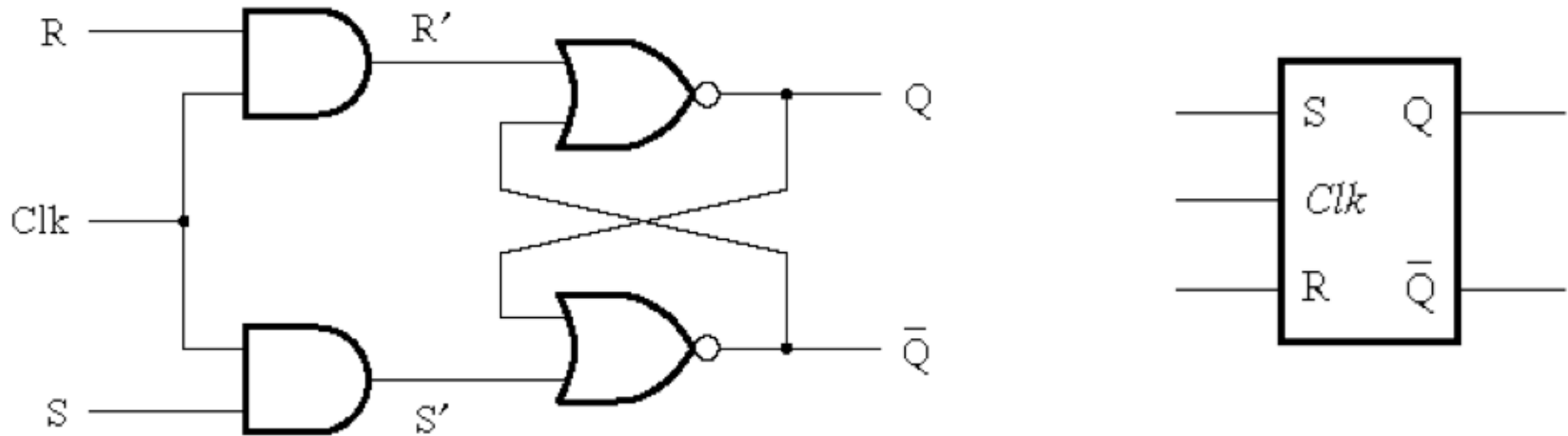


## Gated SR latch with NAND gates

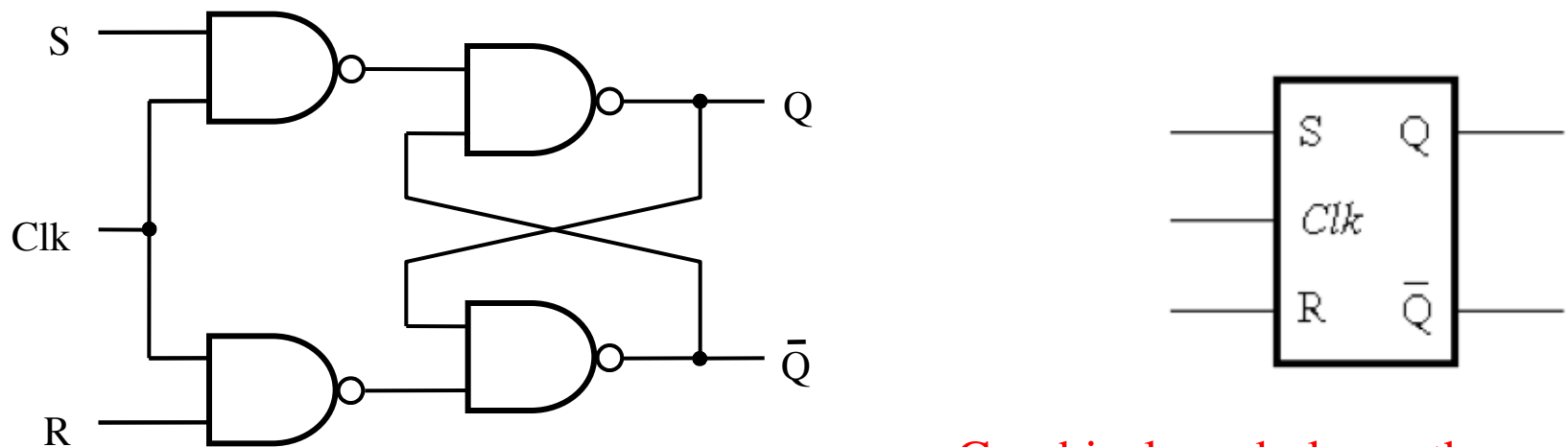


Graphical symbols are the same

# Gated SR latch with NOR gates

 

Clk	S	R	Q(t + 1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)

# Gated SR latch with NAND gates

 


Clk	S	R	Q(t + 1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)

Characteristic tables are the same

# **Gated D Latch**


# Circuit Diagram for the Gated D Latch

 


[ Figure 5.7a from the textbook ]



# Gated D Latch: Alternative Design

 
 
# Gated D Latch: Circuit Diagram, Characteristic Table, and Graphical Symbol




Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

Note that it is now impossible to have  $S=R=1$ .


When  $Clk=1$  the output follows the D input.

When  $Clk=0$  the output cannot be changed.

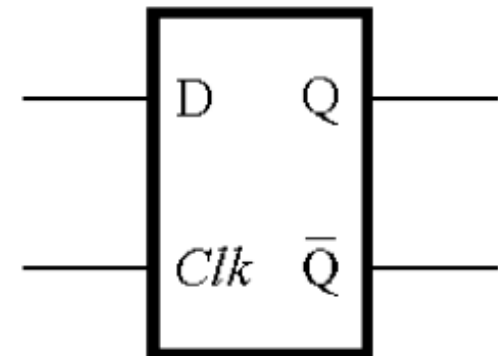

[ Figure 5.7a,b from the textbook ]

# Setup and hold times for Gated D latch

 


Setup time ( $t_{su}$ ) – the minimum time that the D signal must be stable prior to the the negative edge of the Clock signal

Hold time ( $t_h$ ) – the minimum time that the D signal must remain stable after the the negative edge of the Clock signal


# **Master-Slave D Flip-Flop**

# Constructing a Master-Slave D Flip-Flop From Two D Latches

Master

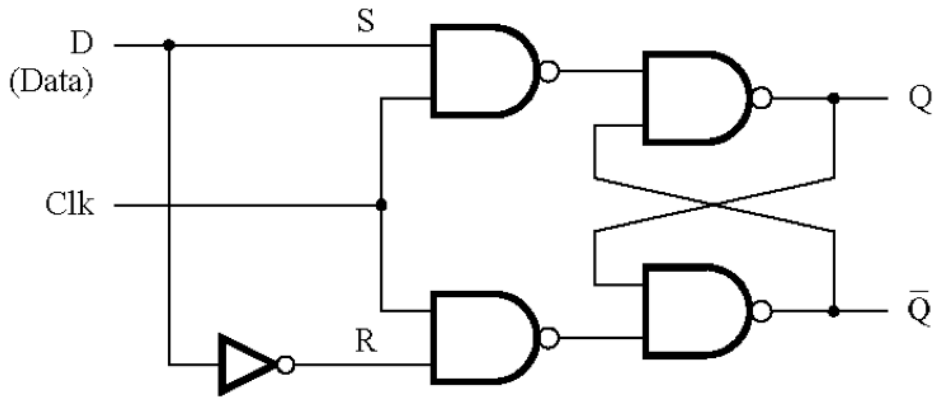


Slave

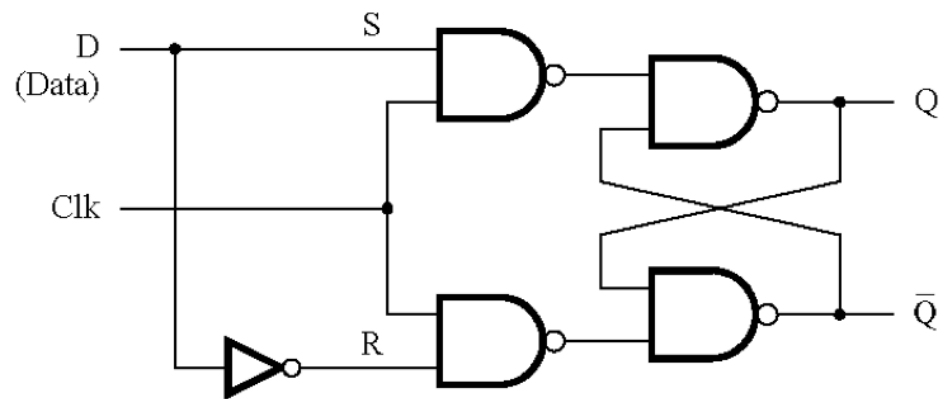

# Constructing a Master-Slave D Flip-Flop From Two D Latches

Master


Slave

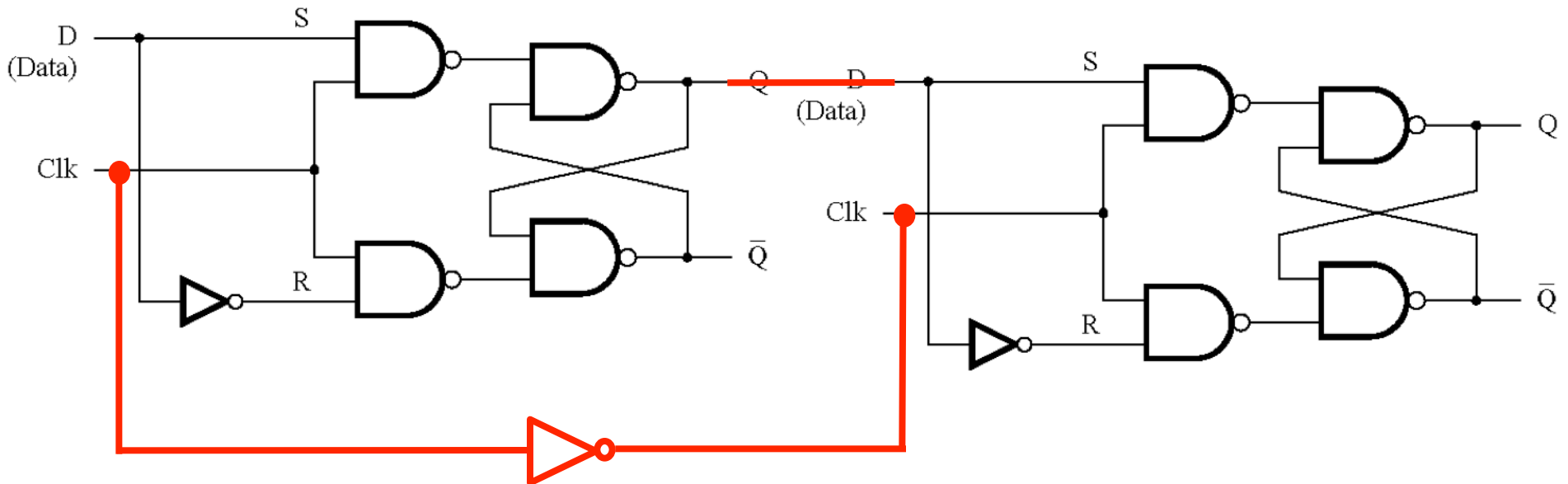


# Constructing a Master-Slave D Flip-Flop From Two D Latches

Master

Slave

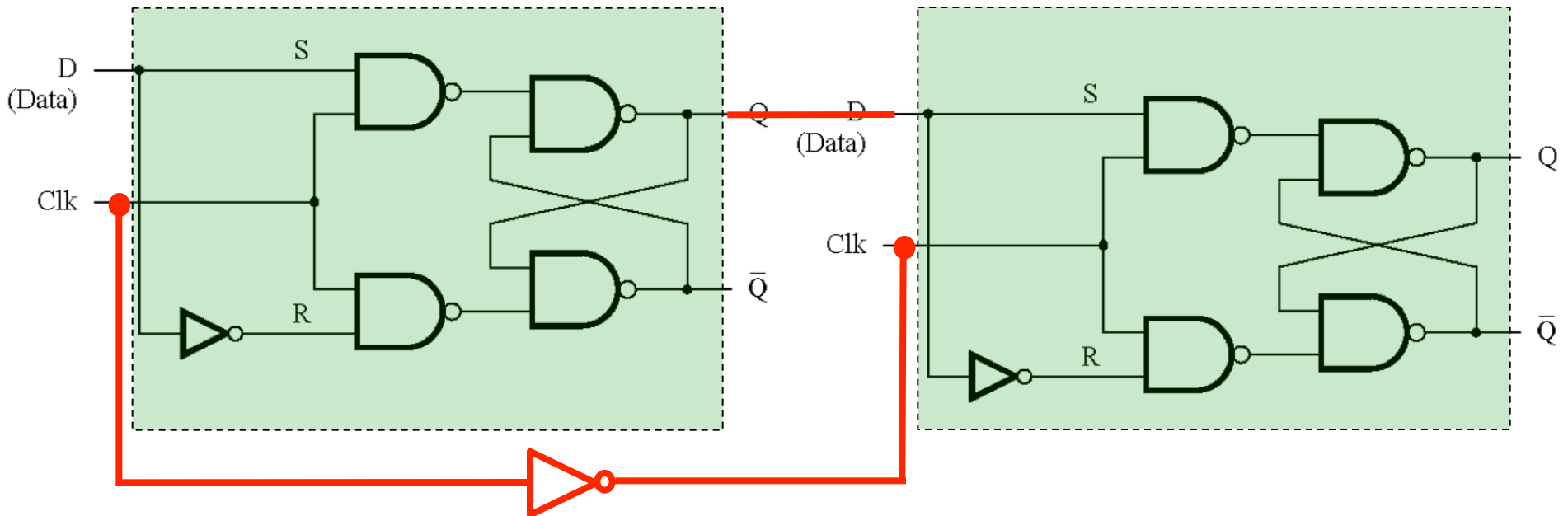

# Constructing a Master-Slave D Flip-Flop From Two D Latches

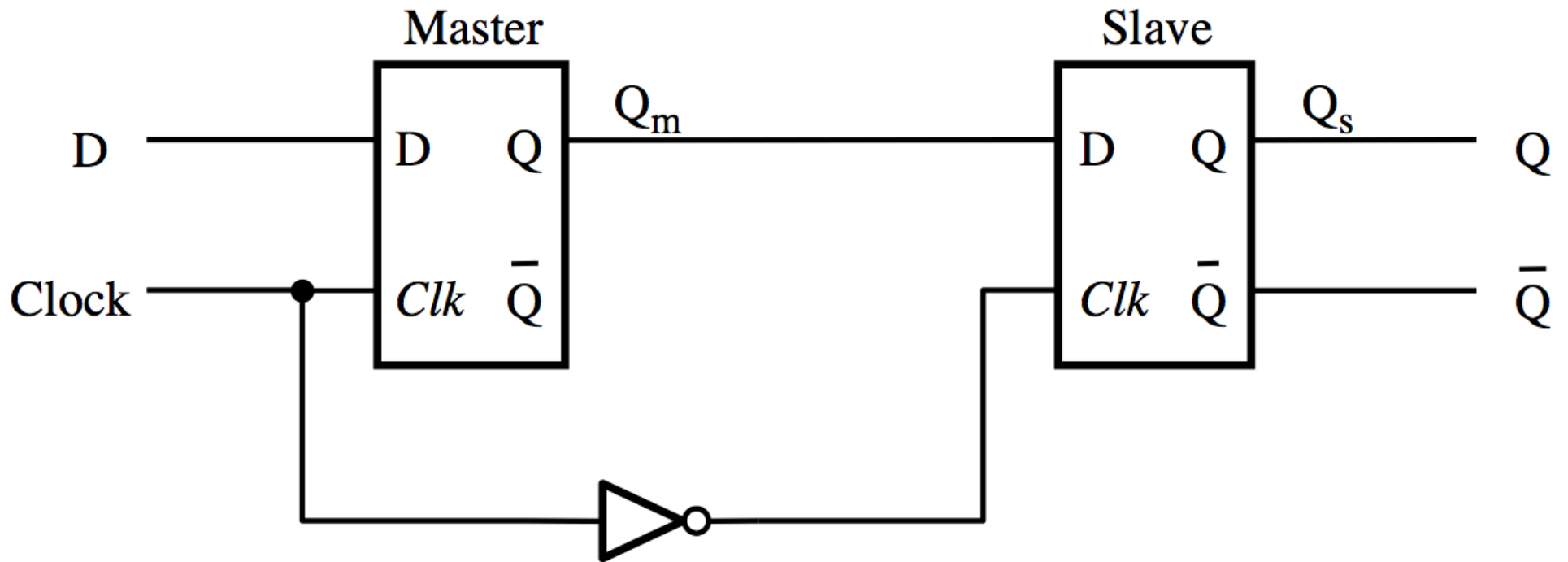


[ Figure 5.9a from the textbook ]




# Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

Master

 


Slave

 




# **Edge-Triggered D Flip-Flops**

# Master-Slave D Flip-Flop

 


(a) Circuit

 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



 
# Positive-Edge-Triggered Master-Slave D Flip-Flop



 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



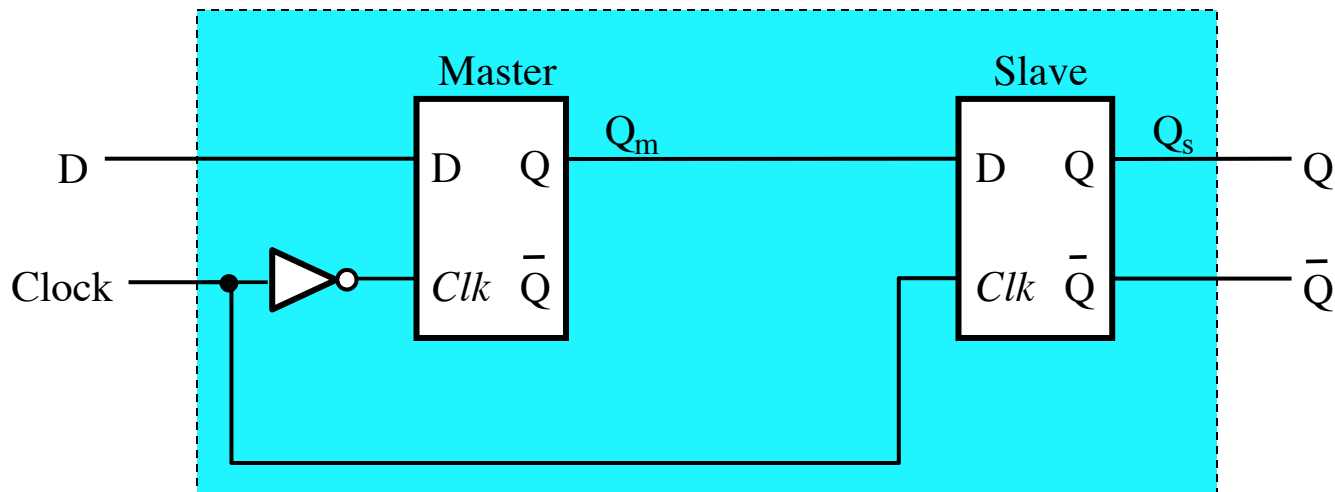
# Positive-Edge-Triggered Master-Slave D Flip-Flop


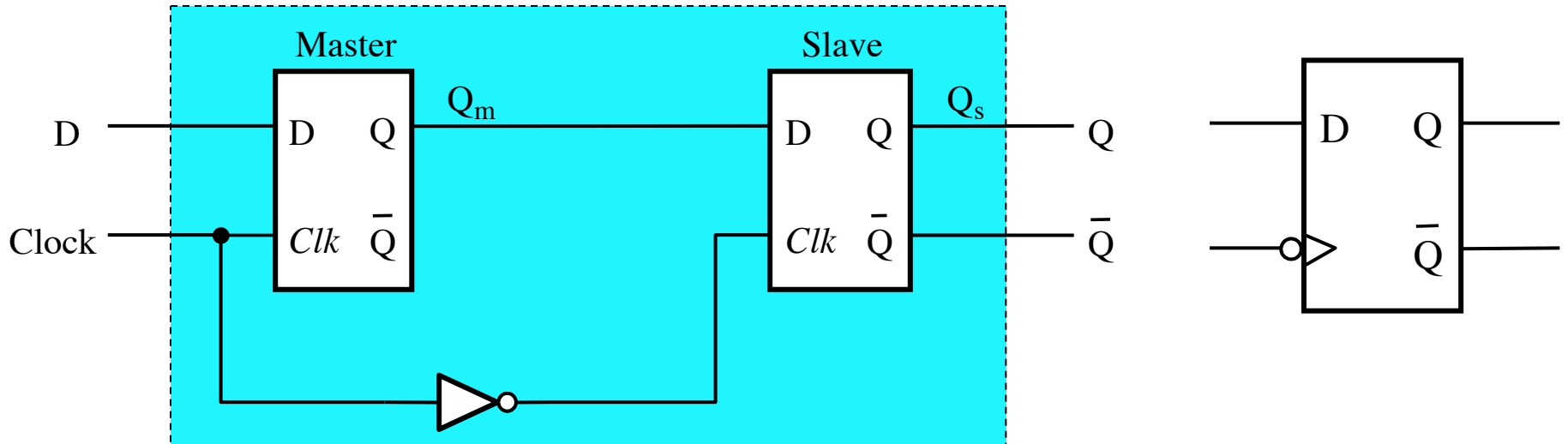
# Negative-Edge-Triggered Master-Slave D Flip-Flop



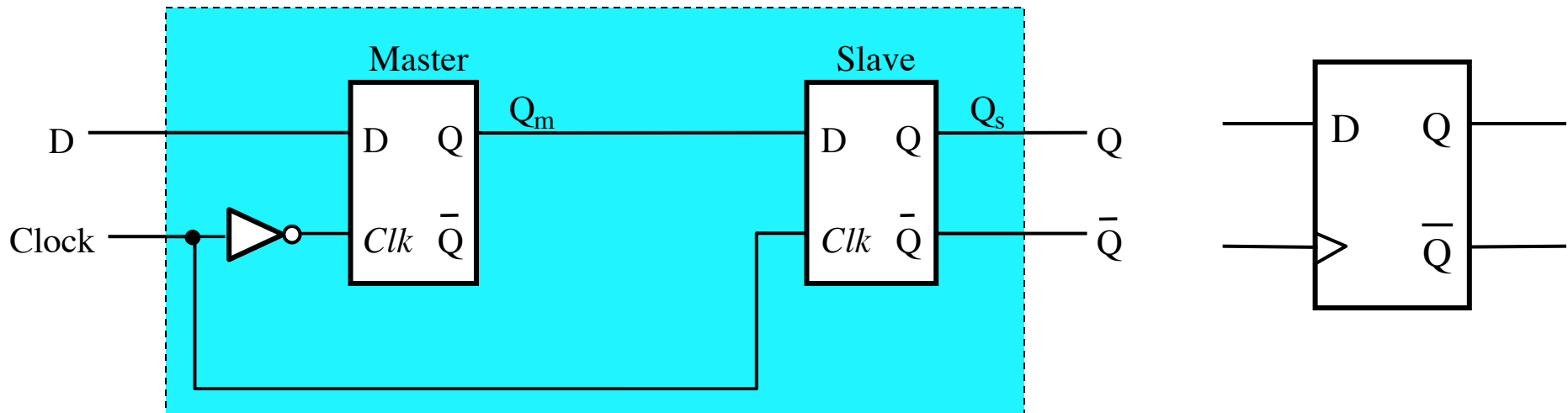
# Positive-Edge-Triggered Master-Slave D Flip-Flop



# T Flip-Flop




# T Flip-Flop

 

[ Figure 5.15a from the textbook ]


# T Flip-Flop

 

Positive-edge-triggered  
D Flip-Flop

[ Figure 5.15a from the textbook ]


# T Flip-Flop

 


What is this?

[ Figure 5.15a from the textbook ]


**What is this?**

 

# What is this?

 


# T Flip-Flop

 

# What is this?




**+**  
Clock

 

**= ?**


# T Flip-Flop

 




# T Flip-Flop
 
## (circuit, truth table and graphical symbol)



T	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q(t)}$

 

[ Figure 5.15a-c from the textbook ]

# **T Flip-Flop (How it Works)**


**If  $T=0$  then it stays in its current state**

**If  $T=1$  then it reverses its current state**

**In other words the circuit “toggles” its state when  $T=1$ . This is why it is called T flip-flop.**

# **JK Flip-Flop**


# JK Flip-Flop

 

$$D = \overline{JQ} + \overline{KQ}$$

[ Figure 5.16a from the textbook ]


# JK Flip-Flop

 

(a) Circuit

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

 

(c) Graphical symbol

# **JK Flip-Flop (How it Works)**

**A versatile circuit that can be used both as a SR flip-flop and as a T flip flop**

**If  $J=0$  and  $S=0$  it stays in the same state**

**Just like SR It can be set and reset**

**$J=S$  and  $K=R$**

**If  $J=K=1$  then it behaves as a T flip-flop**

# Registers


# **Register (Definition)**

**An n-bit structure consisting of flip-flops**




# **Parallel-Access Register**

# 1-Bit Parallel-Access Register

 


# 1-Bit Parallel-Access Register

 

**The 2-to-1 multiplexer is used to select whether to load a new value into the D flip-flop or to retain the old value.**

**The output of this circuit is the Q output of the flip-flop.**


# 1-Bit Parallel-Access Register

 


**If Load = 0, then retain the old value.**

**If Load = 1, then load the new value from In.**


# 2-Bit Parallel-Access Register

 

# 2-Bit Parallel-Access Register

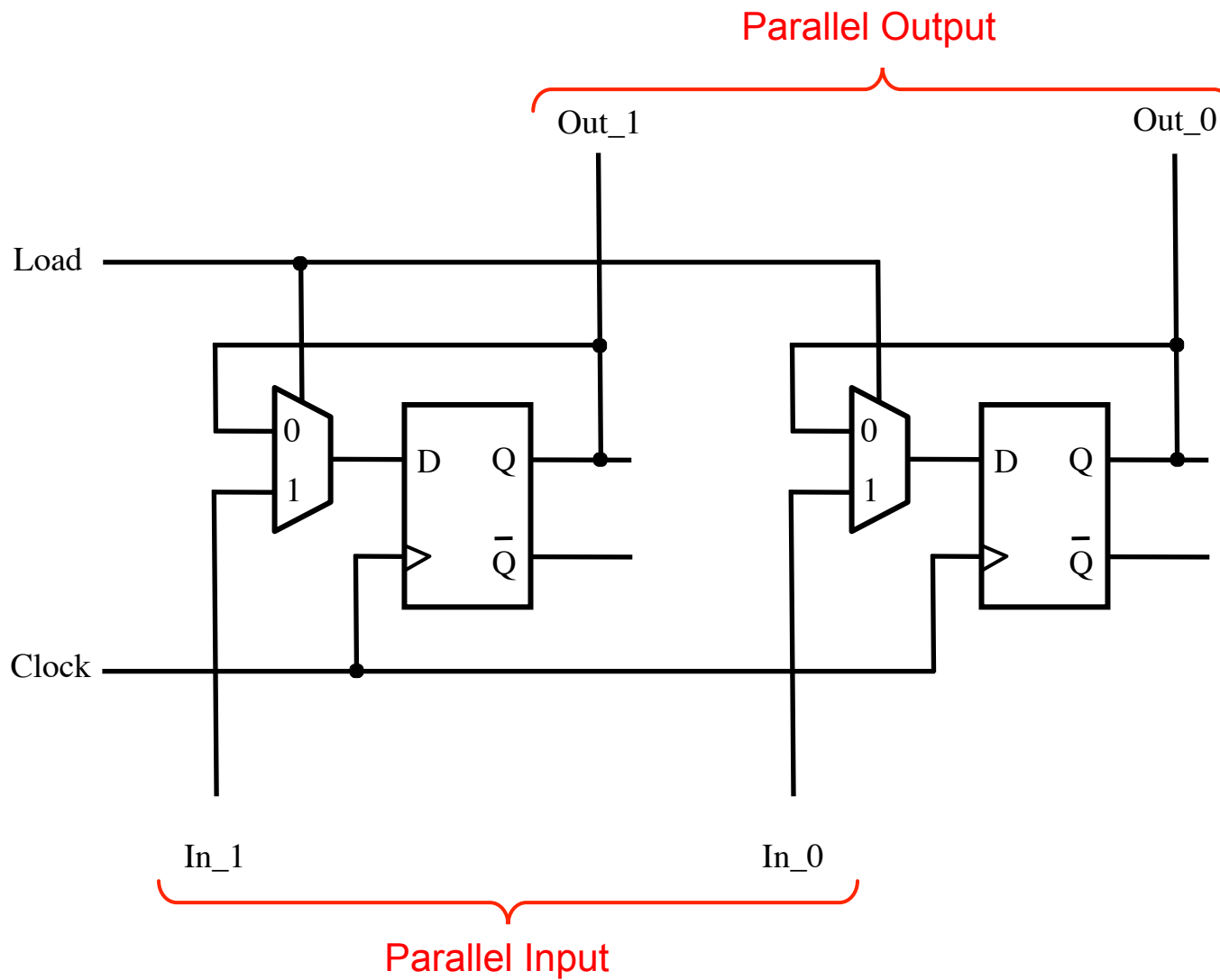


# 3-Bit Parallel-Access Register

 


Notice that all flip-flops are on the same clock cycle.

# 3-Bit Parallel-Access Register

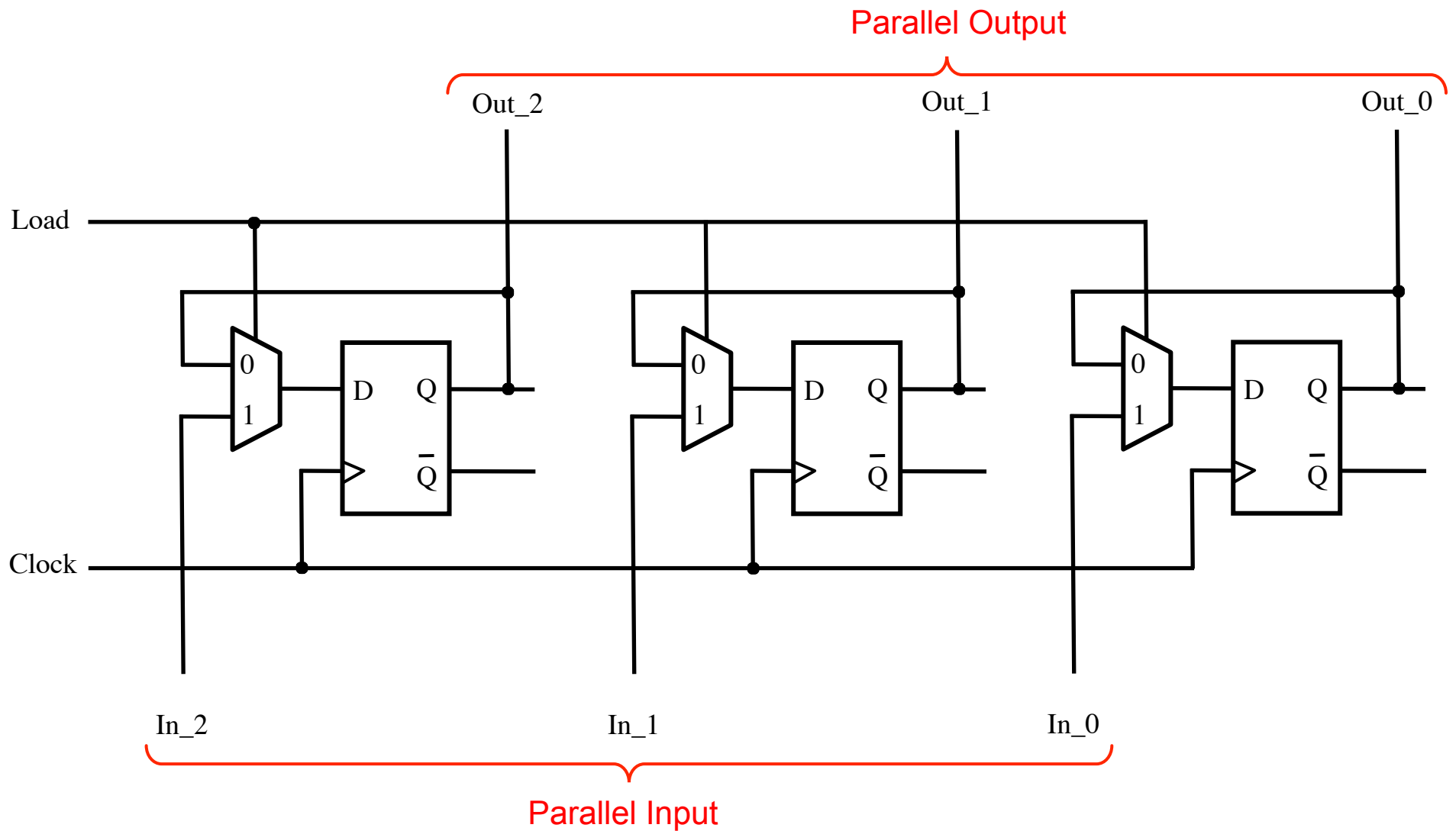




# 4-Bit Parallel-Access Register

 


# 4-Bit Parallel-Access Register

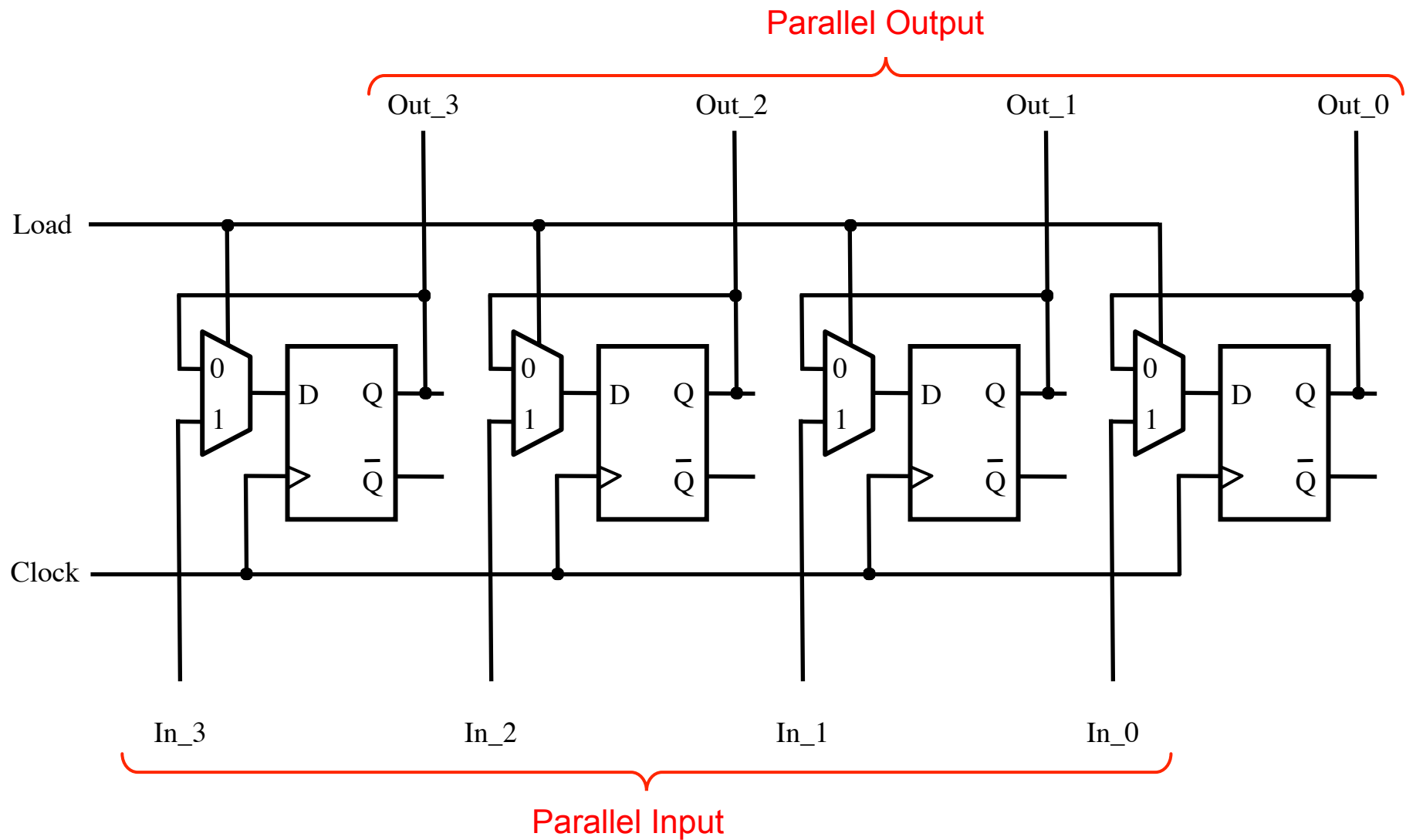


# Shift Register

# A simple shift register


 


# A simple shift register


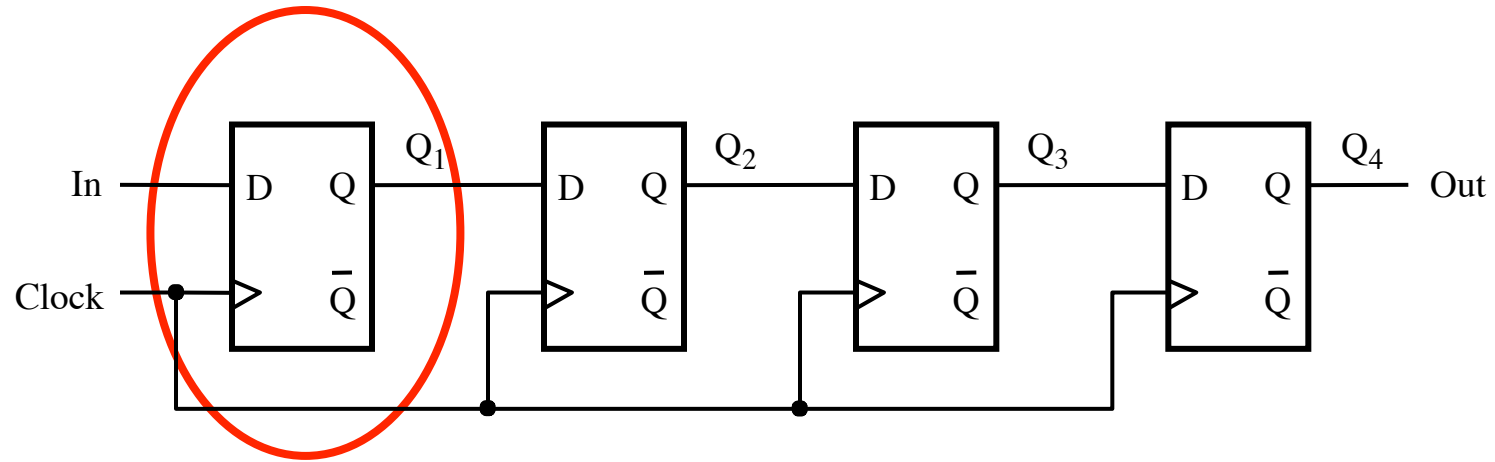


Positive-edge-triggered  
D Flip-Flop


# A simple shift register

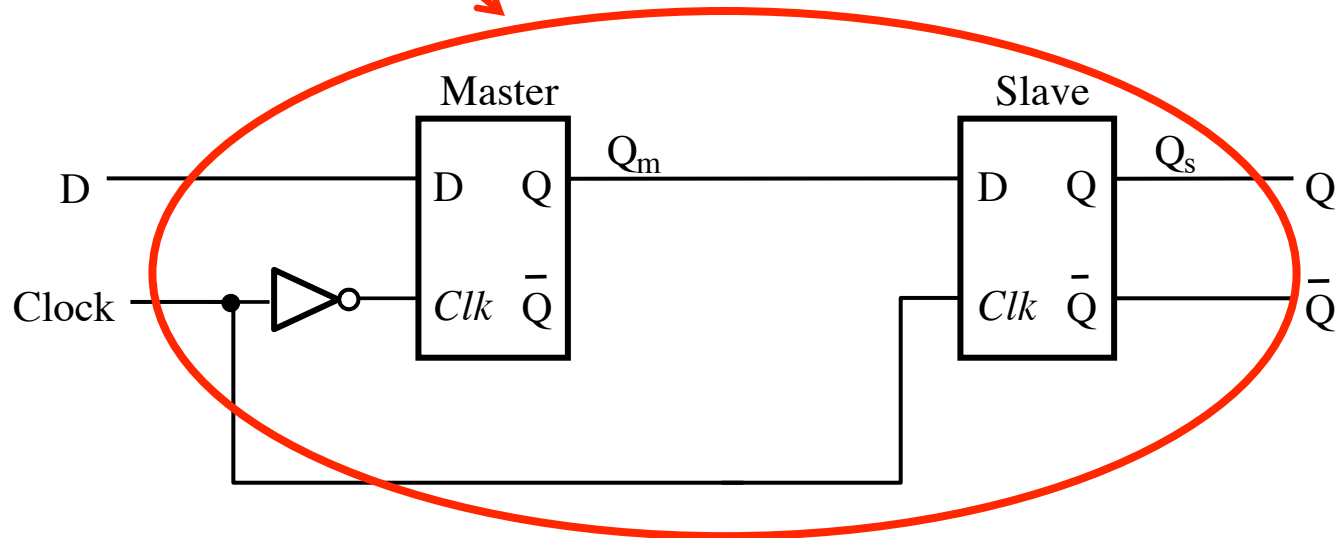 

# A simple shift register

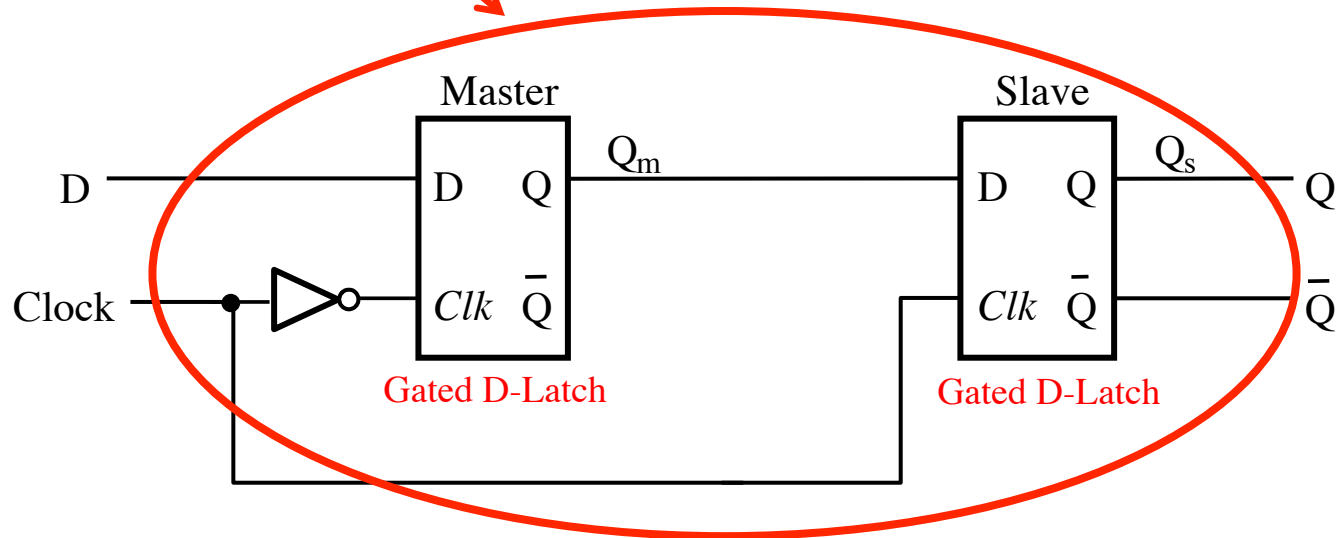
 


# A simple shift register


 






# A simple shift register

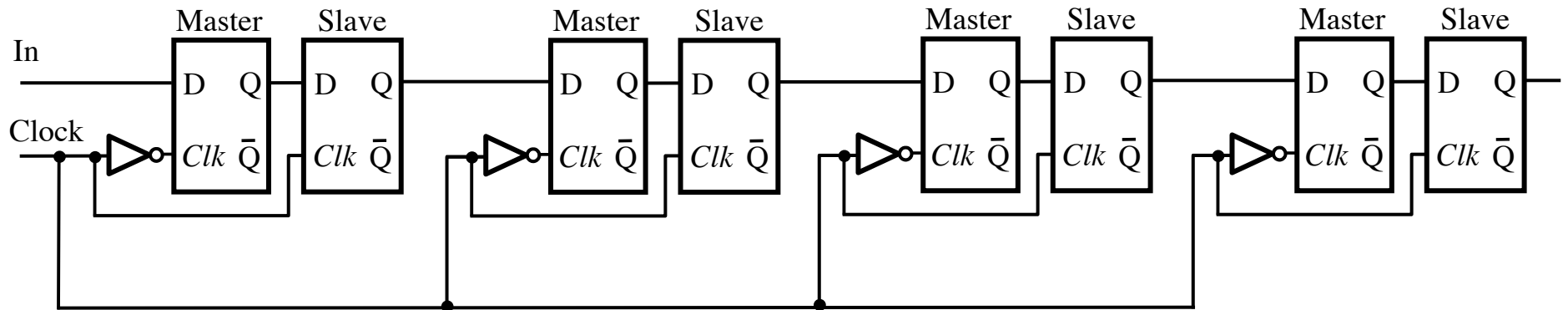 



# A simple shift register

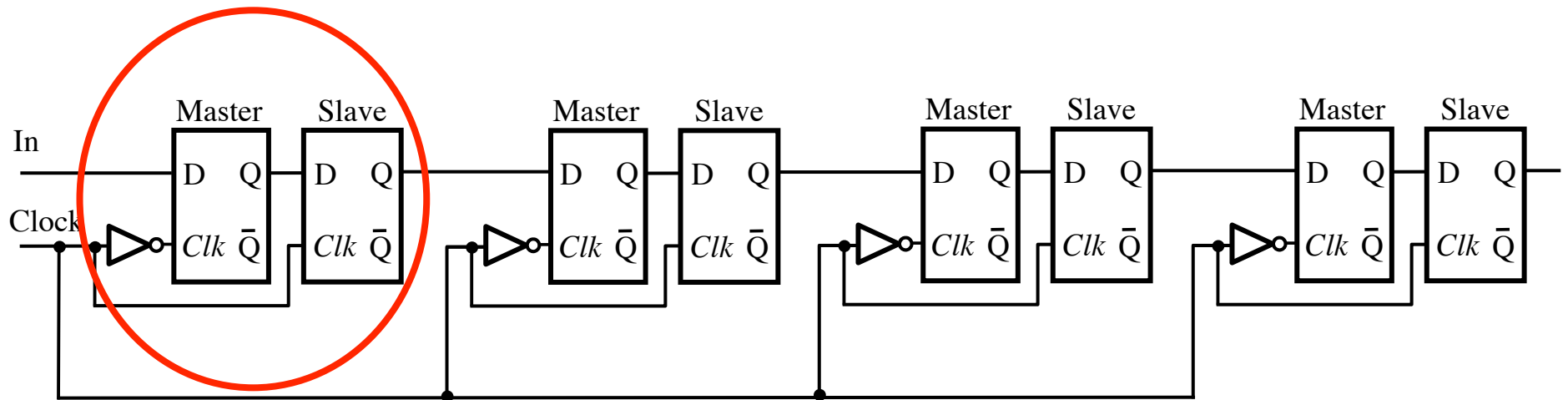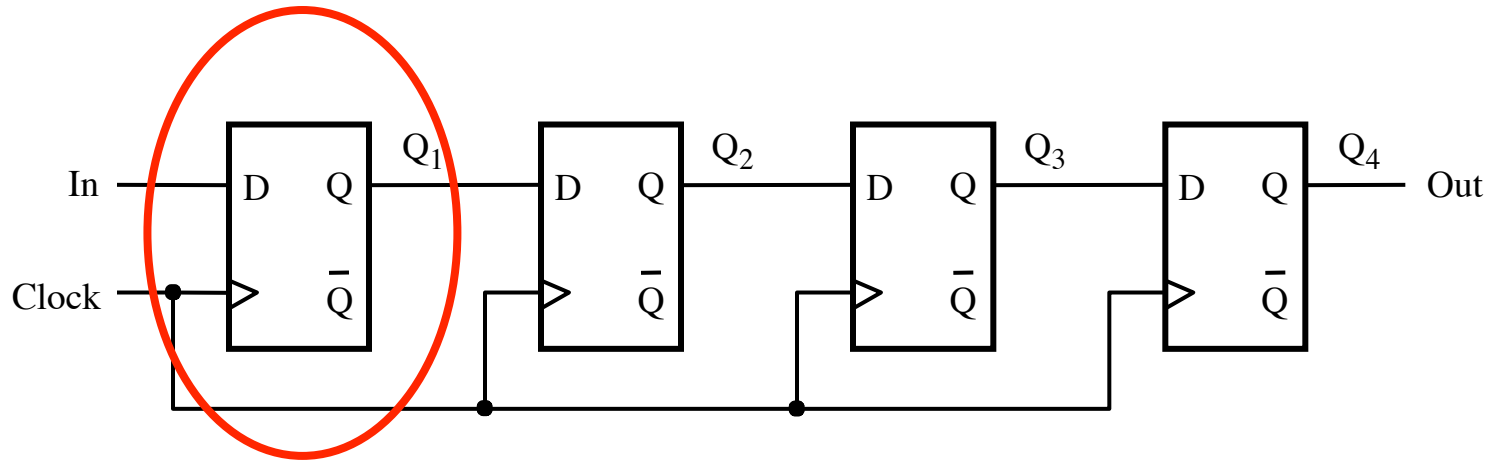



# A simple shift register

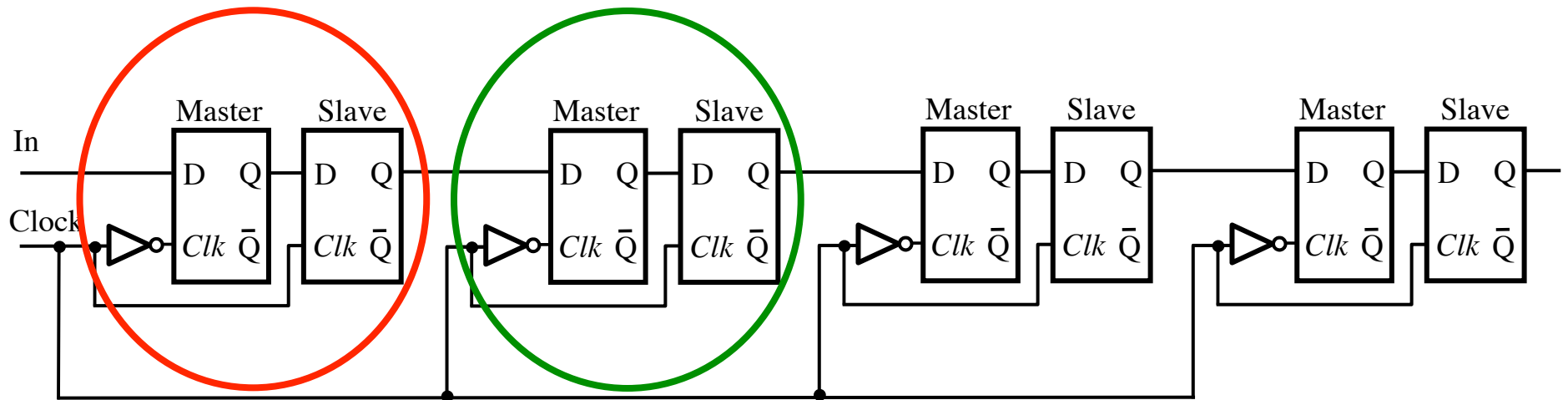 


# A simple shift register

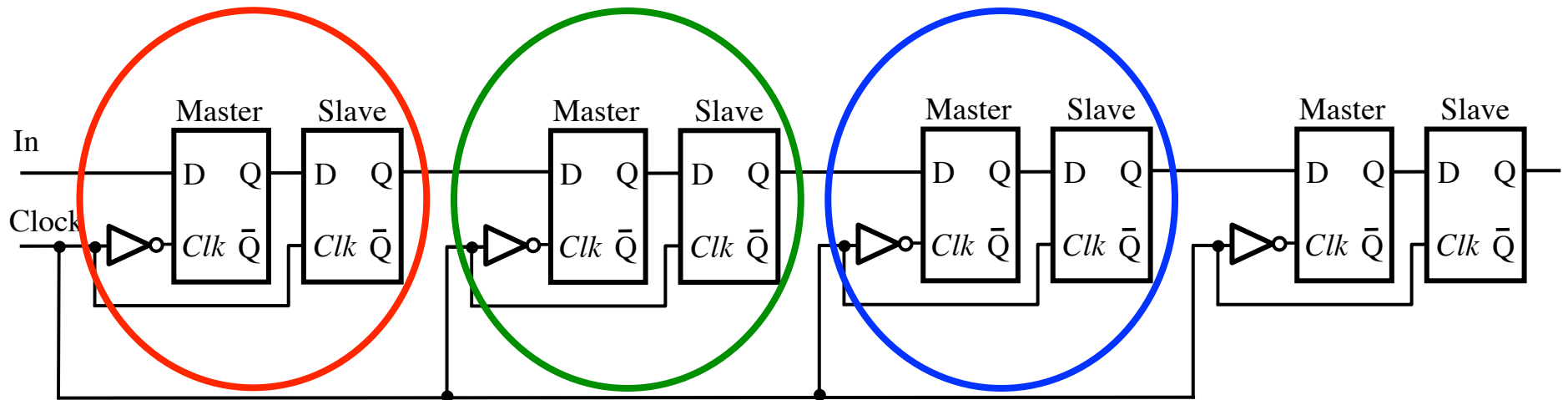 


# A simple shift register

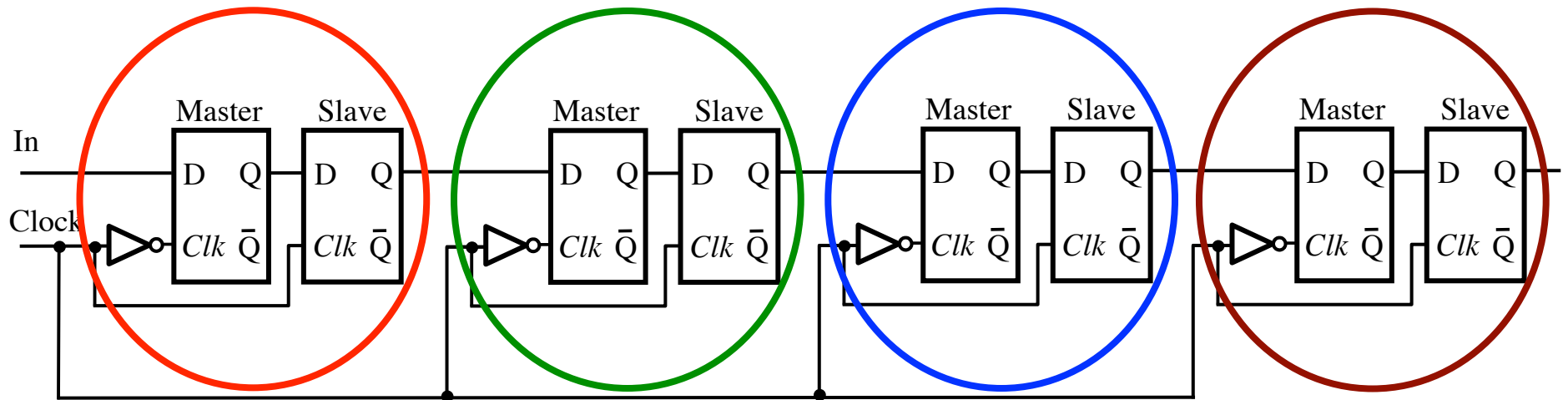 

# A simple shift register

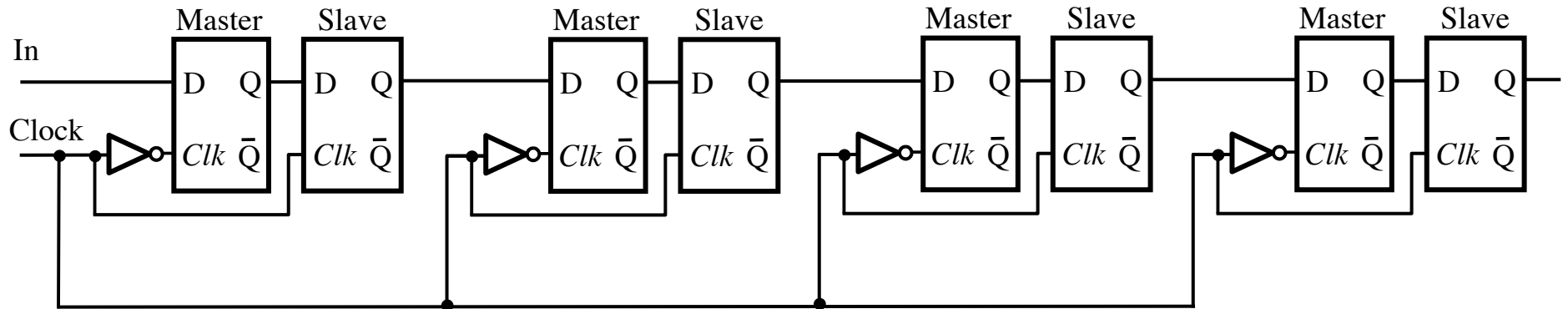

# A simple shift register

 

(a) Circuit

	In	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub> = Out
$t_0$	1	0	0	0	0
$t_1$	0	1	0	0	0
$t_2$	1	0	1	0	0
$t_3$	1	1	0	1	0
$t_4$	1	1	1	0	1
$t_5$	0	1	1	1	0
$t_6$	0	0	1	1	1
$t_7$	0	0	0	1	1


(b) A sample sequence

[ Figure 5.17 from the textbook ]

# **Parallel-Access Shift Register**




# Parallel-access shift register

 

[ Figure 5.18 from the textbook ]


# A shift register with parallel load and enable control inputs

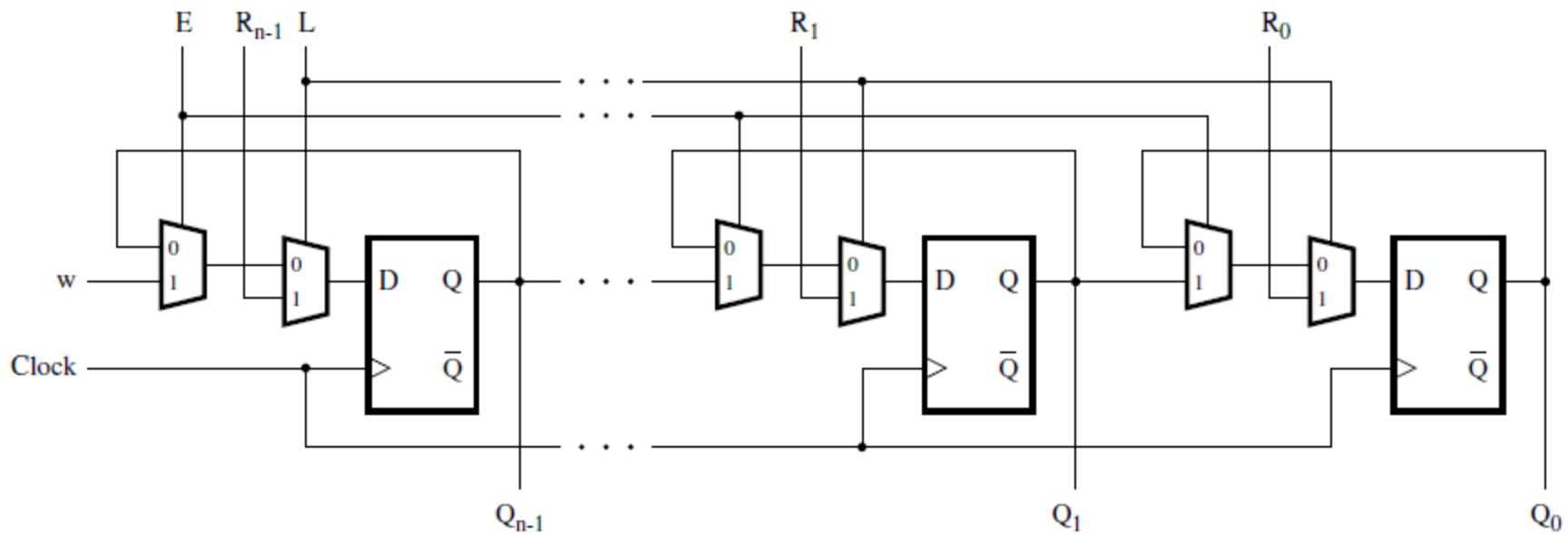


[ Figure 5.59 from the textbook ]


# Register File


# Register File

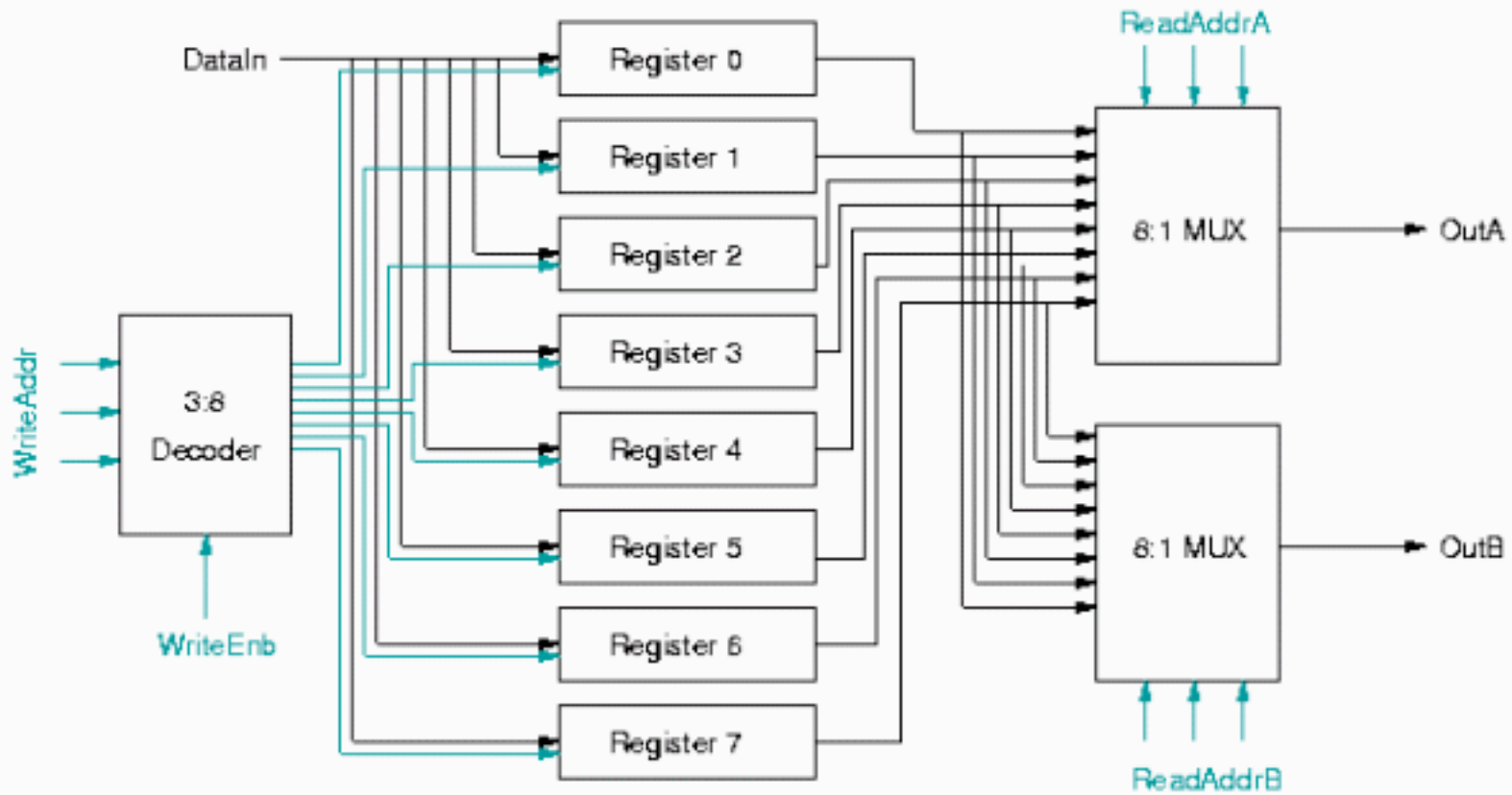

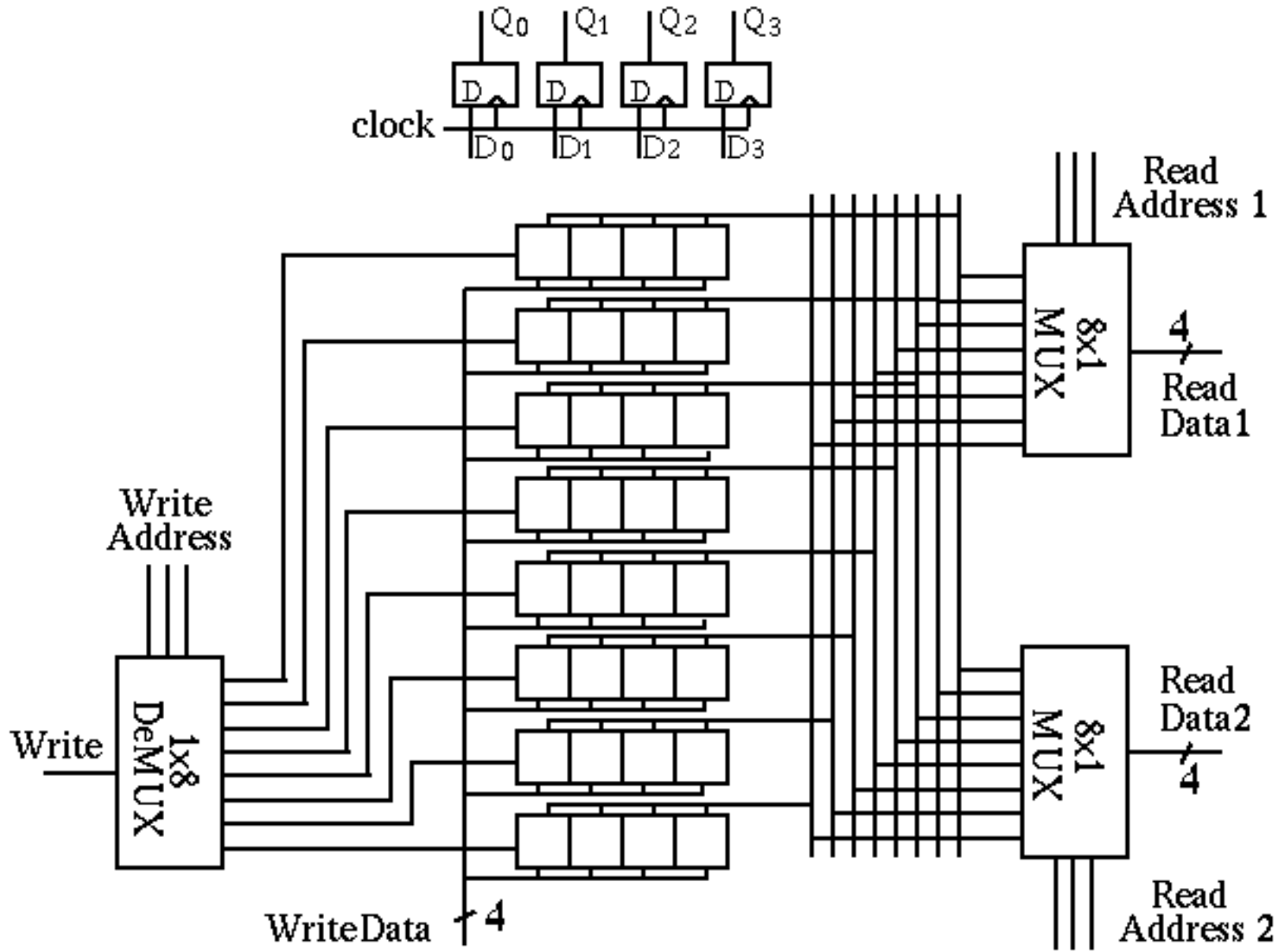Gray lines are 1-bit signals  
Black lines are 10-bit signals




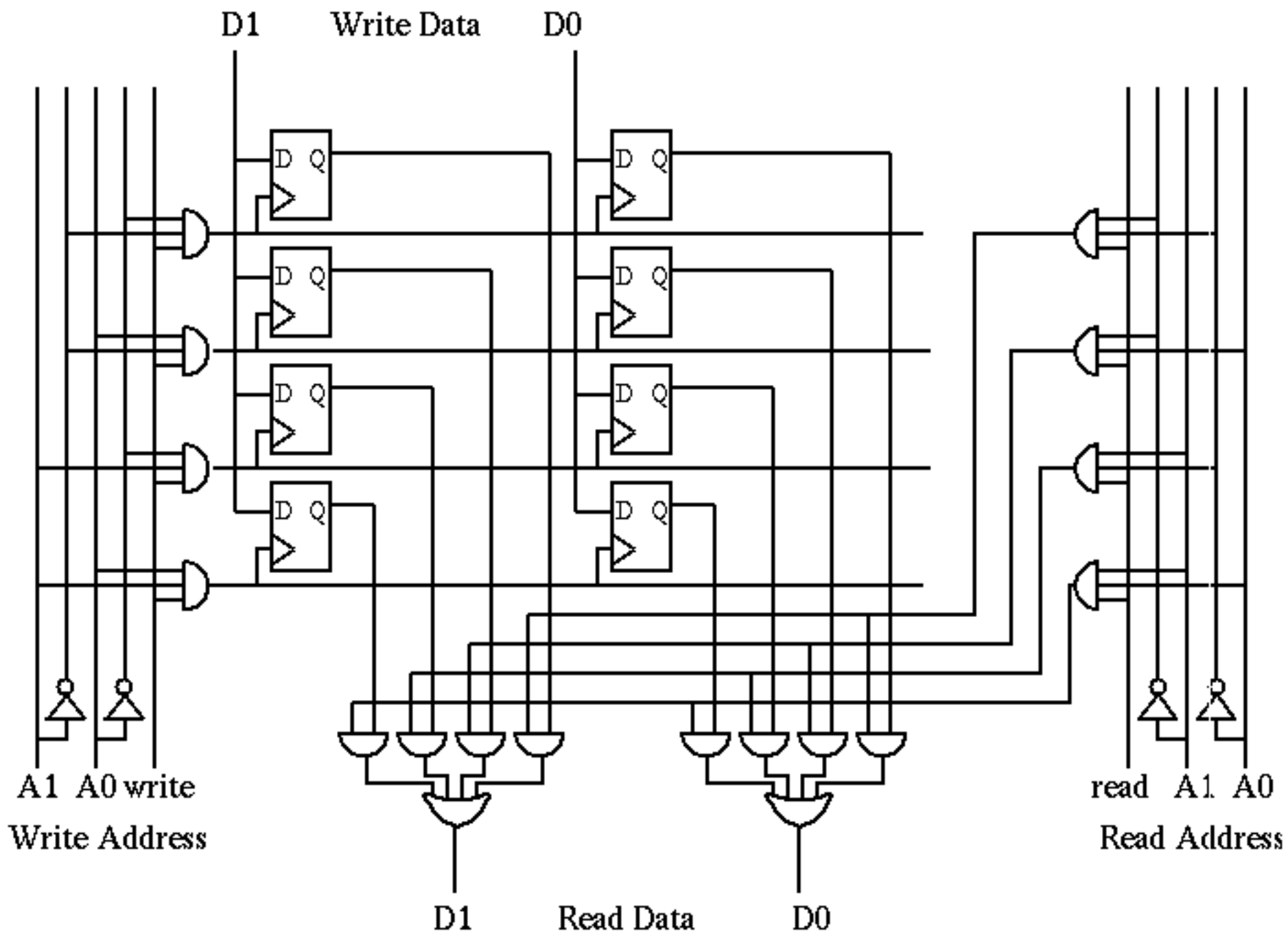

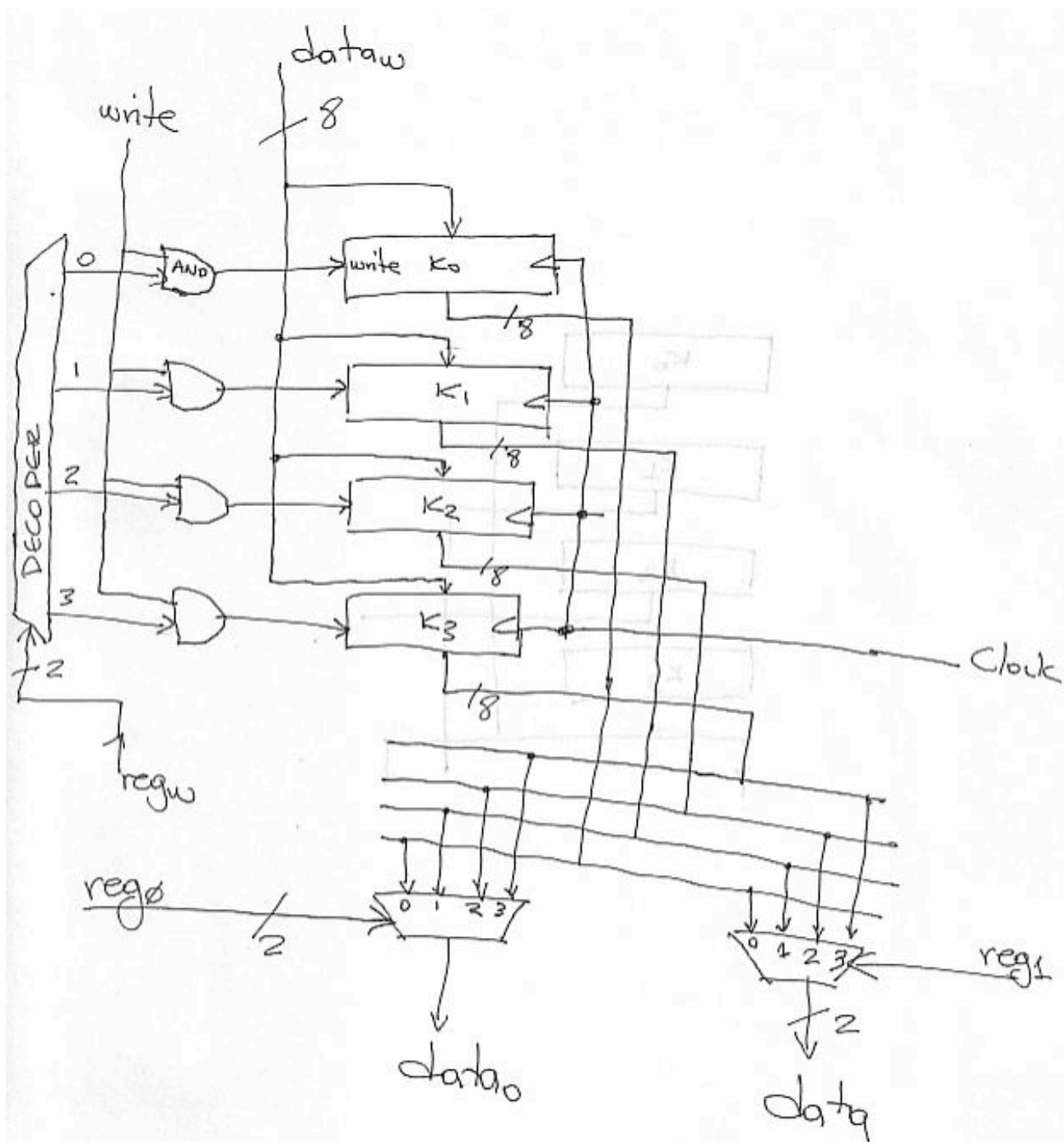
 
# Register File

- **Register file is a unit containing  $r$  registers**
  - $r$  can be 4, 8, 16, 32, etc.
- **Each register has  $n$  bits**
  - $n$  can be 4, 8, 16, 32, etc.
  - $n$  defines the data path width
- **Output ports (DATA1 and DATA2) are used for reading the register file**
  - Any register can be read from any of the ports
  - Each port needs a  $\log_2 r$  bits to specify the read address (RA1 and RA2)
- **Input port (LD\_DATA) is used for writing data to the register file**
  - Write address is also specified by  $\log_2 r$  bits (WA)
  - Writing is enabled by a 1-bit signal (WR)






# Register File: Exercise

- Suppose that a register file
  - contains 32 registers
  - width of data path is 16 bits (i.e., each register has 16 bits)


- How many bits are there for each of the signals?

 - RA1                    5
- RA2                    5
- DATA1                16
- DATA2                16
- WA                     5
- LD\_DATA               16
- WR                     1



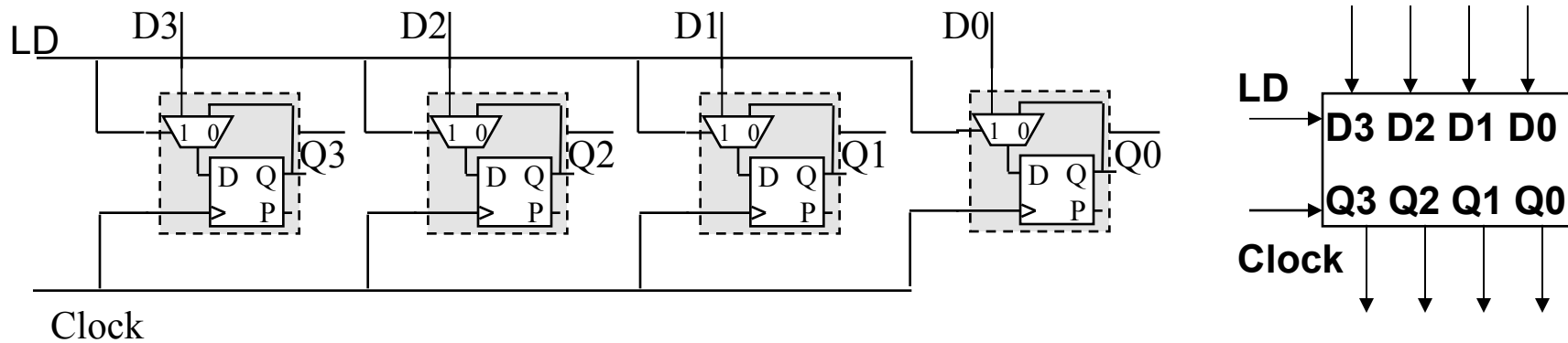
# Register file design

- We will design an eight-register file with 4-bit wide registers
- A single 4-bit register and its abstraction are shown below



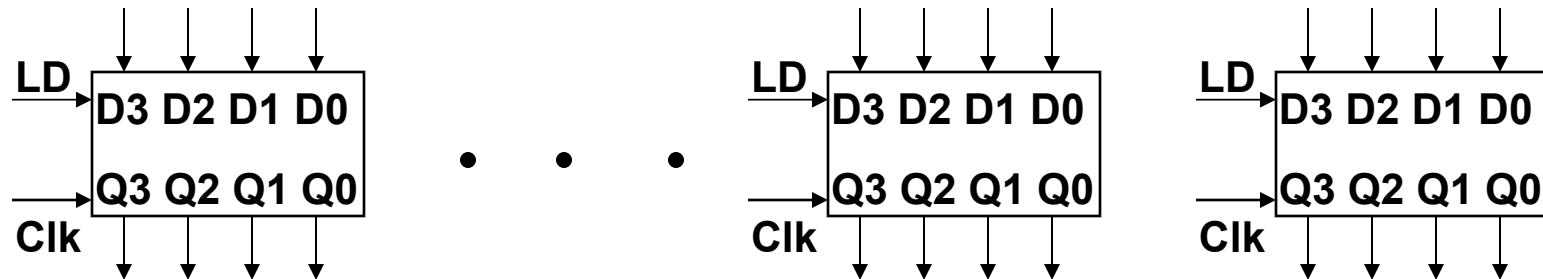- We have to use eight such registers to make an eight register file




- How many bits are required to specify a register address?


 
# Adding write control to register file

- To write to any register, we need the register's address (WA) and a write register signal (WR)
- A 3-bit write address is decoded if write register signal is present
- One of the eight registers gets a LD signal from the decoder



**Questions?**

**THE END**