

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Incompletely Specified Functions & Multiple-Output Circuits

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW4 is out**
- **It is due on Monday Sep 18 @ 4pm.**
- **Please write clearly on the first page (in block capital letters) the following three things:**
 - **Your First and Last Name**
 - **Your Student ID Number**
 - **Your Lab Section Letter**
- **Also, staple all of your pages together**

Administrative Stuff

- **Midterm Exam #1**
- **When: Friday Sep 22.**
- **Where: This classroom**
- **What: Chapter 1 and Chapter 2 plus number systems**
- **The exam will be open book and open notes (you can bring up to 3 pages of handwritten notes).**
- **Sample exams are posted on the class web page**

Topics for the Midterm Exam

- Binary Numbers
- Octal Numbers
- Hexadecimal Numbers
- Conversion between the different number systems
- Truth Tables
- Boolean Algebra
- Logic Gates
- Circuit Synthesis with AND, OR, NOT
- Circuit Synthesis with NAND, NOR
- Converting an AND/OR/NOT circuit to NAND circuit
- Converting an AND/OR/NOT circuit to NOR circuit
- SOP and POS expressions

Topics for the Midterm Exam

- Mapping a Circuit to Verilog code
- Mapping Verilog code to a circuit
- Multiplexers
- Venn Diagrams
- K-maps for 2, 3, and 4 variables
- Minimization of Boolean expressions using theorems
- Minimization of Boolean expressions with K-maps
- Incompletely specified functions (with don't cares)
- Functions with multiple outputs


Quick Review

The Combining Theorems of Boolean Algebra


14a. $x \cdot y + x \cdot \bar{y} = x$

14b. $(x + y) \cdot (x + \bar{y}) = x$

One-Variable K-map

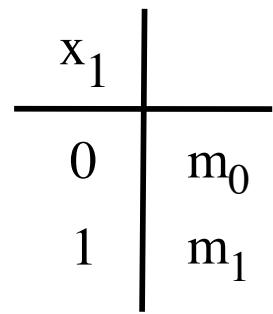

(a) Truth table

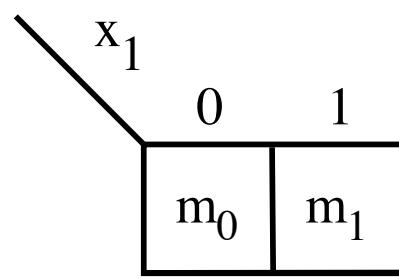


(b) Karnaugh map

One-Variable K-map

		x_1
		0
x_1	0	1
	1	0

(a) Truth table

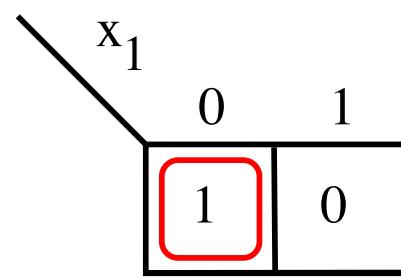


(b) Karnaugh map

Two-Variable K-map


x_1	x_2	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

(a) Truth table

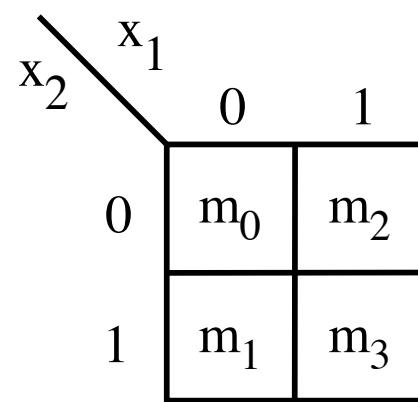

(b) Karnaugh map

Two-Variable K-map

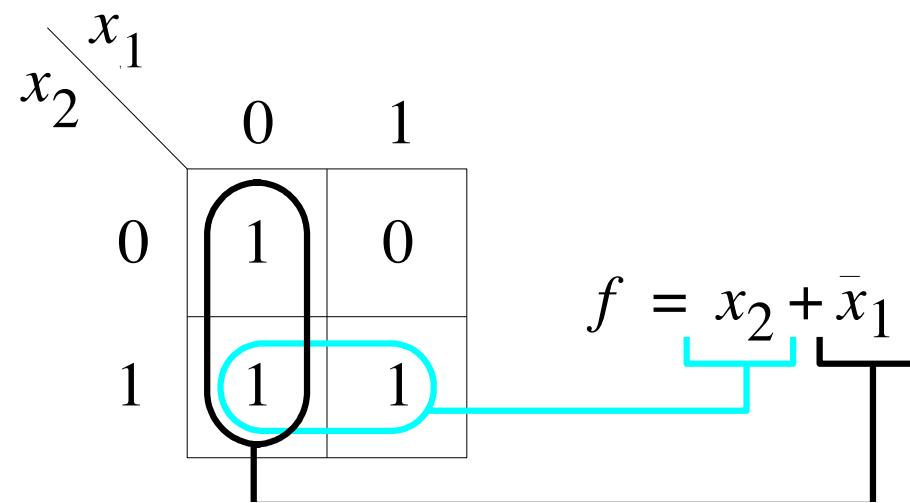

[Figure 2.50 from the textbook]

These are all valid groupings

	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

These are also valid

	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

But try to use larger rectangles if possible.

These two are not valid


	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

	x_1	
x_2	0	1
0	m_0	m_2
1	m_1	m_3

Three-Variable K-map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

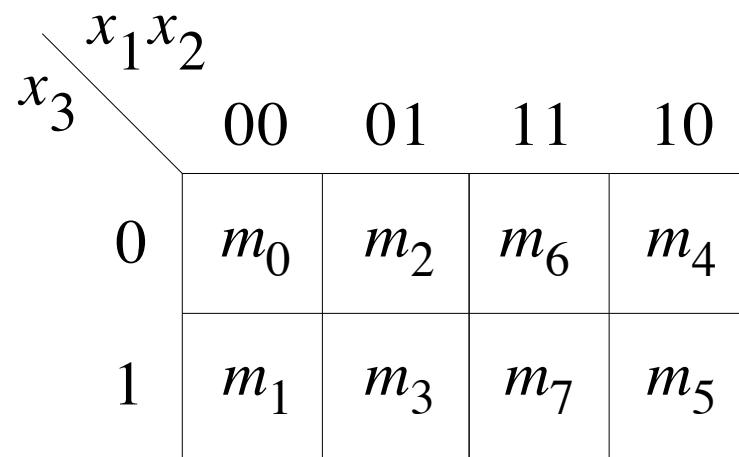


(b) Karnaugh map

Location of three-variable minterms

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

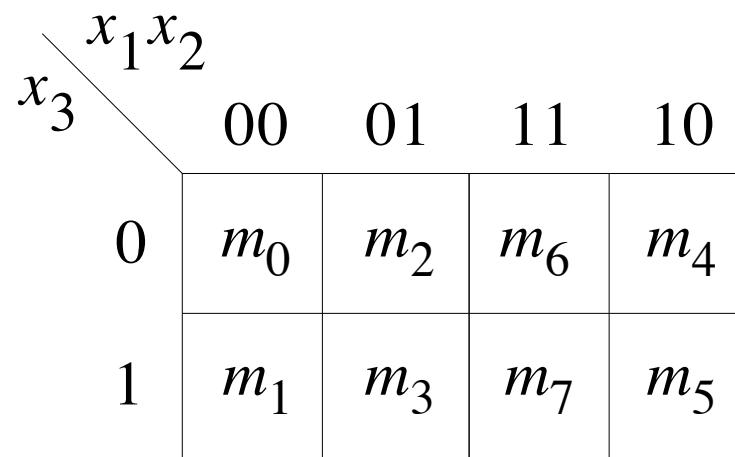

(b) Karnaugh map

Notice the placement of


- Variables
- Binary pair values
- Minterms

Adjacency Rules

Karnaugh map for x_1x_2 vs x_3 :

		00	01	11	10	
		0	m_0	m_2	m_6	m_4
		1	m_1	m_3	m_7	m_5

adjacent
columns

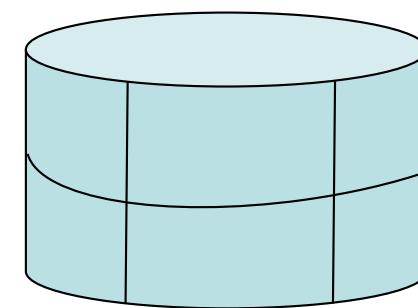


As if the K-map were
drawn on a cylinder

Adjacency Rules


		x_1x_2	x_3		
		00	01	11	10
0		m_0	m_2	m_6	m_4
1	0	m_1	m_3	m_7	m_5

adjacent
columns

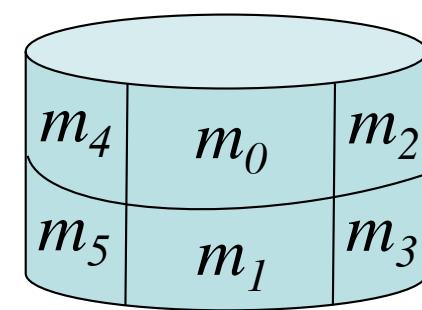


As if the K-map were
drawn on a cylinder

Three-Variable K-map

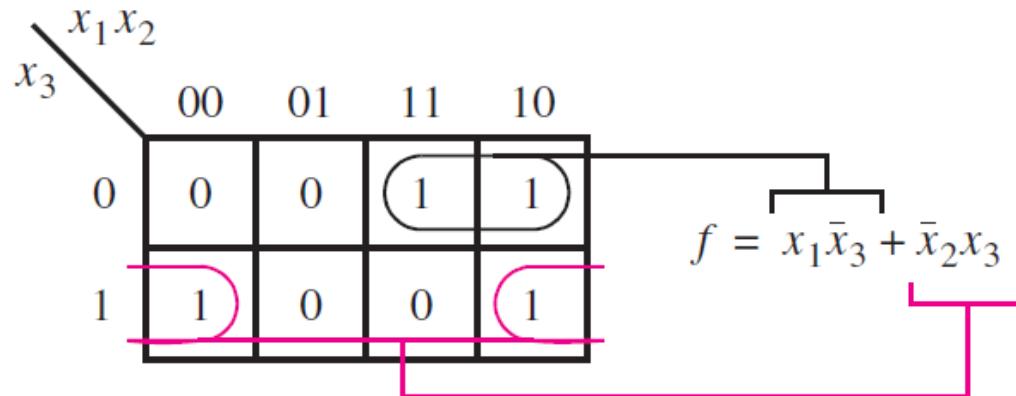

(a) The function of Figure 2.23

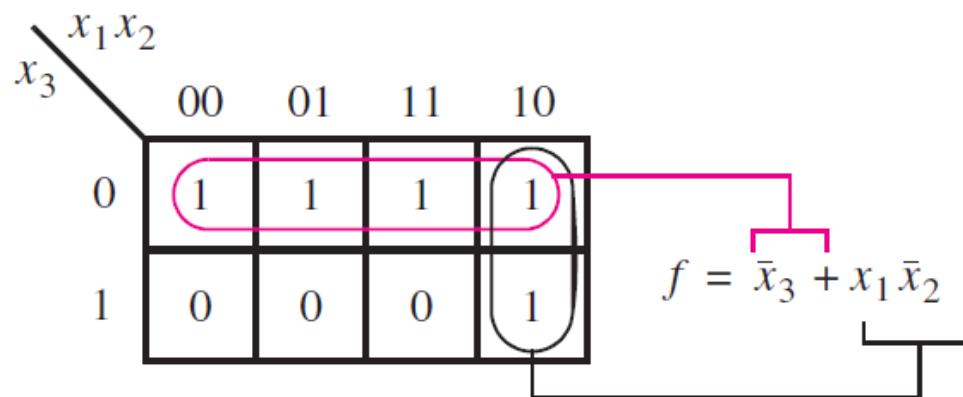


(b) The function of Figure 2.48


Two Different Ways to Draw the K-map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
<hr/>			
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

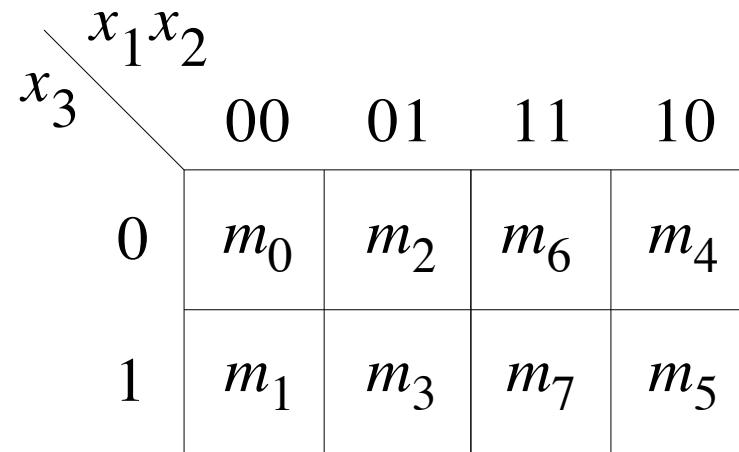

(b) Karnaugh map

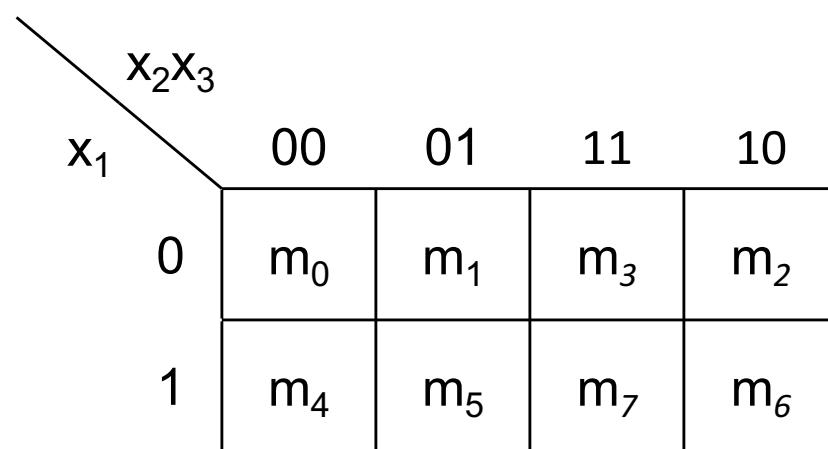

Another Way to Draw 3-variable K-map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
<hr/>			
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

$x_3 \backslash x_1x_2$

	00	01	11	10
0	m_0	m_2	m_6	m_4
1	m_1	m_3	m_7	m_5

(b) Karnaugh map

$x_2x_3 \backslash x_1$

	0	1
00	m_0	m_4
01	m_1	m_5
11	m_3	m_7
10	m_2	m_6


Gray Code

- Sequence of binary codes
- Consecutive lines vary by only 1 bit

	000
	001
00	011
01	010
11	110
10	111
	101
	100

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

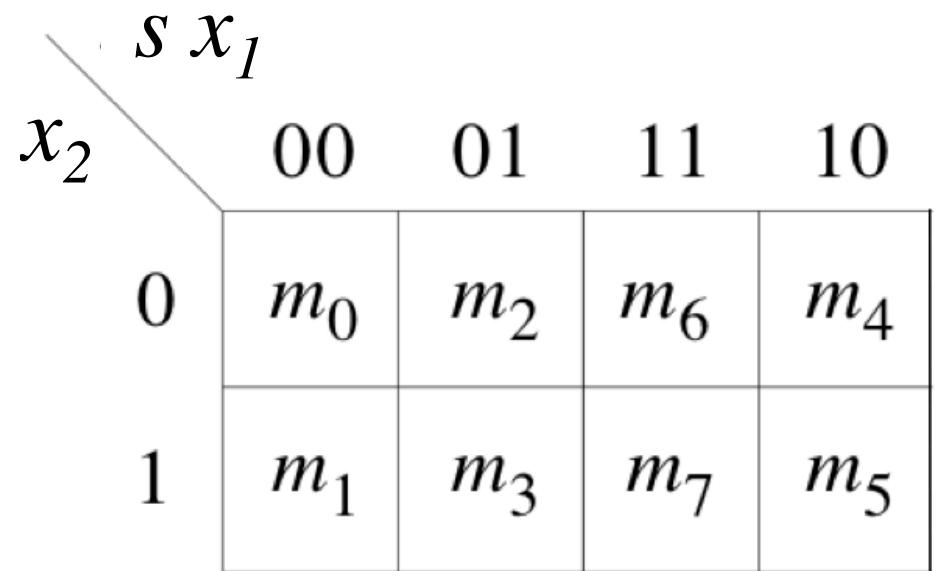


Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

	s	x_1			
	x_2	00	01	11	10
0	0	000	010	110	100
1	1	001	011	111	101

Gray Code & K-map


	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

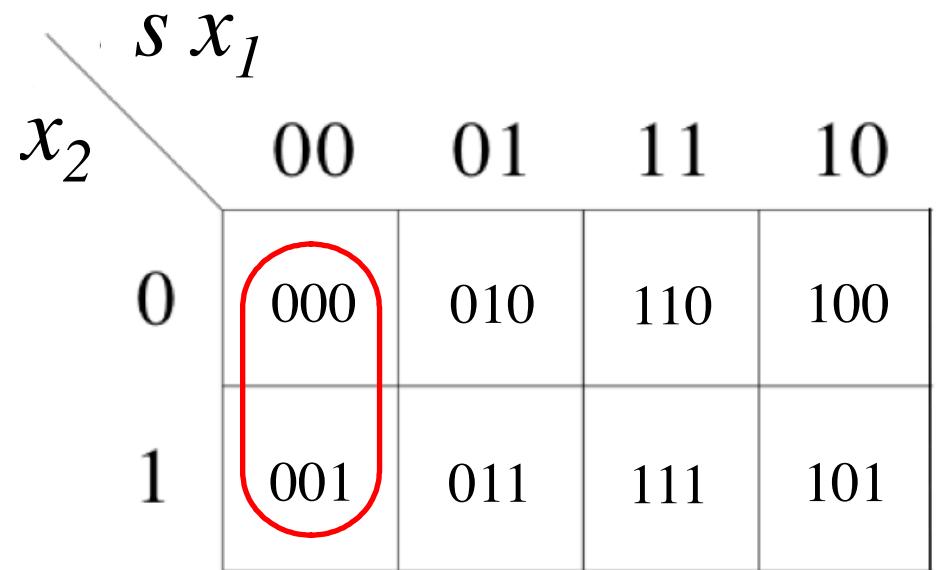

These two neighbors
differ only in the LAST bit

Gray Code & K-map


	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

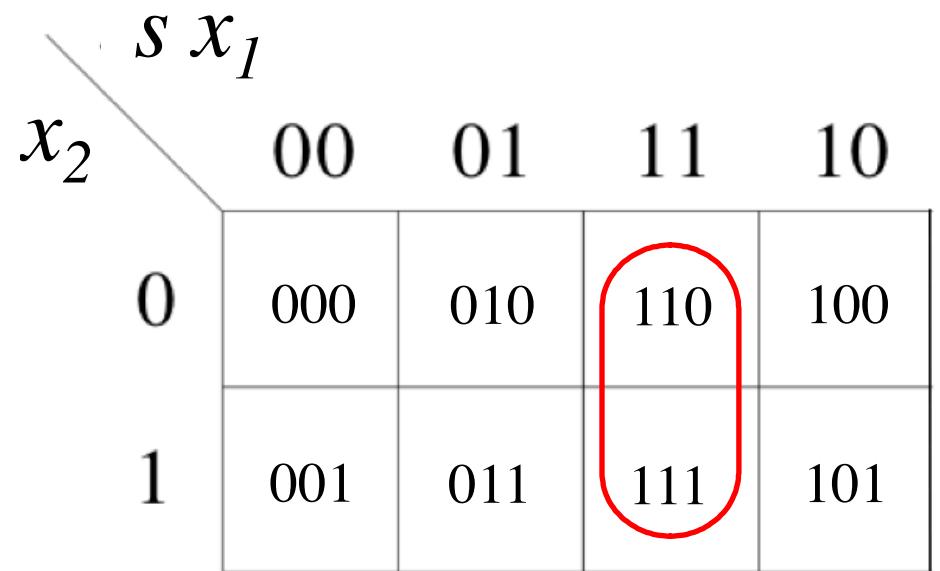

These two neighbors
differ only in the LAST bit

Gray Code & K-map


	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

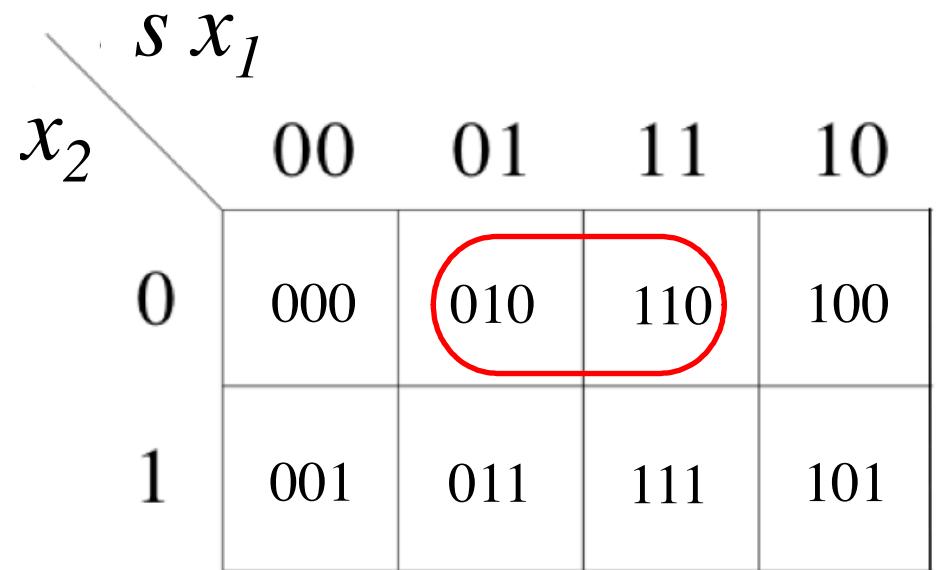

These two neighbors
differ only in the FIRST bit

Gray Code & K-map


	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

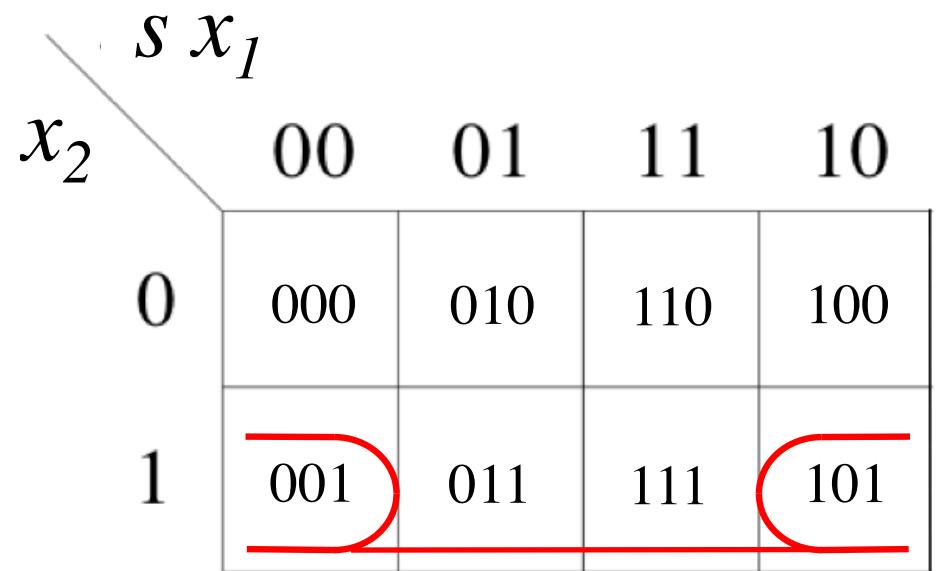

These two neighbors
differ only in the FIRST bit

Gray Code & K-map


	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

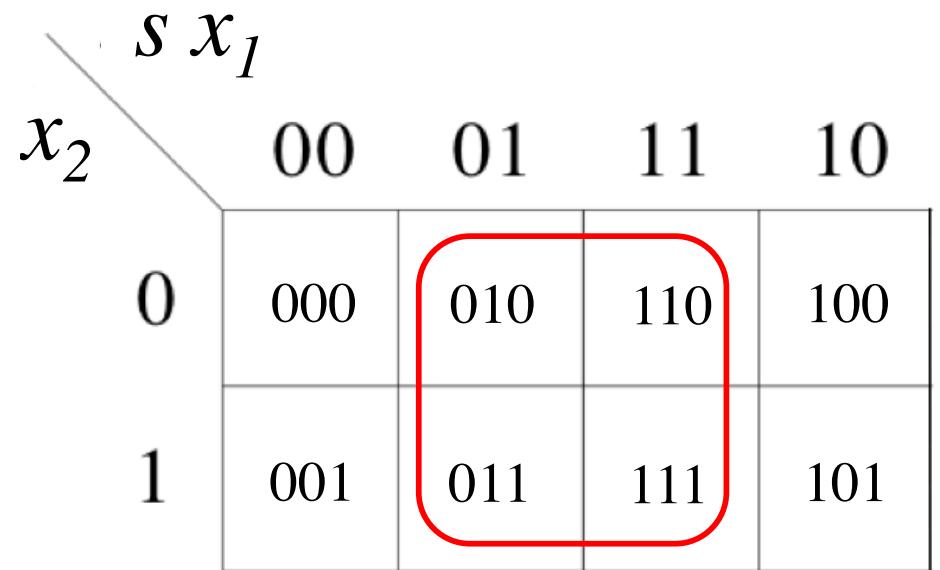

These four neighbors
differ in the FIRST and LAST bit

They are similar in their MIDDLE bit


A four-variable Karnaugh map

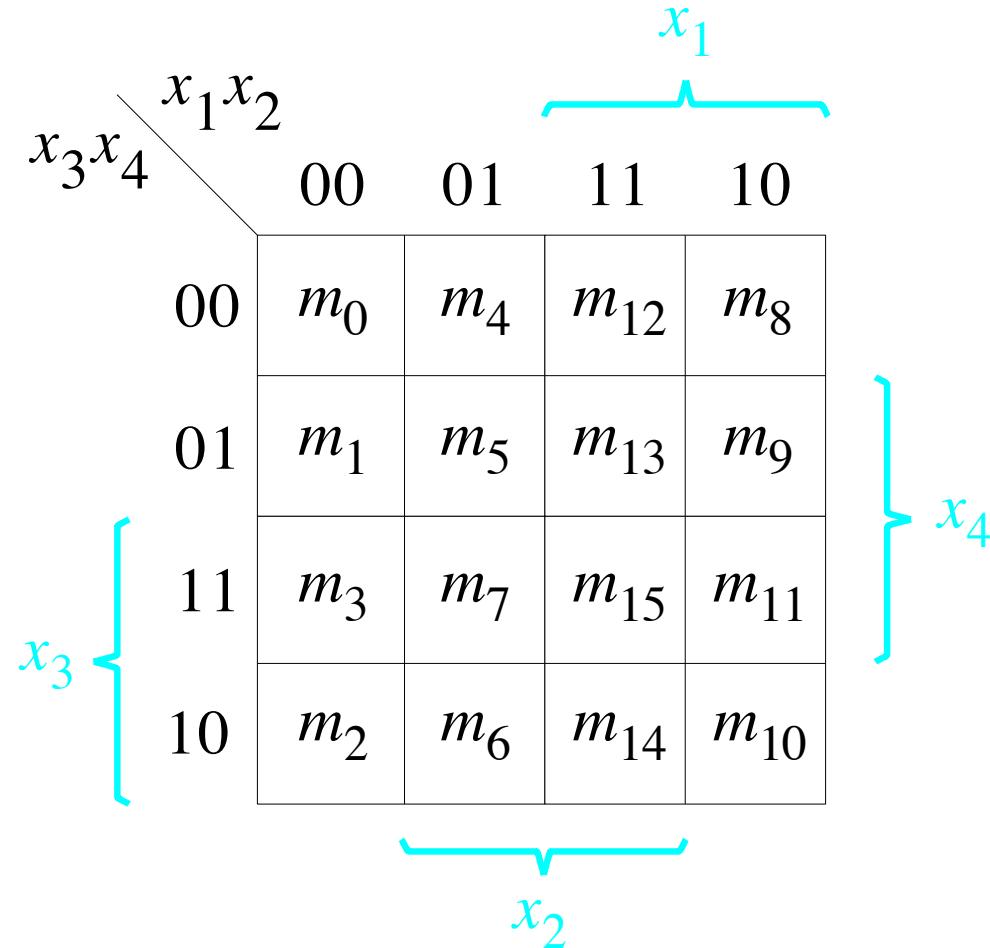

[Figure 2.53 from the textbook]


A four-variable Karnaugh map

x_1	x_2	x_3	x_4	
0	0	0	0	m_0
0	0	0	1	m_1
0	0	1	0	m_2
0	0	1	1	m_3
<hr/>				
0	1	0	0	m_4
0	1	0	1	m_5
0	1	1	0	m_6
0	1	1	1	m_7
<hr/>				
1	0	0	0	m_8
1	0	0	1	m_9
1	0	1	0	m_{10}
1	0	1	1	m_{11}
<hr/>				
1	1	0	0	m_{12}
1	1	0	1	m_{13}
1	1	1	0	m_{14}
1	1	1	1	m_{15}

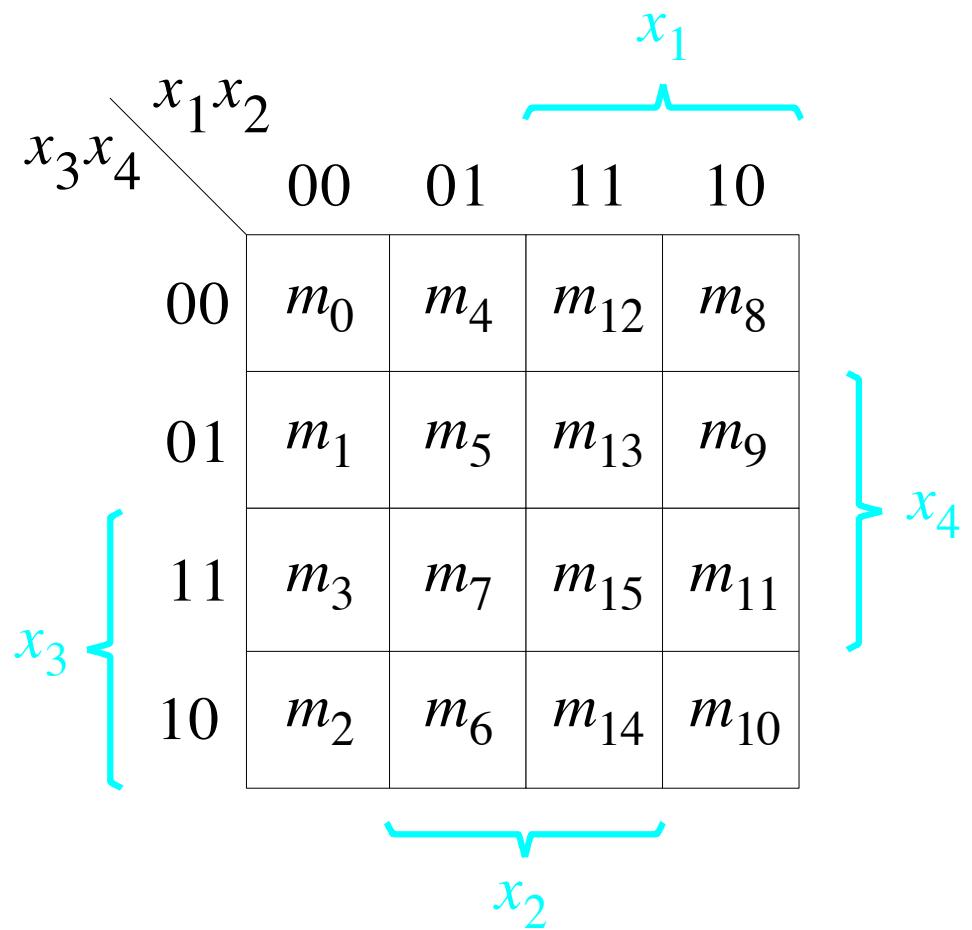


Gray Code & K-map

x_1	x_2	x_3	x_4	
0	0	0	0	m_0
0	0	0	1	m_1
0	0	1	0	m_2
0	0	1	1	m_3
<hr/>				
0	1	0	0	m_4
0	1	0	1	m_5
0	1	1	0	m_6
0	1	1	1	m_7
<hr/>				
1	0	0	0	m_8
1	0	0	1	m_9
1	0	1	0	m_{10}
1	0	1	1	m_{11}
<hr/>				
1	1	0	0	m_{12}
1	1	0	1	m_{13}
1	1	1	0	m_{14}
1	1	1	1	m_{15}

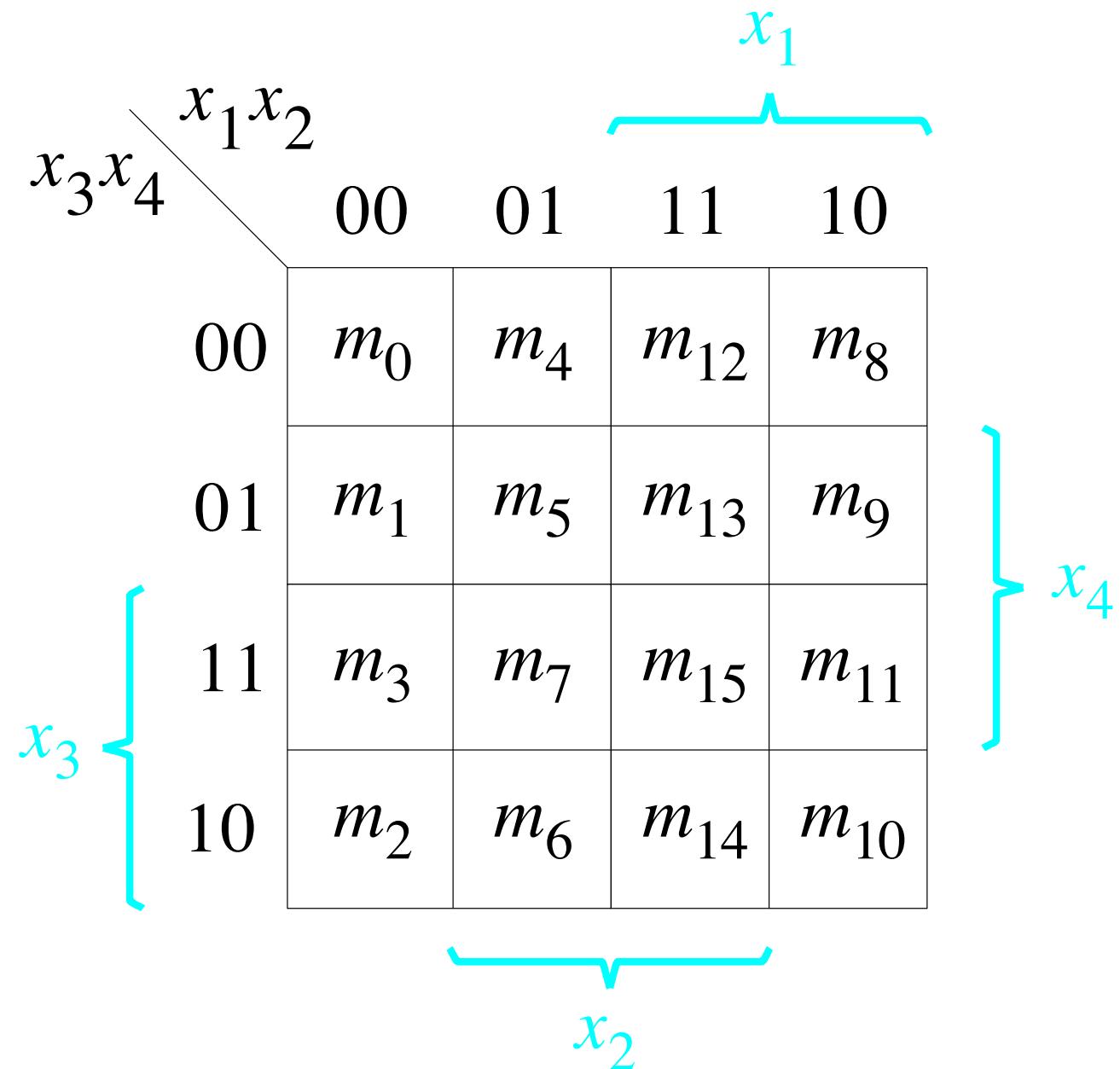

Gray Code & K-map

x_1	x_2	x_3	x_4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
<hr/>				
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
<hr/>				
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
<hr/>				
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

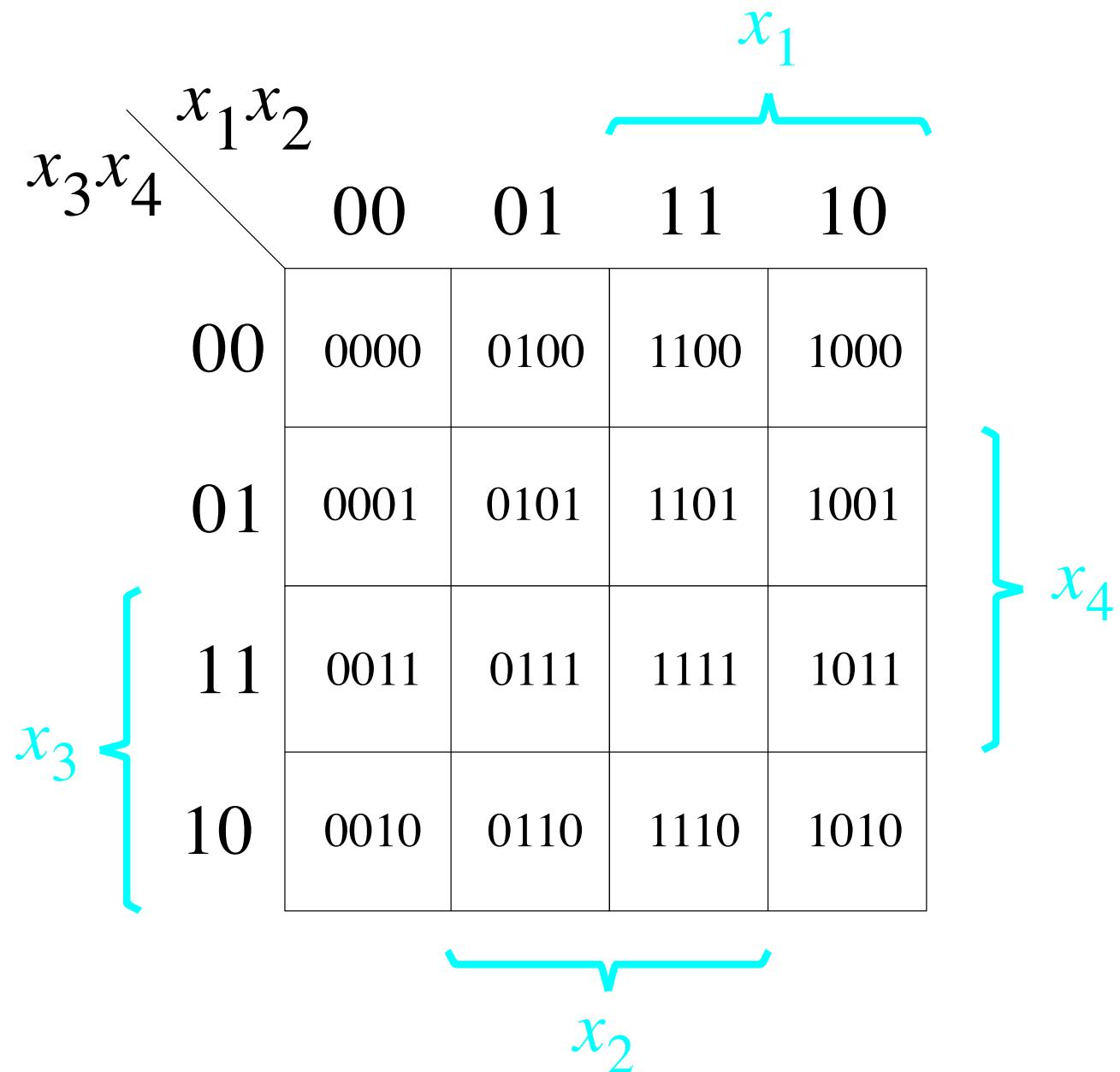

Adjacency Rules

		x_1x_2	x_1x_2		
		00	01	11	10
0	00	m_0	m_2	m_6	m_4
	01	m_1	m_3	m_7	m_5



adjacent columns

		x_1x_2	x_1x_2		
		00	01	11	10
00	00	m_0	m_4	m_{12}	m_8
	01	m_1	m_5	m_{13}	m_9
01	11	m_3	m_7	m_{15}	m_{11}
	10	m_2	m_6	m_{14}	m_{10}

adjacent rows



adjacent columns

Adjacency Rules

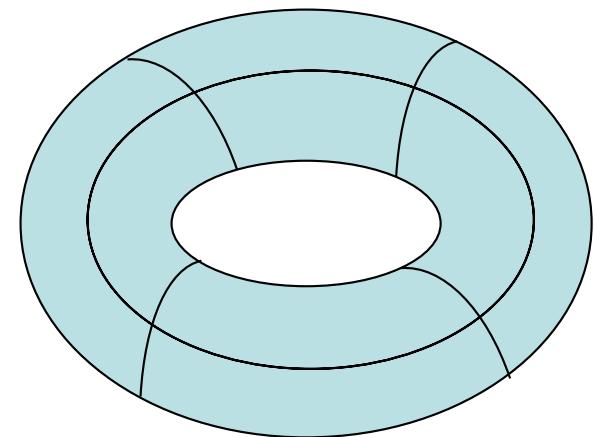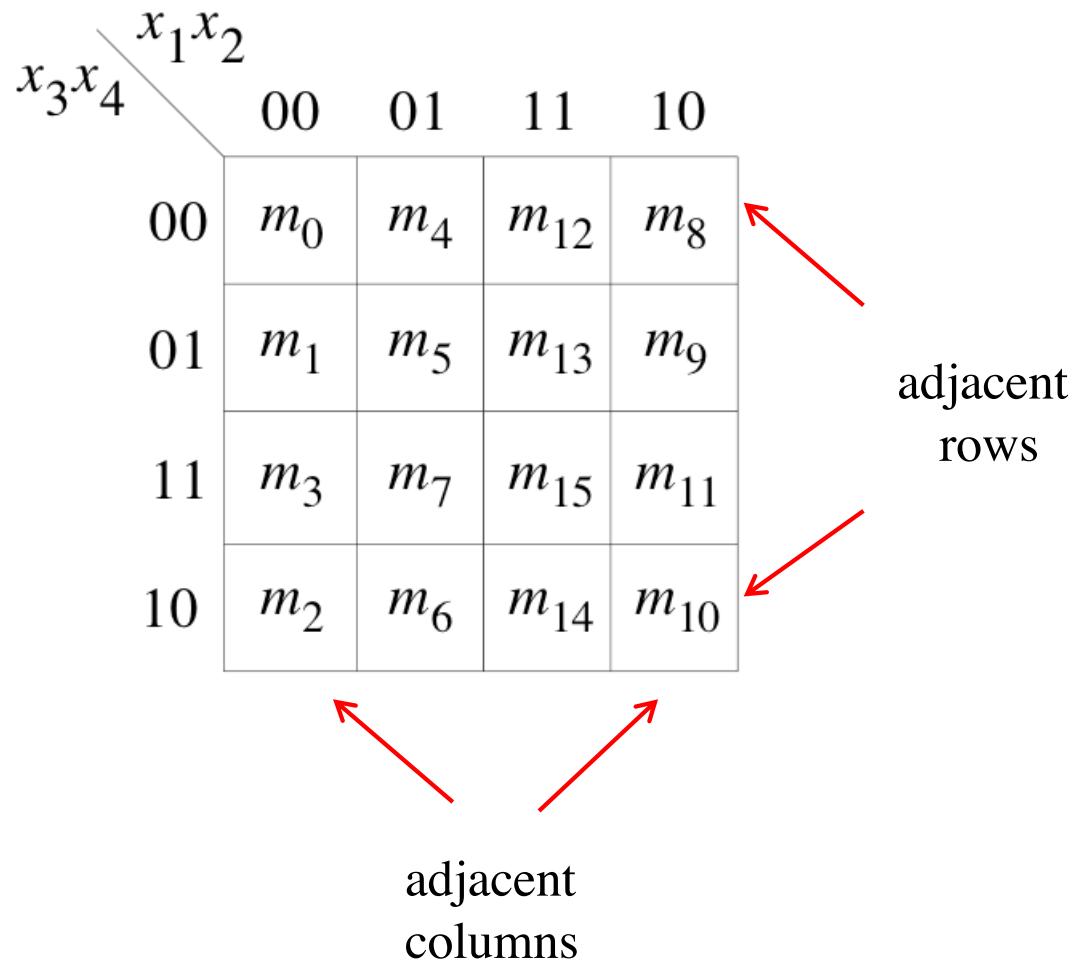


As if the K-map were
drawn on a torus

Adjacency Rules

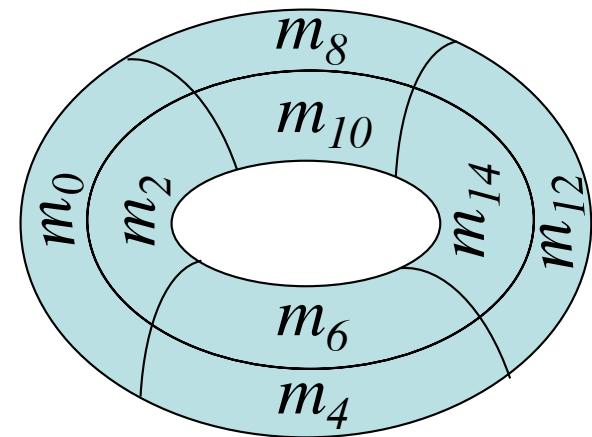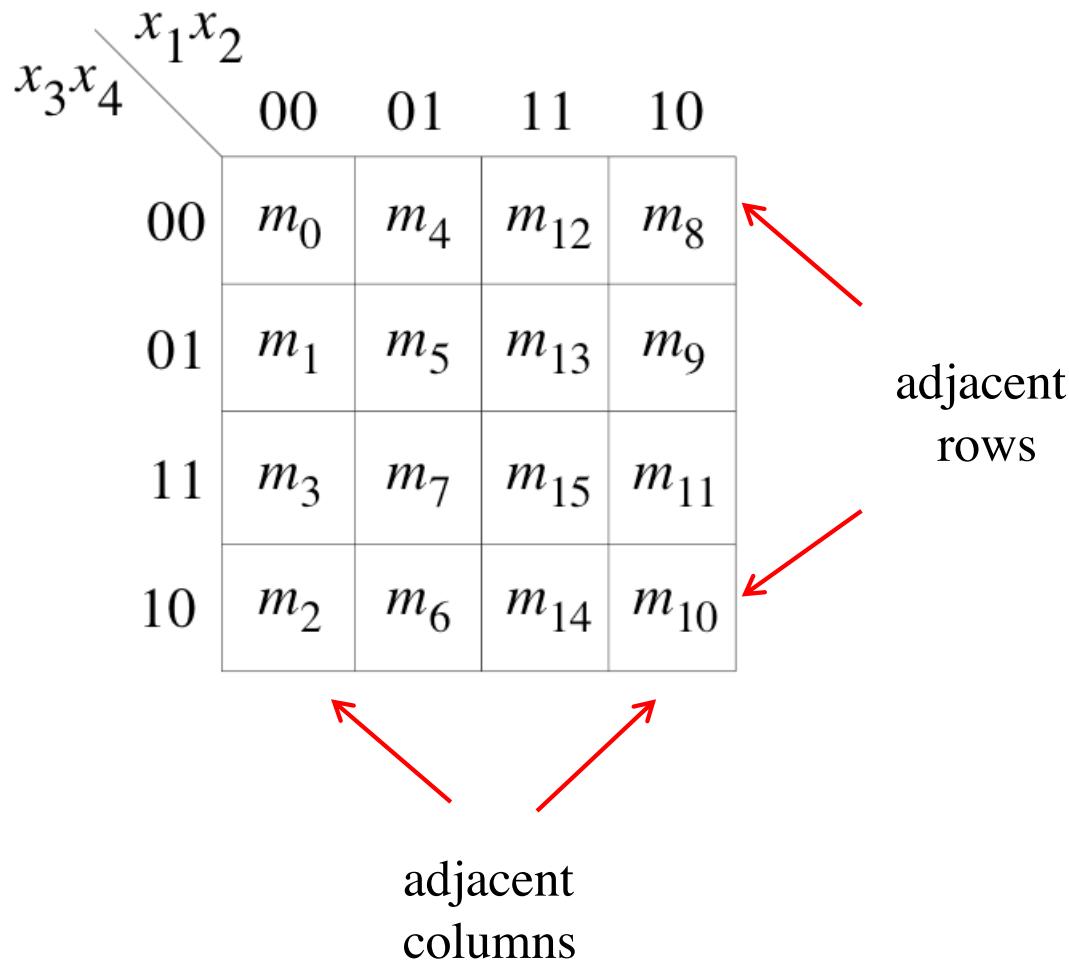


As if the K-map were drawn on a torus

Example of a four-variable Karnaugh map

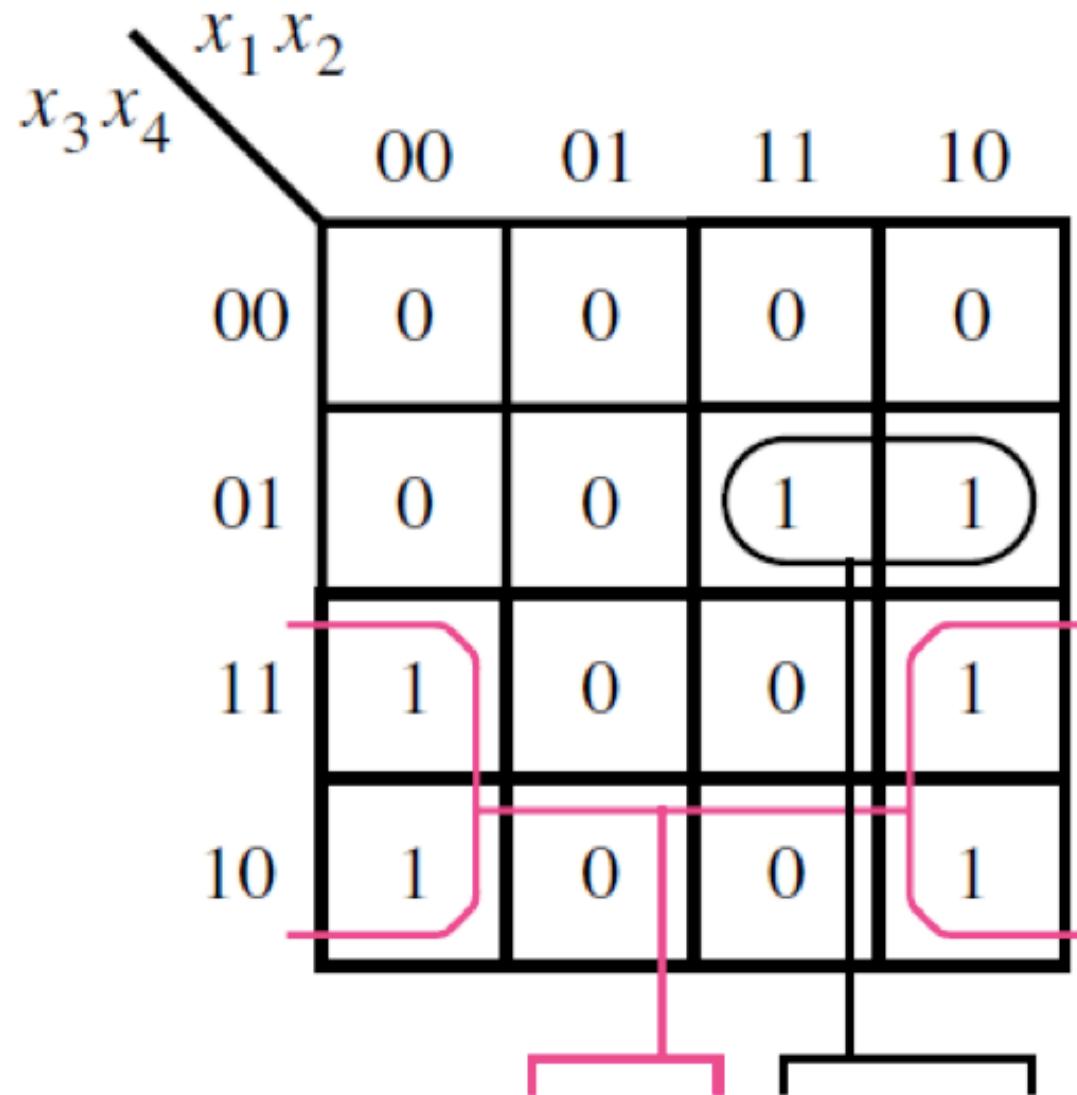


[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

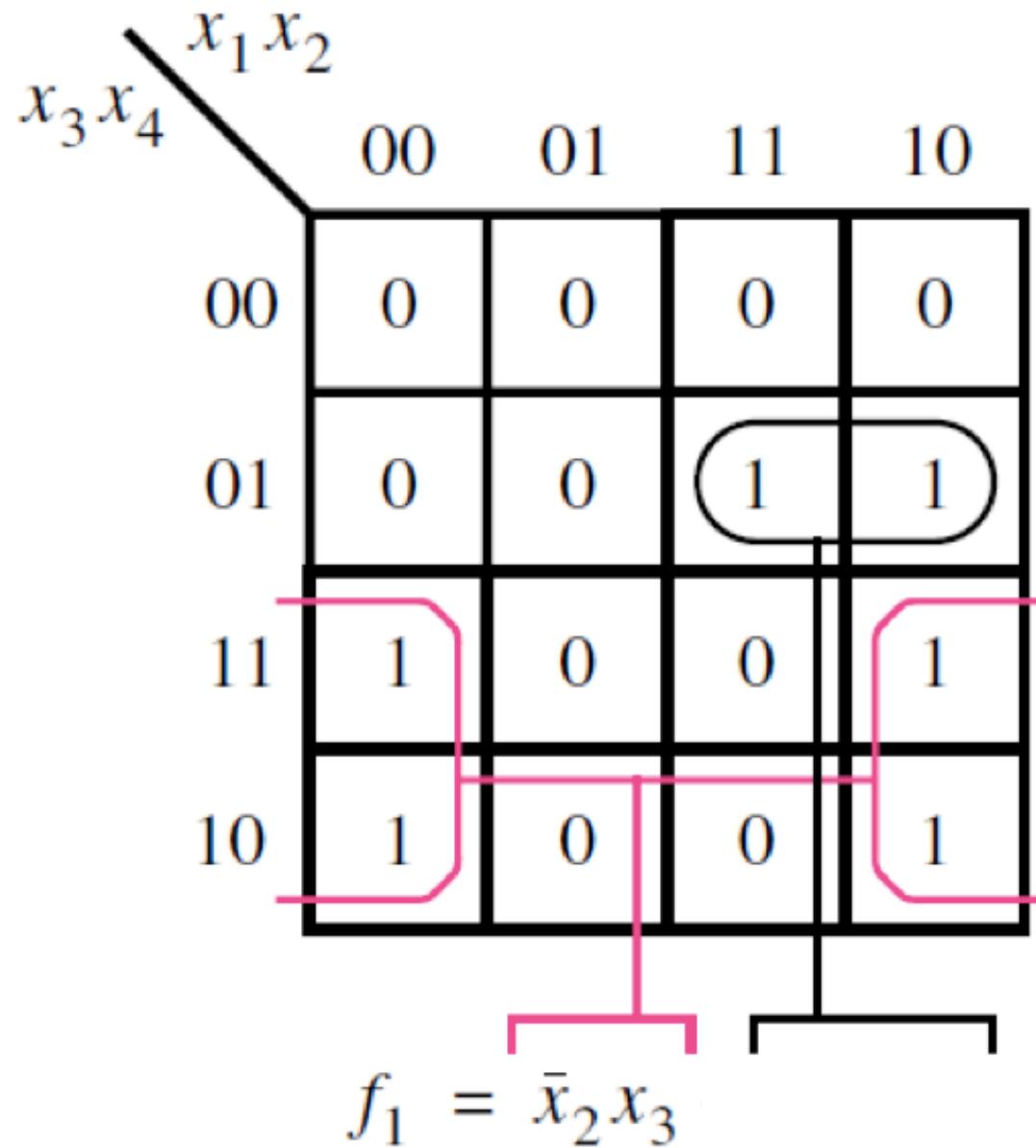


[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

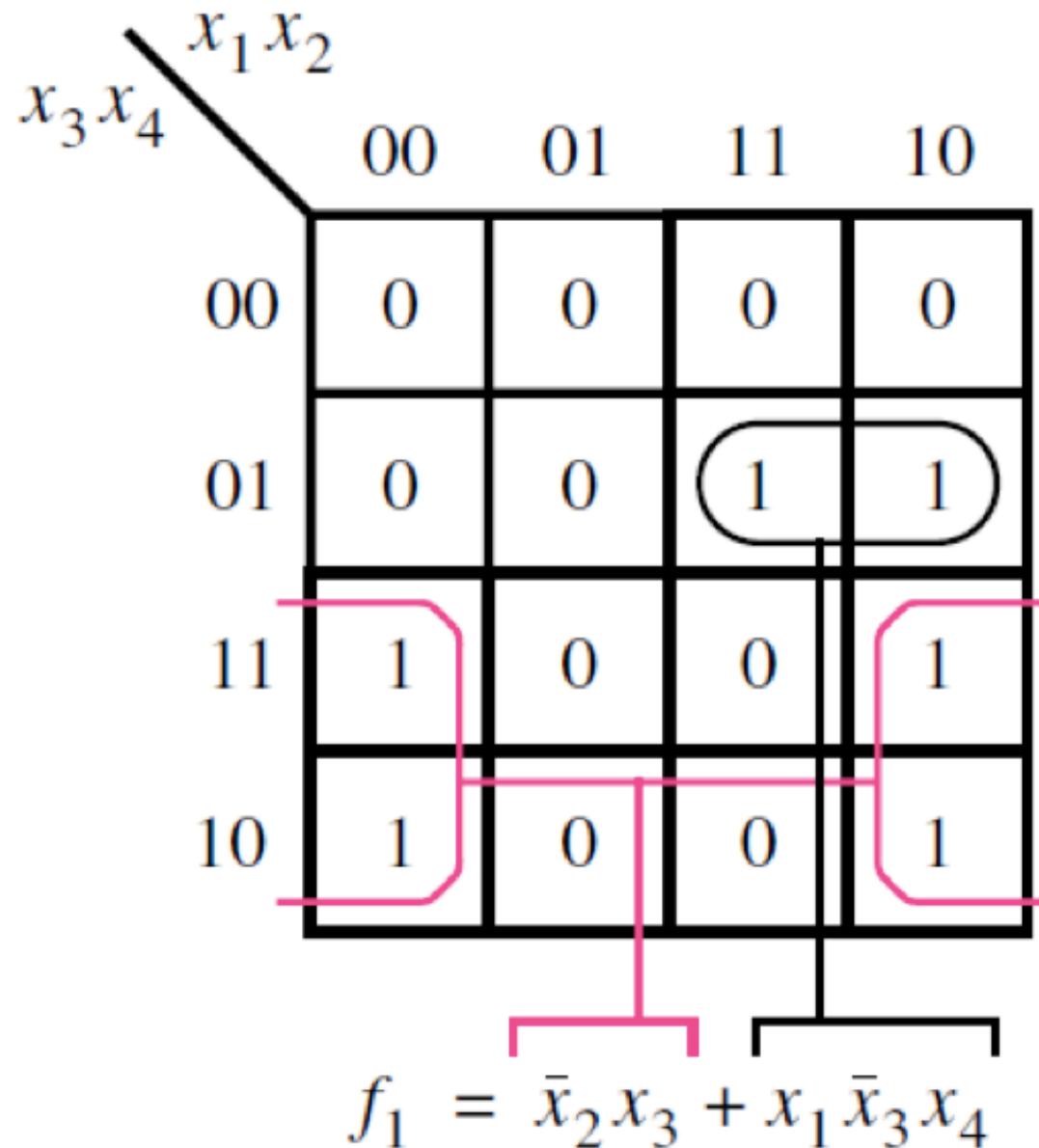


[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

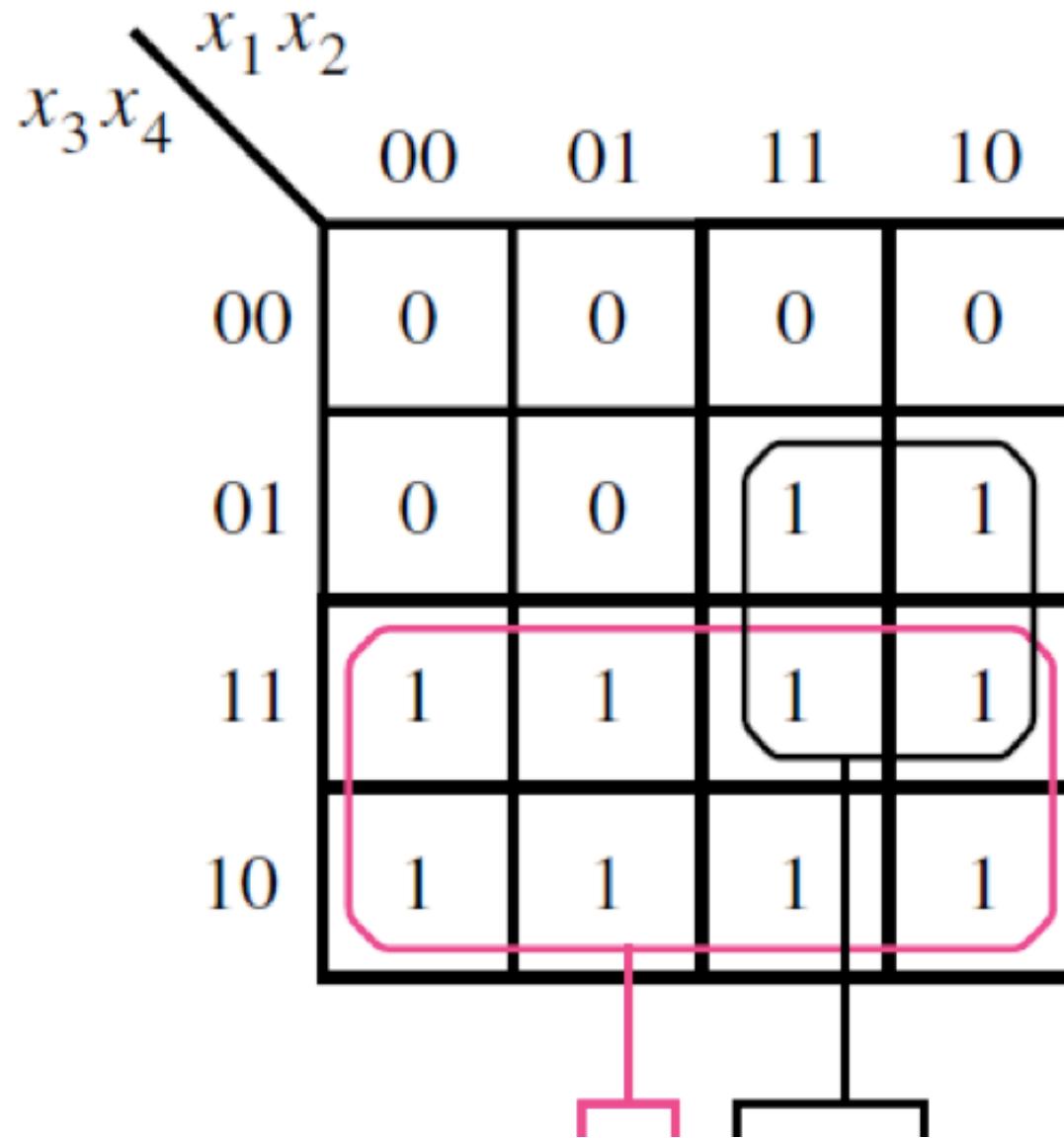


[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

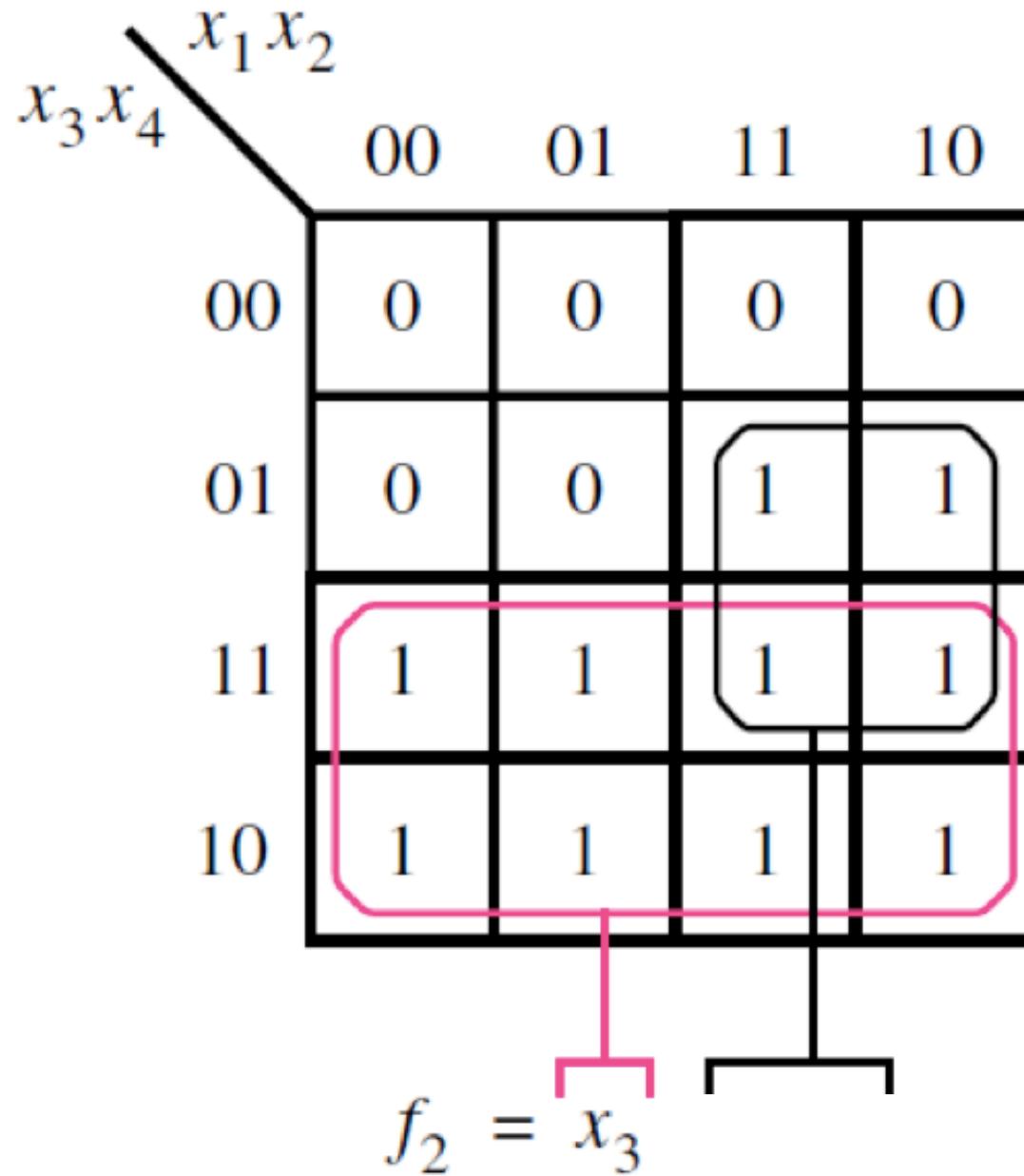





[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

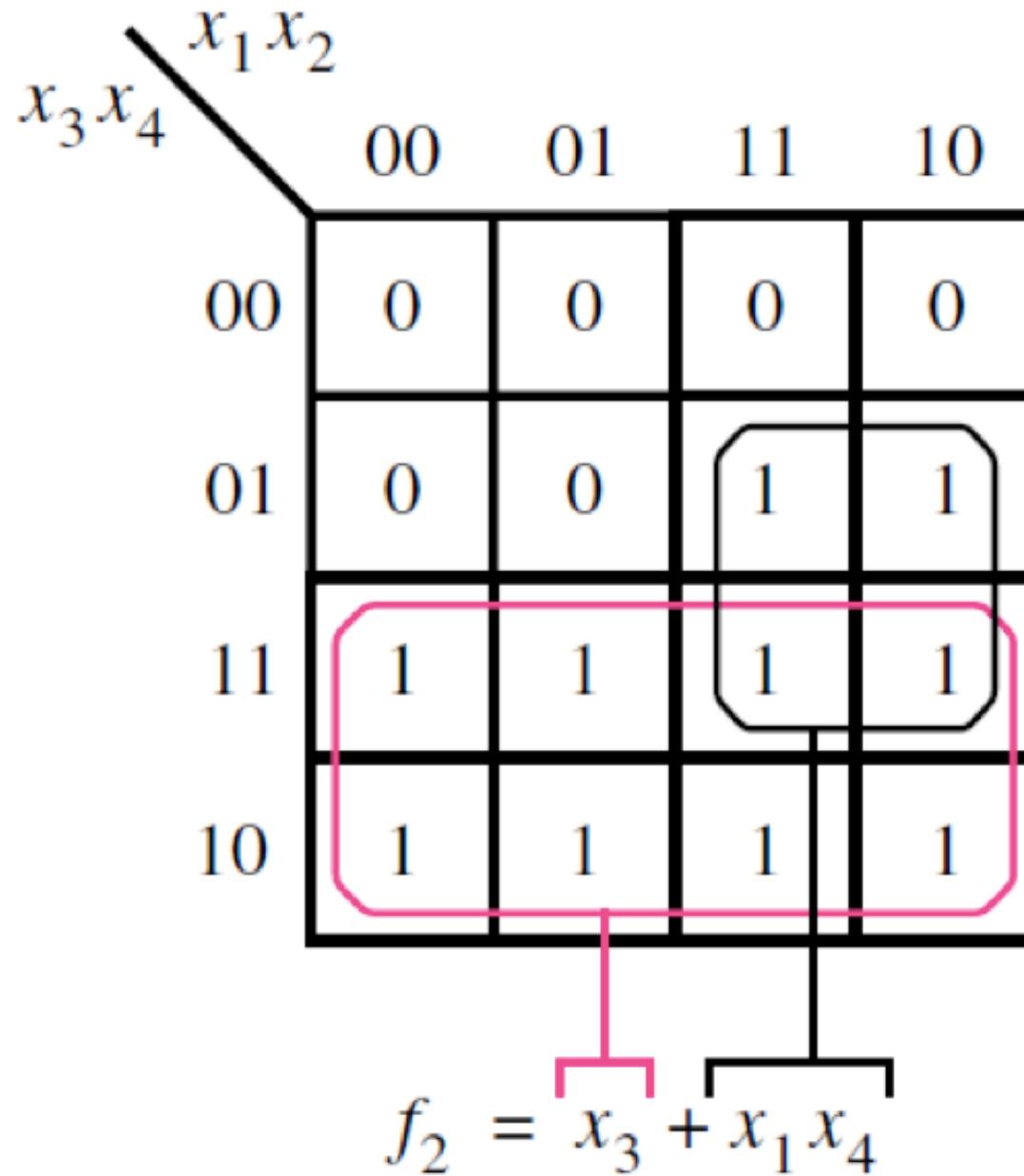

[Figure 2.54 from the textbook]

Other Four-Variable K-map Examples

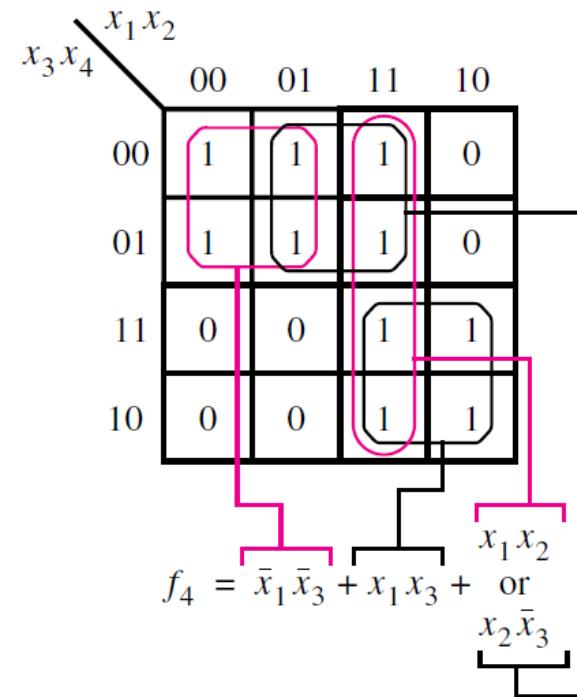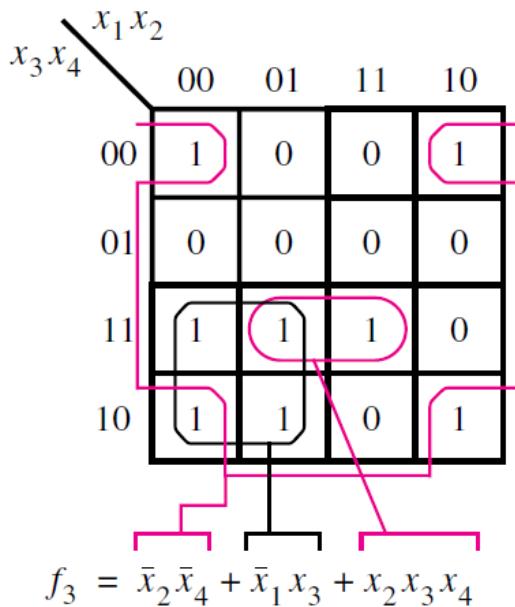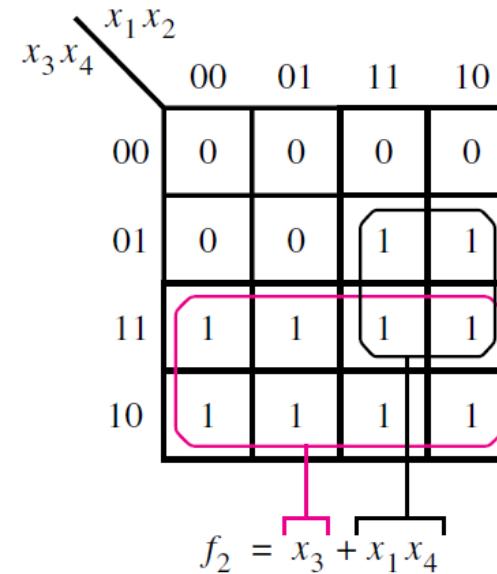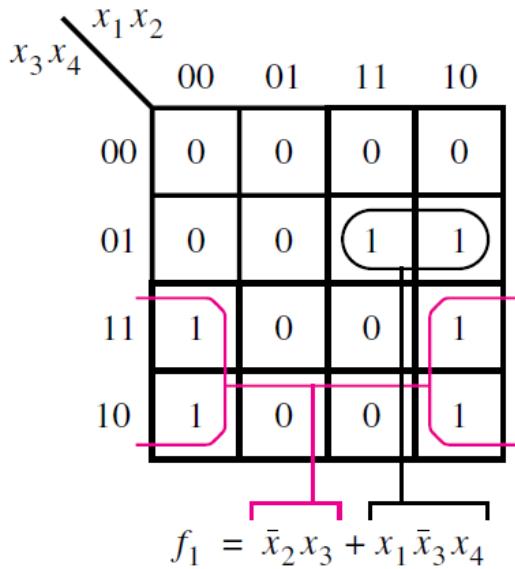

[Figure 2.54 from the textbook]

Strategy For Minimization

Grouping Rules

- **Group “1”s with rectangles**
- **Both sides a power of 2:**
 - 1x1, 1x2, 2x1, 2x2, 1x4, 4x1, 2x4, 4x2, 4x4
- **Can use the same minterm more than once**
- **Can wrap around the edges of the map**
- **Some rules in selecting groups:**
 - Try to use as few groups as possible to cover all “1”s.
 - For each group, try to make it as large as you can (i.e., if you can use a 2x2, don’t use a 2x1 even if that is enough).

Terminology

Literal: a variable, complemented or uncomplemented

Some Examples:

- x_1
- x_2
- \neg

Terminology

- Implicant: product term that indicates the input combinations for which the function output is 1
- Example
 - $\bar{x}_1 \bar{x}_2$ - indicates that $\bar{x}_1 \bar{x}_2$ and $\bar{x}_1 x_2$ yield output of 1

	x_1	0	1
x_2	0	1	0
	1	1	0

Terminology

- Prime Implicant
 - Implicant that cannot be combined into another implicant with fewer literals
 - Some Examples

		$x_1 x_2$				
		x_3	00	01	11	10
x_3	0	0	1	1	1	1
	1	1	1	1	0	

Not prime

		$x_1 x_2$				
		x_3	00	01	11	10
x_3	0	0	1	1	1	1
	1	1	1	1	1	0

Prime

Terminology

- **Essential Prime Implicant**
 - Prime implicant that includes a minterm not covered by any other prime implicant
 - Some Examples

		$x_1 x_2$				
		x_3	00	01	11	10
x_3	0	0	1	1	1	
	1	1	1	0	0	


Terminology

- **Cover**
 - Collection of implicants that account for all possible input valuations where output is 1
 - Ex. $x_1' x_2 x_3 + x_1 x_2 x_3' + x_1 x_2' x_3'$
 - Ex. $x_1' x_2 x_3 + x_1 x_3'$

		$x_1 x_2$				
		x_3	00	01	11	10
x_1	0	0	0	1	1	
	1	0	1	0	0	

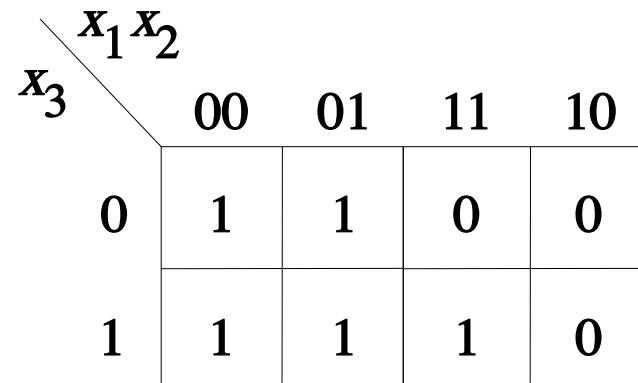Example

- Give the Number of
 - Implicants?
 - Prime Implicants?
 - Essential Prime Implicants?




		$x_1 x_2$	00	01	11	10	
		x_3	0	1	1	0	0
		0	1	1	1	0	
1	1	1	1	1	0		

Why concerned with minimization?

- Simplified function
- Reduce the cost of the circuit
 - Cost: Gates + Inputs
 - Transistors

Three-variable function $f(x_1, x_2, x_3) = \sum m(0, 1, 2, 3, 7)$

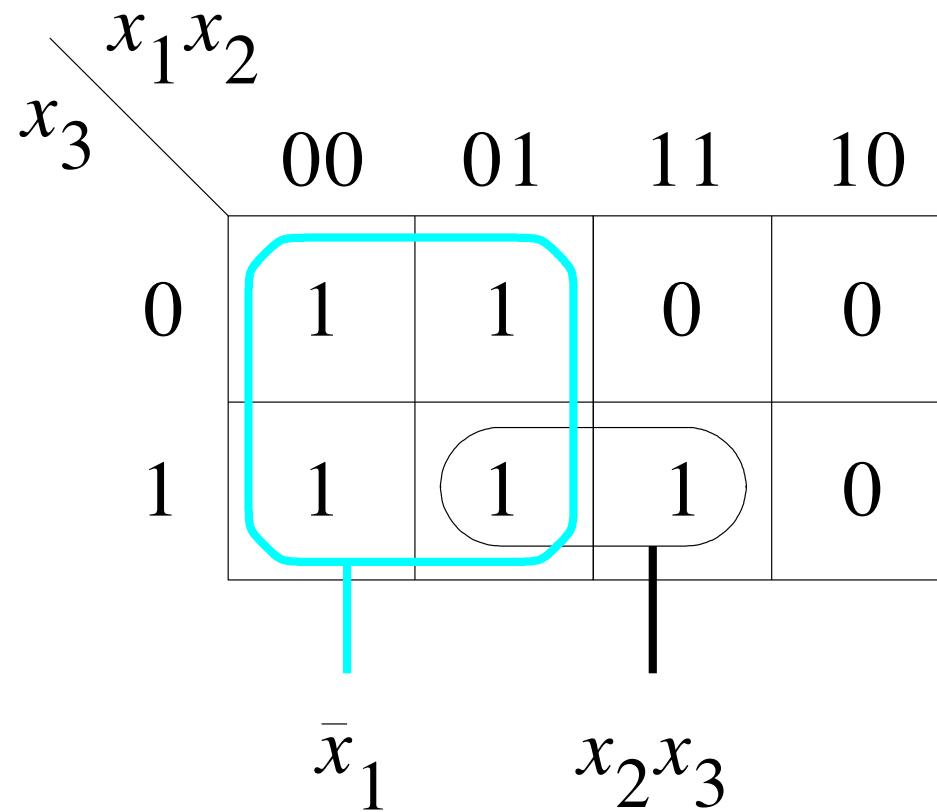


[Figure 2.56 from the textbook]


Example

		$x_1 x_2$			
		00	01	11	
		00	1	1	
		01		1	1
		11			1
		10	1		1


Example

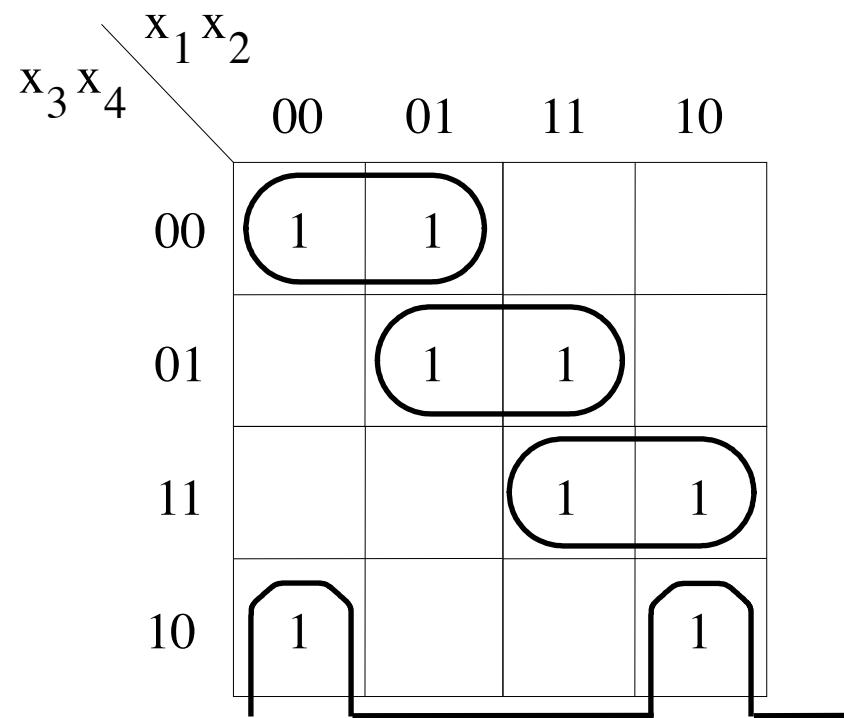

Example

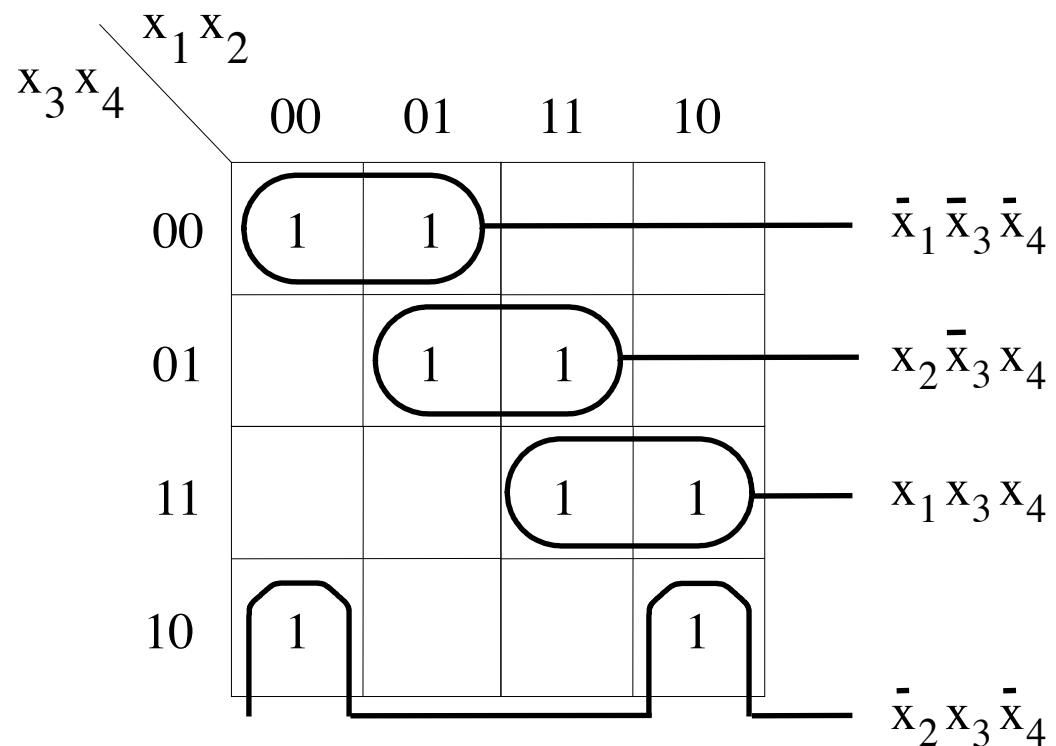

Example

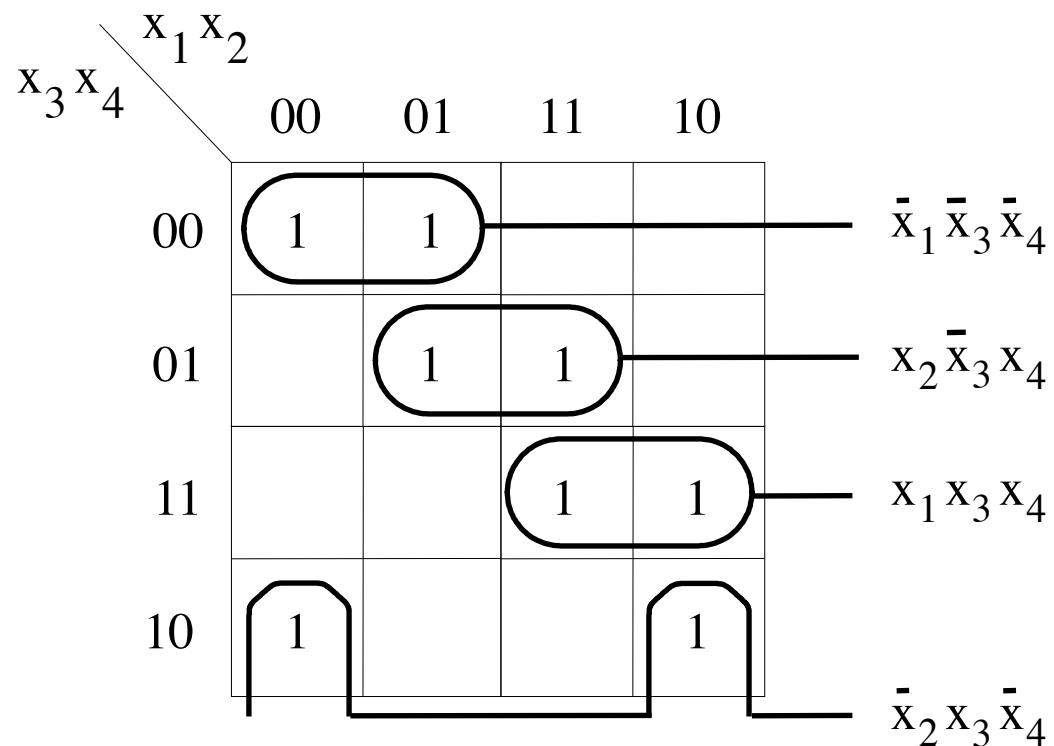


$$f = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_2 \bar{x}_3 x_4 + x_1 x_3 x_4 + \bar{x}_2 x_3 \bar{x}_4$$

Example: Another Solution


		x_1	x_2		
		x_3	x_4		
		00	01	11	10
00		1	1		
01			1	1	
11				1	1
10		1			1

Example: Another Solution

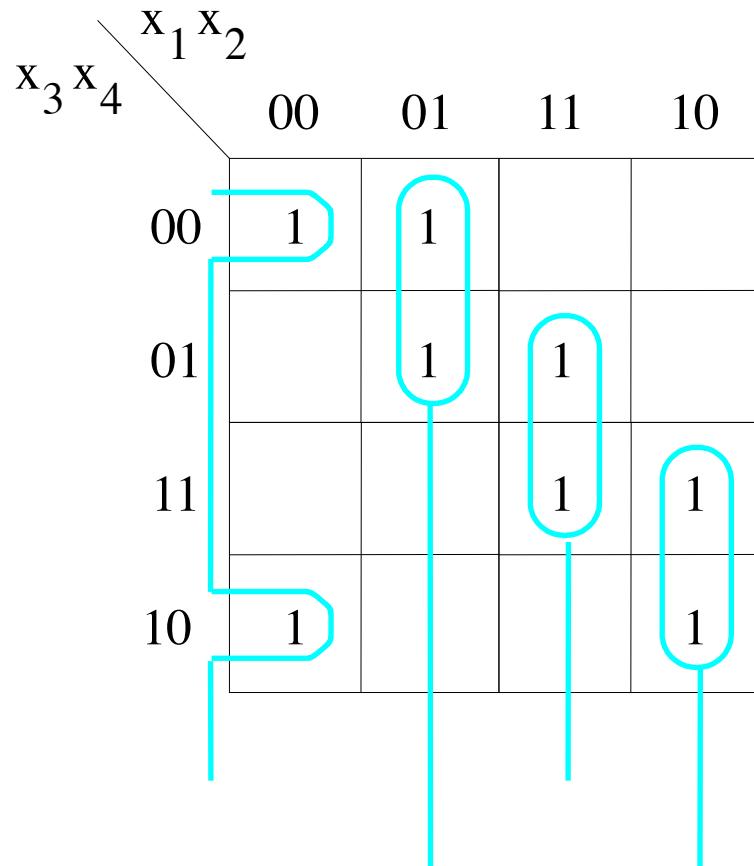


[Figure 2.59 from the textbook]

Example: Another Solution

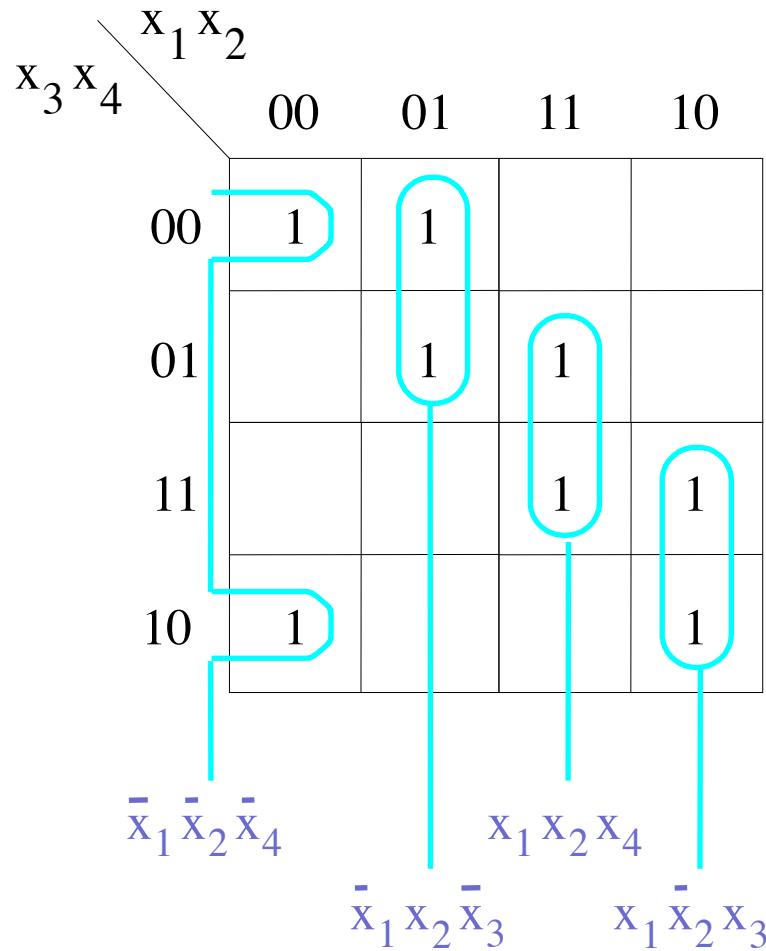


Example: Another Solution

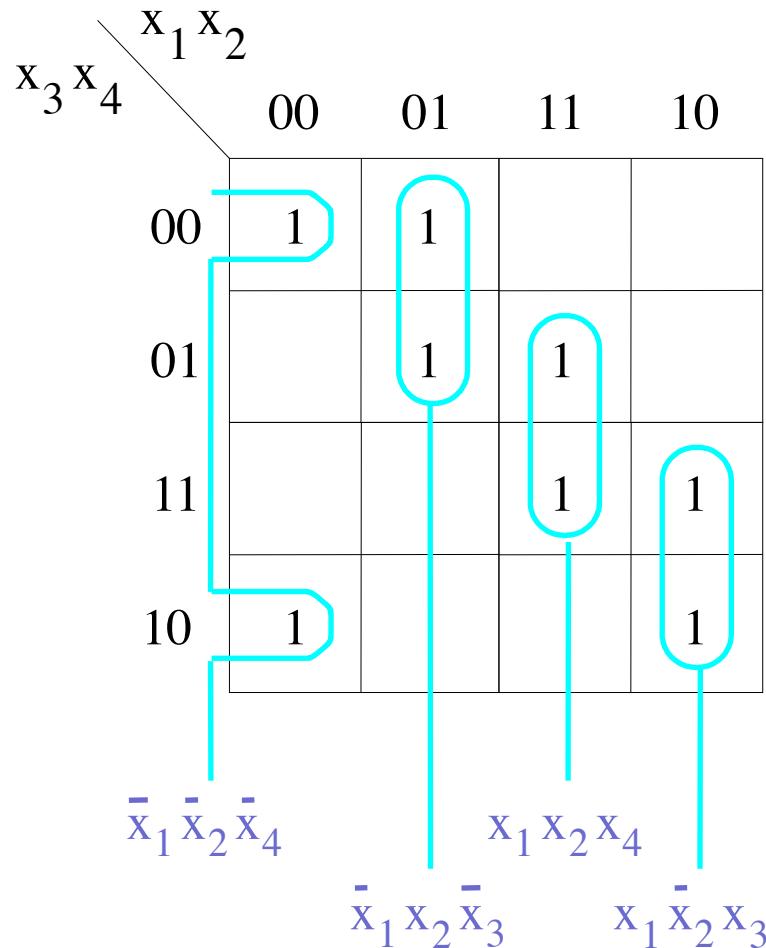


$$f = \bar{x}_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 x_2 \bar{x}_3 + x_1 x_2 x_4 + x_1 \bar{x}_2 x_3$$

Example: Both Are Valid Solutions

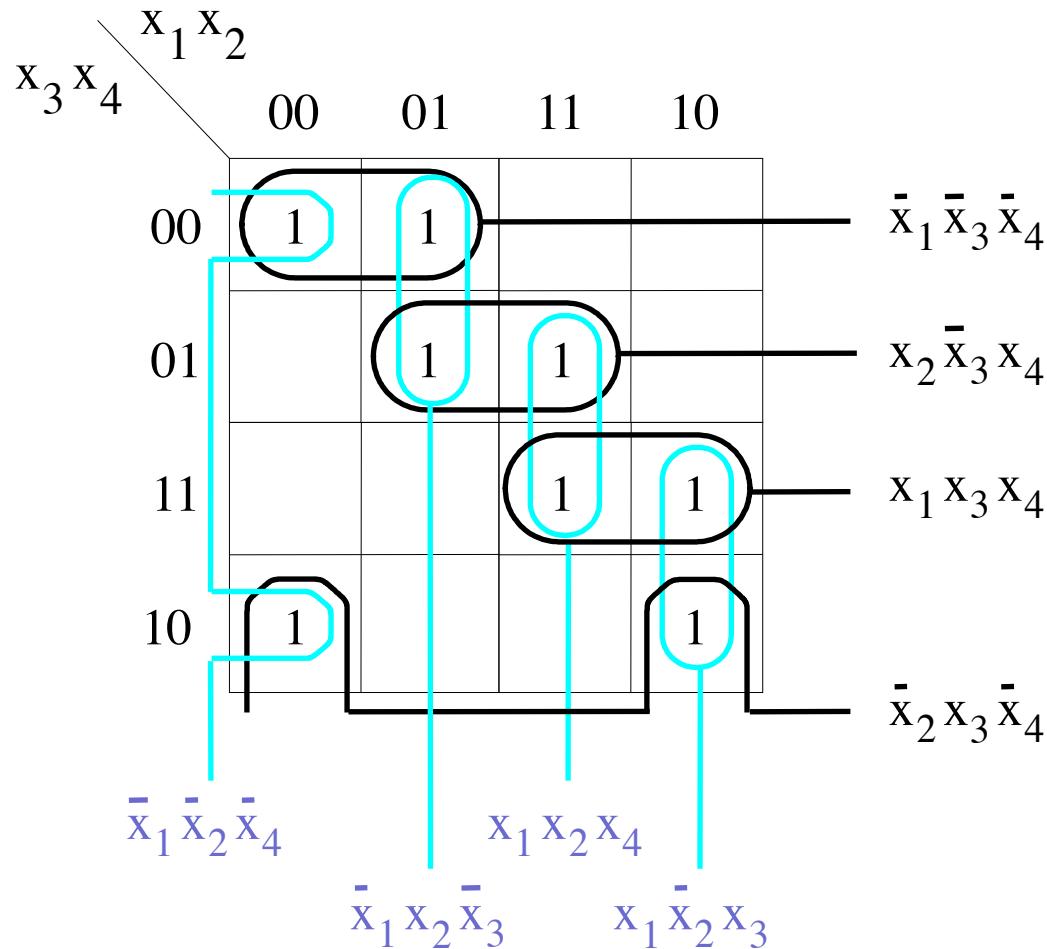

[Figure 2.59 from the textbook]

Example: Both Are Valid Solutions

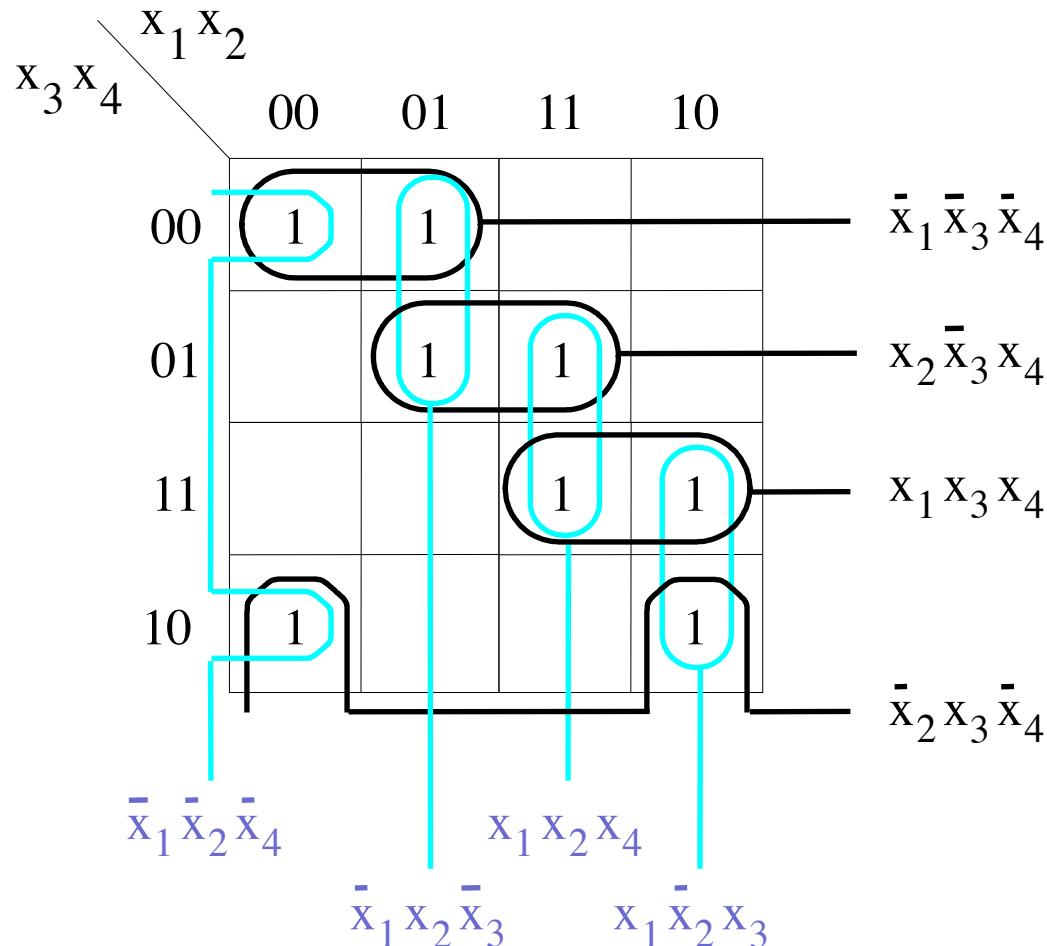

$$f = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_2 \bar{x}_3 x_4 + x_1 x_3 x_4 + \bar{x}_2 x_3 \bar{x}_4$$


$$f = \bar{x}_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 x_2 \bar{x}_3 + x_1 x_2 x_4 + x_1 \bar{x}_2 x_3$$

Example: Incompletely Specified Function

Three Ways to Specify the Function

$$f(x_1, x_2, x_3, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

x_1	x_2	x_3	x_4	f
0	0	0	0	m_0
0	0	0	1	m_1
0	0	1	0	m_2
0	0	1	1	m_3
0	1	0	0	m_4
0	1	0	1	m_5
0	1	1	0	m_6
0	1	1	1	m_7
1	0	0	0	m_8
1	0	0	1	m_9
1	0	1	0	m_{10}
1	0	1	1	m_{11}
1	1	0	0	m_{12}
1	1	0	1	m_{13}
1	1	1	0	m_{14}
1	1	1	1	m_{15}

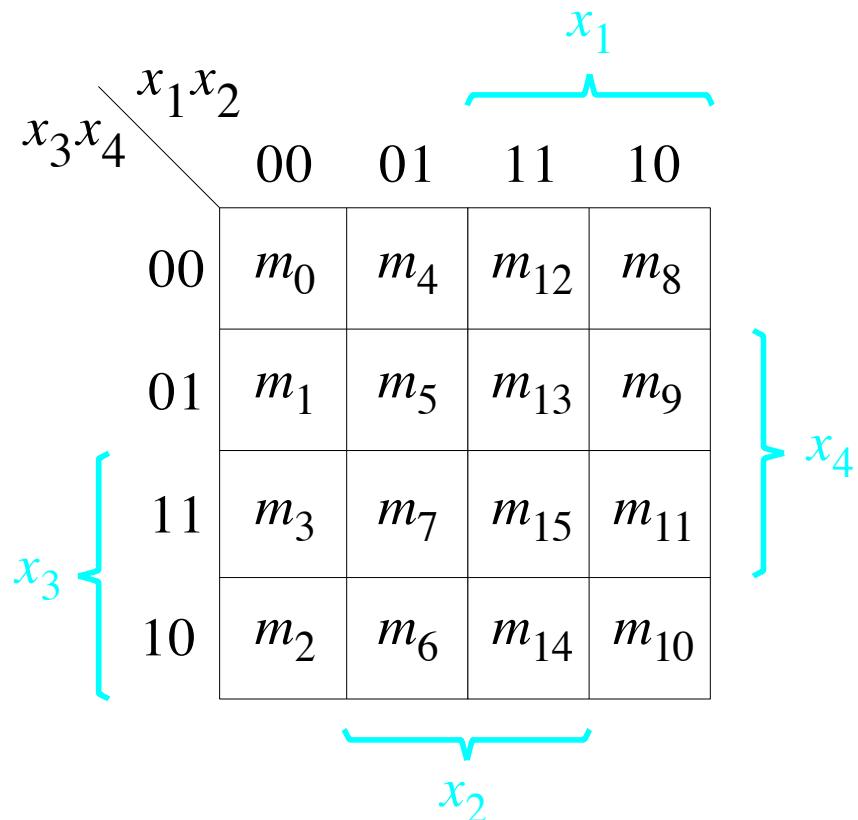


Three Ways to Specify the Function

$$f(x_1, x_2, x_3, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

x_1	x_2	x_3	x_4	f
0	0	0	0	m_0
0	0	0	1	m_1
0	0	1	0	m_2
0	0	1	1	m_3
0	1	0	0	m_4
0	1	0	1	m_5
0	1	1	0	m_6
0	1	1	1	m_7
1	0	0	0	m_8
1	0	0	1	m_9
1	0	1	0	m_{10}
1	0	1	1	m_{11}
1	1	0	0	m_{12}
1	1	0	1	m_{13}
1	1	1	0	m_{14}
1	1	1	1	m_{15}

x_3	x_4	x_1	x_2
00	01	11	10
0	1	d	0
0	1	d	0
0	0	d	0
1	1	d	1


SOP implementation

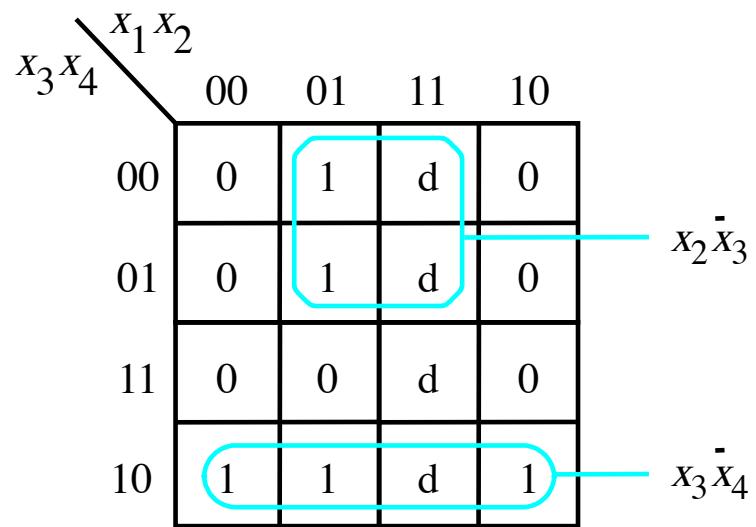

(a) SOP implementation

[Figure 2.62 from the textbook]

POS implementation

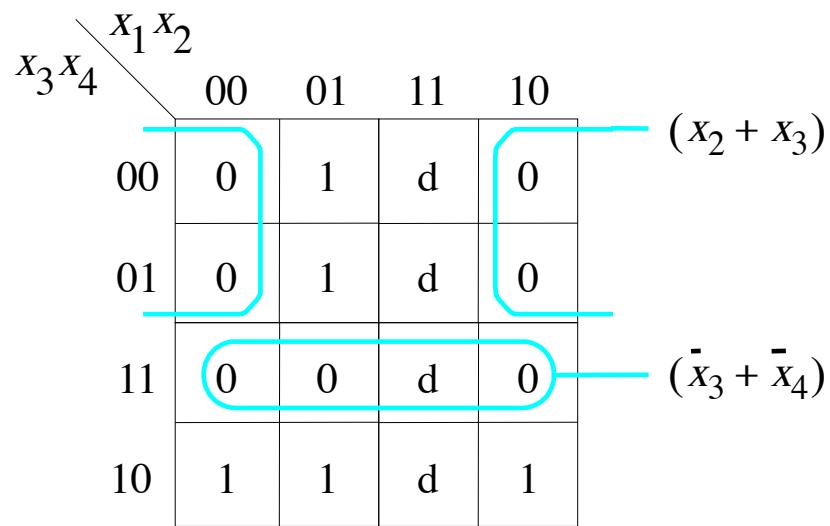


(b) POS implementation

[Figure 2.62 from the textbook]


Example:
A circuit with multiple outputs

Seven-Segment Indicator

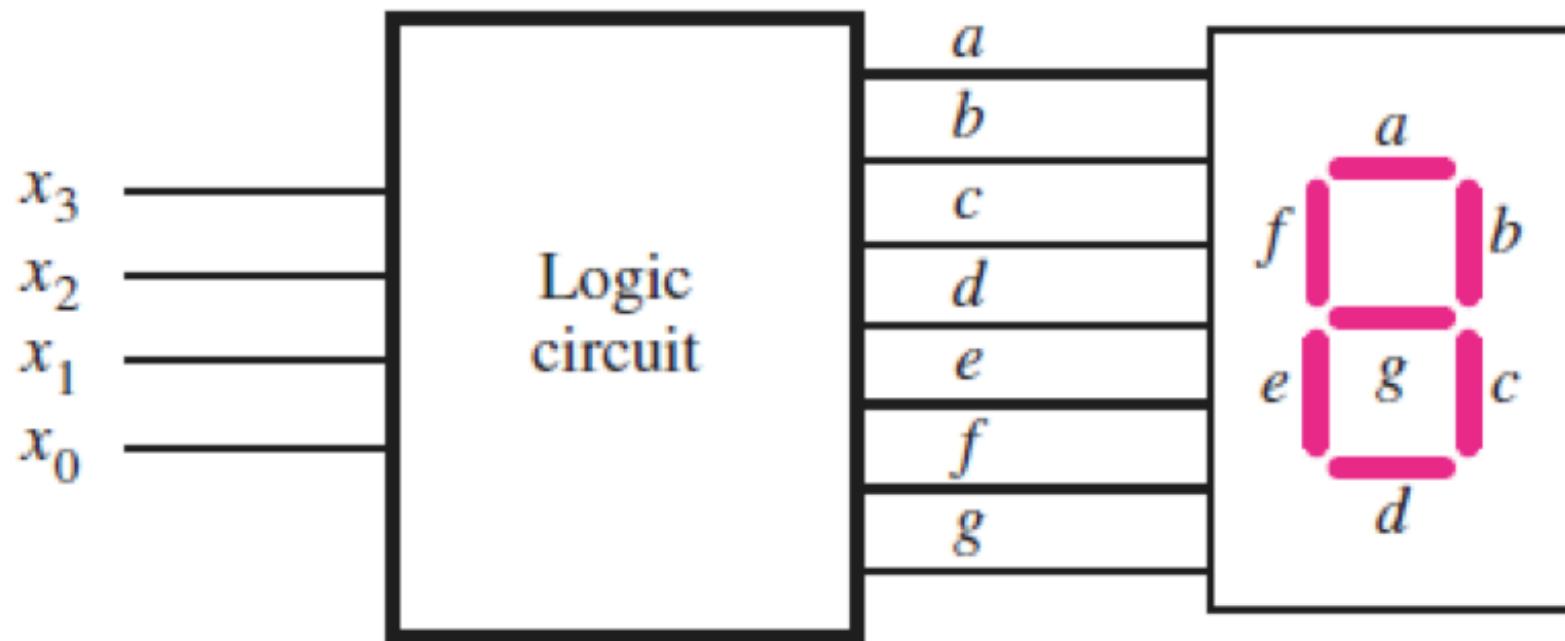

(a) Logic circuit and 7-segment display

Seven-Segment Indicator

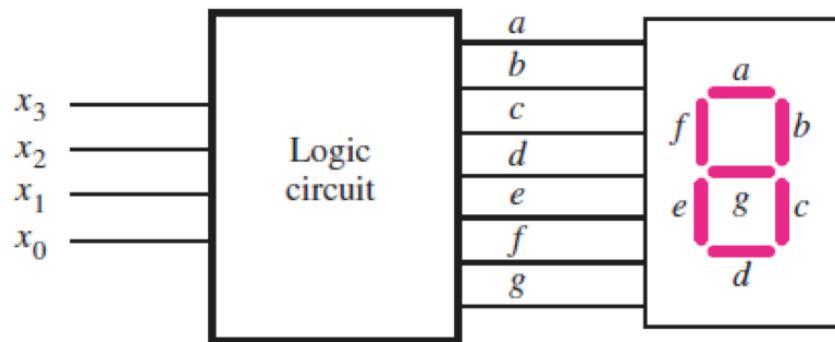

(a) Logic circuit and 7-segment display

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

(b) Truth table

Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	0	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
	1	0	1	0							
	1	0	1	1							
	1	1	0	0							
	1	1	0	1							
	1	1	1	0							
	1	1	1	1							

Seven-Segment Indicator



	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	0	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
	1	0	1	0	d	d	d	d	d	d	d
	1	0	1	1	d	d	d	d	d	d	d
	1	1	0	0	d	d	d	d	d	d	d
	1	1	0	1	d	d	d	d	d	d	d
	1	1	1	0	d	d	d	d	d	d	d
	1	1	1	1	d	d	d	d	d	d	d

Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	0	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	1	1	1
	1	0	1	0	d	d	d	d	d	d	d
	1	0	1	1	d	d	d	d	d	d	d
	1	1	0	0	d	d	d	d	d	d	d
	1	1	0	1	d	d	d	d	d	d	d
	1	1	1	0	d	d	d	d	d	d	d
	1	1	1	1	d	d	d	d	d	d	d



Seven-Segment Indicator

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	0	1	1	0	0	0	0
2	0	0	1	1	1	0	1	1	0	1
3	0	0	1	1	1	1	0	0	0	1
4	0	1	0	0	1	1	0	0	1	1
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	0	1	1	1	1	1
7	0	1	1	1	1	0	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	0	1	1	1
	1	0	1	0	d	d	d	d	d	d
	1	0	1	1	d	d	d	d	d	d
	1	1	0	0	d	d	d	d	d	d
	1	1	0	1	d	d	d	d	d	d
	1	1	1	0	d	d	d	d	d	d
	1	1	1	1	d	d	d	d	d	d

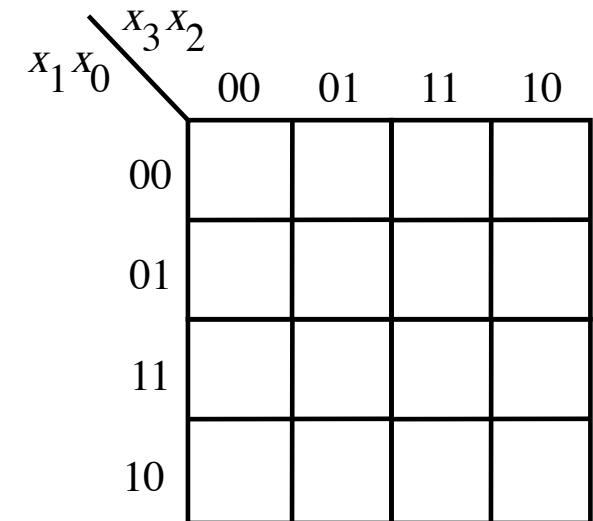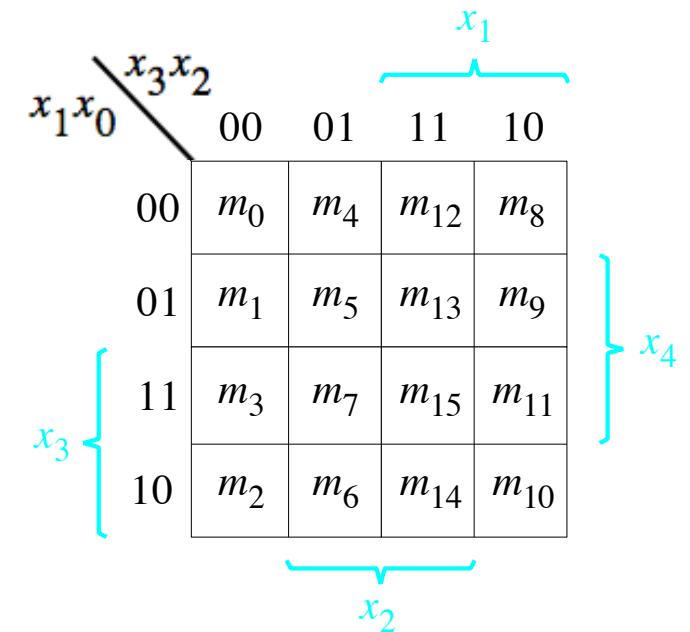



Seven-Segment Indicator

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	0	1	1	0	1
3	0	0	1	1	1	1	0	0	0	1
4	0	1	0	0	1	1	0	0	1	1
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	0	1	1	1	1	1
7	0	1	1	1	1	0	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	0	1	1	1
	1	0	1	0	d	d	d	d	d	d
	1	0	1	1	d	d	d	d	d	d
	1	1	0	0	d	d	d	d	d	d
	1	1	0	1	d	d	d	d	d	d
	1	1	1	0	d	d	d	d	d	d
	1	1	1	1	d	d	d	d	d	d

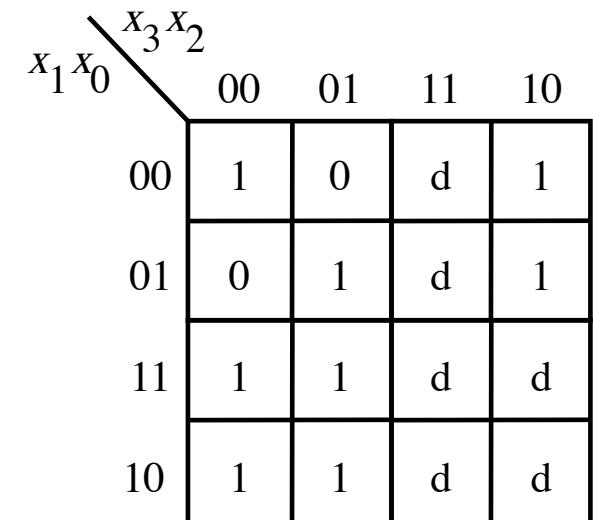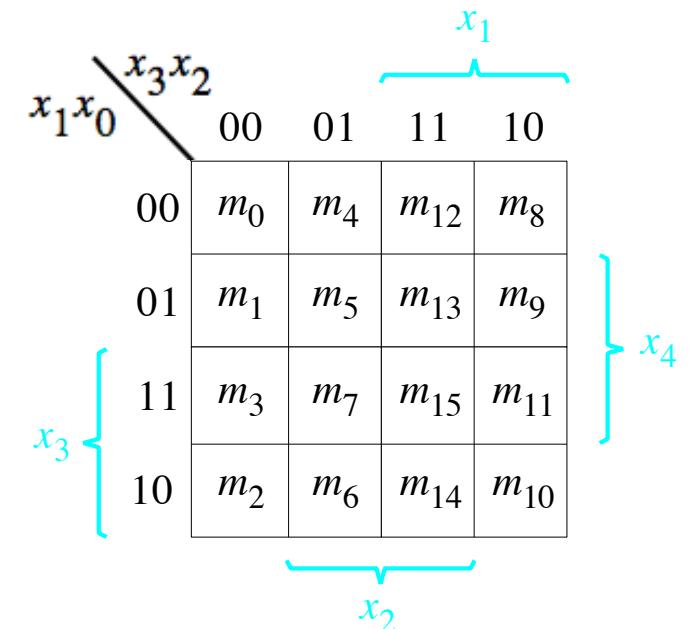



Seven-Segment Indicator

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	0	1	1	0	0	0	0
2	0	0	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	0	0	0	1
4	0	0	1	1	1	1	1	0	0	1
5	0	1	0	0	1	1	0	0	1	1
6	0	1	0	1	0	1	1	0	1	1
7	0	1	0	1	0	1	1	1	1	1
8	0	1	1	1	1	0	0	0	0	0
9	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	0	1	1	1
d	1	0	1	0	d	d	d	d	d	d
d	1	0	1	1	d	d	d	d	d	d
d	1	1	0	0	d	d	d	d	d	d
d	1	1	0	1	d	d	d	d	d	d
d	1	1	1	0	d	d	d	d	d	d
d	1	1	1	0	d	d	d	d	d	d
d	1	1	1	1	d	d	d	d	d	d

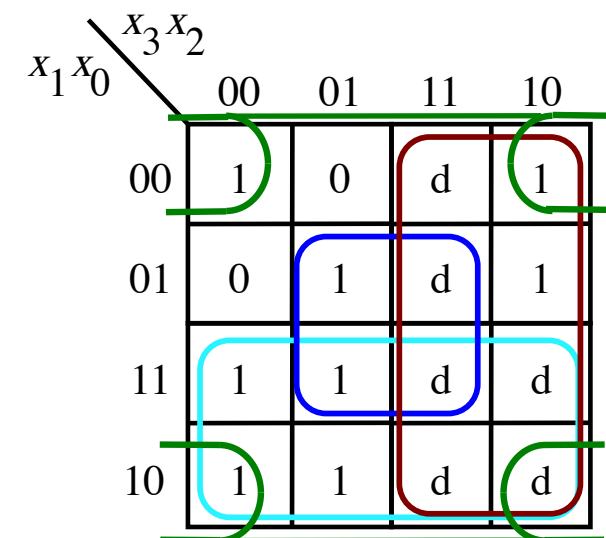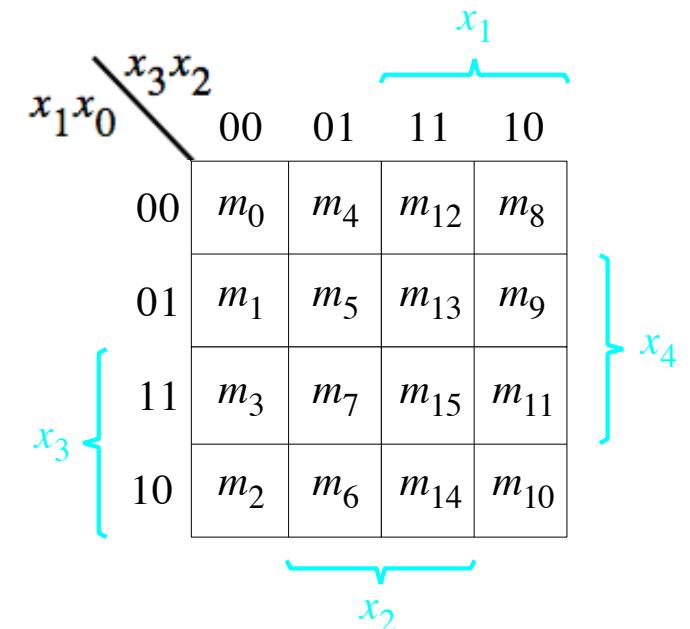

Seven-Segment Indicator

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	0	1	1	0	0	0	0
2	0	0	1	1	1	0	1	1	0	1
3	0	0	1	1	1	1	0	0	0	1
4	0	1	0	0	1	1	0	0	1	1
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	0	1	1	1	1	1
7	0	1	1	1	1	0	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	0	1	1	1
1	0	1	0	1	d	d	d	d	d	d
1	0	1	1	1	d	d	d	d	d	d
1	1	0	0	1	d	d	d	d	d	d
1	1	0	1	1	d	d	d	d	d	d
1	1	1	0	1	d	d	d	d	d	d
1	1	1	1	1	d	d	d	d	d	d

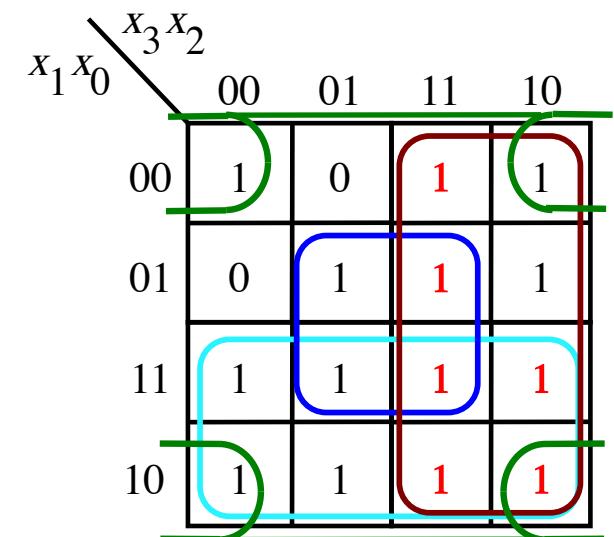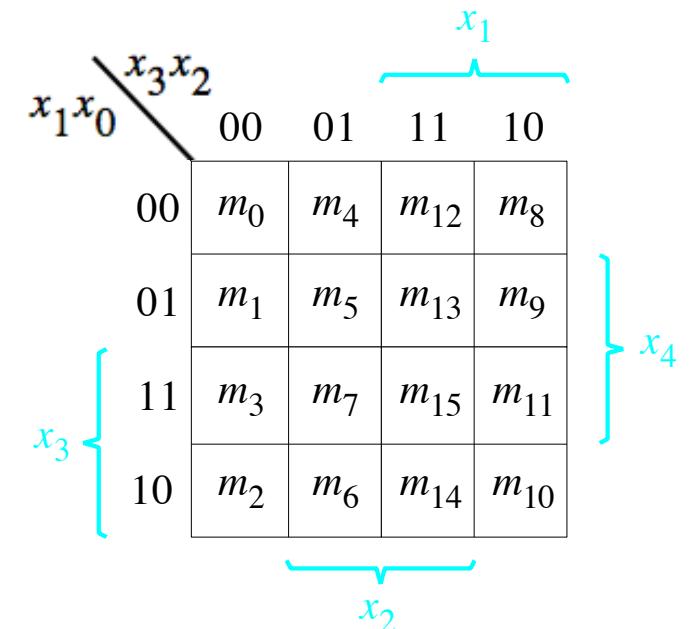



In this case all d's were treated as 1's.

Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
	1	0	1	0	1	d	d	d	d	d	d
	1	0	1	1	1	d	d	d	d	d	d
	1	1	0	0	1	d	d	d	d	d	d
	1	1	0	1	1	d	d	d	d	d	d
	1	1	1	0	1	d	d	d	d	d	d
	1	1	1	1	1	d	d	d	d	d	d



Seven-Segment Indicator

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	0	1
3	0	0	1	1	1	1	1	0	0	1
4	0	1	0	0	1	1	0	0	1	1
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1
7	0	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	1	1
	1	0	1	0	1	d	d	d	d	d
	1	0	1	1	1	d	d	d	d	d
	1	1	0	0	1	d	d	d	d	d
	1	1	0	1	1	d	d	d	d	d
	1	1	1	0	1	d	d	d	d	d
	1	1	1	1	1	d	d	d	d	d

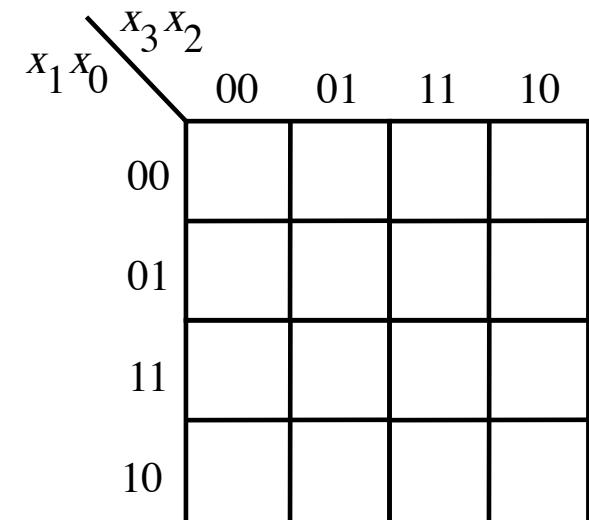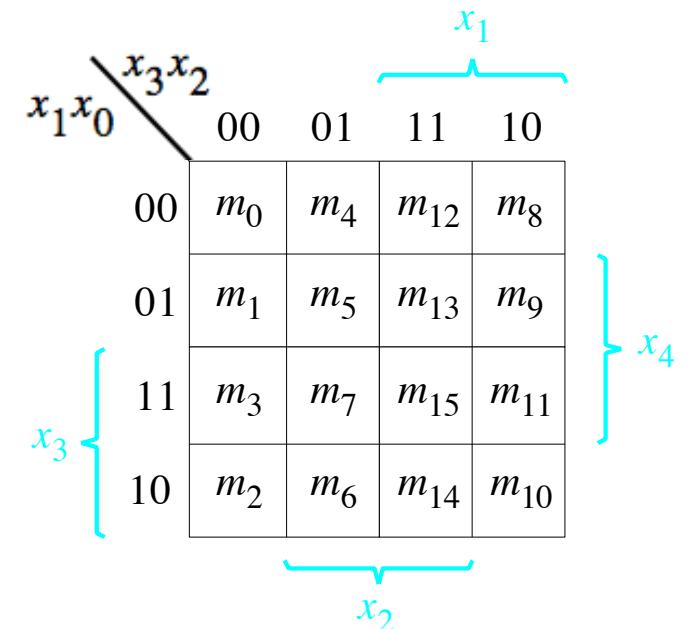



Seven-Segment Indicator

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	0	1
3	0	0	1	1	1	1	1	0	0	1
4	0	1	0	0	1	1	0	0	1	1
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1
7	0	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	1	1
	1	0	1	0	1	d	d	d	d	d
	1	0	1	1	1	d	d	d	d	d
	1	1	0	0	1	d	d	d	d	d
	1	1	0	1	1	d	d	d	d	d
	1	1	1	0	1	d	d	d	d	d
	1	1	1	1	1	d	d	d	d	d

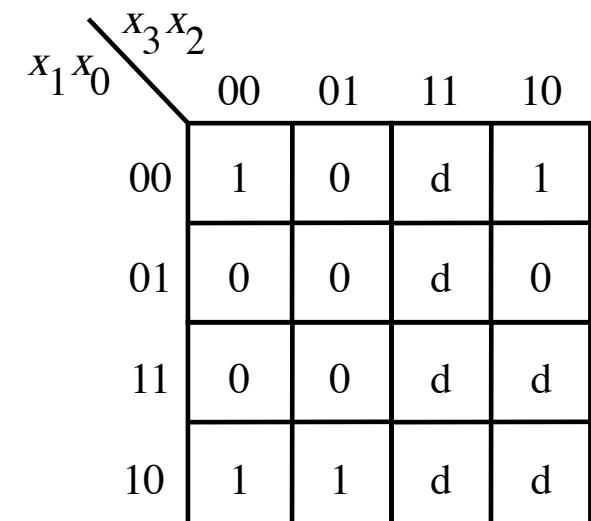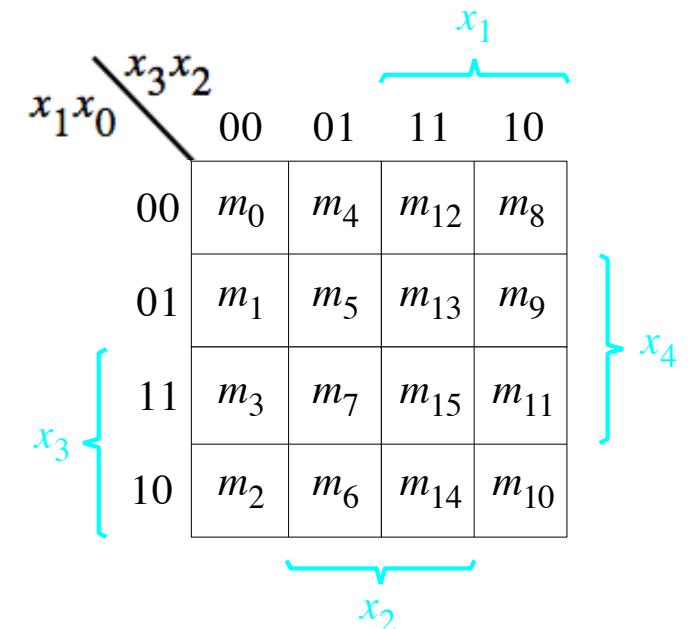



Seven-Segment Indicator

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	0	1
3	0	0	1	1	1	1	1	0	0	1
4	0	1	0	0	1	1	0	0	1	1
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1
7	0	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	1	1
	1	0	1	0	1	d	d	d	d	d
	1	0	1	1	1	d	d	d	d	d
	1	1	0	0	1	d	d	d	d	d
	1	1	0	1	1	d	d	d	d	d
	1	1	1	0	1	d	d	d	d	d
	1	1	1	1	1	d	d	d	d	d

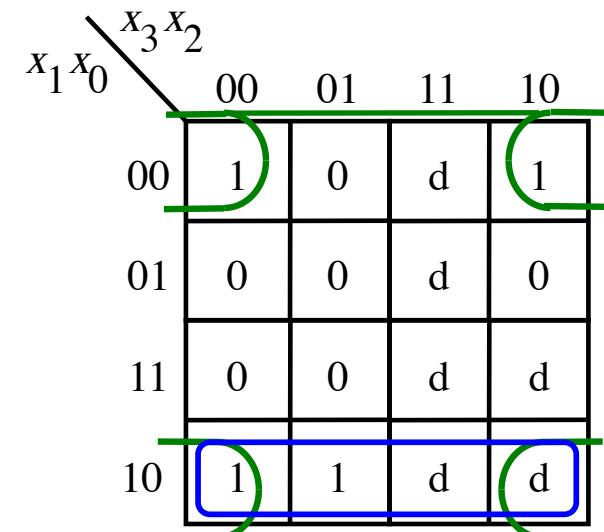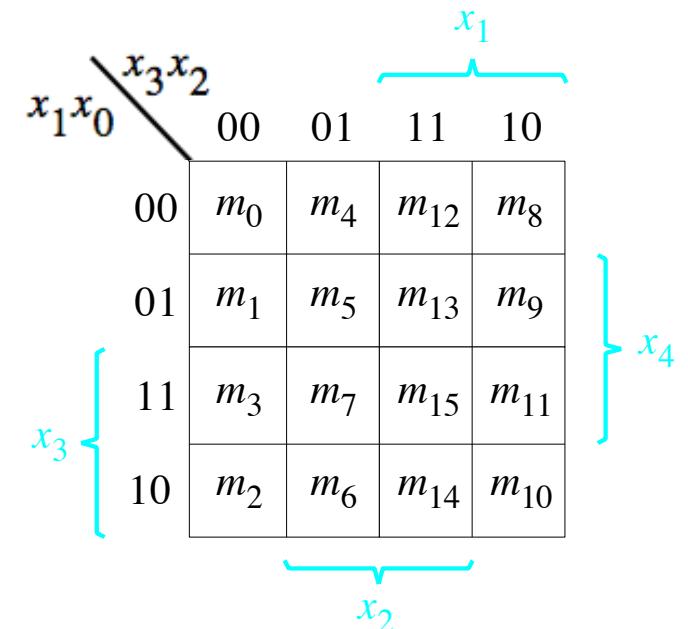

Seven-Segment Indicator

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	0	1
3	0	0	1	1	1	1	1	0	0	1
4	0	1	0	0	1	1	0	0	1	1
5	0	1	0	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1
7	0	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	1	1
	1	0	1	0	1	d	d	1	d	d
	1	0	1	1	1	d	d	0	d	d
	1	1	0	0	1	d	d	0	d	d
	1	1	0	1	1	d	d	0	d	d
	1	1	1	0	1	d	d	1	d	d
	1	1	1	1	1	d	d	0	d	d

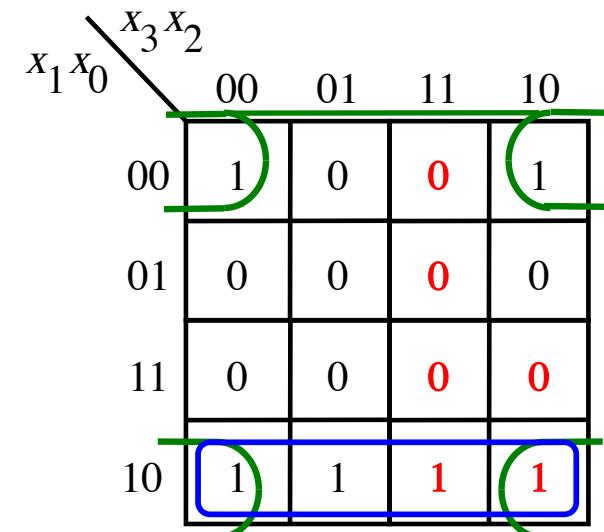
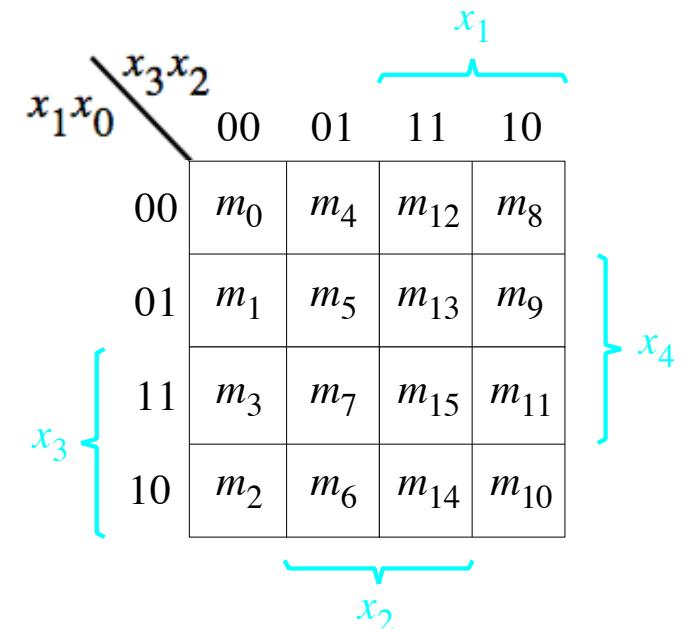


In this case some d's were treated as 1's, others as 0's.

Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

(b) Truth table

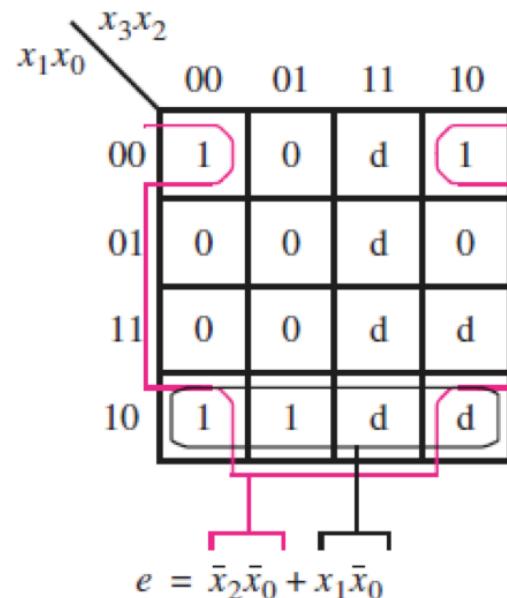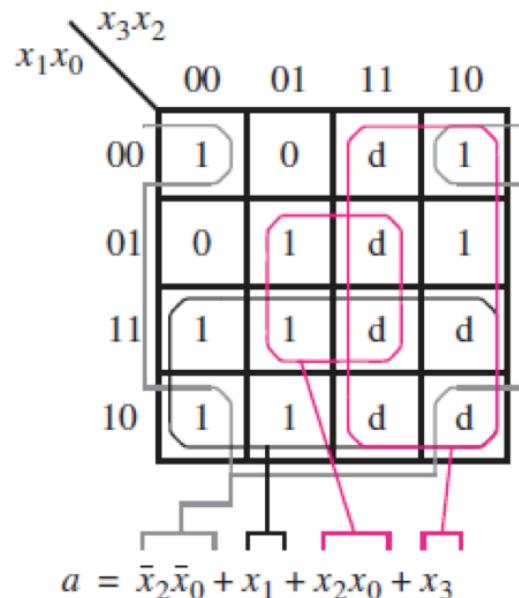

(c) The Karnaugh maps for outputs a and e .

Another Example

x_3	x_4	x_1	x_2
00	01	11	10
00			
01	1	1	1
11	1	1	
10	1	1	

(a) Function f_1

x_3	x_4	x_1	x_2
00	01	11	10
00			
01	1	1	1
11	1	1	1
10	1	1	

(b) Function f_2

[Figure 2.64 from the textbook]

$x_3 x_4$	$x_1 x_2$	00	01	11	10
00				1	1
01		1	1		1
11		1	1		
10		1	1		

(a) Function f_1

$x_3 x_4$	$x_1 x_2$	00	01	11	10
00				1	1
01				1	1
11		1	1		1
10		1	1		

(b) Function f_2

$x_3 x_4$	$x_1 x_2$	00	01	11	10
00				1	1
01		1	1		1
11		1	1		
10		1	1		

(a) Function f_1

$x_3 x_4$	$x_1 x_2$	00	01	11	10
00				1	1
01				1	1
11		1	1		1
10		1	1		

(b) Function f_2

$\overline{x_1} \ X_3$

$x_3 \ x_4$	$x_1 \ x_2$	00	01	11	10
00				1	1
01		1	1		1
11		1	1		
10		1	1		

(a) Function f_1

$\overline{x_1} \ x_3$

$x_3 \ x_4$	$x_1 \ x_2$	00	01	11	10
00				1	1
01				1	1
11		1	1		1
10		1	1		

(b) Function f_2

$x_3 \backslash x_4$	00	01	11	10
00	0	0	1	1
01	1	1	1	0
11	1	1	0	0
10	1	1	0	0


(a) Function f_1

$\overline{x_1} \ x_3$

$x_3 \backslash x_4$	00	01	11	10
00	0	0	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	0	0


(b) Function f_2

$\overline{x_1} \ x_3$

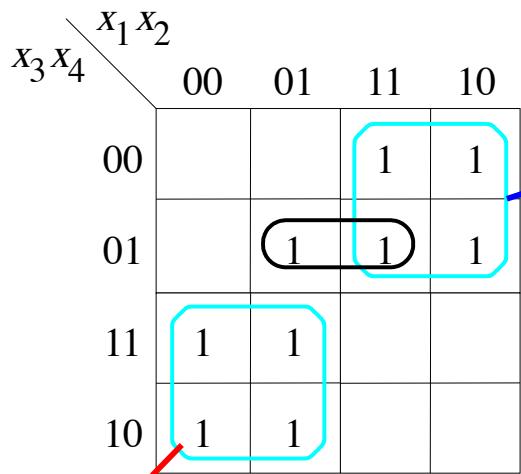

(a) Function f_1

$\overline{x_1} \quad x_3$

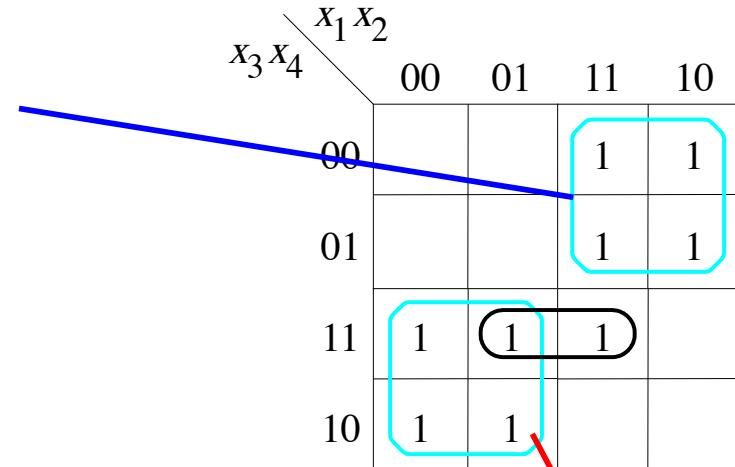

(b) Function f_2

$\overline{x_1} \quad x_3$

$x_3 x_4$	$x_1 x_2$	00	01	11	10
00					
01		1	1		
11		1	1		
10		1	1		

(a) Function f_1


$x_1 \bar{x}_3$

$x_3 x_4$	$x_1 x_2$	00	01	11	10
00					
01					
11		1	1	1	1
10		1	1		

(b) Function f_2

$\bar{x}_1 \bar{x}_3$


$\bar{x}_1 \bar{x}_3$

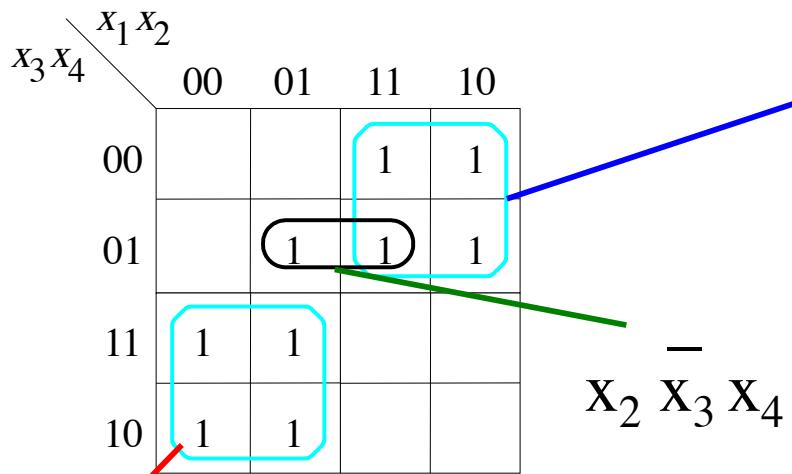

(a) Function f_1

$$\overline{x_1} \quad \overline{x_3}$$

$$x_2 \quad \overline{x_3} \quad x_4$$

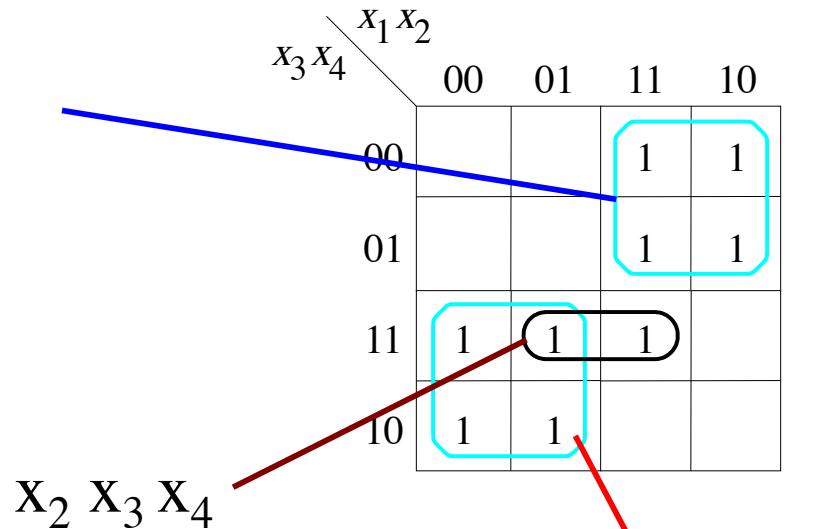


(b) Function f_2



$$\overline{x_2} \quad x_3 \quad x_4$$

$$\overline{x_1} \quad \overline{x_3}$$


$$\overline{x_1} \quad x_3$$

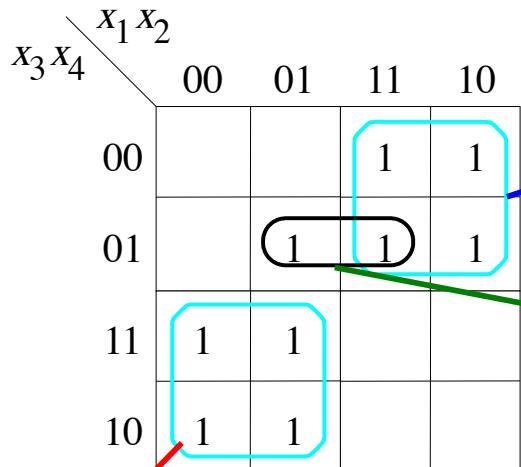


(a) Function f_1

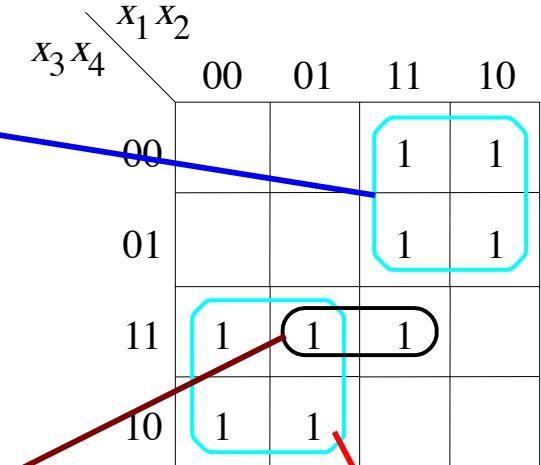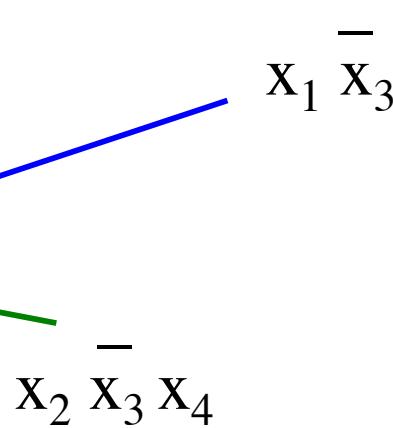



(b) Function f_2

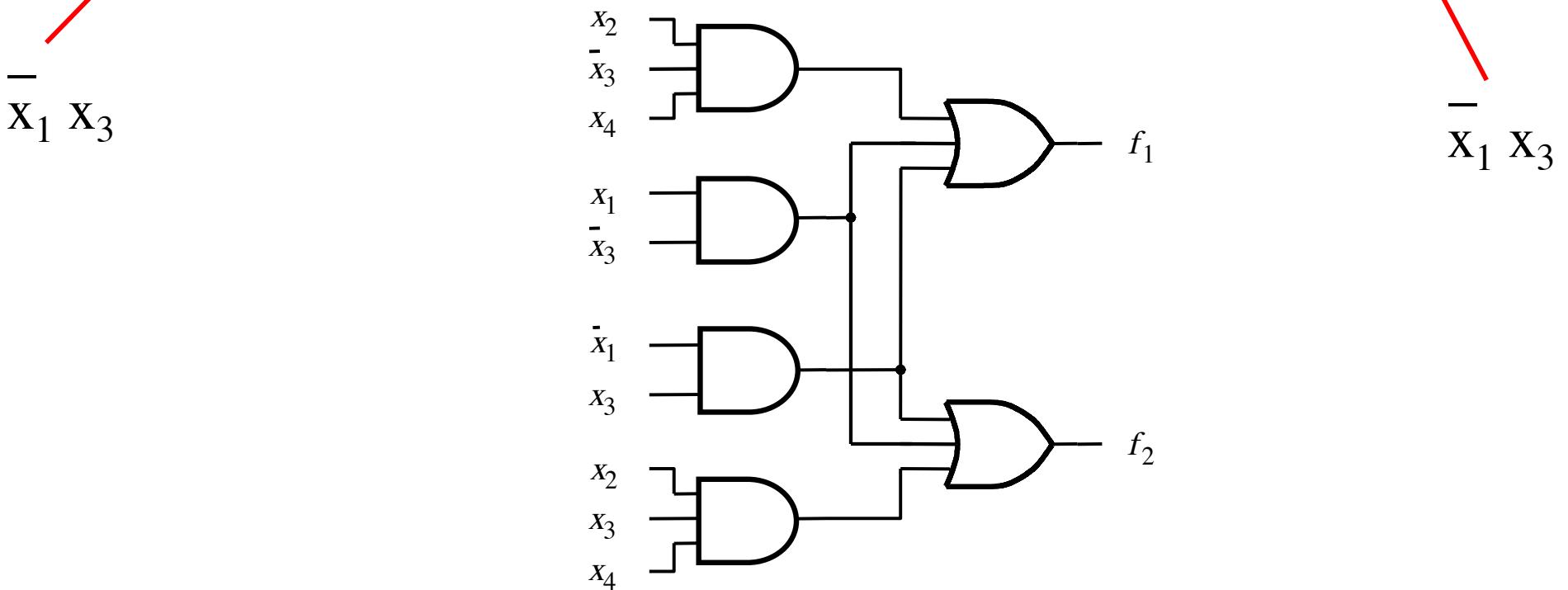


(c) Combined circuit for f_1 and f_2

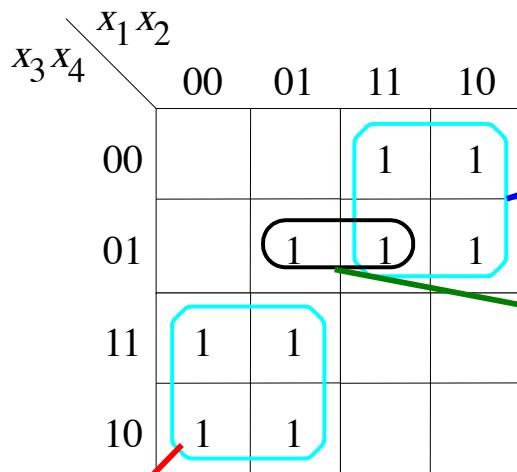


(a) Function f_1

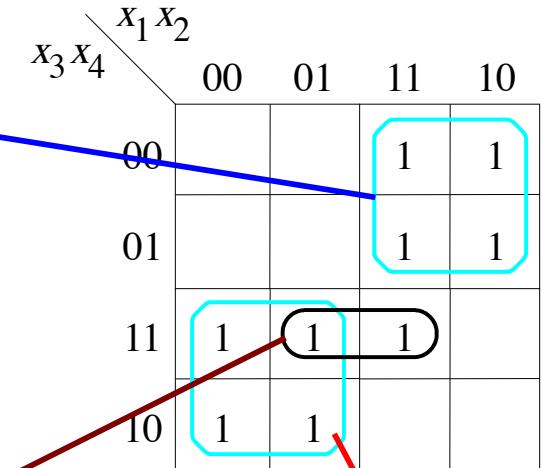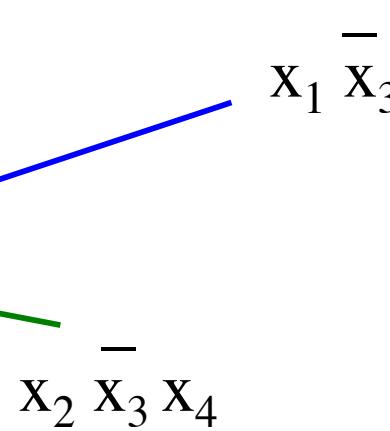

(b) Function f_2

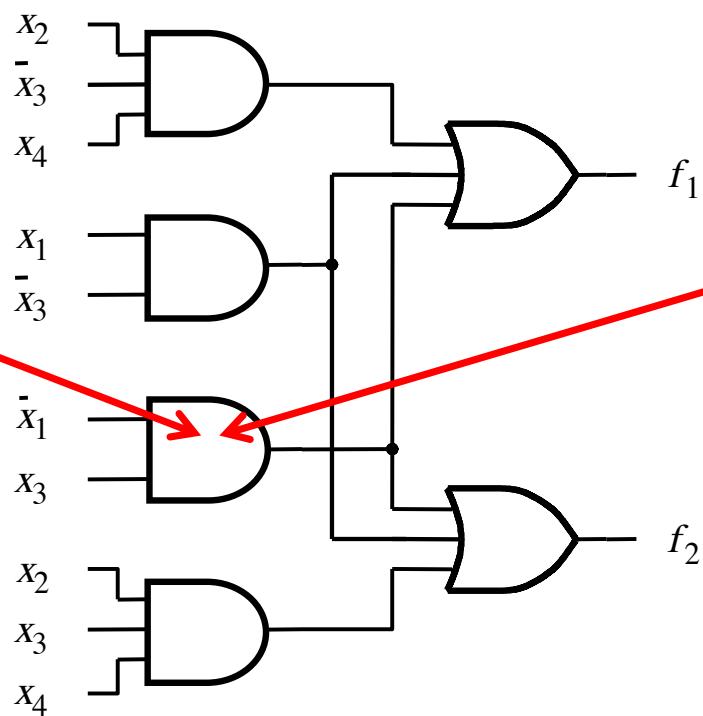


(c) Combined circuit for f_1 and f_2

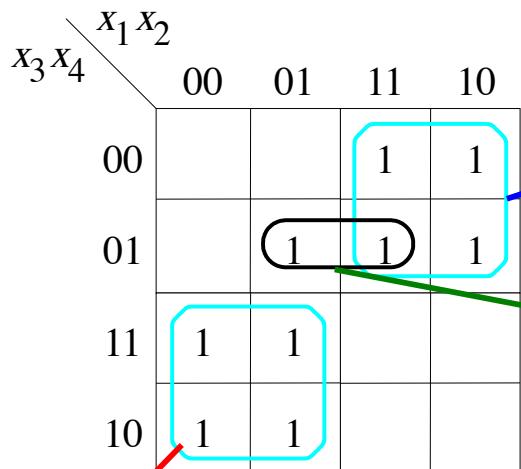


$\bar{x}_1 \bar{x}_3$


$x_2 \bar{x}_3 x_4$

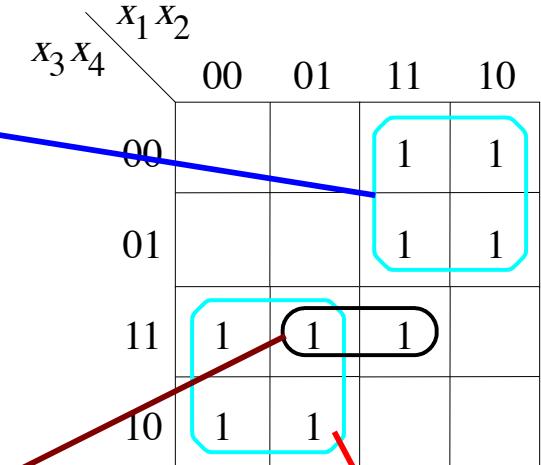


$x_2 x_3 x_4$

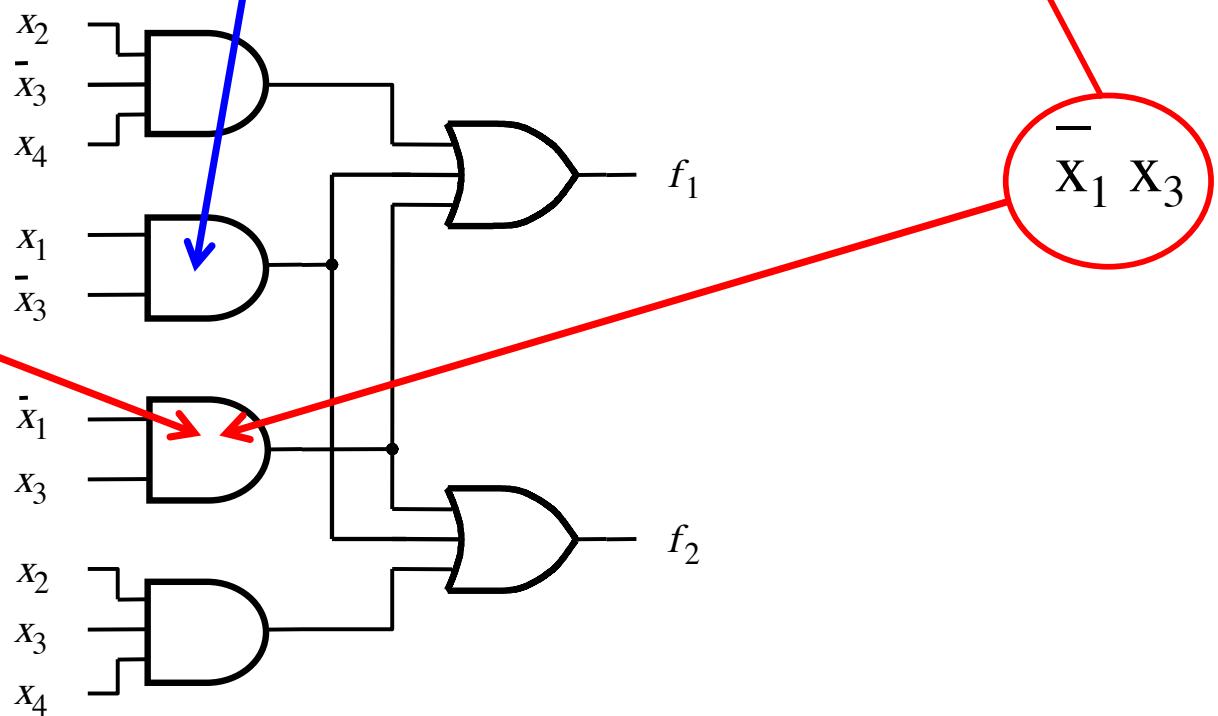


(c) Combined circuit for f_1 and f_2

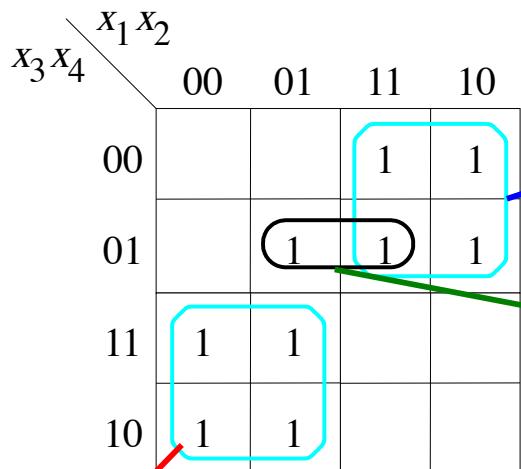





(a) Function f_1

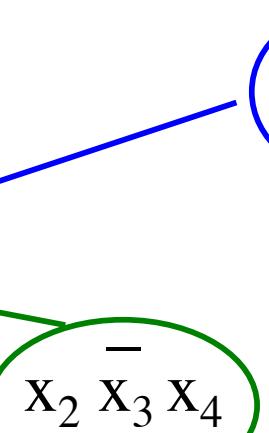


(b) Function f_2

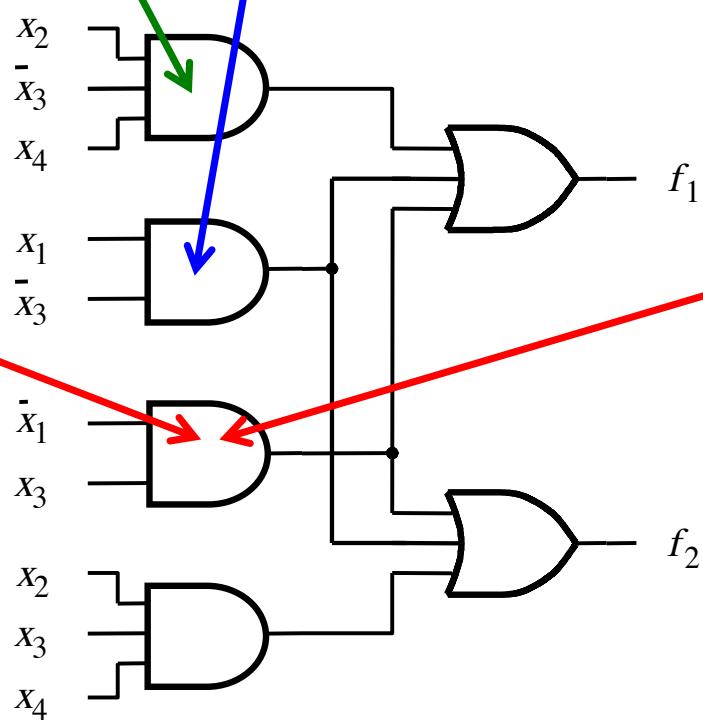


(c) Combined circuit for f_1 and f_2

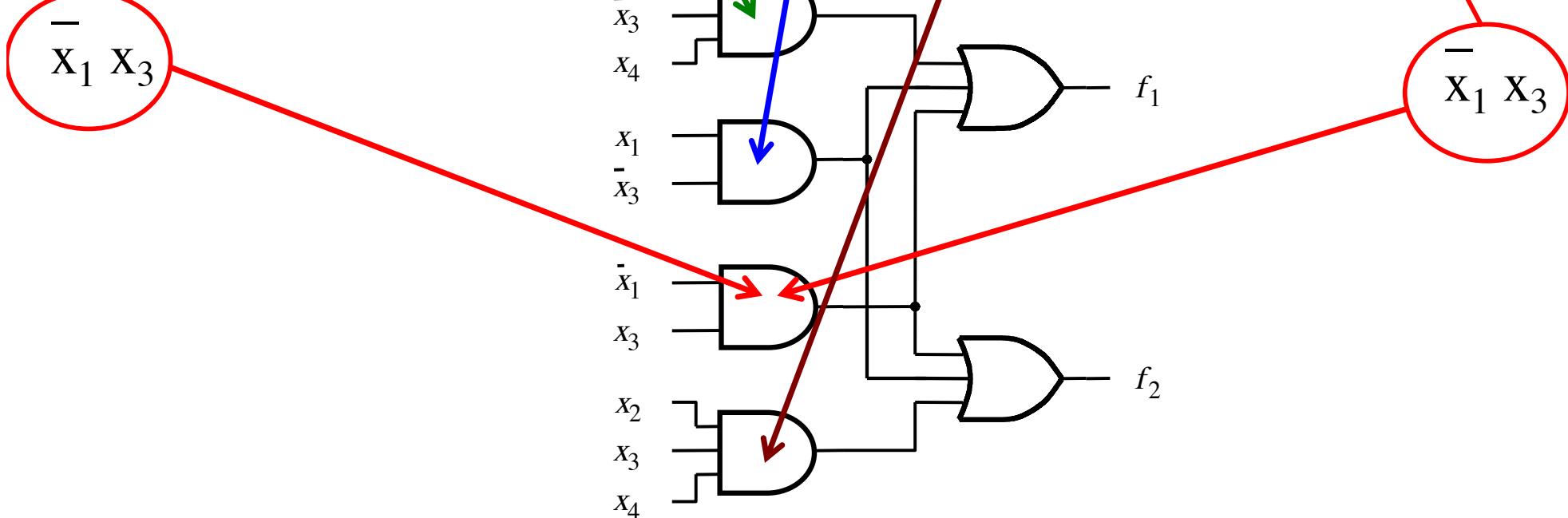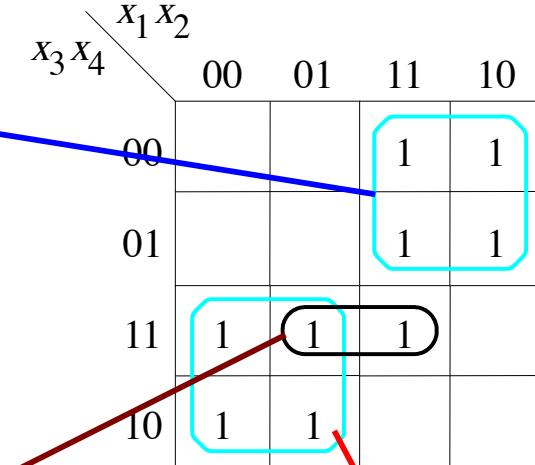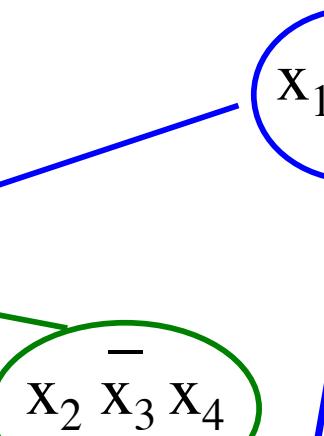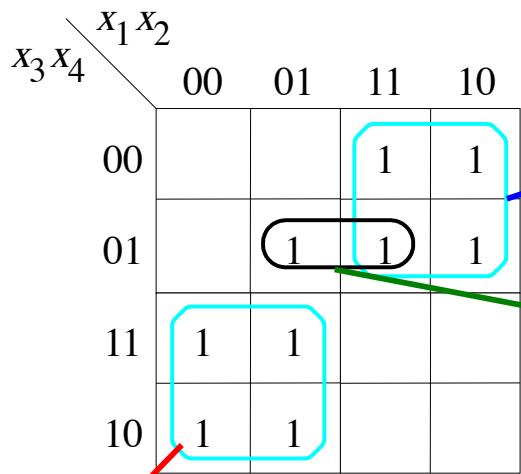


(c) Combined circuit for f_1 and f_2

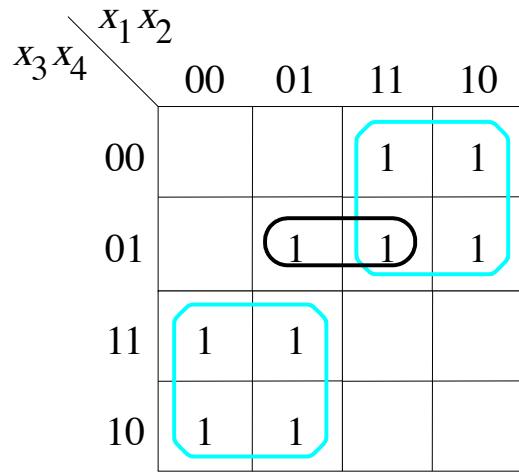

(a) Function f_1

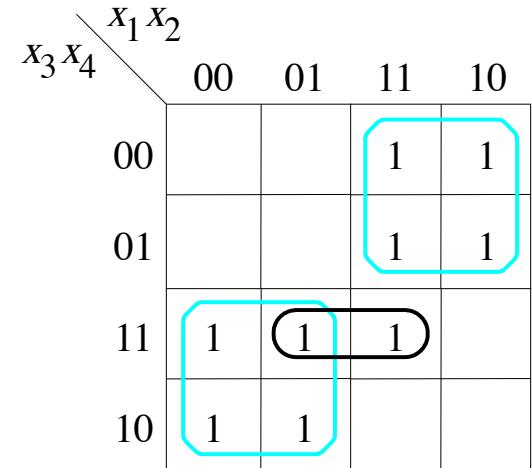

(b) Function f_2

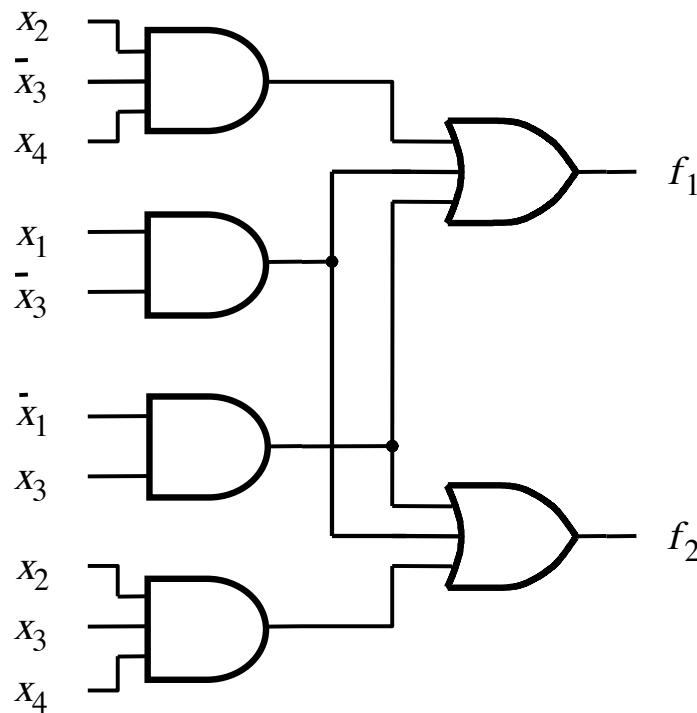


(c) Combined circuit for f_1 and f_2


[Figure 2.64 from the textbook]

Yet Another Example


Individual vs Joint Optimization

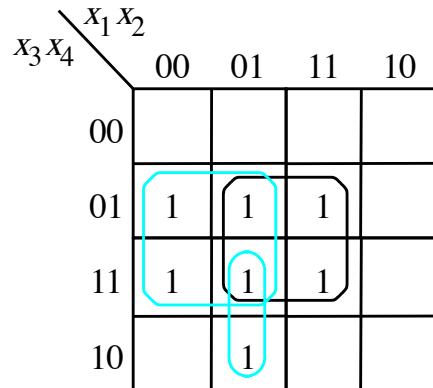


(a) Optimal realization of f_3

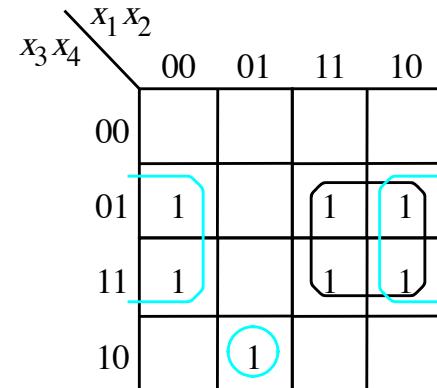

(b) Optimal realization of f_4

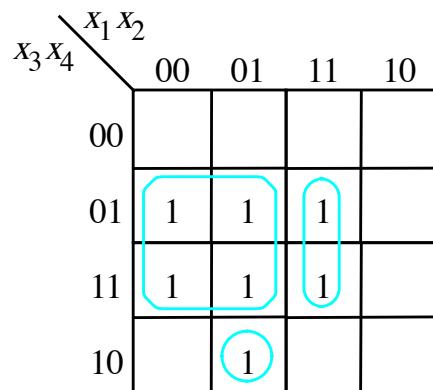

(c) Optimal realization of f_3 and f_4 together

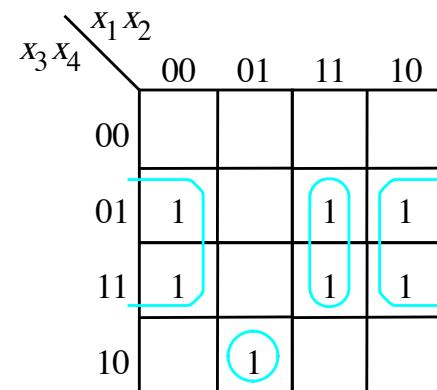


[Figure 2.65 from the textbook]

Individual vs Joint Optimization

$x_3 x_4$	00	01	11	10
00				
01	1	1	1	
11	1	1	1	
10		1		

$x_3 x_4$	00	01	11	10
00				
01	1			1
11	1		1	1
10		1		

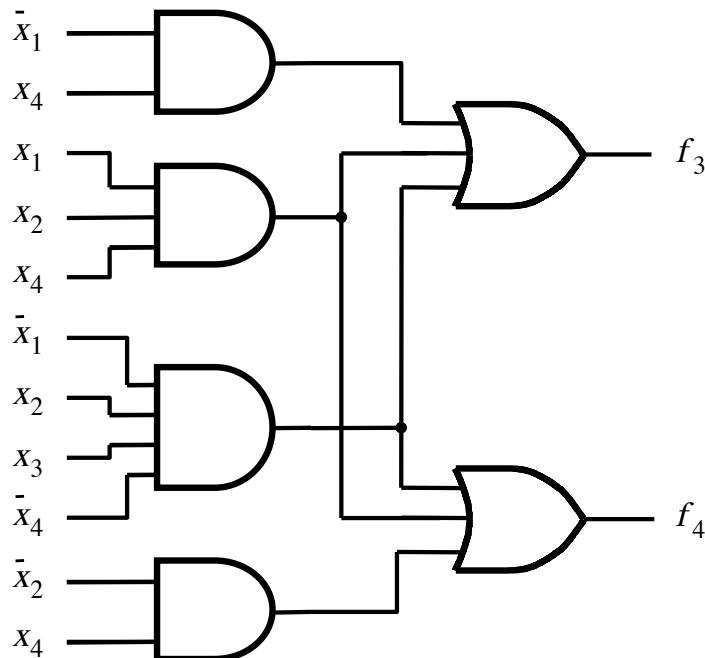(c) Optimal realization of f_3 and f_4 together



(d) Combined circuit for f_3 and f_4


[Figure 2.65 from the textbook]

Individual vs Joint Optimization

$x_3 \ x_4$	00	01	11	10
00				
01	1	1		1
11	1	1	1	
10		1		

$x_3 \ x_4$	00	01	11	10
00				
01	1			
11	1		1	1
10		1		

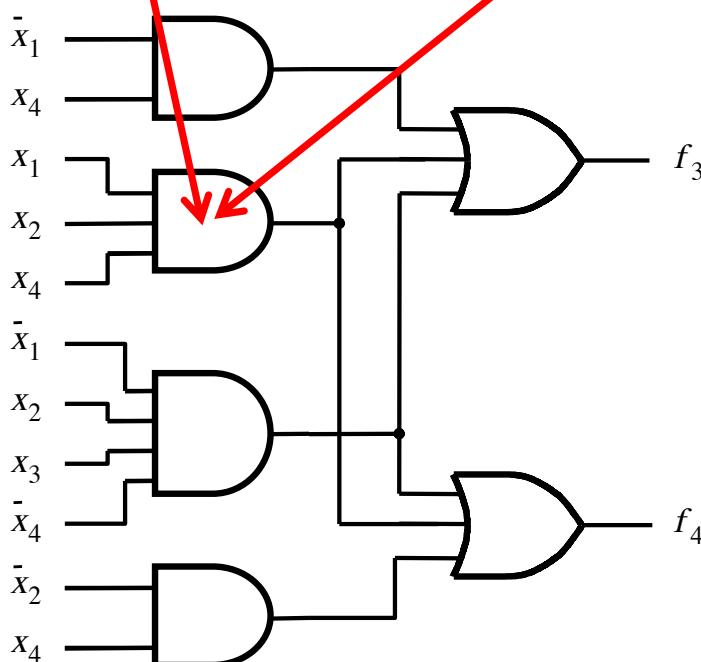(c) Optimal realization of f_3 and f_4 together



(d) Combined circuit for f_3 and f_4


[Figure 2.65 from the textbook]

Individual vs Joint Optimization

$x_3 \ x_4$	00	01	11	10
00				
01	1	1		1
11	1	1	1	
10		1		

$x_3 \ x_4$	00	01	11	10
00				
01		1		
11	1		1	1
10		1		

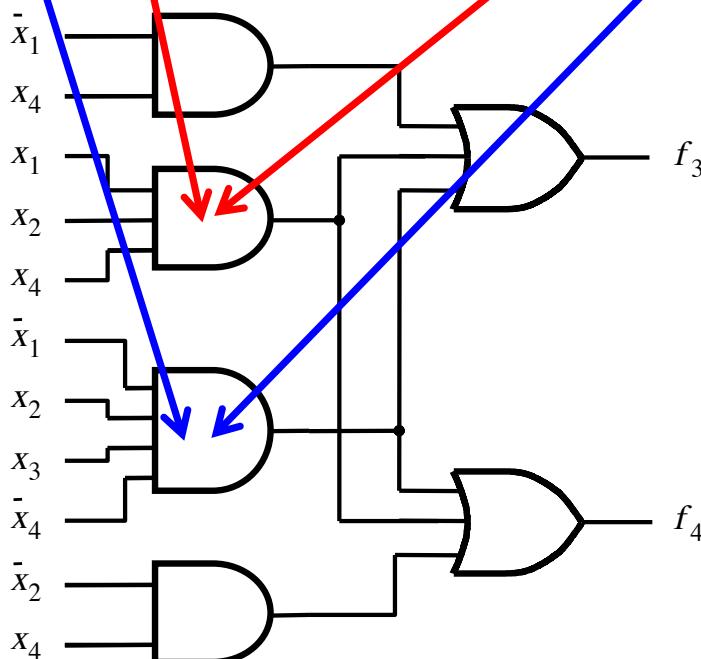(c) Optimal realization of f_3 and f_4 together



(d) Combined circuit for f_3 and f_4

[Figure 2.65 from the textbook]

Questions?

THE END