

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Code Converters

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW 7 is out**
- **It is due next Monday (Oct 16) @ 4pm**

Administrative Stuff

- **The second midterm is in 2 weeks.**

Administrative Stuff

- **Midterm Exam #2**
- **When: Friday October 27 @ 4pm.**
- **Where: This classroom**
- **What: Chapters 1, 2, 3, 4 and 5.1-5.8**
- **The exam will be open book and open notes (you can bring up to 3 pages of handwritten/typed notes).**

Midterm 2: Format

- The exam will be out of 130 points
- You need 95 points to get an A on the exam
- It will be great if you can score more than 100 points.
 - but you can't roll over your extra points 😞

Quick Review

Decoders


2-to-4 Decoder (Definition)

- Has two inputs: w_1 and w_0
- Has four outputs: y_0 , y_1 , y_2 , and y_3
- If $w_1=0$ and $w_0=0$, then the output y_0 is set to 1
- If $w_1=0$ and $w_0=1$, then the output y_1 is set to 1
- If $w_1=1$ and $w_0=0$, then the output y_2 is set to 1
- If $w_1=1$ and $w_0=1$, then the output y_3 is set to 1
- Only one output is set to 1. All others are set to 0.

Truth Table and Graphical Symbol for a 2-to-4 Decoder

w_1	w_0	y_0	y_1	y_2	y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


(a) Truth table

 

(b) Graphical symbol

Truth Table and Graphical Symbol for a 2-to-4 Decoder

w_1	w_0	y_0	y_1	y_2	y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 


The outputs are “one-hot” encoded

(a) Truth table


(b) Graphical symbol

Truth Logic Circuit for a 2-to-4 Decoder

 

[Figure 4.13c from the textbook]

Adding an Enable Input

 


[Figure 4.13c from the textbook]

Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphical symbol

[Figure 4.14a-b from the textbook]


Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

 

 
(a) Truth table

x indicates that it does not matter
what the value of these variable is
for this row of the truth table



 (b) Graphical symbol

Graphical Symbol for a Binary n-to- 2^n Decoder with an Enable Input




(d) An n -to- 2^n decoder

A binary decoder with n inputs has 2^n outputs


The outputs of an enabled binary decoder are “one-hot” encoded, meaning that only a single bit is set to 1, i.e., it is *hot*.

A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

 



[Figure 4.15 from the textbook]

A 4-to-16 decoder built using a decoder tree


 


[Figure 4.16 from the textbook]



Let's build a 5-to-32 decoder

  

Let's build a 5-to-32 decoder

  

Let's build a 5-to-32 decoder

  


Demultiplexers

1-to-4 Demultiplexer (Definition)


- Has one data input line: D
- Has two output select lines: w_1 and w_0
- Has four outputs: y_0 , y_1 , y_2 , and y_3
- If $w_1=0$ and $w_0=0$, then the output y_0 is set to D
- If $w_1=0$ and $w_0=1$, then the output y_1 is set to D
- If $w_1=1$ and $w_0=0$, then the output y_2 is set to D
- If $w_1=1$ and $w_0=1$, then the output y_3 is set to D
- Only one output is set to D. All others are set to 0.

A 1-to-4 demultiplexer built with a 2-to-4 decoder

 

[Figure 4.14c from the textbook]


A 1-to-4 demultiplexer built with a 2-to-4 decoder

 

[Figure 4.14c from the textbook]

Multiplexers (Implemented with Decoders)

A 4-to-1 multiplexer built using a 2-to-4 decoder

 

[Figure 4.17 from the textbook]

Encoders

Binary Encoders

4-to-2 Binary Encoder (Definition)

- Has four inputs: w_3 , w_2 , w_1 , and w_0
- Has two outputs: y_1 and y_0
- Only one input is set to 1 (“one-hot” encoded). All others are set to 0.
- If $w_0=1$ then $y_1=0$ and $y_0=0$
- If $w_1=1$ then $y_1=0$ and $y_0=1$
- If $w_2=1$ then $y_1=1$ and $y_0=0$
- If $w_3=1$ then $y_1=1$ and $y_0=1$

Truth table for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

[Figure 4.19 from the textbook]


Truth table for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

The inputs are “one-hot” encoded

Circuit for a 4-to-2 binary encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

[Figure 4.19 from the textbook]

Circuit for a 4-to-2 binary encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

[Figure 4.19 from the textbook]

Circuit for a 4-to-2 binary encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

[Figure 4.19 from the textbook]

Circuit for a 4-to-2 binary encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

[Figure 4.19 from the textbook]

Circuit for a 4-to-2 binary encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

[Figure 4.19 from the textbook]

Circuit for a 4-to-2 binary encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

[Figure 4.19 from the textbook]


Circuit for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

[Figure 4.19 from the textbook]

A 2^n -to- n binary encoder

 

[Figure 4.18 from the textbook]

Priority Encoders

Truth table for a 4-to-2 priority encoder (abbreviated version)

w_3	w_2	w_1	w_0		y_1	y_0	z
0	0	0	0		d	d	0
0	0	0	1		0	0	1
0	0	1	x		0	1	1
0	1	x	x		1	0	1
1	x	x	x		1	1	1

[Figure 4.20 from the textbook]

Truth table for a 4-to-2 priority encoder (abbreviated version)

w_3	w_2	w_1	w_0		y_1	y_0	z
0	0	0	0	d	d	0	
0	0	0	1	0	0	1	
0	0	1	x	0	1	1	
0	1	x	x	1	0	1	
1	x	x	x	1	1	1	

[Figure 4.20 from the textbook]

Truth table for a 4-to-2 priority encoder

	w_3	w_2	w_1	w_0	y_1	y_0	z
0 0 0 0	0	0	0	0	d	d	0
0 0 0 1	0	0	0	1	0	0	1
0 0 1 x	0	0	1	0	0	1	1
	0	0	1	1	0	1	1
0 1 x x	0	1	0	0	1	0	1
	0	1	0	1	1	0	1
	0	1	1	0	1	0	1
	0	1	1	1	1	0	1
1 x x x	1	0	0	0	1	1	1
	1	0	0	1	1	1	1
	1	0	1	0	1	1	1
	1	0	1	1	1	1	1
	1	1	0	0	1	1	1
	1	1	0	1	1	1	1
	1	1	1	0	1	1	1
	1	1	1	1	1	1	1

Expressions for 4-to-2 priority encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

W₃ W₂


W₁ W₀

00	01	11	10
d	1	1	1
0	1	1	1
0	1	1	1
0	1	1	1

$$y_1 = w_3 + w_2$$

Expressions for 4-to-2 priority encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 

$$y_0 = w_3 + w_1 \bar{w}_2$$

Expressions for 4-to-2 priority encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1


W₃ W₂

W₁ W₀

00	01	11	10
0	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

$$Z = W_3 + W_2 + W_1 + W_0$$

Circuit for the 4-to-2 priority encoder

 

The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$\begin{aligned}i_0 &= \overline{w}_3 \overline{w}_2 \overline{w}_1 w_0 \\i_1 &= \overline{w}_3 \overline{w}_2 w_1 \\i_2 &= \overline{w}_3 w_2 \\i_3 &= w_3\end{aligned}$$

$$\begin{aligned}y_0 &= i_1 + i_3 \\y_1 &= i_2 + i_3\end{aligned}$$

$$z = i_0 + i_1 + i_2 + i_3$$


The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$\begin{aligned}i_0 &= \overline{w}_3 \overline{w}_2 \overline{w}_1 w_0 \\i_1 &= \overline{w}_3 \overline{w}_2 w_1 \\i_2 &= \overline{w}_3 w_2 \\i_3 &= w_3\end{aligned}$$

$$\begin{aligned}y_0 &= i_1 + i_3 \\y_1 &= i_2 + i_3\end{aligned}$$

$$z = i_0 + i_1 + i_2 + i_3$$

 


The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$\begin{aligned} i_0 &= \overline{w}_3 \overline{w}_2 \overline{w}_1 w_0 \\ i_1 &= \overline{w}_3 \overline{w}_2 w_1 \\ i_2 &= \overline{w}_3 w_2 \\ i_3 &= w_3 \end{aligned}$$

$$\begin{aligned} y_0 &= i_1 + i_3 \\ y_1 &= i_2 + i_3 \end{aligned}$$

$$z = i_0 + i_1 + i_2 + i_3$$

 


The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$\begin{aligned} i_0 &= \overline{w}_3 \overline{w}_2 \overline{w}_1 w_0 \\ i_1 &= \overline{w}_3 \overline{w}_2 w_1 \\ i_2 &= \overline{w}_3 w_2 \\ i_3 &= w_3 \end{aligned}$$

$$\begin{aligned} y_0 &= i_1 + i_3 \\ y_1 &= i_2 + i_3 \end{aligned}$$

$$z = i_0 + i_1 + i_2 + i_3$$

 

Try to prove that this is equivalent to the circuit that was derived above.

Code Converters



Code Converter (Definition)

- Converts from one type of input encoding to a different type of output encoding.

Code Converter (Definition)

- Converts from one type of input encoding to a different type of output encoding.
- A decoder does that as well, but its outputs are always one-hot encoded so the output code is really only one type of output code.
- A binary encoder does that as well but its inputs are always one-hot encoded so the input code is really only one type of input code.

  A hex-to-7-segment display code converter





(b) 7-segment display

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

  (c) Truth table

[Figure 4.21 from the textbook]

A hex-to-7-segment display code converter





w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

  (c) Truth table

[Figure 4.21 from the textbook]

A hex-to-7-segment display code converter




w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

 
(c) Truth table

[Figure 4.21 from the textbook]

A hex-to-7-segment display code converter



(a) Code converter

 



(b) 7-segment display

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

  (c) Truth table

[Figure 4.21 from the textbook]

A hex-to-7-segment display code converter



w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table

[Figure 4.21 from the textbook]

What is the circuit for this code converter?

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	0	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1


What is the circuit for this code converter?

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	0	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
1	0	1	0	1	1	0	1	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	0	1	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	1	1	1	1

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 3, 5, 6, 7, 8, 9, 10, 12, 14, 15)$$

What is the circuit for this code converter?

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	0	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	0	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
1	0	1	0	1	1	0	1	1	1	1
1	0	1	1	0	1	1	1	1	1	1
1	1	0	0	1	0	1	1	1	1	0
1	1	0	1	0	1	1	1	0	1	1
1	1	1	0	1	0	1	1	1	1	0
1	1	1	1	1	0	0	1	1	1	1

 


$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 3, 5, 6, 7, 8, 9, 10, 12, 14, 15)$$

What is the circuit for this code converter?

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	1	1	1	1

What is the circuit for this code converter?

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	0	1	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	0	0	0

 

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 3, 5, 6, 8, 9, 11, 12, 13, 14)$$


Arithmetic Comparison Circuits

Truth table for a one-bit digital comparator

Inputs		Outputs		
A	B	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

A one-bit digital comparator circuit


Inputs		Outputs		
A	B	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

 

Truth table for a two-bit digital comparator


Inputs				Outputs		
A_1	A_0	B_1	B_0	$A < B$	$A = B$	$A > B$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

A two-bit digital comparator circuit

 

[<http://forum.allaboutcircuits.com/showthread.php?t=10561>]

A four-bit comparator circuit

 

[Figure 4.22 from the textbook]

Example Problems from Chapter 4


Example 1: SOP vs Decoders

Implement the function

$$f(w_1, w_2, w_3) = \sum m(0, 1, 3, 4, 6, 7)$$

by using a 3-to-8 binary decoder and one OR gate.

Solution Circuit

 


$$f(w_1, w_2, w_3) = \sum m(0, 1, 3, 4, 6, 7)$$

[Figure 4.44 from the textbook]

Solution Circuit

 Notice this swap
of variables in
the two lists.



$$f(w_1, w_2, w_3) = \sum m(0, 1, 3, 4, 6, 7)$$

[Figure 4.44 from the textbook]

Example 2: Implement an 8-to-3 binary encoder

w_7	w_6	w_5	w_4	w_3	w_2	w_1	w_0	y_2	y_1	y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

[Figure 4.45 from the textbook]

Example 2: Implement an 8-to-3 binary encoder

w_7	w_6	w_5	w_4	w_3	w_2	w_1	w_0	y_2	y_1	y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1


$$y_0 = w_1 + w_3 + w_5 + w_7$$

$$y_1 = w_2 + w_3 + w_6 + w_7$$

$$y_2 = w_4 + w_5 + w_6 + w_7$$

[Figure 4.45 from the textbook]

Circuit for the 8-to-3 binary encoder

 

$$y_0 = w_1 + w_3 + w_5 + w_7$$

$$y_1 = w_2 + w_3 + w_6 + w_7$$

$$y_2 = w_4 + w_5 + w_6 + w_7$$

Example 3: Implement an 8-to-3 priority encoder

w_7	w_6	w_5	w_4	w_3	w_2	w_1	w_0	y_2	y_1	y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Example 3: Implement an 8-to-3 priority encoder

w_7	w_6	w_5	w_4	w_3	w_2	w_1	w_0	y_2	y_1	y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	X	0	0	1
0	0	0	0	0	1	X	X	0	1	0
0	0	0	0	1	X	X	X	0	1	1
0	0	0	1	X	X	X	X	1	0	0
0	0	1	X	X	X	X	X	1	0	1
0	1	X	X	X	X	X	X	1	1	0
1	X	X	X	X	X	X	X	1	1	1

Example 3: Implement an 8-to-3 priority encoder

w_7	w_6	w_5	w_4	w_3	w_2	w_1	w_0	y_2	y_1	y_0	z
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	1	X	0	0	1	1
0	0	0	0	0	1	X	X	0	1	0	1
0	0	0	0	1	X	X	X	0	1	1	1
0	0	0	1	X	X	X	X	1	0	0	1
0	0	1	X	X	X	X	X	1	0	1	1
0	1	X	X	X	X	X	X	1	1	0	1
1	X	X	X	X	X	X	X	1	1	1	1
0	0	0	0	0	0	0	0	d	d	d	0


Example 3: Implement an 8-to-3 priority encoder

w_7	w_6	w_5	w_4	w_3	w_2	w_1	w_0	y_2	y_1	y_0	Z
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	1	X	0	0	1	1
0	0	0	0	0	1	X	X	0	1	0	1
0	0	0	0	1	X	X	X	0	1	1	1
0	0	0	1	X	X	X	X	1	0	0	1
0	0	1	X	X	X	X	X	1	0	1	1
0	1	X	X	X	X	X	X	1	1	0	1
1	X	X	X	X	X	X	X	1	1	1	1
0	0	0	0	0	0	0	0	d	d	d	0


Example 3: Implement an 8-to-3 priority encoder

	w_7	w_6	w_5	w_4	w_3	w_2	w_1	w_0	y_2	y_1	y_0	z
$i_0 = \overline{w_7} \overline{w_6} \overline{w_5} \overline{w_4} \overline{w_3} \overline{w_2} \overline{w_1} w_0$	0	0	0	0	0	0	0	1	0	0	0	1
$i_1 = \overline{w_7} \overline{w_6} \overline{w_5} \overline{w_4} \overline{w_3} \overline{w_2} w_1$	0	0	0	0	0	0	1	X	0	0	1	1
$i_2 = \overline{w_7} \overline{w_6} \overline{w_5} \overline{w_4} w_3 w_2$	0	0	0	0	0	1	X	X	0	1	0	1
$i_3 = \overline{w_7} \overline{w_6} \overline{w_5} w_4 w_3$	0	0	0	0	1	X	X	X	0	1	1	1
$i_4 = \overline{w_7} \overline{w_6} w_5 w_4$	0	0	0	1	X	X	X	X	1	0	0	1
$i_5 = \overline{w_7} w_6 w_5$	0	0	1	X	X	X	X	X	1	0	1	1
$i_6 = w_7 w_6$	0	1	X	X	X	X	X	X	1	1	0	1
$i_7 = w_7$	1	X	X	X	X	X	X	X	1	1	1	1
$z = i_0 + i_1 + i_2 + i_3 + i_4 + i_5 + i_6 + i_7$	0	0	0	0	0	0	0	0	d	d	d	0

Circuit for the 8-to-3 binary encoder

 

Circuit for the 8-to-3 priority encoder

 

Example 4:Circuit implementation using a multiplexer

Implement the function

$$f(w_1, w_2, w_3, w_4, w_5) = \overline{w_1} \overline{w_2} \overline{w_4} \overline{w_5} + w_1 w_2 + w_1 w_3 + w_1 w_4 + w_3 w_4 w_5$$

using a 4-to-1 multiplexer

Some Boolean Algebra Leads To

$$\overline{w_1} \overline{w_2} \overline{w_4} \overline{w_5} + w_1 w_2 + w_1 w_3 + w_1 w_4 + w_3 w_4 w_5$$

$$\overline{w_1} \overline{w_4} (\overline{w_5} \overline{w_2}) + w_4 (w_3 w_5) + w_1 (w_2 + w_3) + w_1 w_4 (1)$$


$$\overline{w_1} \overline{w_4} (\overline{w_5} \overline{w_2}) + (\overline{w_1} + w_1) w_4 (w_3 w_5) + w_1 (\overline{w_4} + w_4) (w_2 + w_3) + w_1 w_4 (1)$$

$$\overline{w_1} \overline{w_4} (\overline{w_5} \overline{w_2}) + \overline{w_1} w_4 (w_3 w_5) + w_1 \overline{w_4} (w_2 + w_3) + w_1 w_4 (w_3 w_5 + (w_2 + w_3) + 1)$$

$$\overline{w_1} \overline{w_4} (\overline{w_5} \overline{w_2}) + \overline{w_1} w_4 (w_3 w_5) + w_1 \overline{w_4} (w_2 + w_3) + w_1 w_4 (1)$$

Note that the split is by w_1 and w_4 , not w_1 and w_2

Solution Circuit

 


$$\bar{w}_1 \bar{w}_4 (\bar{w}_5 \bar{w}_2) + \bar{w}_1 w_4 (w_3 w_5) + w_1 \bar{w}_4 (w_2 + w_3) + w_1 w_4 (1)$$

[Figure 4.46 from the textbook]


Some Final Things from Chapter 4

A shifter circuit

 


[Figure 4.50 from the textbook]


A shifter circuit

 

A shifter circuit

 


A shifter circuit

 


No shift in this case.


A shifter circuit

 

A shifter circuit

 


A shifter circuit

 

Shift to the right by 1 bit

A shifter circuit

 


Shift to the right by 1 bit

A barrel shifter circuit

s_1	s_0	y_3	y_2	y_1	y_0
0	0	w_3	w_2	w_1	w_0
0	1	w_0	w_3	w_2	w_1
1	0	w_1	w_0	w_3	w_2
1	1	w_2	w_1	w_0	w_3

(a) Truth table

 

(b) Circuit

[Figure 4.51 from the textbook]

Questions?

THE END