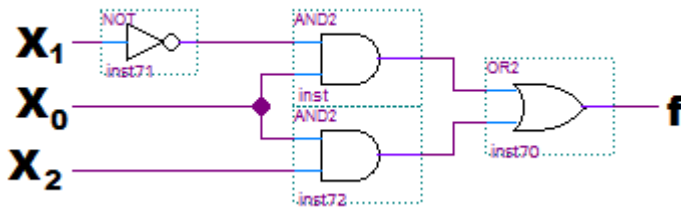


**P1 (10 points):** Given the following circuit:



A: Write the SOP expression for the output f.

B: Show that the POS shorthand expression for f can be written as:  
 $f(x_2, x_1, x_0) = \prod M(0,2,3,4,6)$

C: Assume that the inputs to the circuit  $(x_2, x_1, x_0)$  represent a three-bit integer X where (by convention) the subscript "0" ( $x_0$ ) indicates the least significant bit (LSB). What is the value of f for the input X=6?

D: What decimal values of X will produce an output f=1?

**P2 (9 points):** Produce the simplified sum-of-products (SOP) expressions for the following K-maps:

	BC	00	01	11	10
A	0	0	1	1	0
	1	0	1	1	0

	YZ	00	01	11	10
wX	00	0	1	0	0
	01	0	0	0	0
	11	0	0	0	0
	10	0	1	1	1

	YZ	00	01	11	10
wX	00	1	0	0	0
	01	1	0	0	0
	11	1	0	0	0
	10	0	0	0	1

**P3 (12 points):** Given the shorthand expression  $F(a, b, c) = \prod M(0,1,2,5)$ :

A: Use a K-Map to show that F may simplify to the product-of-sums (POS) expression  $F = (a + c)(b + \bar{c})$ .

B: A second expression is given as  $F_2 = (a + b)(a + c)(b + \bar{c})$ . Prove that these two expressions are equivalent; that is, prove that  $F = F_2$ .

C: What are the implications of implementing the circuit for F with the second expression  $(a + b)(a + c)(b + \bar{c})$  instead of  $(a + c)(b + \bar{c})$ ?

**P4 (12 points):** For each shorthand expression below, derive the simplest SOP expression:

A:  $X_3(a, b, c, d) = \sum m(4,6,9,12,13,14)$

B:  $X_2(a, b, c) = \sum m(0,1,5,7)$

C:  $X_1(a, b, c, d) = \sum m(0,3,4,7,8,9,12,15)$

**P5 (12 points):** For each expression below, derive the simplest POS expression:

A:  $Y_3(P, Q, R) = \prod M(1,2,3,7)$

B:  $Y_2(P, Q, R, S) = \prod M(0,2,5,7,8,10)$

C:  $Y_1(P, Q, R, S) = \prod M(1,4,6,9,10)$

**P6 (10 points):** Given the shorthand expression  $L(W, X, Y, Z) = \sum m(0,1,4,5,6,8,9,11,12,13,14,15)$ :

A: Derive the simplified SOP expression for L,  $L_{SOP}$ .

B: Derive the simplified POS expression for L,  $L_{POS}$ .

C: Which expression will produce a circuit with a lower cost:  $L_{POS}$  or  $L_{SOP}$ ? Why?

D: Is it valid to say that  $L_{SOP} = L_{POS}$ ? Why?

**P7 (15 points):** Use Karnaugh Maps to convert the given expressions to simplified SOP expressions:

I:  $Z_1(A, B, C, D) = \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}B\overline{C} + \overline{A}C\overline{D} + ABD$

II:  $Z_2(D, Q) = DQ + (D \oplus Q)$

III:  $Z_3(a, b, c) = \prod M(2,3,4,6,7)$

**P8 (20 points):** The goal for this problem is to accept a four-bit integer X ( $x_3, x_2, x_1, x_0$ ) and use the constituent bits to derive two expressions:  $P_2=1$  if X is a multiple of 2 (0, 2, 4...) and  $P_3=1$  if X is a multiple of 3 (0, 3, 6...).

A: Show the K-map for  $P_2$  and the K-map for  $P_3$  given the four input bits for X ( $x_3, x_2, x_1, x_0$ )

B: Write a shorthand SOP expression for  $P_2$  and show that the cost of the minimal SOP circuit for  $P_2$  is 2.

C: Write a shorthand SOP expression for  $P_3$  and show that the cost of the minimal SOP circuit for  $P_3$  is 45 (when implemented separately from  $P_2$ ).

D: Let  $P_6=1$  if X is a multiple of 6. Show that its expression is  $P_6 = \overline{x}_3\overline{x}_2\overline{x}_1\overline{x}_0 + \overline{x}_3x_2x_1\overline{x}_0 + x_3x_2\overline{x}_1\overline{x}_0$