


Switches		Output			
00	= 0¢	000	= 0¢	100	= 20¢
01	= 5¢	001	= 5¢	101	= 25¢
10	= 10¢	010	= 10¢	110	= 30¢
11	= 25¢	011	= 15¢	111	= 35¢

Hex Output


	A	B	C	D	E	F	G
0	1	1	1	1	1	1	0
1	0	1	1	0	0	0	0
2	1	1	0	1	1	0	1
3	1	1	1	1	0	0	1
5	1	0	1	1	0	1	1
A	1	1	1	0	1	1	1
6	0	0	1	1	1	1	1

Preference of Purchase

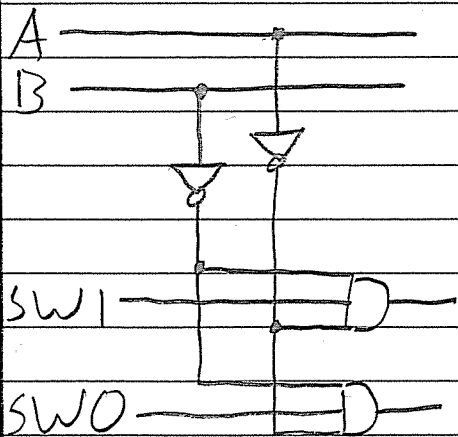A10 and B25 passed through not gates, then an and gate for each switch SW



Purchase overrides coin input

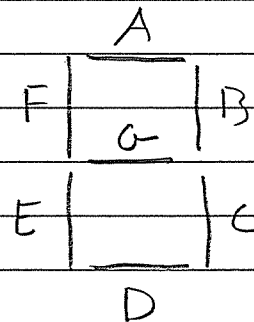

Flip-Flop Logic

Switches SW_1 and SW_2 are input coins described previously. They are added to current state. Then they are passed through Mealy machine to next state.

Current state Y

Next state Q

Y_2, Y_1, Y_0			SW_1, SW_2			
			00	01	10	11
0	0	0	000	001	010	101
0	0	1	001	010	011	110
0	1	0	010	011	100	111
0	1	1	011	100	101	011
1	0	0	100	101	110	100
1	0	1	101	110	111	101
1	1	0	110	111	110	110
1	1	1	111	111	111	111

$Y_1 Y_0$	Y_2			
$S_1 S_0$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	1	1	0	1
10	0	0	1	1

$Y_1 Y_0$	Y_2			
$S_1 S_0$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$(\bar{Y}_1 \bar{S}_1 \bar{S}_0 + \bar{Y}_0 \bar{S}_1 \bar{S}_0 + Y_1 \bar{S}_1 \bar{S}_0 + Y_1 Y_0 \bar{S}_1 \bar{S}_0)$$

$Y_1 Y_0$	Y_2			
$S_1 S_0$	00	01	11	10
00	0	0	1	1
01	0	1	0	1
11	0	1	1	1
10	1	1	0	0

$Y_1 Y_0$	Y_2			
$S_1 S_0$	00	01	11	10
00	0	0	1	1
01	0	1	1	1
11	0	0	1	1
10	1	1	1	1

$$(\bar{Y}_1 \bar{S}_1 \bar{S}_0 + \bar{Y}_1 Y_0 \bar{S}_0 + \bar{Y}_1 \bar{S}_1 \bar{S}_0 + \bar{Y}_0 \bar{S}_1 \bar{S}_0 + \bar{Y}_1 Y_0 \bar{S}_0)$$

$$(\bar{Y}_1 + \bar{S}_1 \bar{S}_0 + \bar{Y}_0 \bar{S}_1 \bar{S}_0)$$


$Y_1 Y_0$	Y_2			
$S_1 S_0$	00	01	11	10
00	0	1	1	0
01	1	0	0	1
11	1	0	1	1
10	0	1	1	0

$Y_1 Y_0$	Y_2			
$S_1 S_0$	00	01	11	10
00	0	1	1	0
01	1	0	1	1
11	0	1	1	0
10	0	1	1	0

$$(\bar{Y}_0 \bar{S}_0 + \bar{Y}_0 \bar{S}_1 + Y_1 \bar{S}_1 \bar{S}_0)$$

$$(\bar{Y}_1 \bar{Y}_0 + \bar{Y}_0 \bar{S}_1 + \bar{Y}_0 \bar{S}_1 \bar{S}_0 + \bar{Y}_0 \bar{S}_0)$$

Flip-Flop Logic

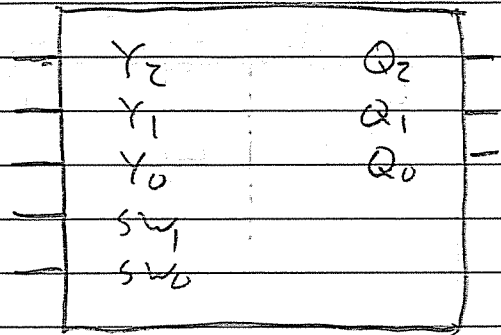


$$Q_2 = Y_2 + \overline{Y_2} (Y_1 SW_1 SW_0 + \overline{Y_0} SW_1 SW_0 + Y_1 SW_1 \overline{SW_0} + Y_1 Y_0 \overline{SW_1} SW_0)$$

$$Q_1 = \overline{Y_2} (Y_1 \overline{SW_1} \overline{SW_0} + Y_1 \overline{Y_0} SW_0 + Y_1 SW_1 \overline{SW_0} + Y_0 SW_1 SW_0 + \overline{Y_1} Y_0 SW_0) + Y_2 (Y_1 + SW_1 \overline{SW_0} + Y_0 SW_1 SW_0)$$

$$Q_0 = \overline{Y_2} (Y_0 SW_0 + \overline{Y_0} SW_0 + Y_1 SW_1 SW_0) + Y_2 (Y_1 Y_0 + Y_0 SW_1 + \overline{Y_0} \overline{SW_1} SW_0 + Y_0 \overline{SW_0})$$

Coin Input to Machine

\overline{sw}_1	sw_0	Hex2	Hex1
0	0	0	0
0	1	5	5
1	0	1	0
1	1	2	5

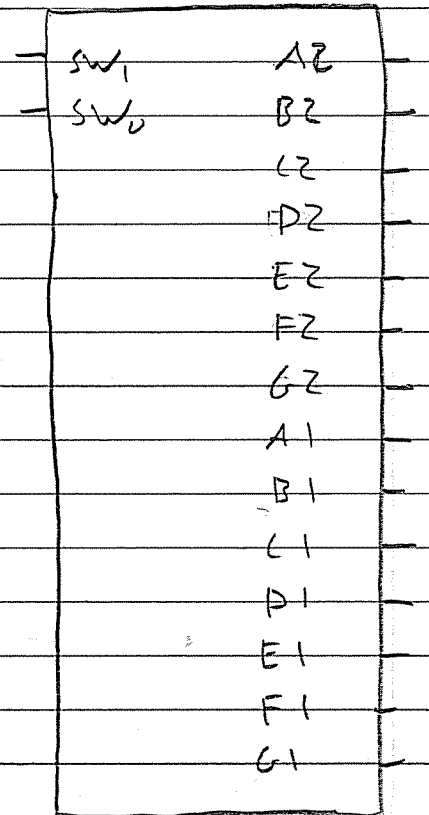

All following logic underwent not in verilog because 1 means off and 0 means on for the hex LEDs. Value is specified on

$$\begin{aligned}
 A1 &= 1 \\
 B1 &= \overline{sw}_0 \\
 C1 &= 1 \\
 D1 &= 1 \\
 E1 &= \overline{sw}_0 \\
 F1 &= 1 \\
 G1 &= \overline{sw}_0
 \end{aligned}$$

$$\begin{aligned}
 A2 &= \overline{sw}_1 + \overline{sw}_0 \\
 B2 &= 1 \\
 C2 &= \overline{sw}_1 + \overline{sw}_0 \\
 D2 &= \overline{sw}_1 + \overline{sw}_0 \\
 E2 &= \overline{sw}_1 + \overline{sw}_0 \\
 F2 &= \overline{sw}_1 \\
 G2 &= \overline{sw}_1 \overline{sw}_0
 \end{aligned}$$

Hex 2

SW ₁	SW ₀	A	B	C	D	E	F	G
0	0	1	1	1	1	1	1	0
0	1	1	1	1	1	1	1	0
1	0	0	1	1	0	0	0	0
1	1	1	1	0	1	1	0	1

Hex 1

SW ₁	SW ₀	A	B	C	D	E	F	G
0	0	1	1	1	1	1	1	0
0	1	1	0	1	1	0	1	1
1	0	1	1	1	1	1	1	0
1	1	1	0	1	1	0	1	1

Coin Output

Y_2	Y_1	Y_0	Hex 2	Hex 1
0	0	0	0	0
0	0	1	0	5
0	1	0	1	0
0	1	1	1	5
1	0	0	2	0
1	1	1	7	5
1	0	0	3	0
1	1	1	7	5

Y_2	A2
Y_1	B2
Y_0	C2
	D2
	E2
	F2
	G2
	A1
	B1
	C1
	D1
	E1
	F1
	G1

All logic passed through not in verilog due to hex on/off logic.
 Coin out put placed after purchase machine to display change return as well as change currently in machine

$$\begin{aligned}
 A1 &= 1 \\
 B1 &= Y_0 \\
 C1 &= 1 \\
 D1 &= 1 \\
 E1 &= Y_0 \\
 F1 &= 1 \\
 G1 &= Y_0
 \end{aligned}$$

$$\begin{aligned}
 A2 &= Y_2 + \overline{Y_1} \\
 B2 &= \overline{1} \\
 C2 &= Y_2 + Y_1 \\
 D2 &= Y_2 + Y_1 \\
 E2 &= \overline{Y_1} \\
 F2 &= \overline{Y_2} \overline{Y_1} \\
 G2 &= Y_2
 \end{aligned}$$


		Hex 2						
Y_2	Y_1	A	B	C	D	E	F	G
0	0	1	1	1	1	1	1	0
0	1	0	1	1	0	0	0	0
1	0	1	1	0	1	1	1	1
1	1	1	1	1	1	0	0	1

		Hex 1						
Y_0		A	B	C	D	E	F	G
0		1	1	1	1	1	1	0
1		1	0	1	1	0	1	1

Inputs Y_2 and Y_1 only affected Hex 2
 Similarly, Hex 1 was only dependent
 on Y_0

Purchase/Change/Clear

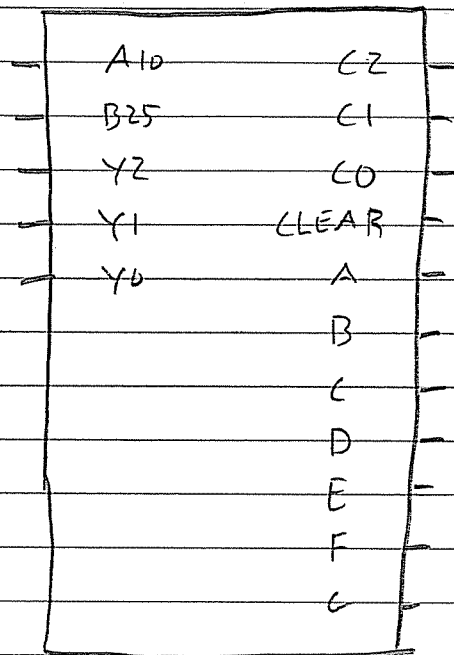Since directions were unclear, I designed this section as follows. Purchase designates if A10, B25, or nothing is purchased. Change displays on two hexes how much change in the machine is returned.



Clear output was passed through a D flip-flop on the same clock as the state machine. Clear resets the state machine, enabling more purchases.

Hex	A	B	C	D	E	F	G
0	1	1	1	1	1	1	0
1	1	1	1	1	1	1	0
2	1	1	1	1	1	1	0
3	1	1	1	1	1	1	0
4	1	1	1	1	1	1	0
5	1	1	1	1	1	1	0
6	1	1	1	1	1	1	0
7	1	1	1	1	1	1	0
8	1	1	1	1	1	1	0
9	1	1	1	1	1	1	0
A	1	1	1	0	1	1	1
B	1	1	1	0	1	1	1
C	1	1	1	0	1	1	1
D	1	1	1	0	1	1	1
E	1	1	1	0	1	1	1
F	1	1	1	1	1	1	0
G	1	1	1	1	1	1	0
H	1	1	1	1	1	1	0
I	1	1	1	1	1	1	0
J	1	1	1	1	1	1	0
K	1	1	1	1	1	1	0
L	1	1	1	1	1	1	0
M	1	1	1	1	1	1	0
N	1	1	1	1	1	1	0
O	1	1	1	1	1	1	0
P	1	1	1	1	1	1	0
Q	1	1	1	1	1	1	0
R	1	1	1	1	1	1	0
S	1	1	1	1	1	1	0
T	1	1	1	1	1	1	0
U	1	1	1	1	1	1	0
V	1	1	1	1	1	1	0
W	1	1	1	1	1	1	0
X	1	1	1	1	1	1	0
Y	1	1	1	1	1	1	0
Z	1	1	1	1	1	1	0

Purchase Hex

$A \cdot Y_2$ B $A = B$

$Y_1 Y_0$	00	01	11	10
00	1	1	1	1
01	1	0	1	1
11	1	0	1	1
10	1	0	1	1

$$(A \cdot 10 + Y_2 + Y_1 \cdot Y_0) B Z_5 + B Z_5$$

$$C = E = F = 1$$

D

$A \cdot Y_2$

$Y_1 Y_0$	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	1	1	0	0
10	1	1	0	0

$$B Z_5 (A \cdot 10 + Y_2 \cdot Y_1) + B Z_5$$

$A \cdot Y_2$ $\overline{B \cdot Z_5}$ G

$Y_1 Y_0$	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	0	0	1	1
10	0	0	1	1

$$A \cdot 10 \cdot Y_2 + A \cdot 10 \cdot Y_1$$

$A \cdot Y_2$ B Z_5

$Y_1 Y_0$	00	01	11	10
00	0	0	0	0
01	0	1	0	0
11	0	1	0	0
10	0	1	0	0

$$A \cdot 10 \cdot Y_2 \cdot Y_0 + A \cdot 10 \cdot Y_2 \cdot Y_1$$

$A Y_2$	$B_2 \bar{C}_2$			
$Y_1 Y_0$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	1	0
10	0	0	1	0

$$A \bar{1} 0 Y_2 Y_1$$

$A Y_2$	$B_2 \bar{C}_2$			
$Y_1 Y_0$	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	0	0	1	0
10	0	0	1	0

$$A \bar{1} 0 Y_2$$

$A Y_2$	\bar{C}_1			
$Y_1 Y_0$	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	0	0	0	0
10	0	0	0	0

$$A \bar{1} 0 Y_2 \bar{Y}_1$$

$A Y_2$	$B_2 \bar{C}_2$			
$Y_1 Y_0$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	1	1	1
10	0	0	1	1

$$(A \bar{1} 0 Y_1 + Y_2 Y_1 Y_0)$$

$A Y_2$	\bar{C}_0			
$Y_1 Y_0$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	0	0	1	1
10	0	0	0	0

$$(A \bar{1} 0 Y_2 Y_0 + A \bar{1} 0 Y_1 Y_0)$$

$A Y_2$	$B_2 \bar{C}_2$			
$Y_1 Y_0$	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	0	1	1
10	0	1	0	0

$$(A \bar{1} 0 Y_2 + \bar{A} \bar{1} 0 Y_2 Y_1 \bar{Y}_0)$$

$A Y_2$	$B_2 \bar{5}$			
$Y_1 Y_0$	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	0	0	1	1
10	0	0	1	1

$$(A10Y_2 + A10Y_1)$$

$A Y_2$	$B_2 \bar{5}$			
$Y_1 Y_0$	00	01	11	10
00	0	0	1	1
01	0	1	1	1
11	0	1	1	1
10	0	1	1	1

$$(A10 + Y_2 Y_0 + Y_2 Y_1)$$

$$CLEAR = B_2 \bar{5} (A10Y_2 + A10Y_1) + B_2 \bar{5} (A10 + Y_2 Y_0 + Y_2 Y_1)$$

$$C = B_2 \bar{5} (A10Y_2 Y_1) + B_2 \bar{5} A10Y_2$$

$$C1 = A10Y_2 Y_1 B_2 \bar{5} + B_2 \bar{5} (A10Y_1 + Y_2 Y_1 Y_0)$$

$$C0 = B_2 \bar{5} (A10Y_2 Y_0 + A10Y_1 Y_0) + B_2 \bar{5} (A10Y_0 + A10Y_2 Y_1 Y_0)$$

$$A = B_2 \bar{5} + B_2 \bar{5} (A10 + Y_2 + Y_1 Y_0)$$

$$B = B_2 \bar{5} + B_2 \bar{5} (A10 + Y_2 + Y_1 Y_0)$$

$$C = 1$$


$$D = B_2 \bar{5} + B_2 \bar{5} (A10 + Y_2 Y_1)$$

$$E = 1$$

$$F = 1$$

$$G = B_2 \bar{5} (A10Y_2 + A10Y_1) + B_2 \bar{5} (A10Y_2 Y_0 + A10Y_2 Y_1)$$

Coin Rejection

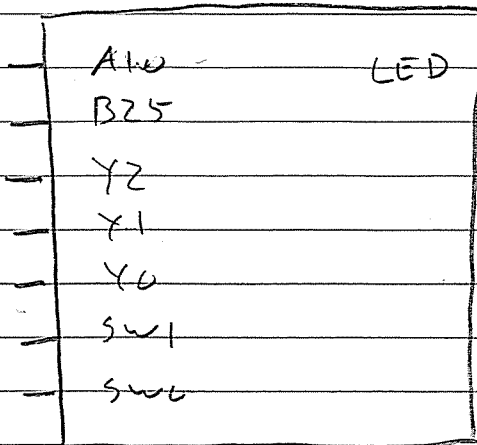

A10/B25	SW ₁	SW ₀	LED
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

A/B	SW ₁	SW ₀	LED
00	0	0	0
01	0	1	0
11	1	0	1
10	1	1	1

$$A10(SW_1 + SW_0) + B25(SW_1 + SW_0)$$

s_1, s_0 Y_1, Y_0	Y_2			
	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	1	0
10	0	0	0	0

$Y_1 Y_0 S W_1 S W_0$

s_1, s_0 Y_1, Y_0	Y_2			
	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	1	1	1	1
10	0	0	1	1

$(S W_1 S W_0 + Y_1 S W_1 + Y_1 Y_0 S W_0)$

$$LED = A 10 (S W_1 + S W_0) + B (S W_1 + S W_0) + \bar{Y}_2 Y_1 Y_0 S W_1 S W_0 + (S W_1 S W_0 + Y_1 S W_1 + Y_1 Y_0 S W_0) Y_2$$

SW₁ = SW17

SW₆ = SW16

A10 = SW14


B25 = SW13

CLOCK = KEY2

Hexes

8	7	6	5	4	3	2	1
---	---	---	---	---	---	---	---

Coin	Current	Item X	Change
Entered	Change	Purchased	returned

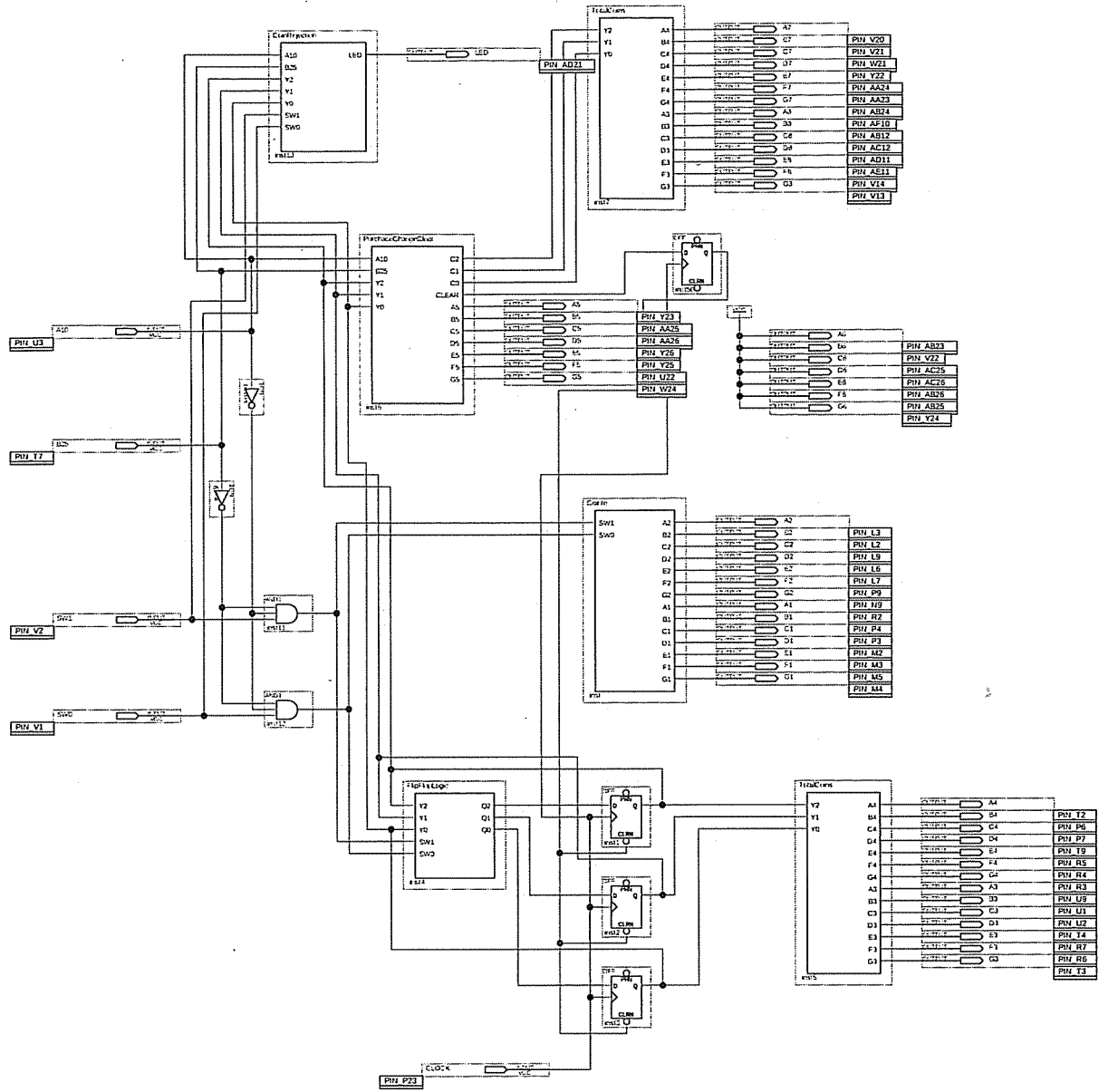

```

2   input I2, I1, I0, SW1, SW0;
3   output Q2, Q1, Q0;
4
5   assign Q2 = Y2 | (~Y2 & ((~Y1 & SW1 & SW0) | (~Y0 & SW1 & SW0) | (Y1 & SW1 & ~SW0) | (Y1 & Y0 & ~SW1 & SW0
))) );
6   assign Q1 = (~Y2 & ((Y1 & ~SW1 & ~SW0) | (Y1 & ~Y0 & SW0) | (~Y1 & SW1 & ~SW0) | (Y0 & SW1 & SW0) | (~Y1
& Y0 & SW0))) | (Y2 & (Y1 | (SW1 & ~SW0) | (Y0 & ~SW1 & SW0)));
7   assign Q0 = (~Y2 & ((Y0 & ~SW0) | (~Y0 & SW0) | (Y1 & SW1 & SW0))) | (Y2 & ((Y1 & Y0) | (Y0 & SW1) | (~
Y0 & ~SW1 & SW0) | (Y0 & ~SW0)));
8
9   endmodule

```

```

1    D5, E5, F5, G5);
2    input A10, B25, Y2, Y1, Y0;
3    output C2, C1, C0, A5, B5, C5, D5, E5, F5, G5, CLEAR;
4
5    assign CLEAR = ~((~B25&((A10&Y2)|(A10&Y1))|(B25&(A10|(Y2&Y0)|(Y2&Y1))));
6    assign C2 = (~B25&A10&Y2&Y1)|(B25&A10&Y2);
7    assign C1 = (~B25&A10&Y2&~Y1)|(B25&((A10&Y1)|(Y2&Y1&Y0)));
8    assign C0 = (~B25&((A10&Y2&Y0)|(A10&Y1&Y0))|(B25&((A10&Y0)|(~A10&Y2&Y1&~Y0))));
9    assign A5 = ~((~B25)|(B25&(A10|~Y2|(~Y1&~Y0))));
10   assign B5 = ~((~B25)|(B25&(A10|~Y2|(~Y1&~Y0))));
11   assign C5 = 0;
12   assign D5 = ~((B25)|(~B25&(~A10|(~Y2&~Y1))));
13   assign E5 = 0;
14   assign F5 = 0;
15   assign G5 = ~((~B25&((A10&Y2)|(A10&Y1))|(B25&((~A10&Y2&Y0)|(~A10&Y2&Y1))));
16
17   endmodule

```

```
    G3);
2   input Y2, Y1, Y0;
3   output A4, B4, C4, D4, E4, F4, G4, A3, B3, C3, D3, E3, F3, G3;
4
5   assign A3 = 0;
6   assign B3 = Y0;
7   assign C3 = 0;
8   assign D3 = 0;
9   assign E3 = Y0;
10  assign F3 = 0;
11  assign G3 = ~Y0;
12  assign A4 = ~(Y2|~Y1);
13  assign B4 = 0;
14  assign C4 = ~(~Y2|Y1);
15  assign D4 = ~(Y2|~Y1);
16  assign E4 = Y1;
17  assign F4 = ~(~Y2&~Y1);
18  assign G4 = ~Y2;
19
20  endmodule
```

```
2   input A10, B25, I2, I1, I0, SW1, SW0;
3   output LED;
4
5   assign LED = (A10&(SW1|SW0)) | (B25&(SW1|SW0)) | (~Y2&Y1&Y0&SW1&SW0) | (Y2&((SW1&SW0
6   ) | (Y1&SW1) | (Y1&Y0&SW0)));
7   endmodule
```

```
2   input SW1, SW0;
3   output A2, B2, C2, D2, E2, F2, G2, A1, B1, C1, D1, E1, F1, G1;
4
5   assign A1 = 0;
6   assign B1 = SW0;
7   assign C1 = 0;
8   assign D1 = 0;
9   assign E1 = SW0;
10  assign F1 = 0;
11  assign G1 = ~SW0;
12  assign A2 = ~(~SW1|SW0);
13  assign B2 = 0;
14  assign C2 = ~(~SW1|~SW0);
15  assign D2 = ~(~SW1|SW0);
16  assign E2 = ~(~SW1|SW0);
17  assign F2 = SW1;
18  assign G2 = ~(SW1&SW0);
19
20  endmodule
```

Excellent Design Description Docs.

Docs : + 20/20
Overall : 100/100