

Sample Solutions

CprE 281: Digital Logic
Midterm 1: Friday Sep 21, 2018

Student Name: _____

Student ID Number: _____


Lab Section:	Mon 12-3(P)	Tue 11-2(U)	Wed 8-11(J)	Thur 11-2(Q)	Fri 11-2(G)
(circle one)					
	Tue 2-5(M)	Wed 11-2(W)	Thur 11-2(V)		
	Tue 2-5(Z)	Wed 6-9(T)	Thur 2-5(L)		
			Thur 5-8(K)		

1. True/False Questions (10 x 1p each = 10p)

- (a) I forgot to write down my name, student ID, and lab section. TRUE / FALSE
- (b) A NOR gate can be built using one AND gate and two NOT gates. TRUE / FALSE
- (c) It is possible to build an AND gate with a 4-to-1 multiplexer. TRUE / FALSE
- (d) A two-input AND requires more transistors than a three-input OR. TRUE / FALSE
- (e) An XOR can be implemented with a 2-to-1 multiplexer and one NOT. TRUE / FALSE
- (f) $\overline{x+y} + \overline{x}y + x\overline{y} + xy = 1$. TRUE / FALSE
- (g) XOR ($x, 1$) = \overline{x} TRUE / FALSE
- (h) XOR (XOR ($x, 0$), 1) = x TRUE / FALSE
- (i) A NAND can be implemented with fewer transistors than a NOR. TRUE / FALSE
- (j) Tatooine, Alderaan, and Jedha are all planets in the Star Wars universe. TRUE / FALSE
planet planet moon

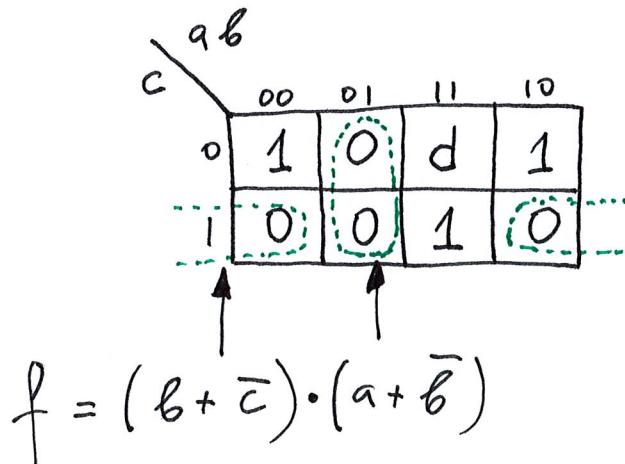2. Three-Variable K-map (5p)

Draw the K-map and derive the minimum POS expression for $f(a,b,c) = \sum m(0,4,7) + D(6)$.



3. Truth Tables (3 x 5p each = 15p)

(a) Draw the truth table for the Boolean function F that has the following K-Map:

X \ YZ	00	01	11	10
0	0	1	0	0
1	0	1	1	1

X Y Z	F
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	0
1 0 1	1
1 1 0	1
1 1 1	1

(b) Prove that $(x + y) \bullet (x + \bar{y}) = x$ using truth tables.

X	Y	$x + y$	$x + \bar{y}$	$(x+y) \bullet (x+\bar{y})$	X
0	0	0	1	0	0
0	1	1	0	0	0
1	0	1	1	1	1
1	1	1	1	1	1

(c) Draw the truth table for the function $f(a,b,c) = \bar{a}b + a\bar{c} + \bar{a}\bar{b}c$.

a	b	c	$\bar{a}b + a\bar{c} + \bar{a}\bar{b}c$	f
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

4. Number Conversions (5 x 4p each = 20p)

(a) Convert 219_{10} to binary

$$\begin{array}{r}
 219/2 = 109 \quad 1 \\
 109/2 = 54 \quad 1 \\
 54/2 = 27 \quad 0 \\
 27/2 = 13 \quad 1 \\
 13/2 = 6 \quad 1 \\
 6/2 = 3 \quad 0 \\
 3/2 = 1 \quad 1 \\
 1/2 = 0 \quad 1
 \end{array}$$

$$11011011_2 = 219_{10}$$

(b) Convert 1101_4 to decimal

$$1 \times 4^3 + 1 \times 4^2 + 0 \times 4^1 + 1 \times 4^0 = 64 + 16 + 0 + 1 = 81_{10}$$

(c) Find the values of the digits x and y in the equation: $XY_5 = \underbrace{1101}_2$

$$\Downarrow x \times 5^1 + y \times 5^0 = 13$$

$$\Downarrow 5x + y = 13$$

$$\Downarrow x = 2 \text{ and } y = 3$$

(given that $x, y \in \{0, 1, 2, 3, 4\}$)

(d) Convert 851304_9 to ternary (base 3)

$$\begin{array}{r}
 22 \quad 12 \quad 01 \quad 10 \quad 00 \quad 11 \\
 \swarrow \quad \searrow \quad \swarrow \quad \searrow \quad \swarrow \quad \searrow \\
 2 \quad 1 \quad 0 \quad 1 \quad 0 \quad 1
 \end{array}$$

base 3	base 9
00	0
01	1
02	2
10	3
11	4
12	5
20	6
21	7
22	8

(e) Compute the following sums where all numbers are in base 5:


$$\begin{array}{r}
 + \quad \overset{\bullet}{4} \overset{\bullet}{3} \\
 \hline
 \quad \overset{\bullet}{1} \overset{\bullet}{0} \overset{\bullet}{2}
 \end{array}$$

$$\begin{array}{r}
 + \quad \overset{\bullet}{1} \overset{\bullet}{4} \overset{\bullet}{2} \\
 \hline
 \quad \overset{\bullet}{2} \overset{\bullet}{1} \overset{\bullet}{0}
 \end{array}$$

5. Minimization (2 x 5p each = 10p)

Consider the Boolean function $f(X, Y, Z) = ((\overline{Z} + \overline{Z}) + Y) + X + (\overline{X} + Y)$

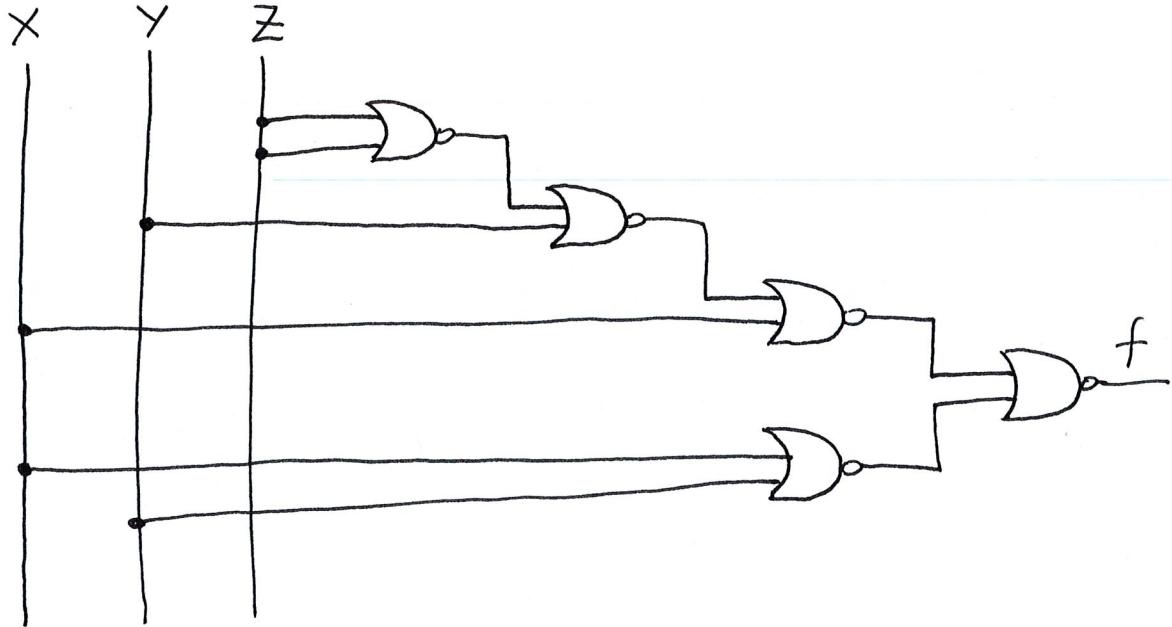(a) Draw the circuit diagram for this expression using only NOR gates.




(b) Use the theorems of Boolean algebra to simplify the expression from part (a).


$$\begin{aligned}
 f &= ((\overline{Z} + \overline{Z}) + Y) + X + (\overline{X} + Y) && (\text{De Morgan's}) \\
 &= (\overline{\overline{Z}} + Y) + X \cdot (\overline{X} + Y) && (\text{remove double negation}) \\
 &= (\overline{\overline{Z}} + Y) + X \cdot (X + Y) && (\text{De Morgan's}) \\
 &= (\overline{\overline{Z}} \cdot \overline{Y} + X) \cdot (X + Y) && (\text{remove double negation and expand}) \\
 &= \overline{Z} \overline{Y} X + \underbrace{\overline{Z} \overline{Y} Y}_{0} + \underbrace{X X}_{X} + X Y \\
 &= X \overline{Y} \overline{Z} + X + X Y \\
 &= X(\overline{Y} \overline{Z} + 1 + Y) \\
 &= X
 \end{aligned}$$

6. Venn Diagrams (3 x 5p each = 15p)

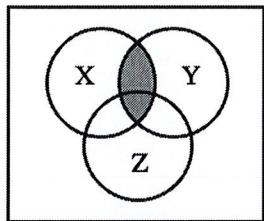
(a) Write the expression that is represented by each of the three Venn diagrams:



(A)

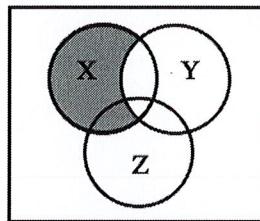

(B)

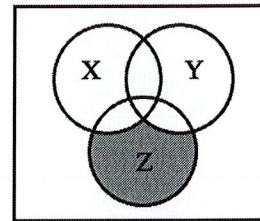


(C)

$$A = X \cdot Y$$


$$B = X \cdot \bar{Y}$$

$$C = \bar{X} \bar{Y} Z$$

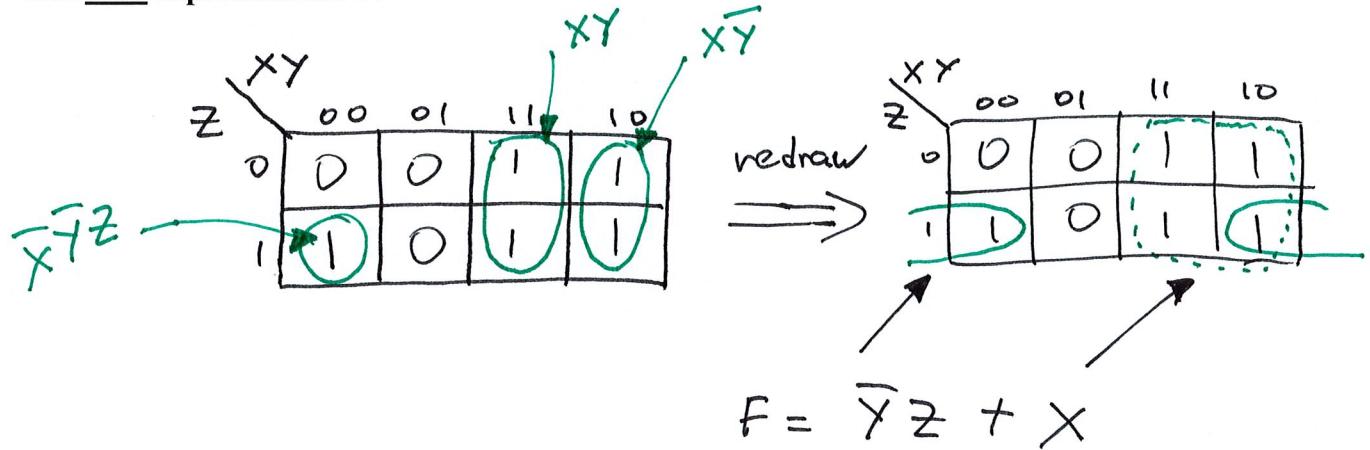(b) Let $F(X, Y, Z) = A + B + C$. Use the expressions that you derived in part (a) to draw the K-map for the Boolean function F . Then use the K-map to derive the minimum-cost SOP expression for F .



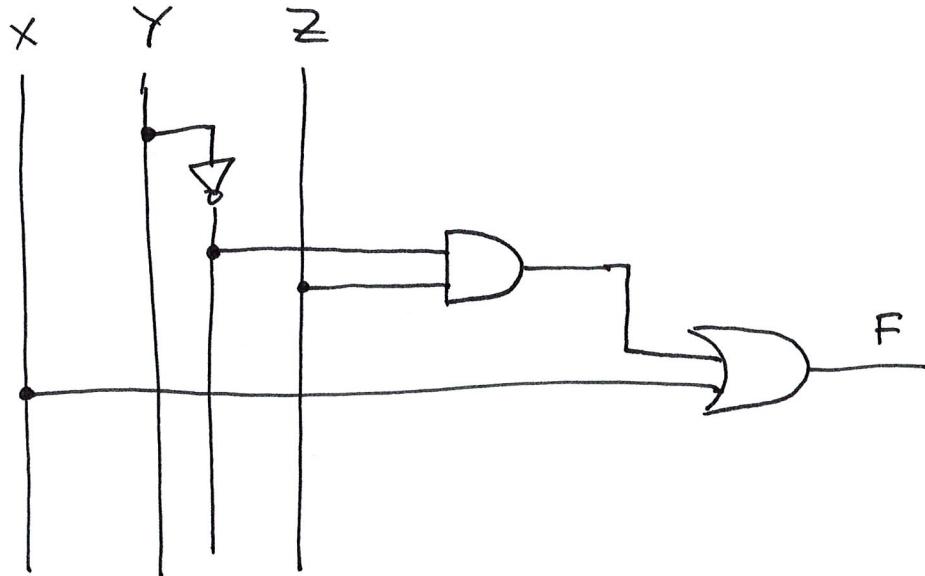
(c) Draw the circuit for your expression from part (b). Label all inputs and outputs.



7. Derive the minimum SOP expression using a K-map (3×5 p each = 15p)

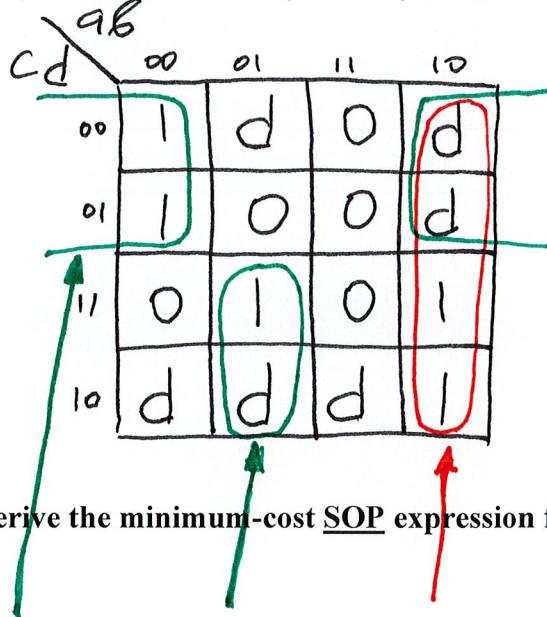(a) Draw the K-map for the following function


$$F(a,b,c,d) = \sum m(0, 1, 7, 10, 11) + D(2, 4, 6, 8, 9, 14)$$



(b) Use the K-map to derive the minimum-cost SOP expression for the function F.


$$F = \overline{b} \overline{c} + \overline{a} \overline{b} c + a \overline{b}$$

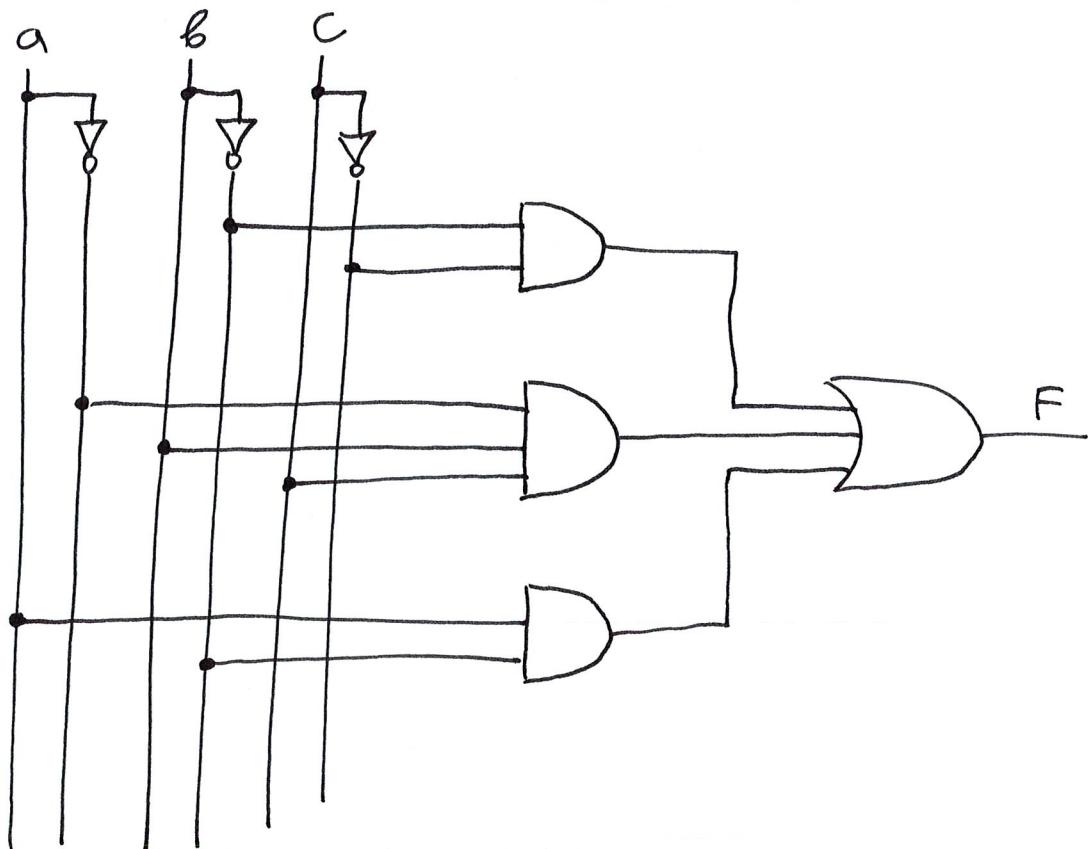(c) Draw the circuit diagram for the minimum expression from part (b).




8. NAND/NOR Logic (2 x 5p each = 10p)

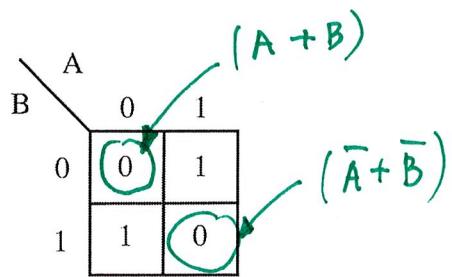(a) Using only NOR gates, draw the logic circuit that corresponds to this K-map:



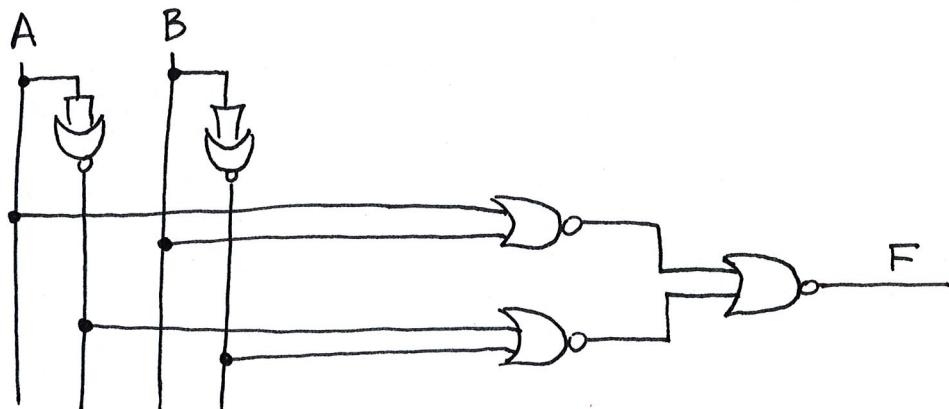
$$\begin{aligned}
 F &= (A + B) \cdot (\bar{A} + \bar{B}) \\
 &= \overline{(A + B)} \cdot \overline{(\bar{A} + \bar{B})} \\
 &= \overline{(A + B)} + \overline{(\bar{A} + \bar{B})}
 \end{aligned}$$



(b) Draw the circuit for $F(X, Y, Z) = \prod M(1, 2, 4, 6, 7)$ using only NAND gates.

$$= \Sigma m(0, 3, 5)$$

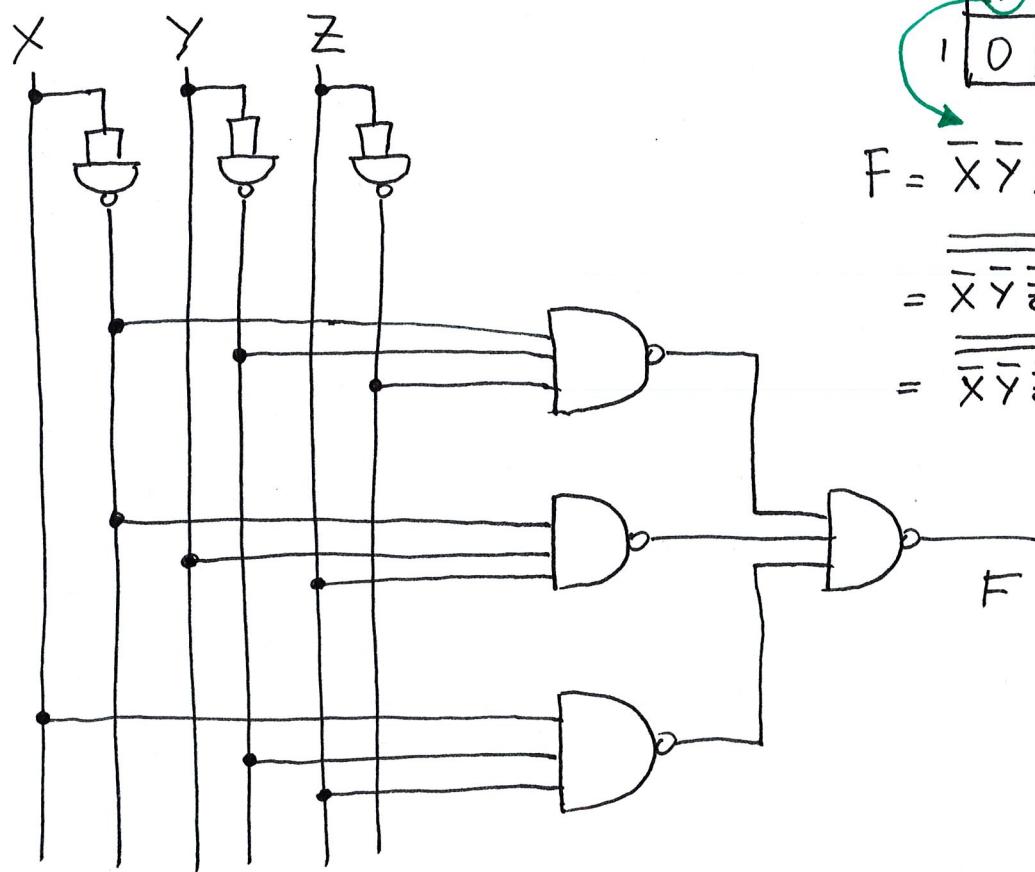

	X\Y	00	01	11	10
Z	0	1	0	0	0
1	0	1	0	1	1

$$\begin{aligned}
 F &= \overline{\overline{X} \overline{Y} \overline{Z}} + \overline{\overline{X} Y Z} + \overline{X \overline{Y} \overline{Z}} \\
 &= \overline{\overline{X} \overline{Y} \overline{Z}} + \overline{\overline{X} Y Z} + X \overline{Y} \overline{Z} \\
 &= \overline{\overline{X} \overline{Y} \overline{Z}} \cdot \overline{\overline{X} Y Z} \cdot X \overline{Y} \overline{Z}
 \end{aligned}$$

9. Seven-Segment Display (3×5 p each = 15p). The truth table for a Boolean function that converts its 4 binary inputs into a 7-segment display code is given below.

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0
3	0	0	1	1	1	1	1	1	0	1
4	0	1	0	0	0	1	1	0	1	1
5	0	1	0	1	1	0	1	1	0	1
6	0	1	1	0	1	0	1	1	1	1
7	0	1	1	1	1	0	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	1	1

six rows of d 's

(a) Derive a minimum-cost SOP expression for the output b.

x_3	x_2	00	01	11	10
x_1	x_0	00	1	d	1
00	1	0	d	1	
01	1	1	d	d	
11	1	0	d	d	
10	1	0	d	d	

$$f = \overline{x}_2 + \overline{x}_1 \overline{x}_0 + x_1 x_0$$

(b) Derive a minimum-cost POS expression for the output f.

x_3	x_2	00	01	11	10
x_1	x_0	1	1	d	1
00	0	1	d	1	
01	0	0	d	d	
11	0	0	d	d	
10	0	1	d	d	

$$f = (\overline{x}_0 + x_2 + x_3) \cdot (\overline{x}_0 + \overline{x}_1) \cdot (\overline{x}_1 + x_2)$$

(c) Derive a minimum-cost POS expression for the output g.

x_3	x_2	00	01	11	10
x_1	x_0	0	1	d	1
00	0	1	d	1	
01	0	0	d	d	
11	1	0	d	d	
10	1	1	d	d	

$$g = (x_1 + x_2 + x_3) \cdot (\overline{x}_0 + \overline{x}_1 + \overline{x}_2)$$

10. Minimization with Theorems (15p)

Use the theorems of Boolean algebra to simplify the following Boolean function

$$f(x, y, z) = \underbrace{xy\bar{z}(x+y)}_A + \underbrace{\bar{z}(x+\bar{y})}_B + \underbrace{x(\bar{x}+yz)}_C + \underbrace{1(z+x\bar{y})}_D + \underbrace{\bar{x}+z}_E$$

$$A = xy\bar{z}(x+y) = \underbrace{xy\bar{z}x}_{\text{repeated}} + \underbrace{xy\bar{z}y}_{\text{repeated}} = \underbrace{xy\bar{z}}_{\text{repeated}} + \underbrace{xy\bar{z}}_{\text{repeated}} = xy\bar{z}$$

$$B = \bar{z}(\bar{x}+\bar{y}) = \bar{z}(\bar{x} \cdot \bar{y}) = \bar{z}(\bar{x} \cdot \bar{y}) = \bar{x}y\bar{z}$$

$$C = x(\bar{x}+yz) = x(\bar{x} \cdot \bar{y}\bar{z}) = x(x \cdot (\bar{y}+\bar{z})) = x\bar{y} + x\bar{z}$$

$$D = 1(z+x\bar{y}) = z + x\bar{y}$$

$$E = \overline{\bar{x}+z} = \bar{\bar{x}} \cdot \bar{\bar{z}} = x\bar{z}$$

$$\begin{aligned}
 f &= A + B + C + D + E \\
 &= xy\bar{z} + \bar{x}y\bar{z} + \underbrace{x\bar{y}}_{\text{repeated term}} + \underbrace{x\bar{z}}_{\text{repeated term}} + z + x\bar{y} + x\bar{z} \\
 &= \underbrace{y\bar{z}(x+\bar{x})}_1 + x\bar{y} + x\bar{z} + z \\
 &= y\bar{z} + x\bar{y} + \underbrace{x\bar{z}+z}_{x+z} \quad // \text{Theorem 16.9} \\
 &= y\bar{z} + x\bar{y} + x + z \quad // \text{Theorem 16.9} \\
 &= \underbrace{y + x\bar{y}}_{y+x} + x + z \quad // \text{Theorem 16.9} \\
 &= y + x + x + z \\
 &= \underbrace{x + y + z}_{\text{repeated}}
 \end{aligned}$$

Question	Max	Score
1. True/False	10	
2. Three-variable K-map	5	
3. Truth Tables	15	
4. Number Conversions	20	
5. Minimization	10	
6. Venn Diagrams	15	
7. SOP with K-Map	15	
8. NAND/NOR Logic	10	
9. Seven-Segment Display	15	
10. Minimization	15	
TOTAL:	130	