

# Sample Solutions

CprE 281: Digital Logic  
Midterm 2: Friday Oct. 26, 2018

Student Name: \_\_\_\_\_ Student ID Number: \_\_\_\_\_


Lab Section: Mon 12-3(P) Tue 11-2(U) Wed 8-11(J) Thur 11-2(Q) Fri 11-2(G)  
(circle one) Tue 2-5(M) Wed 11-2(W) Thur 11-2(V)  
Tue 2-5(Z) Wed 6-9(T) Thur 2-5(L)  
Thur 5-8(K)

## 1. True/False Questions (10 x 1p each = 10p)

- (a) I forgot to write down my name or student ID number or lab section. TRUE / FALSE
- (b) The total delay through a half-adder is 2 gate delays. TRUE / FALSE
- (c) The two inputs of a gated D-latch are called S and R. TRUE / FALSE
- (d) A register file can have more than one read port. TRUE / FALSE
- (e) A JK flip-flop reduces to a T flip-flop when J=K. TRUE / FALSE
- (f) The undesirable state of a basic latch with NAND gates is when  $Q = \overline{Q} = 1$ . TRUE / FALSE
- (g) A priority encoder has one-hot encoded inputs. TRUE / FALSE
- (h) In 32-bit IEEE 754 format, 11000000011000...0 is equal to -3. TRUE / FALSE
- (i) A T flip-flop and an XOR gate can be used to implement a D flip-flop. TRUE / FALSE
- (j) In binary, Yoda is more than 10000000000 years old. TRUE / FALSE

 
## 2. Venn Diagrams (5 x 1p each = 5p)

Write the Boolean expression that corresponds to each Venn diagram below each figure.




(A)

$$X \cdot Y$$

 


(B)

$$Y + Z$$

 

(C)

$$X \overline{Y}$$

 


(D)

$$\overline{X} \overline{Y} Z$$

OR

$$\overline{(X + Y)} Z$$

 

(E)

$$(X + Z) \overline{Y}$$

3. Minimization (3 x 4p each = 12p)


(a) Draw the truth table for the function  $f(a, b, c, d) = \sum m(1, 2, 4, 6, 7, 14, 15) + D(5, 10)$

(b) Use a K-Map to derive the minimum cost SOP expression for f.


(c) Use a K-Map to derive the minimum cost POS expression for f.

(a)

#	a	b	c	d	f
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	d
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	d
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

 
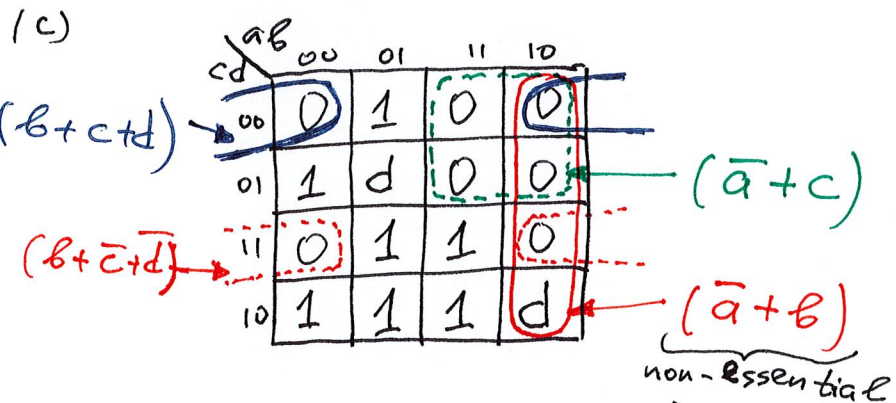
$$f = \bar{a}b + \bar{a}cd + bc + cd\bar{d}$$




$$f = (b+c+d) \cdot (b+\bar{c}+\bar{d}) \cdot (\bar{a}+c) \cdot (\bar{a}+b)$$

4. Fill in the Blanks (2 x 4p = 8p).


Given the inputs, outputs, and wires of a familiar circuit, fill in the names of the logic gates inside the square blocks. Also, write the name of each circuit.

a)

 

Circuit name: Gated latch with NOR gates


b)

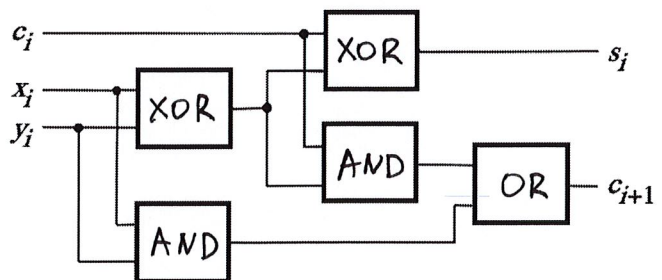


Circuit name: Full adder

5. Circuits (5p + 10p = 15p).

 (a) Draw the wiring diagram for an  $\overline{\overline{S}} \overline{\overline{R}}$  - Latch. Label all inputs, outputs, and pins.



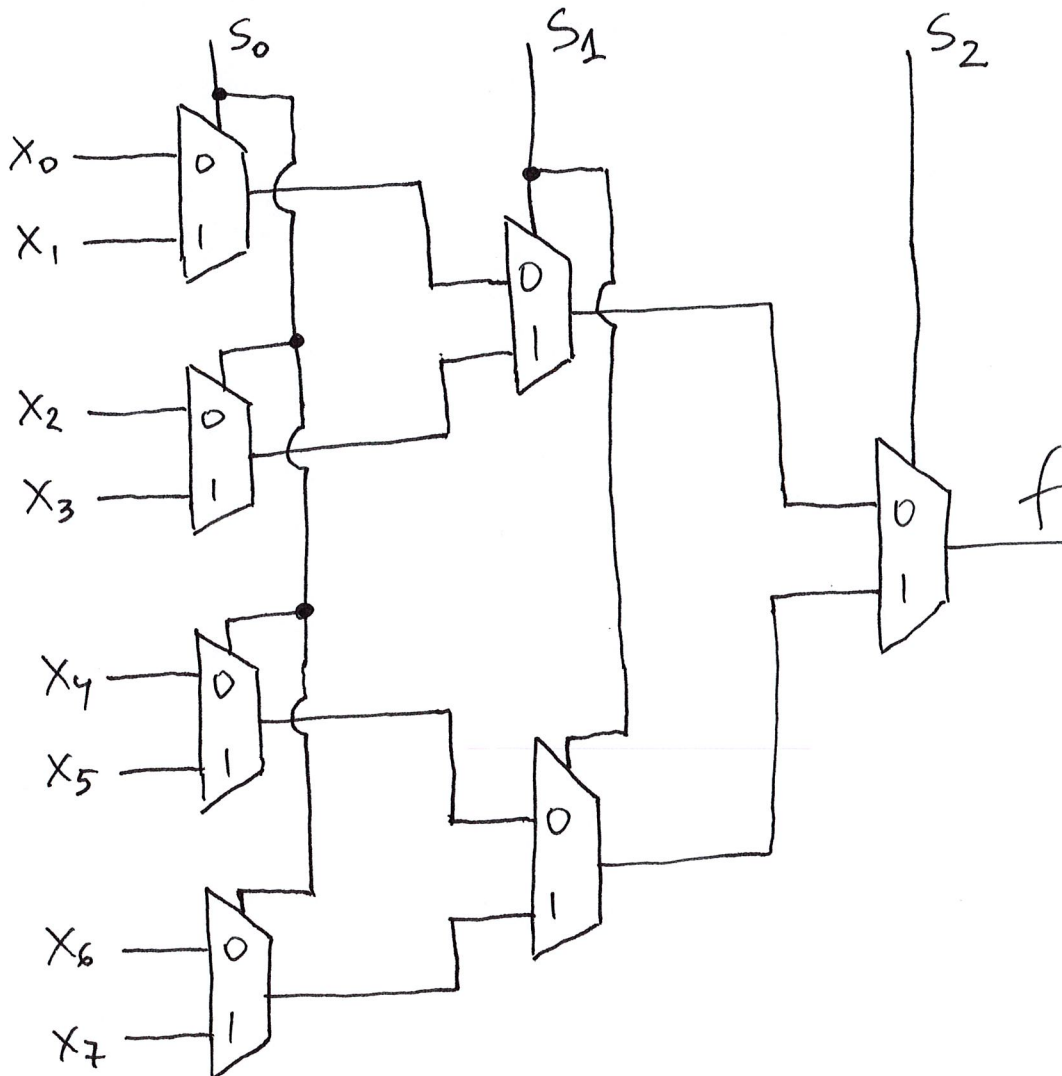(b) Draw the circuit for an 8-to-1 multiplexer using only 2-to-1 multiplexers. Clearly label all inputs, outputs, and pins. Hint: think of a tree.







6. Computations with Adders ( 5 x 3p each = 15p)

In all problems below, the binary numbers are stored in 2's complement representation.

For each of the following, assign either a 0 or a 1 to each input and output of the 5-bit adder such that it computes the given expression. The problem in a) is already solved.



a)  $(+5) + (+6) = +11$

b)  $(+12) + (+2) = +14$

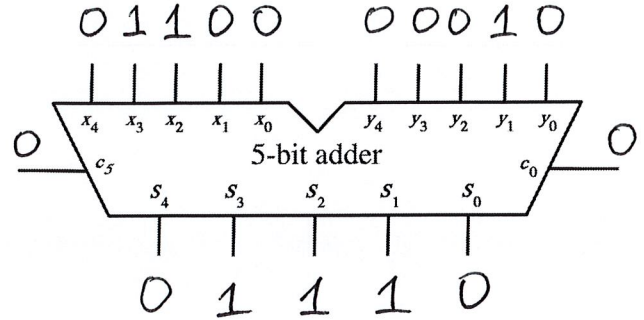 



c)  $(-11) + (+7) = -4$

d)  $(+15) + (-7) = +8$

  

e)  $(+9) + (-13) = -4$


f)  $(-3) - (-10) = +7$

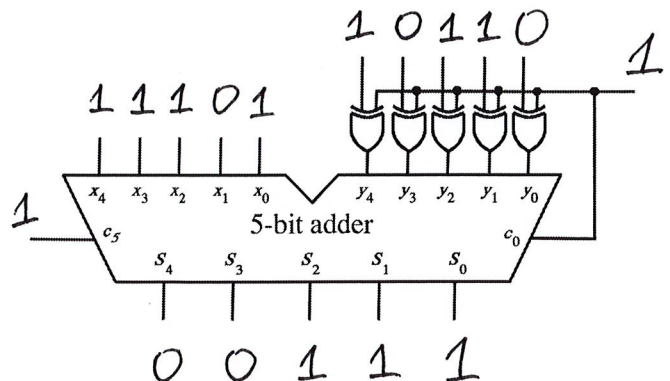 


7. Flip-Flops and Timing Diagrams ( 3 x 5p = 15p)

Complete the timing diagram for the specified flip-flop such that the output Q will be as indicated. Assume that the input signal can change only on the vertical lines. Also, assume that the setup time  $t_{su}$  and the hold time  $t_h$  are each equal to the width of one square.

 
a) Complete the timing diagram for the D input to a positive-edge triggered D flip-flop.



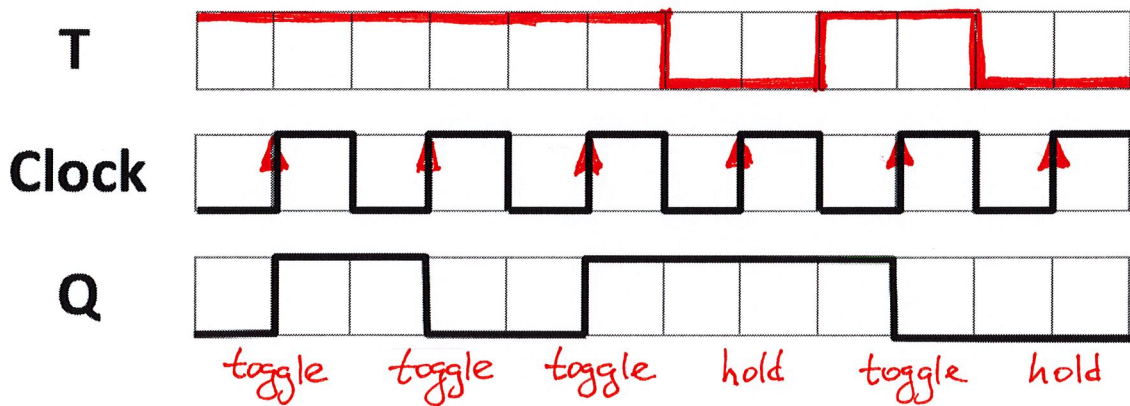b) Complete the timing diagram for the T input to a positive-edge triggered T flip-flop.



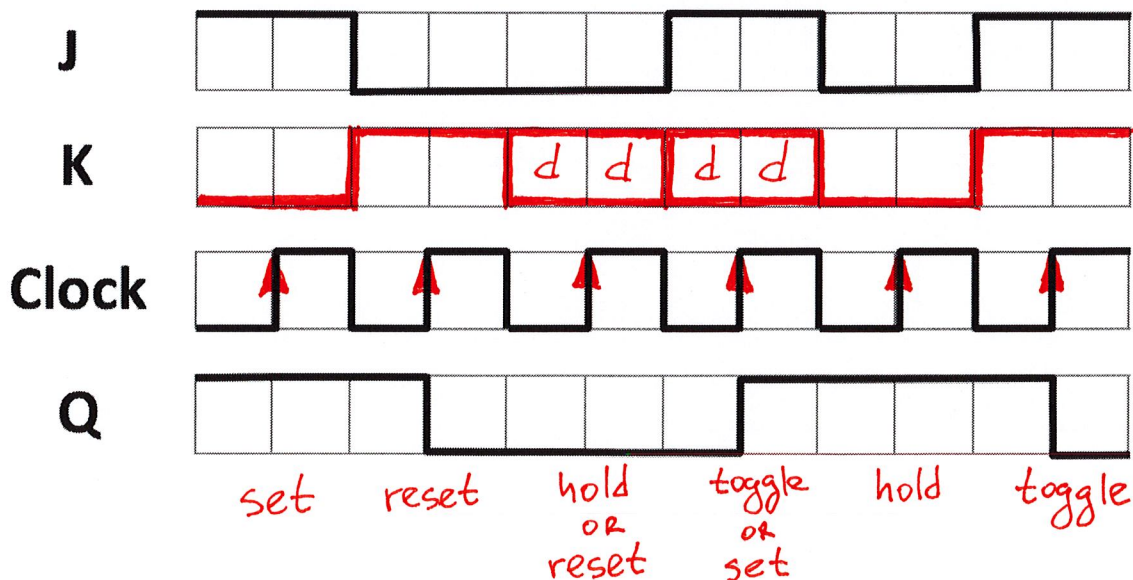c) Complete the timing diagram for the K input to a positive-edge triggered JK flip-flop.



8. Multiplexers (3 x 5p each = 15p)


a) Draw the truth table for the function  $f(a, b, c) = a c + a \bar{b} + \bar{b} c$ .

a	b	c	$ac$	$a\bar{b}$	$\bar{b}c$	f
0	0	0	0	0	0	0
0	0	1	0	0	1	1
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	0	0	0
1	1	1	1	0	0	1


b) Implement this function using a minimal number of 2-to-1 multiplexers. You must use only 2-to-1 multiplexers and no other logic gates. Assume that the signals a, b, and c are available only in their non-inverted form as well as the constants 0 and 1. Clearly label all inputs, outputs, and pins.

b	c	g
0	0	0
0	1	1
1	0	0
1	1	0

b	c	h
0	0	1
0	1	1
1	0	0
1	1	1

 

 c) Implement this function using a minimal number of 8-to-1 multiplexers. Clearly label all inputs, outputs, and pins.





Some of these problems have more than one solution.

### 9. Alternative Implementation (10p)

Implement the logic expression in each sub-problem in three different ways: 1) using a 2-to-1 multiplexer; 2) using NAND-NAND logic; and 3) using NOR-NOR logic. In this problem, you are not allowed to use any other logic gates. Assume that  $a$  and  $b$  are available in both their inverted and non-inverted form, along with the constants 0 and 1. If some implementation is not possible, then indicate that with words. Label all inputs and outputs.

a) Implement in three different ways:  $f(a,b) = a + b$ .

a	b	f
0	0	0
0	1	1
1	0	1
1	1	1




SOP

$$f = a + b = a \cdot 1 + b \cdot 1$$

POS

$$f = (a + b) = (a + b) \cdot (1 + 1)$$

a	b	f
0	0	0
0	1	1
1	0	1
1	1	1

   

b) Implement in three different ways:  $f(a,b) = a \bar{b}$ .

a	b	f
0	0	0
0	1	0
1	0	1
1	1	0




SOP

$$f = a \bar{b} = a \cdot \bar{b} + 0 \cdot 0$$

POS

$$f = (a) \cdot (\bar{b}) = (a + 0) \cdot (\bar{b} + 0)$$

a	b	f
0	0	0
0	1	0
1	0	1
1	1	0

   

c) Implement in three different ways:  $f(a,b) = \bar{a} \bar{b} + a b$ .




a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

SOP

POS


$$f = (a + \bar{b}) \cdot (\bar{a} + b)$$

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

   


 10. Faulty Circuits ( 3p + 3p + 4p = 10p )

The circuits below have a manufacturing defect such that one of their wires is broken and is permanently stuck to zero volts (ground). Your task is to find a set of input and output patterns that can be used to distinguish between a working circuit and a faulty circuit. The figure below gives an example in which the second input of the AND gate may be faulty.




Normal Circuit

 


Faulty Circuit

(a)

 


Normal Circuit

3 different solutions

 


Faulty Circuit

(b)

 


Normal Circuit

 


Faulty Circuit

2 different solutions

(c)

 

Normal Circuit

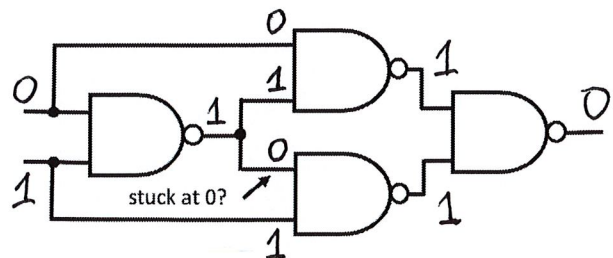

Faulty Circuit




### 11. Register (15p)

Complete the following circuit diagram by drawing wires and adding any other circuits or logic gates to implement a 3-bit register. The register has two control inputs ( $C_1$  and  $C_0$ ), three parallel input lines ( $I_2$ ,  $I_1$ , and  $I_0$ ), and three output lines ( $Q_2$ ,  $Q_1$ , and  $Q_0$ ). Depending on the values of  $C_1$  and  $C_0$ , the register performs one of the following four operations:

$C_1$	$C_0$	Operation
0	0	Hold the current value (i.e., $Q_2$ $Q_1$ $Q_0$ remain unchanged)
0	1	Cyclic shift left (i.e., new $Q_2=Q_1$ , new $Q_1=Q_0$ , new $Q_0=Q_2$ )
1	0	Load new data (i.e., new $Q_2=I_2$ , new $Q_1=I_1$ , new $Q_0=I_0$ )
1	1	Invert all bits (i.e., new $Q_2=\overline{Q_2}$ , new $Q_1=\overline{Q_1}$ , new $Q_0=\overline{Q_0}$ )

 Clearly label all inputs, outputs, and pins.



Note that these are T flip-flops!  
 Also, note that XOR + T flip-flop  $\Rightarrow$  D flip-flop.

<b>Question</b>	<b>Max</b>	<b>Score</b>
1. True/False	10	
2. Venn Diagrams	5	
3. Minimization with K-Maps	12	
4. Fill in the Blanks	8	
5. Circuits	15	
6. Computations with Adders	15	
7. Flip-Flops	15	
8. Multiplexers	15	
9. Alternative Implementation	10	
10. Faulty Circuits	10	
11. Register	15	
<b>TOTAL:</b>	<b>130</b>	