



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Minimization

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff


- **HW4 is out**
- **It is due on Monday Sep 17 @ 4 pm**
- **It is posted on the class web page**
- **I also sent you an e-mail with the link.**

Example:
K-Map for the 2-1 Multiplexer


2-1 Multiplexer (Definition)

- Has two inputs: x_1 and x_2
- Also has another input line s
- If $s=0$, then the output is equal to x_1
- If $s=1$, then the output is equal to x_2

Circuit for 2-1 Multiplexer

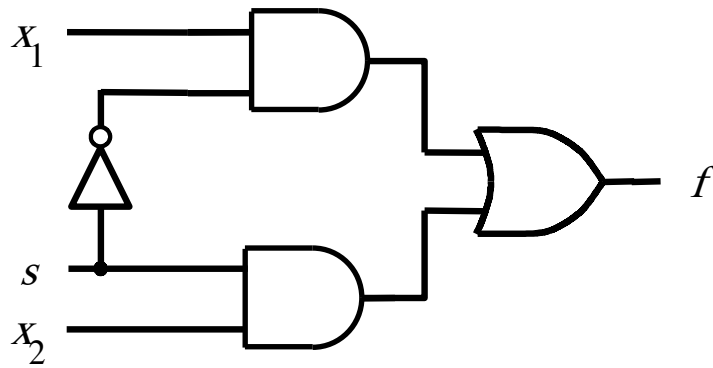

(b) Circuit

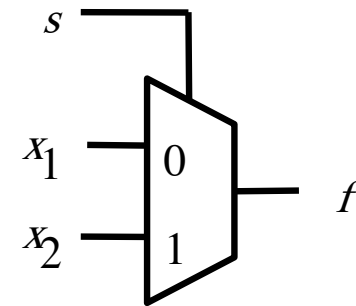

(c) Graphical symbol

Truth Table for a 2-1 Multiplexer

s x_1 x_2	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Let's Draw the K-map

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

[Figure 2.33a from the textbook]

Let's Draw the K-map

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

Let's Draw the K-map

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

		$x_1 x_2$			
		00	01	11	10
s	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

Let's Draw the K-map

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

		x_1x_2			
		00	01	11	10
s	0	0	1	0	0
	1	0	1	1	1

Let's Draw the K-map

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

A Karnaugh map for the function $f(s, x_1, x_2)$. The vertical axis is labeled s with values 0 and 1. The horizontal axis is labeled $x_1 x_2$ with values 00, 01, 11, and 10. The map contains 1s in the following cells: (0, 01), (0, 11), (1, 01), (1, 11), and (1, 10). Two prime implicants are circled in cyan: a vertical oval around the 1s in the 01 and 11 columns, and a horizontal oval around the 1s in the 11 and 10 rows.

$s \backslash x_1 x_2$	00	01	11	10
0	0	1	0	0
1	0	1	1	1

Let's Draw the K-map

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

$s \backslash x_1 x_2$	00	01	11	10
0	0	1	0	0
1	0	1	1	1

$$f(s, x_1, x_2) = \bar{x}_1 x_2 + s x_1$$

Let's Draw the K-map

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

$s \backslash x_1 x_2$	00	01	11	10
0	0	1	0	0
1	0	1	1	1

$$f(s, x_1, x_2) = \bar{x}_1 x_2 + s x_1$$

Something is wrong!

Compare this with the SOP derivation

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Where should we
put the negation signs?

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$	
0 0 0	0	
0 0 1	0	
0 1 0	1	$\bar{s} \ x_1 \ \bar{x}_2$
0 1 1	1	$\bar{s} \ x_1 \ x_2$
1 0 0	0	
1 0 1	1	$s \ \bar{x}_1 \ x_2$
1 1 0	0	
1 1 1	1	$s \ x_1 \ x_2$

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$	
0 0 0	0	
0 0 1	0	
0 1 0	1	$\bar{s} x_1 \bar{x}_2$
0 1 1	1	$\bar{s} x_1 x_2$
1 0 0	0	
1 0 1	1	$s \bar{x}_1 x_2$
1 1 0	0	
1 1 1	1	$s x_1 x_2$

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 (\bar{x}_2 + x_2) + s (\bar{x}_1 + x_1) x_2$$

Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 (\bar{x}_2 + x_2) + s (\bar{x}_1 + x_1) x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$

Let's Draw the K-map again

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Let's Draw the K-map again

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

Let's Draw the K-map again

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

		$x_1 x_2$			
		00	01	11	10
s	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

Let's Draw the K-map again

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

	s	$x_1 x_2$	00	01	11	10
0			m_0	m_2	m_6	m_4
1			m_1	m_3	m_7	m_5

Let's Draw the K-map again

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

		s	x_1		
	x_2	00	01	11	10
0		m_0	m_2	m_6	m_4
1		m_1	m_3	m_7	m_5

The order of the labeling matters.

Let's Draw the K-map again

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

		$s x_1$			
		00	01	11	10
x_2	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

Let's Draw the K-map again

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

		$s x_1$			
		00	01	11	10
x_2	0	0	1	0	0
	1	0	1	1	1

Let's Draw the K-map again

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

A Karnaugh map for the function $f(s, x_1, x_2)$. The vertical axis is labeled x_2 with values 0 and 1. The horizontal axis is labeled $s x_1$ with values 00, 01, 11, and 10. The map contains 1s at the following cells: (0, 01), (1, 01), (1, 11), and (1, 10). Two groups are circled in cyan: a vertical group covering the 1s at (0, 01) and (1, 01), and a horizontal group covering the 1s at (1, 11) and (1, 10). Vertical lines extend from the bottom of each group.

x_2	$s x_1$	00	01	11	10
0		0	1	0	0
1		0	1	1	1

Let's Draw the K-map again

	s	x_1	x_2	$f(s, x_1, x_2)$
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1

$s \backslash x_1$	00	01	11	10
0	0	1	0	0
1	0	1	1	1

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$

This is correct!

Two Different Ways to Draw the K-map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map

		$x_2 x_3$			
		00	01	11	10
x_1	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Another Way to Draw 3-variable K-map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map

		x_1	
		0	1
$x_2 x_3$	00	m_0	m_4
	01	m_1	m_5
	11	m_3	m_7
	10	m_2	m_6

Gray Code

- **Sequence of binary codes**
- **Neighboring lines vary by only 1 bit**

	000
	001
00	011
01	010
11	110
10	111
	101
	100

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

		$s x_1$			
		00	01	11	10
x_2	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

		$s x_1$			
		00	01	11	10
x_2	0	000	010	110	100
	1	001	011	111	101

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

		$s x_1$			
		00	01	11	10
x_2	0	000	010	110	100
	1	001	011	111	101

These two neighbors
differ only in the LAST bit

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

		$s \ x_1$			
		00	01	11	10
x_2	0	000	010	110	100
	1	001	011	111	101

These two neighbors
differ only in the LAST bit

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

		$s \ x_1$			
		00	01	11	10
x_2	0	000	010	110	100
	1	001	011	111	101

These two neighbors
differ only in the FIRST bit

Gray Code & K-map


	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

x_2	s	x_1				
			00	01	11	10
0			000	010	110	100
1			001	011	111	101

These two neighbors
differ only in the FIRST bit

Adjacency Rules

$x_2 \backslash s x_1$	00	01	11	10
0	000	010	110	100
1	001	011	111	101

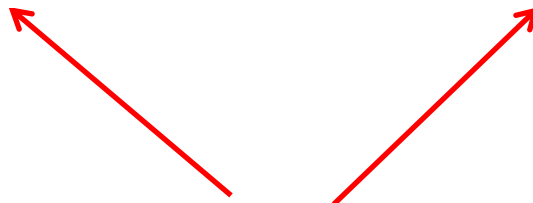

adjacent
columns

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

		$s \ x_1$			
		00	01	11	10
x_2	0	000	010	110	100
	1	001	011	111	101

These four neighbors
differ in the FIRST and LAST bit

They are similar in their MIDDLE bit

Gray Code & K-map


	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

x_2	$s x_1$			
	00	01	11	10
0	000	010	110	100
1	001	011	111	101

These four neighbors
differ in the FIRST and LAST bit


They are similar in their MIDDLE bit

A four-variable Karnaugh map

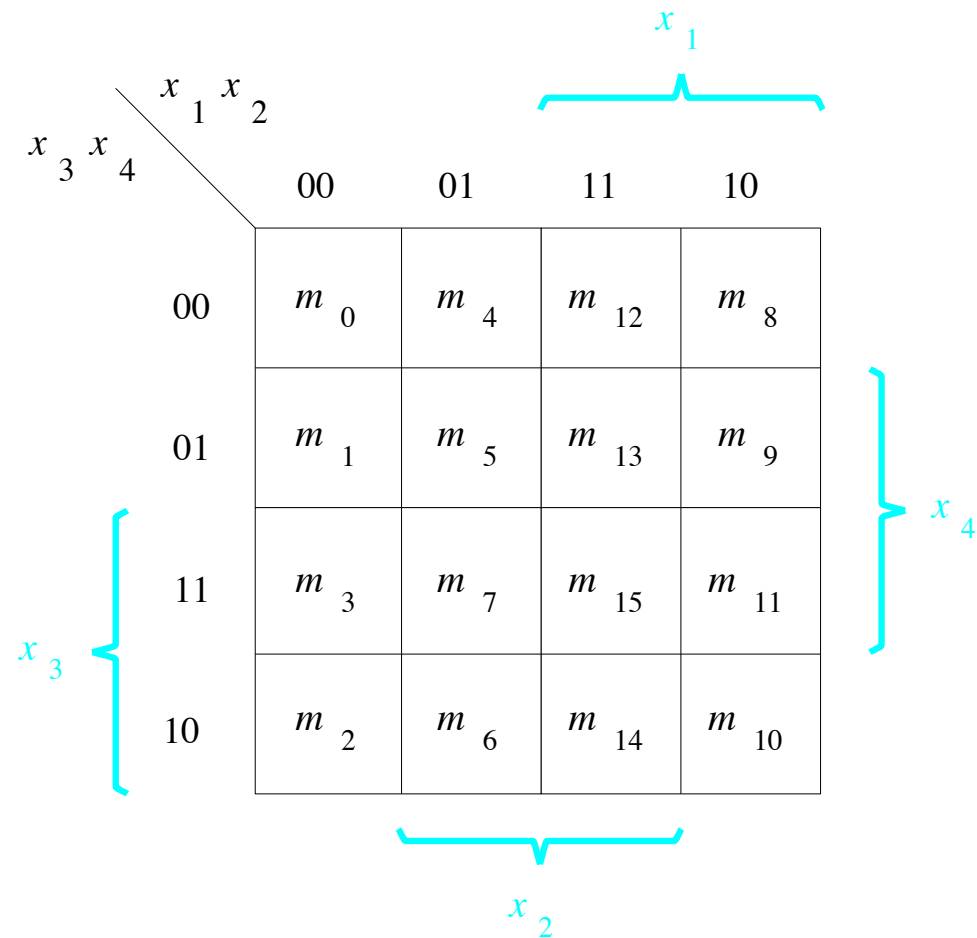

A four-variable Karnaugh map

x1	x2	x3	x4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

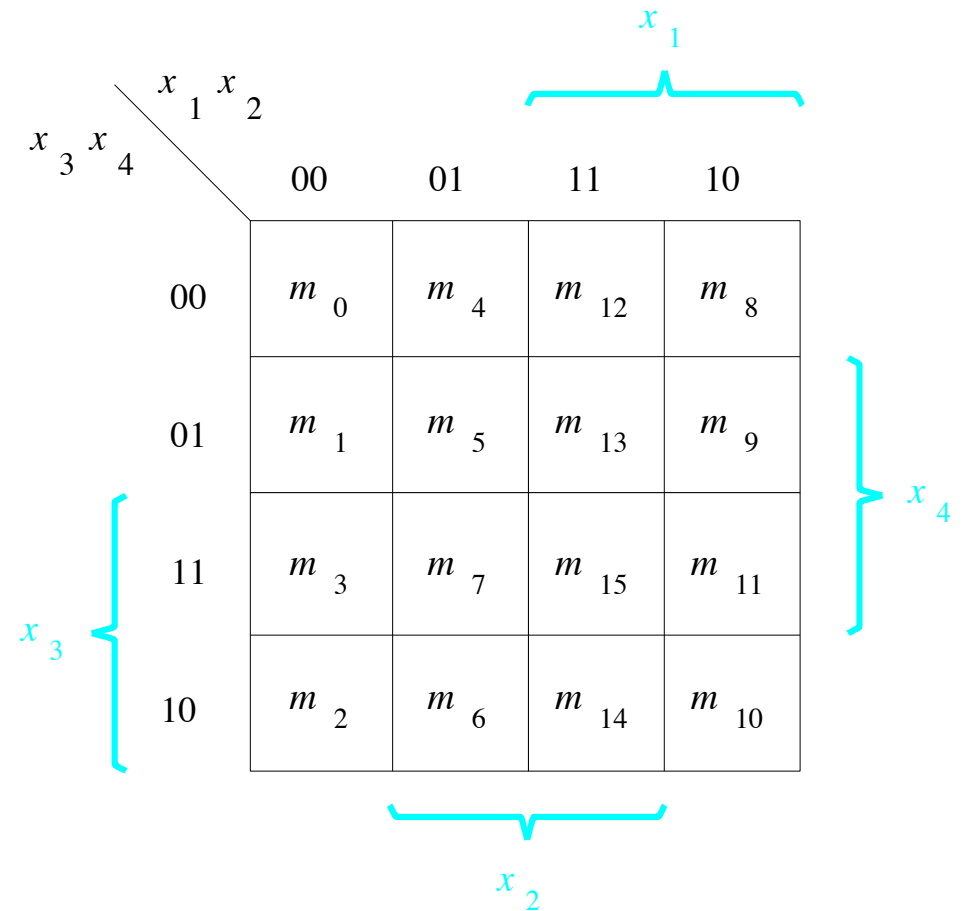

Adjacency Rules

x_3	x_1x_2	00	01	11	10
0	m_0	m_2	m_6	m_4	
1	m_1	m_3	m_7	m_5	

adjacent
columns

x_3x_4	x_1x_2	00	01	11	10
00	m_0	m_4	m_{12}	m_8	
01	m_1	m_5	m_{13}	m_9	
11	m_3	m_7	m_{15}	m_{11}	
10	m_2	m_6	m_{14}	m_{10}	

adjacent
columns


adjacent
rows

Adjacency Rules

		x_1x_2			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5



adjacent
columns

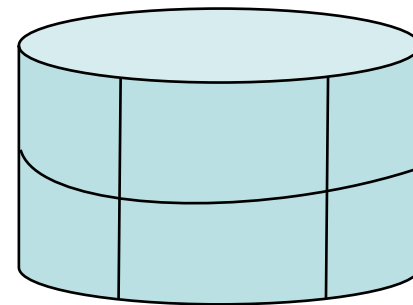


As if the K-map were
drawn on a cylinder

Adjacency Rules

		x_1x_2			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5



adjacent
columns

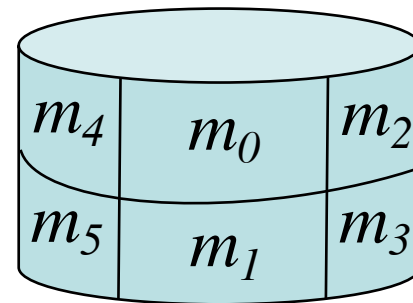


As if the K-map were
drawn on a cylinder

Adjacency Rules

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	m_0	m_4	m_{12}	m_8
01	m_1	m_5	m_{13}	m_9
11	m_3	m_7	m_{15}	m_{11}
10	m_2	m_6	m_{14}	m_{10}

adjacent
rows

adjacent
columns

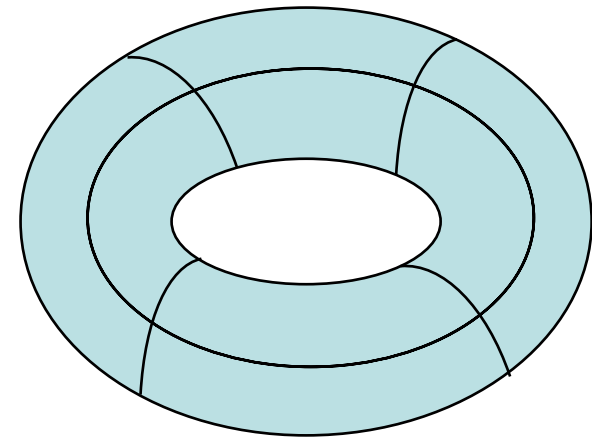


As if the K-map were
drawn on a torus

Adjacency Rules

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	m_0	m_4	m_{12}	m_8
01	m_1	m_5	m_{13}	m_9
11	m_3	m_7	m_{15}	m_{11}
10	m_2	m_6	m_{14}	m_{10}

adjacent
rows


adjacent
columns

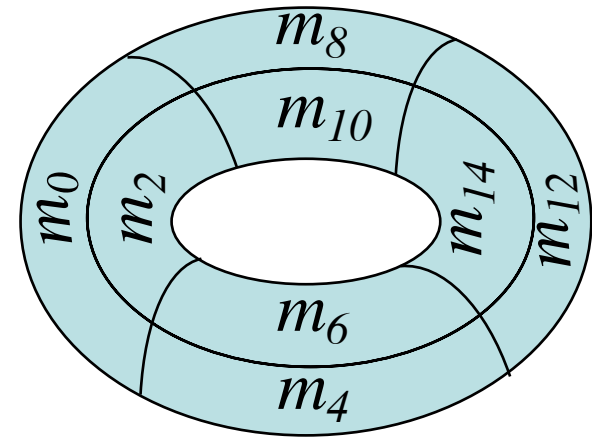

As if the K-map were
drawn on a torus


Gray Code & K-map

x1	x2	x3	x4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

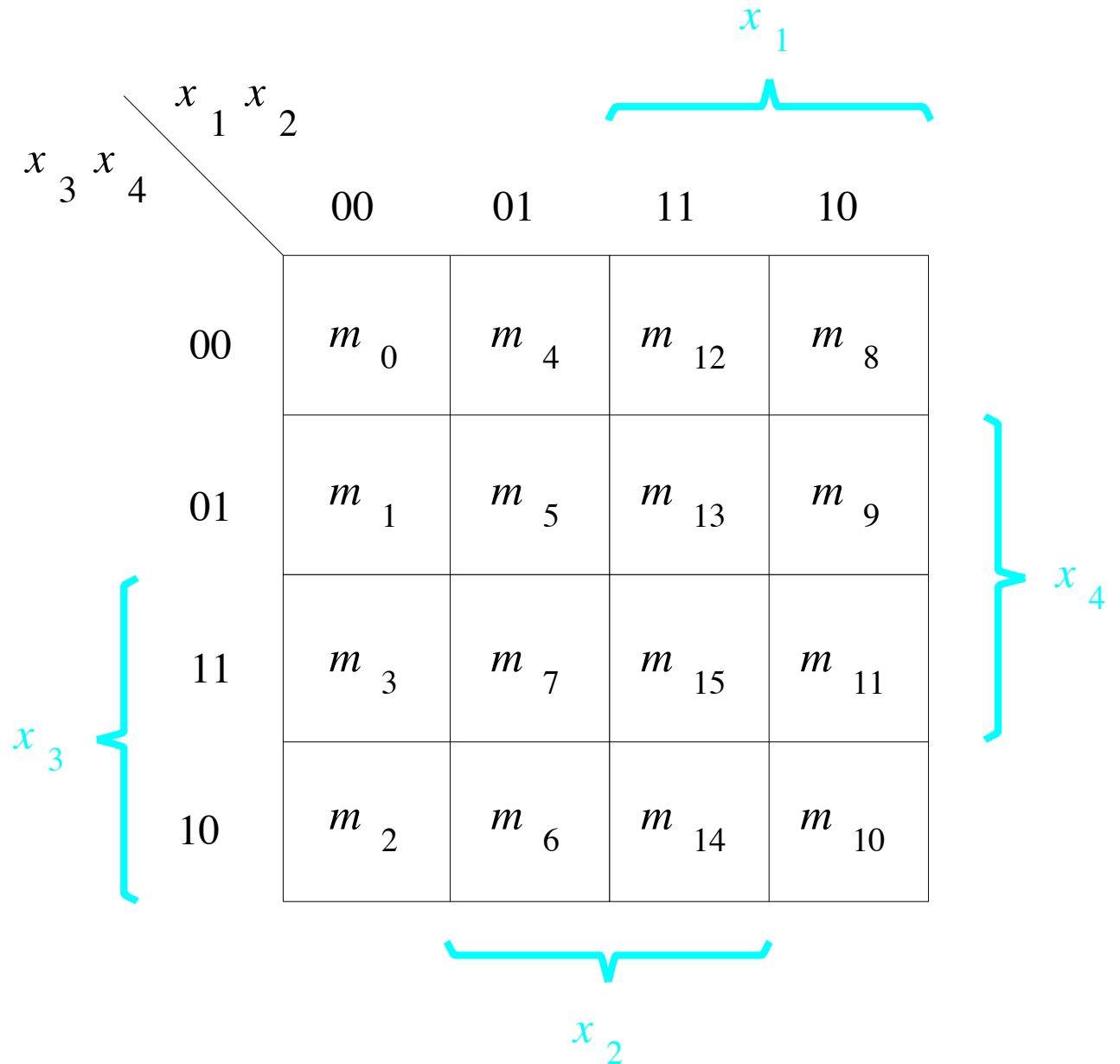


Gray Code & K-map


x1	x2	x3	x4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
<hr/>				
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
<hr/>				
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
<hr/>				
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

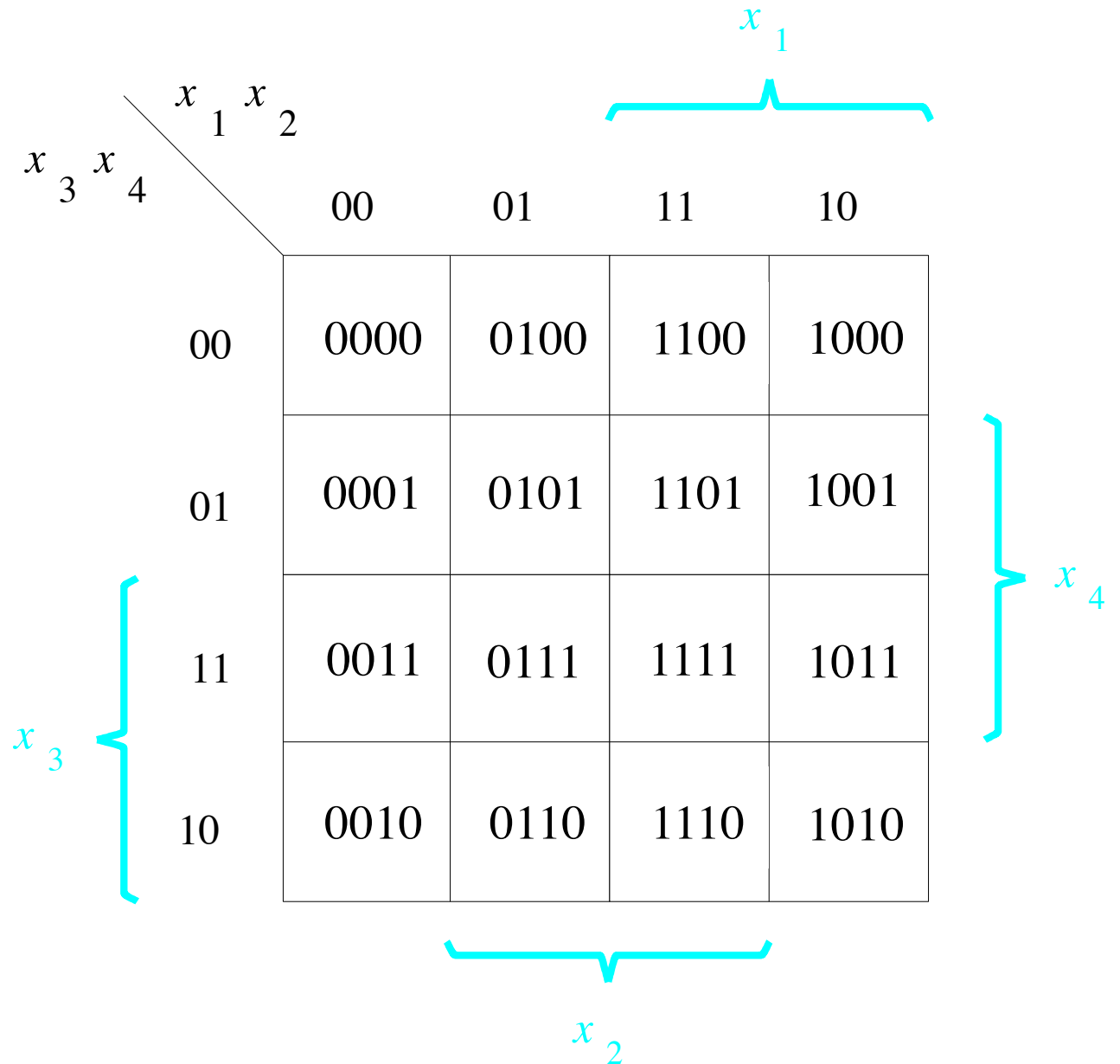

Example of a four-variable Karnaugh map

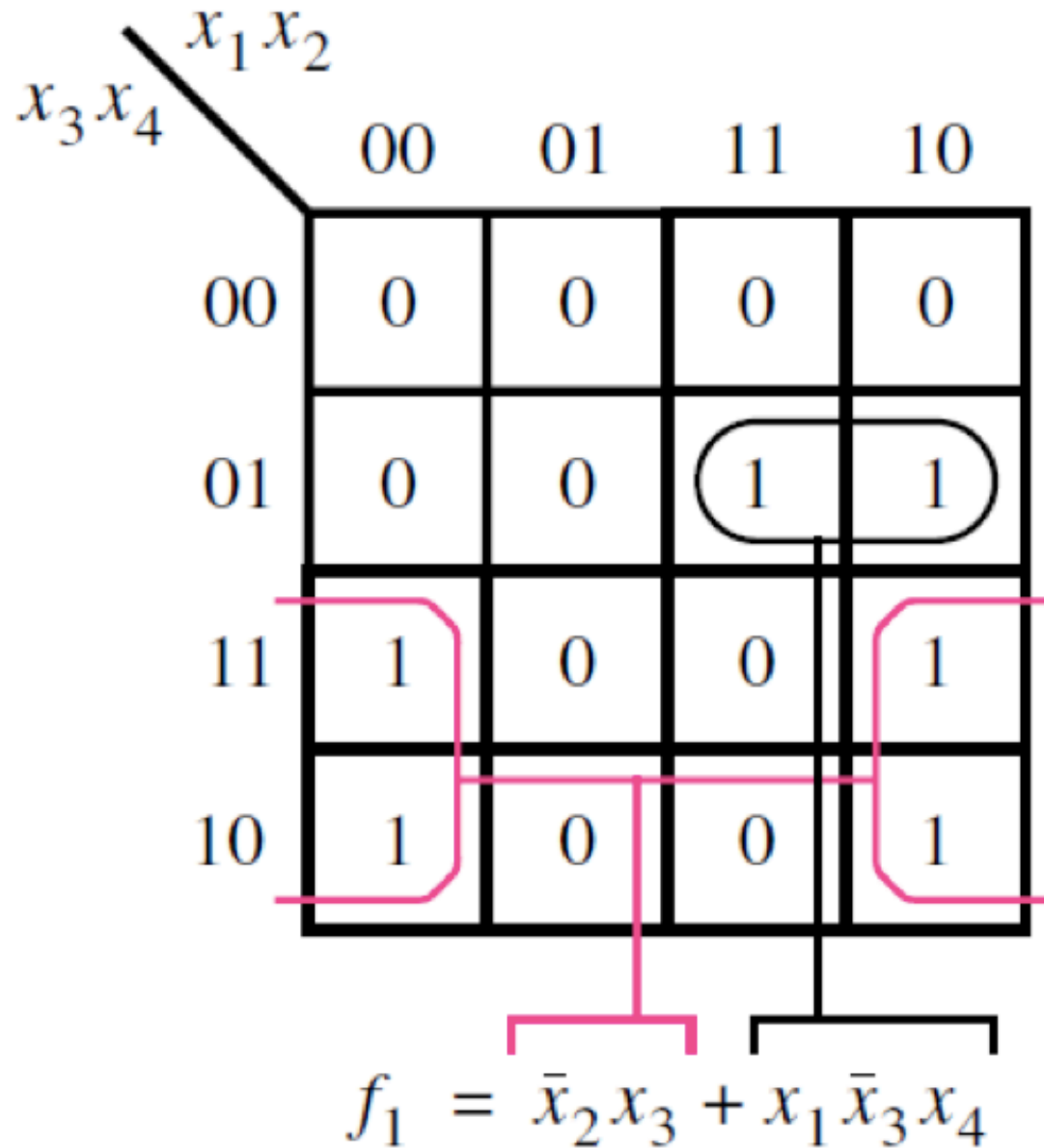

Example of a four-variable Karnaugh map

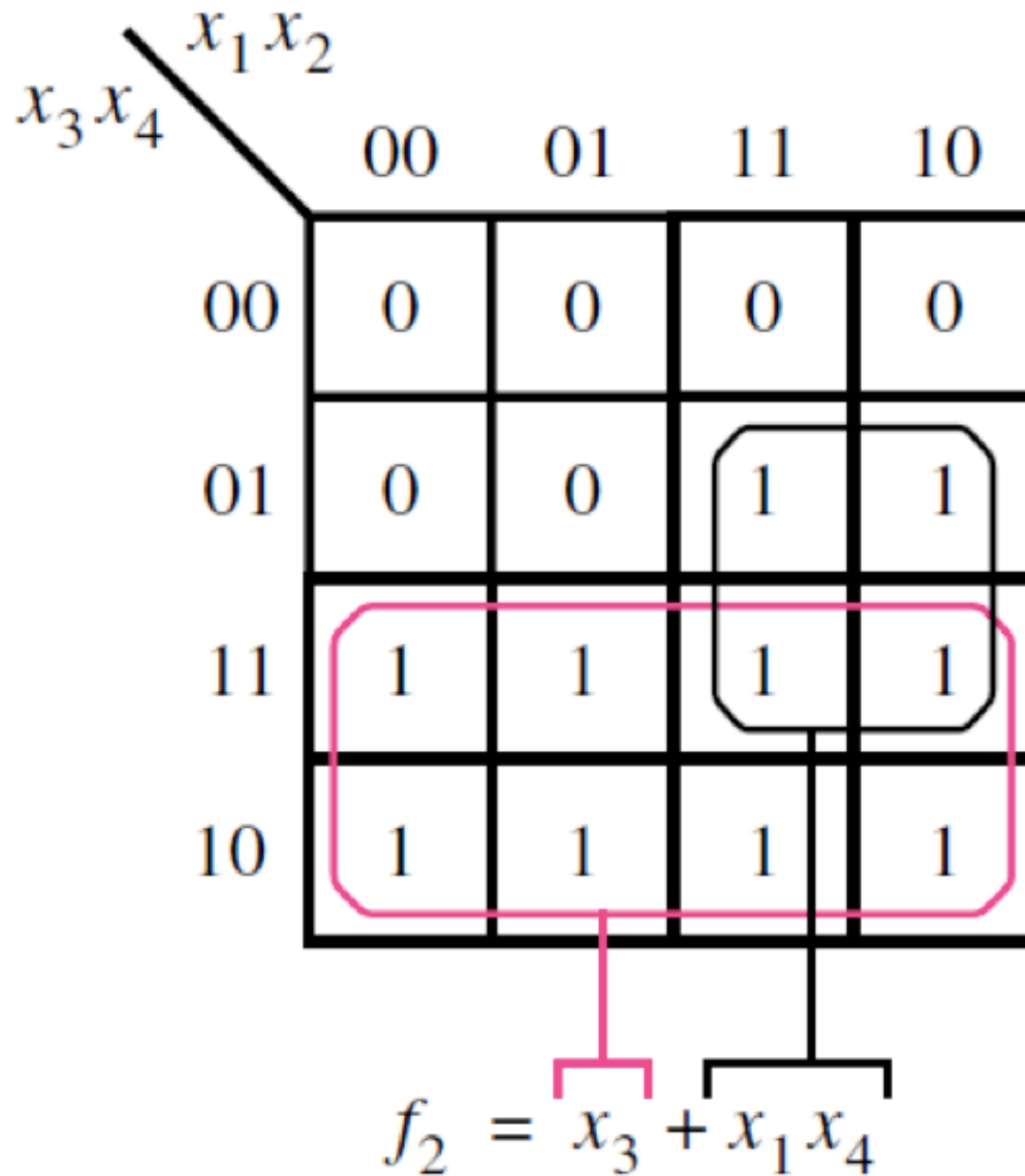

Strategy For Minimization

Grouping Rules

- **Group “1”s with rectangles**
- **Both sides a power of 2:**
 - **1x1, 1x2, 2x1, 2x2, 1x4, 4x1, 2x4, 4x2, 4x4**
- **Can use the same minterm more than once**
- **Can wrap around the edges of the map**
- **Some rules in selecting groups:**
 - **Try to use as few groups as possible to cover all “1”s.**
 - **For each group, try to make it as large as you can (i.e., if you can use a 2x2, don't use a 2x1 even if that is enough).**

Terminology

Literal: a variable, complemented or uncomplemented

Some Examples:

- \bar{X}_1
- X_2

Terminology

- **Implicant: product term that indicates the input combinations for which the function output is 1**

- **Example**

- \bar{x}_1 - indicates that $\bar{x}_1\bar{x}_2$ and \bar{x}_1x_2 yield output of 1

$x_2 \backslash x_1$	0	1
0	1	0
1	1	0

Terminology

- **Prime Implicant**

- Implicant that cannot be combined into another implicant with fewer literals

- **Some Examples**

x_3 \ $x_1 x_2$	00	01	11	10
0	0	1	1	1
1	1	1	1	0

Not prime

x_3 \ $x_1 x_2$	00	01	11	10
0	0	1	1	1
1	1	1	1	0

Prime

Terminology

- **Essential Prime Implicant**
 - Prime implicant that includes a minterm not covered by any other prime implicant
 - **Some Examples**

A Karnaugh map for a 3-variable function with variables x_1 , x_2 , and x_3 . The map is a 2x4 grid. The columns are labeled $x_1 x_2$ with values 00, 01, 11, and 10. The rows are labeled x_3 with values 0 and 1. The cells contain the following values: (0,00)=0, (0,01)=1, (0,11)=1, (0,10)=1, (1,00)=1, (1,01)=1, (1,11)=0, (1,10)=0. There are four prime implicants highlighted: a blue circle around the cell (0,01), a red circle around the cell (0,11), a red circle around the cell (0,10), and a red circle around the cell (1,00). The cell (1,01) is also circled in blue.

$x_3 \backslash x_1 x_2$	00	01	11	10
0	0	1	1	1
1	1	1	0	0

Terminology

- **Cover**

- **Collection of implicants that account for all possible input valuations where output is 1**

- **Ex. $x_1' x_2 x_3 + x_1 x_2 x_3' + x_1 x_2' x_3'$**

- **Ex. $x_1' x_2 x_3 + x_1 x_3'$**

		$x_1 x_2$			
		00	01	11	10
x_3	0	0	0	1	1
	1	0	1	0	0

Example


- Give the Number of
 - Implicants?
 - Prime Implicants?
 - Essential Prime Implicants?

x_3 \ $x_1 x_2$	00	01	11	10
0	1	1	0	0
1	1	1	1	0

Why concerned with minimization?

- **Simplified function**
- **Reduce the cost of the circuit**
 - **Cost: Gates + Inputs**
 - **Transistors**

Three-variable function $f(x_1, x_2, x_3) = \sum m(0, 1, 2, 3, 7)$

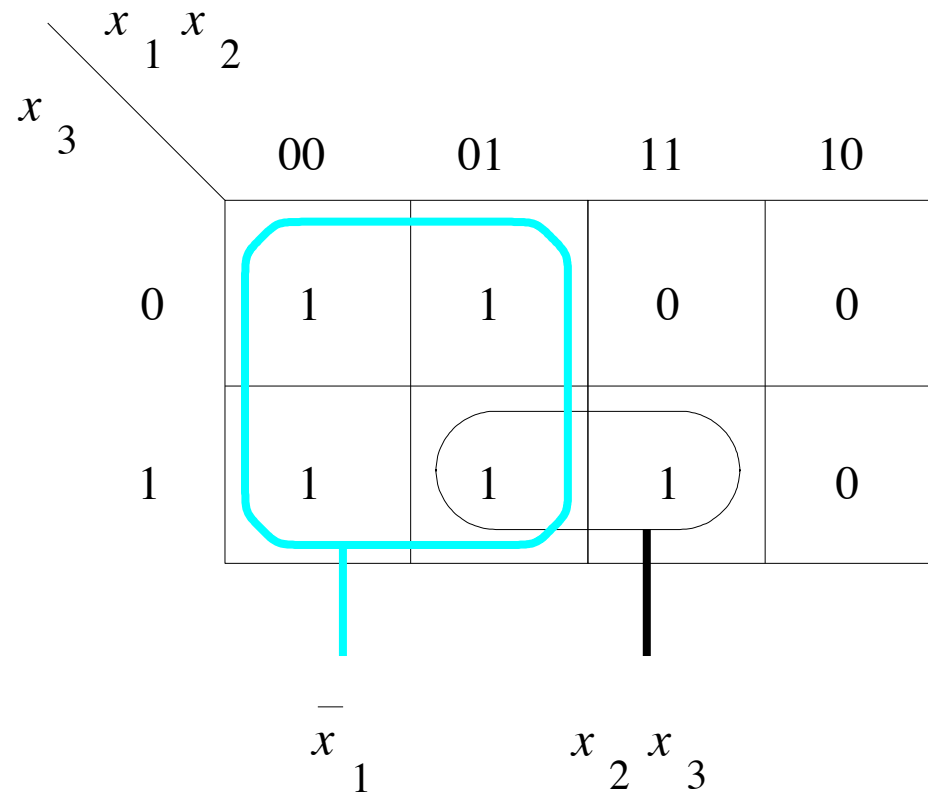


[Figure 2.56 from the textbook]


Example

		$x_1 x_2$			
		x_3	x_4		
		00	01	11	10
		00	1	1	
01		1	1		
11			1	1	
10	1			1	


Example

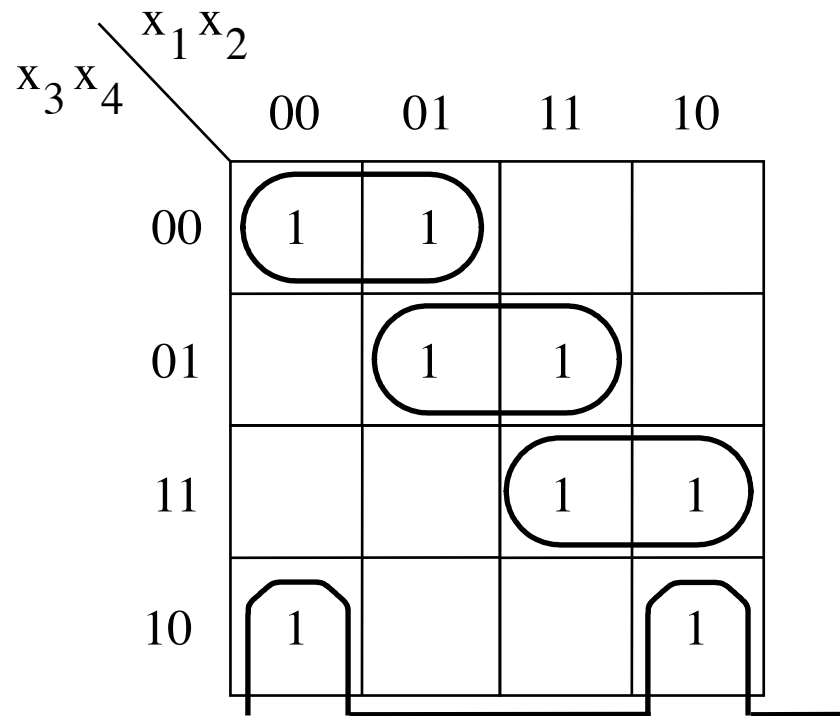

Example

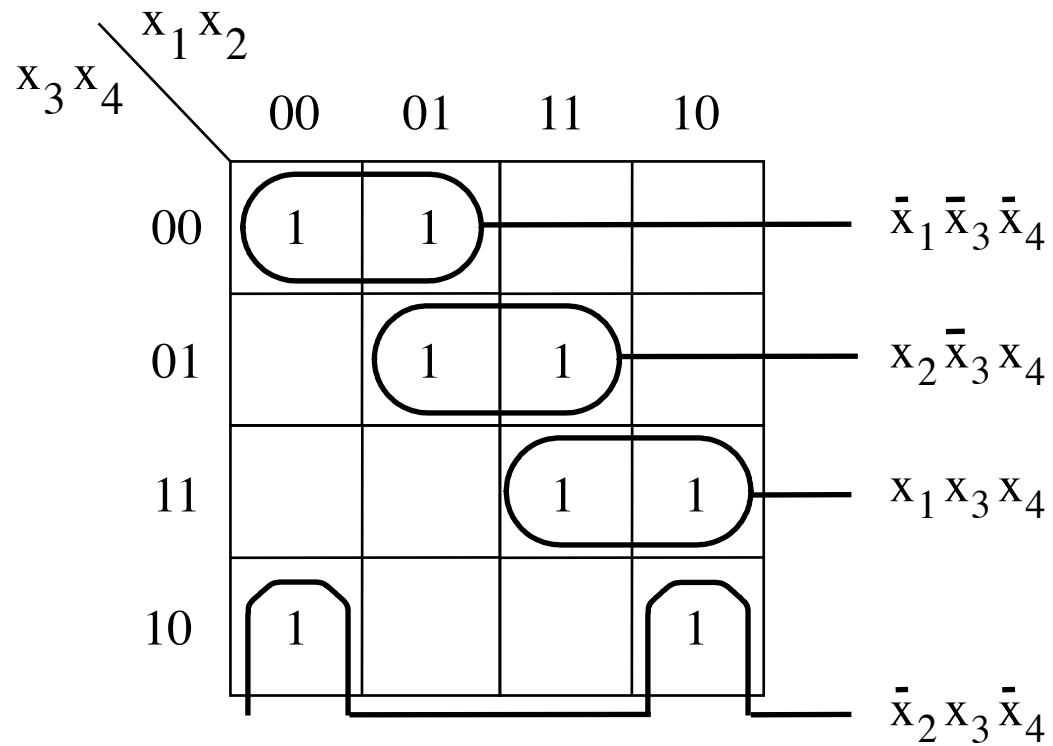

Example

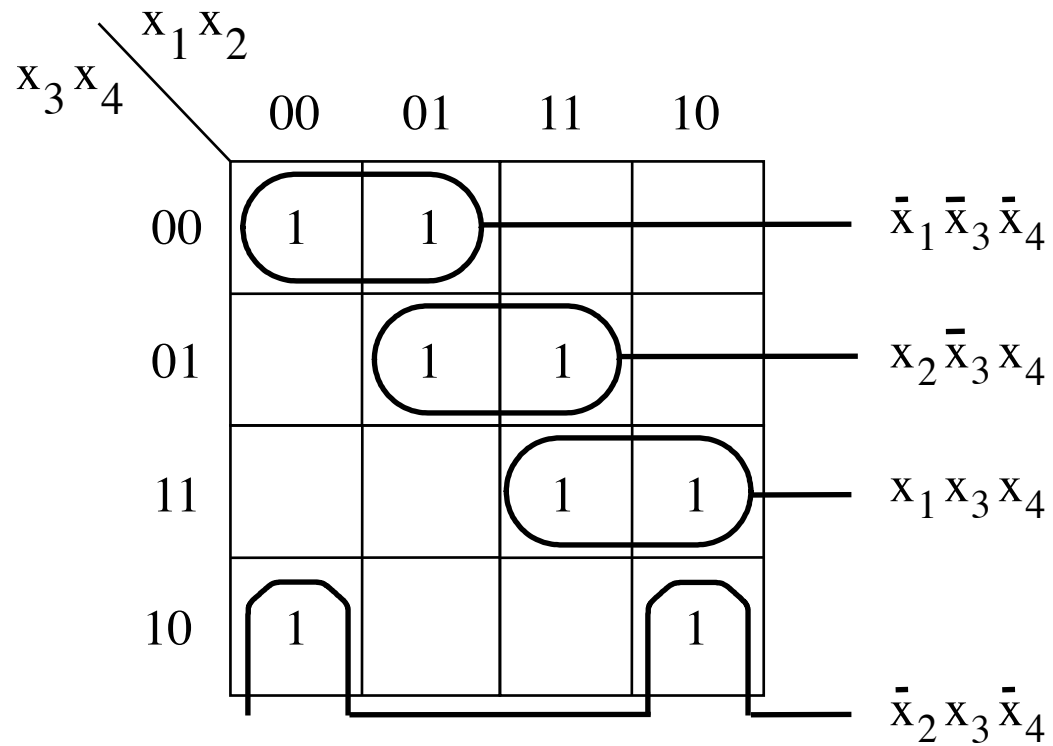


$$f = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_2 \bar{x}_3 x_4 + x_1 x_3 x_4 + \bar{x}_2 x_3 \bar{x}_4$$


Example: Another Solution

$x_3 x_4$		$x_1 x_2$			
		00	01	11	10
00	1	1			
01		1	1		
11			1	1	
10	1			1	


Example: Another Solution

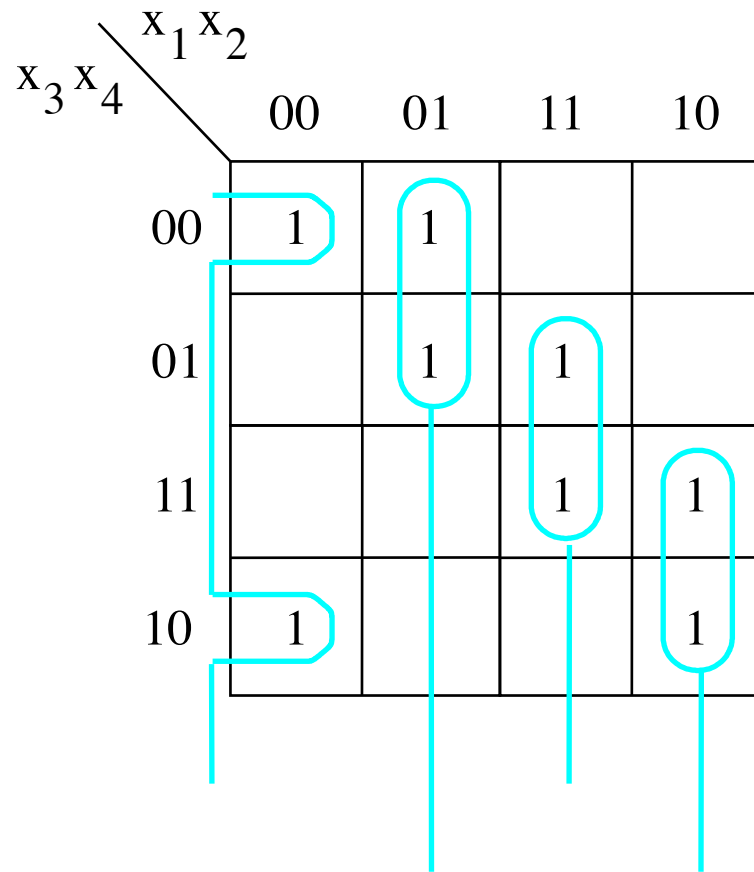

Example: Another Solution

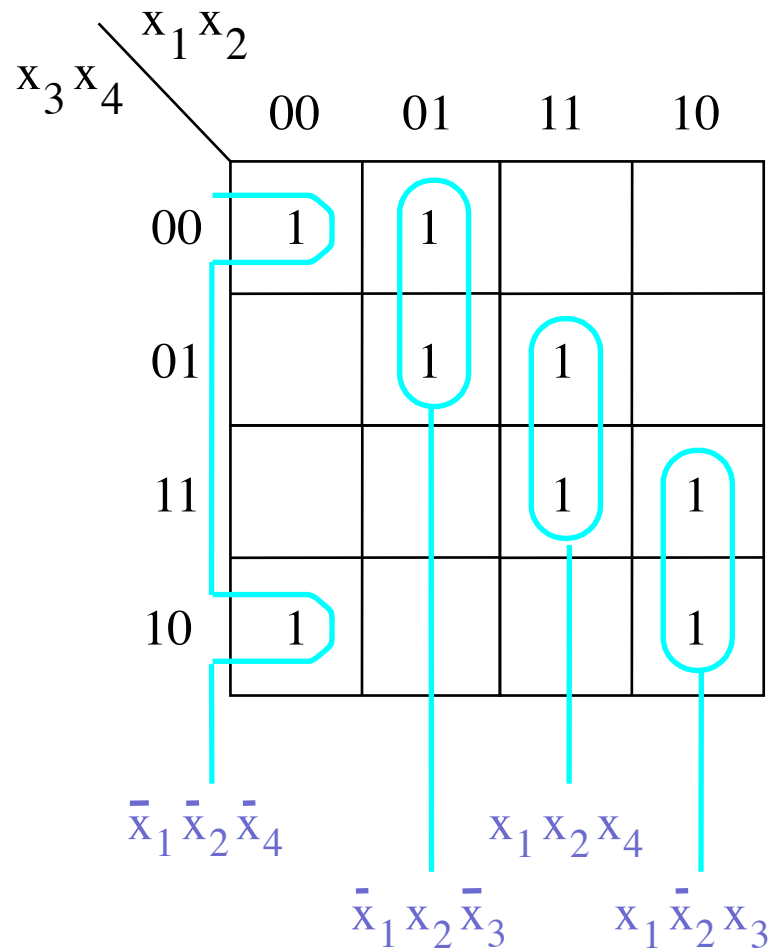


Example: Another Solution

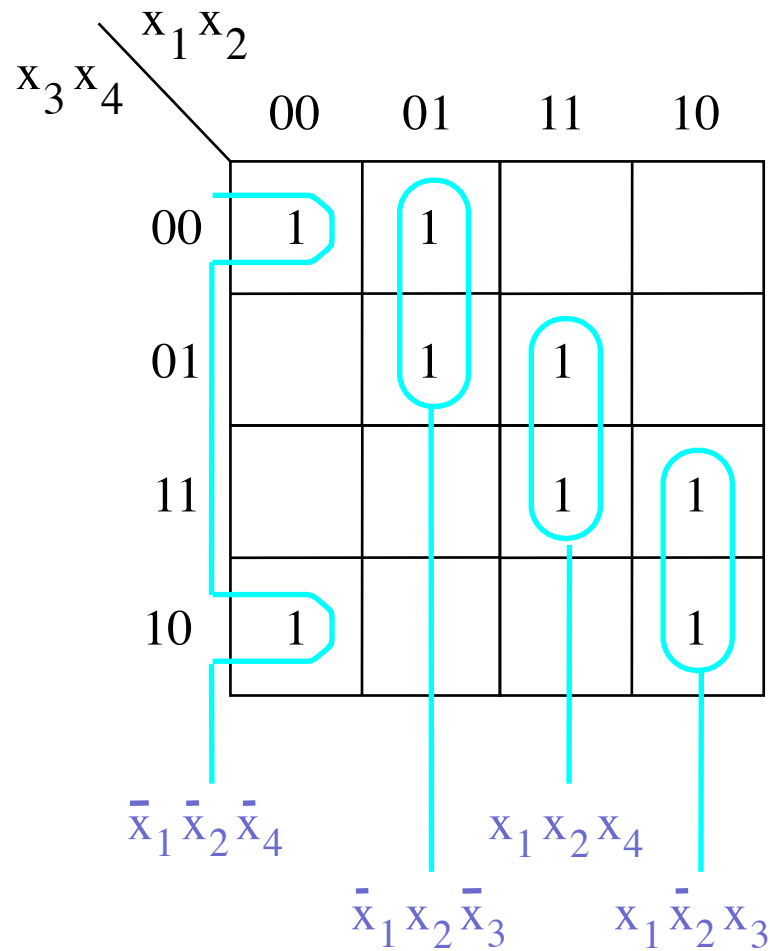


$$f = \bar{x}_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 x_2 \bar{x}_3 + x_1 x_2 x_4 + x_1 \bar{x}_2 x_3$$

Example: Both Are Valid Solutions

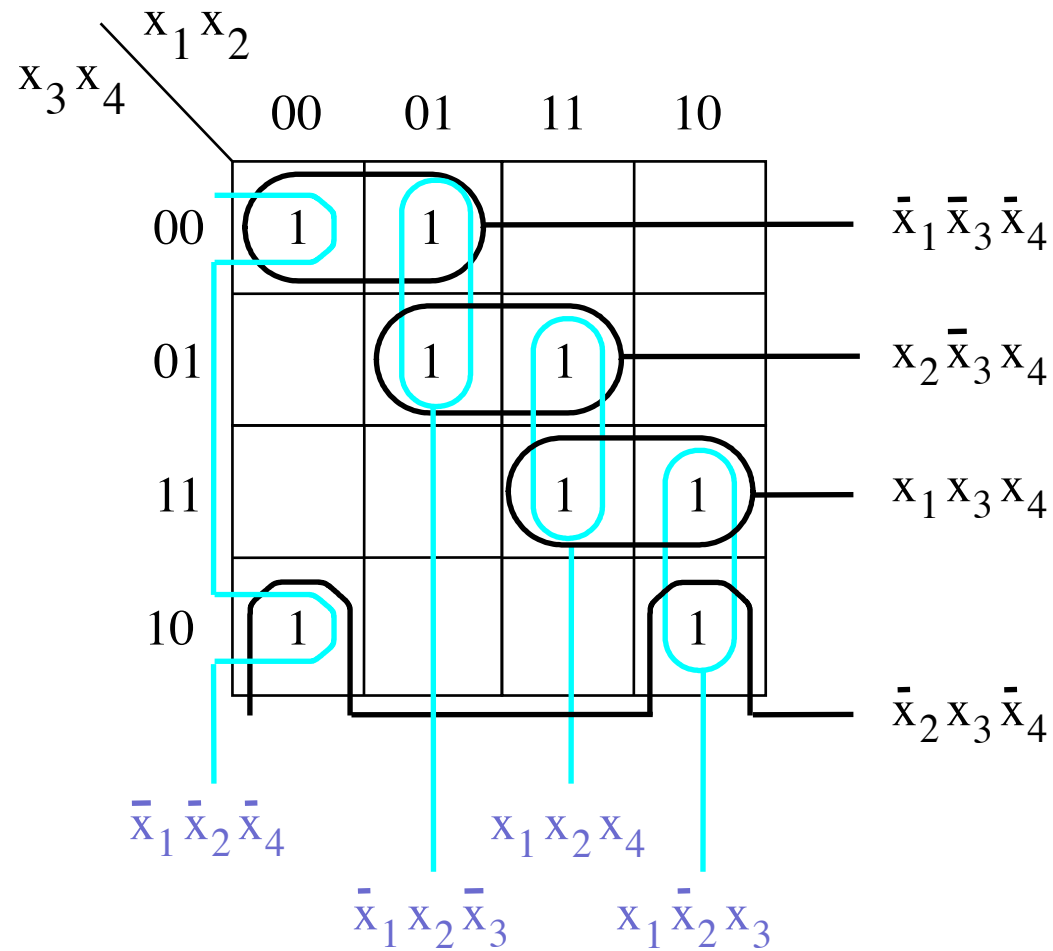

[Figure 2.59 from the textbook]

Example: Both Are Valid Solutions

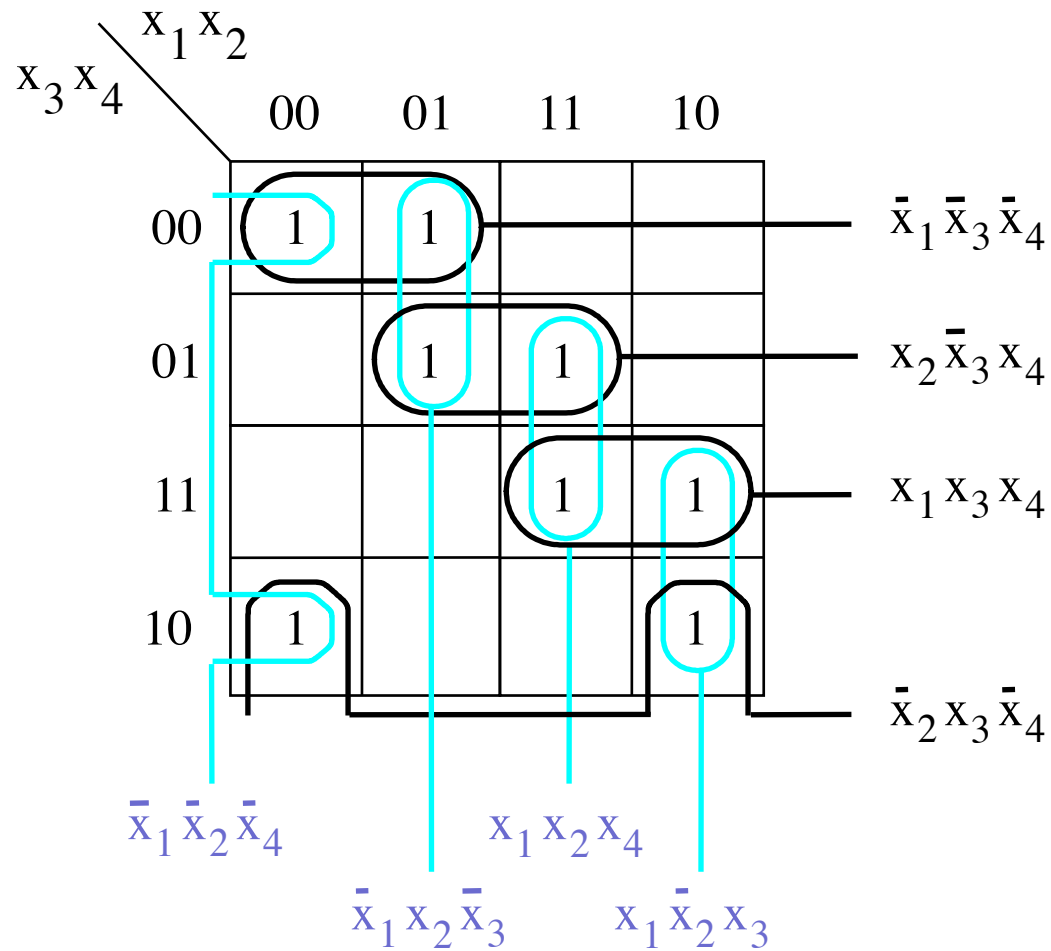

$$f = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_2 \bar{x}_3 x_4 + x_1 x_3 x_4 + \bar{x}_2 x_3 \bar{x}_4$$

$$f = \bar{x}_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 x_2 \bar{x}_3 + x_1 x_2 x_4 + x_1 \bar{x}_2 x_3$$

Minimization of Product-of-Sums Forms

Do You Still Remember This Boolean Algebra Theorem?

14a. $x \cdot y + x \cdot \bar{y} = x$

Combining

14b. $(x + y) \cdot (x + \bar{y}) = x$

Let's prove 14.b

x	y	$(\mathbf{x} + \mathbf{y}) \cdot (\mathbf{x} + \overline{\mathbf{y}}) = \mathbf{x}$
0	0	
0	1	
1	0	
1	1	

Let's prove 14.b

x	y	$(\mathbf{x} + \mathbf{y}) \bullet (\mathbf{x} + \overline{\mathbf{y}}) = \mathbf{x}$
0	0	0
0	1	1
1	0	1
1	1	1

Let's prove 14.b

x	y	$(\mathbf{x} + \mathbf{y}) \cdot (\mathbf{x} + \overline{\mathbf{y}}) = \mathbf{x}$
0	0	0
0	1	0
1	0	1
1	1	1

Let's prove 14.b

x	y	$(\mathbf{x} + \mathbf{y}) \bullet (\mathbf{x} + \overline{\mathbf{y}}) = \mathbf{x}$			
0	0	0	0	1	
0	1	1	0	0	
1	0	1	1	1	
1	1	1	1	1	

Let's prove 14.b

x	y	$(x + y) \cdot (x + \bar{y}) = x$				
0	0	0	0	1	0	
0	1	1	0	0	0	
1	0	1	1	1	1	
1	1	1	1	1	1	

Let's prove 14.b

x	y	$(x + y) \cdot (x + \bar{y}) = x$				
0	0	0	0	1	0	
0	1	1	0	0	0	
1	0	1	1	1	1	
1	1	1	1	1	1	

They are equal.

Grouping Example

		x_1	
	x_2		
		0	1
0		0	1
1		1	1

M_0

		x_1	
	x_2		
		0	1
0		1	0
1		1	1

M_2

Grouping Example

	x_1	0	1
x_2			
0		0	1
1		1	1

M_0

*

	x_1	0	1
x_2			
0		1	0
1		1	1

M_2

=

	x_1	0	1
x_2			
0		0	0
1		1	1

$M_0 * M_2$

Grouping Example

	x_1	0	1
x_2	0	0	1
	1	1	1

M_0

*

	x_1	0	1
x_2	0	1	0
	1	1	1

M_2

=

	x_1	0	1
x_2	0	0	0
	1	1	1

$M_0 * M_2$

Grouping Example

	x_1	0	1
x_2			
0		0	1
1		1	1

M_0

*

	x_1	0	1
x_2			
0		1	0
1		1	1

M_2

=

	x_1	0	1
x_2			
0		0	0
1		1	1

$M_0 * M_2$

Grouping Example

	x_1	0	1
x_2	0	0	1
	1	1	1

M_0

$(x_1 + x_2)$

	x_1	0	1
x_2	0	1	0
	1	1	1

M_2

$(\bar{x}_1 + x_2)$

*

*

*

=

=

=


	x_1	0	1
x_2	0	0	0
	1	1	1

$M_0 * M_2$


x_2

Property 14b (Combining)

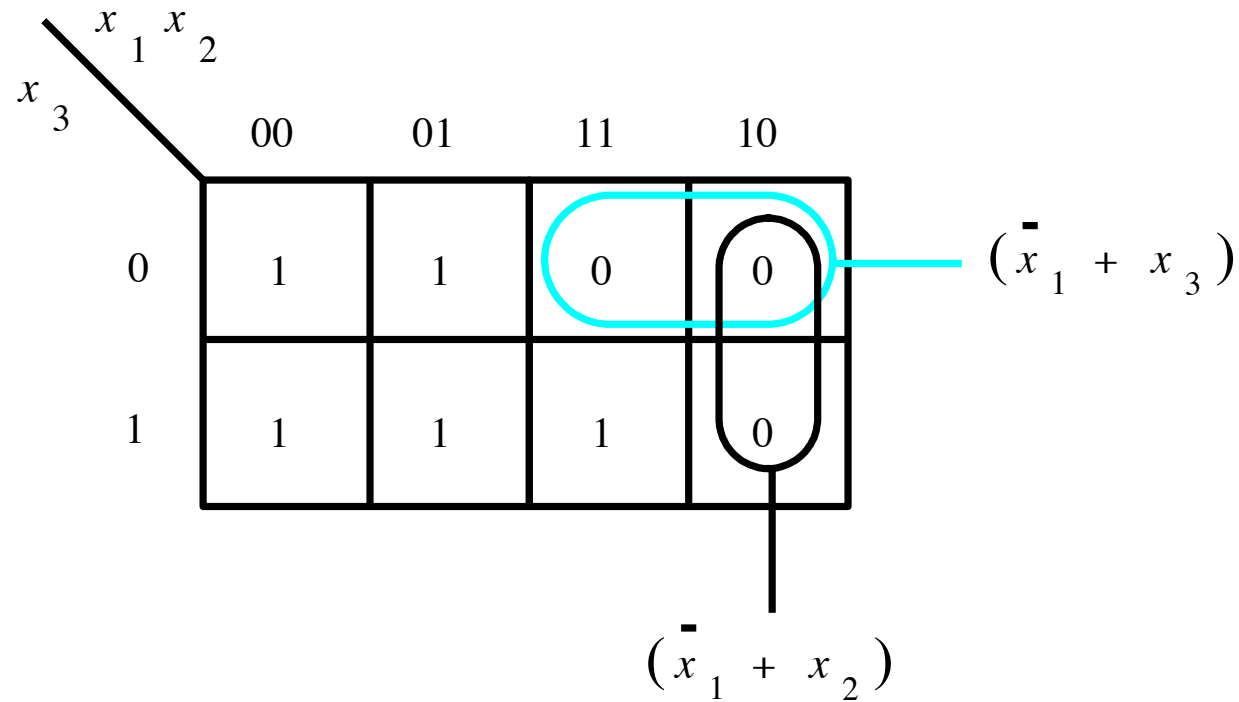POS minimization of $f(x_1, x_2, x_3) = \prod M(4, 5, 6)$



POS minimization of $f(x_1, \dots, x_4) = \prod M(0, 1, 4, 8, 9, 12, 15)$

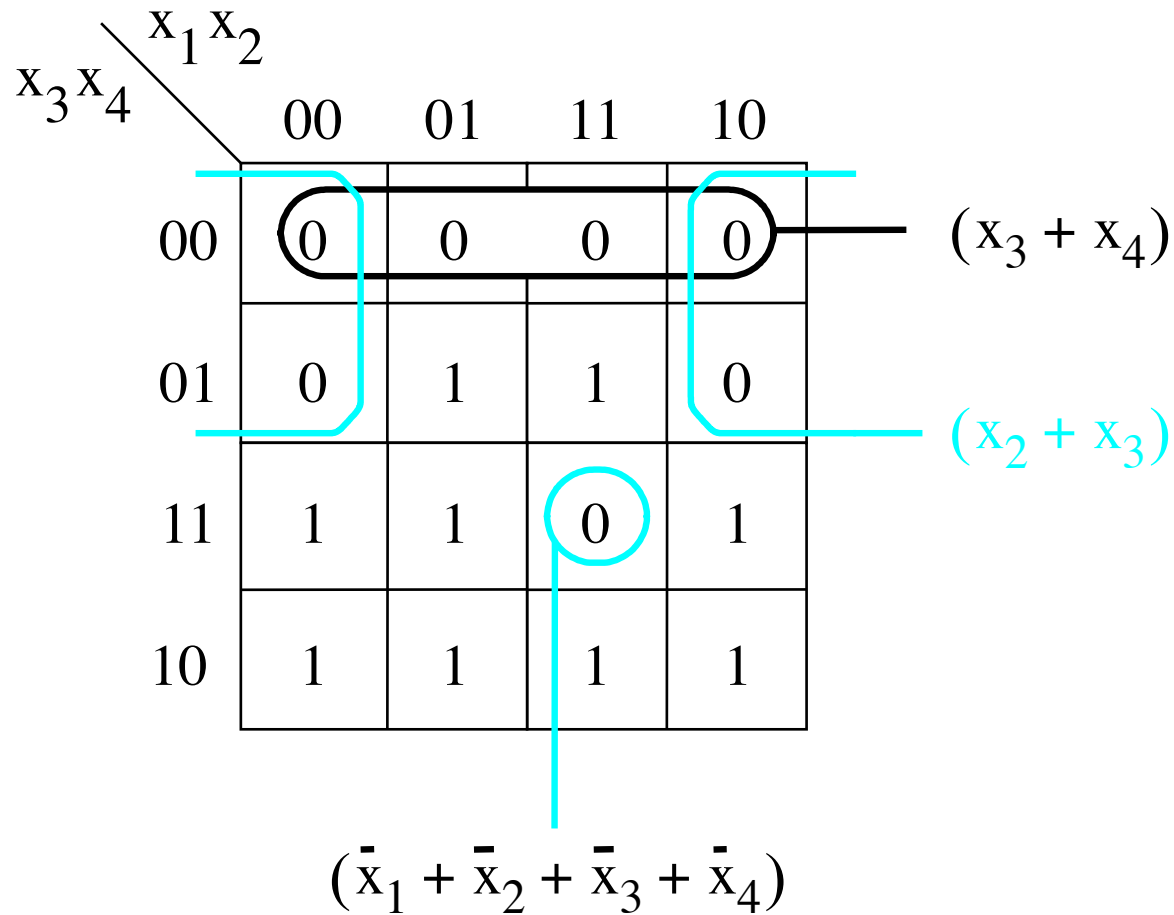

[Figure 2.61 from the textbook]

Questions?

THE END