



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Designing a Counter

(Using the Sequential Circuit Approach)


CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev

Example:
Implement a modulo-8 counter


Mini Review

Asynchronous Counters


A three-bit down-counter

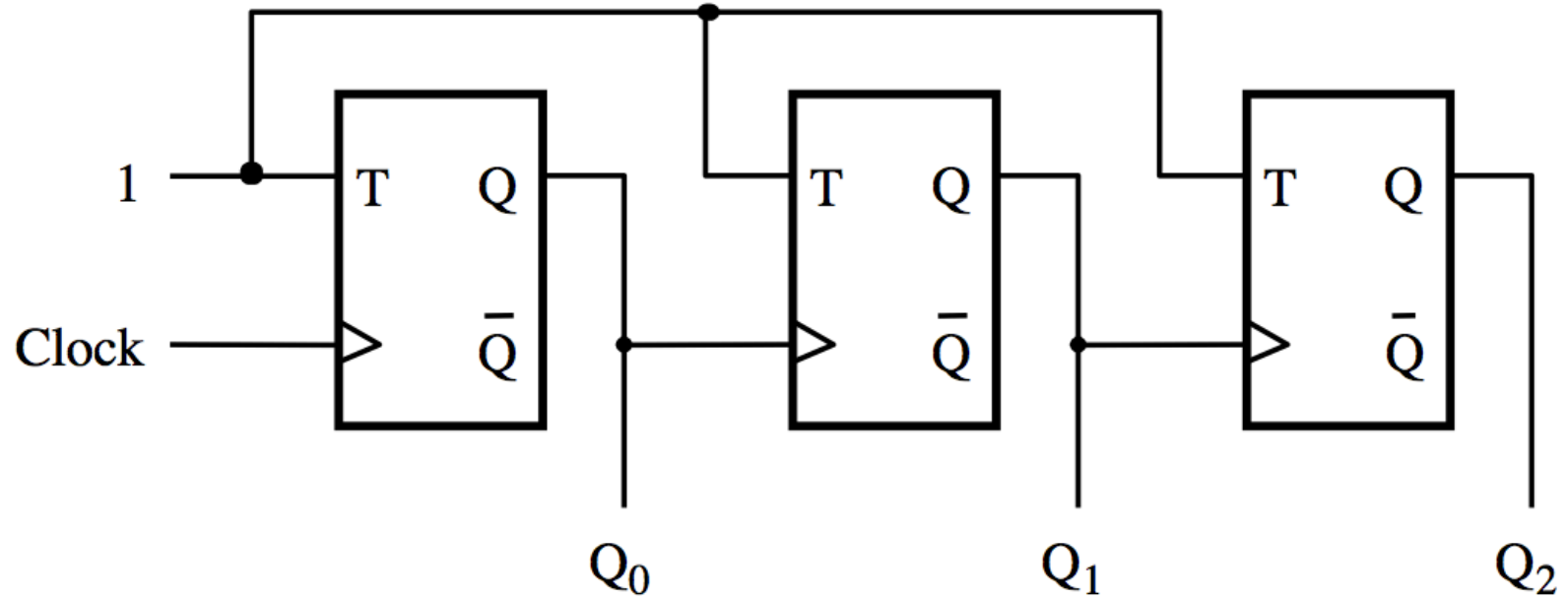

A three-bit down-counter

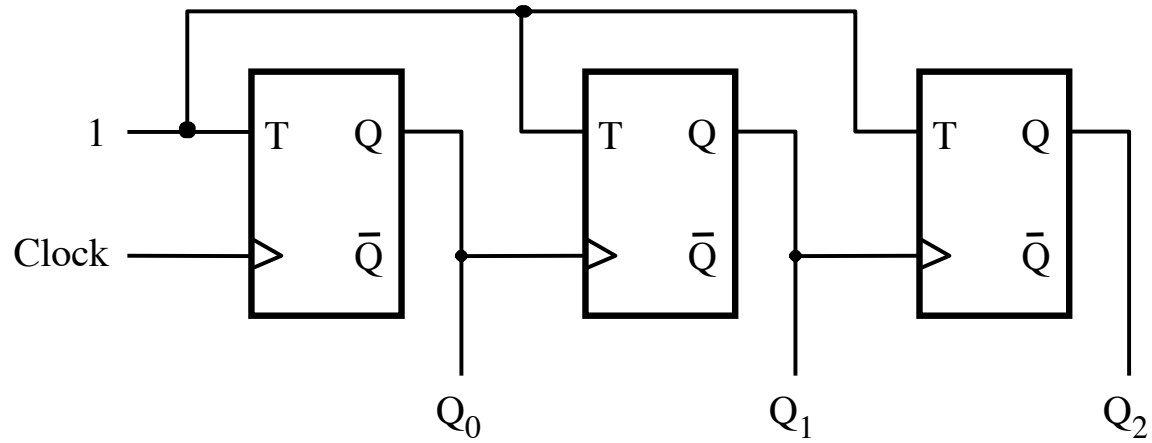


(a) Circuit

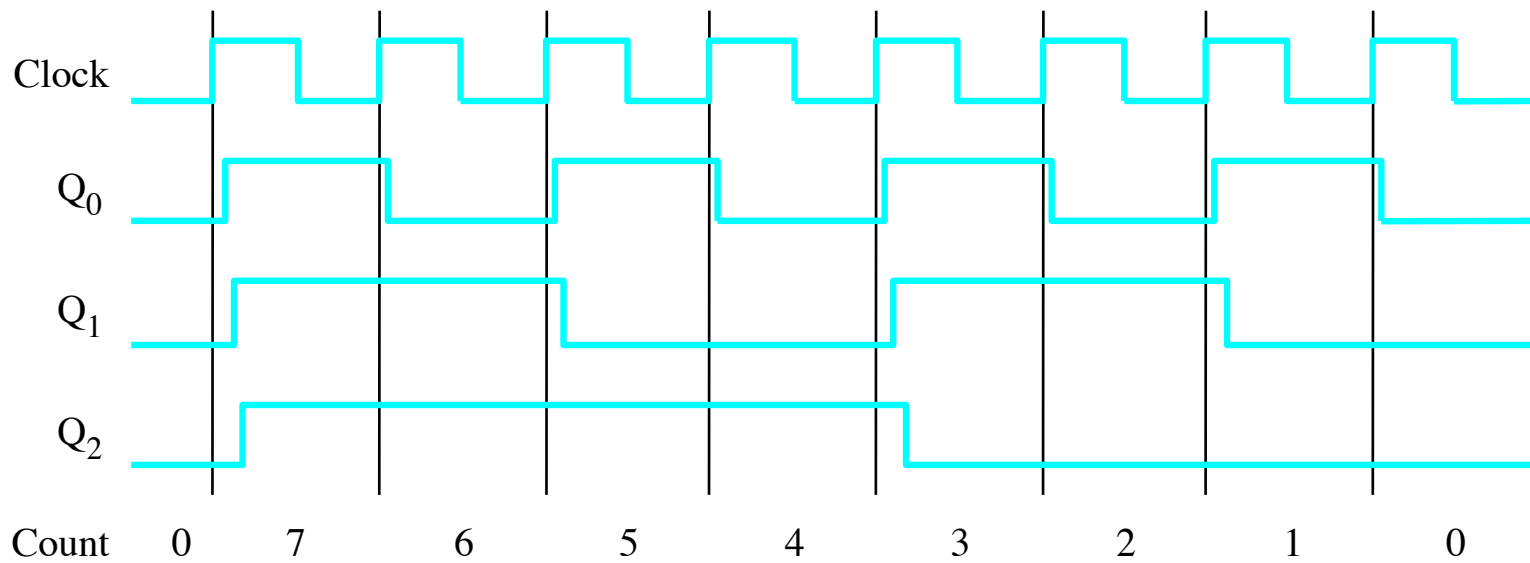


(b) Timing diagram

A three-bit down-counter

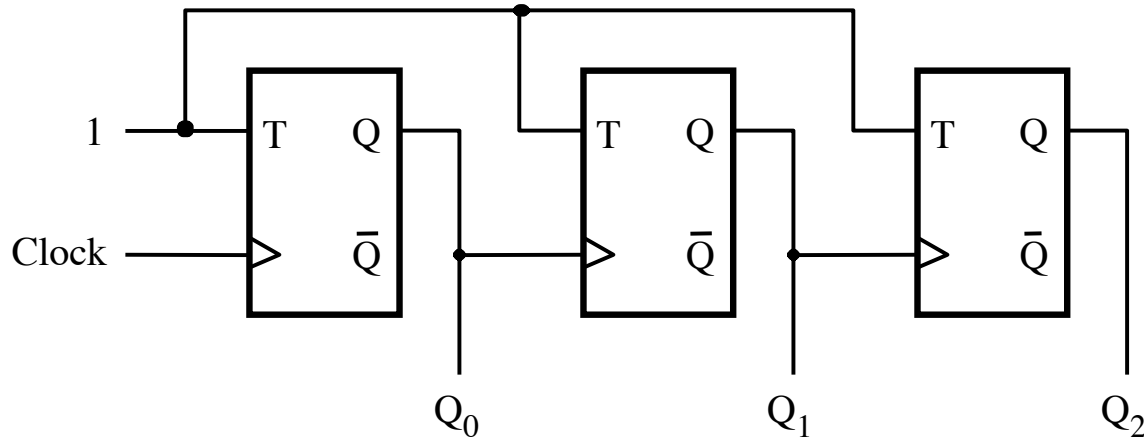


(a) Circuit

The propagation delays get longer

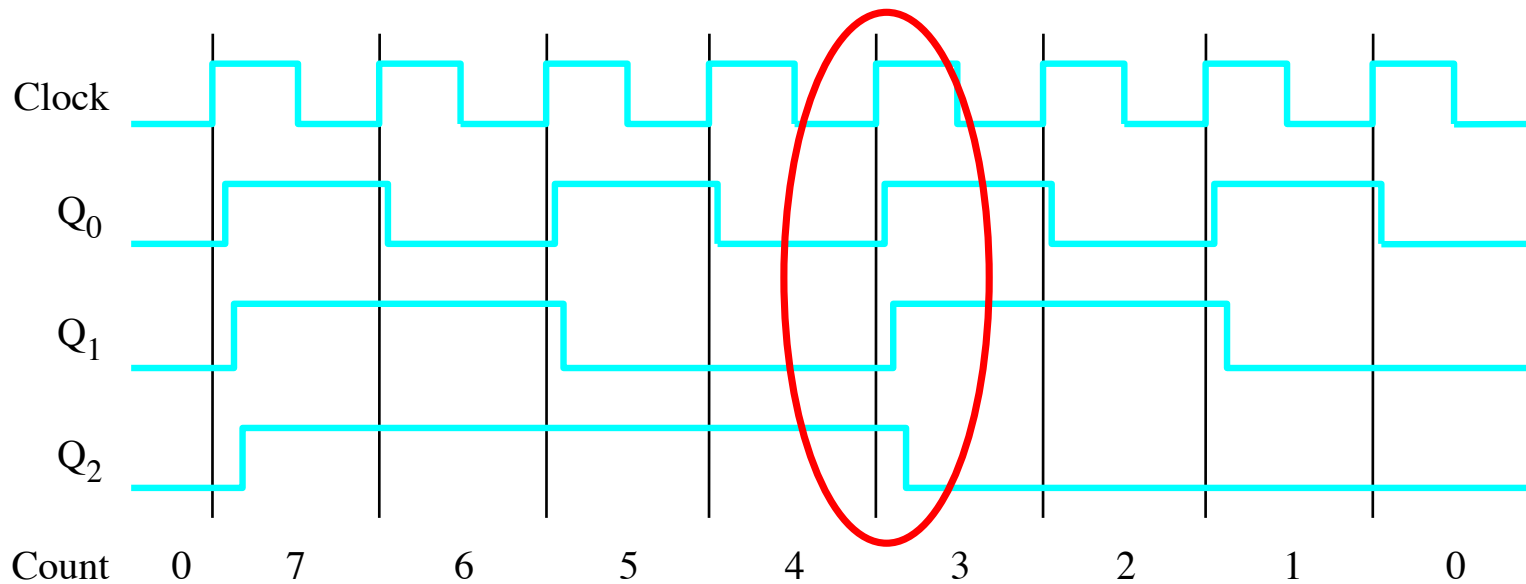


(b) Timing diagram

A three-bit up-counter

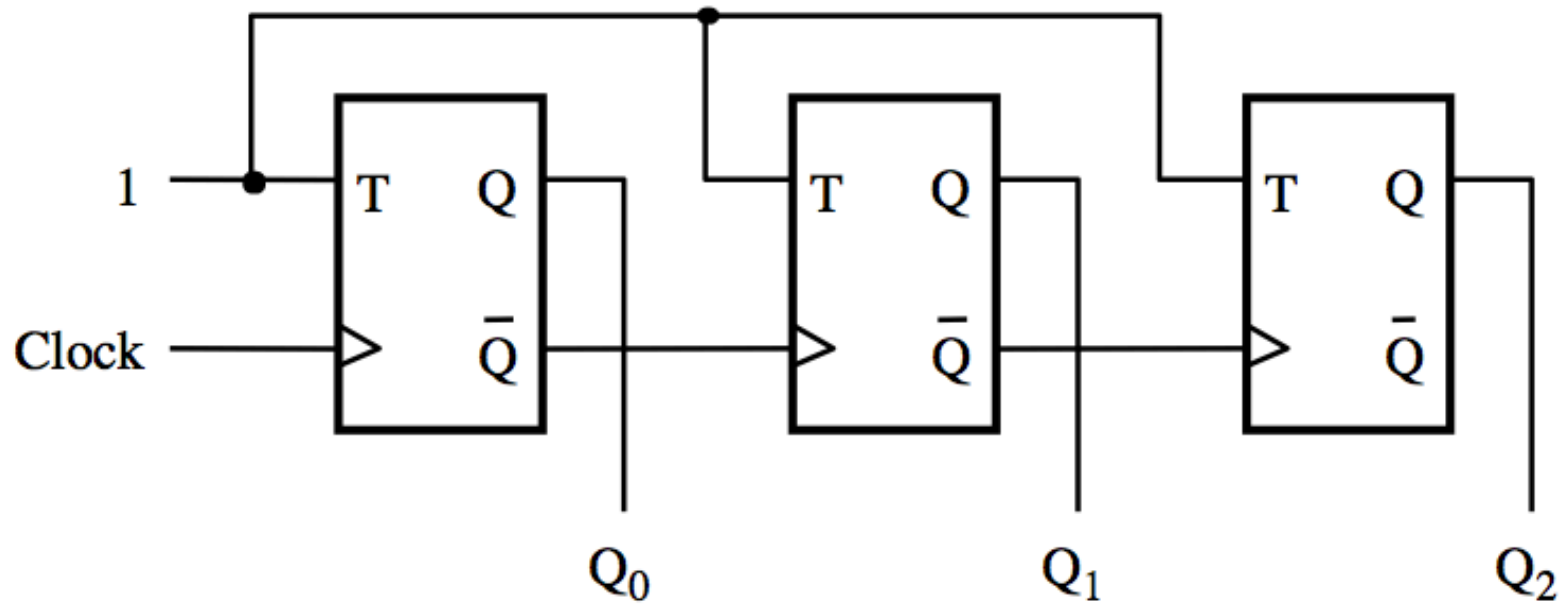


A three-bit up-counter

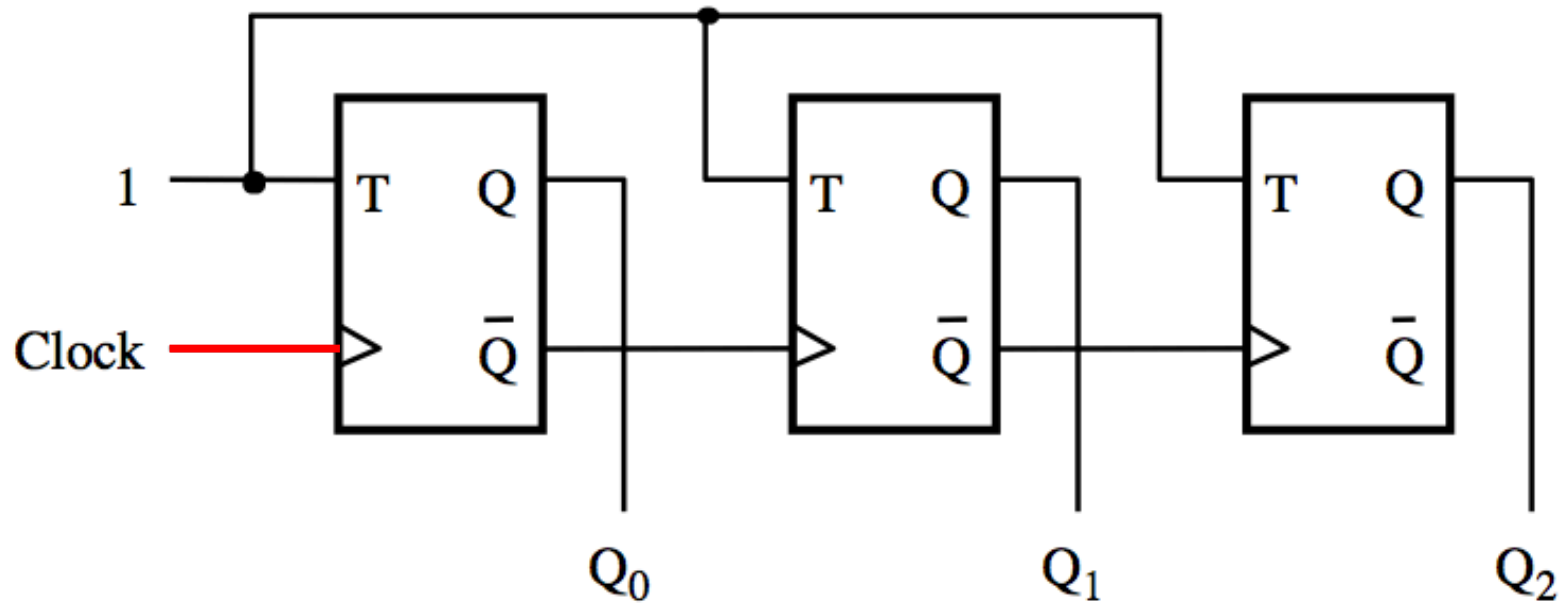

The first flip-flop changes
on the positive edge of the clock


A three-bit up-counter

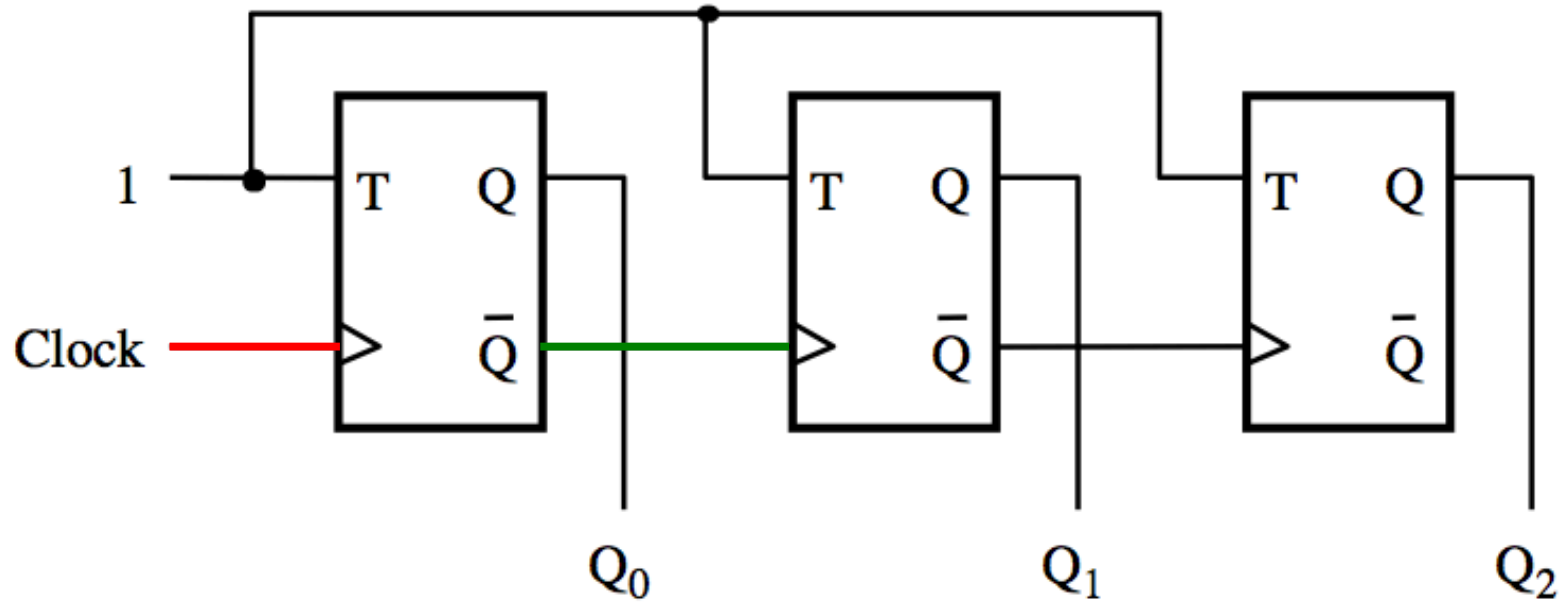

The first flip-flop changes
on the positive edge of the clock

The second flip-flop changes
on the positive edge of \bar{Q}_0

A three-bit up-counter

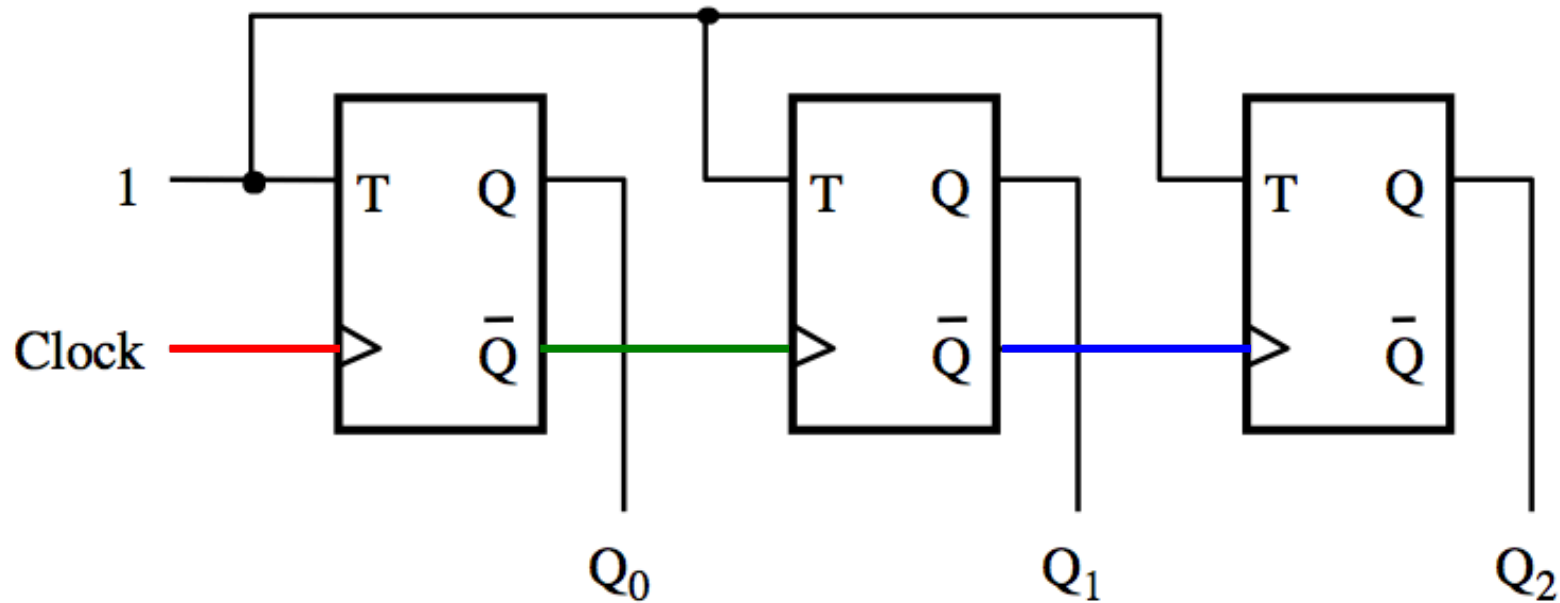


The first flip-flop changes
on the positive edge of the clock


The second flip-flop changes
on the positive edge of \bar{Q}_0

The third flip-flop changes
on the positive edge of \bar{Q}_1

A three-bit up-counter

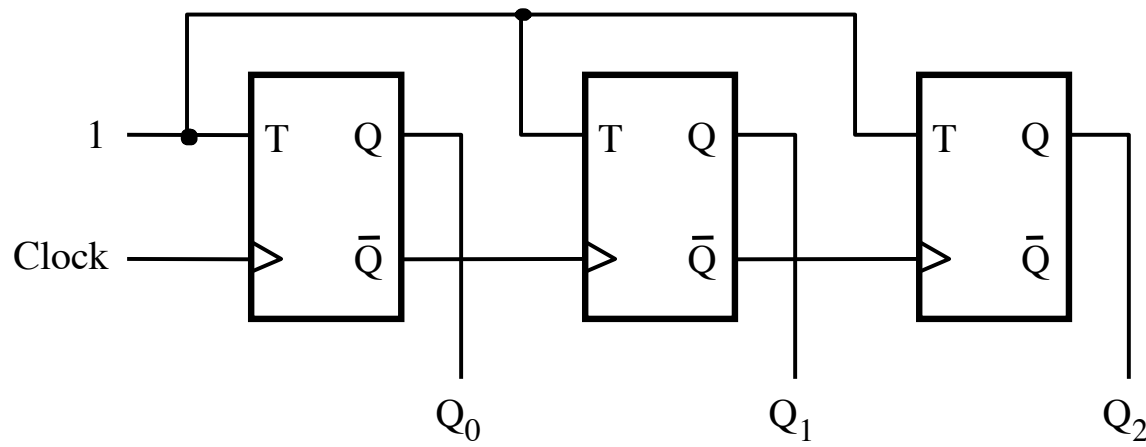


(a) Circuit

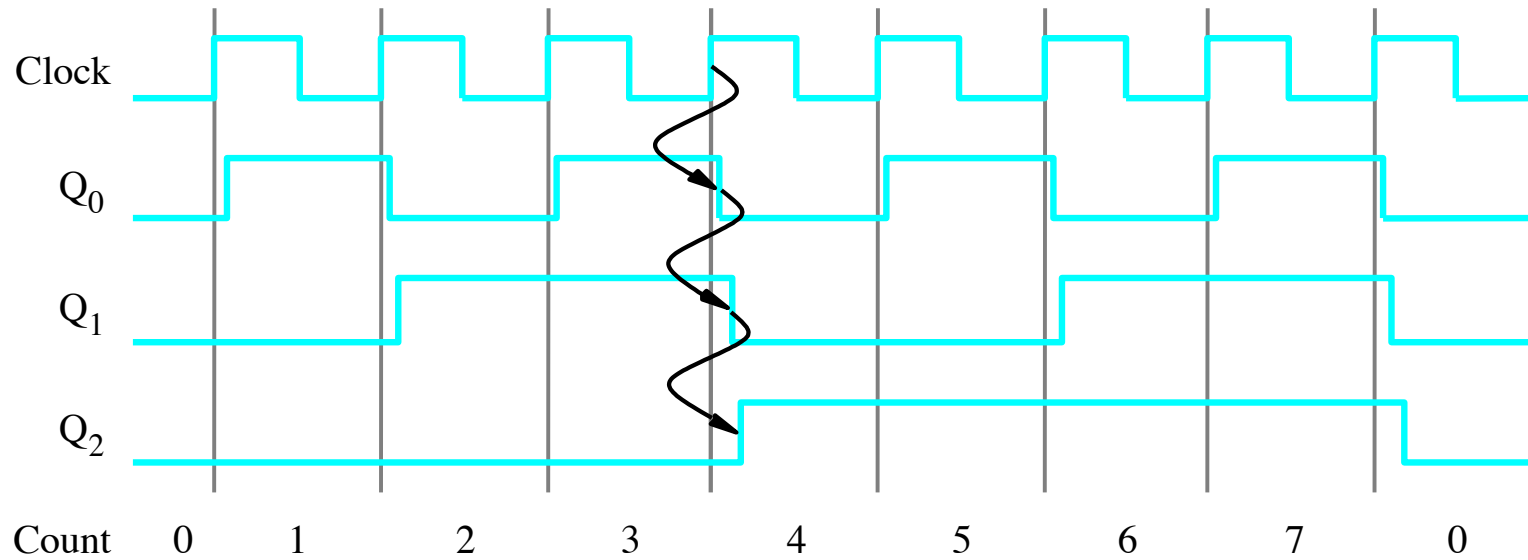


(b) Timing diagram

A three-bit up-counter

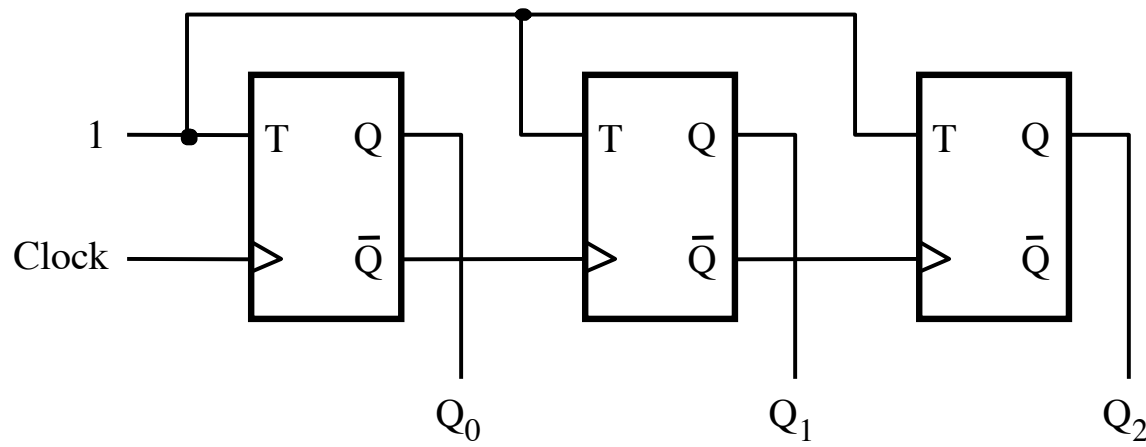

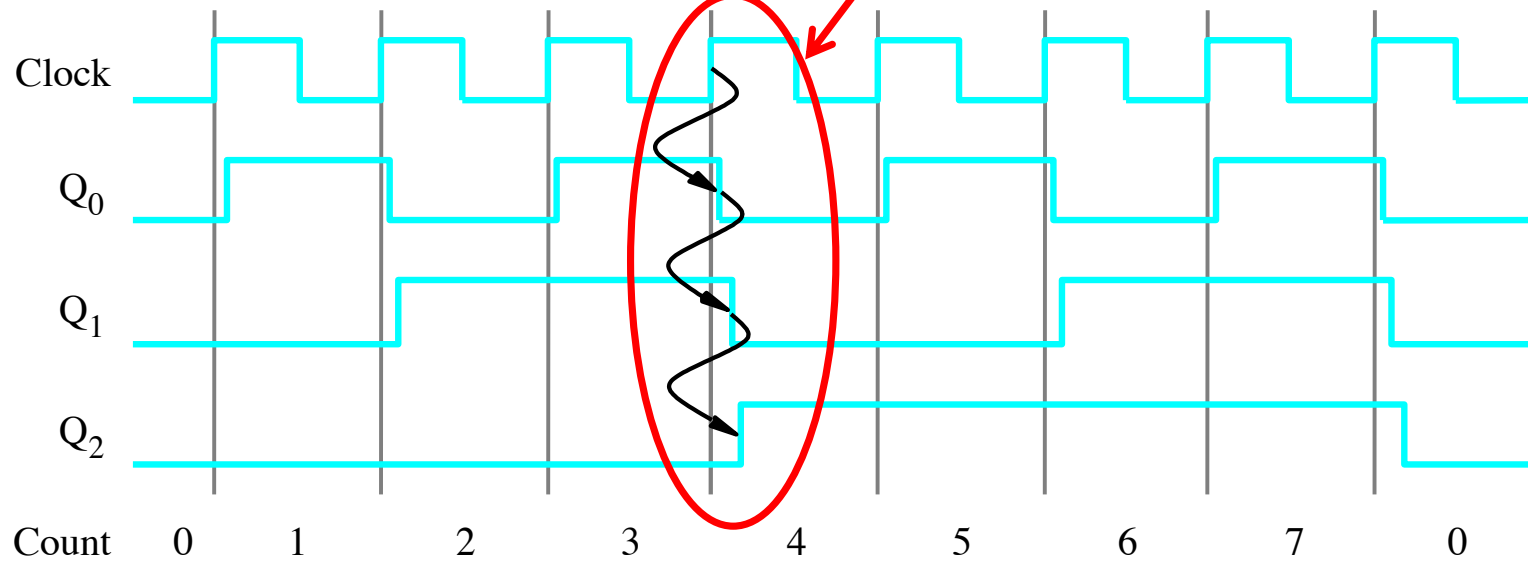
(a) Circuit **The propagation delays get longer**




(b) Timing diagram

Synchronous Counters

A four-bit synchronous up-counter

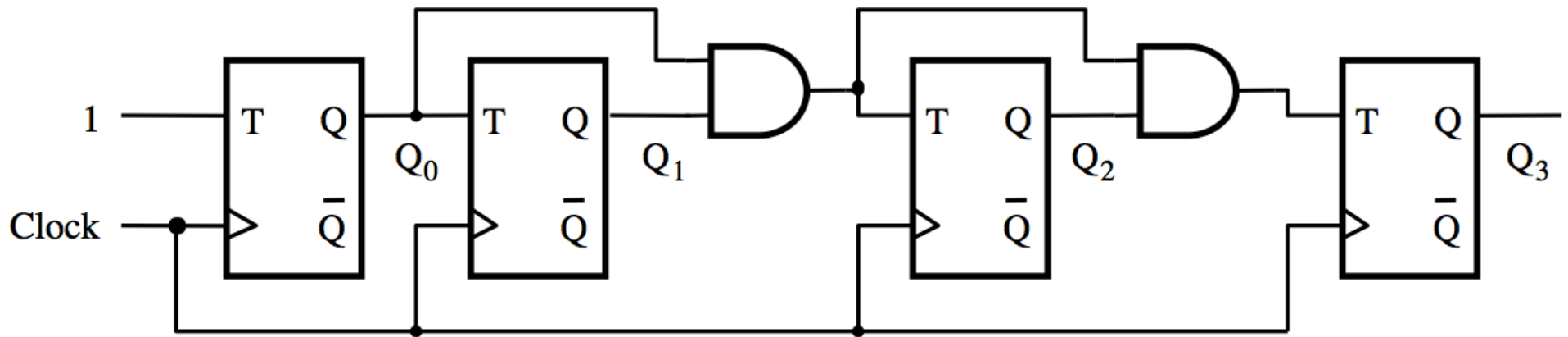


A four-bit synchronous up-counter

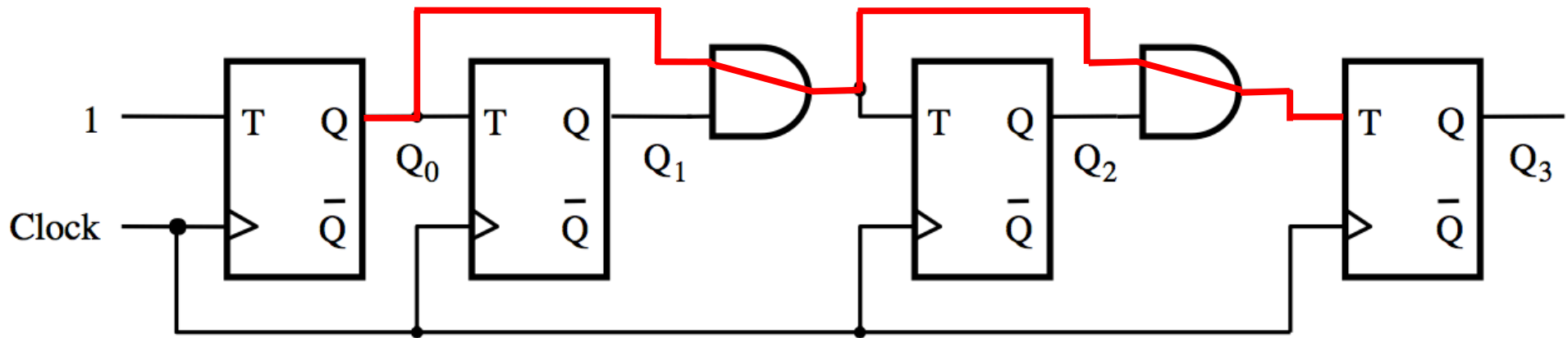


The propagation delay through all AND gates combined must not exceed the clock period minus the setup time for the flip-flops

A four-bit synchronous up-counter

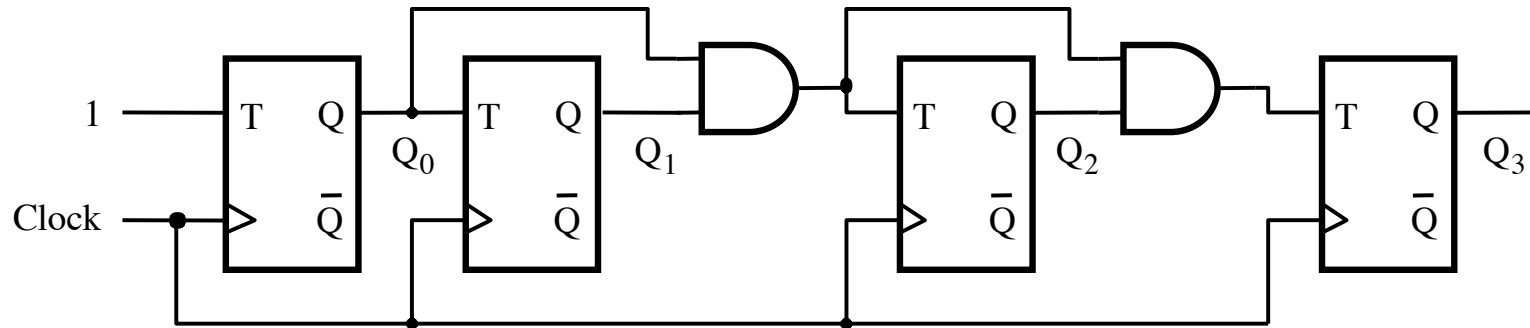

(a) Circuit

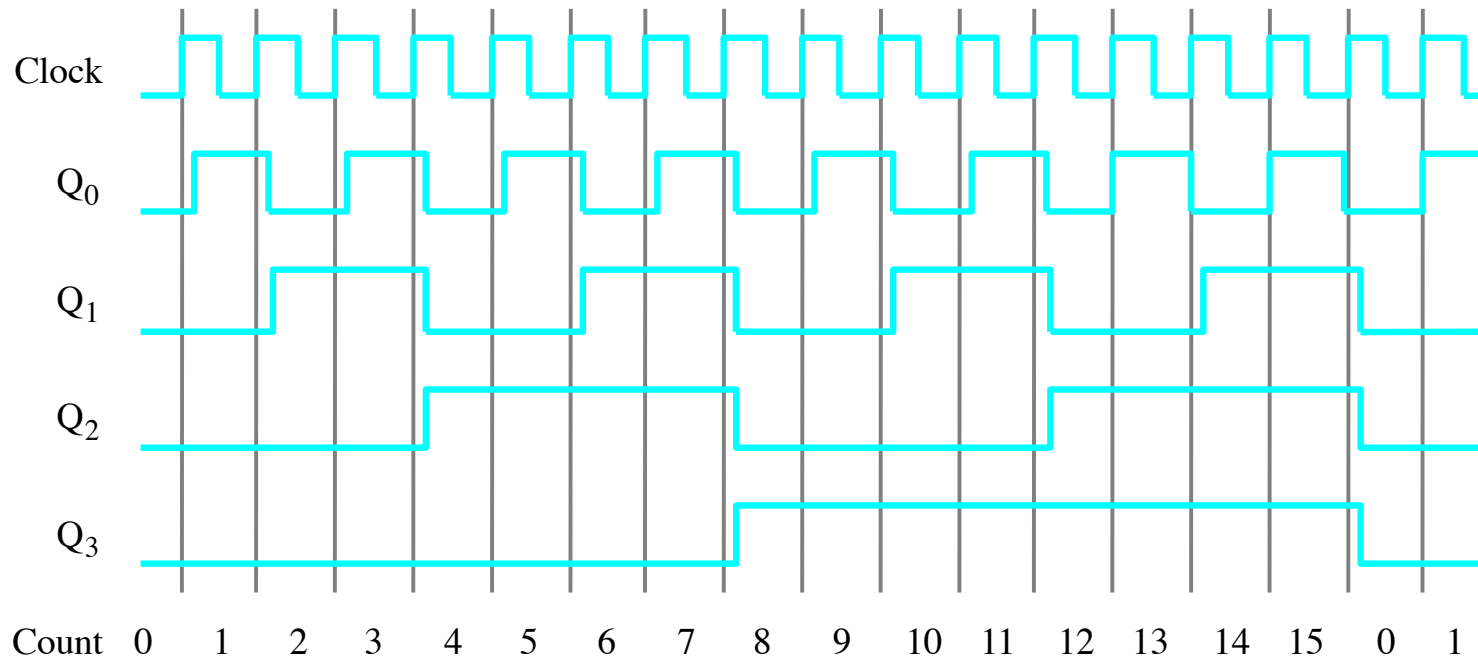

(b) Timing diagram

Derivation of the synchronous up-counter

| Clock cycle | Q ₂ | Q ₁ | Q ₀ |
|-------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 2 | 0 | 1 | 0 |
| 3 | 0 | 1 | 1 |
| 4 | 1 | 0 | 0 |
| 5 | 1 | 0 | 1 |
| 6 | 1 | 1 | 0 |
| 7 | 1 | 1 | 1 |
| 8 | 0 | 0 | 0 |

Q₁ changes

Q₂ changes

Derivation of the synchronous up-counter

| Clock cycle | Q ₂ | Q ₁ | Q ₀ |
|-------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 2 | 0 | 1 | 0 |
| 3 | 0 | 1 | 1 |
| 4 | 1 | 0 | 0 |
| 5 | 1 | 0 | 1 |
| 6 | 1 | 1 | 0 |
| 7 | 1 | 1 | 1 |
| 8 | 0 | 0 | 0 |

Q₁ changes


Q₂ changes

$$T_0 = 1$$

$$T_1 = Q_0$$

$$T_2 = Q_0 Q_1$$

A four-bit synchronous up-counter

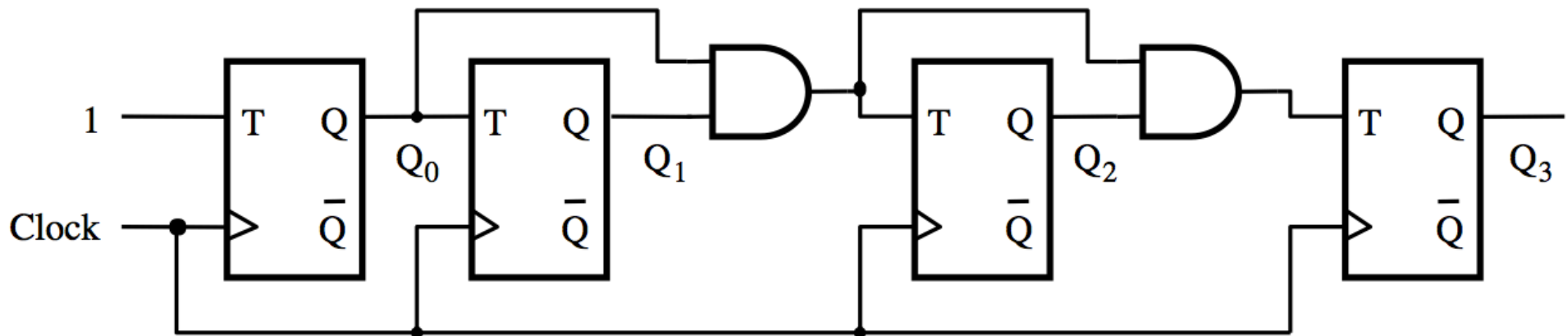

$$T_0 = 1$$

$$T_1 = Q_0$$

$$T_2 = Q_0 Q_1$$

In general we have

$$T_0 = 1$$

$$T_1 = Q_0$$


$$T_2 = Q_0 Q_1$$

$$T_3 = Q_0 Q_1 Q_2$$

...

$$T_n = Q_0 Q_1 Q_2 \cdots Q_{n-1}$$


Inclusion of Enable and Clear capability

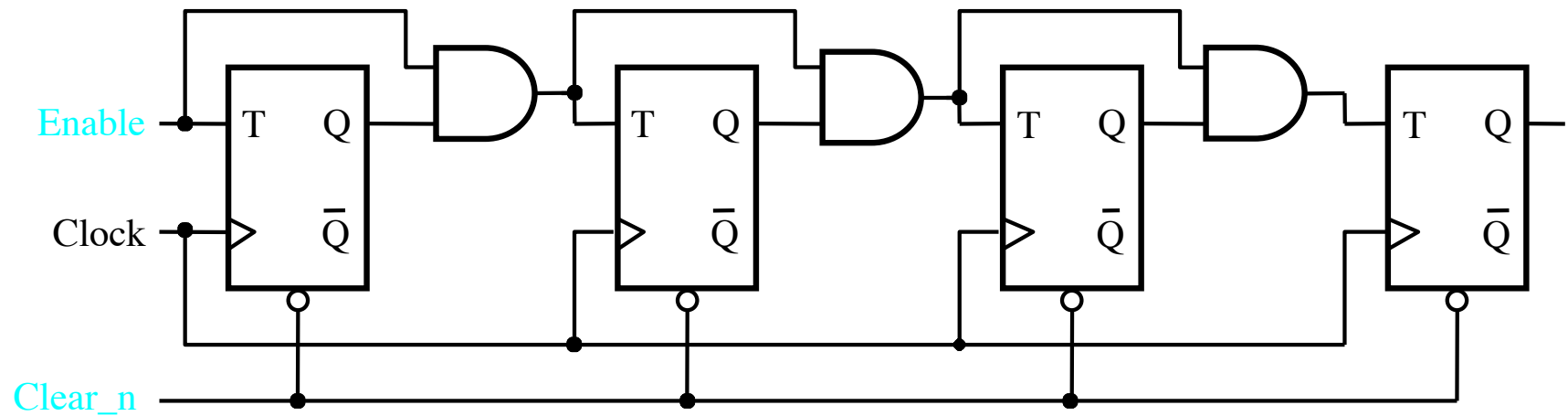


[Figure 5.22 from the textbook]

Inclusion of Enable and Clear capability

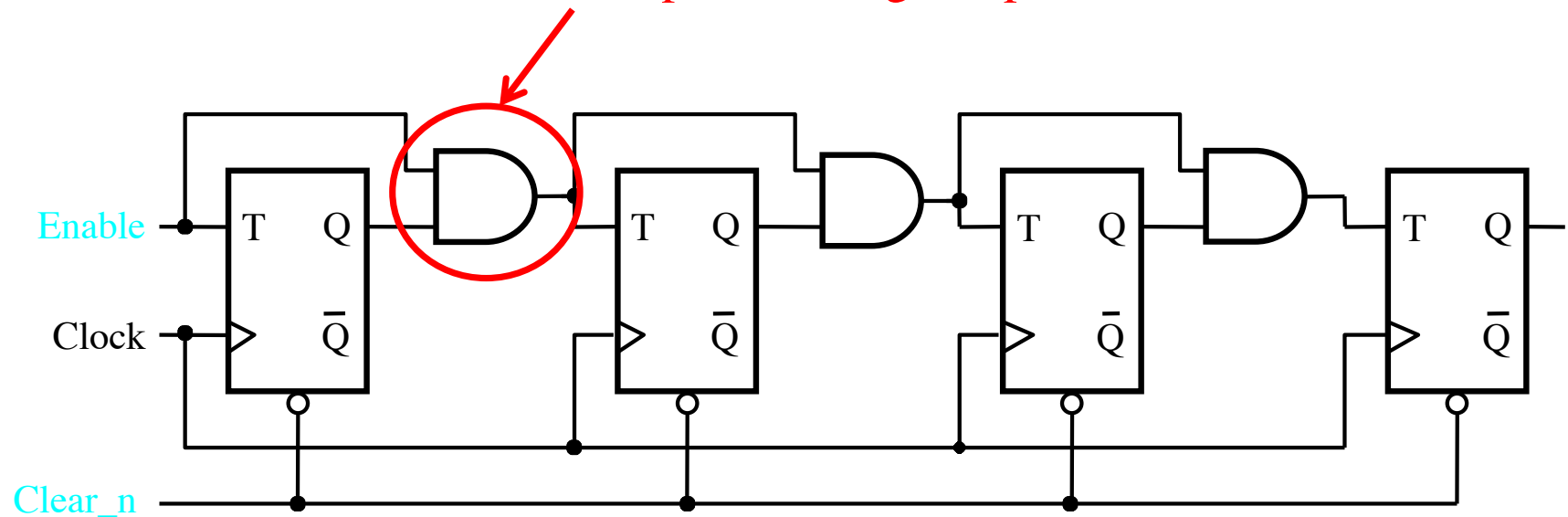This is the new thing relative to the previous figure, plus the clear_n line




T Flip-Flop

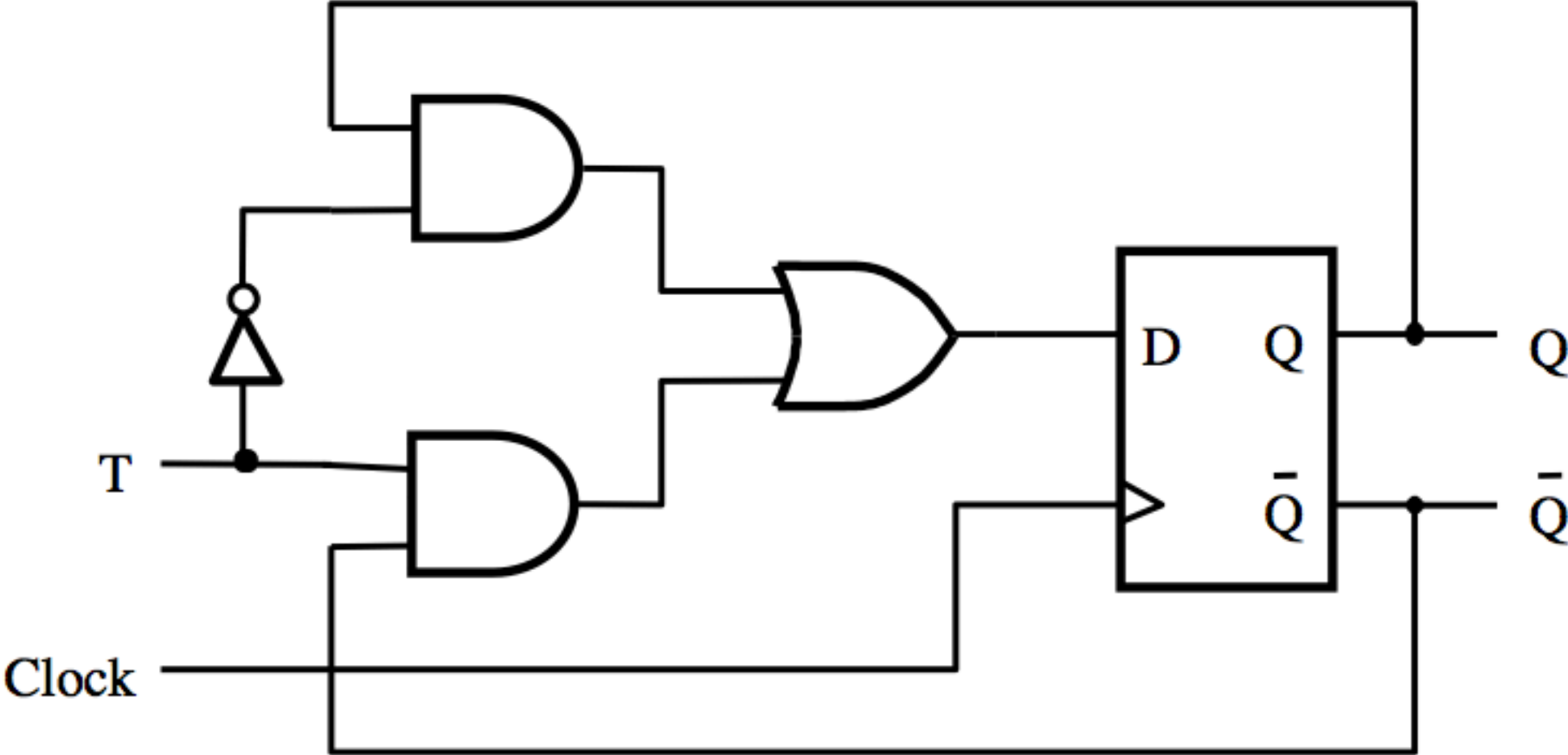

[Figure 5.15a from the textbook]


T Flip-Flop

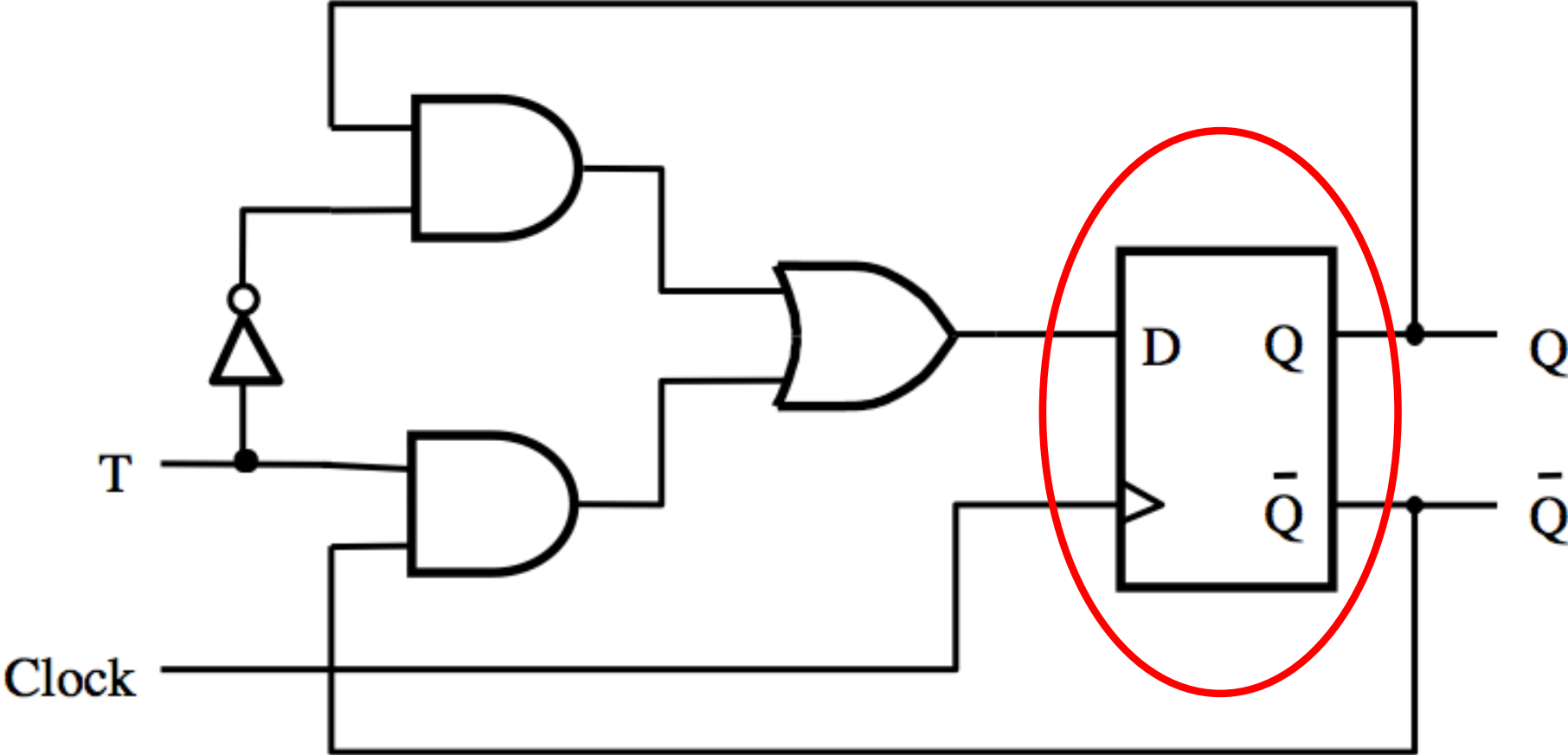

Positive-edge-triggered
D Flip-Flop


[Figure 5.15a from the textbook]

T Flip-Flop

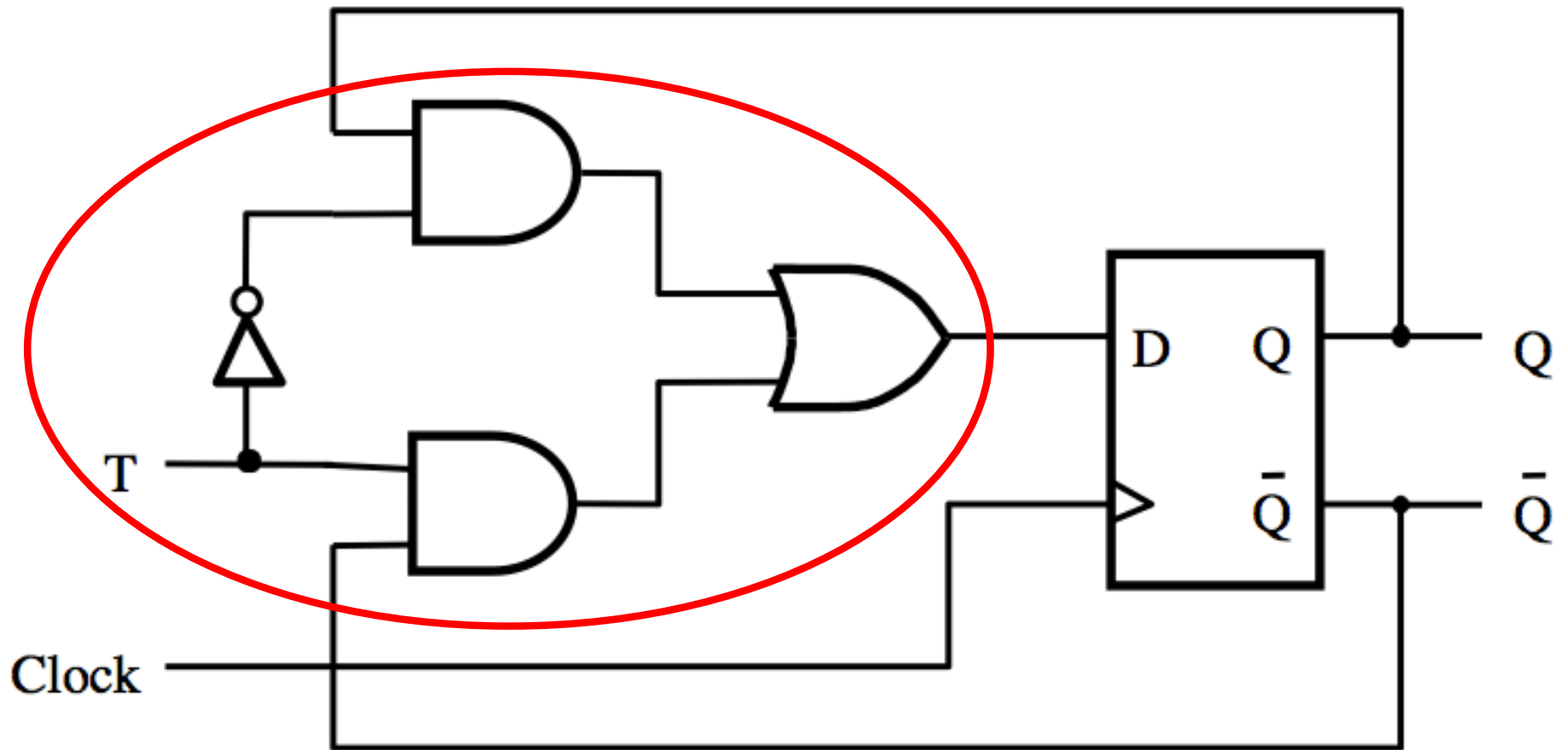


2-to-1 multiplexer


2-to-1 Multiplexer

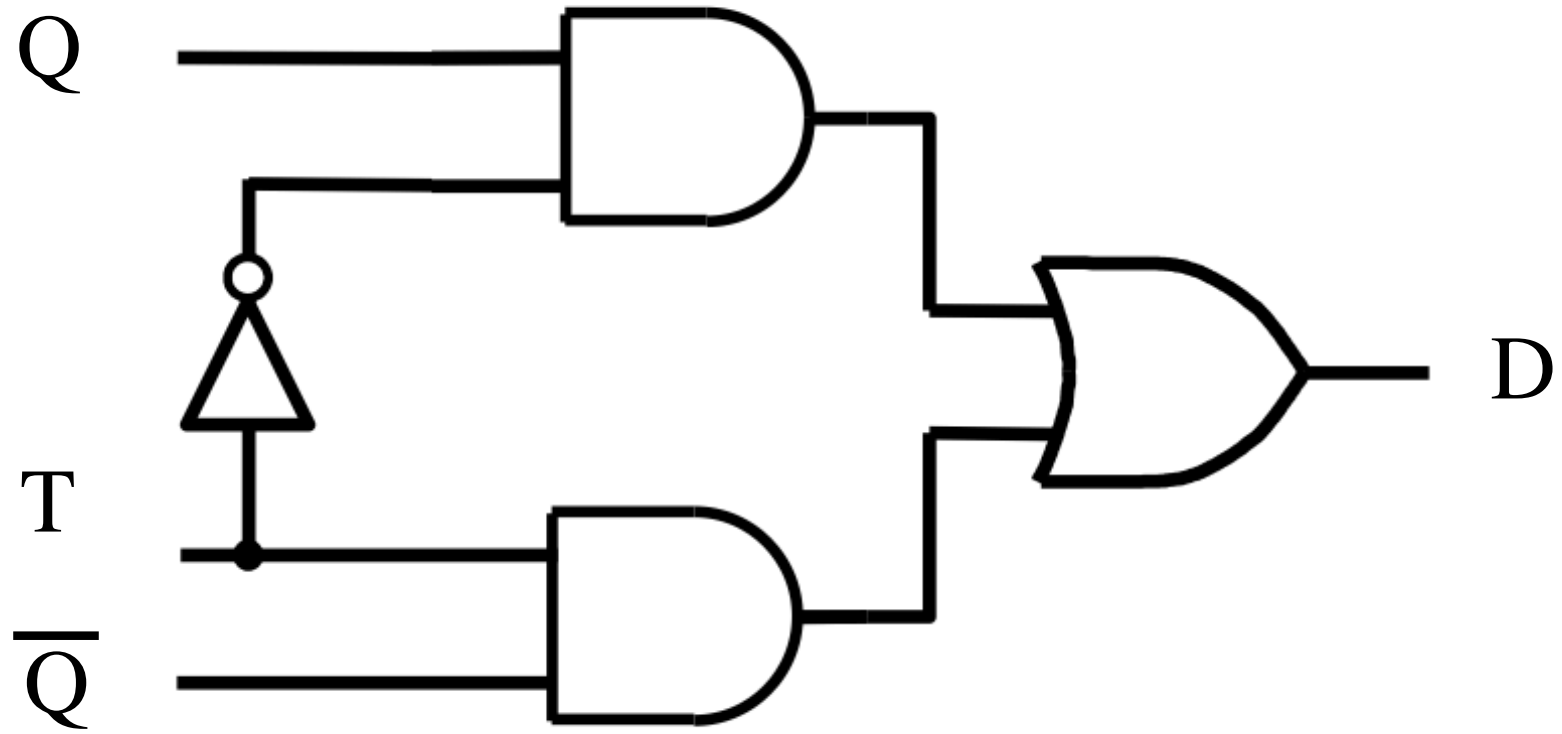


What is this?

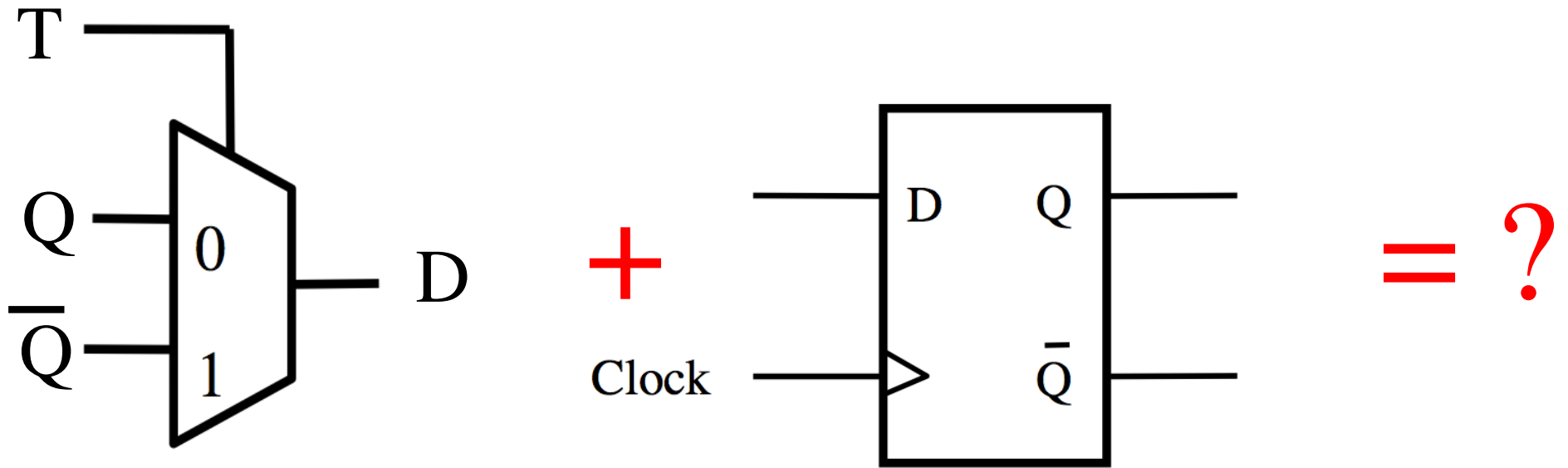


T Flip-Flop

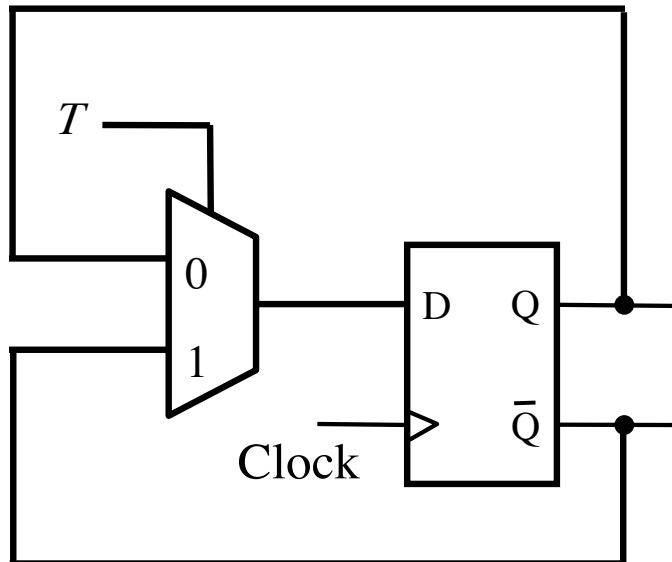


T Flip-Flop

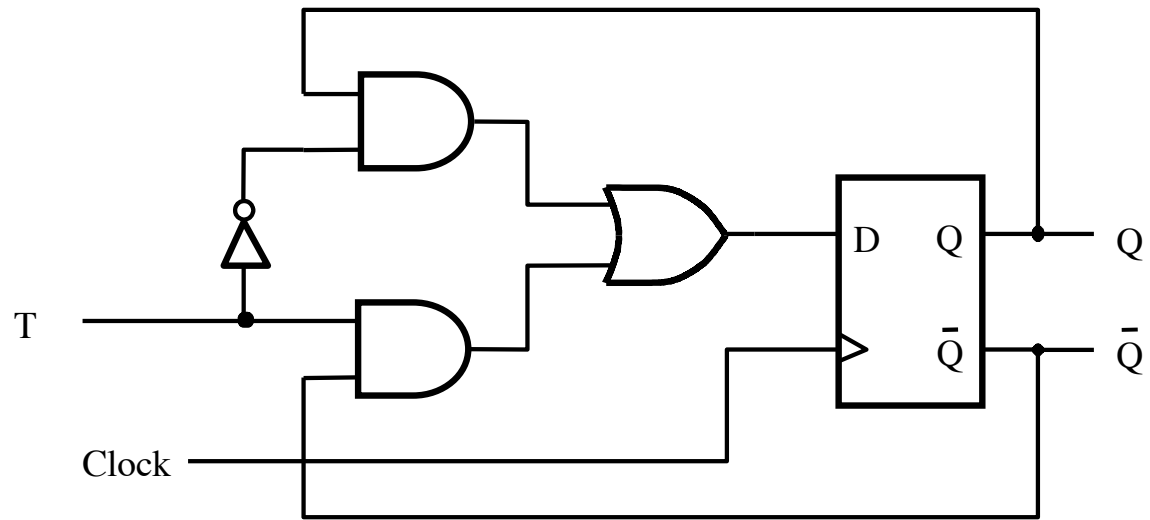



T Flip-Flop

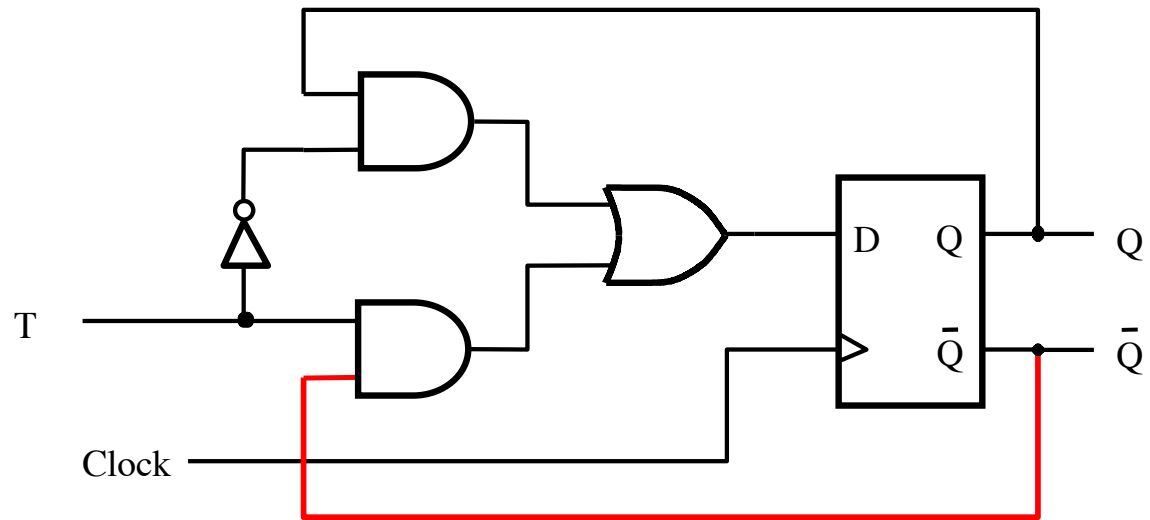


T Flip-Flop

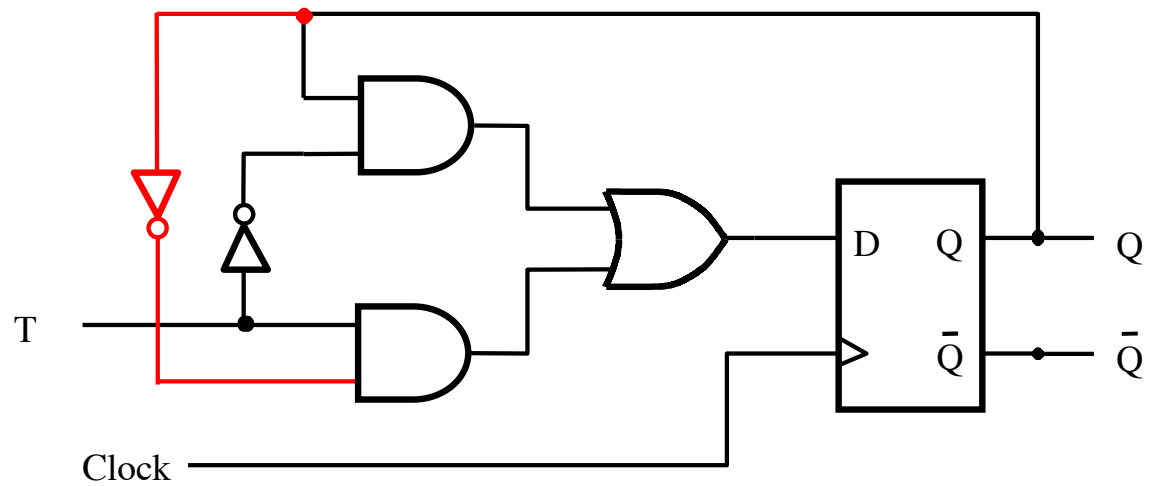


These two circuits are equivalent

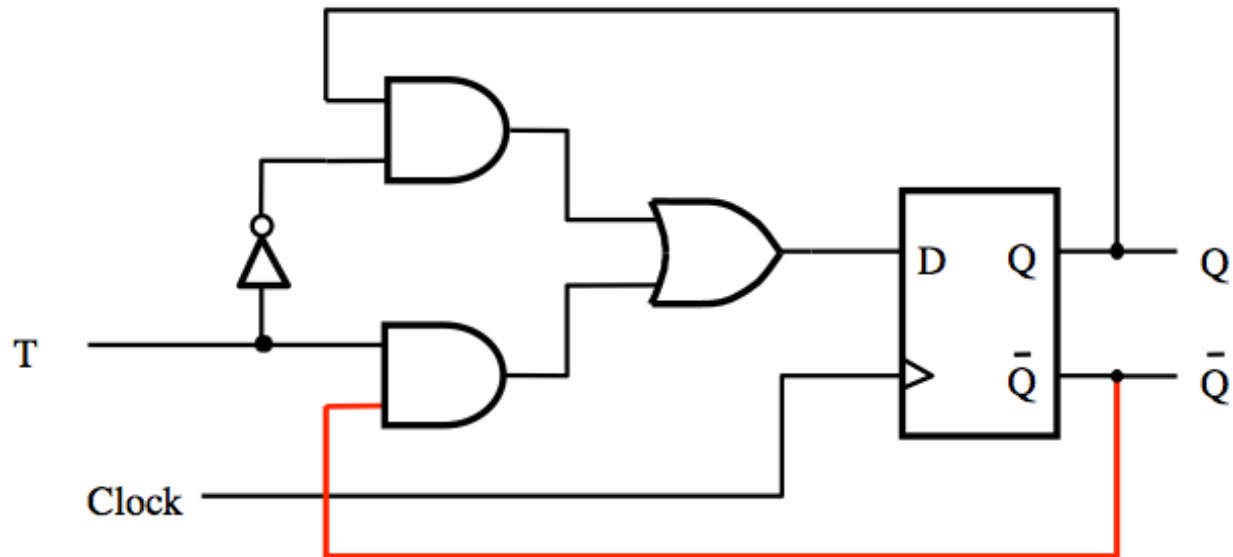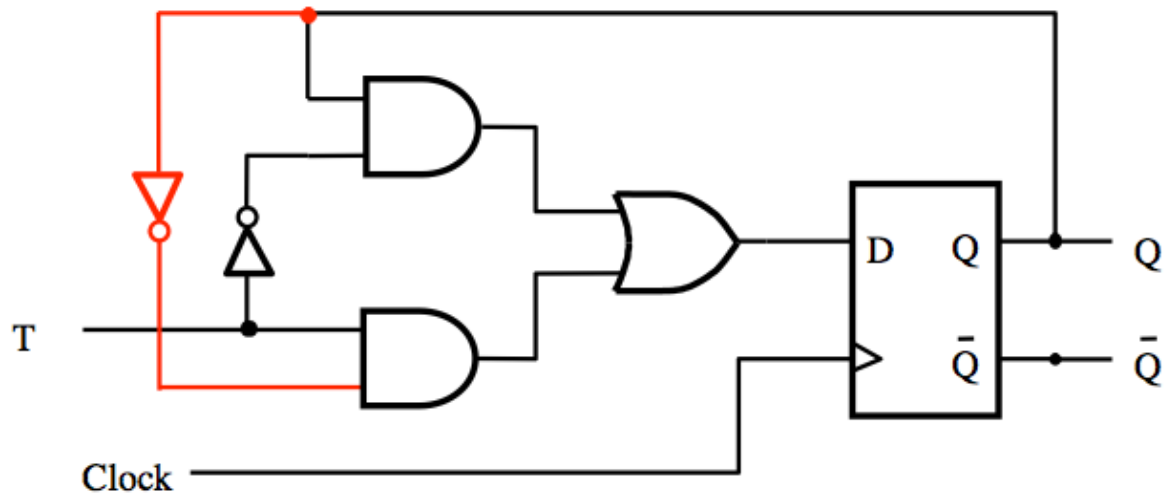

What is this?

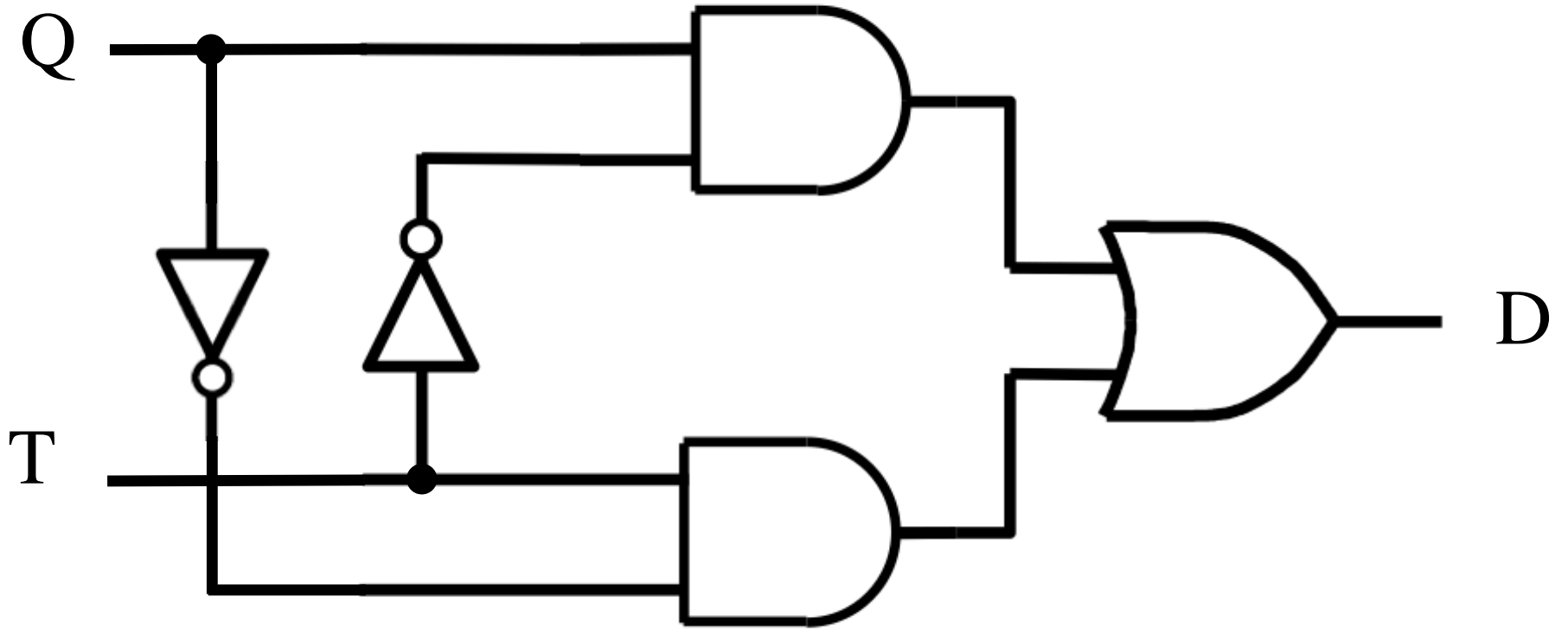


What is this?

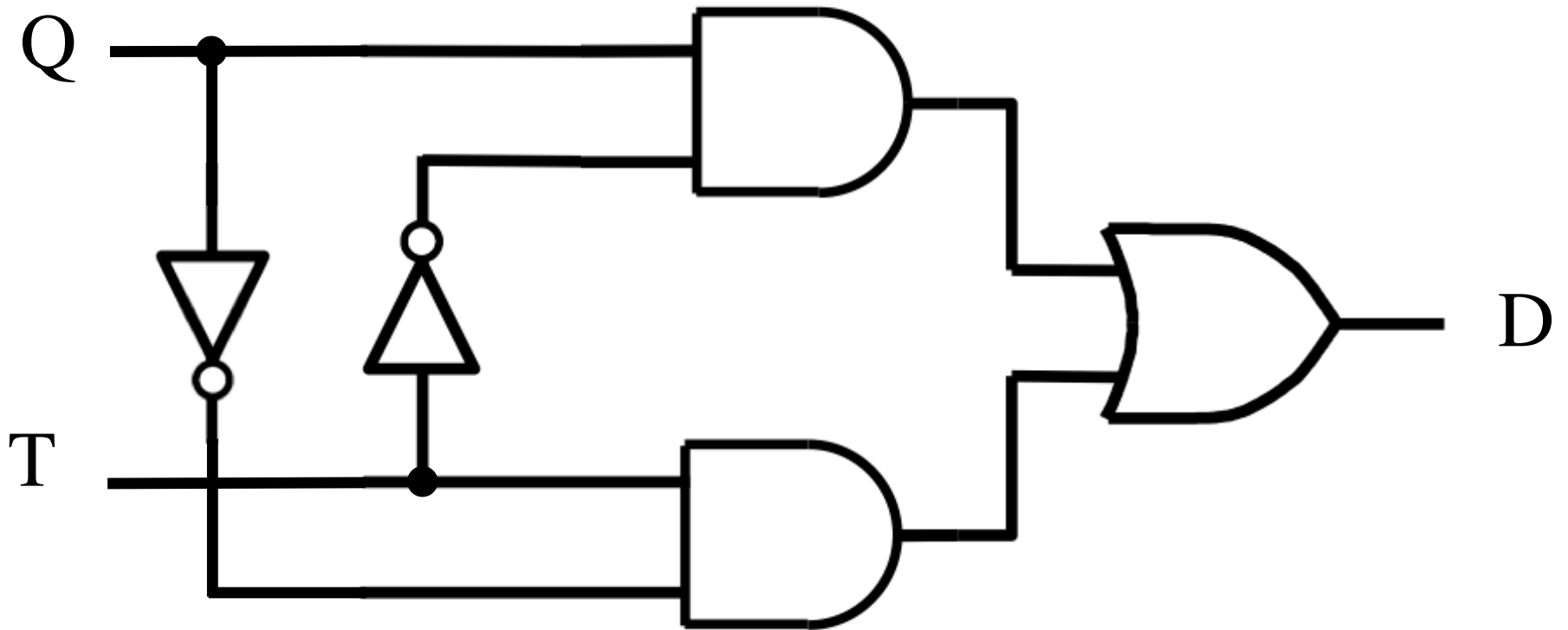


$$D = \overline{Q}T + Q\overline{T}$$

What is this?

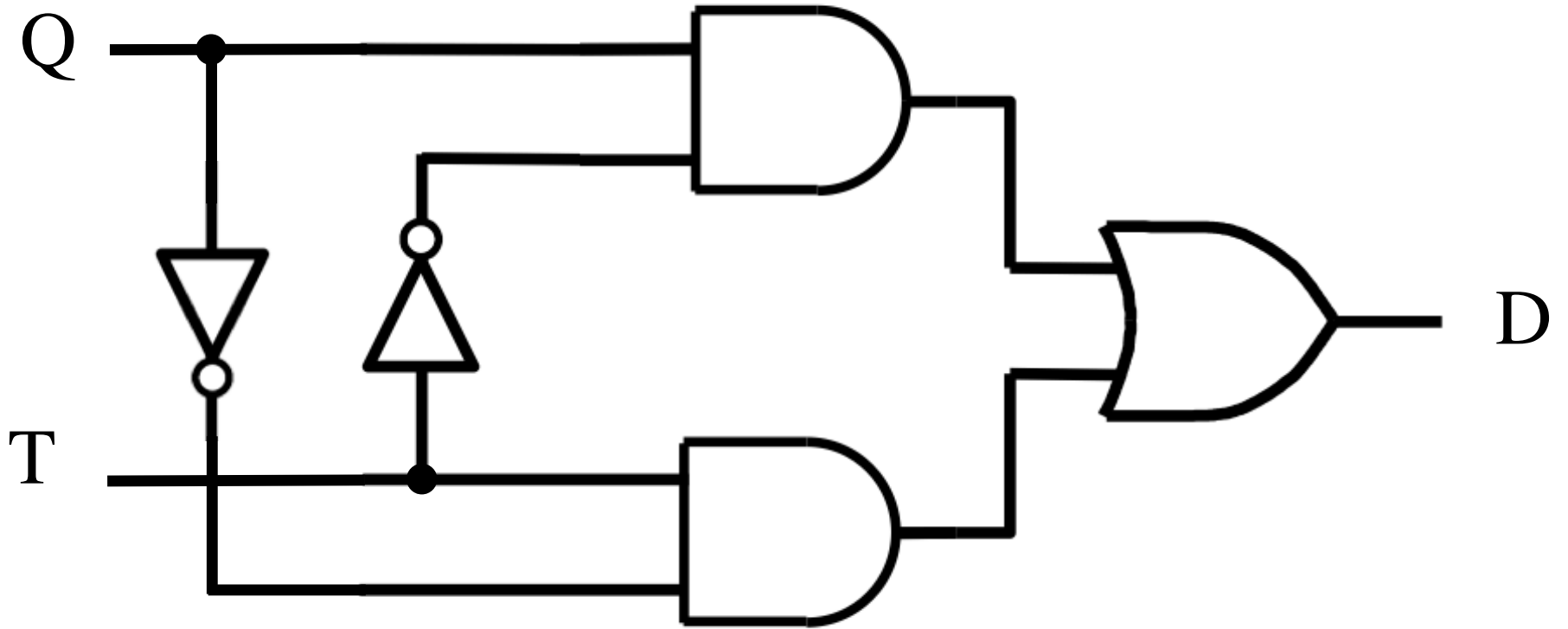


$$D = Q \oplus T$$

What is this?

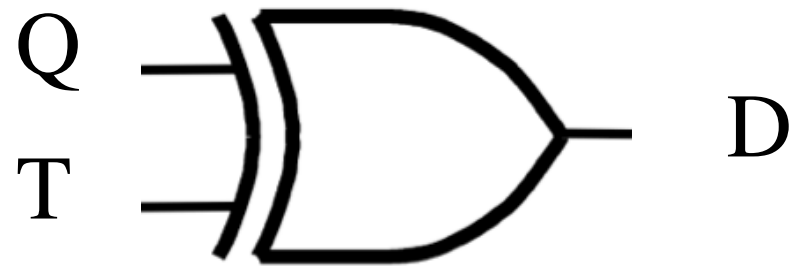


$$D = Q \oplus T$$

What is this?

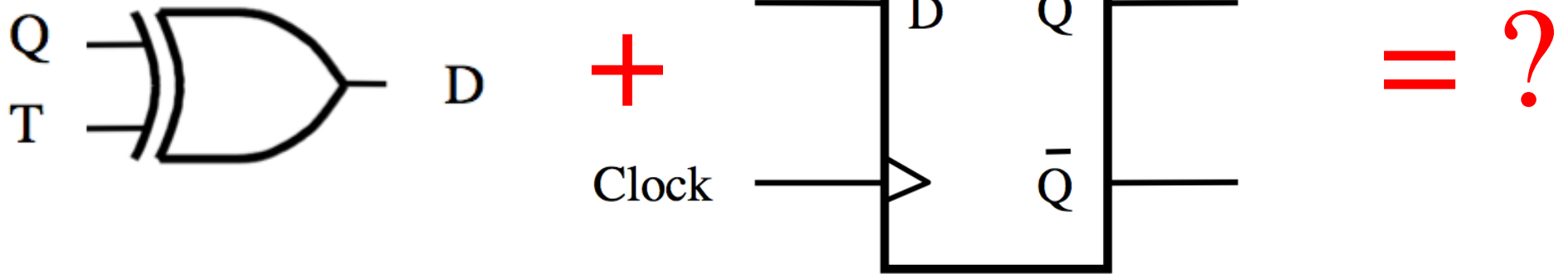


T Flip-Flop



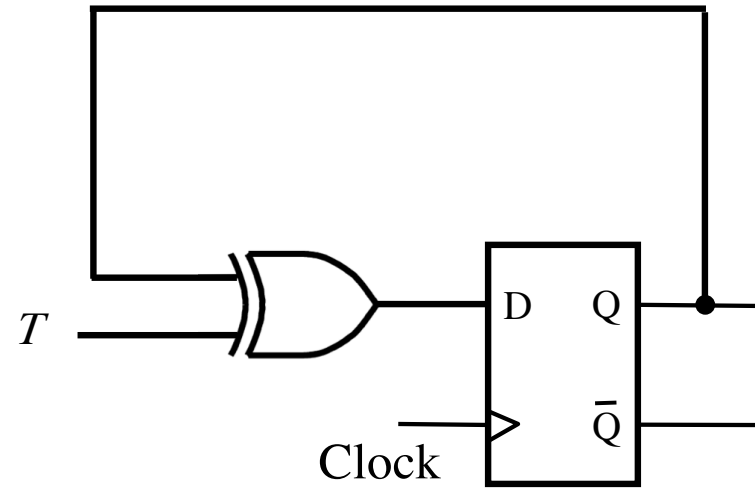


Synchronous Counter with D Flip-Flops


A three-bit up-counter with T flip-flops

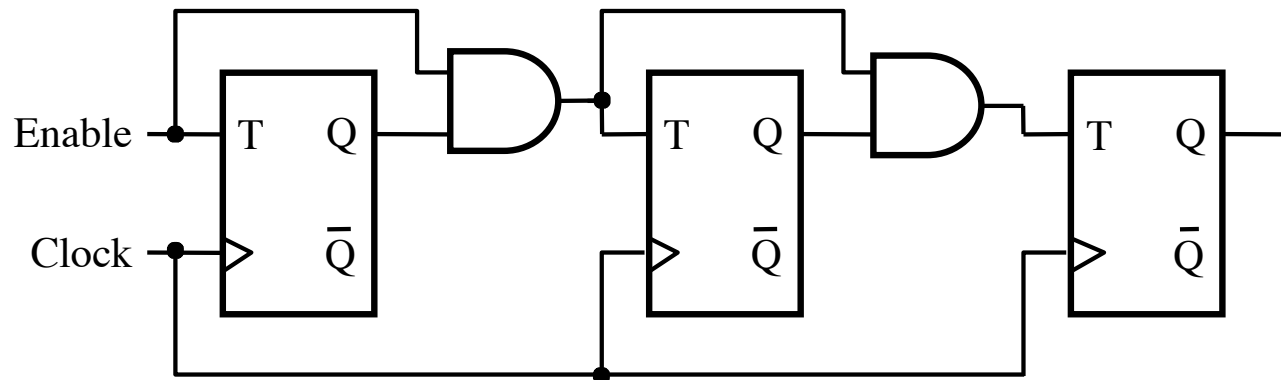


A three-bit up-counter with D flip-flops

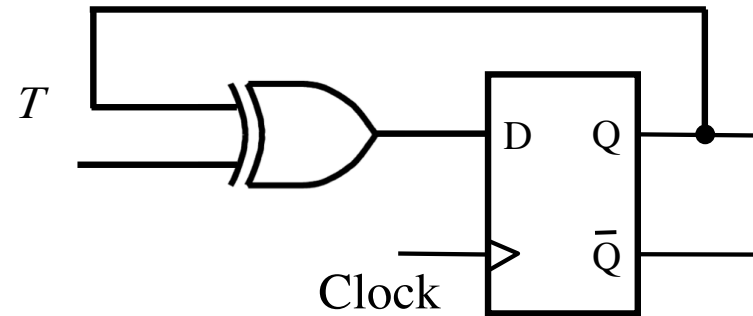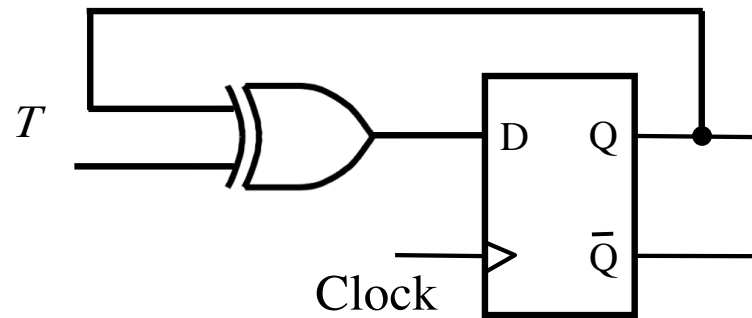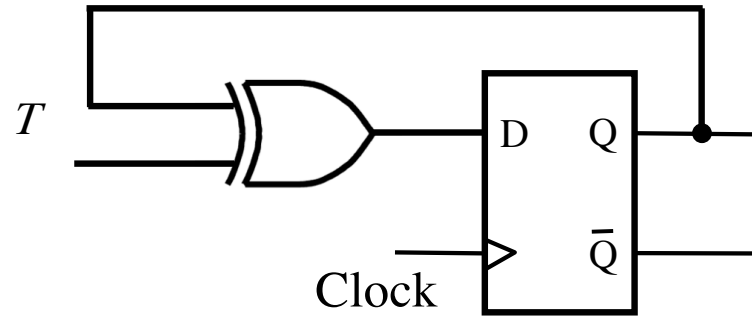


A three-bit up-counter with D flip-flops

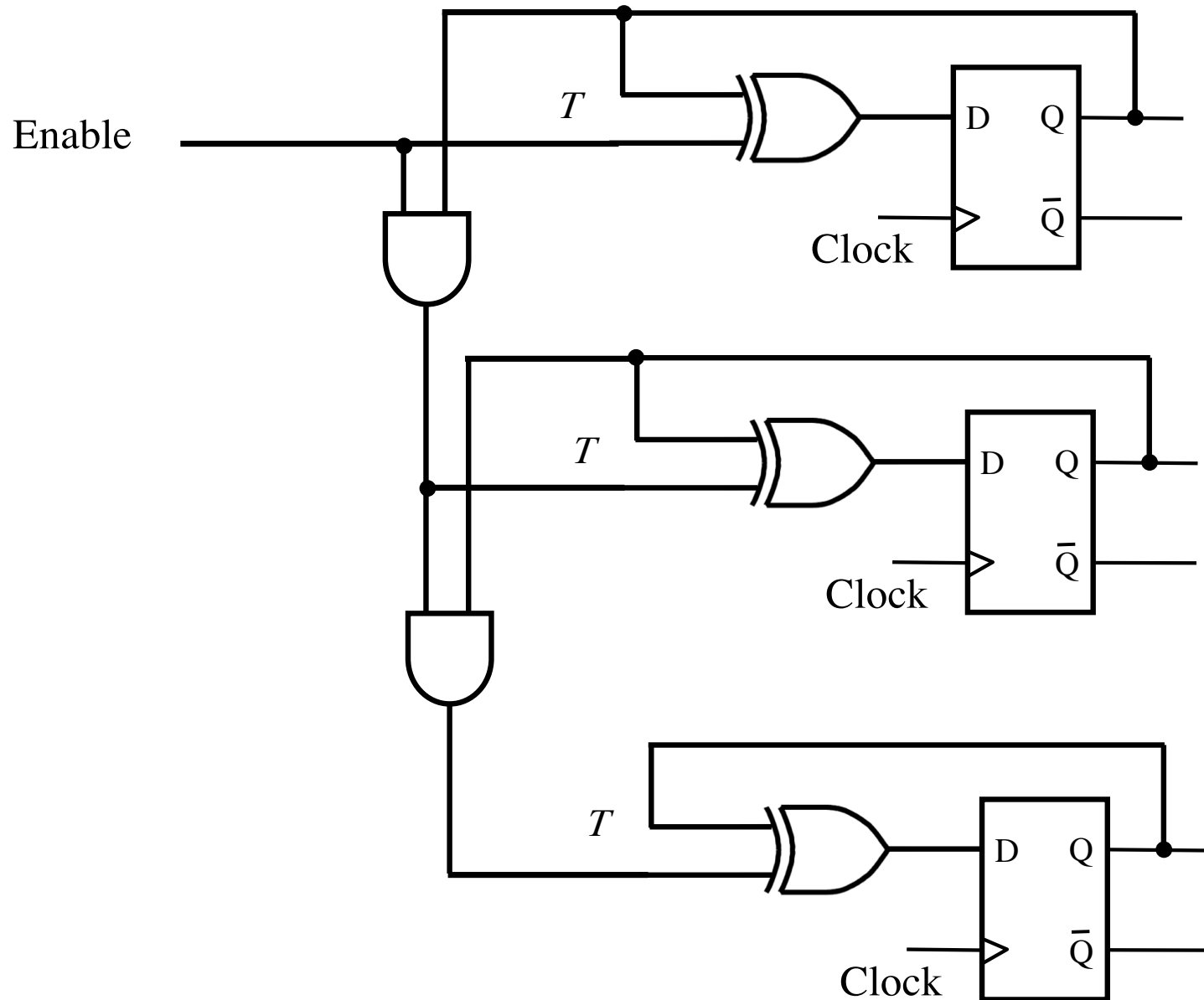


A three-bit up-counter with D flip-flops

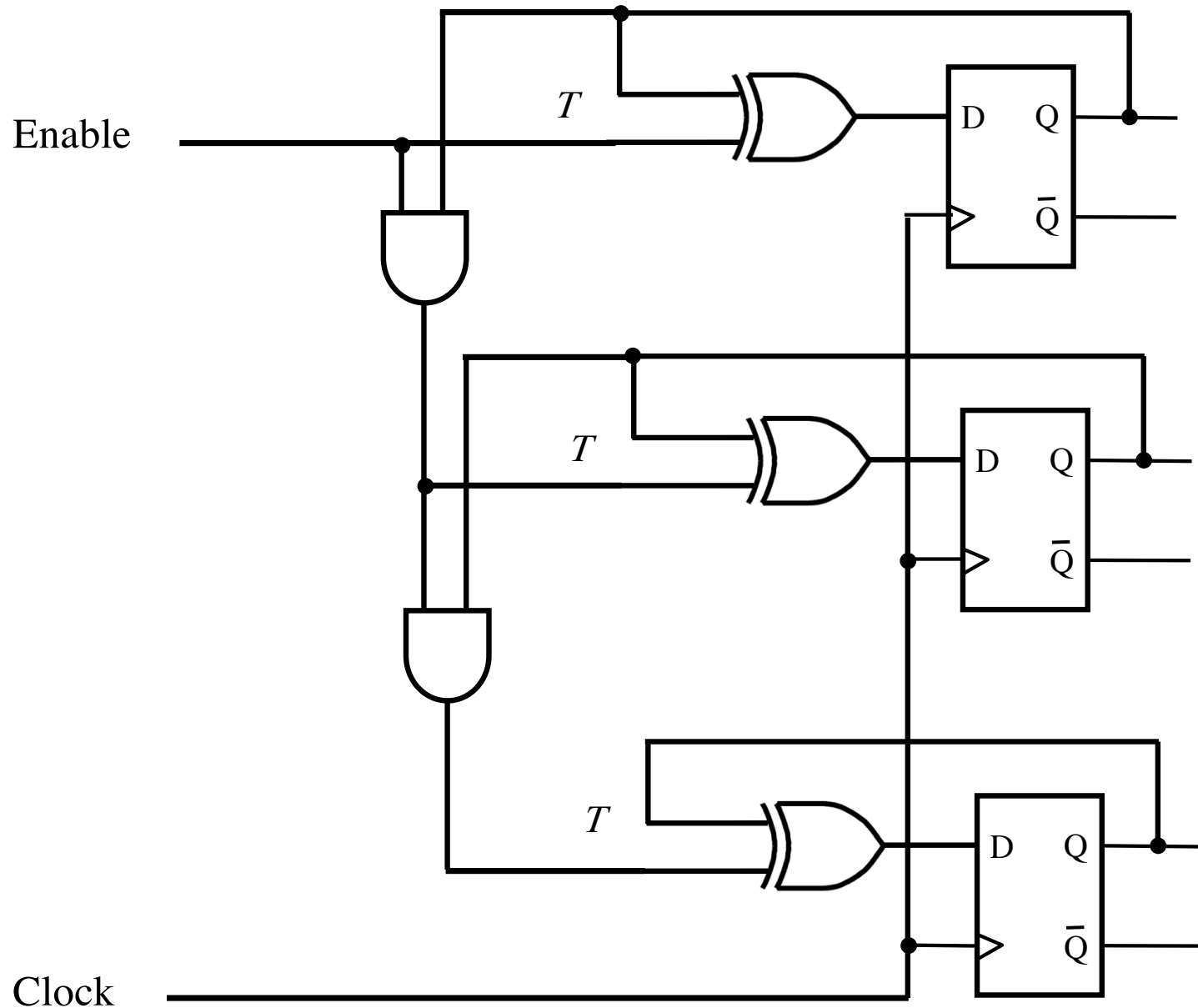

A four-bit up-counter with T flip-flops

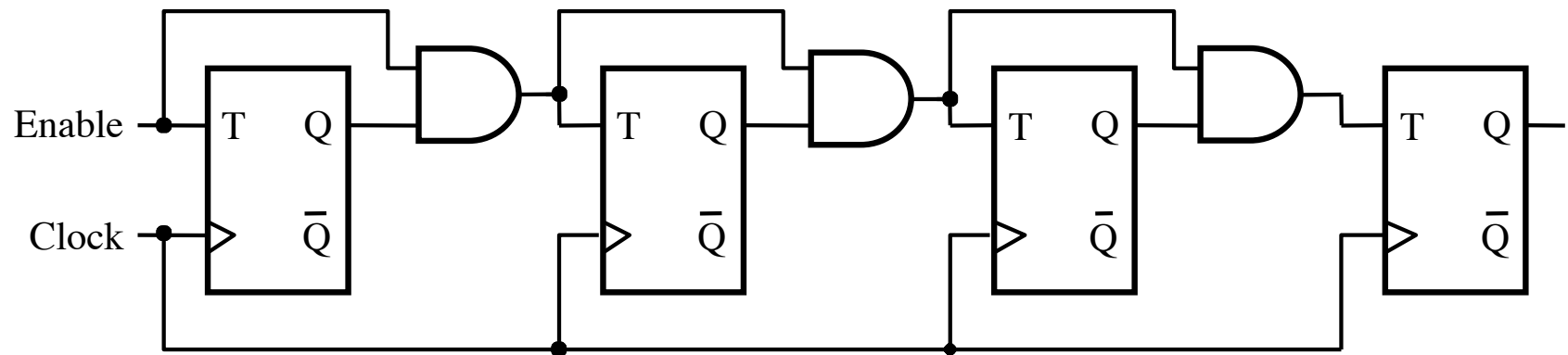

A four-bit up-counter with D flip-flops

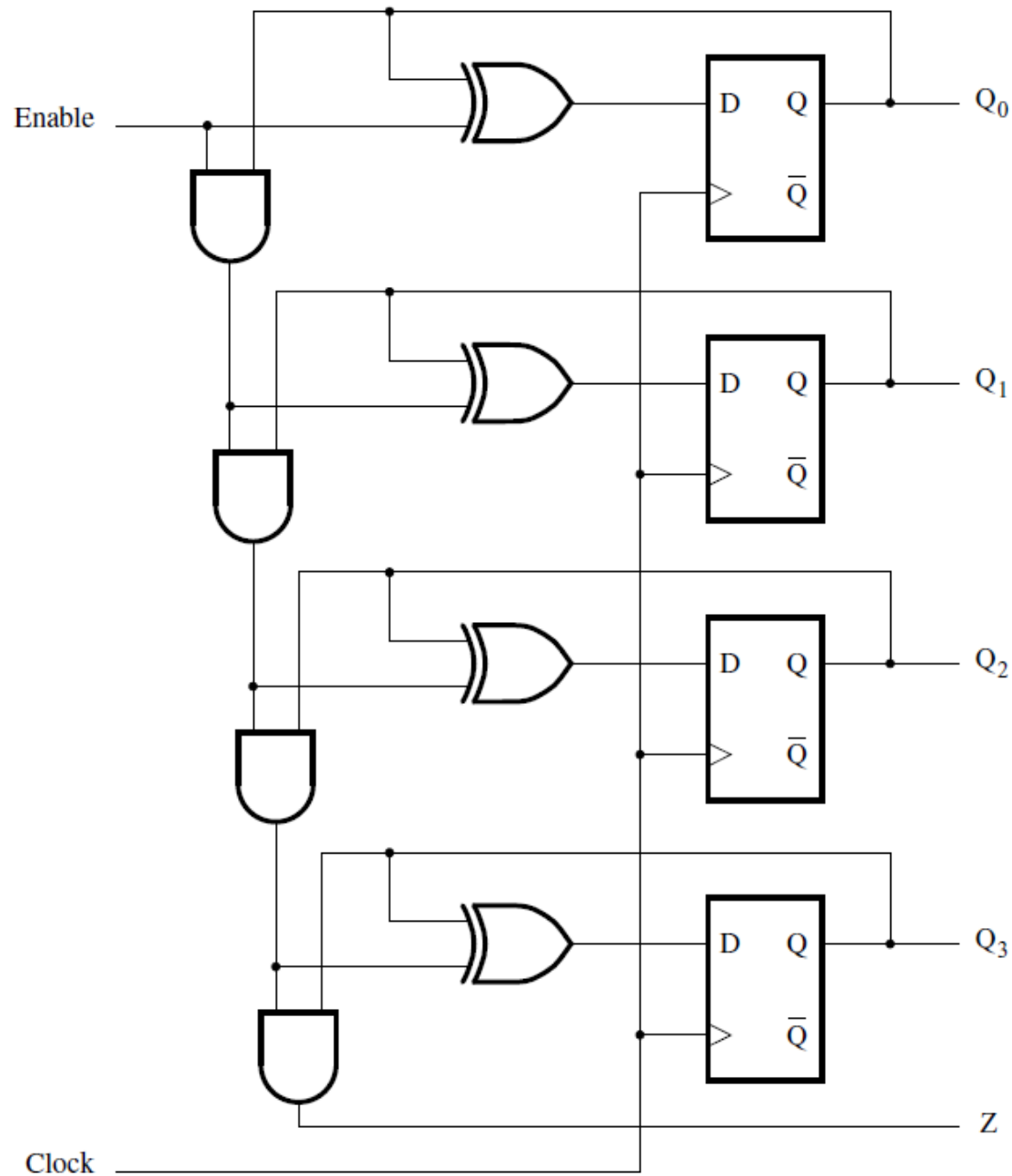


[Figure 5.23 from the textbook]

End of Mini Review

Goal

- **Implement a modulo-8 counter using the sequential circuit approach**
- **In other words, the counting sequence must be 0, 1, 2, 3, 4, 5, 6, 7, 0, 1, 2, ...**
- **The count changes based on the input signal w :**
 - **If $w=0$, then the count remains the same**
 - **If $w=1$, then the count is advanced by one**

State diagram for the counter

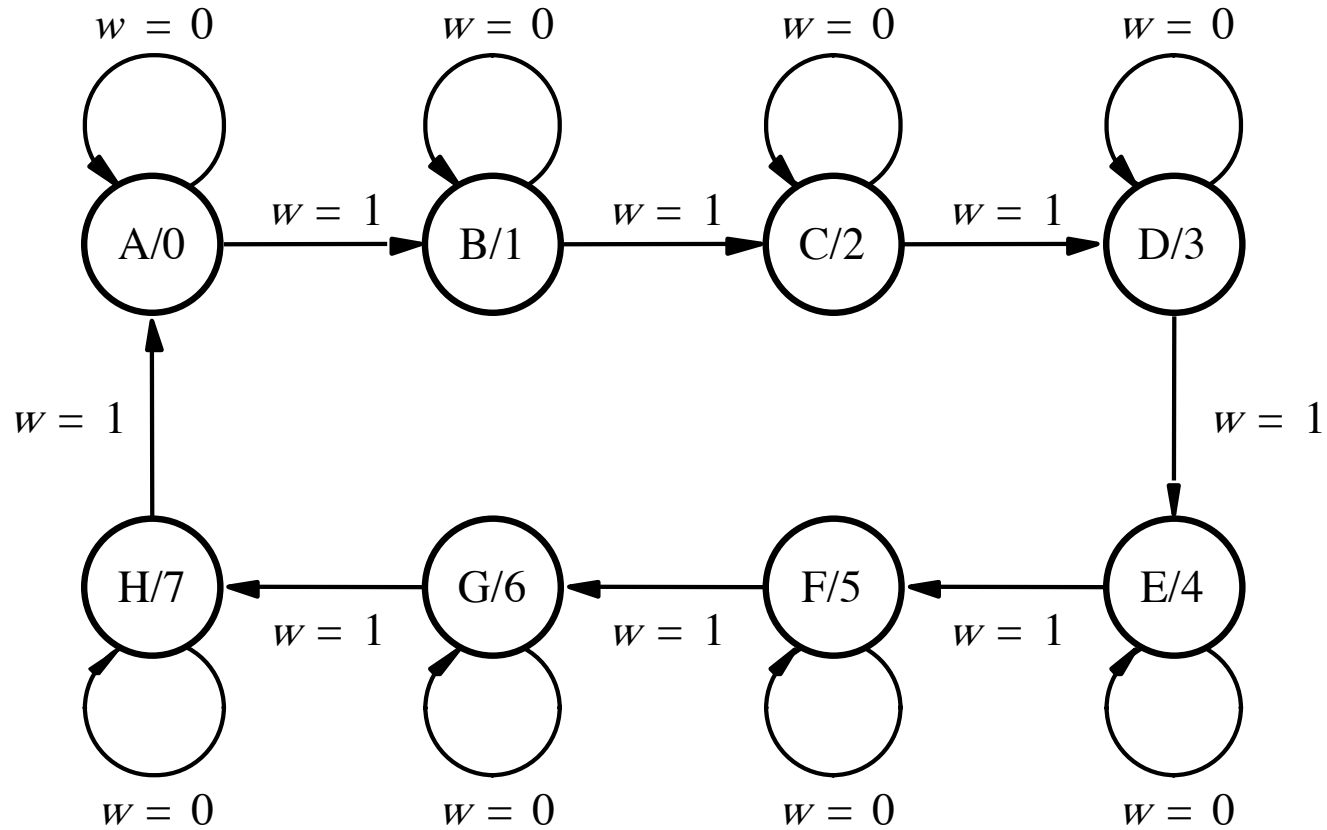

[Figure 6.60 from the textbook]

State table for the counter

| Present state | Next state | | Output |
|---------------|------------|---------|--------|
| | $w = 0$ | $w = 1$ | |
| A | A | B | 0 |
| B | B | C | 1 |
| C | C | D | 2 |
| D | D | E | 3 |
| E | E | F | 4 |
| F | F | G | 5 |
| G | G | H | 6 |
| H | H | A | 7 |

State-assigned table for the counter

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|---------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 000 | 001 | 000 |
| B | 001 | 001 | 010 | 001 |
| C | 010 | 010 | 011 | 010 |
| D | 011 | 011 | 100 | 011 |
| E | 100 | 100 | 101 | 100 |
| F | 101 | 101 | 110 | 101 |
| G | 110 | 110 | 111 | 110 |
| H | 111 | 111 | 000 | 111 |

K-map for Y_0

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 000 | 001 | 000 |
| B | 001 | 001 | 010 | 001 |
| C | 010 | 010 | 011 | 010 |
| D | 011 | 011 | 100 | 011 |
| E | 100 | 100 | 101 | 100 |
| F | 101 | 101 | 110 | 101 |
| G | 110 | 110 | 111 | 110 |
| H | 111 | 111 | 000 | 111 |

| | | | | | |
|----|--------|----------|----|----|----|
| | | y_1y_0 | | | |
| | wy_2 | 00 | 01 | 11 | 10 |
| 00 | | | | | |
| 01 | | | | | |
| 11 | | | | | |
| 10 | | | | | |

K-map for Y_0

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 0 | 1 | 000 |
| B | 001 | 1 | 0 | 001 |
| C | 010 | 0 | 1 | 010 |
| D | 011 | 1 | 0 | 011 |
| E | 100 | 0 | 1 | 100 |
| F | 101 | 1 | 0 | 101 |
| G | 110 | 0 | 1 | 110 |
| H | 111 | 1 | 0 | 111 |

| | | | | | |
|----|--------|----------|----|----|----|
| | | y_1y_0 | | | |
| | wy_2 | 00 | 01 | 11 | 10 |
| 00 | | | | | |
| 01 | | | | | |
| 11 | | | | | |
| 10 | | | | | |

K-map for Y_0

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 0 | 1 | 000 |
| B | 001 | 1 | 0 | 001 |
| C | 010 | 0 | 1 | 010 |
| D | 011 | 1 | 0 | 011 |
| E | 100 | 0 | 1 | 100 |
| F | 101 | 1 | 0 | 101 |
| G | 110 | 0 | 1 | 110 |
| H | 111 | 1 | 0 | 111 |

| wy_2 \ y_1y_0 | 00 | 01 | 11 | 10 |
|-------------------|----|----|----|----|
| 00 | 0 | 1 | 1 | 0 |
| 01 | 0 | 1 | 1 | 0 |
| 11 | 1 | 0 | 0 | 1 |
| 10 | 1 | 0 | 0 | 1 |

K-map for Y_0

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 0 | 1 | 000 |
| B | 001 | 1 | 0 | 001 |
| C | 010 | 0 | 1 | 010 |
| D | 011 | 1 | 0 | 011 |
| E | 100 | 0 | 1 | 100 |
| F | 101 | 1 | 0 | 101 |
| G | 110 | 0 | 1 | 110 |
| H | 111 | 1 | 0 | 111 |

| $wy_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 00 | 0 | 1 | 1 | 0 |
| 01 | 0 | 1 | 1 | 0 |
| 11 | 1 | 0 | 0 | 1 |
| 10 | 1 | 0 | 0 | 1 |

$$Y_0 = \bar{w}y_0 + w\bar{y}_0$$

K-map for Y_1

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 000 | 001 | 000 |
| B | 001 | 001 | 010 | 001 |
| C | 010 | 010 | 011 | 010 |
| D | 011 | 011 | 100 | 011 |
| E | 100 | 100 | 101 | 100 |
| F | 101 | 101 | 110 | 101 |
| G | 110 | 110 | 111 | 110 |
| H | 111 | 111 | 000 | 111 |

| | | | | | |
|----|--------|----------|----|----|----|
| | | y_1y_0 | | | |
| | wy_2 | 00 | 01 | 11 | 10 |
| 00 | | | | | |
| 01 | | | | | |
| 11 | | | | | |
| 10 | | | | | |

K-map for Y_1

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 0 | 0 | 000 |
| B | 001 | 0 | 1 | 001 |
| C | 010 | 1 | 1 | 010 |
| D | 011 | 1 | 0 | 011 |
| E | 100 | 0 | 0 | 100 |
| F | 101 | 0 | 1 | 101 |
| G | 110 | 1 | 1 | 110 |
| H | 111 | 1 | 0 | 111 |

| | | | | | |
|--------|----------|----|----|----|----|
| | y_1y_0 | 00 | 01 | 11 | 10 |
| wy_2 | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

K-map for Y_1

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 0 | 0 | 000 |
| B | 001 | 0 | 1 | 001 |
| C | 010 | 1 | 1 | 010 |
| D | 011 | 1 | 0 | 011 |
| E | 100 | 0 | 0 | 100 |
| F | 101 | 0 | 1 | 101 |
| G | 110 | 1 | 1 | 110 |
| H | 111 | 1 | 0 | 111 |

| | | | | | |
|--------|----|----------|----|----|----|
| | | y_1y_0 | | | |
| | | 00 | 01 | 11 | 10 |
| wy_2 | 00 | 0 | 0 | 1 | 1 |
| | 01 | 0 | 0 | 1 | 1 |
| | 11 | 0 | 1 | 0 | 1 |
| | 10 | 0 | 1 | 0 | 1 |

K-map for Y_1

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 0 | 0 | 000 |
| B | 001 | 0 | 1 | 001 |
| C | 010 | 1 | 1 | 010 |
| D | 011 | 1 | 0 | 011 |
| E | 100 | 0 | 0 | 100 |
| F | 101 | 0 | 1 | 101 |
| G | 110 | 1 | 1 | 110 |
| H | 111 | 1 | 0 | 111 |

| | | | | | |
|--------|--|----------|----|----|----|
| | | y_1y_0 | | | |
| wy_2 | | 00 | 01 | 11 | 10 |
| 00 | | 0 | 0 | 1 | 1 |
| 01 | | 0 | 0 | 1 | 1 |
| 11 | | 0 | 1 | 0 | 1 |
| 10 | | 0 | 1 | 0 | 1 |

$$Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1$$

K-map for Y_2

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 000 | 001 | 000 |
| B | 001 | 001 | 010 | 001 |
| C | 010 | 010 | 011 | 010 |
| D | 011 | 011 | 100 | 011 |
| E | 100 | 100 | 101 | 100 |
| F | 101 | 101 | 110 | 101 |
| G | 110 | 110 | 111 | 110 |
| H | 111 | 111 | 000 | 111 |

| | | | | | |
|--------|----------|----|----|----|----|
| | y_1y_0 | 00 | 01 | 11 | 10 |
| wy_2 | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

K-map for Y_2

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 0 | 0 | 000 |
| B | 001 | 0 | 0 | 001 |
| C | 010 | 0 | 0 | 010 |
| D | 011 | 0 | 1 | 011 |
| E | 100 | 1 | 1 | 100 |
| F | 101 | 1 | 1 | 101 |
| G | 110 | 1 | 1 | 110 |
| H | 111 | 1 | 0 | 111 |

| | | | | | |
|--------|----------|----|----|----|----|
| | y_1y_0 | 00 | 01 | 11 | 10 |
| wy_2 | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

K-map for Y_2

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 0 | 0 | 000 |
| B | 001 | 0 | 0 | 001 |
| C | 010 | 0 | 0 | 010 |
| D | 011 | 0 | 1 | 011 |
| E | 100 | 1 | 1 | 100 |
| F | 101 | 1 | 1 | 101 |
| G | 110 | 1 | 1 | 110 |
| H | 111 | 1 | 0 | 111 |

| | | | | | |
|--------|----|----------|----|----|----|
| | | y_1y_0 | | | |
| | | 00 | 01 | 11 | 10 |
| wy_2 | 00 | 0 | 0 | 0 | 0 |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | 1 | 1 | 0 | 1 |
| | 10 | 0 | 0 | 1 | 0 |

K-map for Y_2

| | Present state $y_2y_1y_0$ | Next state | | Count $z_2z_1z_0$ |
|---|------------------------------|-------------|-------------|----------------------|
| | | $w = 0$ | $w = 1$ | |
| | | $Y_2Y_1Y_0$ | $Y_2Y_1Y_0$ | |
| A | 000 | 0 | 0 | 000 |
| B | 001 | 0 | 0 | 001 |
| C | 010 | 0 | 0 | 010 |
| D | 011 | 0 | 1 | 011 |
| E | 100 | 1 | 1 | 100 |
| F | 101 | 1 | 1 | 101 |
| G | 110 | 1 | 1 | 110 |
| H | 111 | 1 | 0 | 111 |

| | | | | | |
|--------|----|----------|----|----|----|
| | | y_1y_0 | | | |
| | | 00 | 01 | 11 | 10 |
| wy_2 | 00 | 0 | 0 | 0 | 0 |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | 1 | 1 | 0 | 1 |
| | 10 | 0 | 0 | 1 | 0 |

$$Y_2 = \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + wy_0y_1\bar{y}_2$$

Karnaugh maps for D flip-flops for the counter

| | | | | | |
|--------|----|----------|----|----|----|
| | | y_1y_0 | | | |
| | | 00 | 01 | 11 | 10 |
| wy_2 | 00 | 0 | 1 | 1 | 0 |
| | 01 | 0 | 1 | 1 | 0 |
| | 11 | 1 | 0 | 0 | 1 |
| | 10 | 1 | 0 | 0 | 1 |

$$Y_0 = \bar{w}y_0 + wy_0$$


| | | | | | |
|--------|----|----------|----|----|----|
| | | y_1y_0 | | | |
| | | 00 | 01 | 11 | 10 |
| wy_2 | 00 | 0 | 0 | 1 | 1 |
| | 01 | 0 | 0 | 1 | 1 |
| | 11 | 0 | 1 | 0 | 1 |
| | 10 | 0 | 1 | 0 | 1 |

$$Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1$$

| | | | | | |
|--------|----|----------|----|----|----|
| | | y_1y_0 | | | |
| | | 00 | 01 | 11 | 10 |
| wy_2 | 00 | 0 | 0 | 0 | 0 |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | 1 | 1 | 0 | 1 |
| | 10 | 0 | 0 | 1 | 0 |


$$Y_2 = \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + wy_0y_1\bar{y}_2$$

Circuit diagram
for the counter
implemented
with D flip-flops

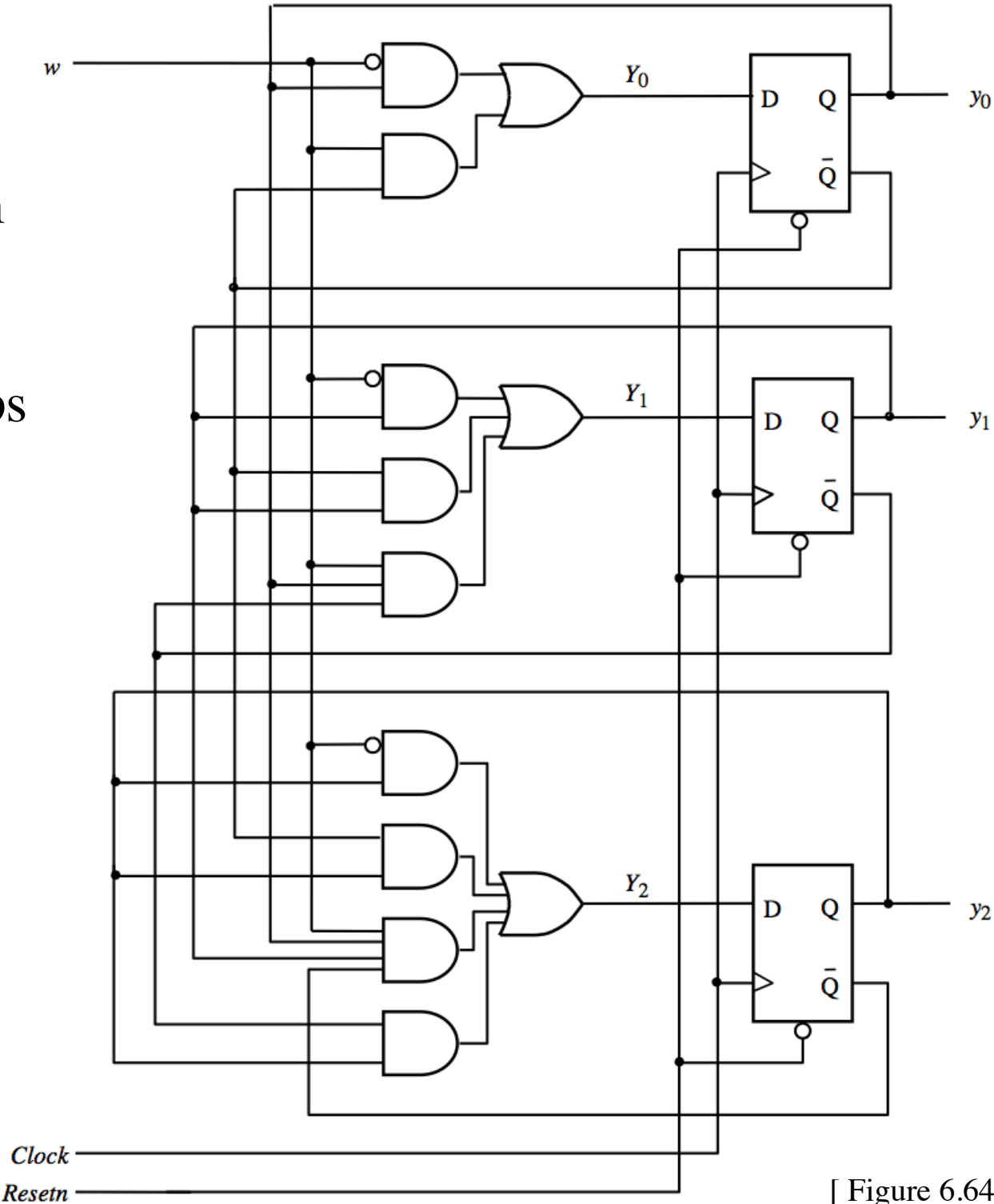


[Figure 6.64 from the textbook]

Circuit diagram
for the counter
implemented
with D flip-flops

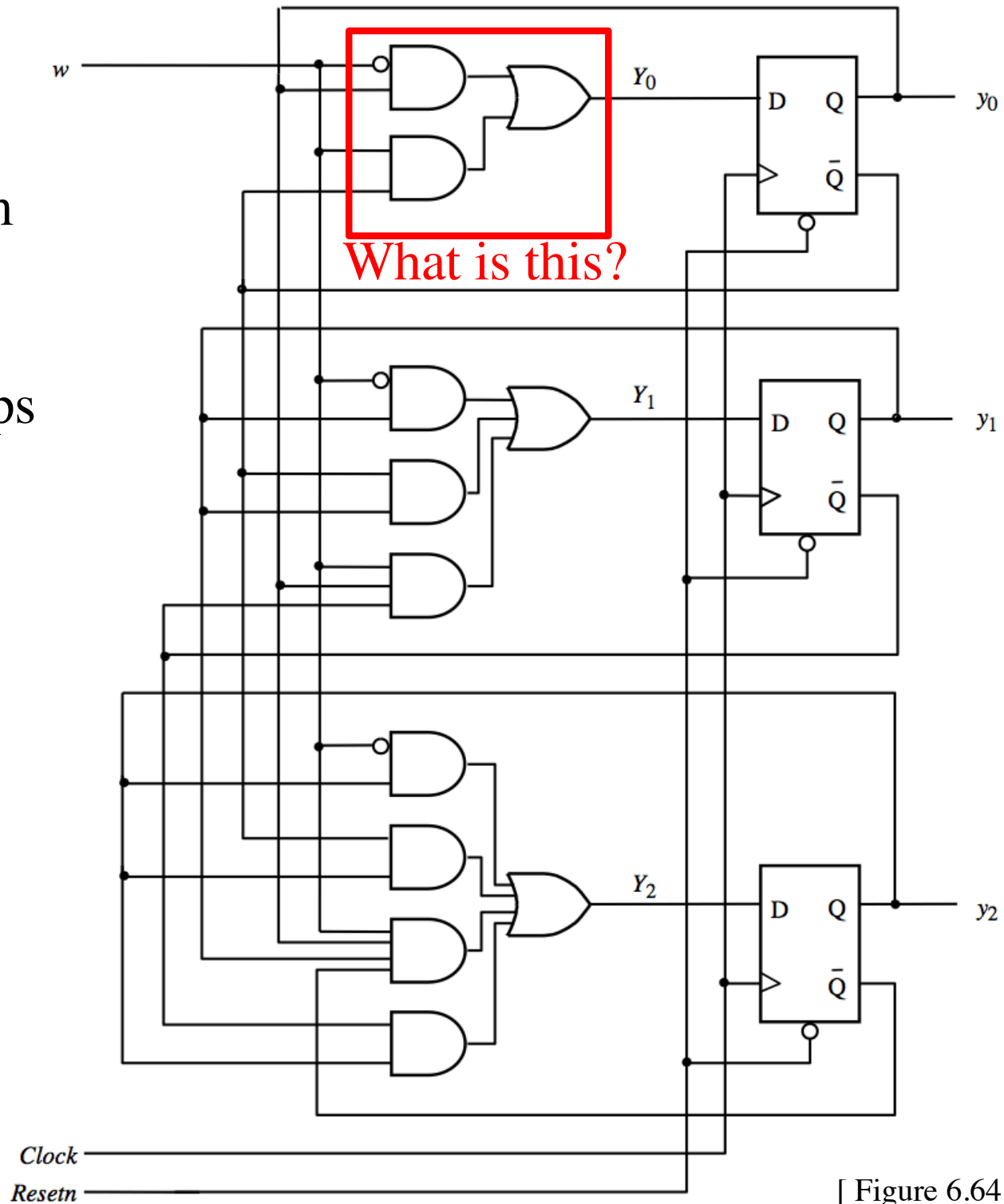

[Figure 6.64 from the textbook]

Circuit diagram
for the counter
implemented
with D flip-flops

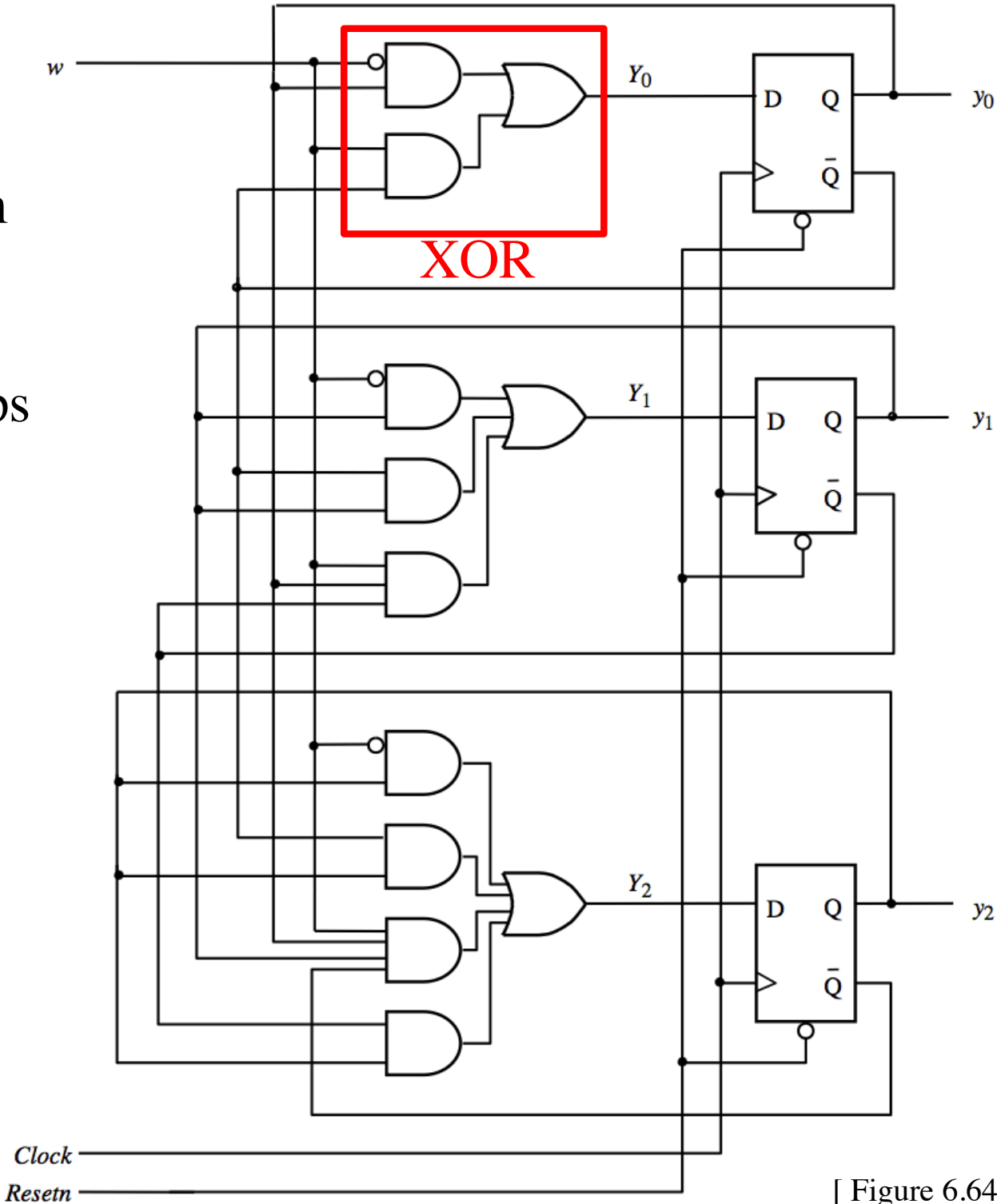

[Figure 6.64 from the textbook]

We can simplify all three expressions

$$Y_0 = \bar{w}y_0 + wy_0\bar{y}_0$$

$$Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1$$

$$Y_2 = \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + wy_0y_1\bar{y}_2$$

We can simplify all three expressions

$$Y_0 = \bar{w}y_0 + w\bar{y}_0$$

$$\begin{aligned} D_0 &= \bar{w}y_0 + w\bar{y}_0 \\ &= w \oplus y_0 \end{aligned}$$


$$Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1$$

$$\begin{aligned} D_1 &= \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1 \\ &= (\bar{w} + \bar{y}_0)y_1 + wy_0\bar{y}_1 \\ &= \bar{w}\bar{y}_0y_1 + wy_0\bar{y}_1 \\ &= wy_0 \oplus y_1 \end{aligned}$$


$$Y_2 = \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + wy_0y_1\bar{y}_2$$

$$\begin{aligned} D_2 &= \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + wy_0y_1\bar{y}_2 \\ &= (\bar{w} + \bar{y}_0 + \bar{y}_1)y_2 + wy_0y_1\bar{y}_2 \\ &= \bar{w}\bar{y}_0\bar{y}_1y_2 + wy_0y_1\bar{y}_2 \\ &= wy_0y_1 \oplus y_2 \end{aligned}$$

A three-bit counter with D flip-flops

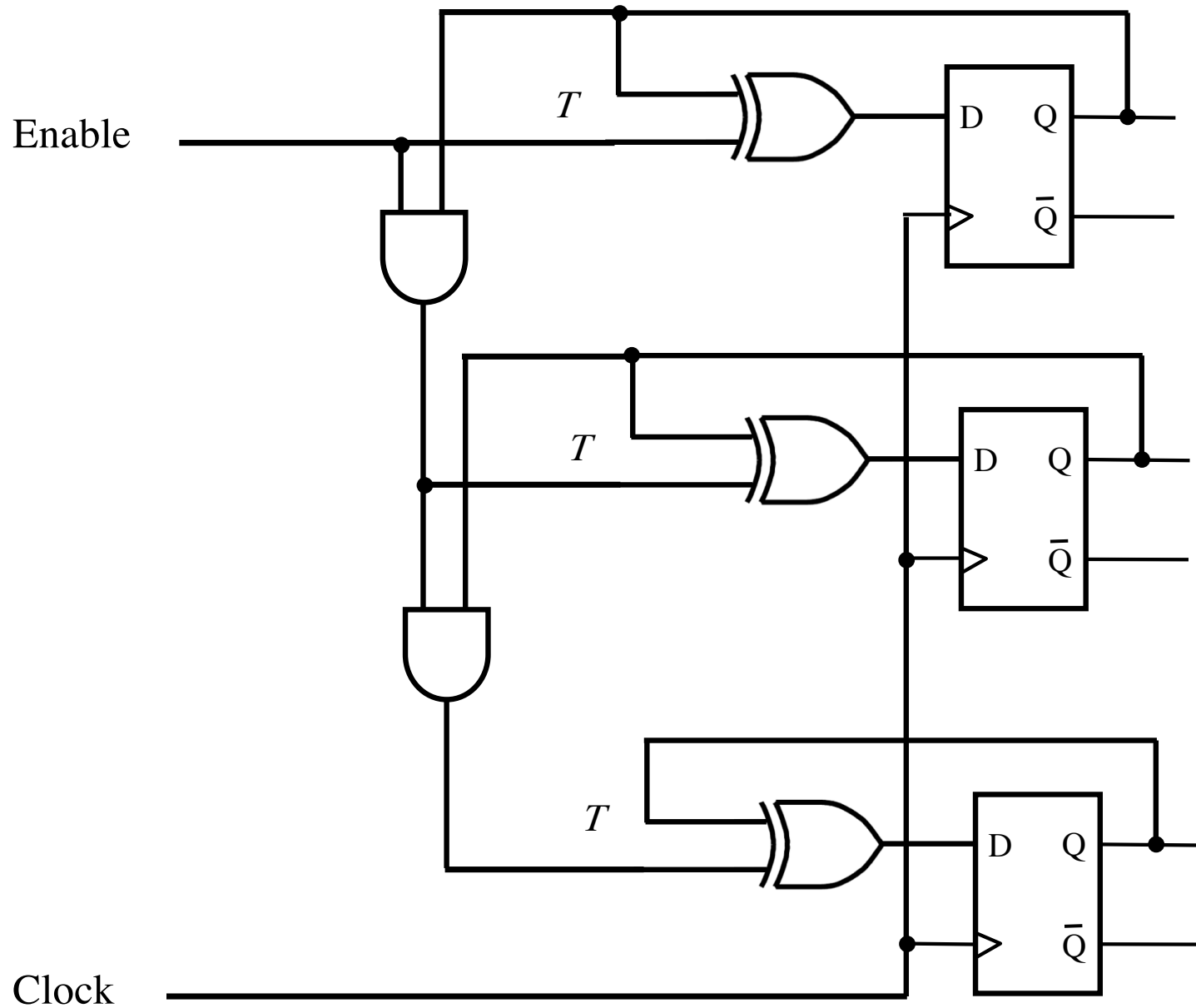

A four-bit counter with D flip-flops

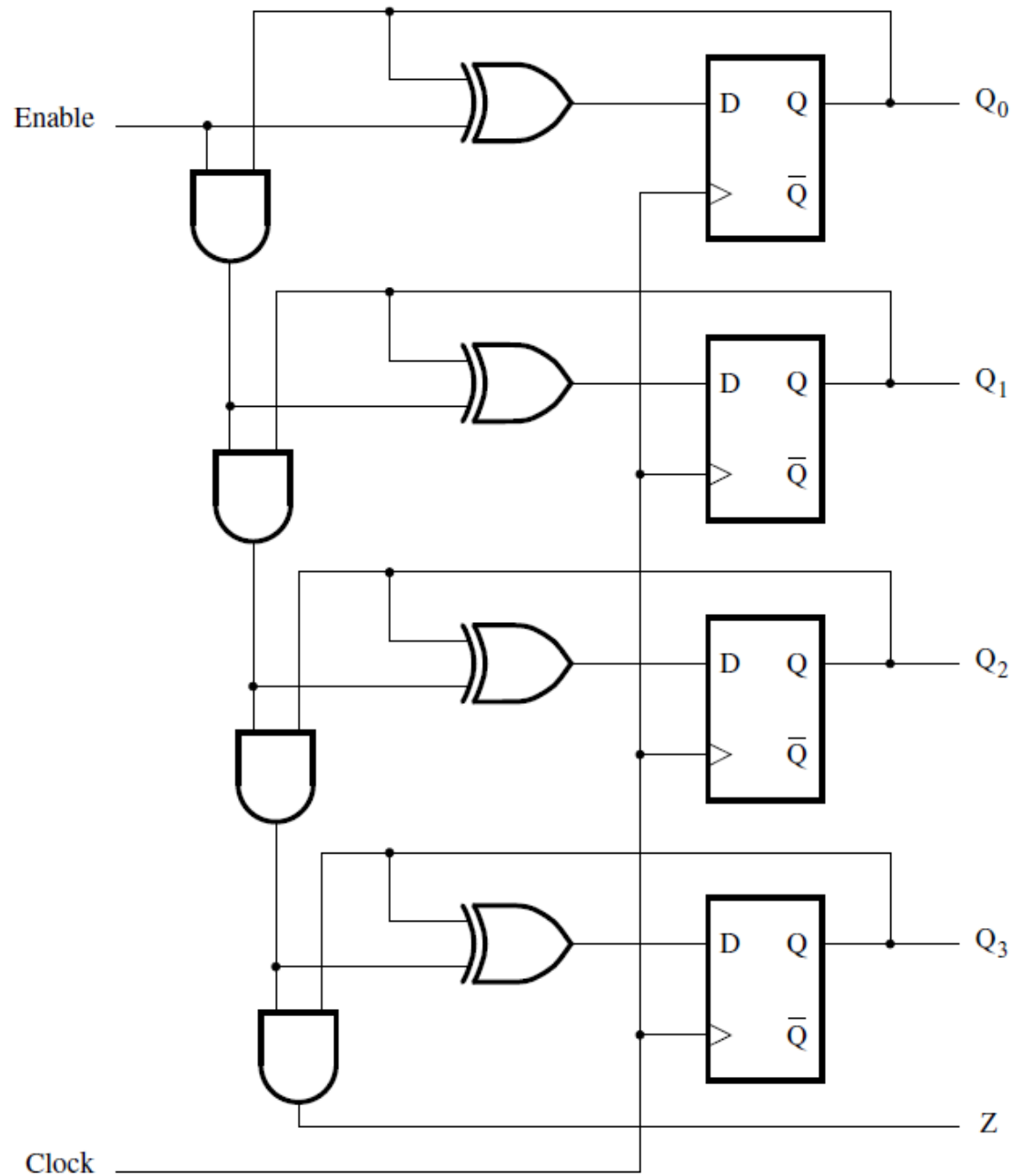


[Figure 5.23 from the textbook]

Summary

- **The up-counters that we studied in Chapter 5 can now be derived using the sequential circuit approach**
- **We get the same circuit diagrams as before**


Example 2:
Implement a modulo-8 counter
using JK Flip-Flops

JK Flip-Flop

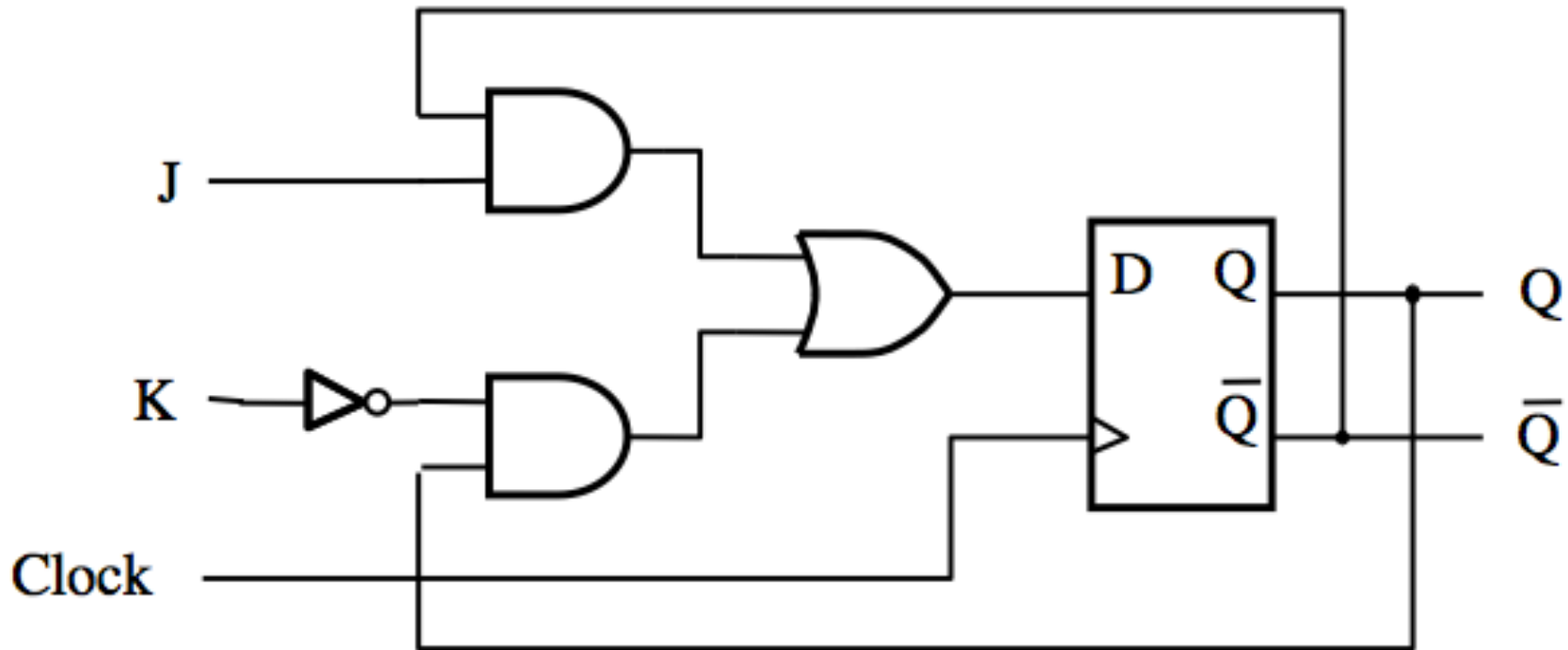

$$D = \overline{JQ} + \overline{KQ}$$


JK Flip-Flop

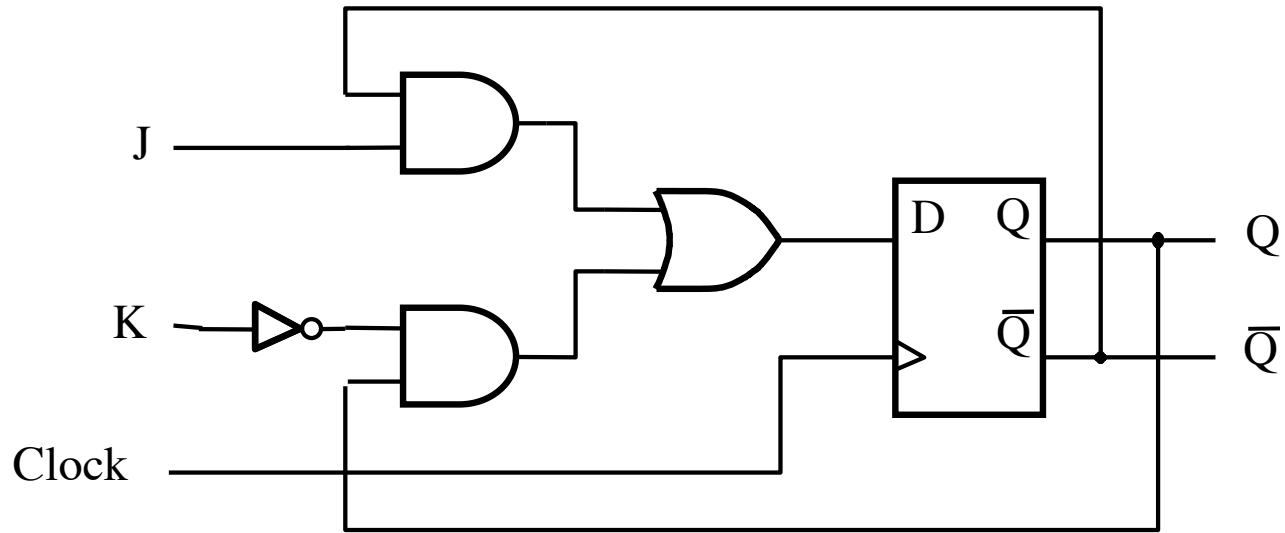

(a) Circuit

| J | K | $Q(t+1)$ |
|---|---|--------------|
| 0 | 0 | $Q(t)$ |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | $\bar{Q}(t)$ |

(b) Truth table

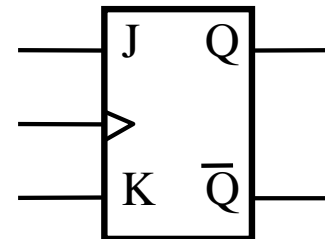

(c) Graphical symbol

JK Flip-Flop (How it Works)

**A versatile circuit that can be used both as a
SR flip-flop and as a T flip flop**

If $J=0$ and $K=0$ it stays in the same state

Just like SR It can be set and reset

$J=S$ and $K=R$

If $J=K$ then it behaves as a T flip-flop

Transition Rules in terms of J and K

Current State
of the Flip-flop: $Q(t)$

Next State
of the Flip-flop: $Q(t+1)$

| J | K | $Q(t+1)$ |
|---|---|--------------|
| 0 | 0 | $Q(t)$ |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | $\bar{Q}(t)$ |

- From 0 to 0 $J=0$ and $K=d$
- From 0 to 1 $J=1$ and $K=d$
- From 1 to 0 $J=d$ and $K=1$
- From 1 to 1 $J=d$ and $K=0$

Transition Rules in terms of J and K

Current State of the Flip-flop: $Q(t)$ Next State of the Flip-flop: $Q(t+1)$

- From 0 to 0 $J=0$ and $K=d$
- From 0 to 1 $J=1$ and $K=d$
- From 1 to 0 $J=d$ and $K=1$
- From 1 to 1 $J=d$ and $K=0$

| J | K | $Q(t+1)$ |
|---|---|--------------|
| 0 | 0 | $Q(t)$ |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | $\bar{Q}(t)$ |

| $Q(t) \rightarrow Q(t+1)$ | J | K |
|---------------------------|---|---|
| $0 \rightarrow 0$ | 0 | d |
| $0 \rightarrow 1$ | 1 | d |
| $1 \rightarrow 0$ | d | 1 |
| $1 \rightarrow 1$ | d | 0 |

Excitation table for the counter with JK flip-flops

| | Present state $y_2y_1y_0$ | Flip-flop inputs | | | | | | | | Count $z_2z_1z_0$ |
|---|------------------------------|------------------|----------|----------|----------|-------------|----------|----------|----------|----------------------|
| | | $w = 0$ | | | | $w = 1$ | | | | |
| | | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | |
| A | 000 | 000 | 0d | 0d | 0d | 001 | 0d | 0d | 1d | 000 |
| B | 001 | 001 | 0d | 0d | d0 | 010 | 0d | 1d | d1 | 001 |
| C | 010 | 010 | 0d | d0 | 0d | 011 | 0d | d0 | 1d | 010 |
| D | 011 | 011 | 0d | d0 | d0 | 100 | 1d | d1 | d1 | 011 |
| E | 100 | 100 | d0 | 0d | 0d | 101 | d0 | 0d | 1d | 100 |
| F | 101 | 101 | d0 | 0d | d0 | 110 | d0 | 1d | d1 | 101 |
| G | 110 | 110 | d0 | d0 | 0d | 111 | d0 | d0 | 1d | 110 |
| H | 111 | 111 | d0 | d0 | d0 | 000 | d1 | d1 | d1 | 111 |

Excitation table for the counter with JK flip-flops



| | Present state $y_2y_1y_0$ | Flip-flop inputs | | | | | | | | Count $z_2z_1z_0$ |
|---|------------------------------|------------------|----------|----------|----------|-------------|----------|----------|----------|----------------------|
| | | $w = 0$ | | | | $w = 1$ | | | | |
| | | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | |
| A | 000 | 000 | 0d | 0d | 0d | 001 | 0d | 0d | 1d | 000 |
| B | 001 | 001 | 0d | 0d | d0 | 010 | 0d | 1d | d1 | 001 |
| C | 010 | 010 | 0d | d0 | 0d | 011 | 0d | d0 | 1d | 010 |
| D | 011 | 011 | 0d | d0 | d0 | 100 | 1d | d1 | d1 | 011 |
| E | 100 | 100 | d0 | 0d | 0d | 101 | d0 | 0d | 1d | 100 |
| F | 101 | 101 | d0 | 0d | d0 | 110 | d0 | 1d | d1 | 101 |
| G | 110 | 110 | d0 | d0 | 0d | 111 | d0 | d0 | 1d | 110 |
| H | 111 | 111 | d0 | d0 | d0 | 000 | d1 | d1 | d1 | 111 |

| $Q(t) \rightarrow Q(t+1)$ | J K |
|---------------------------|------------|
| 0 → 0 | 0 d |
| 0 → 1 | 1 d |
| 1 → 0 | d 1 |
| 1 → 1 | d 0 |

[Figure 6.65 from the textbook]



Karnaugh maps for the first JK flip-flop

| | Present state $y_2y_1y_0$ | Flip-flop inputs | | | | | | | Count $z_2z_1z_0$ | |
|---|------------------------------|------------------|----------|----------|----------|-------------|----------|----------|----------------------|----------|
| | | $w = 0$ | | | | $w = 1$ | | | | |
| | | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | | J_0K_0 |
| A | 000 | 000 | 0d | 0d | 0d | 001 | 0d | 0d | 1d | 000 |
| B | 001 | 001 | 0d | 0d | d0 | 010 | 0d | 1d | d1 | 001 |
| C | 010 | 010 | 0d | d0 | 0d | 011 | 0d | d0 | 1d | 010 |
| D | 011 | 011 | 0d | d0 | d0 | 100 | 1d | d1 | d1 | 011 |
| E | 100 | 100 | d0 | 0d | 0d | 101 | d0 | 0d | 1d | 100 |
| F | 101 | 101 | d0 | 0d | d0 | 110 | d0 | 1d | d1 | 101 |
| G | 110 | 110 | d0 | d0 | 0d | 111 | d0 | d0 | 1d | 110 |
| H | 111 | 111 | d0 | d0 | d0 | 000 | d1 | d1 | d1 | 111 |

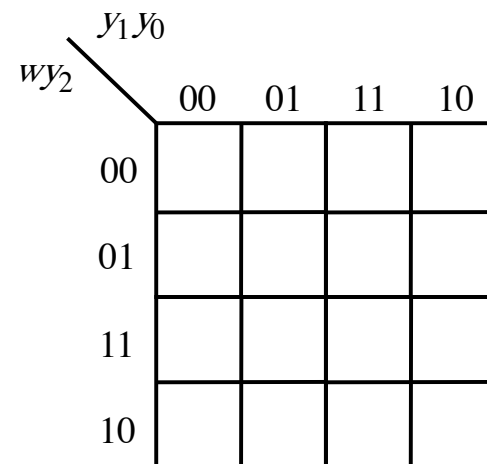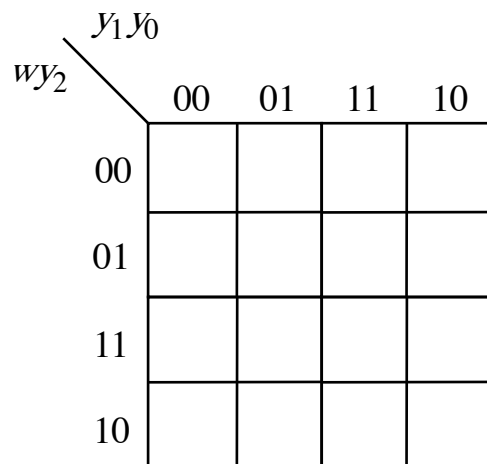



Karnaugh maps for the first JK flip-flop

| | Present state $y_2y_1y_0$ | Flip-flop inputs | | | | | | | Count $z_2z_1z_0$ | |
|---|------------------------------|------------------|----------|----------|----------|-------------|----------|----------|----------------------|----------|
| | | $w = 0$ | | | $w = 1$ | | | | | |
| | | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | | J_0K_0 |
| A | 000 | 000 | 0d | 0d | 0d | 001 | 0d | 0d | 1d | 000 |
| B | 001 | 001 | 0d | 0d | d0 | 010 | 0d | 1d | d1 | 001 |
| C | 010 | 010 | 0d | d0 | 0d | 011 | 0d | d0 | 1d | 010 |
| D | 011 | 011 | 0d | d0 | d0 | 100 | 1d | d1 | d1 | 011 |
| E | 100 | 100 | d0 | 0d | 0d | 101 | d0 | 0d | 1d | 100 |
| F | 101 | 101 | d0 | 0d | d0 | 110 | d0 | 1d | d1 | 101 |
| G | 110 | 110 | d0 | d0 | 0d | 111 | d0 | d0 | 1d | 110 |
| H | 111 | 111 | d0 | d0 | d0 | 000 | d1 | d1 | d1 | 111 |

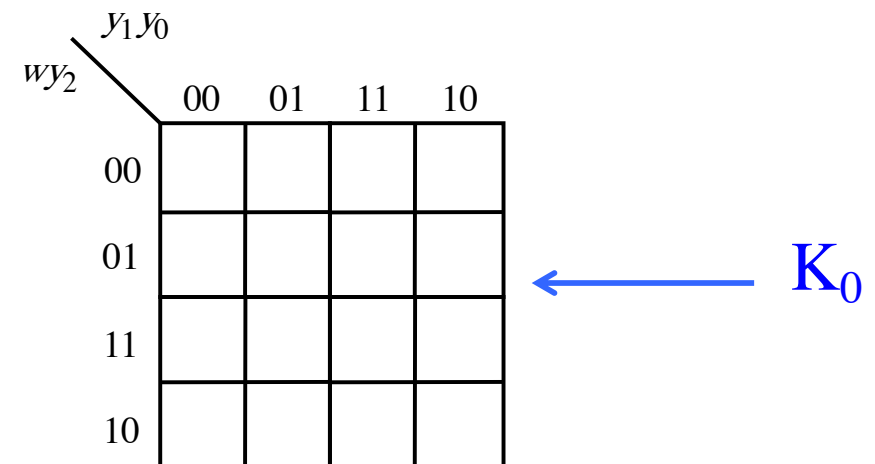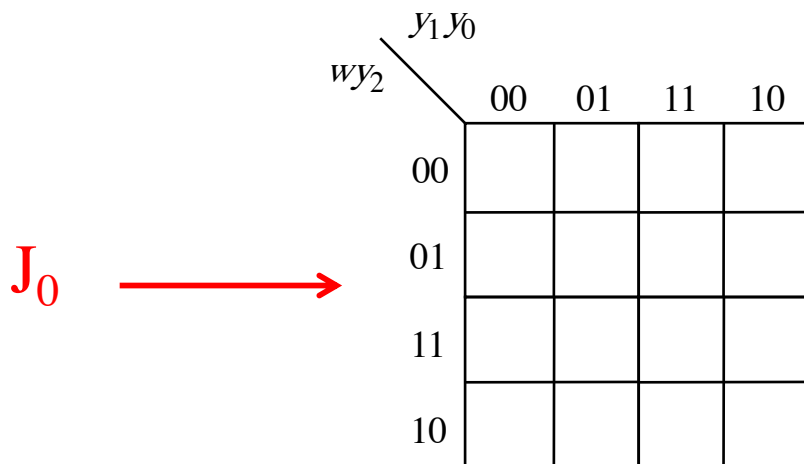



Karnaugh maps for the first JK flip-flop

| | Present state $y_2y_1y_0$ | Flip-flop inputs | | | | | | | Count $z_2z_1z_0$ | |
|---|------------------------------|------------------|----------|----------|----------|-------------|----------|----------|----------------------|----------|
| | | $w = 0$ | | | $w = 1$ | | | | | |
| | | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | | J_0K_0 |
| A | 000 | 000 | 0d | 0d | 0d | 001 | 0d | 0d | 1d | 000 |
| B | 001 | 001 | 0d | 0d | d0 | 010 | 0d | 1d | d1 | 001 |
| C | 010 | 010 | 0d | d0 | 0d | 011 | 0d | d0 | 1d | 010 |
| D | 011 | 011 | 0d | d0 | d0 | 100 | 1d | d1 | d1 | 011 |
| E | 100 | 100 | d0 | 0d | 0d | 101 | d0 | 0d | 1d | 100 |
| F | 101 | 101 | d0 | 0d | d0 | 110 | d0 | 1d | d1 | 101 |
| G | 110 | 110 | d0 | d0 | 0d | 111 | d0 | d0 | 1d | 110 |
| H | 111 | 111 | d0 | d0 | d0 | 000 | d1 | d1 | d1 | 111 |

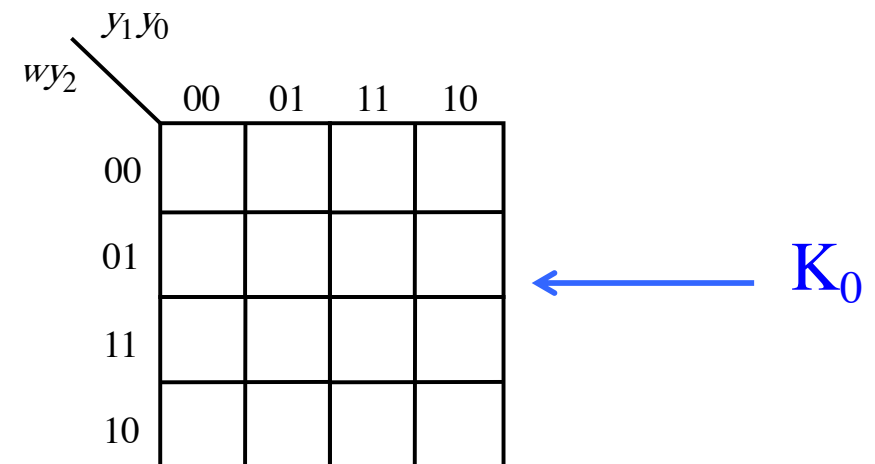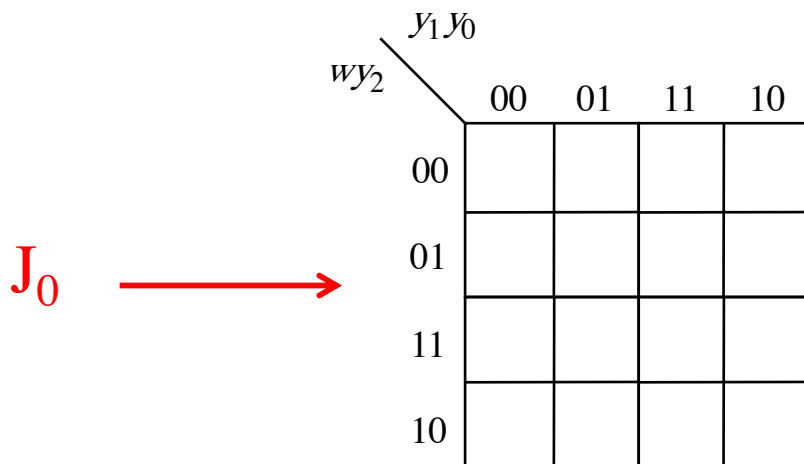



Karnaugh maps for the first JK flip-flop

| | Present state $y_2y_1y_0$ | Flip-flop inputs | | | | | | | Count $z_2z_1z_0$ | |
|---|------------------------------|------------------|----------|----------|----------|-------------|----------|----------|----------------------|----------|
| | | $w = 0$ | | | | $w = 1$ | | | | |
| | | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | | J_0K_0 |
| A | 000 | 000 | 0d | 0d | 0d | 001 | 0d | 0d | 1d | 000 |
| B | 001 | 001 | 0d | 0d | d0 | 010 | 0d | 1d | d1 | 001 |
| C | 010 | 010 | 0d | d0 | 0d | 011 | 0d | d0 | 1d | 010 |
| D | 011 | 011 | 0d | d0 | d0 | 100 | 1d | d1 | d1 | 011 |
| E | 100 | 100 | d0 | 0d | 0d | 101 | d0 | 0d | 1d | 100 |
| F | 101 | 101 | d0 | 0d | d0 | 110 | d0 | 1d | d1 | 101 |
| G | 110 | 110 | d0 | d0 | 0d | 111 | d0 | d0 | 1d | 110 |
| H | 111 | 111 | d0 | d0 | d0 | 000 | d1 | d1 | d1 | 111 |

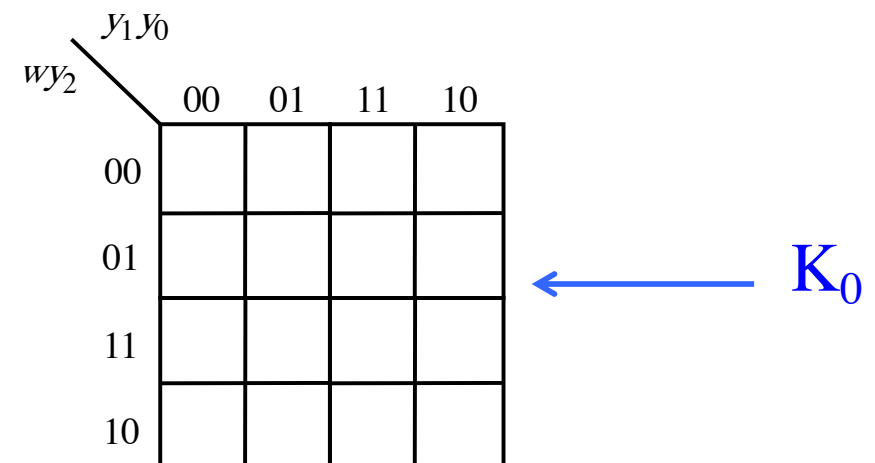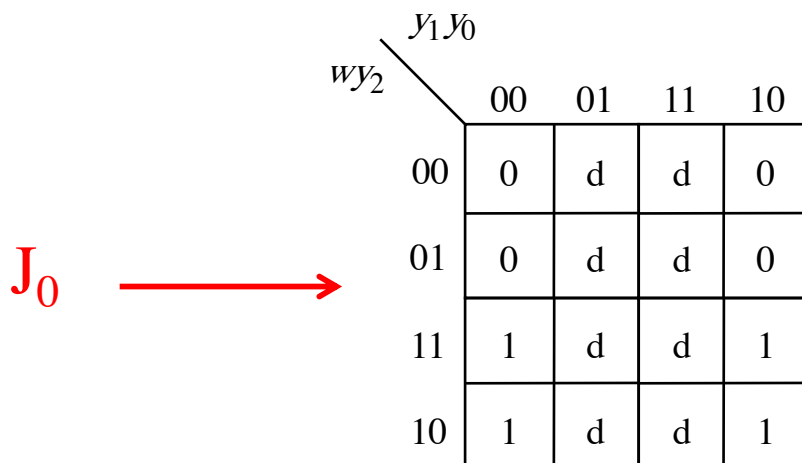



Karnaugh maps for the first JK flip-flop

| | Present state $y_2y_1y_0$ | Flip-flop inputs | | | | | | | Count $z_2z_1z_0$ | |
|---|------------------------------|------------------|----------|----------|----------|-------------|----------|----------|----------------------|----------|
| | | $w = 0$ | | | | $w = 1$ | | | | |
| | | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | | J_0K_0 |
| A | 000 | 000 | 0d | 0d | 0d | 001 | 0d | 0d | 1d | 000 |
| B | 001 | 001 | 0d | 0d | d0 | 010 | 0d | 1d | d1 | 001 |
| C | 010 | 010 | 0d | d0 | 0d | 011 | 0d | d0 | 1d | 010 |
| D | 011 | 011 | 0d | d0 | d0 | 100 | 1d | d1 | d1 | 011 |
| E | 100 | 100 | d0 | 0d | 0d | 101 | d0 | 0d | 1d | 100 |
| F | 101 | 101 | d0 | 0d | d0 | 110 | d0 | 1d | d1 | 101 |
| G | 110 | 110 | d0 | d0 | 0d | 111 | d0 | d0 | 1d | 110 |
| H | 111 | 111 | d0 | d0 | d0 | 000 | d1 | d1 | d1 | 111 |

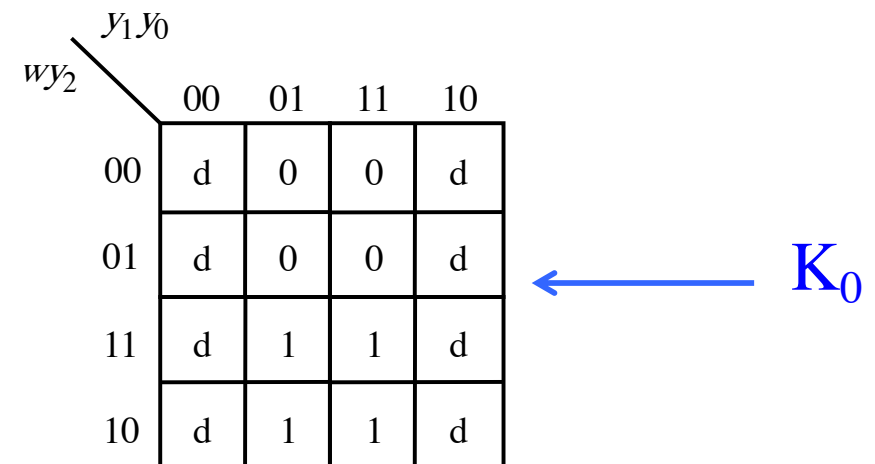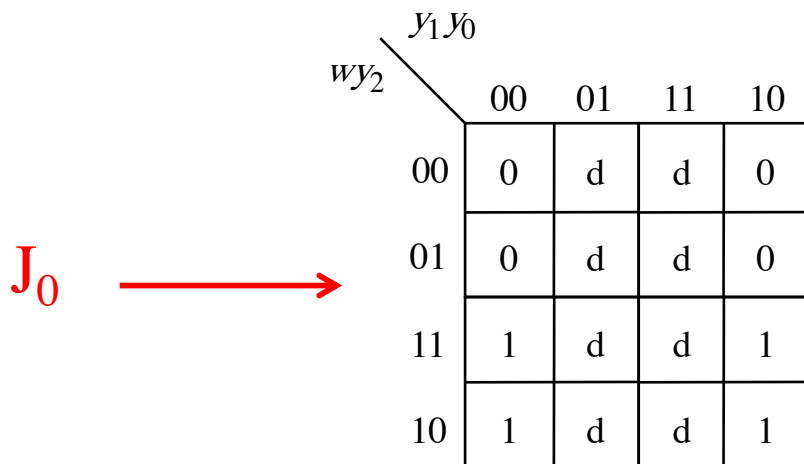



Karnaugh maps for the first JK flip-flop

| | Present state $y_2y_1y_0$ | Flip-flop inputs | | | | | | | | Count $z_2z_1z_0$ |
|---|------------------------------|------------------|----------|----------|----------|-------------|----------|----------|----------|----------------------|
| | | $w = 0$ | | | | $w = 1$ | | | | |
| | | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | |
| A | 000 | 000 | 0d | 0d | 0d | 001 | 0d | 0d | 1d | 000 |
| B | 001 | 001 | 0d | 0d | d0 | 010 | 0d | 1d | d1 | 001 |
| C | 010 | 010 | 0d | d0 | 0d | 011 | 0d | d0 | 1d | 010 |
| D | 011 | 011 | 0d | d0 | d0 | 100 | 1d | d1 | d1 | 011 |
| E | 100 | 100 | d0 | 0d | 0d | 101 | d0 | 0d | 1d | 100 |
| F | 101 | 101 | d0 | 0d | d0 | 110 | d0 | 1d | d1 | 101 |
| G | 110 | 110 | d0 | d0 | 0d | 111 | d0 | d0 | 1d | 110 |
| H | 111 | 111 | d0 | d0 | d0 | 000 | d1 | d1 | d1 | 111 |

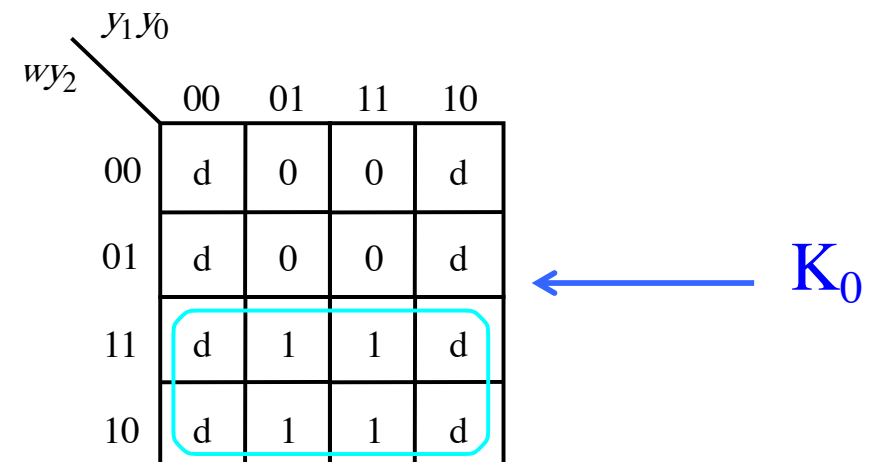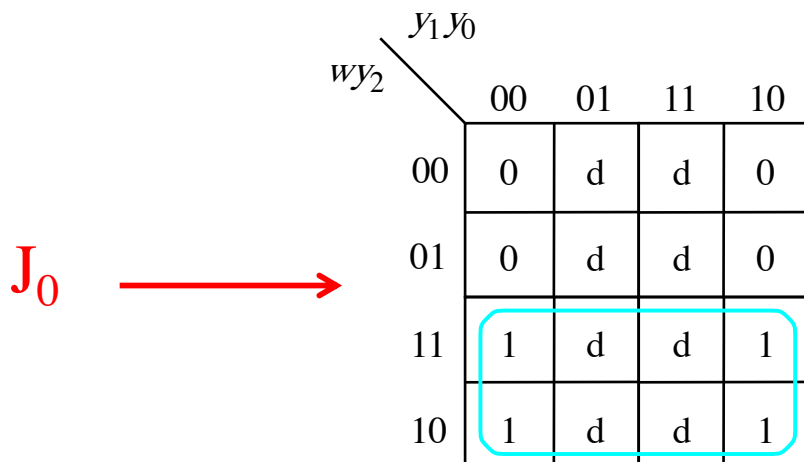


Karnaugh maps for the first JK flip-flop

| | Present state $y_2y_1y_0$ | Flip-flop inputs | | | | | | Count $z_2z_1z_0$ | | |
|---|------------------------------|------------------|----------|----------|----------|-------------|----------|----------------------|----------|----------|
| | | $w = 0$ | | | $w = 1$ | | | | | |
| | | $Y_2Y_1Y_0$ | J_2K_2 | J_1K_1 | J_0K_0 | $Y_2Y_1Y_0$ | J_2K_2 | | J_1K_1 | J_0K_0 |
| A | 000 | 000 | 0d | 0d | 0d | 001 | 0d | 0d | 1d | 000 |
| B | 001 | 001 | 0d | 0d | d0 | 010 | 0d | 1d | d1 | 001 |
| C | 010 | 010 | 0d | d0 | 0d | 011 | 0d | d0 | 1d | 010 |
| D | 011 | 011 | 0d | d0 | d0 | 100 | 1d | d1 | d1 | 011 |
| E | 100 | 100 | d0 | 0d | 0d | 101 | d0 | 0d | 1d | 100 |
| F | 101 | 101 | d0 | 0d | d0 | 110 | d0 | 1d | d1 | 101 |
| G | 110 | 110 | d0 | d0 | 0d | 111 | d0 | d0 | 1d | 110 |
| H | 111 | 111 | d0 | d0 | d0 | 000 | d1 | d1 | d1 | 111 |

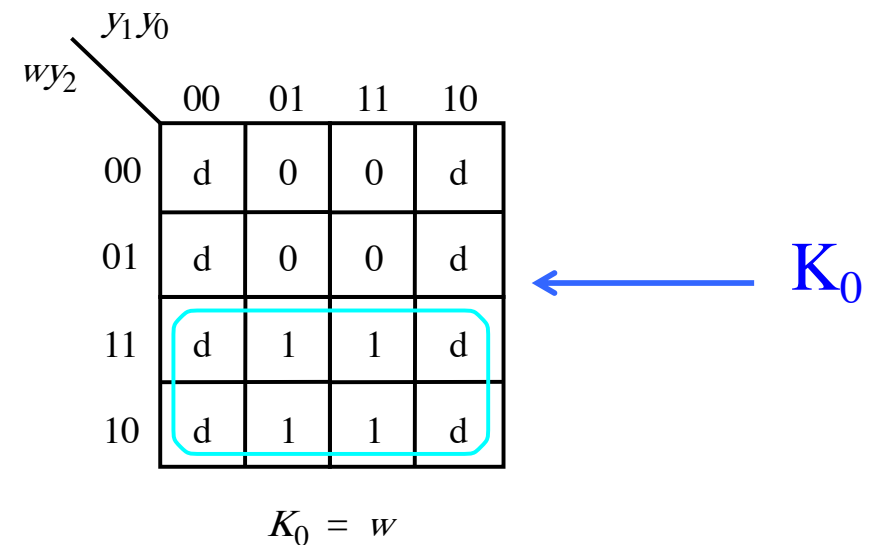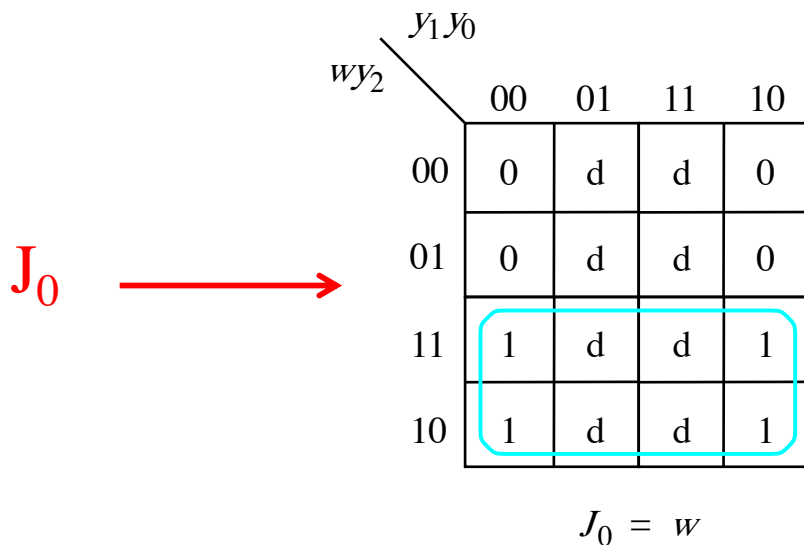


Karnaugh maps for the first JK flip-flop

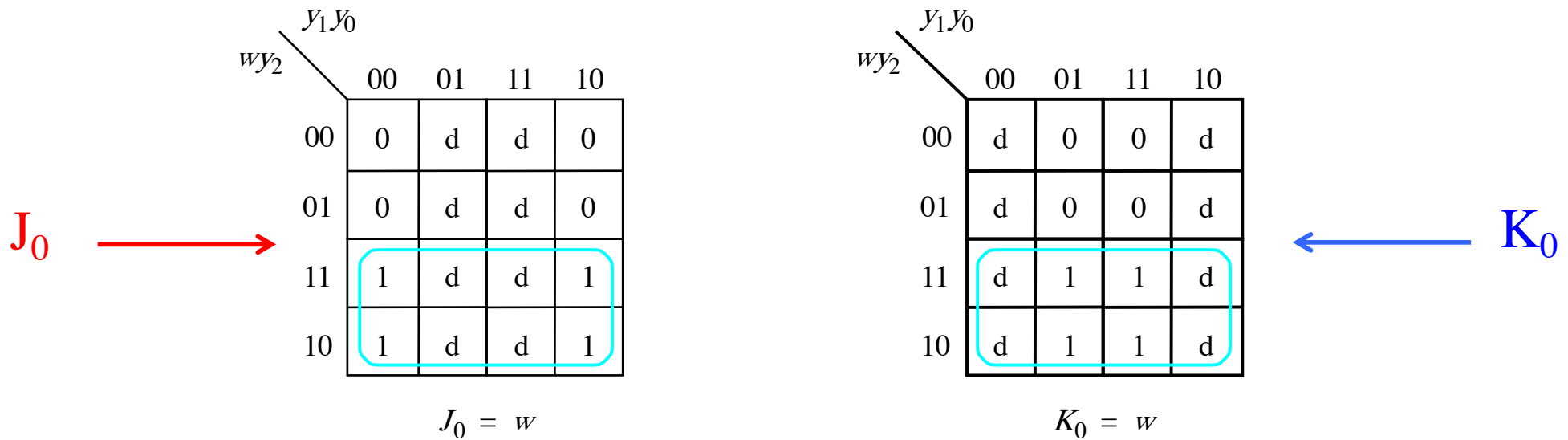


[Figure 6.66 from the textbook]

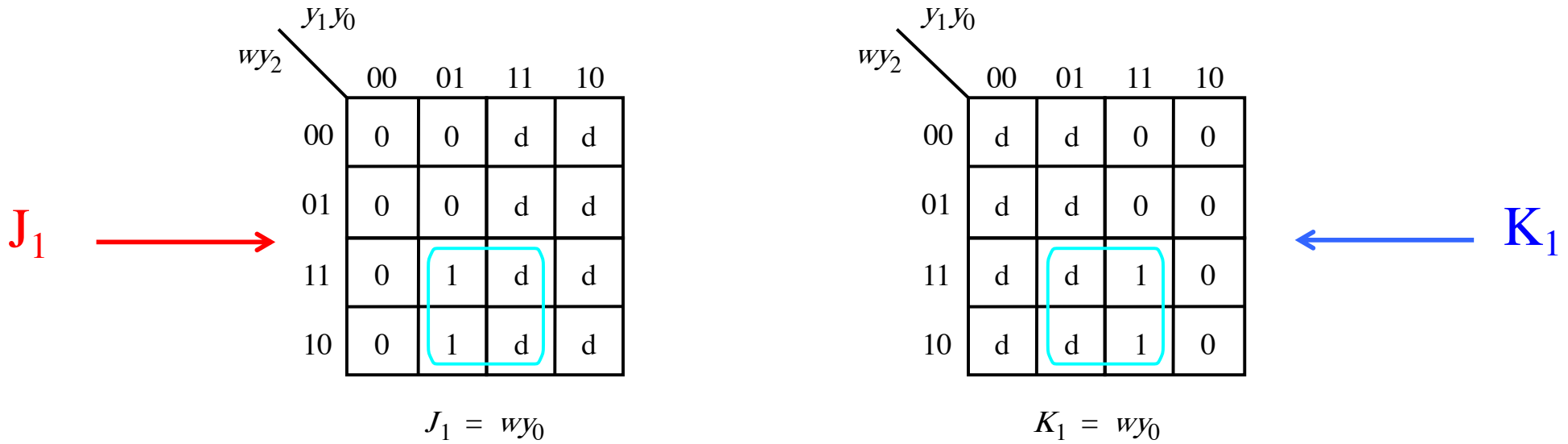Karnaugh maps for the second JK flip-flop



Karnaugh maps for the third JK flip-flop

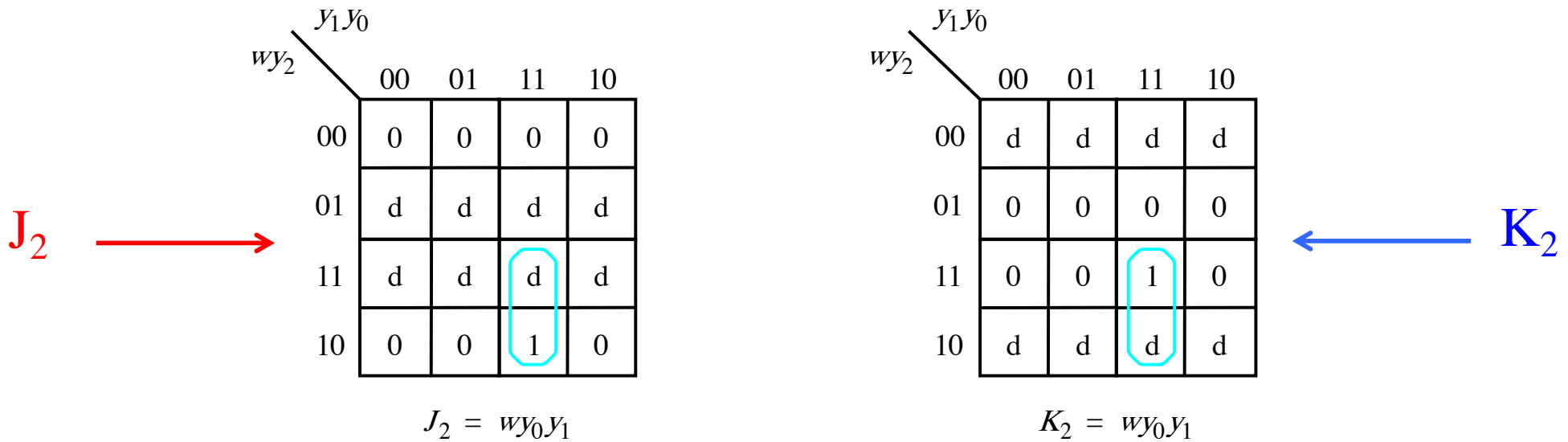

Circuit diagram using JK flip-flops

$$J_0 = w$$


$$K_0 = w$$

$$J_1 = wy_0$$


$$K_1 = wy_0$$

$$J_2 = wy_0y_1$$

$$K_2 = wy_0y_1$$

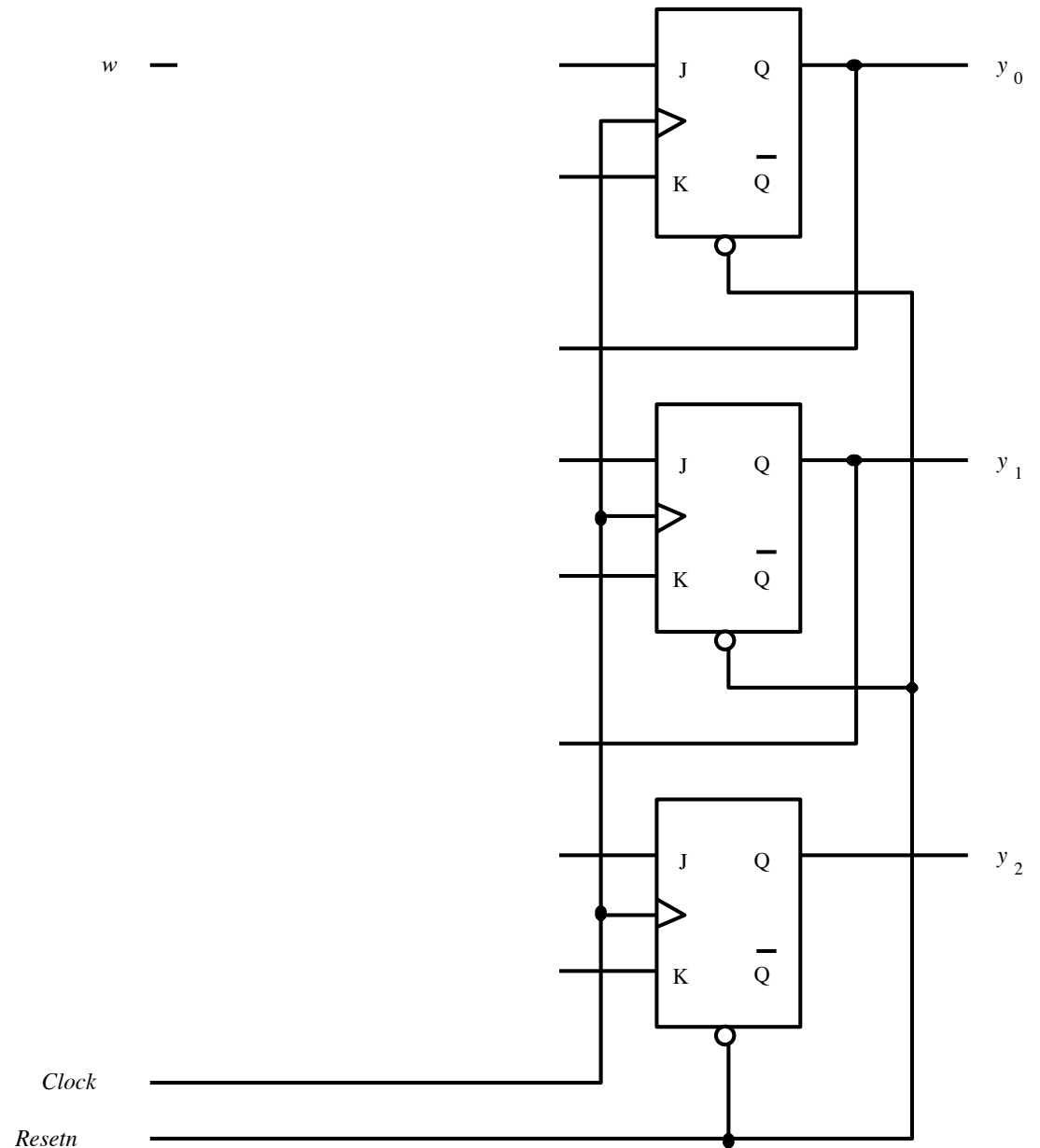

Factored-form implementation of the counter

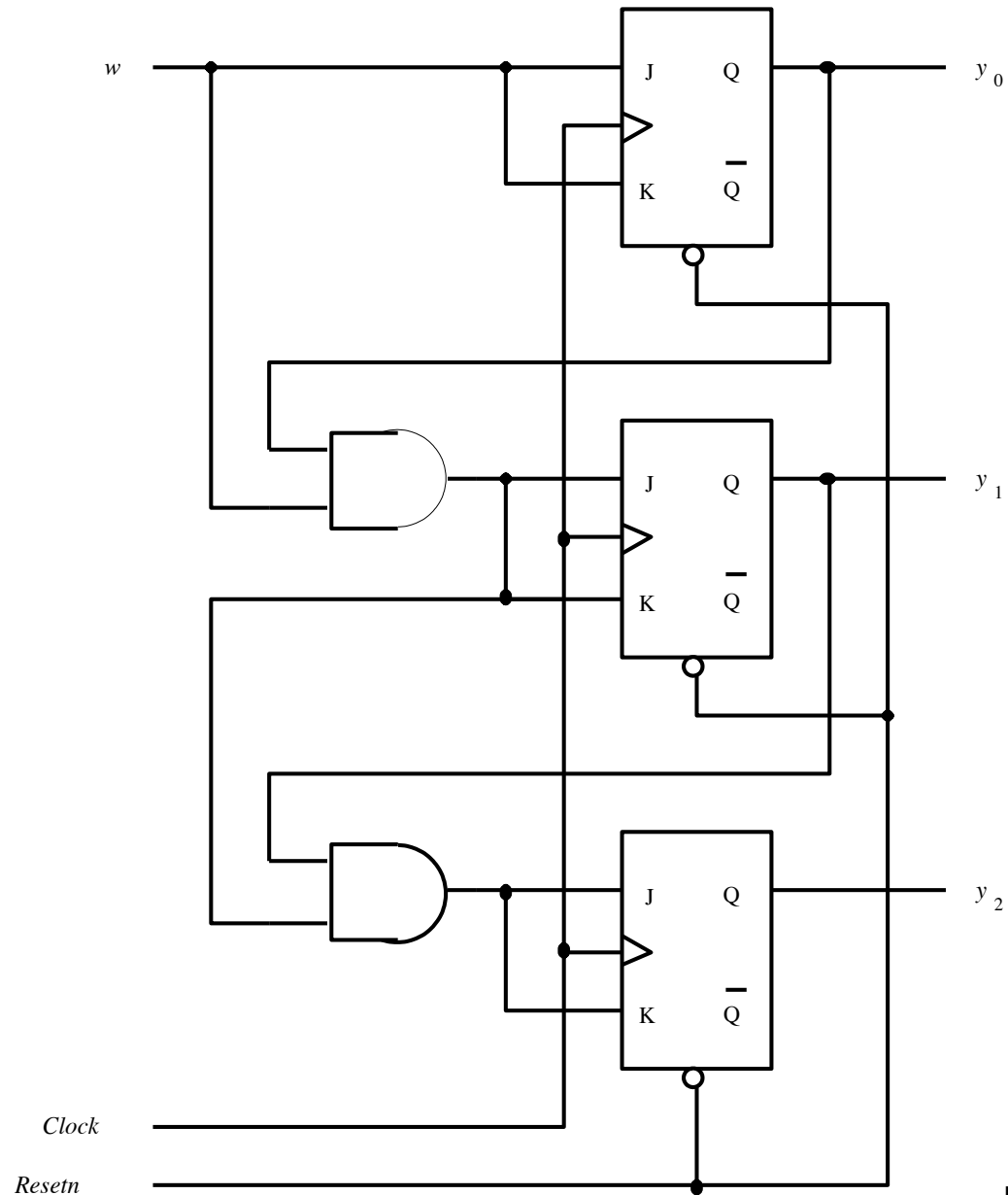

[Figure 6.68 from the textbook]

Another Example (A Different “Counter”)

Goal




- **Implement a 3-bit counter using the sequential circuit approach that counts the pulses on the input line w .**
- **The counter must count in the following sequence:
0, 4, 2, 6, 1, 5, 3, 7, 0, 4, 2, ...**
- **The count must be represented directly by the flip-flop values. No extra gates are allowed.**
- **In other words, count = $Q_2 Q_1 Q_0$**
- **The count changes based on the input signal w :**
 - **If $w=0$, then the count remains the same**
 - **If $w=1$, then the count is advanced by one**

Goal

- Implement a 3-bit counter using the sequential circuit approach that counts the pulses on the input line w .
- The counter must count in the following sequence:
0, 4, 2, 6, 1, 5, 3, 7, 0, 4, 2, ...
- The count must be represented directly by the flip-flop values. No extra gates are allowed.
- In other words, count = $Q_2 Q_1 Q_0$
- The count changes based on the input signal w :
 - If $w=0$, then the count remains the same
 - If $w=1$, then the count is advanced by one

Clock = w

By flipping the order of the bits we get

| | | |
|-----|--|-----|
| 000 |  | 000 |
| 001 |  | 100 |
| 010 | | 010 |
| 011 | | 110 |
| 100 | | 001 |
| 101 | | 101 |
| 110 | | 011 |
| 111 |  | 111 |

By flipping the order of the bits we get

| | | | | |
|---|-----|---|-----|---|
| 0 | 000 | → | 000 | 0 |
| 1 | 001 | → | 100 | 4 |
| 2 | 010 | | 010 | 2 |
| 3 | 011 | | 110 | 6 |
| 4 | 100 | | 001 | 1 |
| 5 | 101 | | 101 | 5 |
| 6 | 110 | | 011 | 3 |
| 7 | 111 | → | 111 | 7 |

State table for the counterlike example

| Present state | Next state | Output $z_2z_1z_0$ |
|---------------|------------|-----------------------|
| A | B | 000 |
| B | C | 100 |
| C | D | 010 |
| D | E | 110 |
| E | F | 001 |
| F | G | 101 |
| G | H | 011 |
| H | A | 111 |

State-assigned table for this example

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

K-maps for Y_2 , Y_1 , and Y_0

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| | | | | | |
|-------|---|----------|----|----|----|
| | | y_1y_0 | | | |
| | | 00 | 01 | 11 | 10 |
| y_2 | 0 | | | | |
| | 1 | | | | |

K-maps for Y_2 , Y_1 , and Y_0

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| | | | | | |
|---|-------|----------|----|----|----|
| | | y_1y_0 | | | |
| | y_2 | 00 | 01 | 11 | 10 |
| 0 | | | | | |
| 1 | | | | | |

Notice that these
are scrambled

K-maps for Y_2 , Y_1 , and Y_0

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | | | | |
| 1 | | | | |

Notice that these
are scrambled

K-map for Y_2

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | | | | |
| 1 | | | | |

K-map for Y_2

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | | | | |
| 1 | | | | |

K-map for Y_2

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |

K-map for Y_2

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |

$$Y_2 = \overline{y_2}$$

K-map for Y_1

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | | | | |
| 1 | | | | |

K-map for Y_1

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | | | | |
| 1 | | | | |

K-map for Y_1

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |

K-map for Y_1

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| | | | | | |
|-------|---|----------|----|----|----|
| | | y_1y_0 | | | |
| | | 00 | 01 | 11 | 10 |
| y_2 | 0 | 0 | 0 | 1 | 1 |
| | 1 | 1 | 1 | 0 | 0 |

$$Y_1 = y_2\bar{y}_1 + \bar{y}_2y_1$$

XOR

K-map for Y_0

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | | | | |
| 1 | | | | |

K-map for Y_0

| Present state $y_2y_1y_0$ | Next state $Y_2Y_1Y_0$ | Output $z_2z_1z_0$ |
|------------------------------|---------------------------|-----------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1y_0$ | 00 | 01 | 11 | 10 |
|-------------------------|----|----|----|----|
| 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |

K-map for Y_0

| Present state $y_2 y_1 y_0$ | Next state $Y_2 Y_1 Y_0$ | Output $z_2 z_1 z_0$ |
|--------------------------------|-----------------------------|-------------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1 y_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |

$$Y_0 = \bar{y}_1 y_0 + \bar{y}_2 y_0 + y_2 y_1 \bar{y}_0$$


K-map for Y_0

| Present state $y_2 y_1 y_0$ | Next state $Y_2 Y_1 Y_0$ | Output $z_2 z_1 z_0$ |
|--------------------------------|-----------------------------|-------------------------|
| 000 | 100 | 000 |
| 100 | 010 | 100 |
| 010 | 110 | 010 |
| 110 | 001 | 110 |
| 001 | 101 | 001 |
| 101 | 011 | 101 |
| 011 | 111 | 011 |
| 111 | 000 | 111 |

| $y_2 \backslash y_1 y_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |

$$\begin{aligned}
 Y_0 &= \bar{y}_1 y_0 + \bar{y}_2 y_0 + y_2 y_1 \bar{y}_0 \\
 &= (\bar{y}_1 + \bar{y}_2) y_0 + y_2 y_1 \bar{y}_0 \\
 &= (\overline{y_1 y_2}) y_0 + (y_2 y_1) \bar{y}_0 \\
 &= (y_1 y_2) \oplus y_0
 \end{aligned}$$

Let's Draw the Circuit for this example

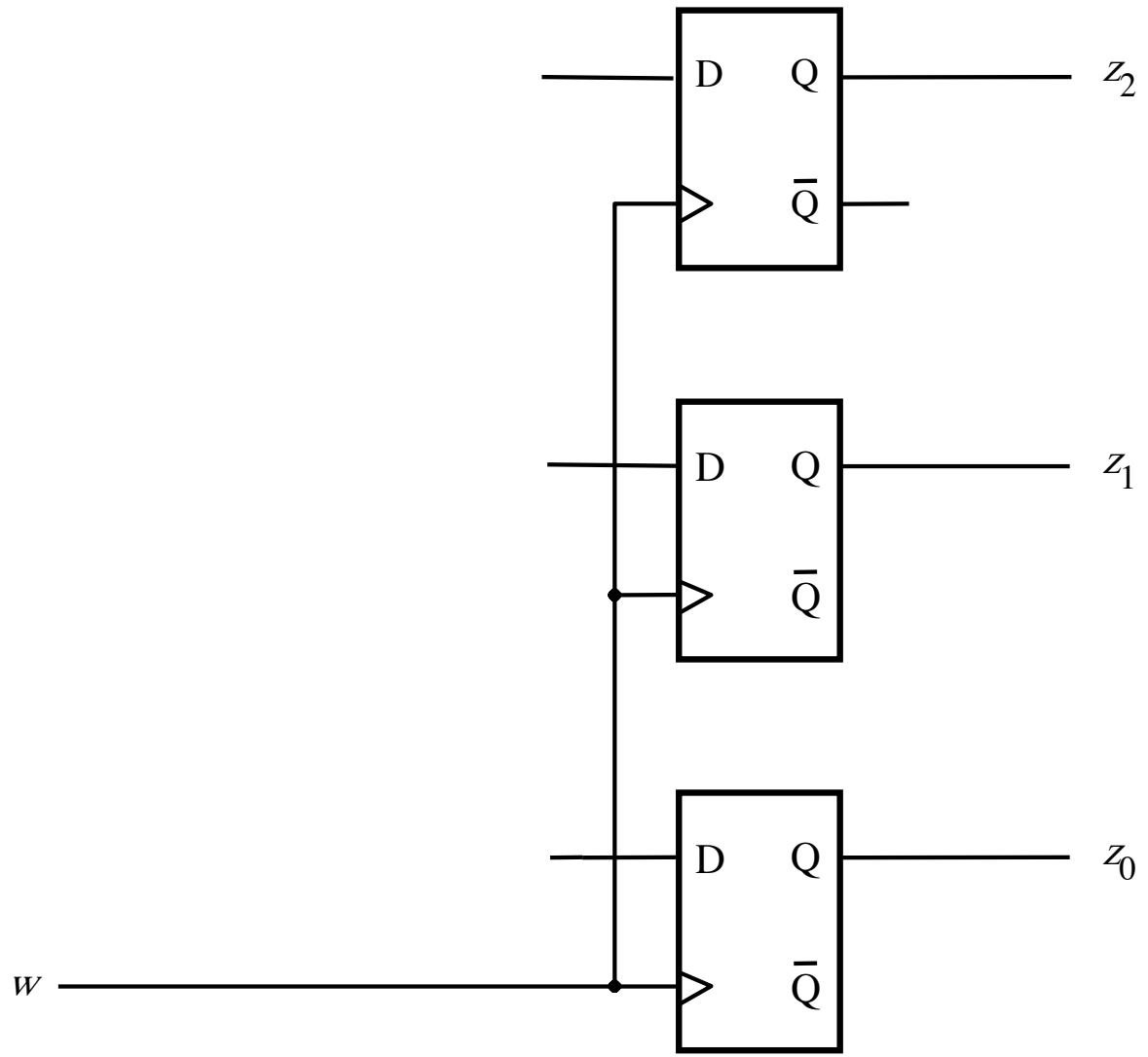


Let's Draw the Circuit for this example

$$Y_2 = \overline{y_2}$$

$$Y_1 = y_1 \oplus y_2$$

$$Y_0 = (y_1 y_2) \oplus y_0$$

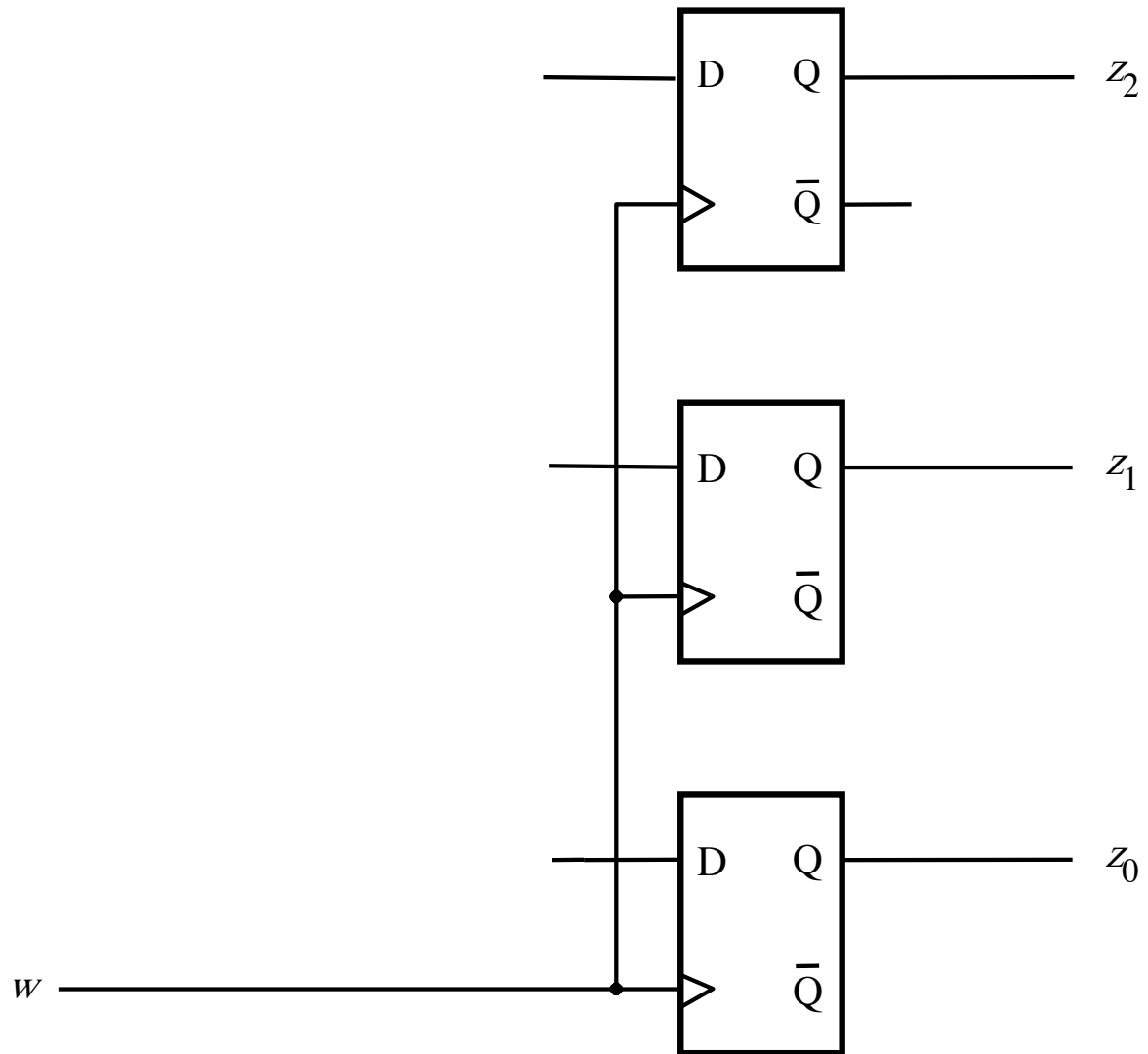


The Circuit for this example

$$Y_2 = \overline{y_2}$$

$$Y_1 = y_1 \oplus y_2$$

$$Y_0 = (y_1 y_2) \oplus y_0$$

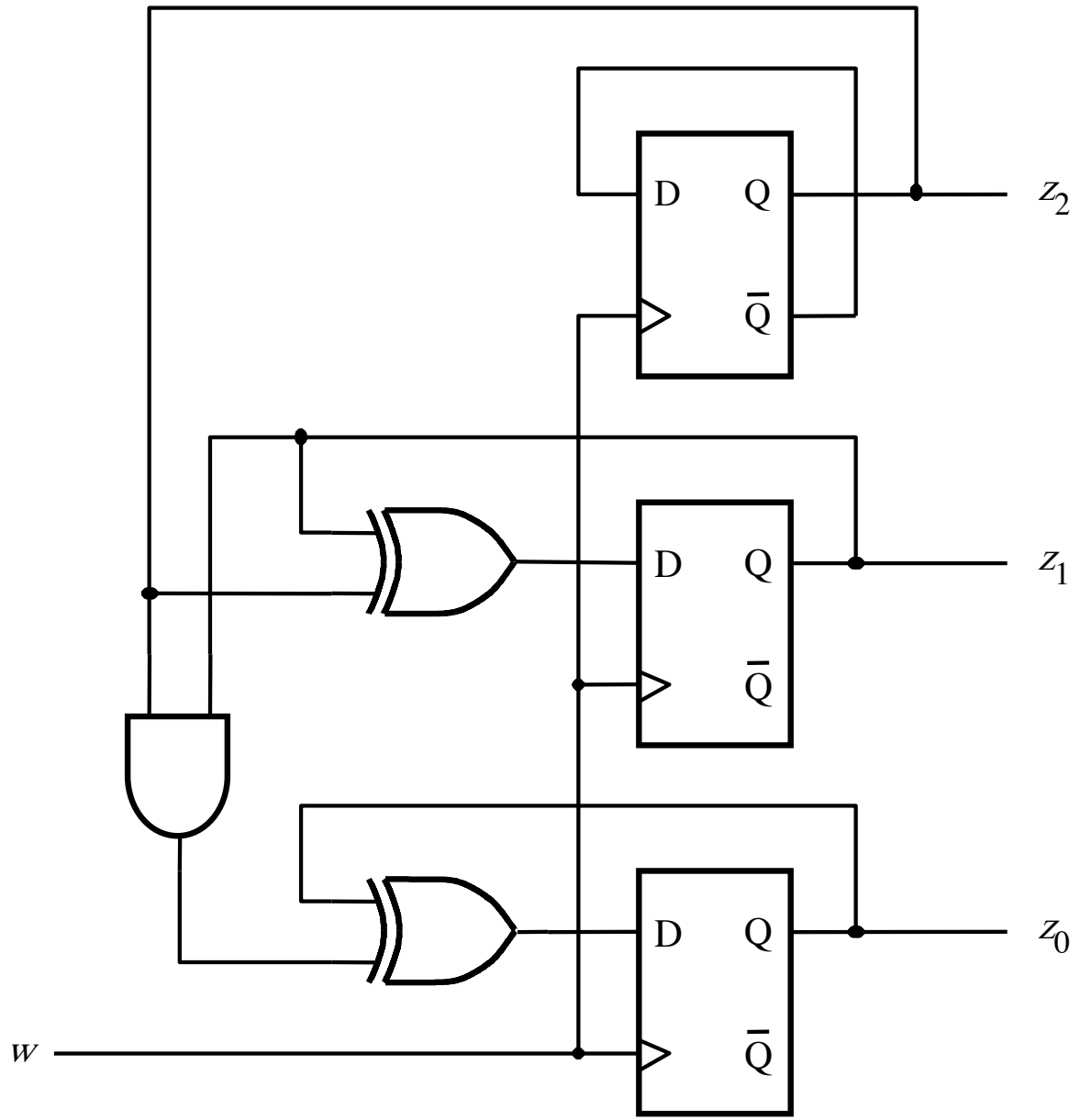

[Figure 6.71 from the textbook]

Questions?

THE END