

**P1 (15 points):** Given a 3-bit input A, 1-bit input P, 1-bit input Q, a 6-bit adder, some 2-to-1 MUXes, some NOT gates, and some XOR gates:


A: Design a circuit that produces a 6-bit integer B such that  $B=3+A$  if  $P=0$  and produces  $B=5-A$  if  $P=1$ .

B: Design a circuit that produces a 6-bit integer C such that  $C=3A$  if  $P=0$  and produces  $C=5A+1$  if  $P=1$ .


C: Design a circuit that outputs 6-bit integer D such that  $D=B$  if  $Q=0$  and  $D=C$  if  $Q=1$ .

**P2 (20 points):** Fill in the timing diagrams below:

A: For a 4-to-2 priority encoder.

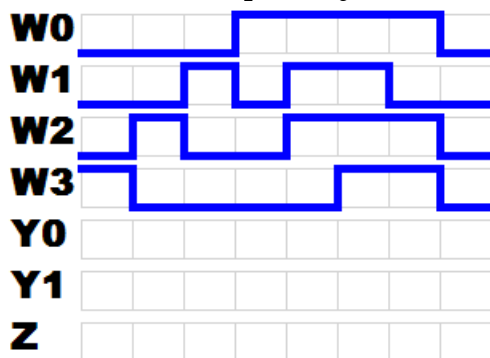


B: For a 4-to-2 binary encoder.

 

C: Which encoder's inputs are contrary to its input assumptions? Why?

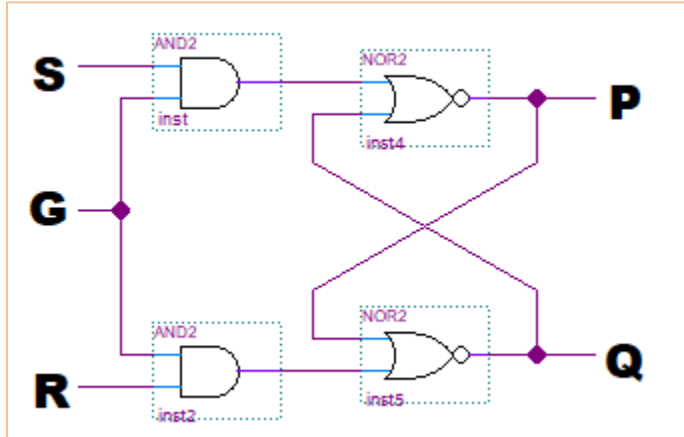
**P3 (10 points):** Consider the SR Latch shown below.




A: Complete the characteristic table.

G	S	R	Q	P
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 B: Complete the timing diagram shown below for outputs Q and P.




 **P4 (10 points):** Answer the following questions based on the circuit shown below.



A: The latch that appears (twice) in the above circuit is a D Latch. Show the characteristic table for a D Latch.

 B: Fill in the timing diagram for the values shown above.




**P5 (10 points):** Show how a D Flip-Flop (DFF) can be made using a T Flip-Flop (TFF). Your circuit must contain all of the functionality of a DFF (PRESET and CLEAR implementations are not necessary), but must use only one TFF and one 2-1 MUX.

**P6 (15 points):** We want to create an LM-latch with the characteristic table shown below:

L	M	Q	P
0	0	0	1
0	1	No change	No change
1	0	No change	No change
1	1	1	0

A: Show the characteristic table for the SR Latch shown below.

S	R	Q	P
0	0		
0	1		
1	0		
1	1		

 

B: For each input combination to the LM-latch characteristic table shown above, write the values of S and R that will produce the output combinations. Then derive expressions for S and R in terms of L and M.  
C: Draw the completed circuit for the LM-latch with the characteristic table based on the expressions derived in part B.

**P7 (20 points):** Answer the following questions about the Negative-Edge-Triggered Master-Slave DFF with PRESET\_N and CLEAR\_N connections, as shown in Figure 5.12 from the book. Suppose that  $D=1$  and  $CLK=0$ . Answer the following questions about Q.

- A: Ignoring PRESET\_N and CLEAR\_N (assume that they are not connected), what effect does pulsing the clock have on Q in this circuit?  
B: What effect does pulsing PRESET\_N have on this circuit?  
C: What effect does pulsing CLEAR\_N have on this circuit?  
D: What will be the value of Q if PRESET\_N=0 and CLEAR\_N=1?  
E: What will be the value of Q if PRESET\_N=0 and CLEAR\_N=0?  
F: What will be the value of Q if the clock is pulsed while PRESET\_N=0?  
G: What will be the value of Q if the clock is pulsed while CLEAR\_N=0?  
H: What will be the value of Q if the clock is pulsed while CLEAR\_N=1 and PRESET\_N=1?