

# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Synthesis

## Using AND, OR, and NOT Gates

# **Administrative Stuff**

- **HW2 is due on Monday Sep 9 @ 4pm**
- **Please write clearly on the first page (in block capital letters) the following three things:**
  - **Your First and Last Name**
  - **Your Student ID Number**
  - **Your Lab Section Letter**
- **If any of these are missing, then you will lose 10%**
  - **Staple all of your pages**
- **If this is not done, then you will lose 10%**

# Administrative Stuff


- **Next week we will start with Lab2**
- **It will be graded!**
- **Print the answer sheet for that lab and do the prelab at home. Otherwise you'll lose 20% of your grade for that lab.**

# Labs Next Week


- **If your lab is on Mondays, i.e.,**
  - **Section 13: Mondays, 12:10 - 3:00 pm**
- **You will have 2 labs in one on September 9.**
- **That is, Lab #1 and Lab #2.**

# **Quick Review**


# The Three Basic Logic Gates

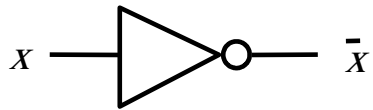

NOT gate

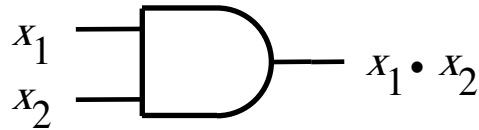


AND gate

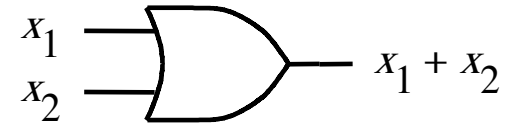

OR gate


# Truth Table for NOT

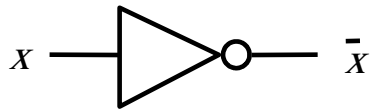

$x$	$\bar{x}$
0	1
1	0




# Truth Table for AND

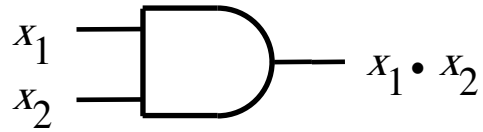

$x_1$	$x_2$	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

# Truth Table for OR

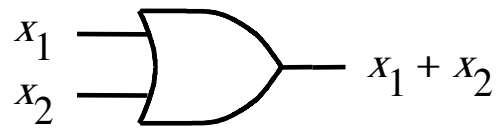

$x_1$	$x_2$	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

# Truth Tables for AND and OR

$x_1$	$x_2$	$x_1$	$x_2$	$x_1 + x_2$
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	1

AND

OR

# Operator Precedence

- **In regular arithmetic and algebra, multiplication takes precedence over addition**
- **This is also true in Boolean algebra**

# Operator Precedence

(three different ways to write the same)

$$x_1 \cdot x_2 + \bar{x}_1 \cdot \bar{x}_2$$

$$(x_1 \cdot x_2) + ((\bar{x}_1) \cdot (\bar{x}_2))$$

$$x_1x_2 + \bar{x}_1\bar{x}_2$$

# Operator Precedence

- Negation of a single variable takes precedence over multiplication of that variable with another variable.

- For example,

$\bar{A} B$  means negate A first and then multiply  $\bar{A}$  by B

# Operator Precedence

- However, a horizontal bar over a product of two variables means that the negation is performed after the product is computed.

- For example,

$\overline{A B}$  means multiply A and B and then negate

# Operator Precedence

- Note that these two expressions are different:

$\overline{A B}$  is not equal to  $\overline{A} \overline{B}$

$\overline{A B}$  means multiply A and B and then negate

$\overline{A} \overline{B}$  means negate A and B separately and then multiply



# Operator Precedence

- Note that these two expressions are different:

$\overline{A B}$  is not equal to  $\overline{A} \overline{B}$

A	B	$\overline{A B}$
0	0	1
0	1	1
1	0	1
1	1	0

A	B	$\overline{A} \overline{B}$
0	0	1
0	1	0
1	0	0
1	1	0

# DeMorgan's Theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

$$15b. \quad \overline{x + y} = \bar{x} \cdot \bar{y}$$

# Function Synthesis

# Synthesize the Following Function

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

# 1) Split the function into a sum of 4 functions

$x_1$	$x_2$	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

# 1) Split the function into a sum of 4 functions

$x_1$	$x_2$	$f(x_1, x_2)$	$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	1	1	0	0	0	1

$$f(x_1, x_2) = 1 \cdot f_{00} + 1 \cdot f_{01} + 0 \cdot f_{10} + 1 \cdot f_{11}$$

## 2) Write the expressions for all four

$x_1$	$x_2$	$f(x_1, x_2)$	$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	1	1	0	0	0	1

$$f(x_1, x_2) = \underbrace{1 \cdot f_{00}} + \underbrace{1 \cdot f_{01}} + \underbrace{0 \cdot f_{10}} + \underbrace{1 \cdot f_{11}}$$

## 2) Write the expressions for all four

$x_1$	$x_2$	$f(x_1, x_2)$	$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	1	1	0	0	0	1

$$f(x_1, x_2) = \underbrace{1 \cdot f_{00}}_{\bar{x}_1 \bar{x}_2} + \underbrace{1 \cdot f_{01}}_{\bar{x}_1 x_2} + \underbrace{0 \cdot f_{10}}_0 + \underbrace{1 \cdot f_{11}}_{x_1 x_2}$$



### 3) Then just add them together

$x_1$	$x_2$	$f(x_1, x_2)$	$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	1	1	0	0	0	1

$$f(x_1, x_2) = \underbrace{1 \cdot f_{00}} + \underbrace{1 \cdot f_{01}} + \underbrace{0 \cdot f_{10}} + \underbrace{1 \cdot f_{11}}$$

$$f(x_1, x_2) = \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2 + 0 + x_1 x_2$$

### 3) Then just add them together

$x_1$	$x_2$	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

$$f(x_1, x_2) = \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + 0 + x_1x_2$$

# A function to be synthesized

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

**Let's look at it row by row.  
How can we express the last row?**

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

**Let's look at it row by row.  
How can we express the last row?**


$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

$x_1x_2$

**Let's look at it row by row.  
How can we express the last row?**

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1


$x_1$   
 $x_2$

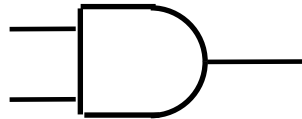

The diagram shows a truth table for a function  $f(x_1, x_2)$ . The last row, where  $x_1=1$  and  $x_2=1$  and  $f=1$ , is highlighted with a green box. To the right of this box is an AND gate symbol with two inputs labeled  $x_1$  and  $x_2$ .

# What about this row?


$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

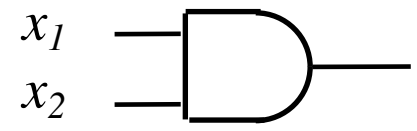

# What about this row?

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1



$\bar{x}_1 x_2$

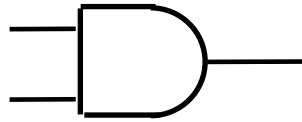$x_1$   
 $x_2$  





# What about this row?

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

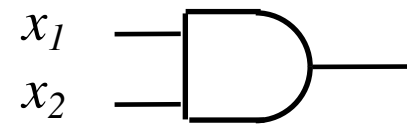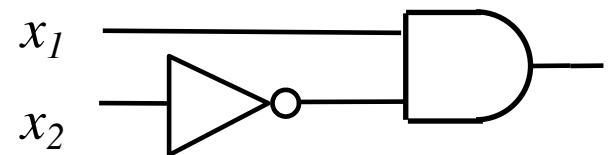

# What about the first row?



$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

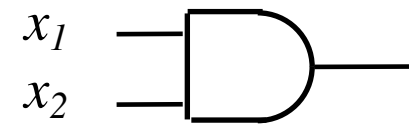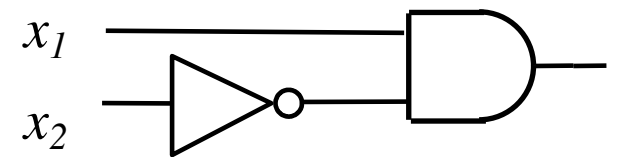




# What about the first row?

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

$$\bar{x}_1 \bar{x}_2$$

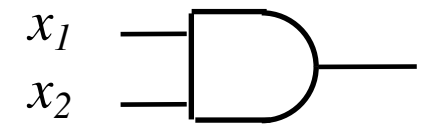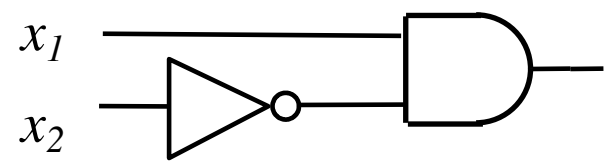

# What about the first row?

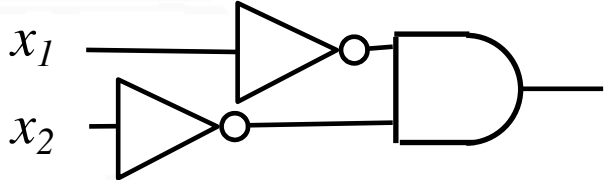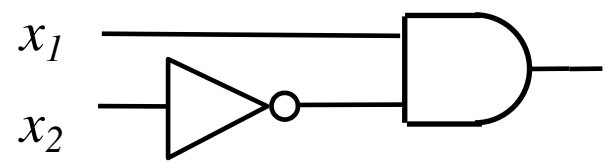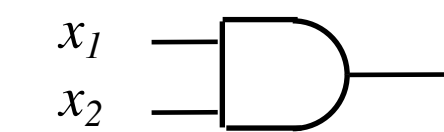$x_1$	$x_2$	$f(x_1, x_2)$	
0	0	1	
0	1	1	
1	0	0	
1	1	1	


# Finally, what about the zero?

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1


Logic diagrams illustrating the implementation of the function  $f(x_1, x_2)$  for each input combination:

- For  $(x_1, x_2) = (0, 0)$ , the output is 1. The diagram shows  $x_1$  and  $x_2$  each passing through an inverter, and the resulting signals being connected to the inputs of an AND gate.
- For  $(x_1, x_2) = (0, 1)$ , the output is 1. The diagram shows  $x_2$  passing through an inverter, and the original  $x_1$  and the inverted  $x_2$  being connected to the inputs of an AND gate.
- For  $(x_1, x_2) = (1, 0)$ , the output is 0. The diagram shows  $x_1$  and  $x_2$  connected directly to the inputs of an AND gate.
- For  $(x_1, x_2) = (1, 1)$ , the output is 1. The diagram shows  $x_1$  and  $x_2$  connected directly to the inputs of an AND gate.


# Putting it all together

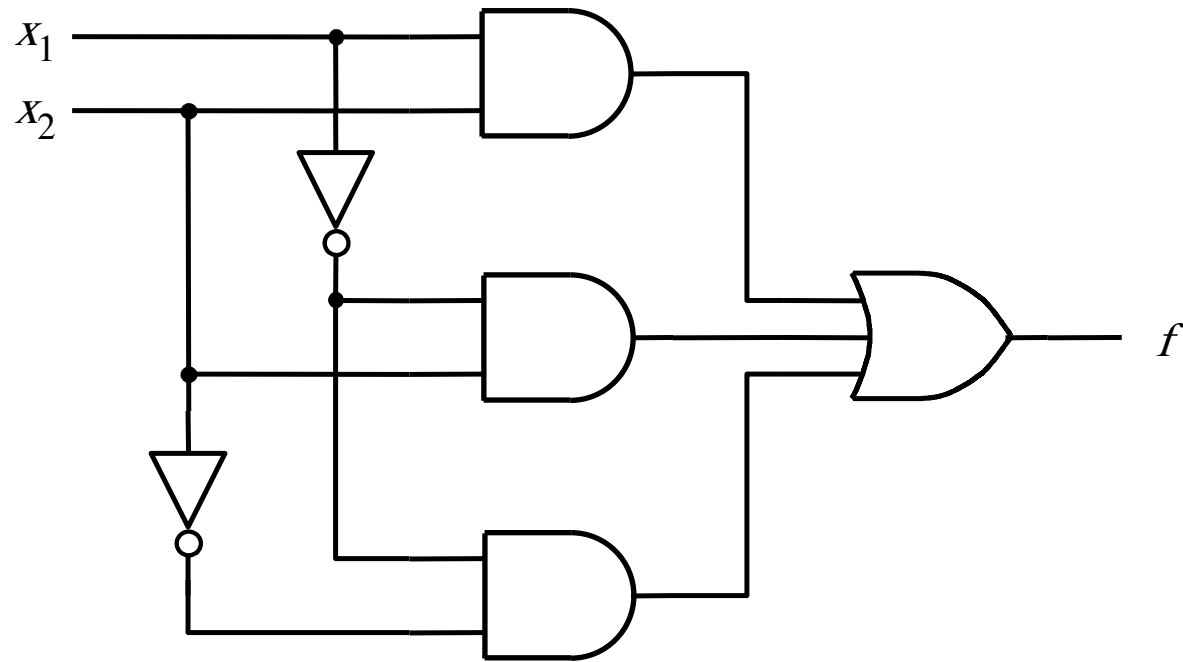

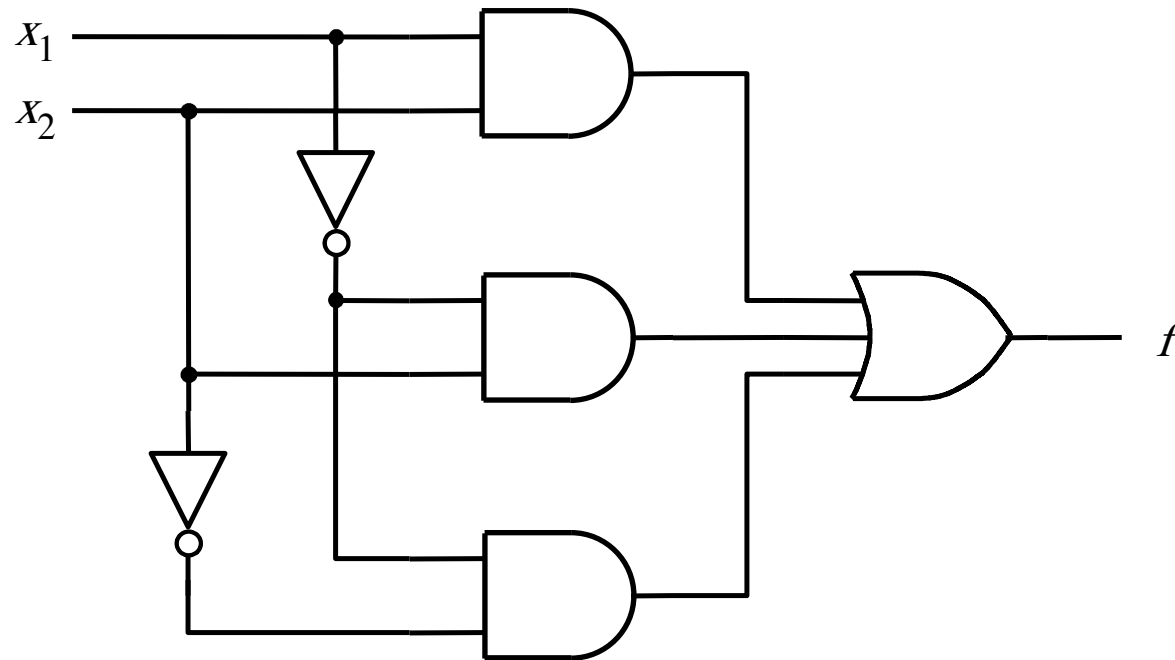**Let's verify that this circuit implements correctly the target truth table**




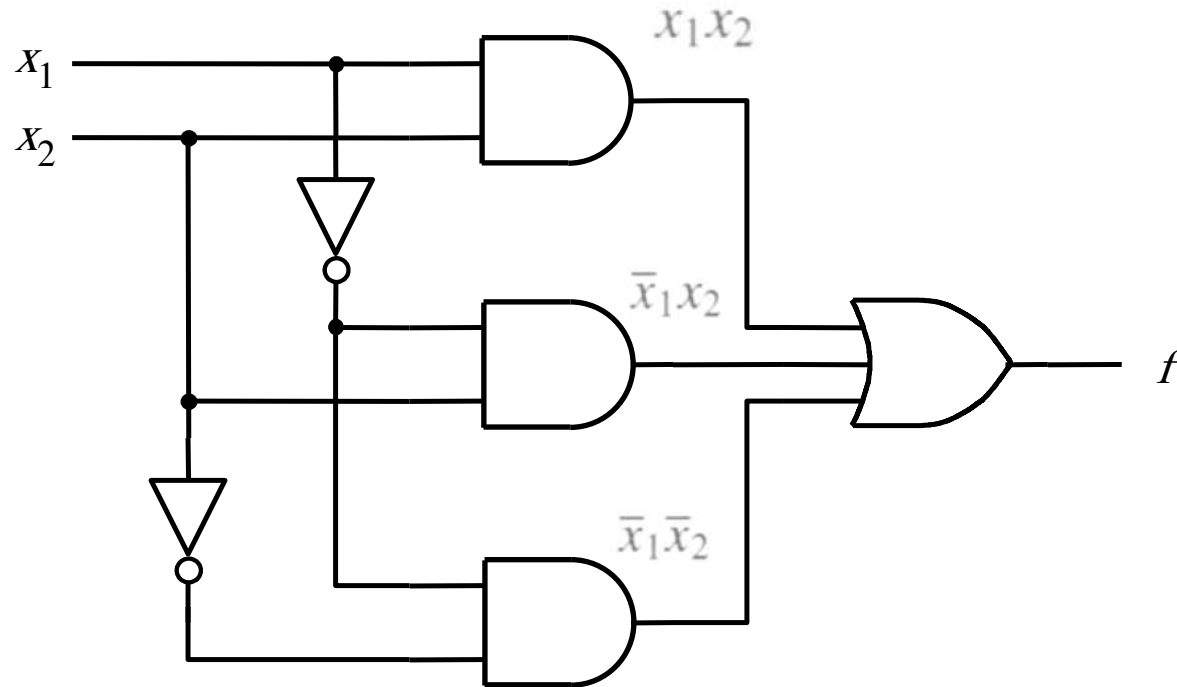**Let's verify that this circuit implements correctly the target truth table**






# Putting it all together

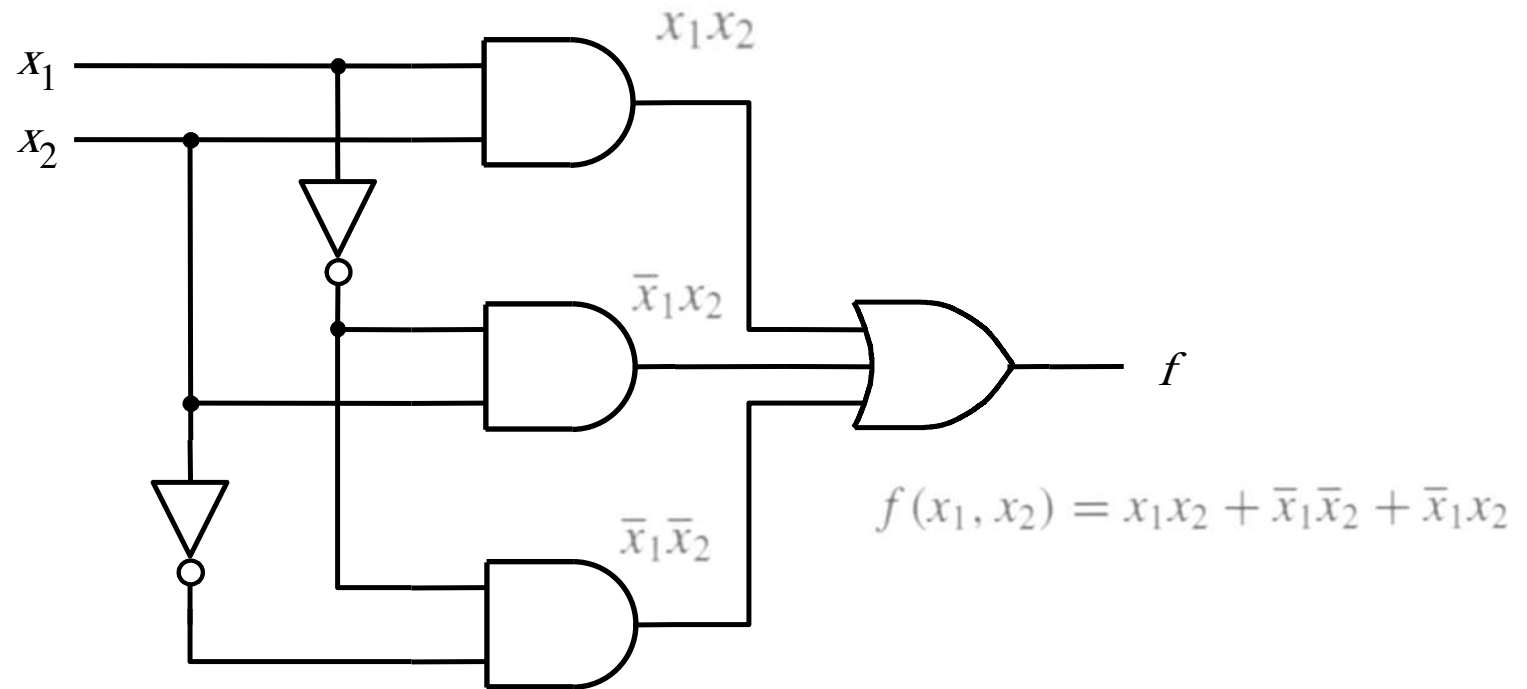

# Canonical Sum-Of-Products (SOP)

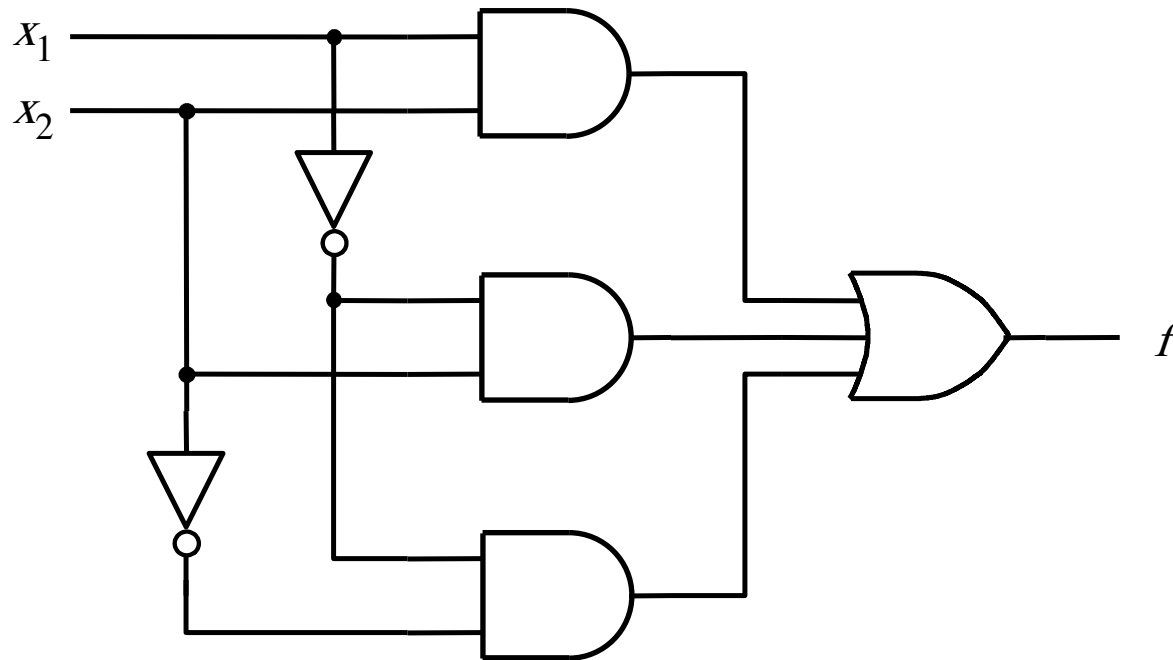


$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$


# Summary of This Procedure

- **Get the truth table of the function**
- **Form a product term (AND gate) for each row of the table for which the function is 1**
- **Each product term contains all input variables**
- **In each row, if  $x_i = 1$  enter it as  $x_i$ , otherwise use  $\overline{x_i}$**
- **Sum all of these products (OR gate) to get the function**
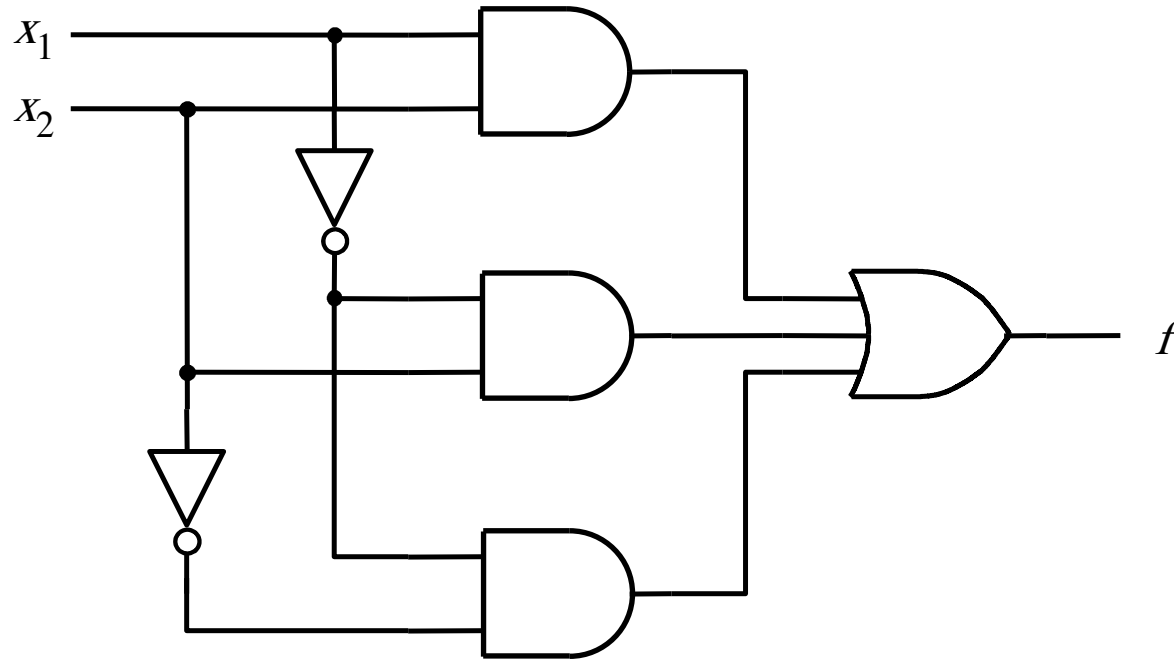
# Two implementations for the same function



(a) Canonical sum-of-products

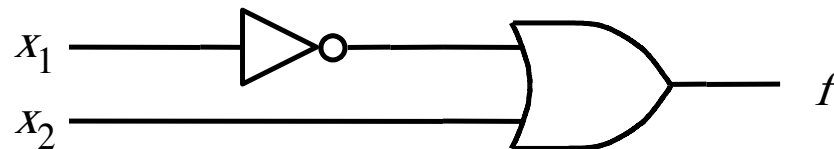

(b) Minimal-cost realization

# Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

# Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$


replicate  
this term

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

# Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

group  
these terms
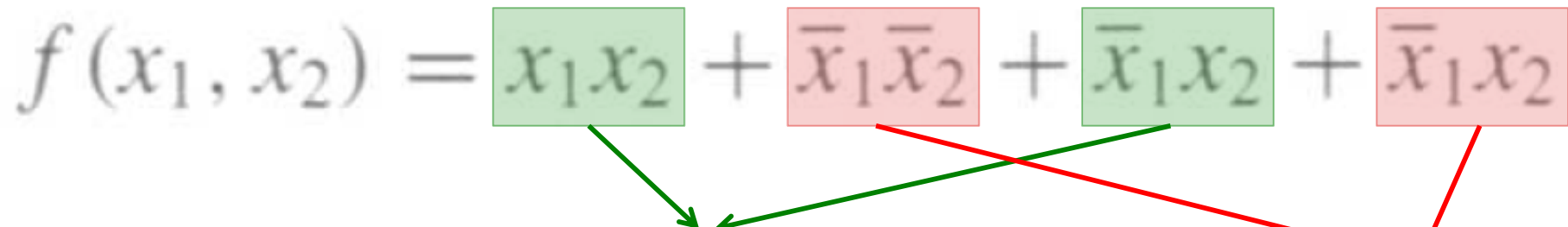
$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$


$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$

# Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

These two terms are trivially equal to 1

$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$

$$f(x_1, x_2) = 1 \cdot x_2 + \bar{x}_1 \cdot 1$$



# Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$


$$f(x_1, x_2) = \boxed{1} \cdot x_2 + \bar{x}_1 \cdot \boxed{1}$$

Drop the 1's


$$f(x_1, x_2) = x_2 + \bar{x}_1$$

# Minimal-cost realization

$$f(x_1, x_2) = x_2 + \bar{x}_1$$

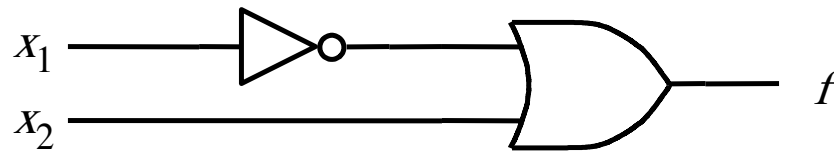

# Let's look at another problem

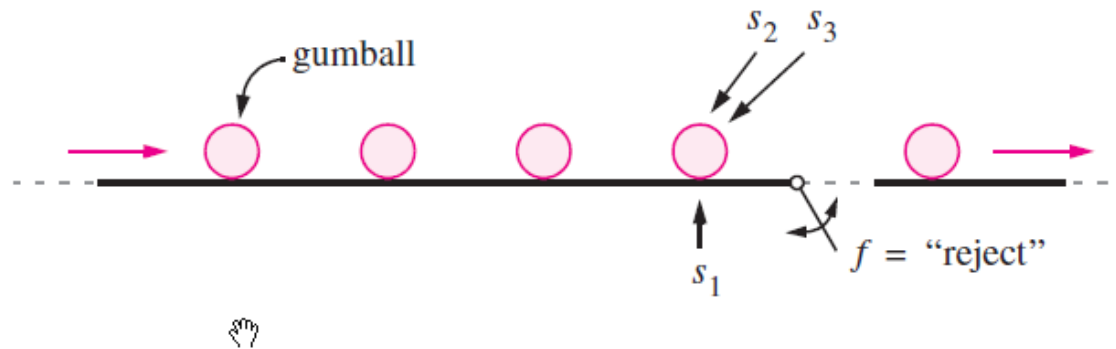

(a) Conveyor and sensors

$s_1$	$s_2$	$s_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(b) Truth table

# Let's look at another problem

$s_1$	$s_2$	$s_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Let's look at another problem

$s_1$	$s_2$	$s_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Let's look at another problem

$s_1$	$s_2$	$s_3$	$f$	
0	0	0	0	
0	0	1	1	$\bar{s}_1 \bar{s}_2 s_3$
0	1	0	0	
0	1	1	1	$\bar{s}_1 s_2 s_3$
1	0	0	0	
1	0	1	1	$s_1 \bar{s}_2 s_3$
1	1	0	1	$s_1 s_2 \bar{s}_3$
1	1	1	1	$s_1 s_2 s_3$

# Let's look at another problem

$s_1$	$s_2$	$s_3$	$f$	
0	0	0	0	
0	0	1	1	$\bar{s}_1\bar{s}_2s_3$
0	1	0	0	
0	1	1	1	$\bar{s}_1s_2s_3$
1	0	0	0	
1	0	1	1	$s_1\bar{s}_2s_3$
1	1	0	1	$s_1s_2\bar{s}_3$
1	1	1	1	$s_1s_2s_3$

$$f = \bar{s}_1\bar{s}_2s_3 + \bar{s}_1s_2s_3 + s_1\bar{s}_2s_3 + s_1s_2\bar{s}_3 + s_1s_2s_3$$


# Let's look at another problem (minimization)

$$\begin{aligned} f &= \bar{s}_1 \bar{s}_2 s_3 + \bar{s}_1 s_2 s_3 + s_1 \bar{s}_2 s_3 + s_1 s_2 s_3 + s_1 s_2 \bar{s}_3 + s_1 s_2 s_3 \\ &= \bar{s}_1 s_3 (\bar{s}_2 + s_2) + s_1 s_3 (\bar{s}_2 + s_2) + s_1 s_2 (\bar{s}_3 + s_3) \\ &= \bar{s}_1 s_3 + s_1 s_3 + s_1 s_2 \\ &= s_3 + s_1 s_2 \end{aligned}$$


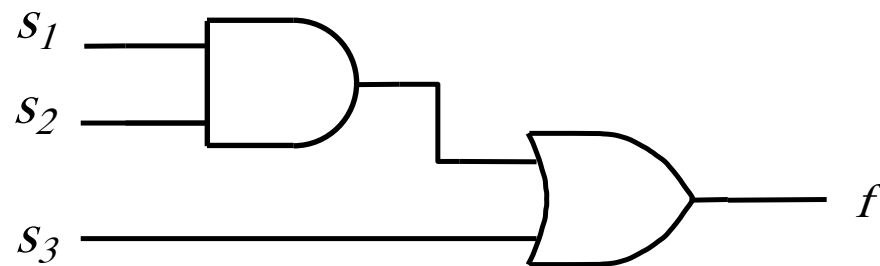
# Let's look at another problem (minimization)

$$\begin{aligned} f &= \bar{s}_1\bar{s}_2s_3 + \bar{s}_1s_2s_3 + s_1\bar{s}_2s_3 + s_1s_2s_3 + s_1s_2\bar{s}_3 + s_1s_2s_3 \\ &= \bar{s}_1s_3(\bar{s}_2 + s_2) + s_1s_3(\bar{s}_2 + s_2) + s_1s_2(\bar{s}_3 + s_3) \\ &= \bar{s}_1s_3 + s_1s_3 + s_1s_2 \\ &= s_3 + s_1s_2 \end{aligned}$$



# Minterms and Maxterms

Row number	$x_1$	$x_2$	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1\bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

# Minterms and Maxterms

Row number	$x_1$	$x_2$	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1\bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

Use these for  
Sum-of-Products  
Minimization  
(1's of the function)

Use these for  
Product-of-Sums  
Minimization  
(0's of the function)

# Sum-of-Products Form

(uses the **ones** of the function)

# Sum-of-Products Form

(for the AND logic function)

Row number	$x_1$	$x_2$	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	0
1	0	1	$m_1 = \bar{x}_1x_2$	0
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

# Sum-of-Products Form

(for the AND logic function)

Row number	$x_1$	$x_2$	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	0
1	0	1	$m_1 = \bar{x}_1x_2$	0
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

# Sum-of-Products Form

(for the AND logic function)

Row number	$x_1$	$x_2$	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1 \bar{x}_2$	0
1	0	1	$m_1 = \bar{x}_1 x_2$	0
2	1	0	$m_2 = x_1 \bar{x}_2$	0
3	1	1	$m_3 = x_1 x_2$	1

$$f(x_1, x_2) = m_3 = x_1 x_2$$

(In this case there is just one product and there is no need for a sum)

# **Another Example**



# Sum-of-Products Form

Row number	$x_1$	$x_2$	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

# Sum-of-Products Form

Row number	$x_1$	$x_2$	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

# Sum-of-Products Form

Row number	$x_1$	$x_2$	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

$$\begin{aligned}f &= m_0 \cdot 1 + m_1 \cdot 1 + m_2 \cdot 0 + m_3 \cdot 1 \\&= m_0 + m_1 + m_3 \\&= \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + x_1x_2\end{aligned}$$

# Product-of-Sums Form

(uses the **zeros** of the function)

# Product-of-Sums Form

## (for the OR logic function)

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

# Product-of-Sums Form (for the OR logic function)

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

# Product-of-Sums Form (for the OR logic function)

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

$$f(x_1, x_2) = M_0 = x_1 + x_2$$

(In this case there is just one sum and there is no need for a product)

# **Another Example**



# Product-of-Sums Form (for this logic function)

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

# Product-of-Sums Form

(for this logic function)

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

# Product-of-Sums Form (for this logic function)

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

$$f(x_1, x_2) = M_0 \cdot M_2 = (x_1 + x_2) \cdot (\bar{x}_1 + x_2)$$

**Yet Another Example**

# Product-of-Sums Form

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

We need to minimize using the zeros of the function  $f$ .  
 But let's first minimize the inverse of  $f$ , i.e.,  $\bar{f}$ .

# Product-of-Sums Form

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x_2}$	1	0
2	1	0	$M_2 = \overline{x_1} + x_2$	0	1
3	1	1	$M_3 = \overline{x_1} + \overline{x_2}$	1	0

# Product-of-Sums Form

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x}_2$	1	0
2	1	0	$M_2 = \overline{x}_1 + x_2$	0	1
3	1	1	$M_3 = \overline{x}_1 + \overline{x}_2$	1	0

$$\begin{aligned}\overline{f}(x_1, x_2) &= m_2 \\ &= x_1 \overline{x}_2\end{aligned}$$

# Product-of-Sums Form

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$	$\bar{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1	0
2	1	0	$M_2 = \bar{x}_1 + x_2$	0	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1	0

$$\begin{aligned} \bar{f} &= f = \overline{x_1 \bar{x}_2} & \bar{f}(x_1, x_2) &= m_2 \\ &= \bar{x}_1 + x_2 & &= x_1 \bar{x}_2 \end{aligned}$$



# Product-of-Sums Form

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$	$\bar{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1	0
2	1	0	$M_2 = \bar{x}_1 + x_2$	0	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1	0

$$\begin{aligned} \bar{f} &= f = \overline{x_1 \bar{x}_2} & \bar{f}(x_1, x_2) &= m_2 \\ &= \bar{x}_1 + x_2 & &= x_1 \bar{x}_2 \end{aligned}$$

$$f = \bar{m}_2 = M_2$$

# Minterms and Maxterms (with three variables)

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

# A three-variable function

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

# Sum-of-Products Form

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

# Sum-of-Products Form

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \bar{x}_1\bar{x}_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3$$

# Sum-of-Products Form

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \bar{x}_1\bar{x}_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3$$

$$\begin{aligned} f &= (\bar{x}_1 + x_1)\bar{x}_2x_3 + x_1(\bar{x}_2 + x_2)\bar{x}_3 \\ &= 1 \cdot \bar{x}_2x_3 + x_1 \cdot 1 \cdot \bar{x}_3 \\ &= \bar{x}_2x_3 + x_1\bar{x}_3 \end{aligned}$$

# A three-variable function

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

# Product-of-Sums Form

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0



# Product-of-Sums Form

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f = \overline{m_0 + m_2 + m_3 + m_7}$$

$$= \overline{m_0} \cdot \overline{m_2} \cdot \overline{m_3} \cdot \overline{m_7}$$

$$= M_0 \cdot M_2 \cdot M_3 \cdot M_7$$

$$= (x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3)$$

# Product-of-Sums Form

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f = ((x_1 + x_3) + x_2)((x_1 + x_3) + \bar{x}_2)(x_1 + (\bar{x}_2 + \bar{x}_3))(\bar{x}_1 + (\bar{x}_2 + \bar{x}_3))$$

$$f = (x_1 + x_3)(\bar{x}_2 + \bar{x}_3)$$

# Shorthand Notation

- **Sum-of-Products**

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

or

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$


- **Product-of-sums**

$$f(x_1, x_2, x_3) = \Pi (M_0, M_2, M_3, M_7)$$


or

$$f(x_1, x_2, x_3) = \Pi M (0, 2, 3, 7)$$

# Two realizations of that function

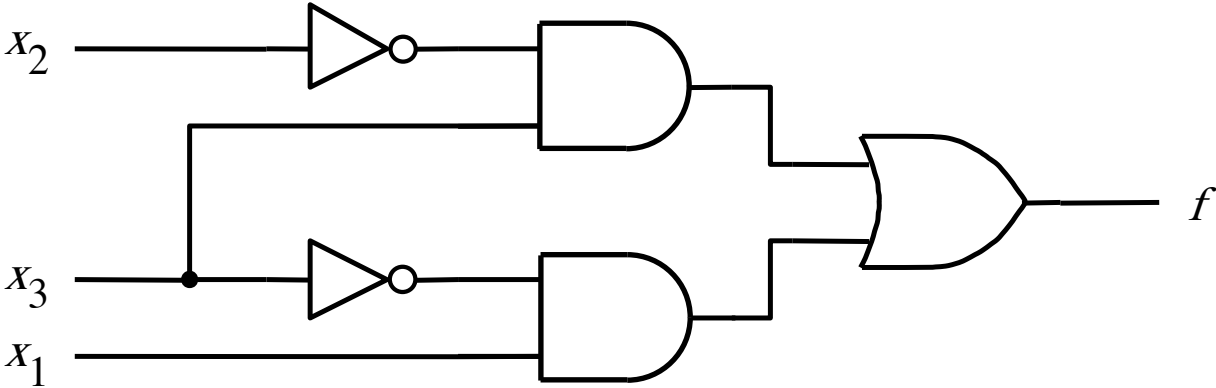

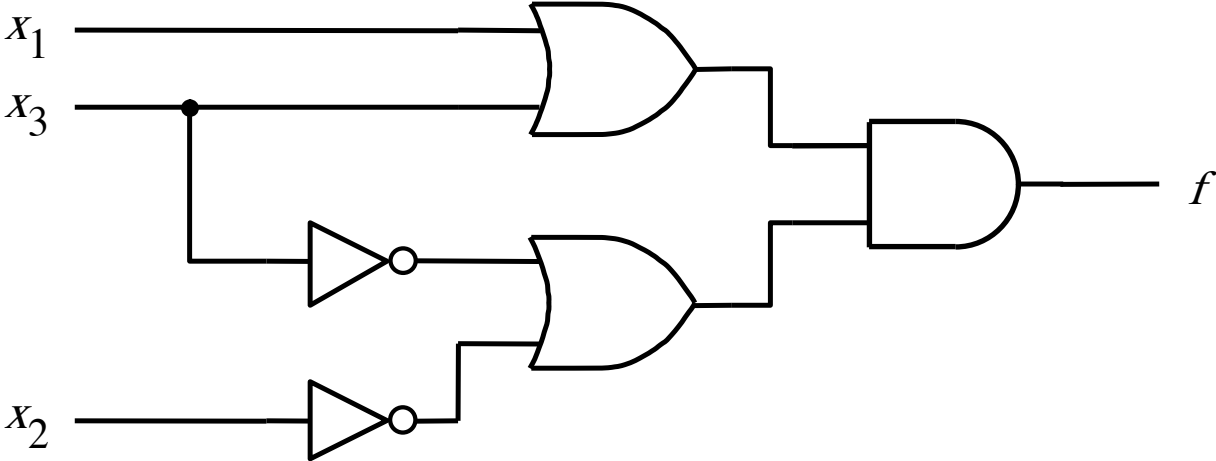(a) A minimal sum-of-products realization




(b) A minimal product-of-sums realization

[ Figure 2.24 from the textbook ]


# The Cost of a Circuit

- **Count all gates**
- **Count all inputs/wires to the gates**

# What is the cost of each circuit?

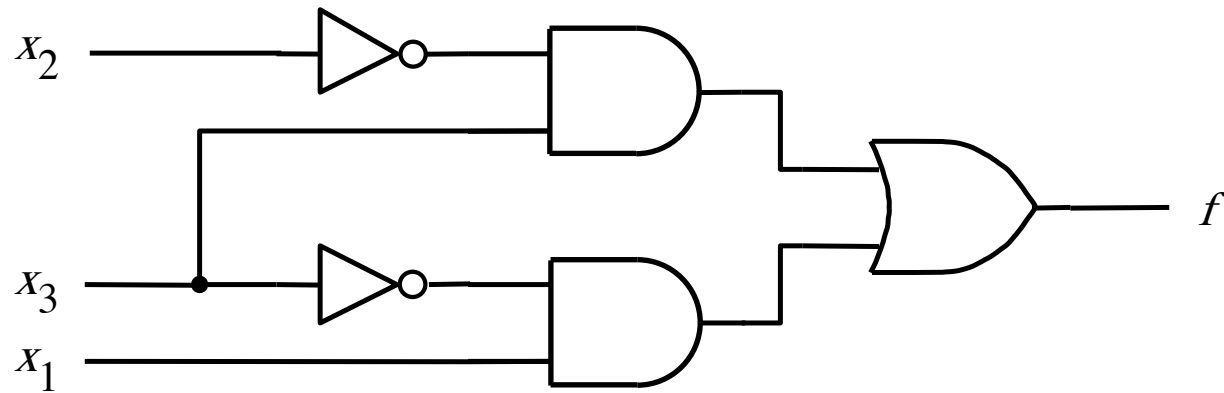

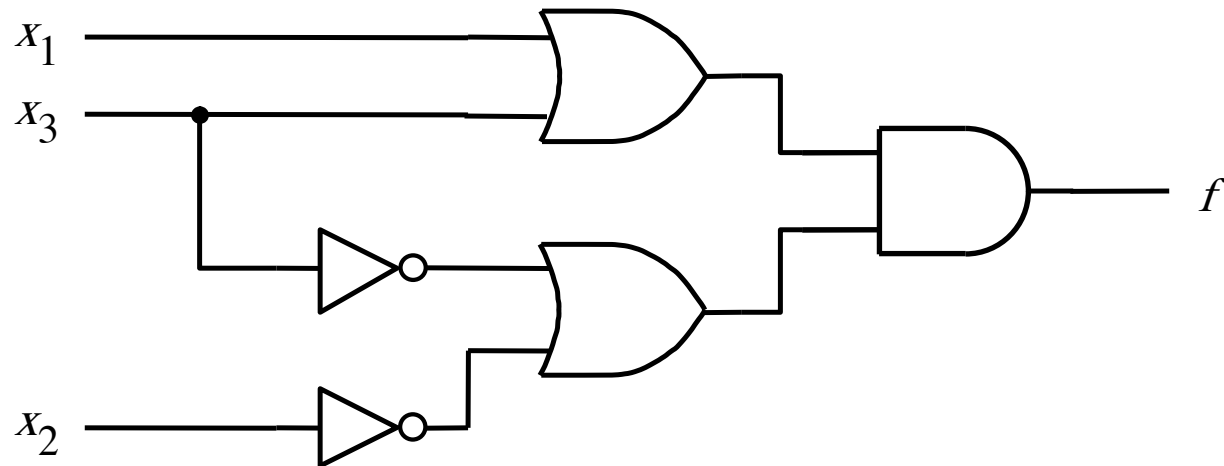
(a) A minimal sum-of-products realization



(b) A minimal product-of-sums realization

[ Figure 2.24 from the textbook ]

# What is the cost of this circuit?

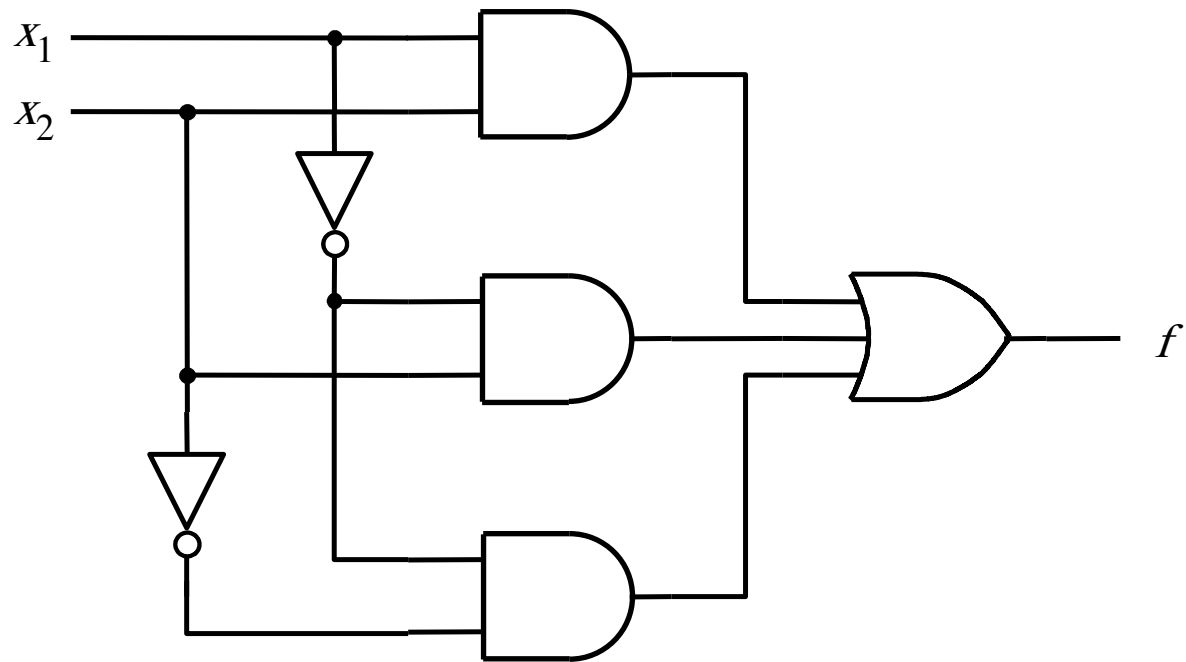

**Questions?**



**THE END**