

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Intro to Verilog

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW3 is due on Monday Sep 16 @ 4p**

Administrative Stuff

- **HW4 is out**
- **It is due on Monday Sep 23 @ 4pm.**
- **Please write clearly on the first page (in BLOCK CAPITAL letters) the following three things:**
 - **Your First and Last Name**
 - **Your Student ID Number**
 - **Your Lab Section Letter**
- **Also, please**
 - **Staple your pages**

Administrative Stuff


- **Midterm Exam #1**
- **When: Friday Sep 27.**
- **Where: This classroom**
- **What: Chapter 1 and Chapter 2 plus number systems**
- **The exam will be closed book but open notes (you can bring up to 3 pages of handwritten notes).**
- **More details to follow.**

Quick Review

2-1 Multiplexer (Definition)

- **Has two inputs: x_1 and x_2**
- **Also has another input line s**
- **If $s=0$, then the output is equal to x_1**
- **If $s=1$, then the output is equal to x_2**

Graphical Symbol for a 2-1 Multiplexer

 

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$	
0 0 0	0	
0 0 1	0	
0 1 0	1	$\bar{s} x_1 \bar{x}_2$
0 1 1	1	$\bar{s} x_1 x_2$
1 0 0	0	
1 0 1	1	$s \bar{x}_1 x_2$
1 1 0	0	
1 1 1	1	$s x_1 x_2$

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$


Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$


$$f(s, x_1, x_2) = \bar{s} x_1 (\bar{x}_2 + x_2) + s (\bar{x}_1 + x_1) x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$

Circuit for 2-1 Multiplexer

 

(b) Circuit

 


(c) Graphical symbol

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$


Analogy: Railroad Switch



Analogy: Railroad Switch

 

Analogy: Railroad Switch

 

This is not a perfect analogy because the trains can go in either direction, while the multiplexer would only allow them to go from top to bottom.

More Compact Truth-Table Representation

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

(a) Truth table


s	$f(s, x_1, x_2)$
0	x_1
1	x_2

4-1 Multiplexer (Definition)

- Has four inputs: w_0 , w_1 , w_2 , w_3
- Also has two select lines: s_1 and s_0
- If $s_1=0$ and $s_0=0$, then the output f is equal to w_0
- If $s_1=0$ and $s_0=1$, then the output f is equal to w_1
- If $s_1=1$ and $s_0=0$, then the output f is equal to w_2
- If $s_1=1$ and $s_0=1$, then the output f is equal to w_3

We'll talk more about this when we get to chapter 4, but here is a quick preview.

Graphical Symbol and Truth Table

 

(a) Graphic symbol


s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

The long-form truth table


$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F
0 0	0 0 0 0	0	0 1	0 0 0 0	0	1 0	0 0 0 0	0	1 1	0 0 0 0	0
	0 0 0 1	1		0 0 0 1	0		0 0 0 1	0		0 0 0 1	0
	0 0 1 0	0		0 0 1 0	1		0 0 1 0	0		0 0 1 0	0
	0 0 1 1	1		0 0 1 1	1		0 0 1 1	0		0 0 1 1	0
	0 1 0 0	0		0 1 0 0	0		0 1 0 0	1		0 1 0 0	0
	0 1 0 1	1		0 1 0 1	0		0 1 0 1	1		0 1 0 1	0
	0 1 1 0	0		0 1 1 0	1		0 1 1 0	1		0 1 1 0	0
	0 1 1 1	1		0 1 1 1	1		0 1 1 1	1		0 1 1 1	0
	1 0 0 0	0		1 0 0 0	0		1 0 0 0	0		1 0 0 0	1
	1 0 0 1	1		1 0 0 1	0		1 0 0 1	0		1 0 0 1	1
	1 0 1 0	0		1 0 1 0	1		1 0 1 0	0		1 0 1 0	1
	1 0 1 1	1		1 0 1 1	1		1 0 1 1	0		1 0 1 1	1
	1 1 0 0	0		1 1 0 0	0		1 1 0 0	1		1 1 0 0	1
	1 1 0 1	1		1 1 0 1	0		1 1 0 1	1		1 1 0 1	1
	1 1 1 0	0		1 1 1 0	1		1 1 1 0	1		1 1 1 0	1
	1 1 1 1	1		1 1 1 1	1		1 1 1 1	1		1 1 1 1	1

4-1 Multiplexer (SOP circuit)



 


[Figure 4.2c from the textbook]



 
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



Analogy: Railroad Switches

  
 


Analogy: Railroad Switches

   


S_1

Analogy: Railroad Switches

  



S_0

 these two
switches are
controlled
together




S_1

  
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 That is different from the SOP form of the 4-1 multiplexer shown below, which uses fewer gates



16-1 Multiplexer

 


[Figure 4.4 from the textbook]



[<http://upload.wikimedia.org/wikipedia/commons/2/26/SunsetTracksCrop.JPG>]

7-Segment Display Example

Display of numbers

 

(a) Logic circuit and 7-segment display

	s_1	s_0	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

(b) Truth table

Display of numbers

	s_1	s_0	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

Display of numbers

	s_1	s_0	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

$$a = \overline{s_0}$$

$$c = \overline{s_1}$$

$$e = \overline{s_0}$$

$$g = s_1 \overline{s_0}$$

$$b = 1$$

$$d = \overline{s_0}$$

$$f = \overline{s_1} \overline{s_0}$$

Intro to Verilog

History


- **Created in 1983/1984**
- **Verilog-95 (IEEE standard 1364-1995)**
- **Verilog 2001 (IEEE Standard 1364-2001)**
- **Verilog 2005 (IEEE Standard 1364-2005)**
- **SystemVerilog**
- **SystemVerilog 2009 (IEEE Standard 1800-2009).**

HDL

- **Hardware Description Language**
- **Verilog HDL**
- **VHDL**

Verilog HDL \neq VHDL

- **These are two different Languages!**
- **Verilog is closer to C**
- **VHDL is closer to Ada**

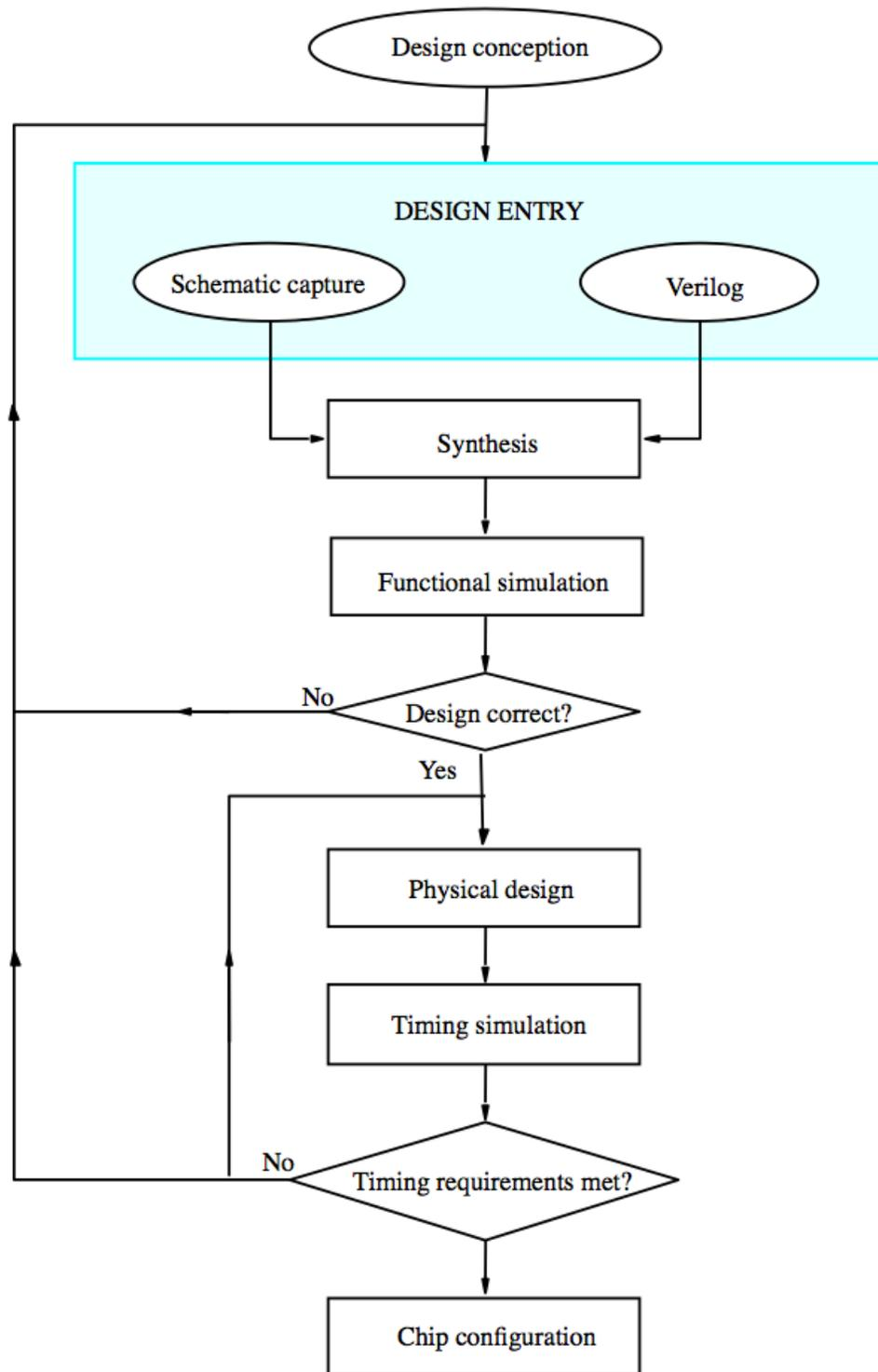


[Figure 2.35 from the textbook]


“Hello World” in Verilog

```
module main;  
  initial  
    begin  
      $display("Hello world!");  
      $finish;  
    end  
endmodule
```


The Three Basic Logic Gates

 

NOT gate

 


AND gate

 

OR gate

You can build any circuit using only these three gates


How to specify a NOT gate in Verilog

 

NOT gate


How to specify a NOT gate in Verilog

we'll use the letter *y* for the output

 

NOT gate

How to specify a NOT gate in Verilog

 


`not (y, x)`

NOT gate

Verilog code

How to specify an AND gate in Verilog

 


AND gate

`and (f, x1, x2)`

Verilog code

How to specify an OR gate in Verilog

 


`or (f, x1, x2)`


OR gate

Verilog code

2-1 Multiplexer

 


Verilog Code for a 2-1 Multiplexer

 


```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

Verilog Code for a 2-1 Multiplexer

 

```
module example3 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  assign f = (~s & x1) | (s & x2);  
  
endmodule
```

Verilog Code for a 2-1 Multiplexer

 

[Figure 2.36 from the textbook]


```
// Behavioral specification
module example5 (x1, x2, s, f);
  input x1, x2, s;
  output f;
  reg f;

  always @(x1 or x2 or s)
    if (s == 0)
      f = x1;
    else
      f = x2;

endmodule
```

[Figure 2.42 from the textbook]

Verilog Code for a 2-1 Multiplexer

 

// Behavioral specification

```
module example5 (input x1, x2, s, output reg f);
```

```
    always @(x1, x2, s)
```

```
        if (s == 0)
```

```
            f = x1;
```


```
        else
```

```
            f = x2;
```

```
endmodule
```


Another Example

Let's Write the Code for This Circuit

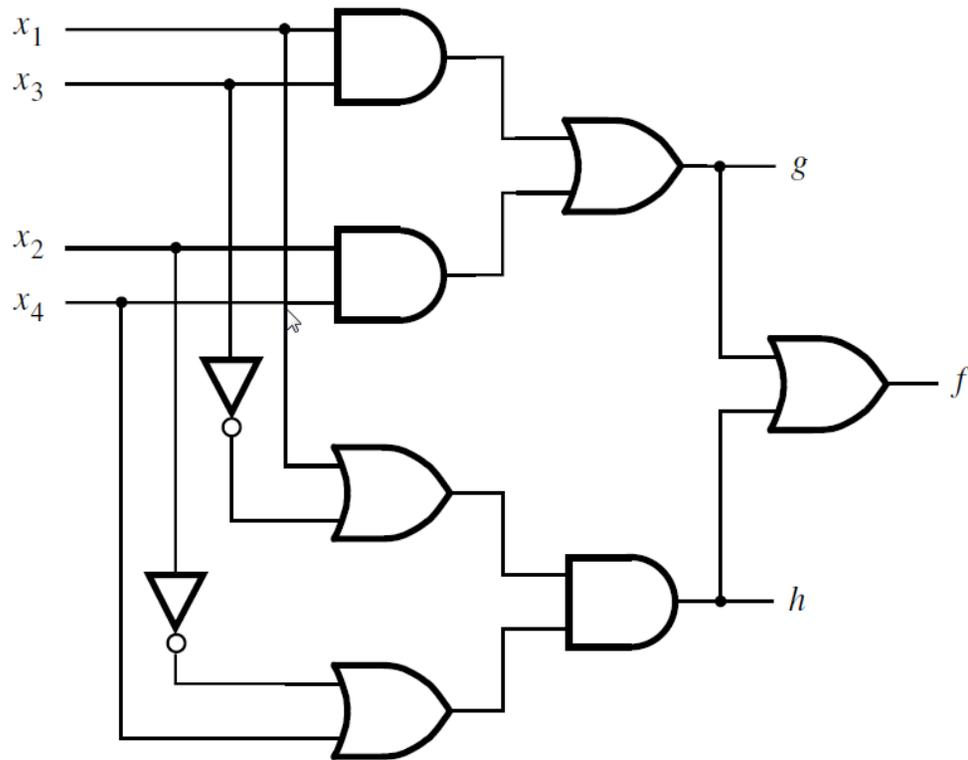

[Figure 2.39 from the textbook]


Let's Write the Code for This Circuit

 

```
module example4 (x1, x2, x3, x4, f, g, h);  
  input x1, x2, x3, x4;  
  output f, g, h;  
  
  assign g = (x1 & x3) | (x2 & x4);  
  assign h = (x1 | ~x3) & (~x2 | x4);  
  assign f = g | h;  
  
endmodule
```

Yet Another Example

A logic circuit with two modules

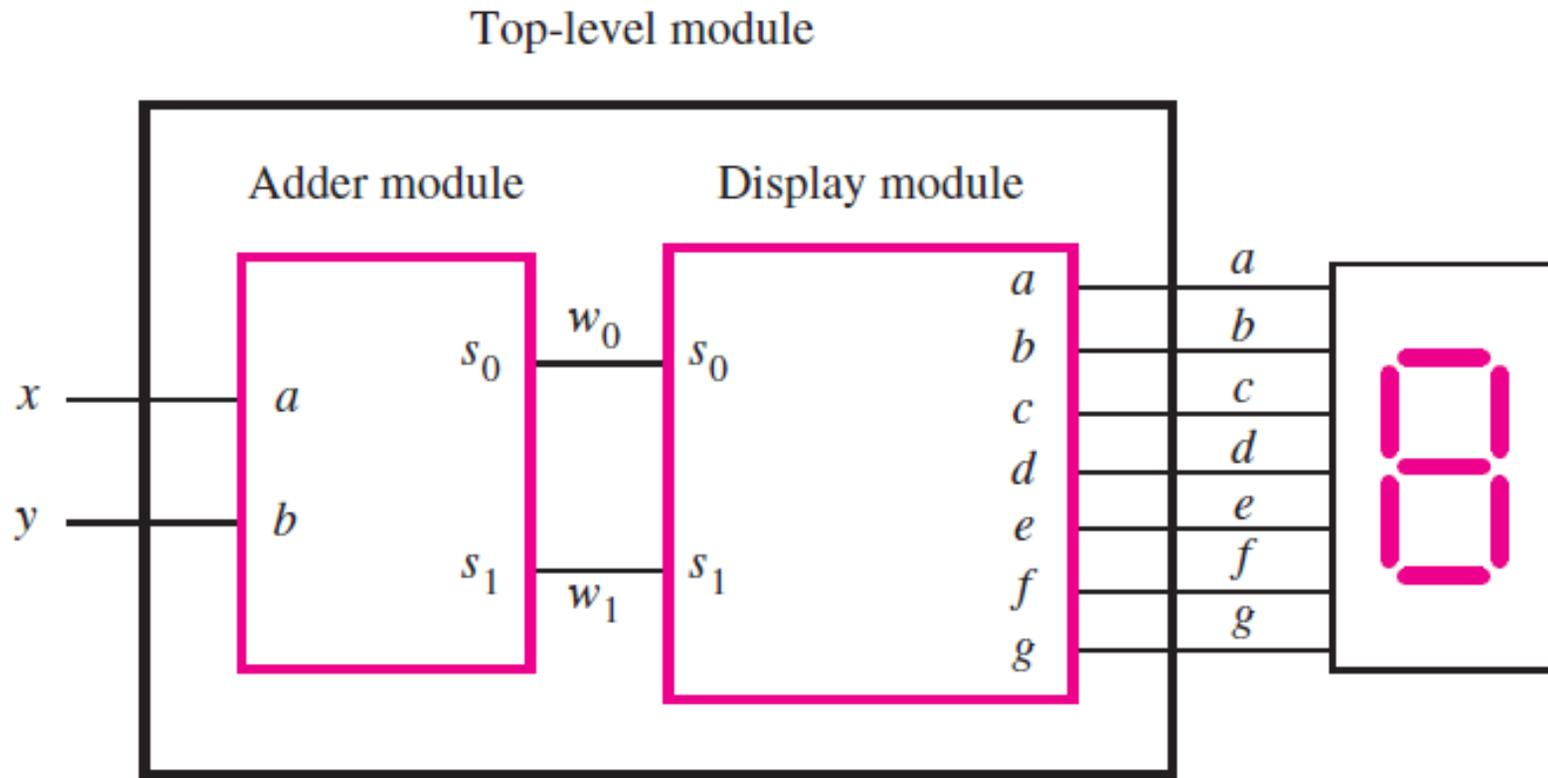


The adder module

a	0	0	1	1
$+b$	$+0$	$+1$	$+0$	$+1$
<hr style="width: 100%;"/>	<hr style="width: 100%;"/>	<hr style="width: 100%;"/>	<hr style="width: 100%;"/>	<hr style="width: 100%;"/>
$s_1 s_0$	0 0	0 1	0 1	1 0

(a) Evaluation of $S = a + b$


a	b	s_1	s_0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

 

(c) Logic network

The adder module

 

```
// An adder module
module adder (a, b, s1, s0);
  input a, b;
  output s1, s0;

  assign s1 = a & b;
  assign s0 = a ^ b;

endmodule
```

The display module

	s_1	s_0	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

$$a = \overline{s_0}$$

$$c = \overline{s_1}$$

$$e = \overline{s_0}$$

$$g = s_1 \overline{s_0}$$

$$b = 1$$

$$d = \overline{s_0}$$

$$f = \overline{s_1} \overline{s_0}$$

The display module

$$a = \overline{s_0}$$

$$b = 1$$

$$c = \overline{s_1}$$

$$d = \overline{s_0}$$

$$e = \overline{s_0}$$

$$f = \overline{s_1} \overline{s_0}$$

$$g = s_1 \overline{s_0}$$

// A module for driving a 7-segment display

```
module display (s1, s0, a, b, c, d, e, f, g);
```

```
  input s1, s0;
```

```
  output a, b, c, d, e, f, g;
```

```
  assign a = ~s0;
```

```
  assign b = 1;
```

```
  assign c = ~s1;
```

```
  assign d = ~s0;
```

```
  assign e = ~s0;
```


```
  assign f = ~s1 & ~s0;
```

```
  assign g = s1 & ~s0;
```

```
endmodule
```

Putting it all together

Top-level module

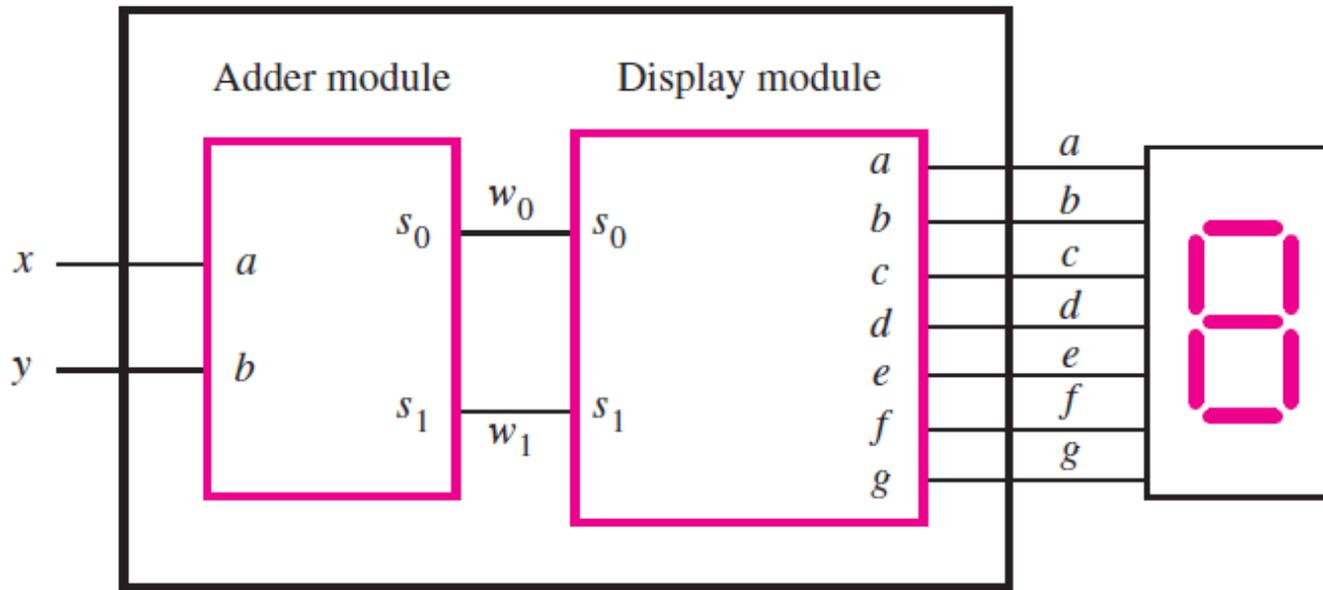

```
// An adder module
module adder (a, b, s1, s0)
  input a, b;
  output s1, s0;

  assign s1 = a & b;
  assign s0 = a ^ b;

endmodule
```

```
// A module for driving a 7-segment display
module display (s1, s0, a, b, c, d, e, f, g);
  input s1, s0;
  output a, b, c, d, e, f, g;

  assign a = ~s0;
  assign b = 1;
  assign c = ~s1;
  assign d = ~s0;
  assign e = ~s0;
  assign f = ~s1 & ~s0;
  assign g = s1 & ~s0;

endmodule
```

```
module adder_display (x, y, a, b, c, d, e, f, g);
  input x, y;
  output a, b, c, d, e, f, g;
  wire w1, w0;

  adder U1 (x, y, w1, w0);
  display U2 (w1, w0, a, b, c, d, e, f, g);

endmodule
```

Questions?

THE END