



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Multiplexers

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW 6 is due on Monday**


Administrative Stuff

- **HW 7 is out**
- **It is due on Monday Oct 21 @ 4pm**

2-1 Multiplexer (Definition)

- **Has two inputs: x_1 and x_2**
- **Also has another input line s**
- **If $s=0$, then the output is equal to x_1**
- **If $s=1$, then the output is equal to x_2**

Graphical Symbol for a 2-1 Multiplexer

 

Truth Table for a 2-1 Multiplexer

| s x_1 x_2 | $f(s, x_1, x_2)$ |
|-----------------|------------------|
| 0 0 0 | 0 |
| 0 0 1 | 0 |
| 0 1 0 | 1 |
| 0 1 1 | 1 |
| 1 0 0 | 0 |
| 1 0 1 | 1 |
| 1 1 0 | 0 |
| 1 1 1 | 1 |

Let's Derive the SOP form

| $s \ x_1 \ x_2$ | $f(s, x_1, x_2)$ |
|-----------------|------------------|
| 0 0 0 | 0 |
| 0 0 1 | 0 |
| 0 1 0 | 1 |
| 0 1 1 | 1 |
| 1 0 0 | 0 |
| 1 0 1 | 1 |
| 1 1 0 | 0 |
| 1 1 1 | 1 |

Let's Derive the SOP form

| $s \ x_1 \ x_2$ | $f(s, x_1, x_2)$ |
|-----------------|------------------|
| 0 0 0 | 0 |
| 0 0 1 | 0 |
| 0 1 0 | 1 |
| 0 1 1 | 1 |
| 1 0 0 | 0 |
| 1 0 1 | 1 |
| 1 1 0 | 0 |
| 1 1 1 | 1 |

Let's Derive the SOP form

| $s \ x_1 \ x_2$ | $f(s, x_1, x_2)$ |
|-----------------|------------------|
| 0 0 0 | 0 |
| 0 0 1 | 0 |
| 0 1 0 | 1 |
| 0 1 1 | 1 |
| 1 0 0 | 0 |
| 1 0 1 | 1 |
| 1 1 0 | 0 |
| 1 1 1 | 1 |

Where should we
put the negation signs?

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

Let's Derive the SOP form

| $s \ x_1 \ x_2$ | $f(s, x_1, x_2)$ | |
|-----------------|------------------|-----------------------------|
| 0 0 0 | 0 | |
| 0 0 1 | 0 | |
| 0 1 0 | 1 | $\bar{s} \ x_1 \ \bar{x}_2$ |
| 0 1 1 | 1 | $\bar{s} \ x_1 \ x_2$ |
| 1 0 0 | 0 | |
| 1 0 1 | 1 | $s \ \bar{x}_1 \ x_2$ |
| 1 1 0 | 0 | |
| 1 1 1 | 1 | $s \ x_1 \ x_2$ |

Let's Derive the SOP form

| $s \ x_1 \ x_2$ | $f(s, x_1, x_2)$ | |
|-----------------|------------------|-------------------------|
| 0 0 0 | 0 | |
| 0 0 1 | 0 | |
| 0 1 0 | 1 | $\bar{s} x_1 \bar{x}_2$ |
| 0 1 1 | 1 | $\bar{s} x_1 x_2$ |
| 1 0 0 | 0 | |
| 1 0 1 | 1 | $s \bar{x}_1 x_2$ |
| 1 1 0 | 0 | |
| 1 1 1 | 1 | $s x_1 x_2$ |

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 (\bar{x}_2 + x_2) + s (\bar{x}_1 + x_1) x_2$$


Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$


$$f(s, x_1, x_2) = \bar{s} x_1 (\bar{x}_2 + x_2) + s (\bar{x}_1 + x_1) x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$

Circuit for 2-1 Multiplexer

 


(b) Circuit

 

 
(c) Graphical symbol

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$


Analysis of the 2-1 Multiplexer (when the input $s=0$)



 
Analysis of the 2-1 Multiplexer (when the input $s=1$)



 Analysis of the 2-1 Multiplexer (when the input $s=0$)



 Analysis of the 2-1 Multiplexer (when the input $s=1$)



More Compact Truth-Table Representation

| $s \ x_1 \ x_2$ | $f(s, x_1, x_2)$ |
|-----------------|------------------|
| 0 0 0 | 0 |
| 0 0 1 | 0 |
| 0 1 0 | 1 |
| 0 1 1 | 1 |
| 1 0 0 | 0 |
| 1 0 1 | 1 |
| 1 1 0 | 0 |
| 1 1 1 | 1 |


(a) Truth table

| s | $f(s, x_1, x_2)$ |
|-----|------------------|
| 0 | x_1 |
| 1 | x_2 |

4-1 Multiplexer (Definition)

- Has four inputs: w_0 , w_1 , w_2 , w_3
- Also has two select lines: s_1 and s_0
- If $s_1=0$ and $s_0=0$, then the output f is equal to w_0
- If $s_1=0$ and $s_0=1$, then the output f is equal to w_1
- If $s_1=1$ and $s_0=0$, then the output f is equal to w_2
- If $s_1=1$ and $s_0=1$, then the output f is equal to w_3

Graphical Symbol and Truth Table

 

(a) Graphic symbol

| s_1 | s_0 | f |
|-------|-------|-------|
| 0 | 0 | w_0 |
| 0 | 1 | w_1 |
| 1 | 0 | w_2 |
| 1 | 1 | w_3 |


(b) Truth table

The long-form truth table

The long-form truth table


| $S_1 S_0$ | $I_3 I_2 I_1 I_0$ | F | $S_1 S_0$ | $I_3 I_2 I_1 I_0$ | F | $S_1 S_0$ | $I_3 I_2 I_1 I_0$ | F | $S_1 S_0$ | $I_3 I_2 I_1 I_0$ | F |
|-----------|-------------------|---|-----------|-------------------|---|-----------|-------------------|---|-----------|-------------------|---|
| 0 0 | 0 0 0 0 | 0 | 0 1 | 0 0 0 0 | 0 | 1 0 | 0 0 0 0 | 0 | 1 1 | 0 0 0 0 | 0 |
| | 0 0 0 1 | 1 | | 0 0 0 1 | 0 | | 0 0 0 1 | 0 | | 0 0 0 1 | 0 |
| | 0 0 1 0 | 0 | | 0 0 1 0 | 1 | | 0 0 1 0 | 0 | | 0 0 1 0 | 0 |
| | 0 0 1 1 | 1 | | 0 0 1 1 | 1 | | 0 0 1 1 | 0 | | 0 0 1 1 | 0 |
| | 0 1 0 0 | 0 | | 0 1 0 0 | 0 | | 0 1 0 0 | 1 | | 0 1 0 0 | 0 |
| | 0 1 0 1 | 1 | | 0 1 0 1 | 0 | | 0 1 0 1 | 1 | | 0 1 0 1 | 0 |
| | 0 1 1 0 | 0 | | 0 1 1 0 | 1 | | 0 1 1 0 | 1 | | 0 1 1 0 | 0 |
| | 0 1 1 1 | 1 | | 0 1 1 1 | 1 | | 0 1 1 1 | 1 | | 0 1 1 1 | 0 |
| | 1 0 0 0 | 0 | | 1 0 0 0 | 0 | | 1 0 0 0 | 0 | | 1 0 0 0 | 1 |
| | 1 0 0 1 | 1 | | 1 0 0 1 | 0 | | 1 0 0 1 | 0 | | 1 0 0 1 | 1 |
| | 1 0 1 0 | 0 | | 1 0 1 0 | 1 | | 1 0 1 0 | 0 | | 1 0 1 0 | 1 |
| | 1 0 1 1 | 1 | | 1 0 1 1 | 1 | | 1 0 1 1 | 0 | | 1 0 1 1 | 1 |
| | 1 1 0 0 | 0 | | 1 1 0 0 | 0 | | 1 1 0 0 | 1 | | 1 1 0 0 | 1 |
| | 1 1 0 1 | 1 | | 1 1 0 1 | 0 | | 1 1 0 1 | 1 | | 1 1 0 1 | 1 |
| | 1 1 1 0 | 0 | | 1 1 1 0 | 1 | | 1 1 1 0 | 1 | | 1 1 1 0 | 1 |
| | 1 1 1 1 | 1 | | 1 1 1 1 | 1 | | 1 1 1 1 | 1 | | 1 1 1 1 | 1 |

4-1 Multiplexer (SOP circuit)

 


$$f = \overline{s_1} \overline{s_0} w_0 + \overline{s_1} s_0 w_1 + s_1 \overline{s_0} w_2 + s_1 s_0 w_3$$

 
Analysis of the 4-1 Multiplexer ($s_1=0$ and $s_0=0$)



 
Analysis of the 4-1 Multiplexer ($s_1=0$ and $s_0=0$)



 
Analysis of the 4-1 Multiplexer ($s_1=0$ and $s_0=0$)



 
Analysis of the 4-1 Multiplexer ($s_1=0$ and $s_0=0$)



 
Analysis of the 4-1 Multiplexer ($s_1=0$ and $s_0=1$)



 
Analysis of the 4-1 Multiplexer ($s_1=1$ and $s_0=0$)



 
Analysis of the 4-1 Multiplexer ($s_1=1$ and $s_0=1$)



 
Analysis of the 4-1 Multiplexer ($s_1=0$ and $s_0=0$)



 
Analysis of the 4-1 Multiplexer ($s_1=0$ and $s_0=1$)



 
Analysis of the 4-1 Multiplexer ($s_1=1$ and $s_0=0$)




 
Analysis of the 4-1 Multiplexer ($s_1=1$ and $s_0=1$)



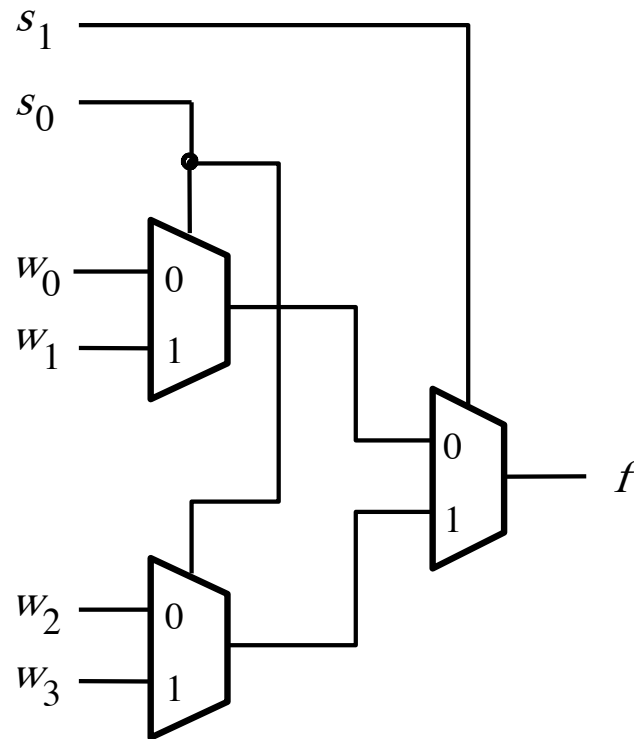
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



  
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 That is different from the SOP form of the 4-1 multiplexer shown below, which uses less gates




Analysis of the Hierarchical Implementation ($s_1=0$ and $s_0=0$)

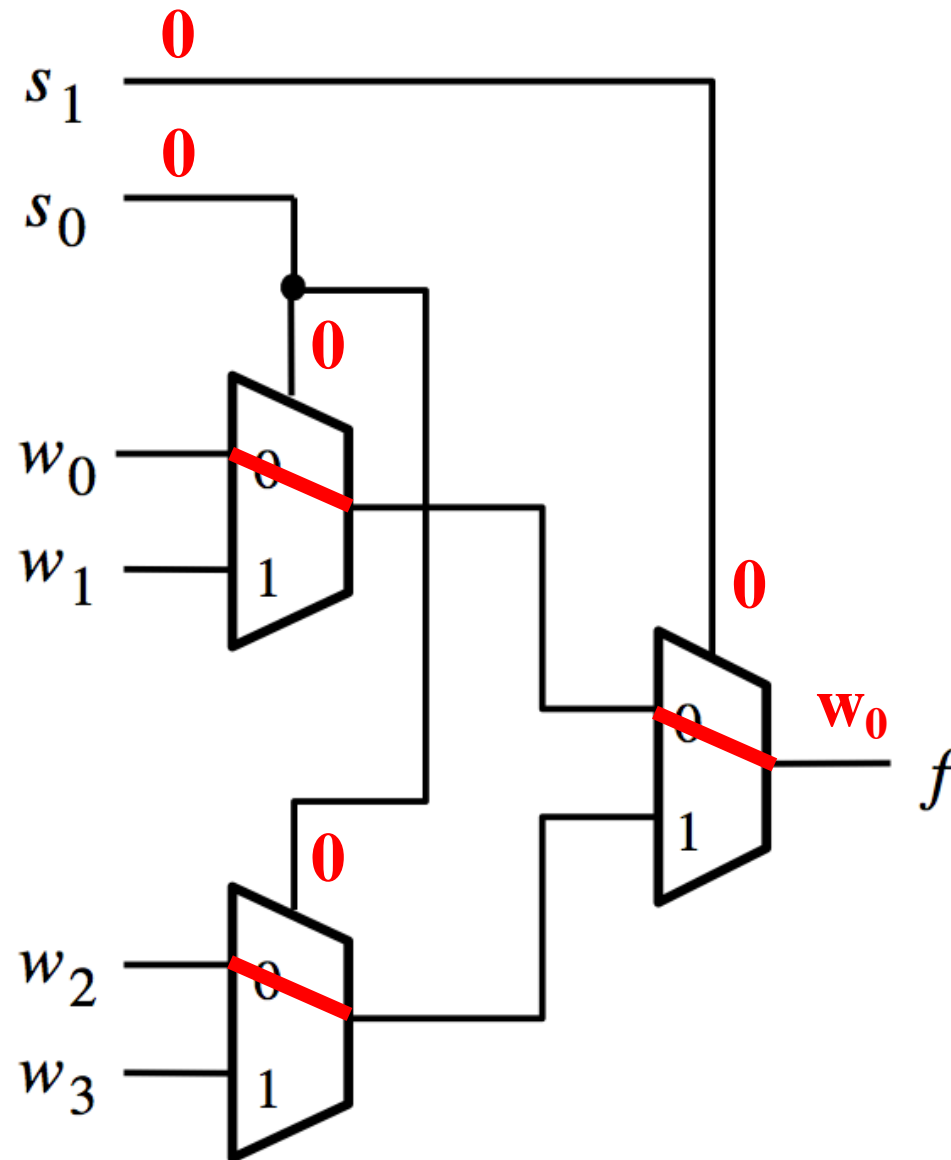


[Figure 4.3 from the textbook]

Analysis of the Hierarchical Implementation ($s_1=0$ and $s_0=1$)

 


[Figure 4.3 from the textbook]

Analysis of the Hierarchical Implementation ($s_1=1$ and $s_0=0$)

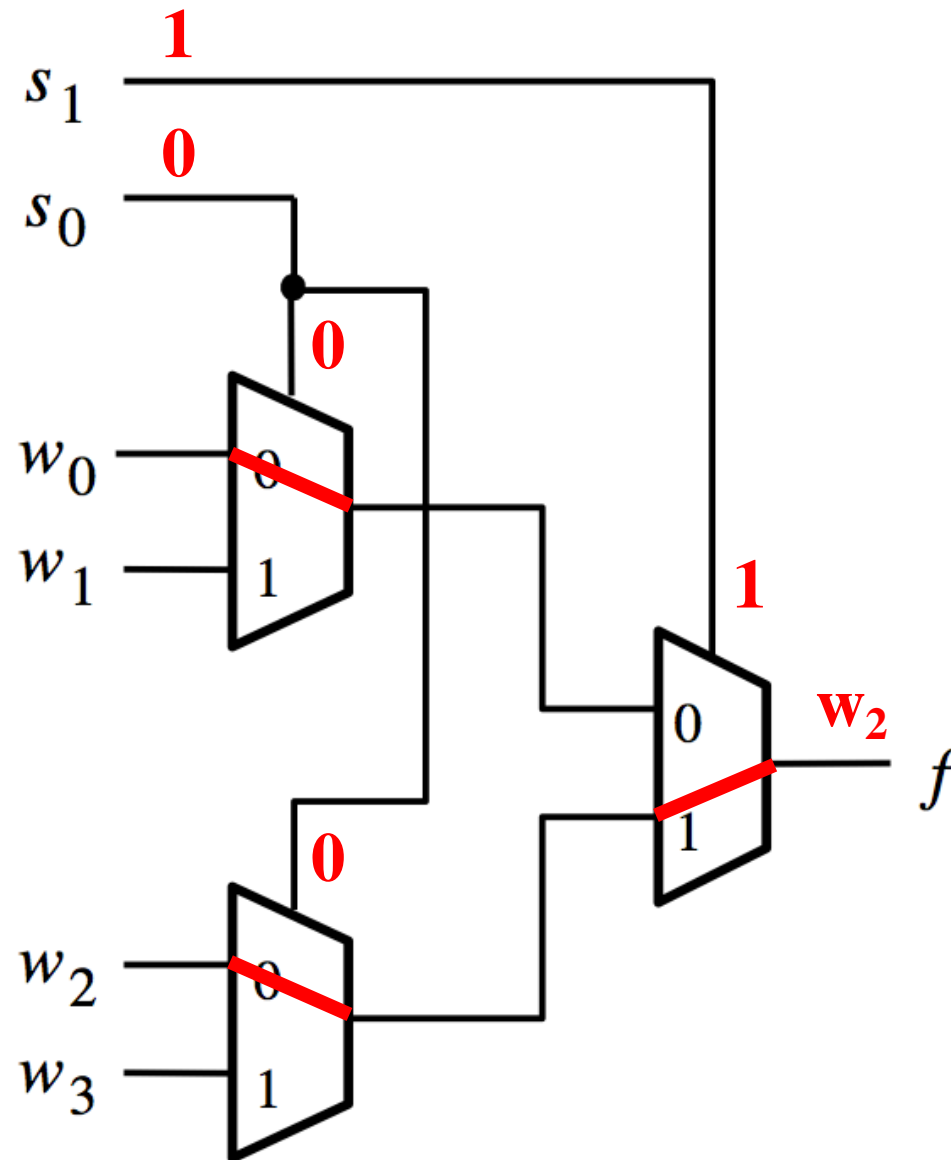


[Figure 4.3 from the textbook]

Analysis of the Hierarchical Implementation ($s_1=1$ and $s_0=1$)

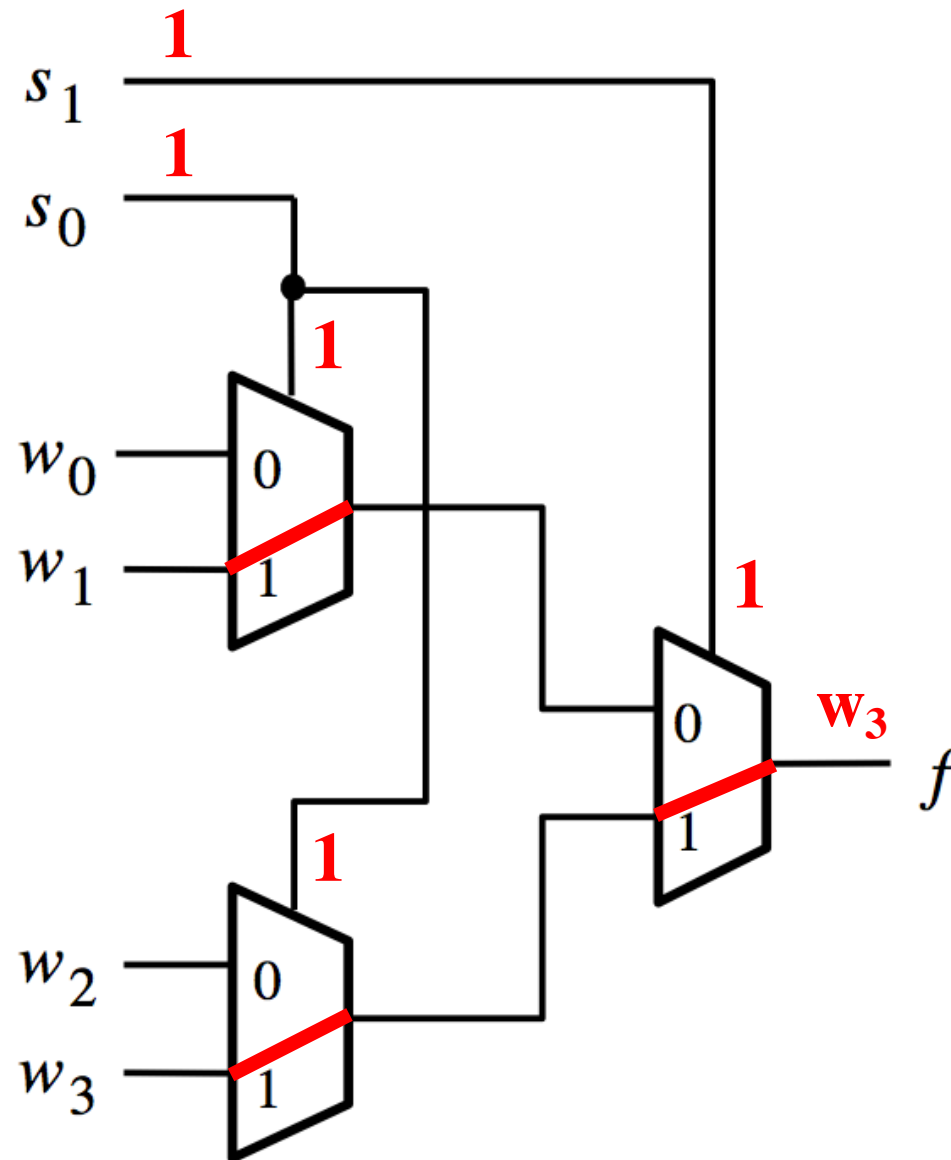

[Figure 4.3 from the textbook]


16-1 Multiplexer

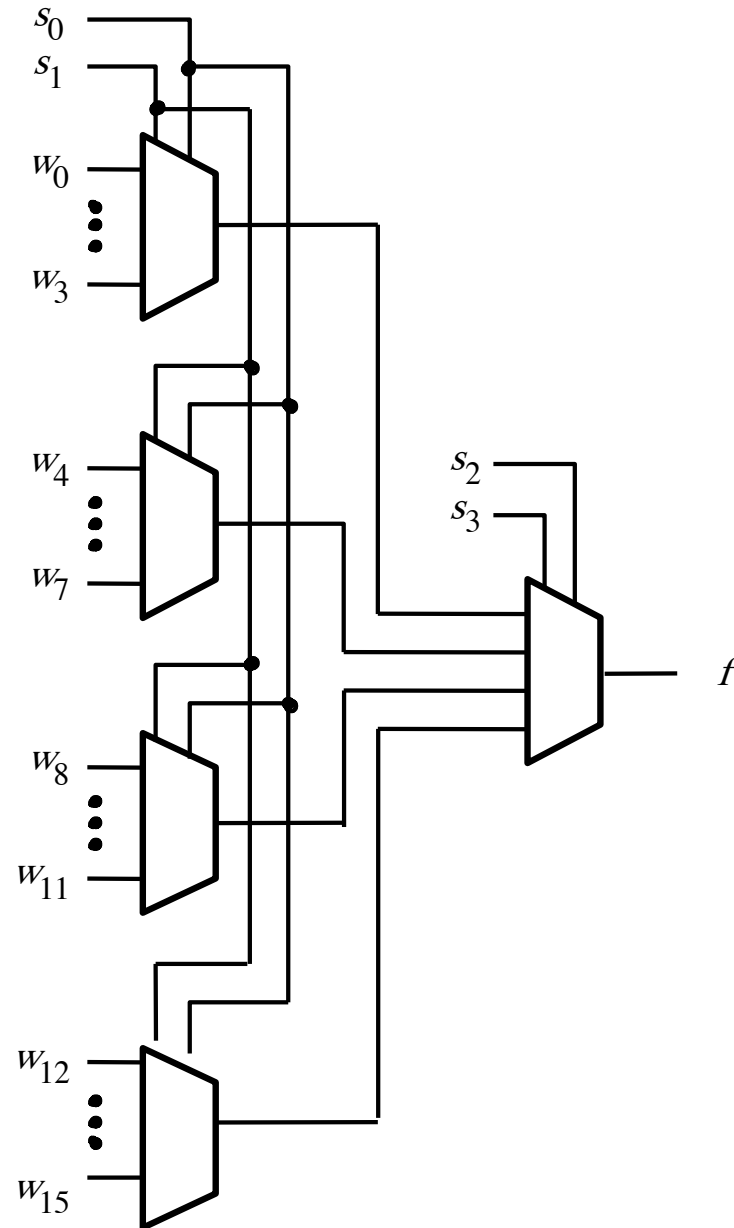


[Figure 4.4 from the textbook]

Multiplexers Are Special


The Three Basic Logic Gates

 

NOT gate

 


AND gate

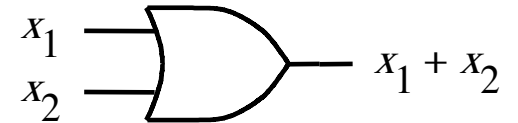


OR gate

Truth Table for NOT

 


| x | \bar{x} |
|-----|-----------|
| 0 | 1 |
| 1 | 0 |

Truth Table for AND

 


| x_1 | x_2 | $x_1 \cdot x_2$ |
|-------|-------|-----------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Truth Table for OR

 


| x_1 | x_2 | $x_1 + x_2$ |
|-------|-------|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |


Building an AND Gate with 4-to-1 Mux

 


| x_1 | x_2 | $x_1 \cdot x_2$ |
|-------|-------|-----------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

 

Building an AND Gate with 4-to-1 Mux

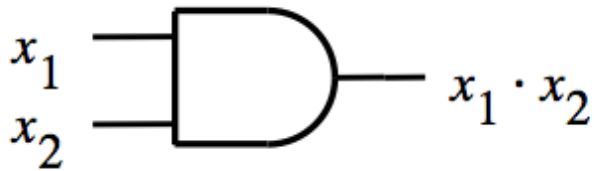


| x_1 | x_2 | $x_1 \cdot x_2$ |
|-------|-------|-----------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

 


These two are the same.

Building an AND Gate with 4-to-1 Mux

 


| x_1 | x_2 | $x_1 \cdot x_2$ |
|-------|-------|-----------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

 


These two are the same.

And so are these two.


Building an OR Gate with 4-to-1 Mux

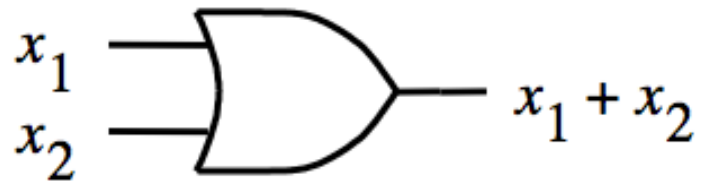


| x_1 | x_2 | $x_1 + x_2$ |
|-------|-------|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

 

Building an OR Gate with 4-to-1 Mux

 


| x_1 | x_2 | $x_1 + x_2$ |
|-------|-------|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

 


These two are the same.

Building an OR Gate with 4-to-1 Mux

 


| x_1 | x_2 | $x_1 + x_2$ |
|-------|-------|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

 


These two are the same.

And so are these two.


Building a NOT Gate with 4-to-1 Mux

 


| x | \bar{x} |
|-----|-----------|
| 0 | 1 |
| 1 | 0 |

 

Building a NOT Gate with 4-to-1 Mux

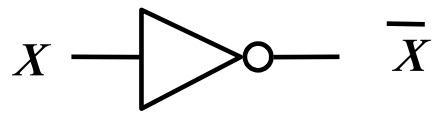


| x | y | f |
|-----|-----|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

 


Introduce a dummy variable y .


Building a NOT Gate with 4-to-1 Mux

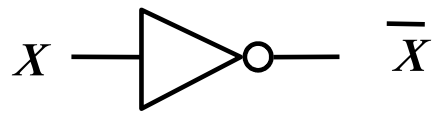


| x | y | f |
|-----|-----|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

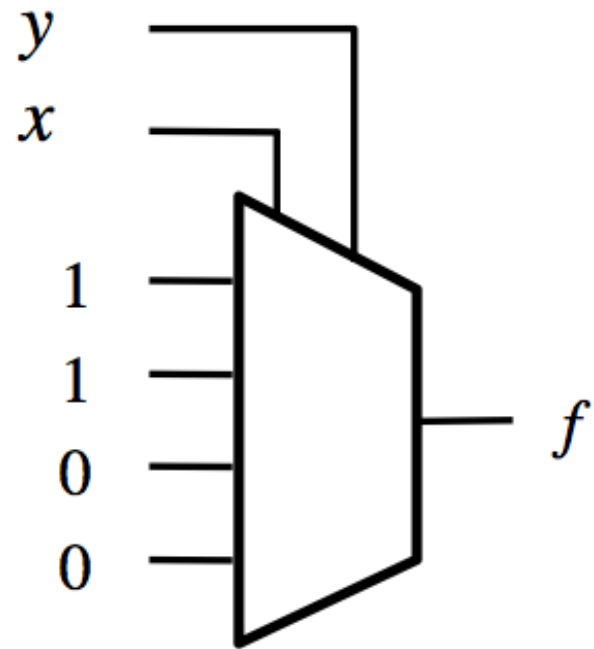

Building a NOT Gate with 4-to-1 Mux

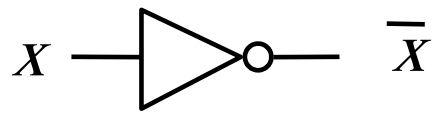


| x | y | f |
|-----|-----|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


 


Now set y to either 0 or 1 (both will work). Why?

Building a NOT Gate with 4-to-1 Mux

 

| x | \bar{x} |
|-----|-----------|
| 0 | 1 |
| 1 | 0 |

  


Two alternative solutions.


Implications

**Any Boolean function can be implemented
using only 4-to-1 multiplexers!**


Building an AND Gate with 2-to-1 Mux

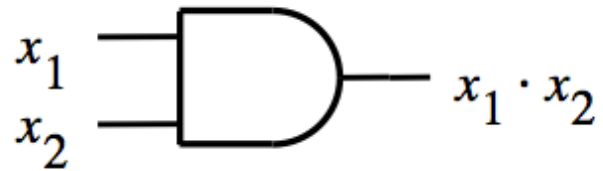


| x_1 | x_2 | $x_1 \cdot x_2$ |
|-------|-------|-----------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

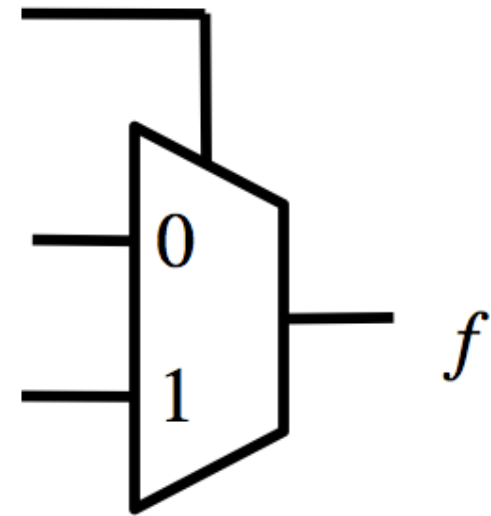


Building an AND Gate with 2-to-1 Mux

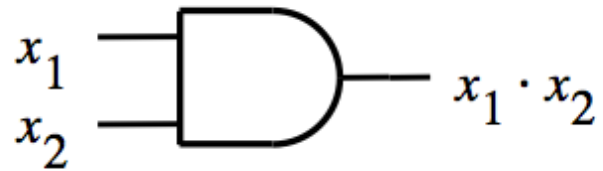

| x_1 | x_2 | $x_1 \cdot x_2$ |
|-------|-------|-----------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

 


Building an AND Gate with 2-to-1 Mux

 


| x_1 | x_2 | $x_1 \cdot x_2$ |
|-------|-------|-----------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

 
Red annotations: A vertical red line is drawn between the x_1 and x_2 columns. A horizontal red line is drawn between the second and third rows. Red curly braces group the output values: the first two rows are grouped and labeled 0 , and the last two rows are grouped and labeled x_2 .




Building an OR Gate with 2-to-1 Mux

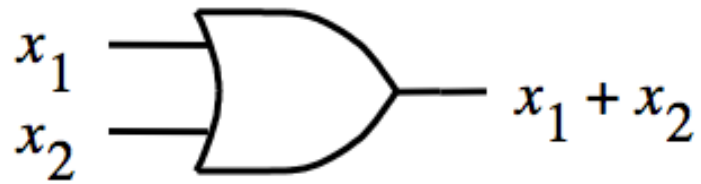


| x_1 | x_2 | $x_1 + x_2$ |
|-------|-------|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

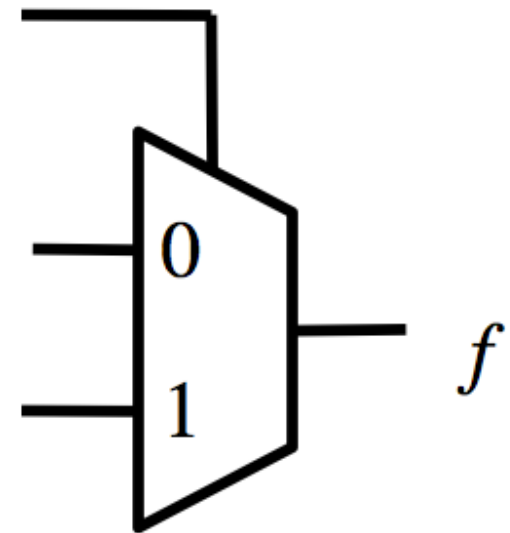


Building an OR Gate with 2-to-1 Mux

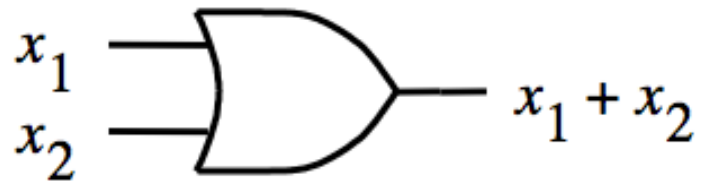

| x_1 | x_2 | $x_1 + x_2$ |
|-------|-------|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

 


Building an OR Gate with 2-to-1 Mux

 


| x_1 | x_2 | $x_1 + x_2$ |
|-------|-------|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

 
Red annotations: A vertical red line is between the x_1 and x_2 columns. A horizontal red line is between the second and third rows. Red curly braces on the right group the output values: the first two rows are grouped and labeled x_2 , and the last two rows are grouped and labeled 1 .




Building a NOT Gate with 2-to-1 Mux

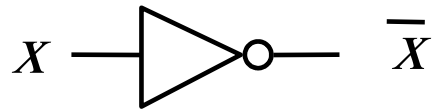


| x | \bar{x} |
|-----|-----------|
| 0 | 1 |
| 1 | 0 |

 

Building a NOT Gate with 2-to-1 Mux

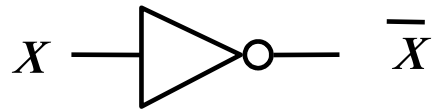

| x | \bar{x} |
|-----|-----------|
| 0 | 1 |
| 1 | 0 |

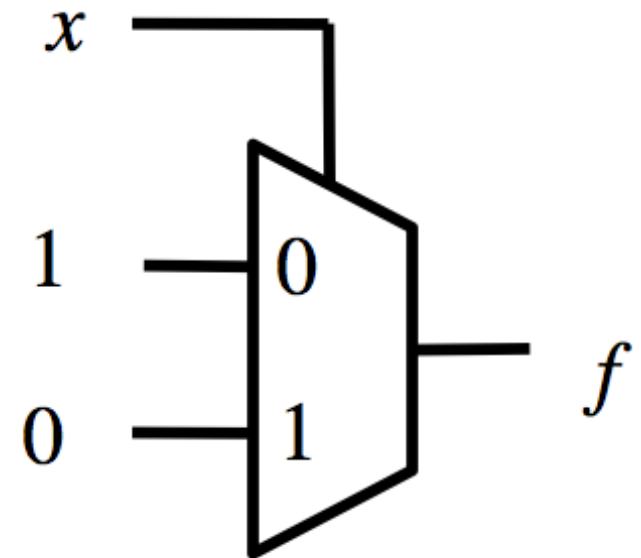


Implications



**Any Boolean function can be implemented
using only 2-to-1 multiplexers!**

Synthesis of Logic Circuits Using Multiplexers


2 x 2 Crossbar switch

 


2 x 2 Crossbar switch

  

 
Implementation of a 2 x 2 crossbar switch with multiplexers



 Implementation of a 2 x 2 crossbar switch with multiplexers




 Implementation of a 2 x 2 crossbar switch with multiplexers



Implementation of a logic function with a 4x1 multiplexer

| w_1 | w_2 | f |
|-------|-------|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

 


Implementation of the same logic function with a 2x1 multiplexer

| w_1 | w_2 | f |
|-------|-------|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


| w_1 | f |
|-------|-------------|
| 0 | w_2 |
| 1 | \bar{w}_2 |

(b) Modified truth table

 

(c) Circuit

The XOR Logic Gate

 


(a) Two switches that control a light

| x | y | L |
|-----|-----|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

(b) Truth table


The XOR Logic Gate

 

(a) Two switches that control a light

| x | y | L |
|-----|-----|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

(b) Truth table

 


(c) Logic network




 (d) XOR gate symbol


Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



 
Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT





 
Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



 These two circuits are equivalent
(the wires of the bottom AND gate are flipped)



   **In other words,
all four of these are equivalent!**




Implementation of another logic function

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |



Implementation of another logic function

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Implementation of another logic function

 

Implementation of another logic function

 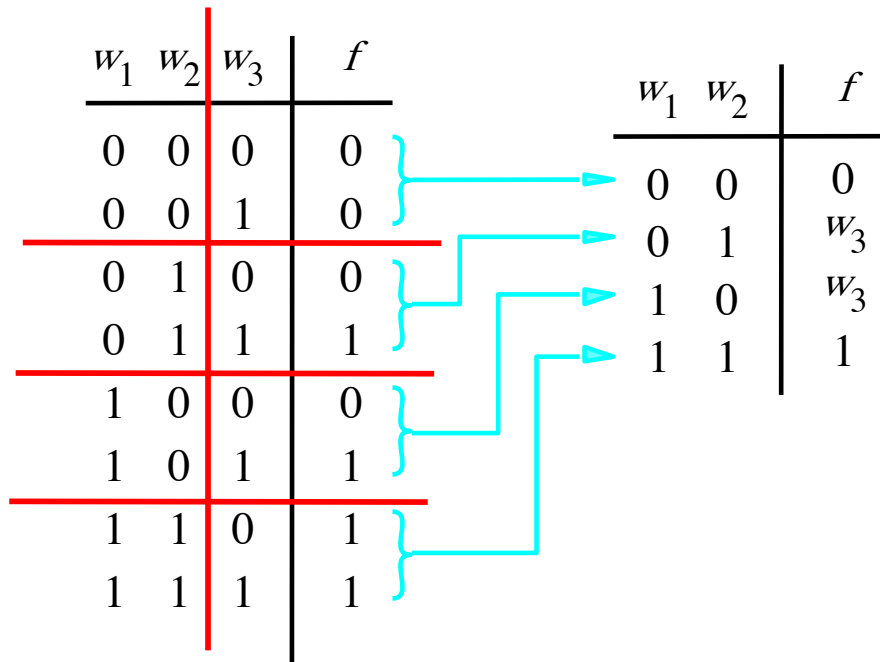

Another Example (3-input XOR)

Implementation of 3-input XOR with 2-to-1 Multiplexers

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Implementation of 3-input XOR with 2-to-1 Multiplexers


| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Red annotations in the original image: A vertical red line is drawn between the w_1 column and the w_2 column. A horizontal red line is drawn between the $w_1 = 0$ rows and the $w_1 = 1$ rows. Red curly braces group the f values for $w_1 = 0$ and $w_1 = 1$. The top brace is labeled $w_2 \oplus w_3$. The bottom brace is labeled $\overline{w_2 \oplus w_3}$.

Implementation of 3-input XOR with 2-to-1 Multiplexers

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

(a) Truth table

 


(b) Circuit

Implementation of 3-input XOR with 2-to-1 Multiplexers

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

} w_3
} $\overline{w_3}$

(a) Truth table

 

(b) Circuit

Implementation of 3-input XOR with a 4-to-1 Multiplexer

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Implementation of 3-input XOR with a 4-to-1 Multiplexer

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |


Implementation of 3-input XOR with a 4-to-1 Multiplexer

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Implementation of 3-input XOR with a 4-to-1 Multiplexer

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

(a) Truth table

 

(b) Circuit

Multiplexor Synthesis Using Shannon's Expansion

Three-input majority function

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Three-input majority function

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

| w_1 | f |
|-------|-----|
| 0 | 0 |
| 0 | 1 |

Three-input majority function

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |


| w_1 | f |
|-------|-------------|
| 0 | $w_2 w_3$ |
| 1 | $w_2 + w_3$ |

Three-input majority function

| w_1 | w_2 | w_3 | f |
|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

| w_1 | f |
|-------|-------------|
| 0 | $w_2 w_3$ |
| 1 | $w_2 + w_3$ |

(b) Truth table

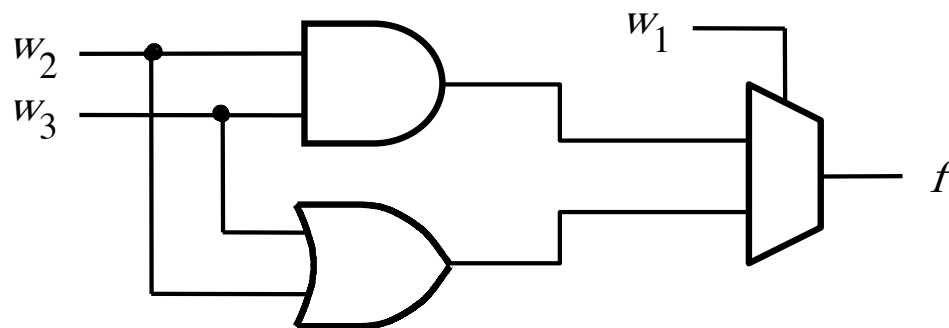


(b) Circuit

Three-input majority function

$$f = \bar{w}_1 w_2 w_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 \bar{w}_3 + w_1 w_2 w_3$$
 
$$\begin{aligned} f &= \bar{w}_1 (w_2 w_3) + w_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3 + w_2 w_3) \\ &= \bar{w}_1 (w_2 w_3) + w_1 (w_2 + w_3) \end{aligned}$$



Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

cofactor

cofactor

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3 (\overline{w_1} + w_1)$$

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3 (\bar{w}_1 + w_1)$$

$$\begin{aligned} f &= \bar{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$

Shannon's Expansion Theorem (In terms of more than one variable)

$$f(w_1, \dots, w_n) = \bar{w}_1 \bar{w}_2 \cdot f(0, 0, w_3, \dots, w_n) + \bar{w}_1 w_2 \cdot f(0, 1, w_3, \dots, w_n) \\ + w_1 \bar{w}_2 \cdot f(1, 0, w_3, \dots, w_n) + w_1 w_2 \cdot f(1, 1, w_3, \dots, w_n)$$

This form is suitable for implementation with a 4x1 multiplexer.

Another Example

Factor and implement the following function with a 2x1 multiplexer


$$f = \bar{w}_1\bar{w}_3 + w_1w_2 + w_1w_3$$

Factor and implement the following function with a 2x1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$

 Factor and implement the following function with a 2x1 multiplexer



$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$

Factor and implement the following function with a 4x1 multiplexer


$$f = \bar{w}_1\bar{w}_3 + w_1w_2 + w_1w_3$$

Factor and implement the following function with a 4x1 multiplexer

$$f = \bar{w}_1\bar{w}_3 + w_1w_2 + w_1w_3$$

$$\begin{aligned} f &= \bar{w}_1\bar{w}_2f_{\bar{w}_1\bar{w}_2} + \bar{w}_1w_2f_{\bar{w}_1w_2} + w_1\bar{w}_2f_{w_1\bar{w}_2} + w_1w_2f_{w_1w_2} \\ &= \bar{w}_1\bar{w}_2(\bar{w}_3) + \bar{w}_1w_2(\bar{w}_3) + w_1\bar{w}_2(w_3) + w_1w_2(1) \end{aligned}$$

 Factor and implement the following function with a 4x1 multiplexer



$$\begin{aligned} f &= \bar{w}_1 \bar{w}_2 f_{\bar{w}_1 \bar{w}_2} + \bar{w}_1 w_2 f_{\bar{w}_1 w_2} + w_1 \bar{w}_2 f_{w_1 \bar{w}_2} + w_1 w_2 f_{w_1 w_2} \\ &= \bar{w}_1 \bar{w}_2 (\bar{w}_3) + \bar{w}_1 w_2 (\bar{w}_3) + w_1 \bar{w}_2 (w_3) + w_1 w_2 (1) \end{aligned}$$

Yet Another Example

Factor and implement the following function using only 2x1 multiplexers

$$f = w_1w_2 + w_1w_3 + w_2w_3$$

Factor and implement the following function using only 2x1 multiplexers

$$f = w_1w_2 + w_1w_3 + w_2w_3$$

$$\begin{aligned} f &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$

Factor and implement the following function using only 2x1 multiplexers


$$f = w_1w_2 + w_1w_3 + w_2w_3$$

$$f = \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3)$$

$$= \bar{w}_1(\underbrace{w_2w_3}) + w_1(\underbrace{w_2 + w_3})$$

$$g = w_2w_3 \quad h = w_2 + w_3$$

 Factor and implement the following function using only 2x1 multiplexers



$$f = \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3)$$

$$= \bar{w}_1(\underbrace{w_2w_3}) + w_1(\underbrace{w_2 + w_3})$$

$$g = w_2w_3 \quad h = w_2 + w_3$$

Factor and implement the following function using only 2x1 multiplexers

$$g = w_2 w_3$$

$$h = w_2 + w_3$$

Factor and implement the following function using only 2x1 multiplexers

$$g = w_2 w_3$$





$$g = \bar{w}_2(0) + w_2(w_3)$$

$$h = w_2 + w_3$$



$$h = \bar{w}_2(w_3) + w_2(1)$$

  
Factor and implement the following function using only 2x1 multiplexers




$$g = \bar{w}_2(0) + w_2(w_3)$$

$$h = \bar{w}_2(w_3) + w_2(1)$$

 
Finally, we are ready to draw the circuit



 Finally, we are ready to draw the circuit



Finally, we are ready to draw the circuit

 

[Figure 4.12 from the textbook]

Questions?

THE END