

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Registers

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **Homework 8 is due next Monday.**
- **The second midterm exam is next Friday.**

Administrative Stuff

- **Midterm Exam #2**
- **When: Friday November 1 @ 4pm.**
- **Where: This classroom**
- **What: Chapters 1, 2, 3, 4 and 5.1-5.8**
- **The exam will be closed book but open notes
(you can bring up to 3 pages of handwritten notes).**

Midterm 2: Format

- **The exam will be out of 130 points**
- **You need 95 points to get an A for this exam**
- **It will be great if you can score more than 100 points.**
 - but you can't roll over your extra points ☹

Midterm 2: Topics


- **Binary Numbers and Hexadecimal Numbers**
- **1's complement and 2's complement representation**
- **Addition and subtraction of binary numbers**
- **Circuits for adders and fast adders**
- **Single and Double precision IEEE floating point formats**
- **Converting a real number to the IEEE format**
- **Converting a floating point number to base 10**
- **Multiplexers (circuits and function)**
- **Synthesis of logic functions using multiplexers**
- **Shannon's Expansion Theorem**

Midterm 2: Topics


- Decoders (circuits and function)
- Demultiplexers
- Encoders (binary and priority)
- Code Converters
- K-maps for 2, 3, and 4 variables
- Synthesis of logic circuits using adders, multiplexers, encoders, decoders, and basic logic gates
- Synthesis of logic circuits given constraints on the available building blocks that you can use
- Latches (circuits, behavior, timing diagrams)
- Flip-Flops (circuits, behavior, timing diagrams)
- Registers and Register Files

Review of Flip-Flops


A simple memory element with NOT Gates

 

A simple memory element with NAND Gates

 


A simple memory element with NOR Gates

 


Basic Latch


A simple memory element with NOR Gates

 


A simple memory element with NOR Gates

 

A simple memory element with NOR Gates


 


A memory element with NOR gates

 


[Figure 5.3 from the textbook]

Two Different Ways to Draw the Same Circuit

  

[Figure 5.3 & 5.4 from the textbook]

SR Latch: Circuit and Truth Table

 


(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	(Undesirable)

(b) Truth table

[Figure 5.4a,b from the textbook]

NOR Gate

 


NOR Gate Truth table

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0


Gated SR Latch

Circuit Diagram for the Gated SR Latch

 


[Figure 5.5a from the textbook]

Circuit Diagram for the Gated SR Latch

 


This is the “gate”
of the gated latch

Circuit Diagram for the Gated SR Latch

 


Notice that these
are complements
of each other

 Gated SR Latch: Circuit Diagram, Characteristic Table, and Graphical Symbol




Clk	S	R	$Q(t + 1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x (Undesirable)

 


[Figure 5.5 from the textbook]

Gated SR latch with NAND gates

 


[Figure 5.6 from the textbook]

Gated SR latch with NAND gates

 


In this case the “gate” is
constructed using NAND
gates! Not AND gates.

Gated SR latch with NAND gates

 


Also, notice that the positions of S and R are now swapped.

Gated SR latch with NAND gates

 


Finally, notice that when $\text{Clk}=1$ this turns into the basic latch with NAND gates, i.e., the $\bar{S}\bar{R}$ Latch.


Gated SR latch with NOR gates

 


Gated SR latch with NAND gates

 

Gated SR latch with NOR gates

 


Gated SR latch with NAND gates

 


Graphical symbols are the same

Gated SR latch with NOR gates

 

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)

Gated SR latch with NAND gates

 


Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)

Characteristic tables are the same


Gated D Latch

Circuit Diagram for the Gated D Latch

 


[Figure 5.7a from the textbook]

Gated D Latch: Alternative Design

 

 Gated D Latch: Circuit Diagram, Characteristic Table, and Graphical Symbol




Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

Note that it is now impossible to have S=R=1.


When Clk=1 the output follows the D input.

When Clk=0 the output cannot be changed.

 

[Figure 5.7a,b from the textbook]

Setup and hold times for Gated D latch

 


Setup time (t_{su}) – the minimum time that the D signal must be stable prior to the the negative edge of the Clock signal

Hold time (t_h) – the minimum time that the D signal must remain stable after the the negative edge of the Clock signal


Master-Slave D Flip-Flop

Constructing a Master-Slave D Flip-Flop From Two D Latches


Master

 


Slave

 

 
Constructing a Master-Slave D Flip-Flop From Two D Latches



 Constructing a Master-Slave D Flip-Flop From Two D Latches



Constructing a Master-Slave D Flip-Flop From Two D Latches

 


[Figure 5.9a from the textbook]


Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

Master

 


Slave

 


Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

 


Edge-Triggered D Flip-Flops

Master-Slave D Flip-Flop

 


[Figure 5.9a from the textbook]

 
Negative-Edge-Triggered Master-Slave D Flip-Flop



 
Positive-Edge-Triggered Master-Slave D Flip-Flop



 
Negative-Edge-Triggered Master-Slave D Flip-Flop



 
Positive-Edge-Triggered Master-Slave D Flip-Flop



 Negative-Edge-Triggered Master-Slave D Flip-Flop




 Positive-Edge-Triggered Master-Slave D Flip-Flop




T Flip-Flop

T Flip-Flop

 

[Figure 5.15a from the textbook]


T Flip-Flop

 

Positive-edge-triggered
D Flip-Flop

[Figure 5.15a from the textbook]


T Flip-Flop

 



What is this?

[Figure 5.15a from the textbook]

What is this?

 


What is this?

  


= ?

T Flip-Flop

 


T Flip-Flop

 


Note that the two inputs to the multiplexer are inverses of each other.

Another Way to Draw This

 


Another Way to Draw This

 


What is this?

What is this?

 


What is this?

 


$$D = Q\bar{T} + \bar{Q}T$$

It is an XOR

 


$$D = Q \oplus T$$

It is an XOR

 


$$D = Q \oplus T$$




What is this?

 

T Flip-Flop

 

T Flip-Flop (circuit, truth table and graphical symbol)

   

[Figure 5.15a-c from the textbook]

T Flip-Flop (How it Works)


If $T=0$ then it stays in its current state

If $T=1$ then it reverses its current state

**In other words the circuit “toggles” its state
when $T=1$. This is why it is called T flip-flop.**

JK Flip-Flop


JK Flip-Flop

 

$$D = \bar{J}\bar{Q} + \bar{K}Q$$


[Figure 5.16a from the textbook]

JK Flip-Flop

 

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

 

(c) Graphical symbol

[Figure 5.16 from the textbook]

JK Flip-Flop

(How it Works)

A versatile circuit that can be used both as a SR flip-flop and as a T flip flop

If $J=0$ and $S =0$ it stays in the same state


Just like SR It can be set and reset

$J=S$ and $K=R$


If $J=K=1$ then it behaves as a T flip-flop

Complete Wiring Diagrams


Positive-Edge-Triggered D Flip-Flop

 


Negative-Edge-Triggered D Flip-Flop

 

 
The Complete Wiring Diagram for a Positive-Edge-Triggered D Flip-Flop



 
The Complete Wiring Diagram for a Negative-Edge-Triggered D Flip-Flop



 
The Complete Wiring Diagram for a **Negative-Edge-Trigged** D Flip-Flop




Positive-Edge-Triggered T Flip-Flop

 


Negative-Edge-Triggered T Flip-Flop

 

 
The Complete Wiring Diagram for a Positive-Edge-Triggered D Flip-Flop



 
The Complete Wiring Diagram for a **Negative-Edge-Trigged** D Flip-Flop




Positive-Edge-Triggered JK Flip-Flop

 


Negative-Edge-Trigged JK Flip-Flop

 

 The Complete Wiring Diagram for a Positive-Edge-Triggered JK Flip-Flop



 The Complete Wiring Diagram for a Negative-Edge-Triggered JK Flip-Flop




Registers

Register (Definition)


An n-bit structure consisting of flip-flops.

Parallel-Access Register

1-Bit Parallel-Access Register

 


1-Bit Parallel-Access Register

 

The 2-to-1 multiplexer is used to select whether to load a new value into the D flip-flop or to retain the old value.


The output of this circuit is the Q output of the flip-flop.

1-Bit Parallel-Access Register

 


If Load = 0, then retain the old value.

1-Bit Parallel-Access Register

 

If Load = 1, then load the new value from In.


1-Bit Parallel-Access Register

 


If Load = 0, then retain the old value.

If Load = 1, then load the new value from In.


2-Bit Parallel-Access Register

 

2-Bit Parallel-Access Register

 


3-Bit Parallel-Access Register

 


Notice that all flip-flops are on the same clock cycle.


3-Bit Parallel-Access Register

 


4-Bit Parallel-Access Register

 


4-Bit Parallel-Access Register

 


4-Bit Parallel-Access Register

 

4-Bit Parallel-Access Register

 


4-Bit Parallel-Access Register

 


Shift Register

A simple shift register

 



[Figure 5.17a from the textbook]

A simple shift register


 


Positive-edge-triggered
D Flip-Flop


A simple shift register

  



A simple shift register

  



A simple shift register

 



A simple shift register

  



A simple shift register

  



A simple shift register

  


A simple shift register

  


A simple shift register

  


A simple shift register

 


A simple shift register

 


A simple shift register

 


A simple shift register

 

A simple shift register

 

A simple shift register

 

(a) Circuit


	In	Q_1	Q_2	Q_3	$Q_4 = \text{Out}$
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

(b) A sample sequence

[Figure 5.17 from the textbook]


Parallel-Access Shift Register

Parallel-access shift register

 


[Figure 5.18 from the textbook]

Parallel-access shift register

 

When Load=0, this behaves like a shift register.


Parallel-access shift register

 

When Load=1, this behaves like a parallel-access register.


Shift Register With Parallel Load and Enable

A shift register with parallel load and enable control inputs

 


[Figure 5.59 from the textbook]

 A shift register with parallel load and enable control inputs




The directions of the input and output lines are switched relative to the previous slides.

A shift register with parallel load and enable control inputs

 


[Figure 5.59 from the textbook]

A shift register with parallel load and enable control inputs

 


[Figure 5.59 from the textbook]

A shift register with parallel load and enable control inputs

 


[Figure 5.59 from the textbook]

A shift register with parallel load and enable control inputs

 

[Figure 5.59 from the textbook]

A shift register with parallel load and enable control inputs

 

[Figure 5.59 from the textbook]





Parallel-access shift left / right register

Parallel-access shift left/right register


Complete the following circuit diagram to implement a 4-bit register that has both parallel load and shift left/right functionality. The register has two control inputs (C_1 and C_0), four parallel input lines (I_3 , I_2 , I_1 , and I_0), and four output lines (Q_3 , Q_2 , Q_1 , and Q_0). Depending on the values of C_1 and C_0 , the register performs one of the following four operations:

C_1	C_0	Operation
0	0	Hold the current value (i.e., $Q_3 Q_2 Q_1 Q_0$ are not changed)
0	1	Shift left (i.e., new $Q_3=Q_2$, new $Q_2=Q_1$, new $Q_1=Q_0$, new $Q_0=I_0$)
1	0	Shift right (i.e., new $Q_3=I_3$, new $Q_2=Q_3$, new $Q_1=Q_2$, new $Q_0=Q_1$)
1	1	Load new data (i.e., new $Q_3=I_3$, new $Q_2=I_2$, new $Q_1=I_1$, new $Q_0=I_0$)

    
Parallel-access shift left/right register



 
Parallel-access shift left/right register



 
Parallel-access shift left/right register



 
Parallel-access shift left/right register



 
Parallel-access shift left/right register



 
Parallel-access shift left/right register



 
Parallel-access shift left/right register



 
Parallel-access shift left/right register



 Parallel-access shift left/right register



 
Parallel-access shift left/right register




Multiplexer Tricks

(select one of two 2-bit numbers)


Select Either $A=A_1A_0$ or $B=B_1B_0$

 

 Select Either $A = A_1A_0$ or $B = B_1B_0$



 
Select Either $A = A_1A_0$ or $B = B_1B_0$




Multiplexer Tricks

(select one of four 2-bit numbers)

 
Select $A=A_1A_0$ or $B=B_1B_0$ or $C=C_1C_0$ or $D=D_1D_0$



 
Select $A = A_1A_0$ or $B = B_1B_0$ or $C = C_1C_0$ or $D = D_1D_0$



 
Select $A = A_1A_0$ or $B = B_1B_0$ or $C = C_1C_0$ or $D = D_1D_0$



 Select $A = A_1A_0$ or $B = B_1B_0$ or $C = C_1C_0$ or $D = D_1D_0$
























 
Select $A = A_1A_0$ or $B = B_1B_0$ or $C = C_1C_0$ or $D = D_1D_0$




Register File


Complete the following circuit diagram to implement a register file with four 2-bit registers, one write port, one read port, and one write enable line.

           

           


 


Register 0

 




Register 1

 


Register 2

 


Register 3

   


 


Register A

 




Register B







 



Register C

 

Register D

   

       



 



Register A


Register B


Register C


Register D

   


 

 

 

 

 

Questions?

THE END