



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Mealy State Model

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **Homework 10 is out**
- **It is due on Wednesday Nov 13 @ 4pm**

Administrative Stuff

- **Homework 11 is out**
- **It is due on Monday Nov 18 @ 4pm**

Administrative Stuff

- **Final Project**
- **Posted on the class web page (Labs section)**
- **Pick one of the problems and solve it.**
- **Your grade will not depend on which project you pick**
- **By next Wednesday you need to select your project and send an e-mail to your lab TAs**

Sample E-mail


Hello TAs,

I decided to pick problem number x for my final project in CprE 281.

Thanks,


[your name, your lab section]

The general form of a synchronous sequential circuit

 


[Figure 6.1 from the textbook]

Moore Type

 

Mealy Type

 

Sample Problem

Implement a 11 detector. In other words, the output should be equal to 1 if two consecutive 1's have been detected on the input line.

The output should become 1 as soon as the second 1 is detected in the input.

Sequences of input and output signals

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0


Sequences of input and output signals

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals


Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 State diagram of an FSM that realizes the task




Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}	
input w :	<input type="checkbox"/>	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0	

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

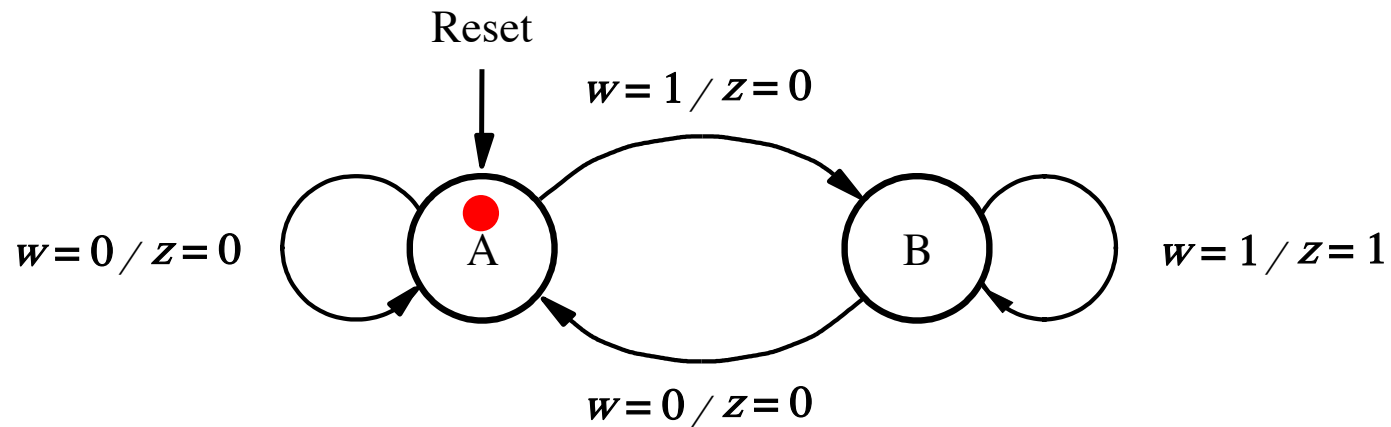


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

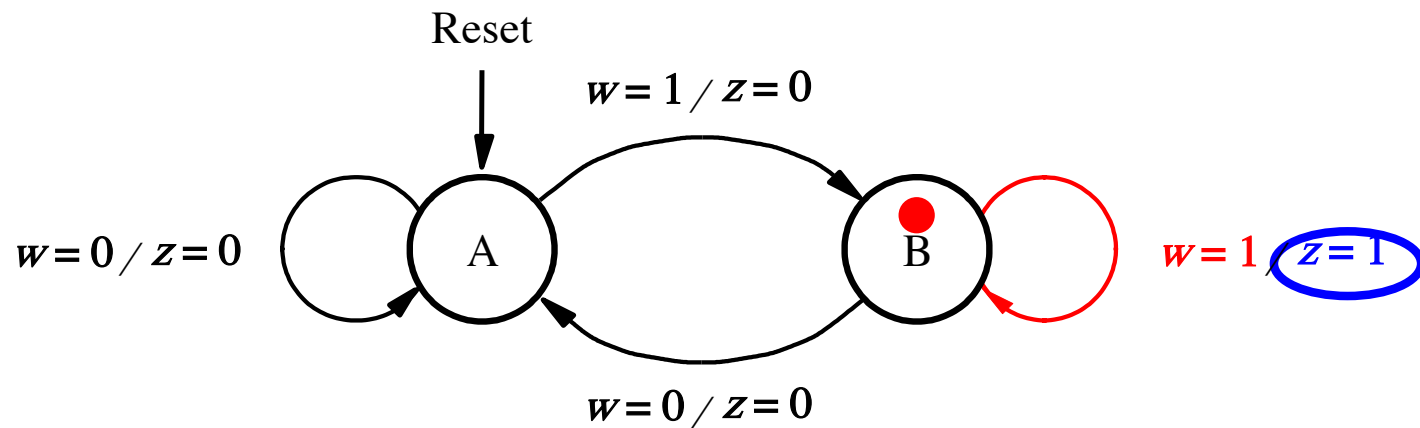


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

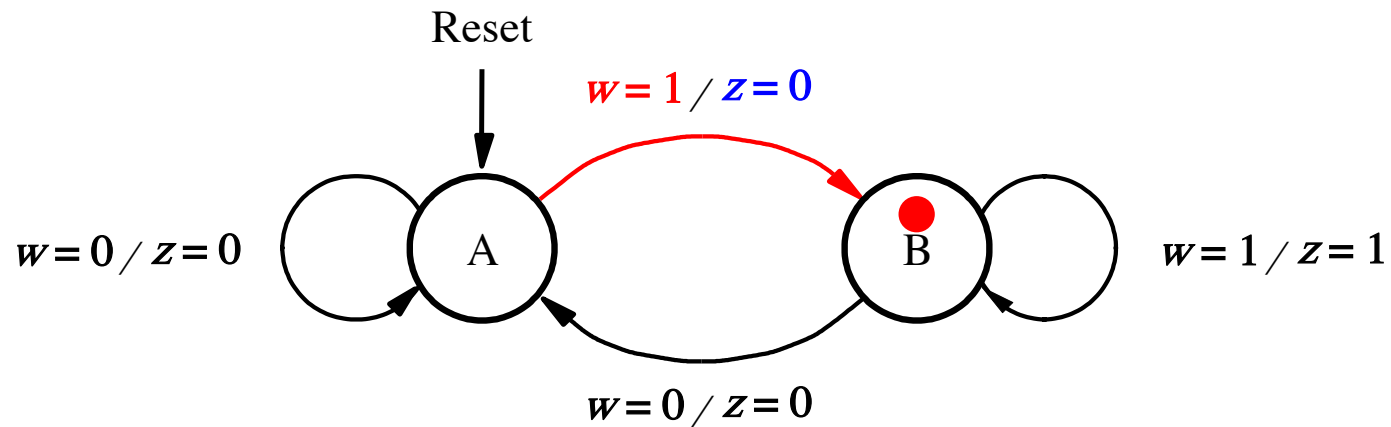


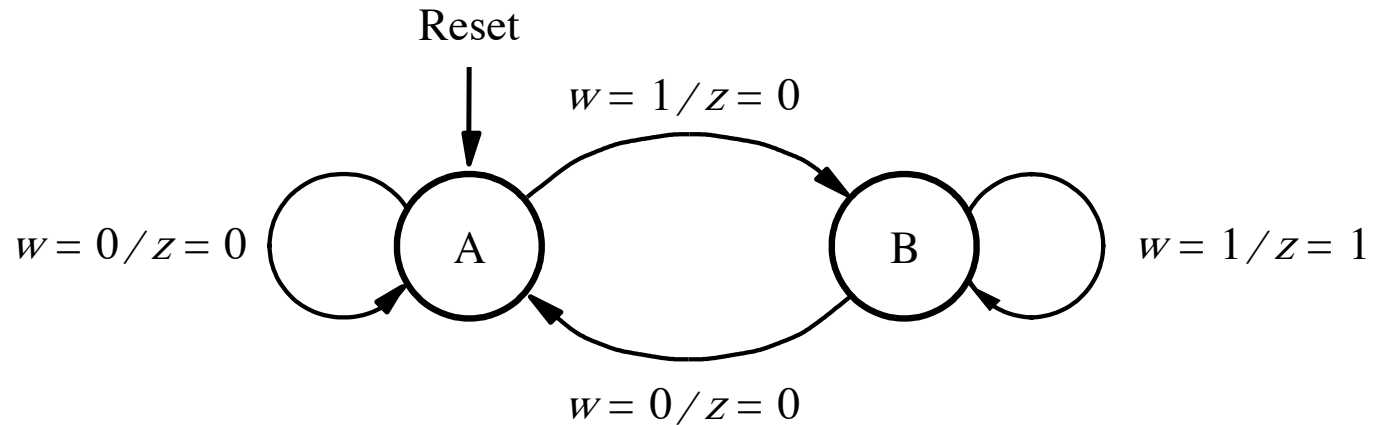Now Let's Do the State Table for this FSM



Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A				
B				

 Now Let's Do the State Table for this FSM



Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

The State Table for this FSM

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Let's Do the State-assigned Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
A 0				
B 1				

Let's Do the State-assigned Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

The State-assigned Table

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

The State-assigned Table


	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

$$Y = D = w \quad z = wy$$

The State-assigned Table


	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

$$Y = D = w \quad z = wy$$

 


This assumes D flip-flop

Circuit Implementation of the FSM

 


$$Y = D = w \quad z = wy$$

Circuit & Timing Diagram

 

(a) Circuit

 


(b) Timing diagram

[Figure 6.26 from the textbook]


What if we wanted the output signal to be delayed by 1 clock cycle?

Circuit Implementation of the Modified FSM

 

[Figure 6.27a from the textbook]

 Circuit Implementation of the Modified FSM




This flip-flop delays the output signal by one clock cycle

We Have Seen This Diagram Before


$$Y_1(w, y_2, y_1) = w$$

$$Y_2(w, y_2, y_1) = wy_1$$


$$z(y_2, y_1) = y_2$$

 


Circuit & Timing Diagram

 


(a) Circuit

 

 
The general form of a synchronous sequential circuit




Moore Type

 


Mealy Type

 



Moore

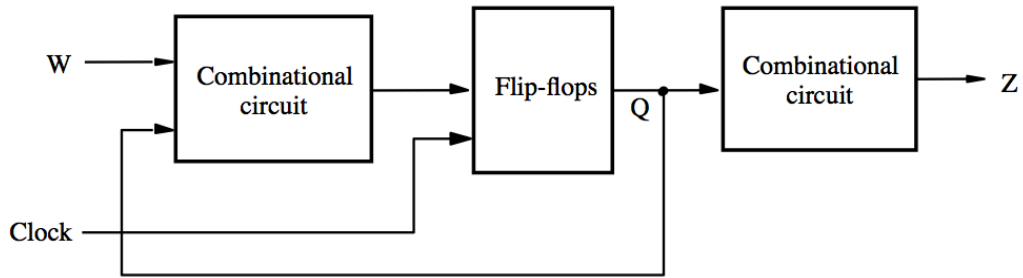



Mealy

 


Moore

  


Mealy

  

Mealy

 


Moore

 


Notice that the output of the Moore machine is delayed by one clock cycle

Mealy

 

Moore

 

Questions?

THE END