



**3. Even Numbers (3 x 5p each = 15p)**

**a) Draw the K-map for the Boolean function  $f(a,b,c,d)$  that is described as follows. The output of this function is 1 if the decimal representation of the 4-bit binary number  $abcd$  is a non-zero even number (i.e., 0 is treated as odd). Otherwise, the output is equal to 0. (5p)**

**b) Use the K-map to derive the minimum-cost POS expression for this function. (5p)**

**c) Draw the circuit diagram for this function. Label all inputs and outputs. (5p)**

**4. Basic Circuits (3 x 5p each = 15p).**

**Draw the wiring diagrams for the circuits below. Clearly label all inputs and outputs.**

**(a) Half-adder.**

**(b) XNOR gate, implemented using only AND, OR, and NOT gates.**

**(c) 8-to-1 multiplexer implemented with two 4-to-1 multiplexers and one 2-to-1 multiplexer.**

**5. Number Conversions (3p + 4p + 4p + 4p = 15p)**

**(a) Convert  $95_{10}$  to binary.**

**(b) Convert  $5735_8$  to hexadecimal.**

**(c) Write down the 32-bit floating point representation (in IEEE 754 format) for  $6.5$**

**(d) Convert  $-49_{10}$  to an 8-bit binary number in 2's complement representation.**

**6. Comparison Logic ( 3 x 5p = 15p)**

**Given two Boolean variables x and y (i.e., both are 1-bit) your task is to draw truth tables and circuit diagrams for functions that perform the comparisons listed below.**

**a) Equal: draw the truth table and the circuit for a function f that outputs a 1 if  $x=y$ .**

**b) Not equal: draw the truth table and the circuit for a function f that outputs a 1 if  $x \neq y$ .**

**c) Greater: draw the truth table and the circuit for a function f that outputs a 1 if  $x>y$ .**

**7. Code Converter (8p + 7p = 15p)**

**A code converter has two inputs  $S_1$  and  $S_0$  and four outputs  $F_3$ ,  $F_2$ ,  $F_1$ , and  $F_0$ . The equations for the outputs are:**

$$F_3 = F_0 = \Sigma m(0, 1, 3)$$

$$F_2 = F_1 = (\overline{S_1} \& S_0) \mid (S_1 \& \overline{S_0})$$


**a) Draw the truth table for this code converter, showing the 2 inputs and 4 outputs. (8p)**

**b) Implement this code converter using a minimal number of 2-to-1 multiplexers and no other logic gates. Assume that the input signals are available only in their non-inverted form, along with the constants 0 and 1. Label all inputs, outputs, and pins of your circuit. (7p)**


**8. Alternative Implementation (5 x 2p each = 10p)**

Complete the circuits below by drawing any additional logic gates, components, or wires to implement the specified flip-flop given another flop-flop type. Label all inputs and outputs.

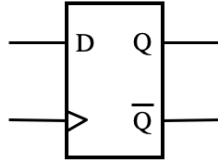
a) Implement a T Flip-Flop using a D Flip-Flop.



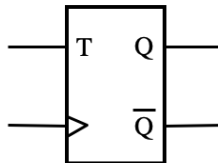
b) Implement a D Flip-Flop using a T Flip-Flop.



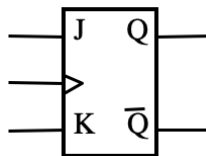
c) Implement a T Flip-Flop using a JK Flip-Flop.



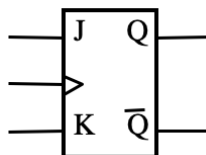d) Implement a D Flip-Flop using a JK Flip-Flop.



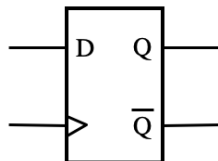e) Implement a JK Flip-Flop using a D Flip-Flop.



**9. Up and Down Counter (10p + 5p = 15p)**

**(a) Use four T Flip-Flops and any other logical gates or high-level components that are needed to implement a 4-bit asynchronous counter that can count either up or down. The counting direction is determined by one of the inputs to this circuit that is called CD. If this input is equal to 0 then the counter counts down. Alternatively, if  $CD = 1$ , then the counter counts up. Draw your circuit below. Clearly label all inputs, outputs, and pins.**

**(b) Explain the correct solution in 3-4 sentences.**



**10. Arithmetic Circuit (10p + 5p = 15p)**

**(a) Let  $A=A_2 A_1 A_0$  and  $B=B_2 B_1 B_0$  be two 3-bit binary numbers in 2's complement representation. You are given three full-adders, one NOT gate, and seven XOR gates. Your task is to design a circuit that can perform two different arithmetic operations:  $A-B$  and  $B-A$ . The operation is selected by one of the inputs to this circuit that is called  $S$ . When  $S=0$  the 3-bit result  $R= R_2 R_1 R_0$  is equal to  $A-B$ . Alternatively, when  $S=1$  the result is  $B-A$ . The circuit must also detect if an overflow has occurred. Draw the wiring diagram for your circuit below. Clearly label all inputs, outputs, and pins.**

**(b) Explain the correct solution in 3-4 sentences.**

<b>Question</b>	<b>Max</b>	<b>Score</b>
1. True/False	10	
2. Venn Diagram	5	
3. Even Numbers	15	
4. Basic Circuits	15	
5. Number Conversions	15	
6. Comparison Logic	15	
7. Code Converter	15	
8. Alternative Implementation	10	
9. Up and Down Counter	15	
10. Arithmetic Circuit	15	
<b>TOTAL:</b>	<b>130</b>	