



# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Code Converters

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **HW 7 is out**
- **It is due on Monday (Oct 12) @ 4pm**

# **Quick Review**

# Decoders


# 2-to-4 Decoder (Definition)

- Has two inputs:  $w_1$  and  $w_0$
- Has four outputs:  $y_0$  ,  $y_1$  ,  $y_2$  , and  $y_3$
- If  $w_1=0$  and  $w_0=0$ , then the output  $y_0$  is set to 1
- If  $w_1=0$  and  $w_0=1$ , then the output  $y_1$  is set to 1
- If  $w_1=1$  and  $w_0=0$ , then the output  $y_2$  is set to 1
- If  $w_1=1$  and  $w_0=1$ , then the output  $y_3$  is set to 1
- Only one output is set to 1. All others are set to 0.

# Truth Table and Graphical Symbol for a 2-to-4 Decoder

$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a) Truth table

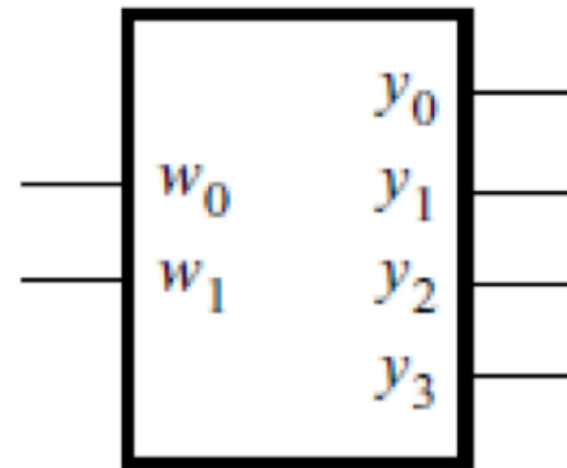


(b) Graphical symbol

# Truth Table and Graphical Symbol for a 2-to-4 Decoder

$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

The outputs are “one-hot” encoded


(a) Truth table

 

(b) Graphical symbol




# Truth Logic Circuit for a 2-to-4 Decoder

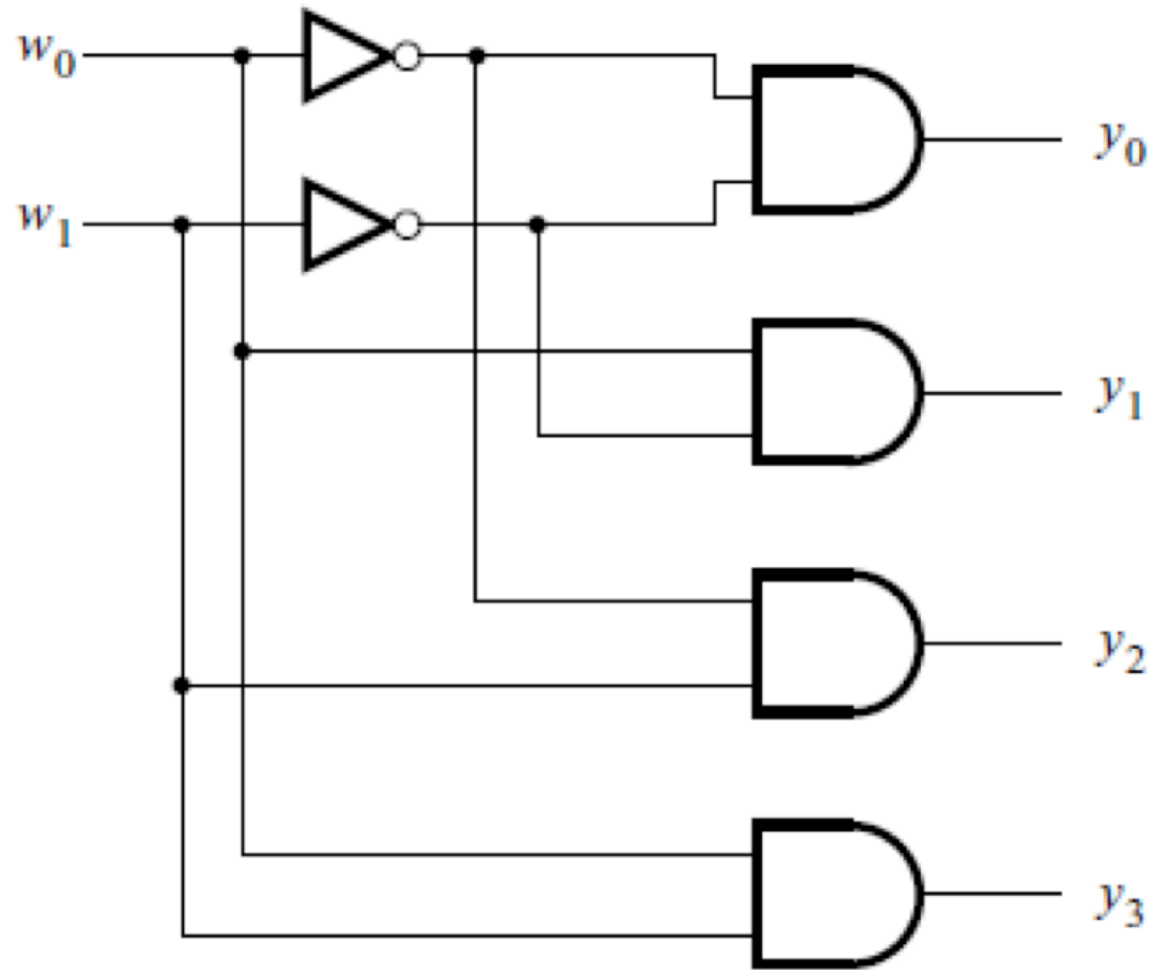

[ Figure 4.13c from the textbook ]

# Adding an Enable Input

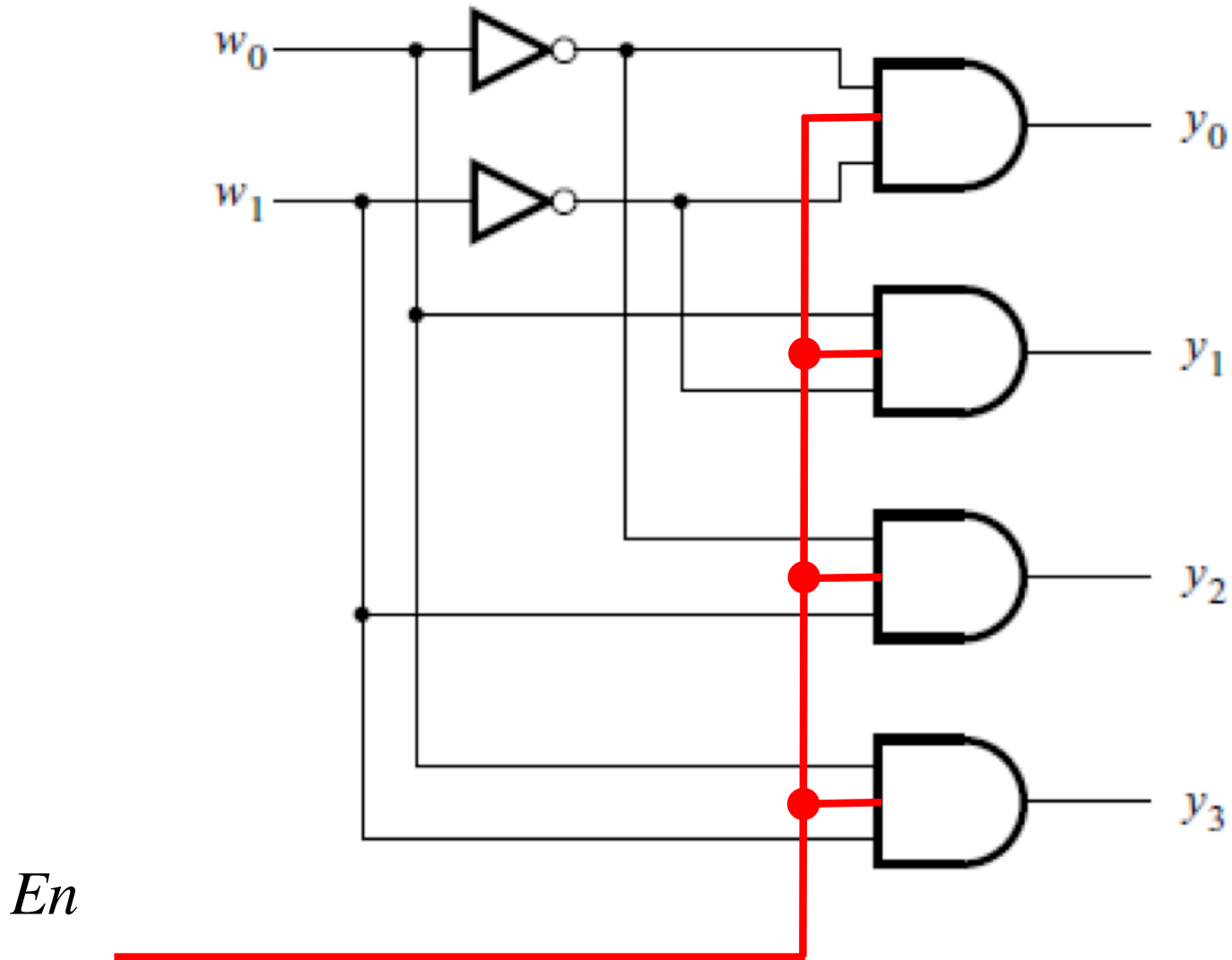


[ Figure 4.13c from the textbook ]

# Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

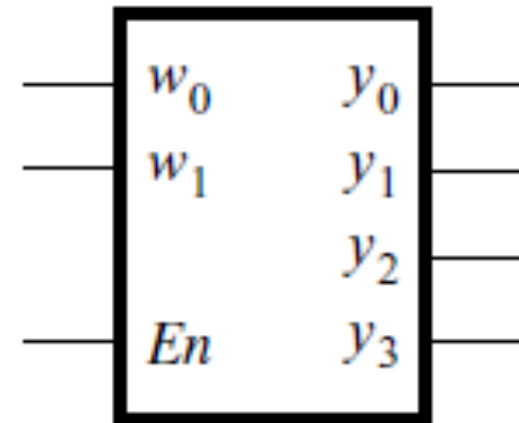


(b) Graphical symbol

# Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0


(a) Truth table

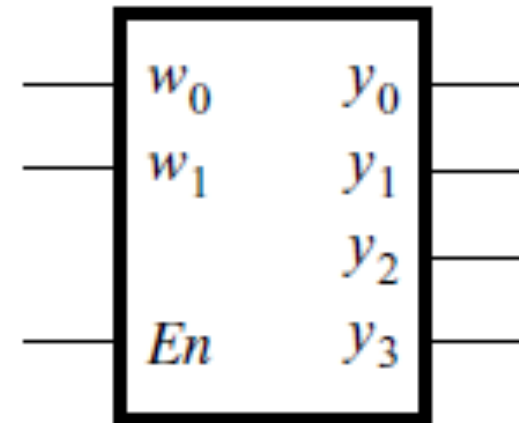

(b) Graphical symbol

x indicates that it does not matter what the value of these variable is for this row of the truth table
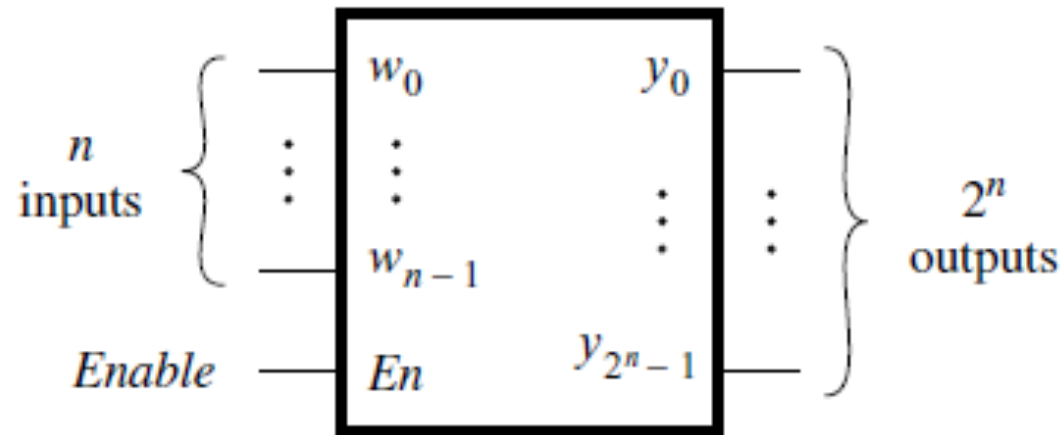
# Graphical Symbol for a Binary $n$ -to- $2^n$ Decoder with an Enable Input




(d) An  $n$ -to- $2^n$  decoder


A binary decoder with  $n$  inputs has  $2^n$  outputs

The outputs of an enabled binary decoder are “one-hot” encoded, meaning that only a single bit is set to 1, i.e., it is *hot*.
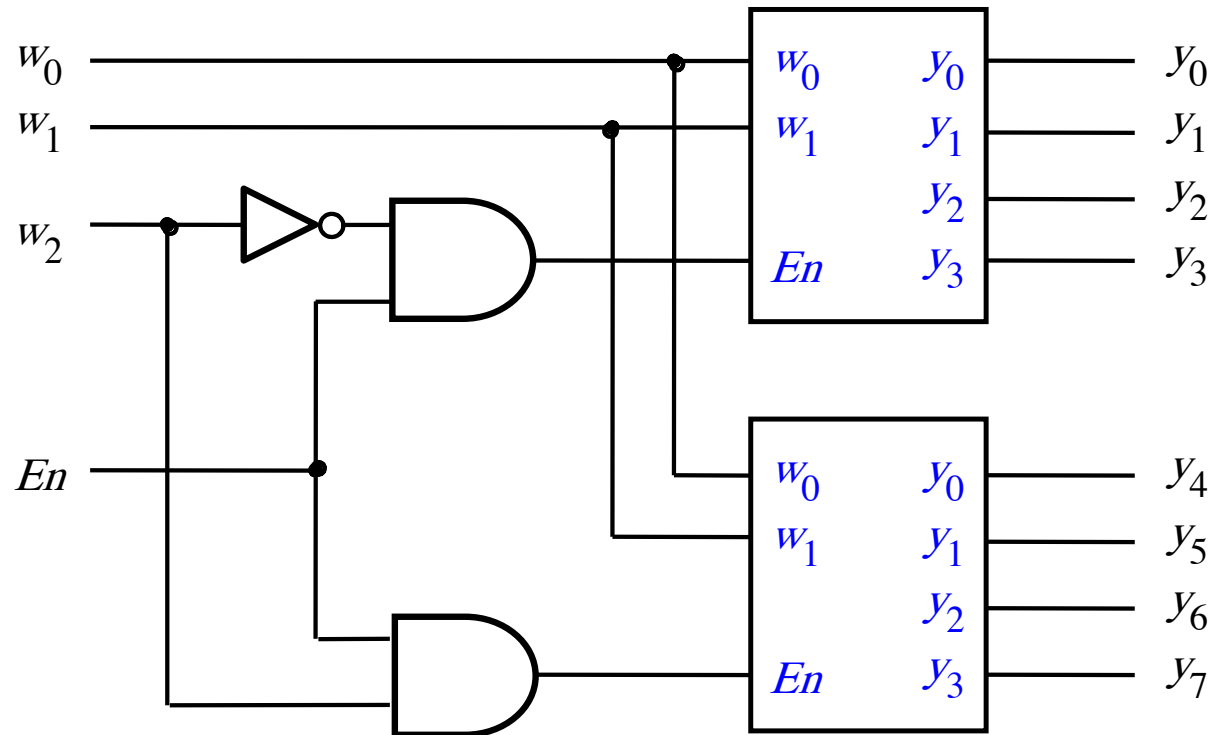
# A 3-to-8 decoder using two 2-to-4 decoders




# A 3-to-8 decoder using two 2-to-4 decoders

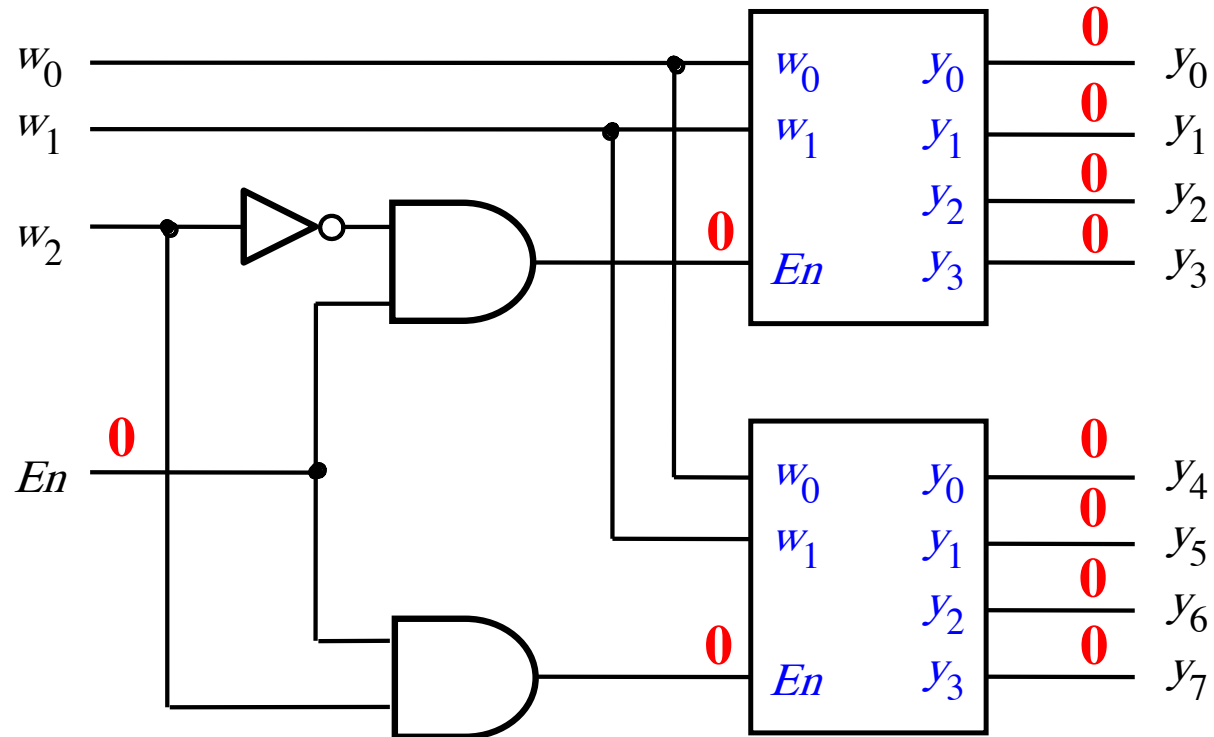


[ Figure 4.15 from the textbook ]
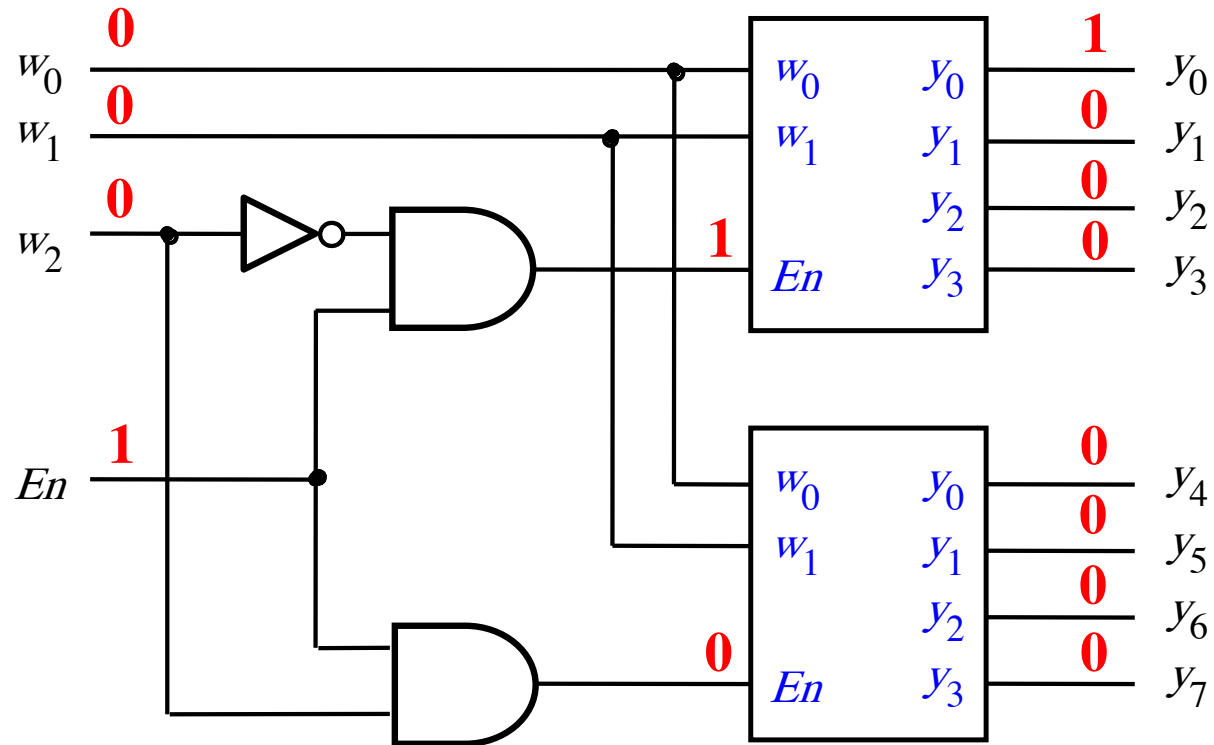
# A 3-to-8 decoder using two 2-to-4 decoders






 
# A 3-to-8 decoder using two 2-to-4 decoders



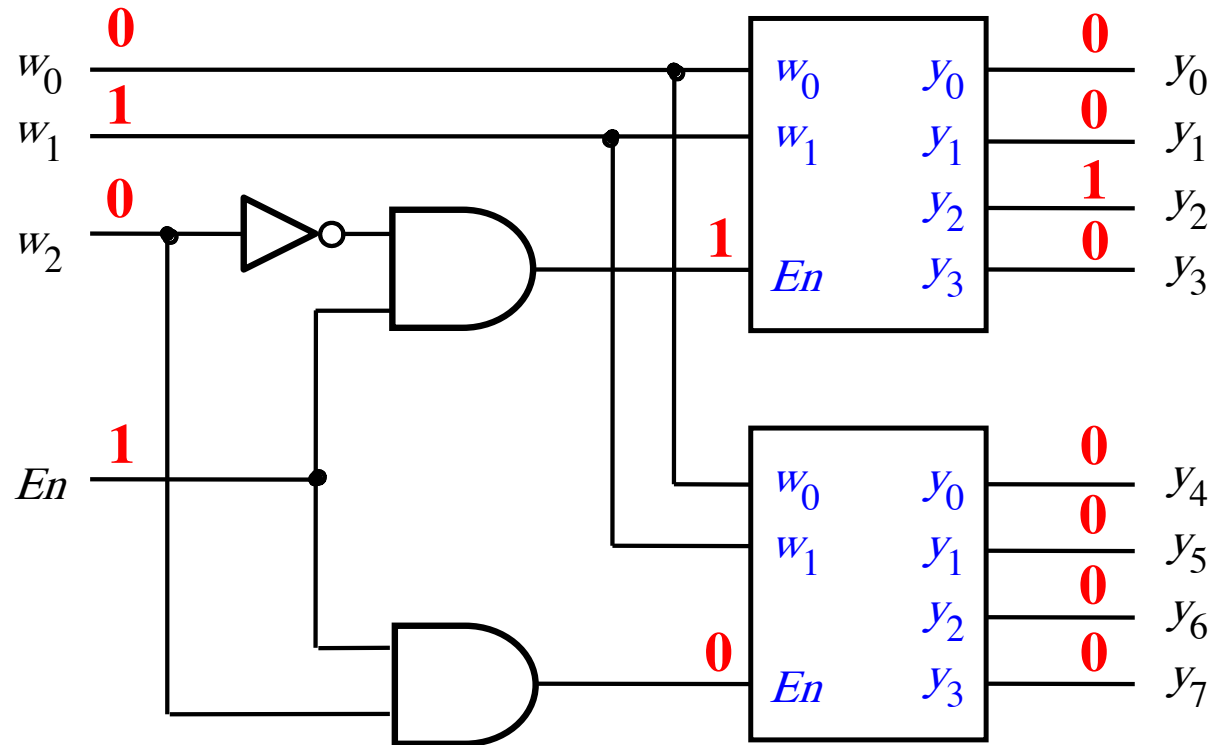
# A 3-to-8 decoder using two 2-to-4 decoders



 
# A 3-to-8 decoder using two 2-to-4 decoders


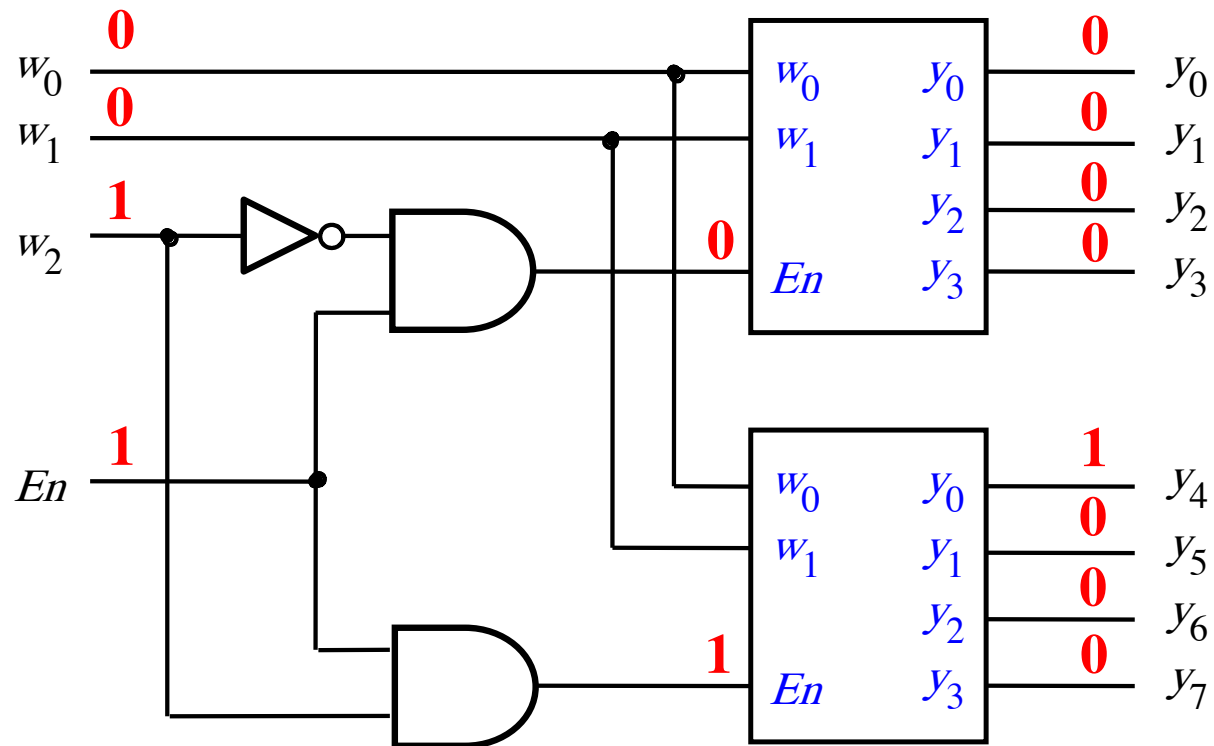
# A 3-to-8 decoder using two 2-to-4 decoders




# A 3-to-8 decoder using two 2-to-4 decoders

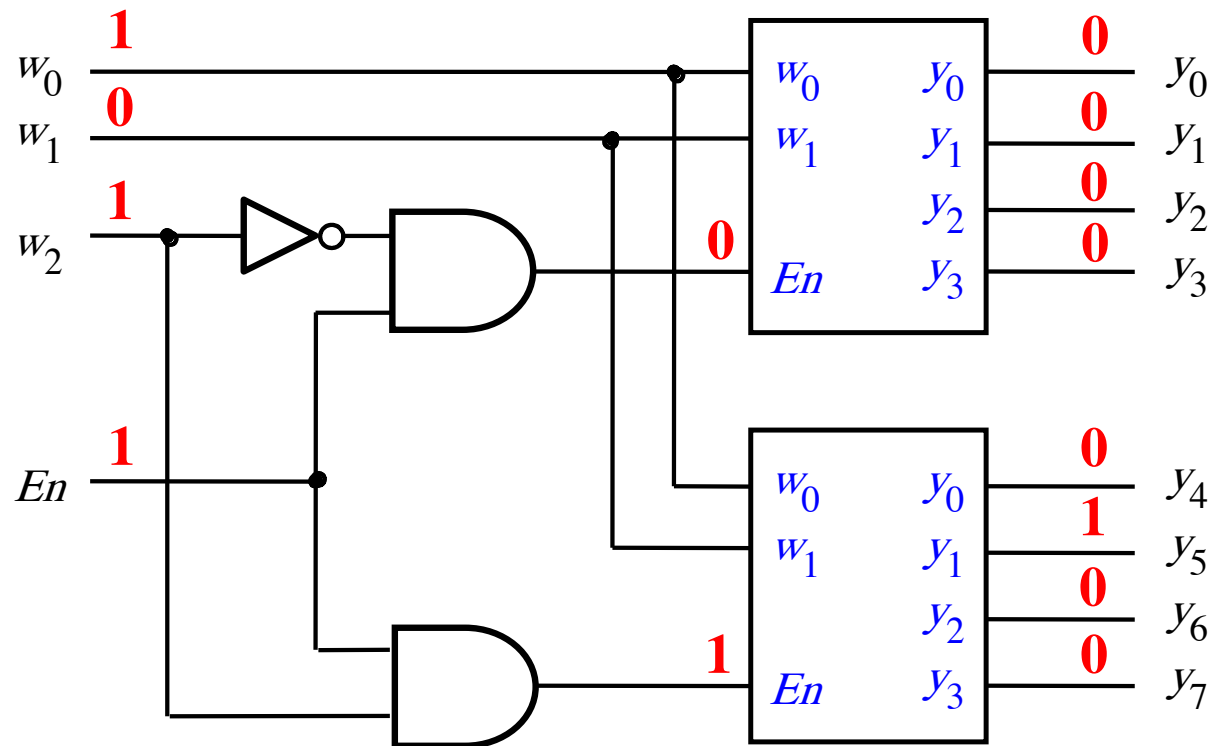


[ Figure 4.15 from the textbook ]
 
# A 3-to-8 decoder using two 2-to-4 decoders




# A 3-to-8 decoder using two 2-to-4 decoders

 

[ Figure 4.15 from the textbook ]



# A 4-to-16 decoder built using a decoder tree

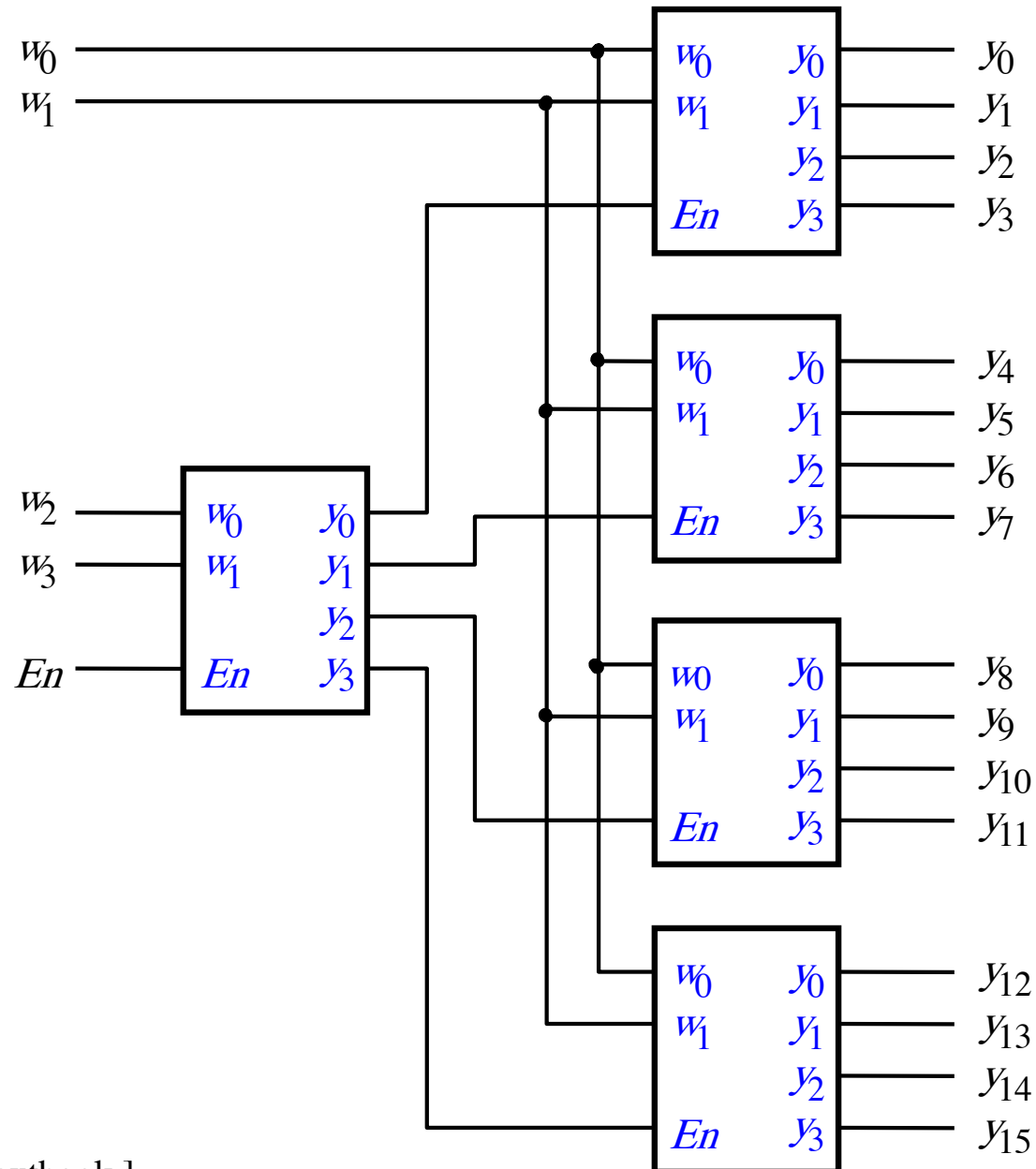


[ Figure 4.16 from the textbook ]




# Let's build a 5-to-32 decoder

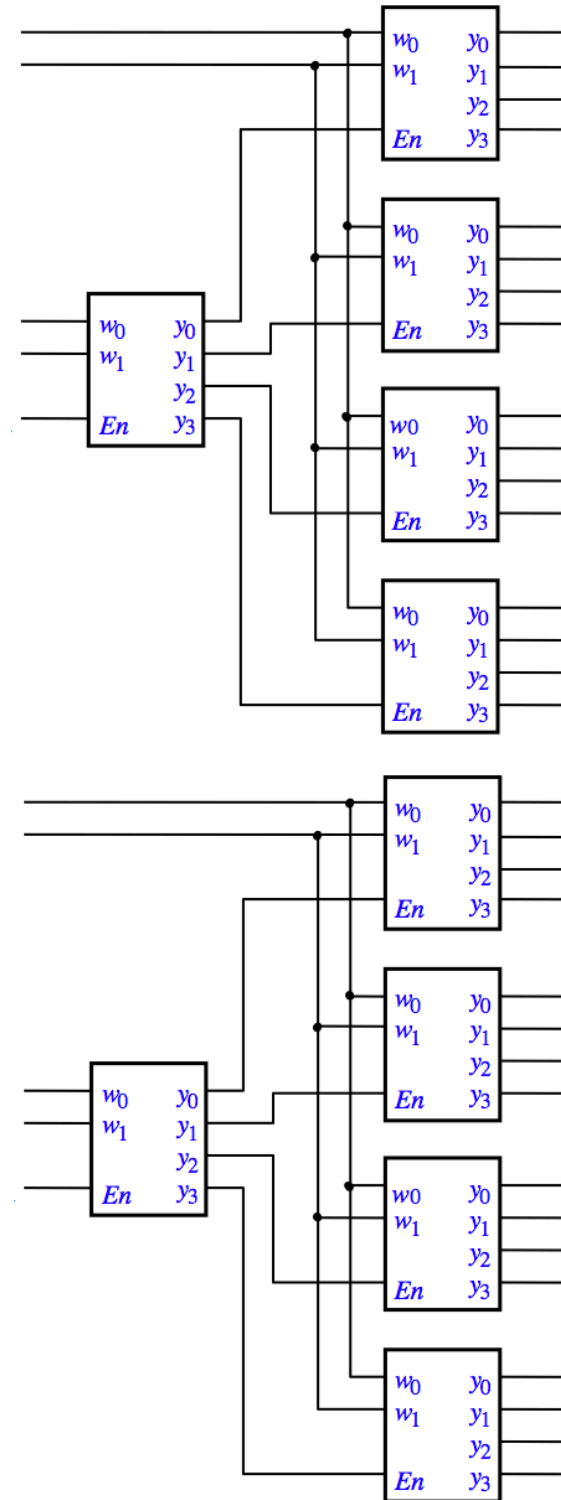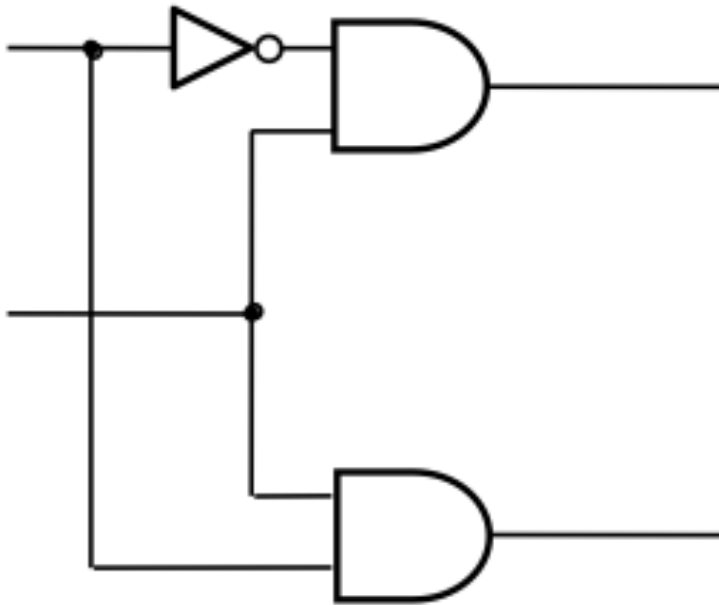

# Let's build a 5-to-32 decoder

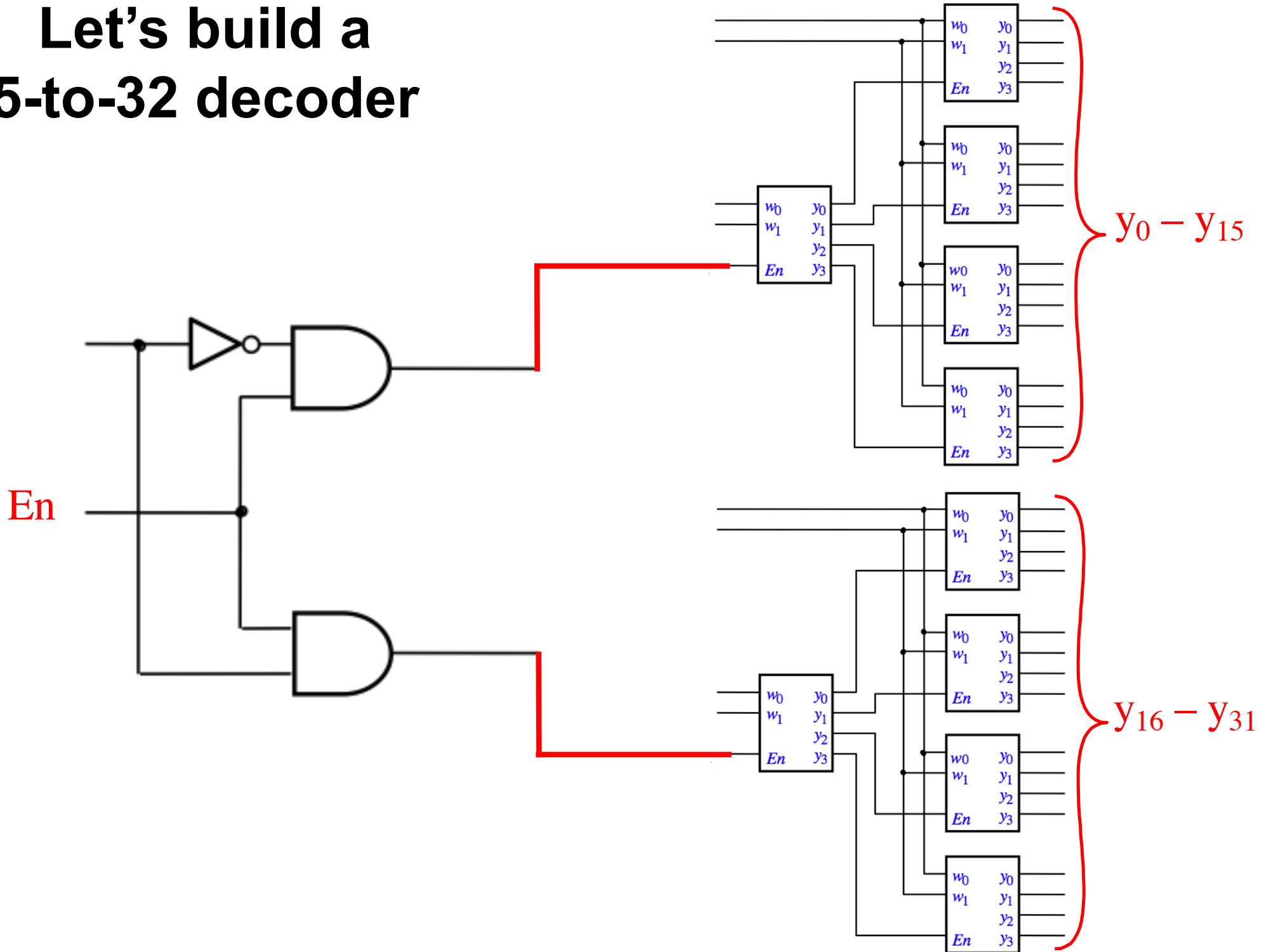

# Let's build a 5-to-32 decoder

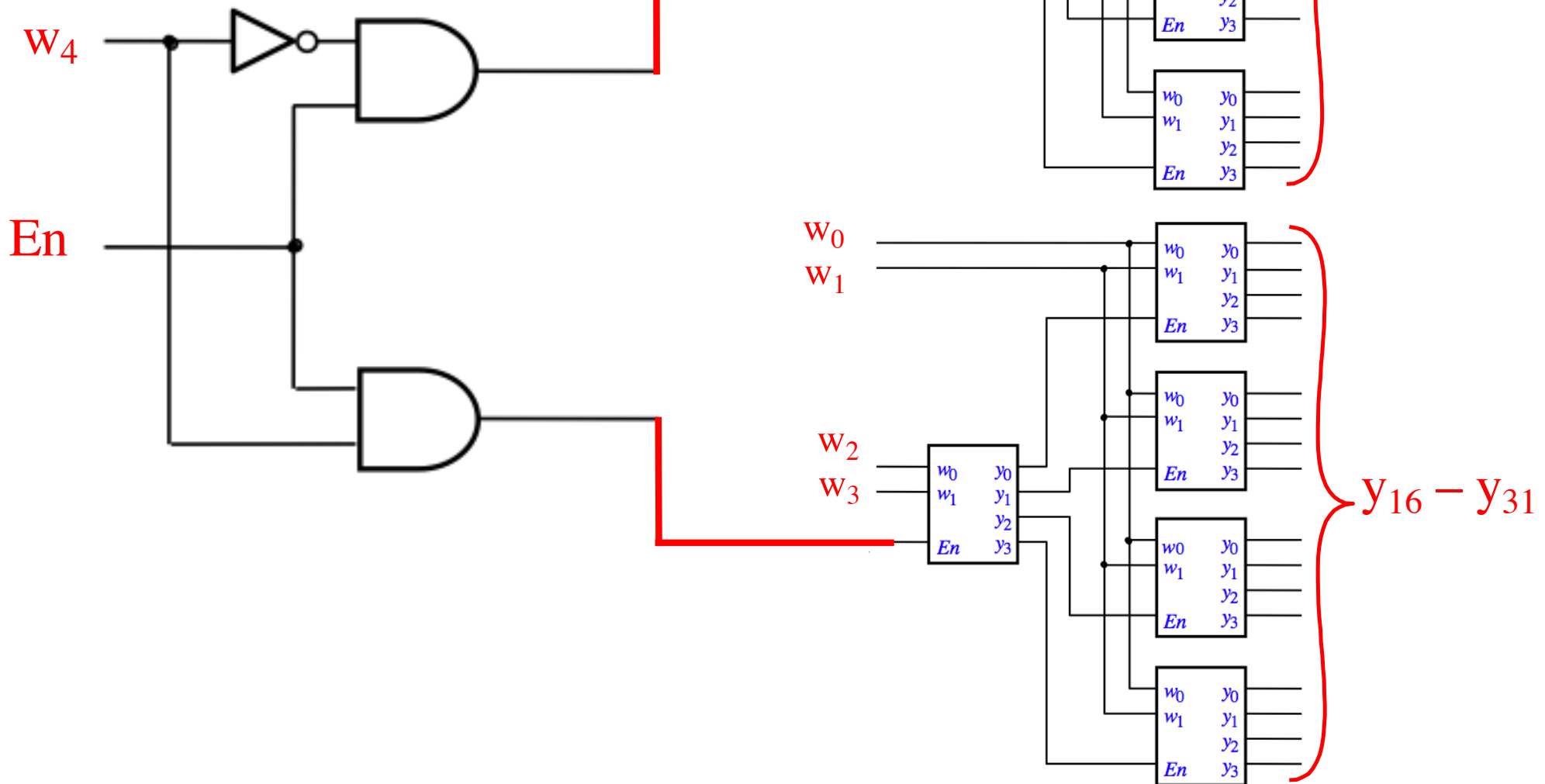


# Demultiplexers

# 1-to-4 Demultiplexer (Definition)


- Has one data input line:  $D$
- Has two output select lines:  $w_1$  and  $w_0$
- Has four outputs:  $y_0$  ,  $y_1$  ,  $y_2$  , and  $y_3$
- If  $w_1=0$  and  $w_0=0$ , then the output  $y_0$  is set to  $D$
- If  $w_1=0$  and  $w_0=1$ , then the output  $y_1$  is set to  $D$
- If  $w_1=1$  and  $w_0=0$ , then the output  $y_2$  is set to  $D$
- If  $w_1=1$  and  $w_0=1$ , then the output  $y_3$  is set to  $D$
- Only one output is set to  $D$ . All others are set to 0.
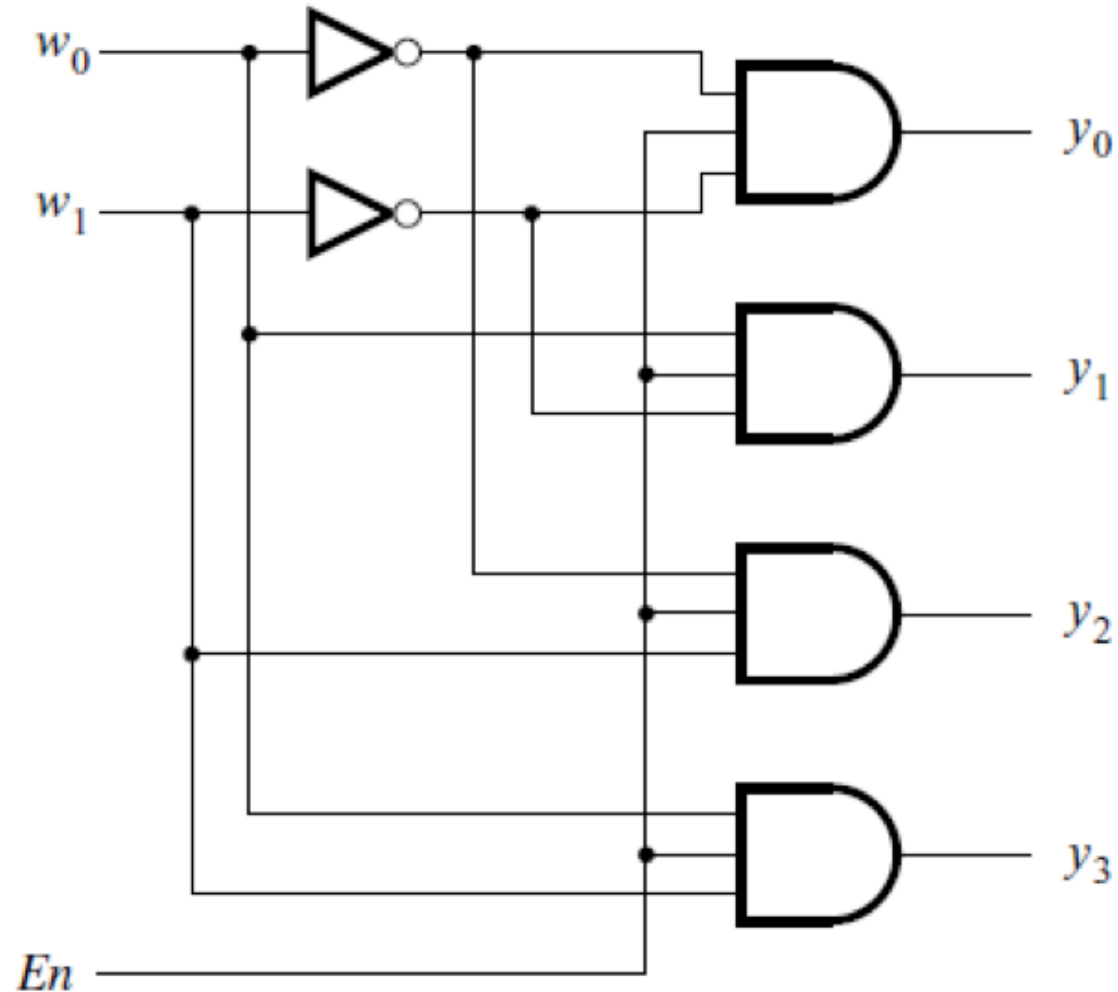
# A 1-to-4 demultiplexer built with a 2-to-4 decoder



# A 1-to-4 demultiplexer built with a 2-to-4 decoder

output  
select  
lines

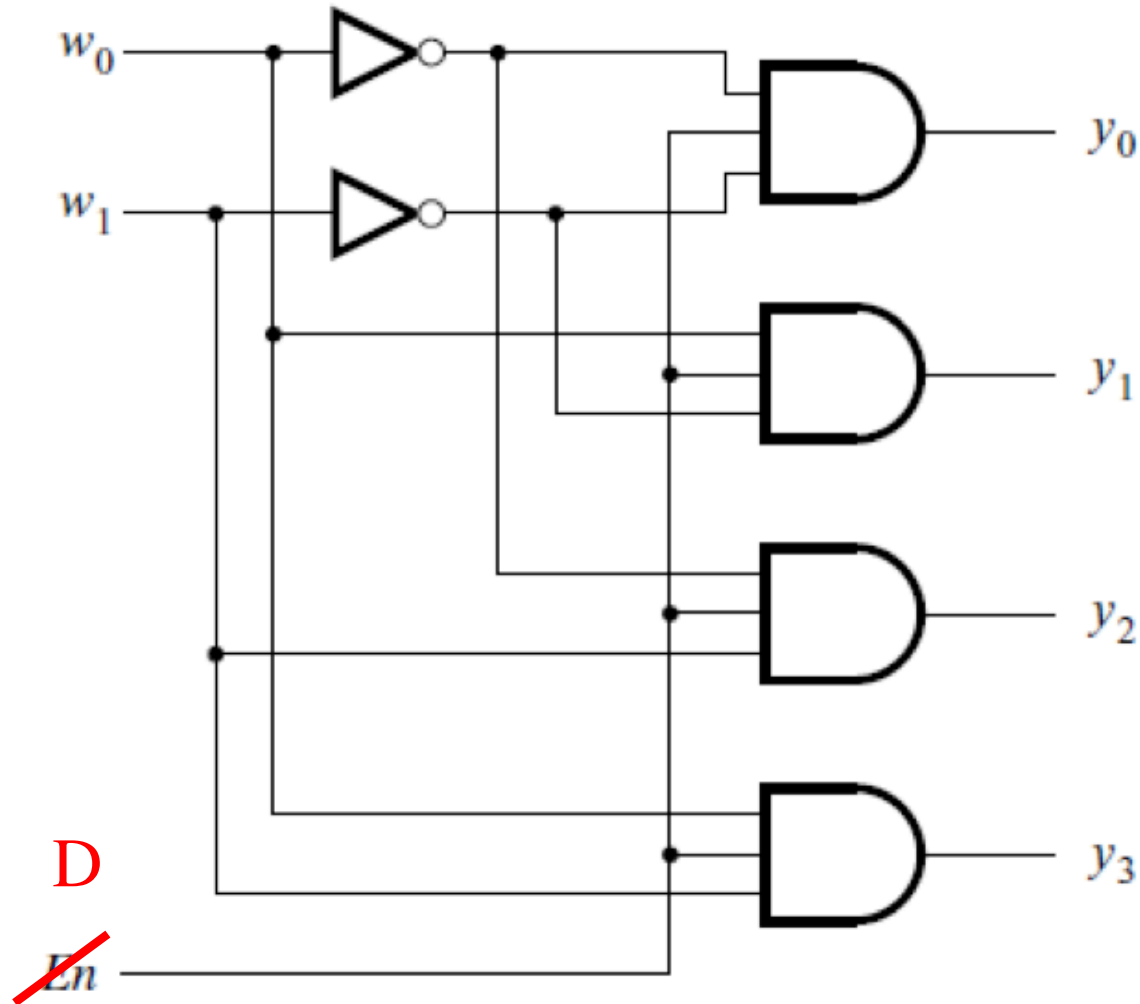


the  
four  
output  
lines

data  
input  
line

# **Multiplexers (Implemented with Decoders)**


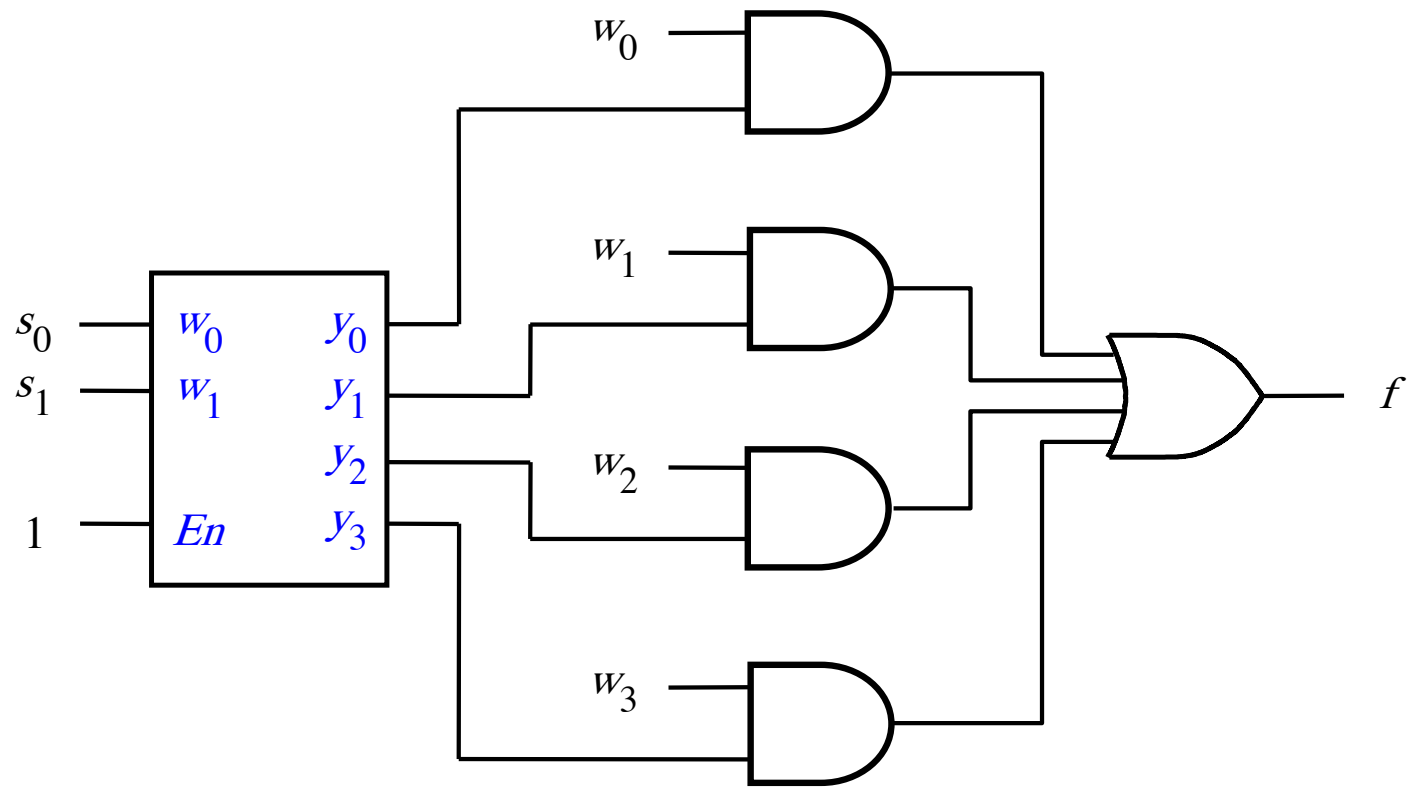
# A 4-to-1 multiplexer built using a 2-to-4 decoder



# Encoders

# Binary Encoders

# 4-to-2 Binary Encoder (Definition)

- Has four inputs:  $w_3$  ,  $w_2$  ,  $w_1$  , and  $w_0$
- Has two outputs:  $y_1$  and  $y_0$
- Only one input is set to 1 (“one-hot” encoded).  
All others are set to 0.
- If  $w_0=1$  then  $y_1=0$  and  $y_0=0$
- If  $w_1=1$  then  $y_1=0$  and  $y_0=1$
- If  $w_2=1$  then  $y_1=1$  and  $y_0=0$
- If  $w_3=1$  then  $y_1=1$  and  $y_0=1$

# Truth table for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


# Truth table for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

The inputs are “one-hot” encoded


# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

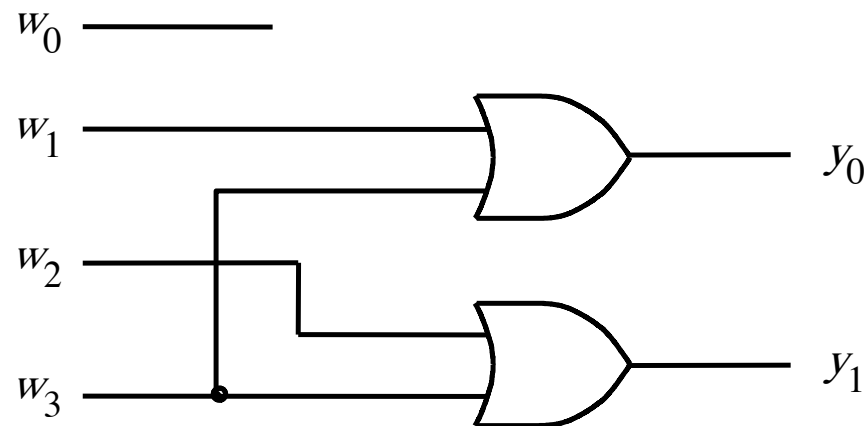

# Circuit for a 4-to-2 binary encoder


$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 




# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

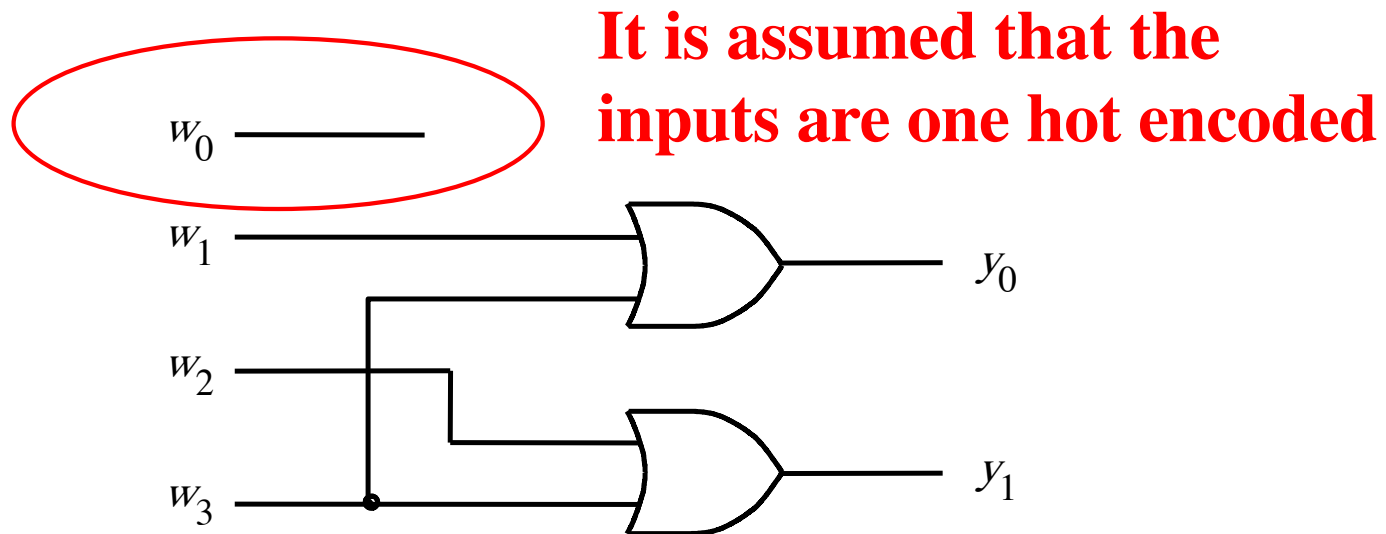

# Circuit for a 4-to-2 binary encoder


$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

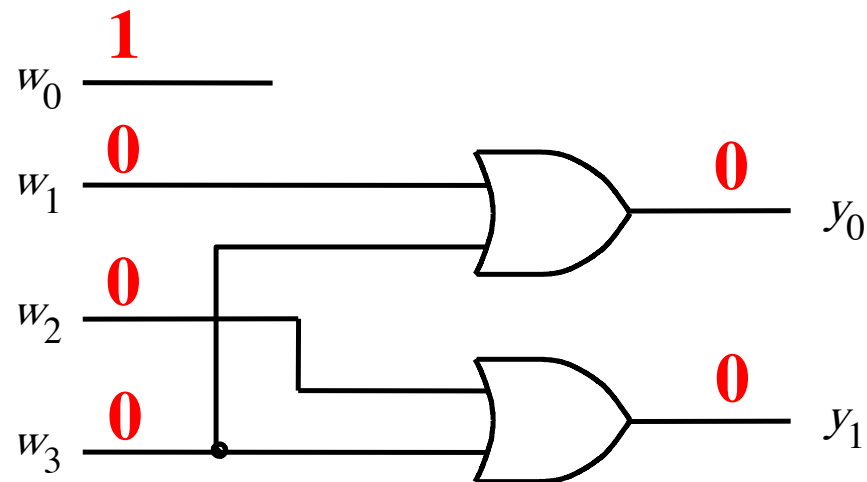

# Circuit for a 4-to-2 binary encoder


$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

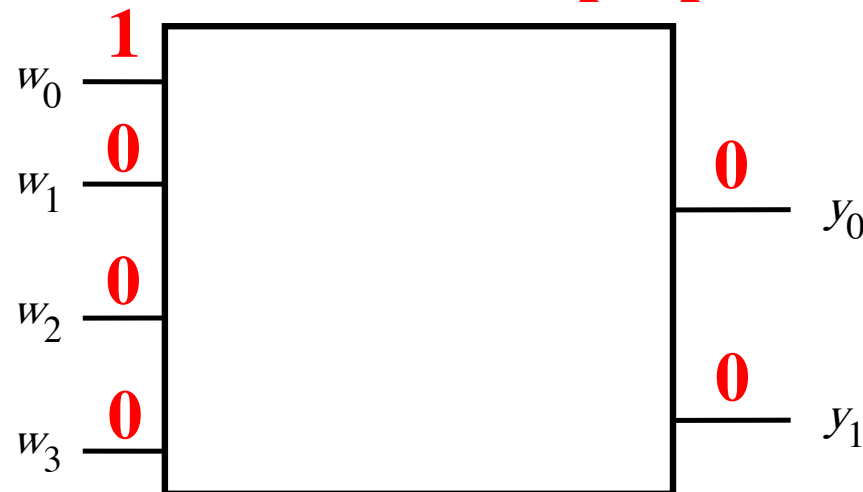**As this level of abstraction we need that  $w_0$  input for this to be a proper 4-to-2 binary encoder.**




# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

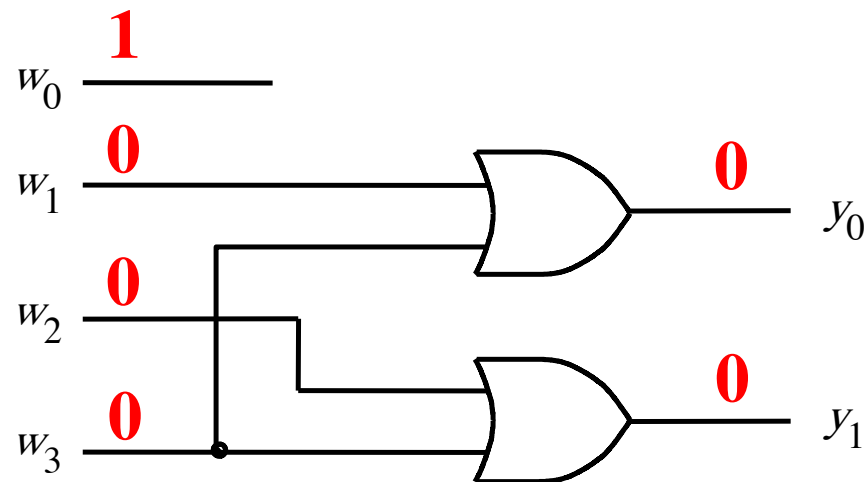


# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

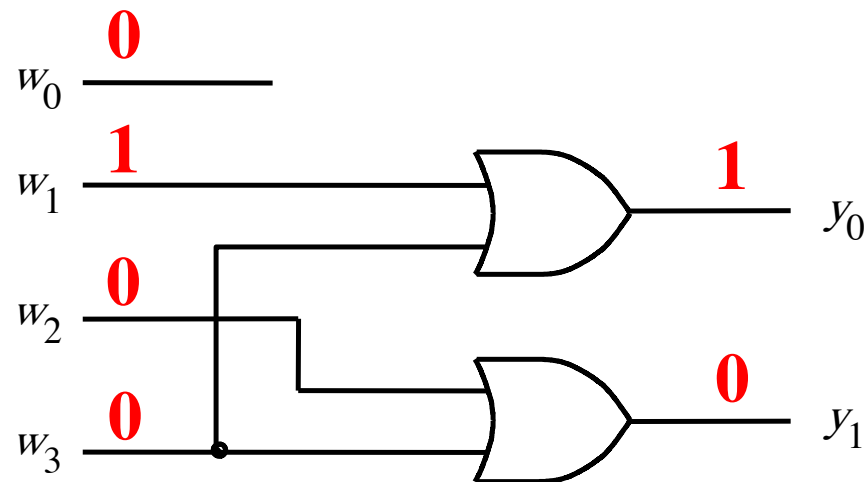

# Circuit for a 4-to-2 binary encoder


$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

[ Figure 4.19 from the textbook ]

# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

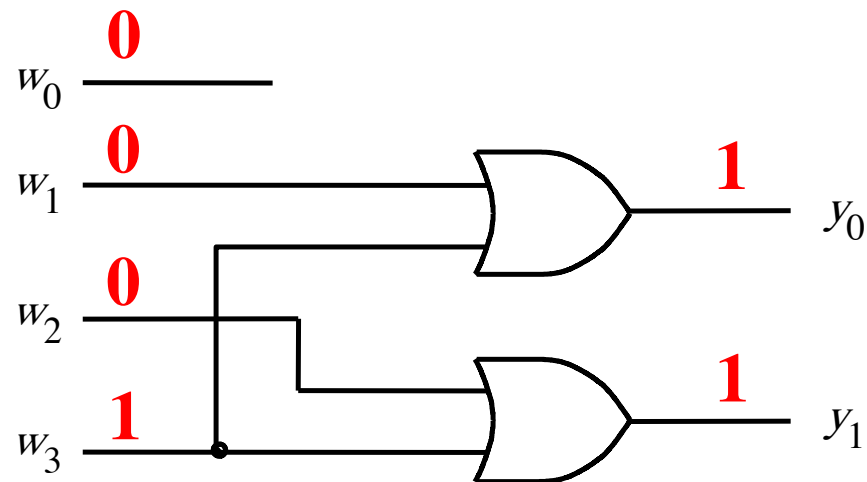

# Expressions for 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	0		
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1		
0	1	0	0	1	0
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0	1	1
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1



# Expressions for 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	0	d	d
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	d	d
0	1	0	0	1	0
0	1	0	1	d	d
0	1	1	0	d	d
0	1	1	1	d	d
1	0	0	0	1	1
1	0	0	1	d	d
1	0	1	0	d	d
1	0	1	1	d	d
1	1	0	0	d	d
1	1	0	1	d	d
1	1	1	0	d	d
1	1	1	1	d	d


$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

# Expressions for 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	0	d	d
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	d	d
0	1	0	0	1	0
0	1	0	1	d	d
0	1	1	0	d	d
0	1	1	1	d	d
1	0	0	0	1	1
1	0	0	1	d	d
1	0	1	0	d	d
1	0	1	1	d	d
1	1	0	0	d	d
1	1	0	1	d	d
1	1	1	0	d	d
1	1	1	1	d	d

		$w_3 w_2$	00	01	11	10
$w_1 w_0$	00	d	0	d	1	
01	0	d	d	d		
11	d	d	d	d		
10	1	d	d	d		

$$y_0 = (w_1 + w_3)$$

 


# Expressions for 4-to-2 binary encoder


$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	0	d	d
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	d	d
0	1	0	0	1	0
0	1	0	1	d	d
0	1	1	0	d	d
0	1	1	1	d	d
1	0	0	0	1	1
1	0	0	1	d	d
1	0	1	0	d	d
1	0	1	1	d	d
1	1	0	0	d	d
1	1	0	1	d	d
1	1	1	0	d	d
1	1	1	1	d	d

$w_3 w_2$	$w_1 w_0$	00	01	11	10
00	00	d	1	d	1
01	00	0	d	d	d
11	00	d	d	d	d
10	00	0	d	d	d

$$y_1 = (w_3 + w_2)$$

 

# A $2^n$ -to- $n$ binary encoder

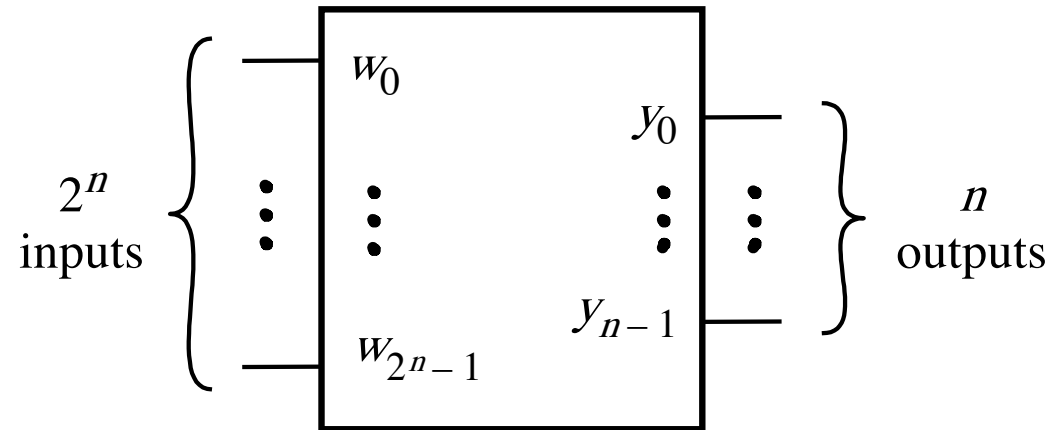

# Priority Encoders

# Truth table for a 4-to-2 priority encoder (abbreviated version)

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

# Truth table for a 4-to-2 priority encoder (abbreviated version)

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

# Truth table for a 4-to-2 priority encoder

	$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0 0 0 0	0	0	0	0	d	d	0
0 0 0 1	0	0	0	1	0	0	1
0 0 1 x	0	0	1	0	0	1	1
	0	0	1	1	0	1	1
0 1 x x	0	1	0	0	1	0	1
	0	1	0	1	1	0	1
	0	1	1	0	1	0	1
	0	1	1	1	1	0	1
1 x x x	1	0	0	0	1	1	1
	1	0	0	1	1	1	1
	1	0	1	0	1	1	1
	1	0	1	1	1	1	1
	1	1	0	0	1	1	1
	1	1	0	1	1	1	1
	1	1	1	0	1	1	1
	1	1	1	1	1	1	1



# Expressions for 4-to-2 priority encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

		$w_3 w_2$			
$w_1 w_0$		00	01	11	10
	00	d	1	1	1
01	0	1	1	1	
11	0	1	1	1	
10	0	1	1	1	

$$y_1 = w_3 + w_2$$

# Expressions for 4-to-2 priority encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

		$w_3 w_2$			
$w_1 w_0$		00	01	11	10
00		d	0	1	1
01		0	0	1	1
11		1	0	1	1
10		1	0	1	1

$$y_0 = w_3 + w_1 \overline{w_2}$$


# Expressions for 4-to-2 priority encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

		$w_3 w_2$			
		00	01	11	10
$w_1 w_0$	00	0	1	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$$Z = w_3 + w_2 + w_1 + w_0$$
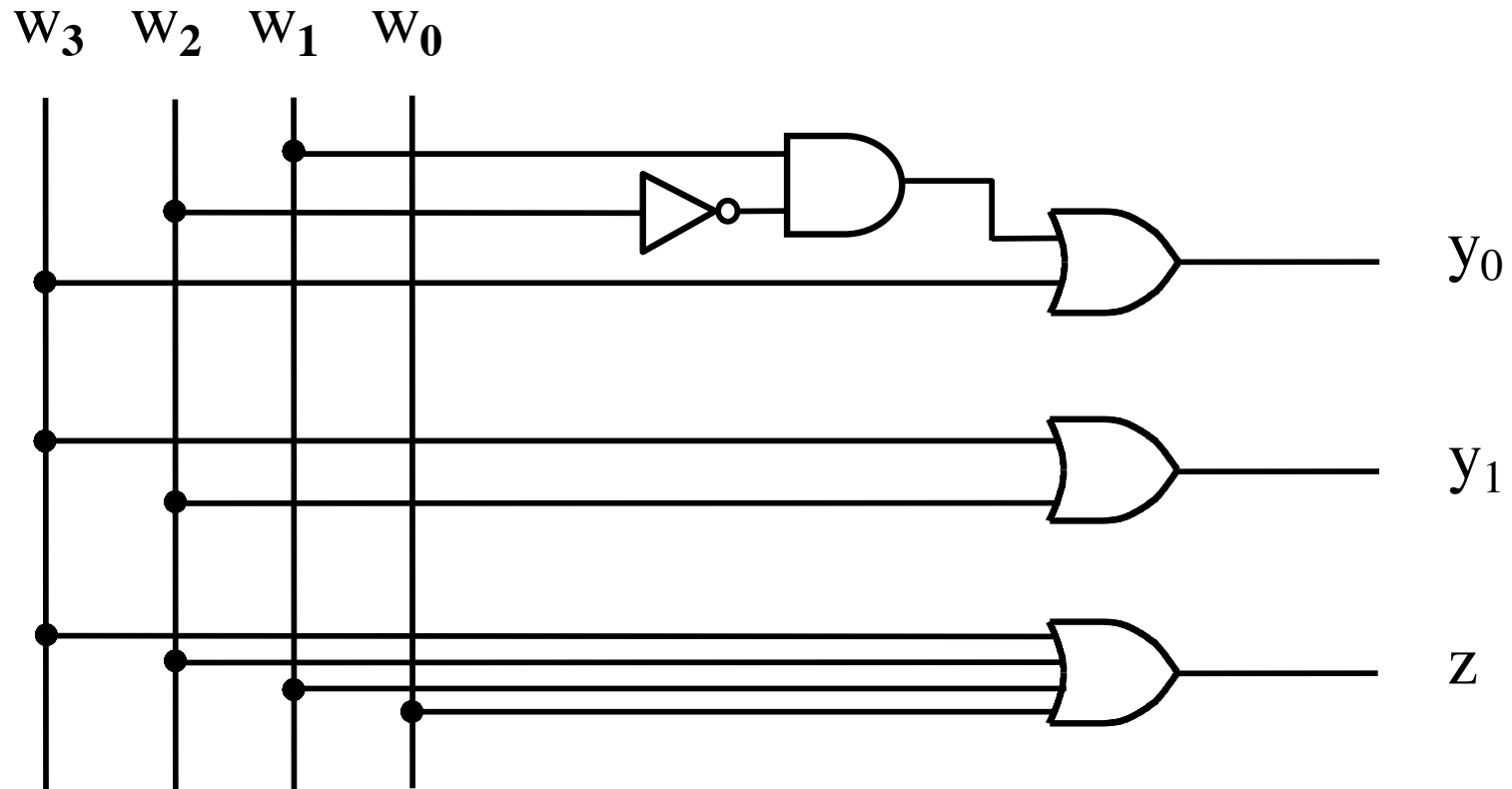
# Circuit for the 4-to-2 priority encoder



# The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

# The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

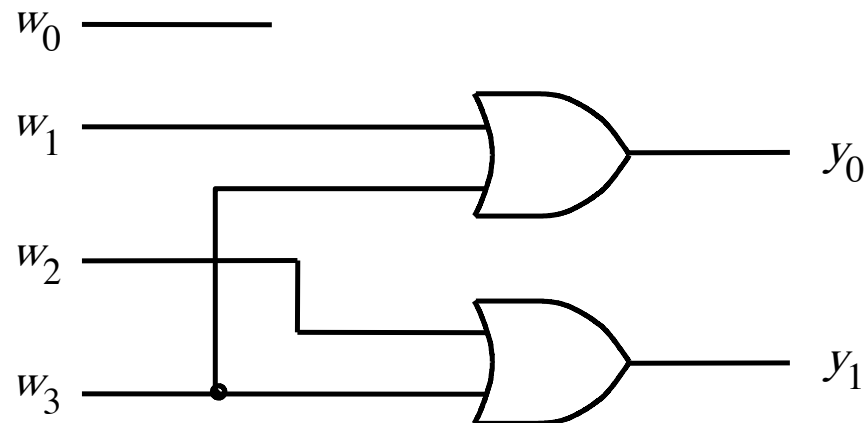

# The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

 

# The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

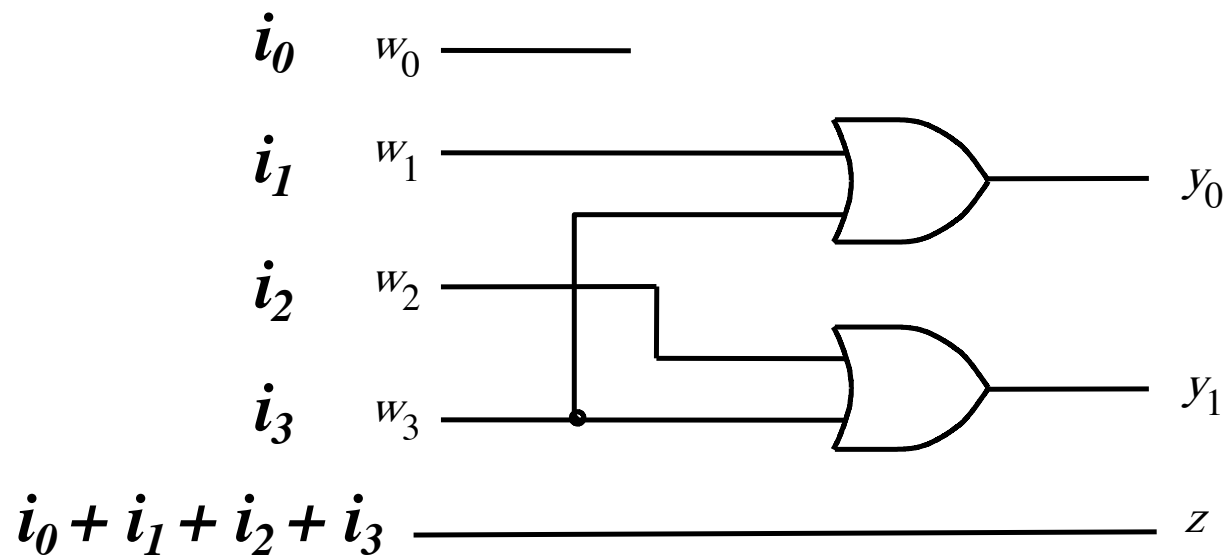

Try to prove that this is equivalent to the circuit that was derived above.



# Code Converters


# **Code Converter (Definition)**

- **Converts from one type of input encoding to a different type of output encoding.**


# **Code Converter (Definition)**

- **Converts from one type of input encoding to a different type of output encoding.**
- **A decoder does that as well, but its outputs are always one-hot encoded so the output code is really only one type of output code.**
- **A binary encoder does that as well but its inputs are always one-hot encoded so the input code is really only one type of input code.**
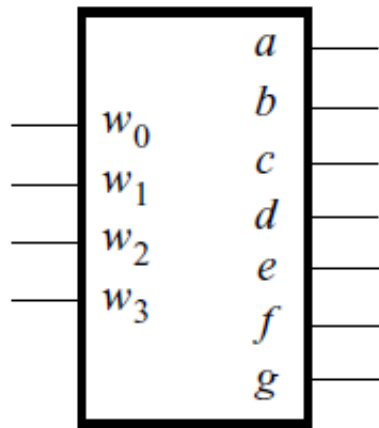
# A hex-to-7-segment display code converter



(a) Code converter

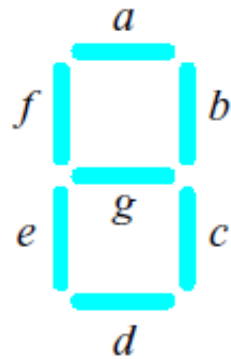


(b) 7-segment display


$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table
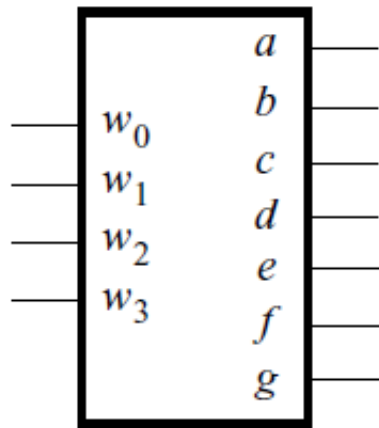
# A hex-to-7-segment display code converter



(a) Code converter

 


(b) 7-segment display


$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table
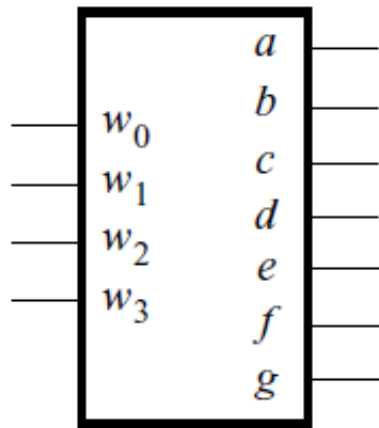
# A hex-to-7-segment display code converter



(a) Code converter

 


(b) 7-segment display


$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table
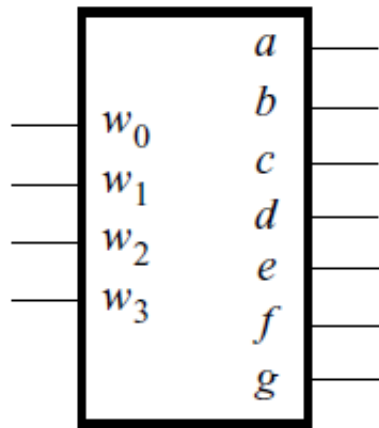
# A hex-to-7-segment display code converter



(a) Code converter

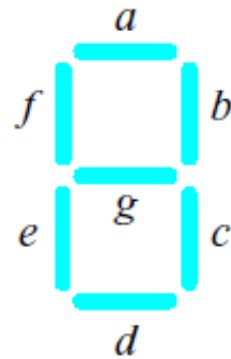


(b) 7-segment display


$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table
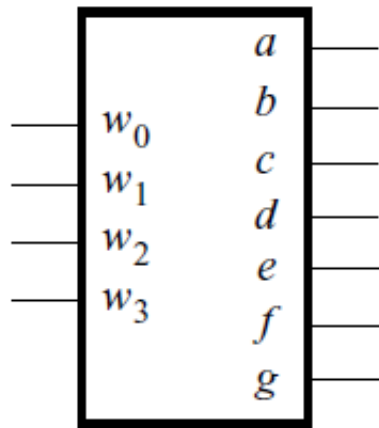
# A hex-to-7-segment display code converter



(a) Code converter

 

(b) 7-segment display

$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table



# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1


# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 3, 5, 6, 7, 8, 9, 10, 12, 14, 15)$$

# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

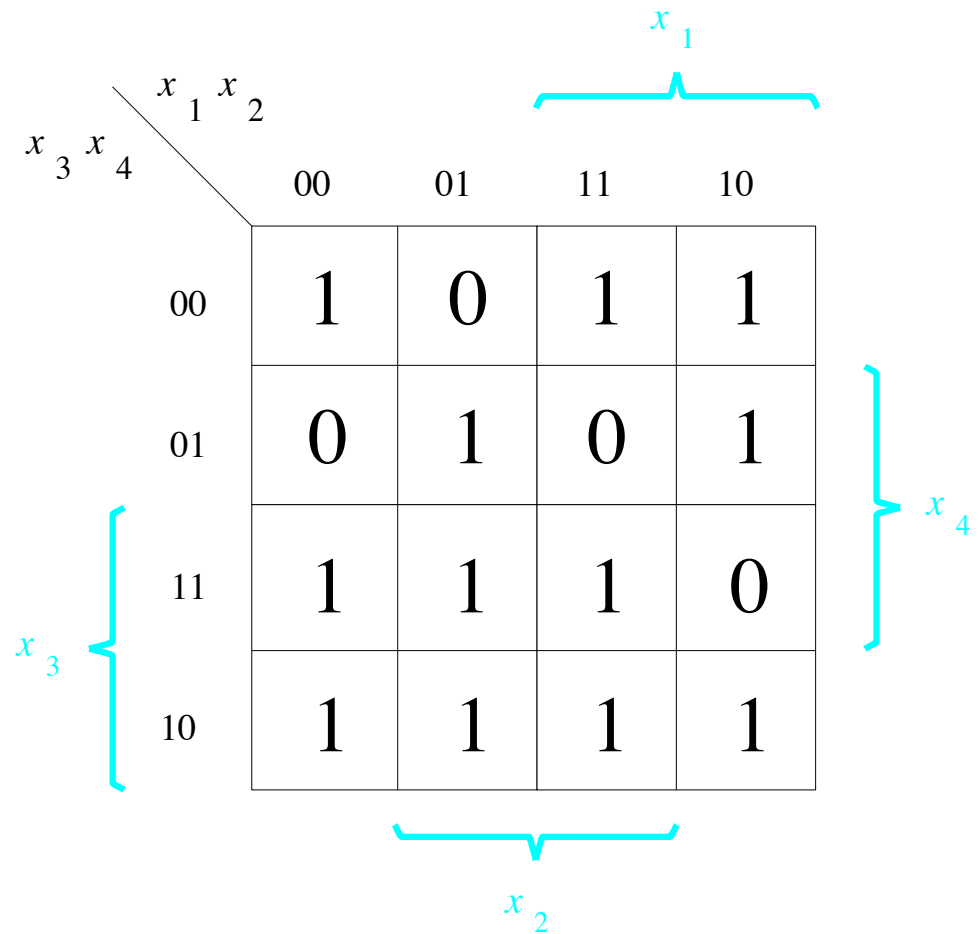


$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 3, 5, 6, 7, 8, 9, 10, 12, 14, 15)$$

# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

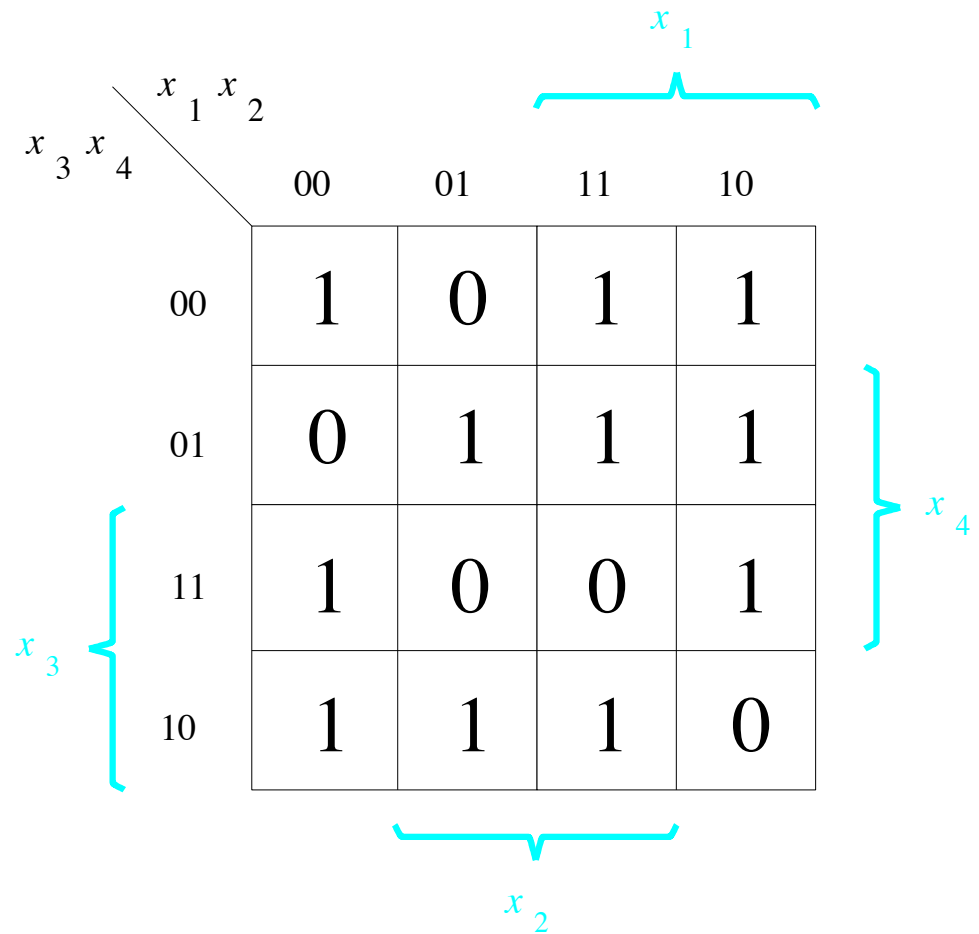

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 3, 5, 6, 8, 9, 11, 12, 13, 14)$$


# **Arithmetic Comparison Circuits**

# Truth table for a one-bit digital comparator

Inputs		Outputs		
$A$	$B$	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

# A one-bit digital comparator circuit

Inputs		Outputs		
$A$	$B$	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

 





# Truth table for a two-bit digital comparator

Inputs				Outputs		
$A_1$	$A_0$	$B_1$	$B_0$	$A < B$	$A = B$	$A > B$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

# A two-bit digital comparator circuit

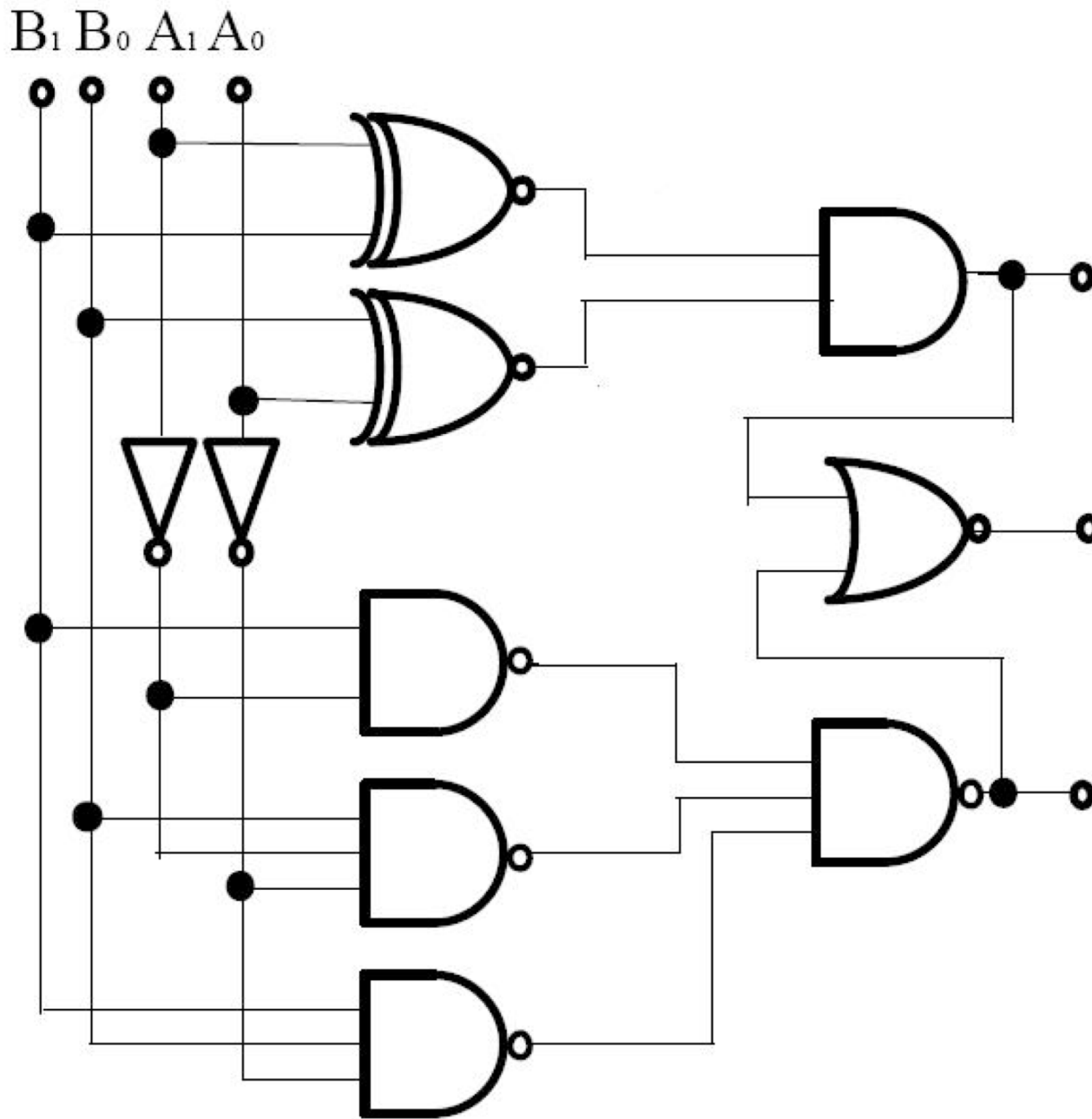

# A four-bit comparator circuit

 

[ Figure 4.22 from the textbook ]


# **Comparison of 1-bit numbers**

# Equal

<b>x</b>	<b>y</b>	<b>x = y</b>
0	0	1
0	1	0
1	0	0
1	1	1

# Equal

<b>x</b>	<b>y</b>	<b>x = y</b>
0	0	1
0	1	0
1	0	0
1	1	1

 


# Not Equal

<b>x</b>	<b>y</b>	<b>x != y</b>
0	0	0
0	1	1
1	0	1
1	1	0

# Not Equal

<b>x</b>	<b>y</b>	<b>x != y</b>
0	0	0
0	1	1
1	0	1
1	1	0

 



# Less

<b>x</b>	<b>y</b>	<b><math>x &lt; y</math></b>
0	0	0
0	1	1
1	0	0
1	1	0

# Less or Equal

<b>x</b>	<b>y</b>	<b>x ≤ y</b>
0	0	1
0	1	1
1	0	0
1	1	1

# Less or Equal

<b>x</b>	<b>y</b>	<b>x &lt; y</b>
0	0	0
0	1	1
1	0	0
1	1	0

or

<b>x</b>	<b>y</b>	<b>x = y</b>
0	0	1
0	1	0
1	0	0
1	1	1

=

<b>x</b>	<b>y</b>	<b>x &lt;= y</b>
0	0	1
0	1	1
1	0	0
1	1	1

# Greater

<b>x</b>	<b>y</b>	<b><math>x &gt; y</math></b>
0	0	0
0	1	0
1	0	1
1	1	0

# Greater or Equal

<b>x</b>	<b>y</b>	<b><math>x \geq y</math></b>
0	0	1
0	1	0
1	0	1
1	1	1

# Greater or Equal

x	y	$x > y$
0	0	0
0	1	0
1	0	1
1	1	0

or

x	y	$x = y$
0	0	1
0	1	0
1	0	0
1	1	1

=

x	y	$x \leq y$
0	0	1
0	1	0
1	0	1
1	1	1

# **Some Interesting Dualities**

# Equal

<b>x</b>	<b>y</b>	<b>x = y</b>
0	0	1
0	1	0
1	0	0
1	1	1

# Not Equal

<b>x</b>	<b>y</b>	<b>x != y</b>
0	0	0
0	1	1
1	0	1
1	1	0



# Greater

<b>x</b>	<b>y</b>	<b><math>x &gt; y</math></b>
0	0	0
0	1	0
1	0	1
1	1	0

# Less or Equal

<b>x</b>	<b>y</b>	<b><math>x \leq y</math></b>
0	0	1
0	1	1
1	0	0
1	1	1

# Greater or Equal

<b>x</b>	<b>y</b>	<b><math>x \geq y</math></b>
0	0	1
0	1	0
1	0	1
1	1	1


# Less

<b>x</b>	<b>y</b>	<b><math>x &lt; y</math></b>
0	0	0
0	1	1
1	0	0
1	1	0

# Some Interesting Dualities


- $\overline{\text{Equal}} = \text{Not Equal}$
- $\overline{\text{Greater}} = \text{Less or Equal}$
- $\overline{\text{Less}} = \text{Greater or Equal}$

# The Adder / Subtractor

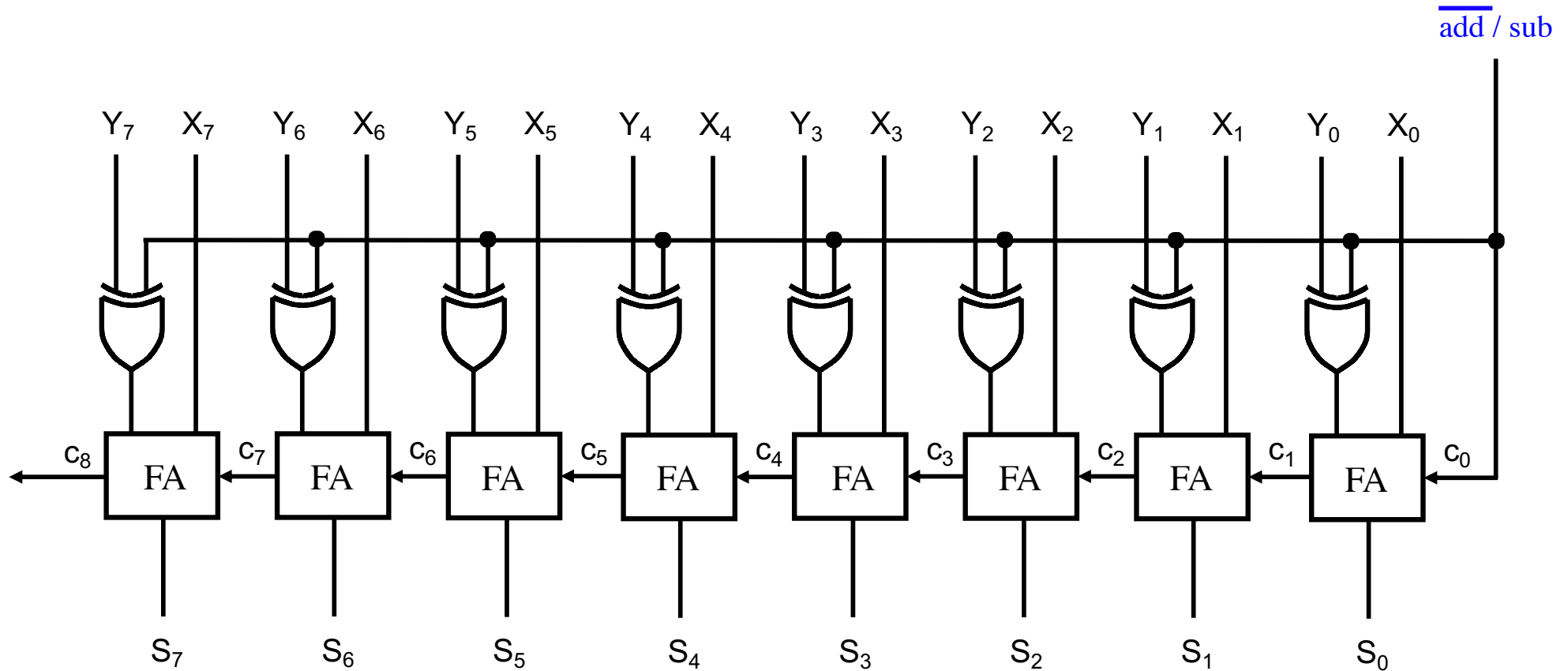


This is an 8-bit ripple-carry adder. Note that the X and Y lines are swapped.

# The Adder / Subtractor

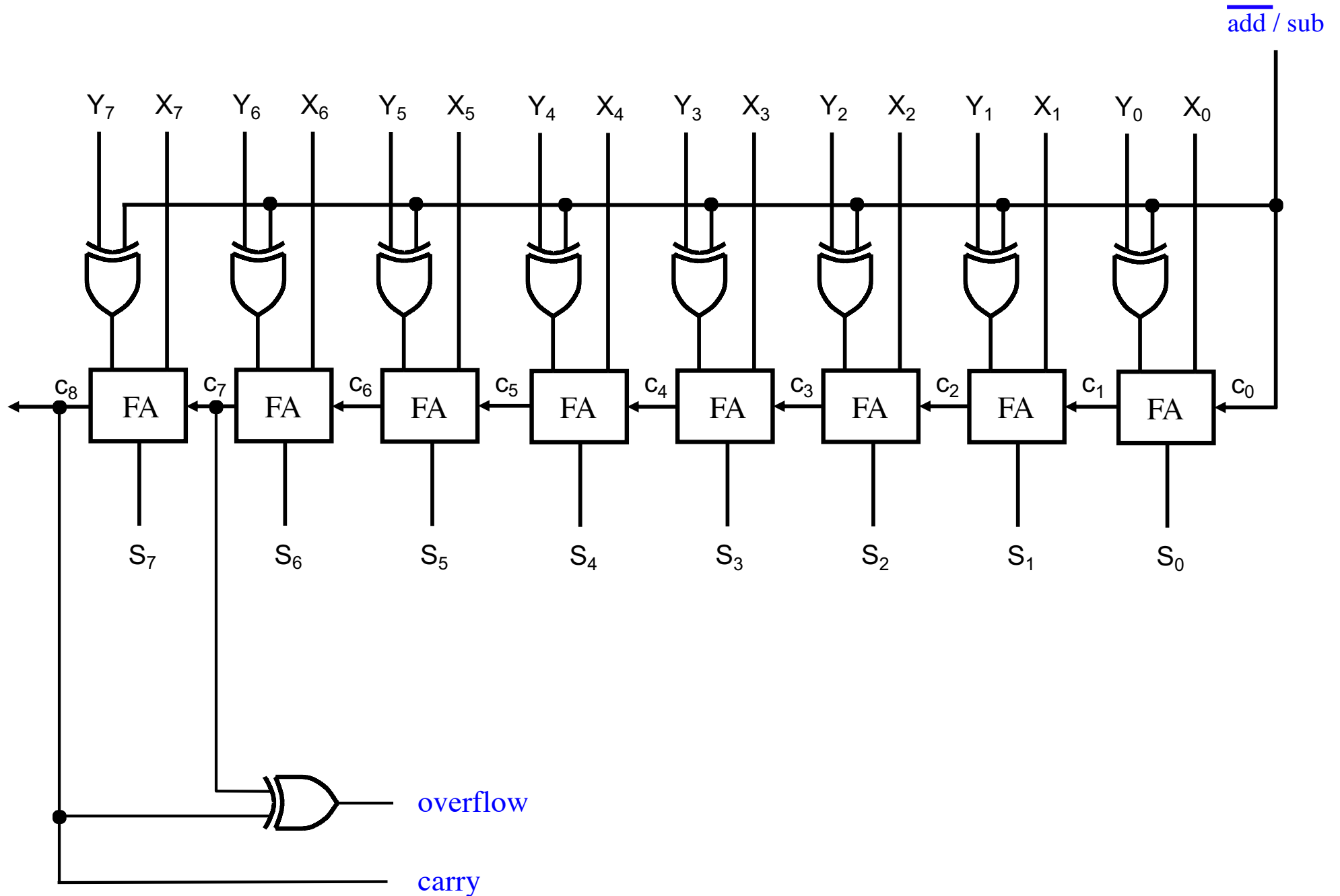

# The Adder / Subtractor

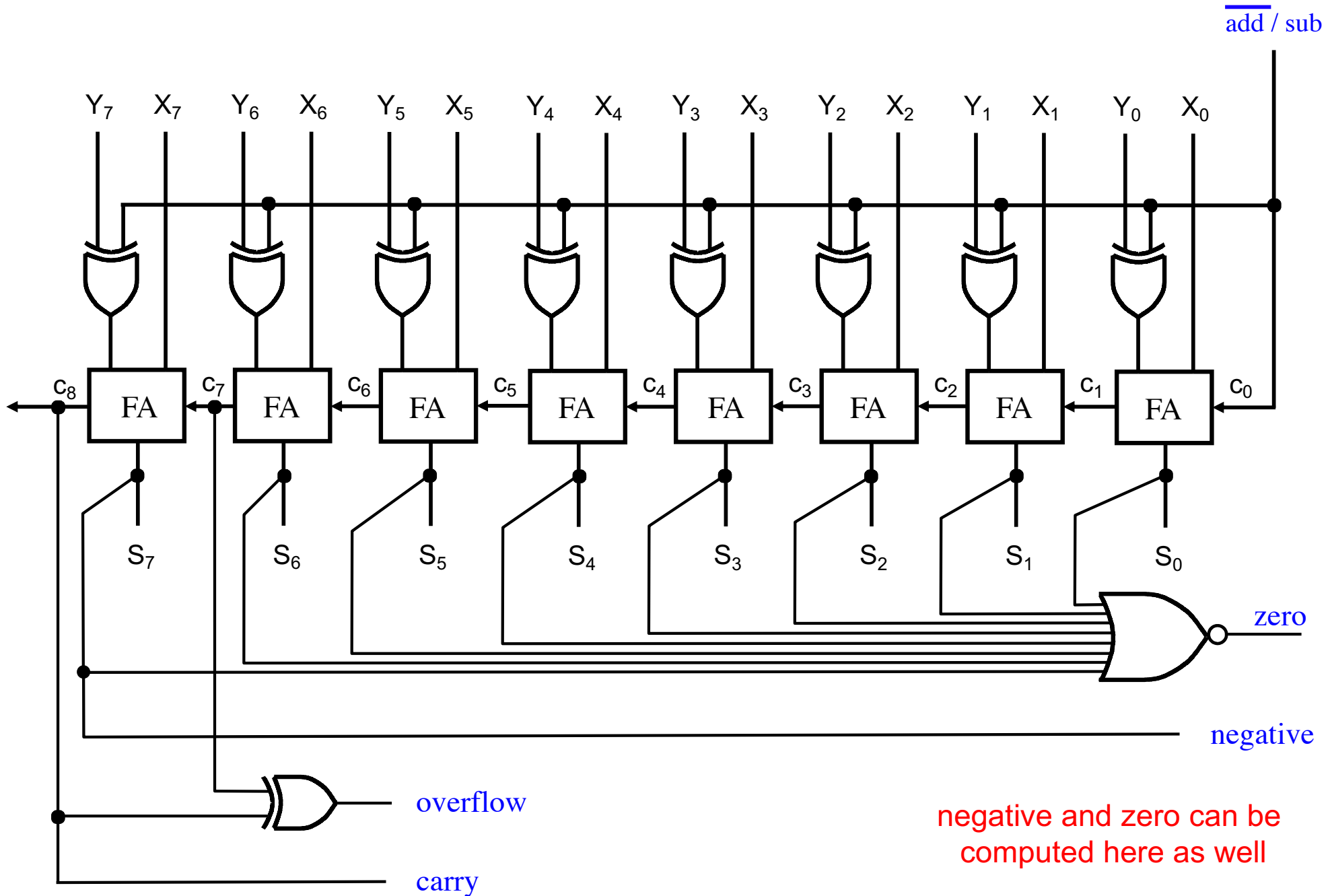

# Abbreviations for the Flags

- **Carry Flag (CF)**
- **Overflow Flag (OF)**
- **Negative Flag (NF)**
- **Zero Flag (ZF)**

# Abbreviations for the Flags

- **Carry Flag (CF)**
- **Overflow Flag (OF)**
- **Negative Flag (NF)**
- **Zero Flag (ZF)**

In some CPU architectures the carry flag means borrow. And it could be inverted relative to the previous diagram.




# Comparison of Signed Numbers

- **Equal**  $ZF = 1$
- **Not equal**  $ZF = 0$
- **Greater**  $ZF = 0$  and  $NF = OF$
- **Greater or Equal**  $NF = OF$
- **Less**  $NF \neq OF$
- **Less or Equal**  $ZF = 1$  or  $NF \neq OF$

# Comparison of Signed Numbers

- **Equal**  $ZF$
- **Not equal**  $\overline{ZF}$
- **Greater**  $\overline{ZF} \cdot XNOR( NF, OF )$
- **Greater or Equal**  $XNOR( NF, OF )$
- **Less**  $XOR( NF, OF )$
- **Less or Equal**  $ZF + XOR( NF, OF )$

# i281 CPU

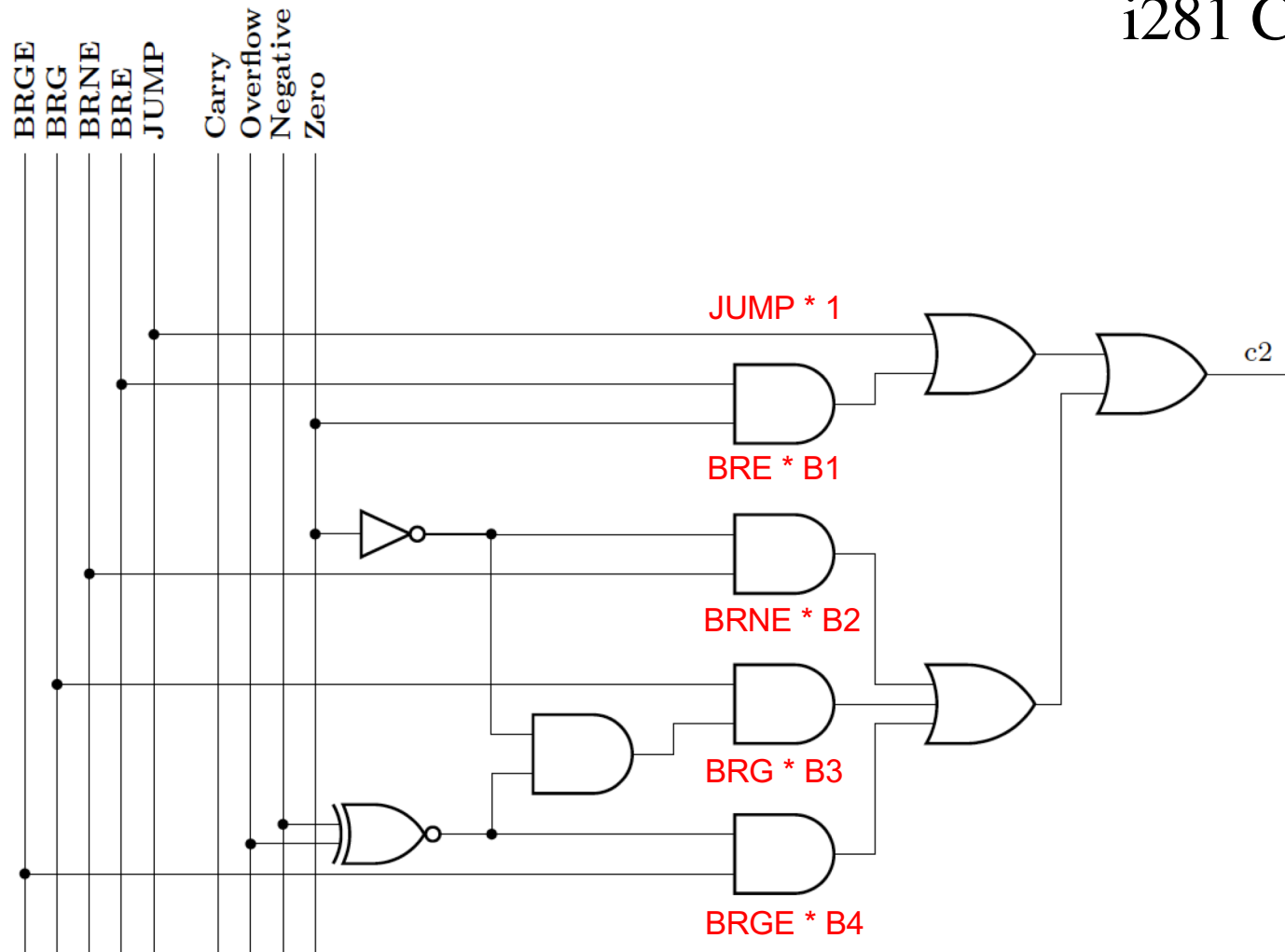


JUMP	1	1																	
BRE/BRZ	B1	1																	
BRNE/BRNZ	B2	1																	
BRG	B3	1																	
BRGE	B4	1																	

C<sub>2</sub> is the OR  
of these five  
times the OPCODE

B1= ZF  
B2= ~ZF  
B3= AND (~ZF, XNOR (NF, OF))  
B4= XNOR (NF, OF)


Zero Flag (ZF)  
Negative Flag (NF)  
Overflow Flag (OF)

# A four-bit comparator circuit

 

[ Figure 3.45 from the textbook ]

# A four-bit comparator circuit

 


OF

NF


ZF

alternative names  
for the flags

# Compare 6 with 5: (+6) - (+5)

 

# Compare 6 with 5: (+6) - (+5)

 


- Equal ZF
- Not equal  $\overline{ZF}$
- Greater  $\overline{ZF} \cdot \text{XNOR}(NF, OF)$
- Greater or Equal XNOR(NF, OF)
- Less XOR(NF, OF)
- Less or Equal ZF + XOR(NF, OF)

0

0


0

# Compare 6 with 5: (+6) - (+5)

 




# Compare 6 with 5: (+6) - (+5)

 




# Compare negative 2 with 3: (-2) - (+3)

 

**0** (overflow)      **1** (negative)      **0** (zero)

- Equal      ZF
- Not equal       $\overline{ZF}$
- Greater       $\overline{ZF \cdot XNOR(NF, OF)}$
- Greater or Equal      XNOR(NF, OF)
- Less      XOR(NF, OF)
- Less or Equal      ZF + XOR(NF, OF)


# Compare negative 2 with 3: (-2) - (+3)

 

**0** (overflow)      **1** (negative)      **0** (zero)


- Equal      0
- Not equal       $\overline{0}$
- Greater       $0 \cdot \text{XNOR}(1, 0)$
- Greater or Equal       $\text{XNOR}(1, 0)$
- Less       $\text{XOR}(1, 0)$
- Less or Equal       $0 + \text{XOR}(1, 0)$

# Compare negative 2 with 3: (-2) - (+3)

 




# Compare 1 with negative 7: (+1) - (-7)

 

**1** (overflow)      **1** (negative)      **0** (zero)

- Equal      ZF
- Not equal       $\overline{ZF}$
- Greater       $\overline{ZF \cdot XNOR(NF, OF)}$
- Greater or Equal       $XNOR(NF, OF)$
- Less       $XOR(NF, OF)$
- Less or Equal       $ZF + XOR(NF, OF)$

# Compare 1 with negative 7: (+1) - (-7)

 

**1**  
(overflow)


**1**  
(negative)

**0**  
(zero)

- Equal 0
- Not equal 0
- Greater 0 • XNOR(1, 1)
- Greater or Equal XNOR(1, 1)
- Less XOR(1, 1)
- Less or Equal 0 + XOR(1, 1)




# Compare 1 with negative 7: (+1) - (-7)

 





# Compare 3 with 3: (+3) - (+3)

 

# Compare 3 with 3: (+3) - (+3)

 


# Compare 3 with 3: (+3) - (+3)

 


# **Comparison of Unsigned Numbers**

# A four-bit comparator circuit

 


# A four-bit comparator circuit

 



# A four-bit comparator circuit

 

C  
(carry)

V  
(overflow)

N  
(negative)

Z  
(zero)

CF

OF

NF

ZF

alternative names  
for the flags

# Comparison of **Unsigned** Numbers

- **Equal**
- **Not equal**
- **Greater**
- **Greater or equal**
- **Less**
- **Less or Equal**

# Comparison of **Unsigned** Numbers

- **Equal**
- **Not equal**
- **Greater / Above**
- **Greater or Equal / Above or Equal**
- **Less / Below**
- **Less or Equal / Below or Equal**

# Comparison of **Unsigned** Numbers

- **Equal**  $ZF = 1$
- **Not equal**  $ZF = 0$
- **Greater**  $ZF = 0$  and  $CF = 1$
- **Greater or Equal**  $CF = 1$
- **Less**  $CF = 0$
- **Less or Equal**  $ZF = 1$  or  $CF = 0$

# Comparison of **Unsigned** Numbers

- Equal  $ZF$
- Not equal  $\overline{ZF}$
- Greater  $\overline{ZF} \cdot CF$
- Greater or Equal  $CF$
- Less  $\overline{CF}$
- Less or Equal  $ZF + \overline{CF}$

# Comparison of **Unsigned** Numbers

- Equal  $ZF$
- Not equal  $\overline{ZF}$
- Above  $\overline{ZF} \cdot CF$
- Above or Equal  $CF$
- Below  $\overline{CF}$
- Below or Equal  $ZF + \overline{CF}$

# **Example Problems from Chapter 4**

# Example 1: SOP vs Decoders


Implement the function

$$f(w_1, w_2, w_3) = \sum m(0, 1, 3, 4, 6, 7)$$

by using a 3-to-8 binary decoder and one OR gate.




# Solution Circuit

 

$$f(w_1, w_2, w_3) = \Sigma m(0, 1, 3, 4, 6, 7)$$
 
# Solution Circuit

Notice this swap  
of variables in  
the two lists.



Need to match the  
least significant  
with the least  
significant in both.

$$f(w_1, w_2, w_3) = \sum m(0, 1, 3, 4, 6, 7)$$

## Example 2: Implement an 8-to-3 binary encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

## Example 2: Implement an 8-to-3 binary encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$y_0 = w_1 + w_3 + w_5 + w_7$$

$$y_1 = w_2 + w_3 + w_6 + w_7$$

$$y_2 = w_4 + w_5 + w_6 + w_7$$

[ Figure 4.45 from the textbook ]

## Example 2: Implement an 8-to-3 binary encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$y_0 = w_1 + w_3 + w_5 + w_7$$

$$y_1 = w_2 + w_3 + w_6 + w_7$$

$$y_2 = w_4 + w_5 + w_6 + w_7$$

## Example 2: Implement an 8-to-3 binary encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$y_0 = w_1 + w_3 + w_5 + w_7$$

$$y_1 = w_2 + w_3 + w_6 + w_7$$

$$y_2 = w_4 + w_5 + w_6 + w_7$$

## Example 2: Implement an 8-to-3 binary encoder


$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$y_0 = w_1 + w_3 + w_5 + w_7$$

$$y_1 = w_2 + w_3 + w_6 + w_7$$

$$y_2 = w_4 + w_5 + w_6 + w_7$$

# Circuit for the 8-to-3 binary encoder

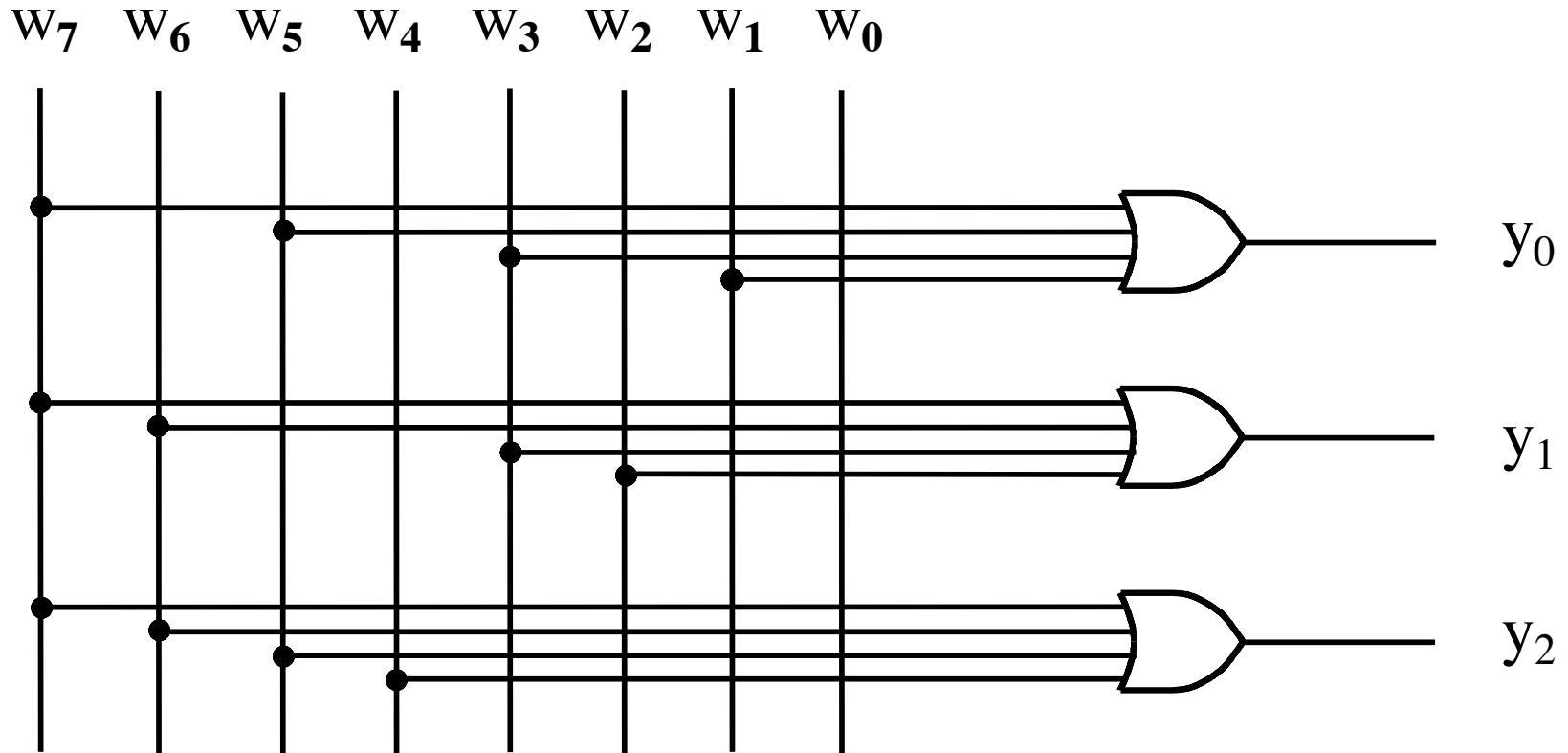

$$y_0 = w_1 + w_3 + w_5 + w_7$$

$$y_1 = w_2 + w_3 + w_6 + w_7$$

$$y_2 = w_4 + w_5 + w_6 + w_7$$



### Example 3: Implement an 8-to-3 priority encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

# Example 3: Implement an 8-to-3 priority encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	X	0	0	1
0	0	0	0	0	1	X	X	0	1	0
0	0	0	0	1	X	X	X	0	1	1
0	0	0	1	X	X	X	X	1	0	0
0	0	1	X	X	X	X	X	1	0	1
0	1	X	X	X	X	X	X	1	1	0
1	X	X	X	X	X	X	X	1	1	1

# Example 3: Implement an 8-to-3 priority encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$	$z$
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	1	X	0	0	1	1
0	0	0	0	0	1	X	X	0	1	0	1
0	0	0	0	1	X	X	X	0	1	1	1
0	0	0	1	X	X	X	X	1	0	0	1
0	0	1	X	X	X	X	X	1	0	1	1
0	1	X	X	X	X	X	X	1	1	0	1
1	X	X	X	X	X	X	X	1	1	1	1
0	0	0	0	0	0	0	0	d	d	d	0


# Example 3: Implement an 8-to-3 priority encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$	$z$
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	1	X	0	0	1	1
0	0	0	0	0	1	X	X	0	1	0	1
0	0	0	0	1	X	X	X	0	1	1	1
0	0	0	1	X	X	X	X	1	0	0	1
0	0	1	X	X	X	X	X	1	0	1	1
0	1	X	X	X	X	X	X	1	1	0	1
1	X	X	X	X	X	X	X	1	1	1	1
0	0	0	0	0	0	0	0	d	d	d	0

# Example 3: Implement an 8-to-3 priority encoder

	$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$	$z$
$i_0 = \overline{w_7} \overline{w_6} \overline{w_5} \overline{w_4} \overline{w_3} \overline{w_2} \overline{w_1} w_0$	0	0	0	0	0	0	0	1	0	0	0	1
$i_1 = \overline{w_7} \overline{w_6} \overline{w_5} \overline{w_4} \overline{w_3} \overline{w_2} w_1$	0	0	0	0	0	0	1	X	0	0	1	1
$i_2 = \overline{w_7} \overline{w_6} \overline{w_5} \overline{w_4} \overline{w_3} w_2$	0	0	0	0	0	1	X	X	0	1	0	1
$i_3 = \overline{w_7} \overline{w_6} \overline{w_5} \overline{w_4} w_3$	0	0	0	0	1	X	X	X	0	1	1	1
$i_4 = \overline{w_7} \overline{w_6} \overline{w_5} w_4$	0	0	0	1	X	X	X	X	1	0	0	1
$i_5 = \overline{w_7} \overline{w_6} w_5$	0	0	1	X	X	X	X	X	1	0	1	1
$i_6 = \overline{w_7} w_6$	0	1	X	X	X	X	X	X	1	1	0	1
$i_7 = w_7$	1	X	X	X	X	X	X	X	1	1	1	1
$z = i_0 + i_1 + i_2 + i_3 + i_4 + i_5 + i_6 + i_7$	0	0	0	0	0	0	0	0	d	d	d	0


# Circuit for the 8-to-3 binary encoder

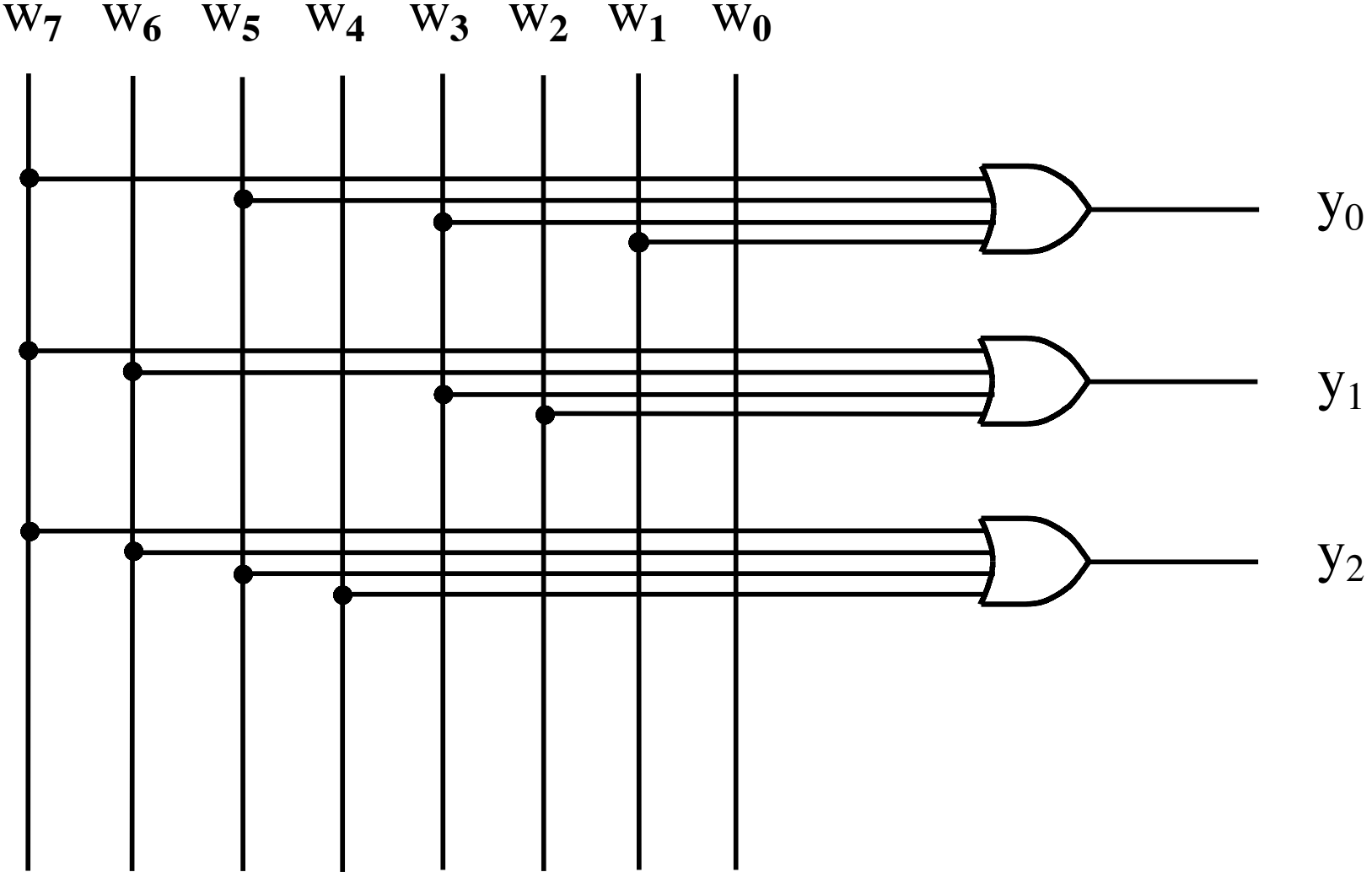
 
# Circuit for the 8-to-3 priority encoder

$i_7$   $i_6$   $i_5$   $i_4$   $i_3$   $i_2$   $i_1$   $i_0$

$w_7$   $w_6$   $w_5$   $w_4$   $w_3$   $w_2$   $w_1$   $w_0$



# Example 4: Circuit implementation using a multiplexer

Implement the function

$$f(w_1, w_2, w_3, w_4, w_5) = \bar{w}_1 \bar{w}_2 \bar{w}_4 \bar{w}_5 + w_1 w_2 + w_1 w_3 + w_1 w_4 + w_3 w_4 w_5$$

using a 4-to-1 multiplexer



# Some Boolean Algebra Leads To

$$\overline{w_1} \overline{w_2} \overline{w_4} \overline{w_5} + w_1 w_2 + w_1 w_3 + w_1 w_4 + w_3 w_4 w_5$$

$$\overline{w_1} \overline{w_4} (\overline{w_5} \overline{w_2}) + w_4 (w_3 w_5) + w_1 (w_2 + w_3) + w_1 w_4 (1)$$


$$\overline{w_1} \overline{w_4} (\overline{w_5} \overline{w_2}) + (\overline{w_1} + w_1) w_4 (w_3 w_5) + w_1 (\overline{w_4} + w_4) (w_2 + w_3) + w_1 w_4 (1)$$

$$\overline{w_1} \overline{w_4} (\overline{w_5} \overline{w_2}) + \overline{w_1} w_4 (w_3 w_5) + w_1 \overline{w_4} (w_2 + w_3) + w_1 w_4 (w_3 w_5 + (w_2 + w_3) + 1)$$

$$\overline{w_1} \overline{w_4} (\overline{w_5} \overline{w_2}) + \overline{w_1} w_4 (w_3 w_5) + w_1 \overline{w_4} (w_2 + w_3) + w_1 w_4 (1)$$

Note that the split is by  $w_1$  and  $w_4$ , not  $w_1$  and  $w_2$

# Solution Circuit

 


$$\bar{w}_1 \bar{w}_4 (\bar{w}_5 \bar{w}_2) + \bar{w}_1 w_4 (w_3 w_5) + w_1 \bar{w}_4 (w_2 + w_3) + w_1 w_4 (1)$$


[ Figure 4.46 from the textbook ]

# **Some Final Things from Chapter 4**


# A shifter circuit

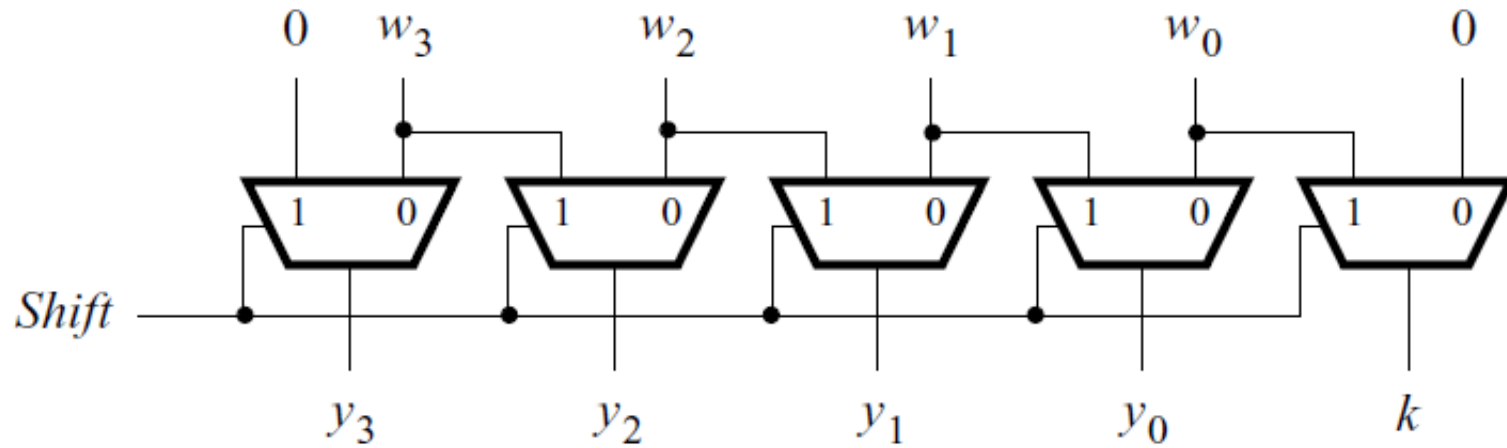


# A shifter circuit

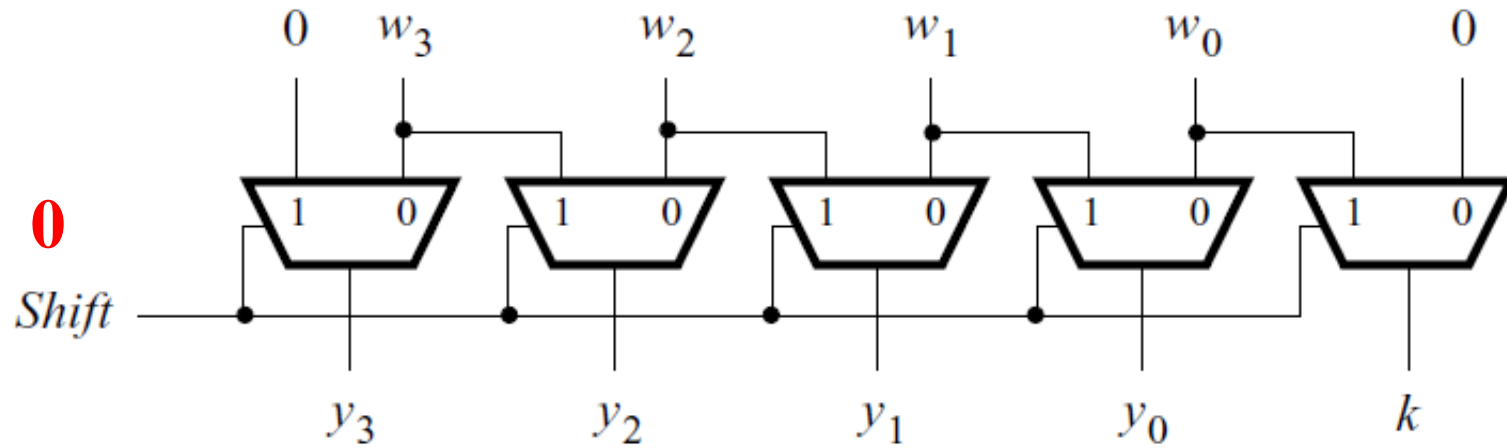

# A shifter circuit

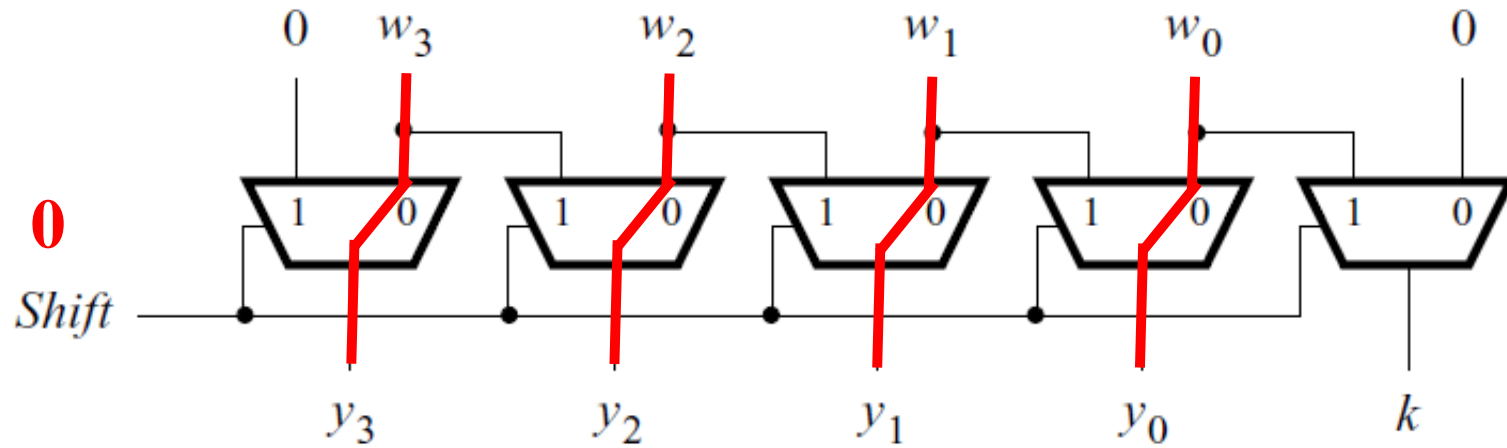


# A shifter circuit

 

No shift in this case.


# A shifter circuit

 


No shift in this case.




# A shifter circuit

 

# A shifter circuit

 


# A shifter circuit

 

Shift to the right by 1 bit

# A shifter circuit

 


Shift to the right by 1 bit

# A barrel shifter circuit

$s_1$	$s_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	$w_3$	$w_2$	$w_1$	$w_0$
0	1	$w_0$	$w_3$	$w_2$	$w_1$
1	0	$w_1$	$w_0$	$w_3$	$w_2$
1	1	$w_2$	$w_1$	$w_0$	$w_3$

(a) Truth table

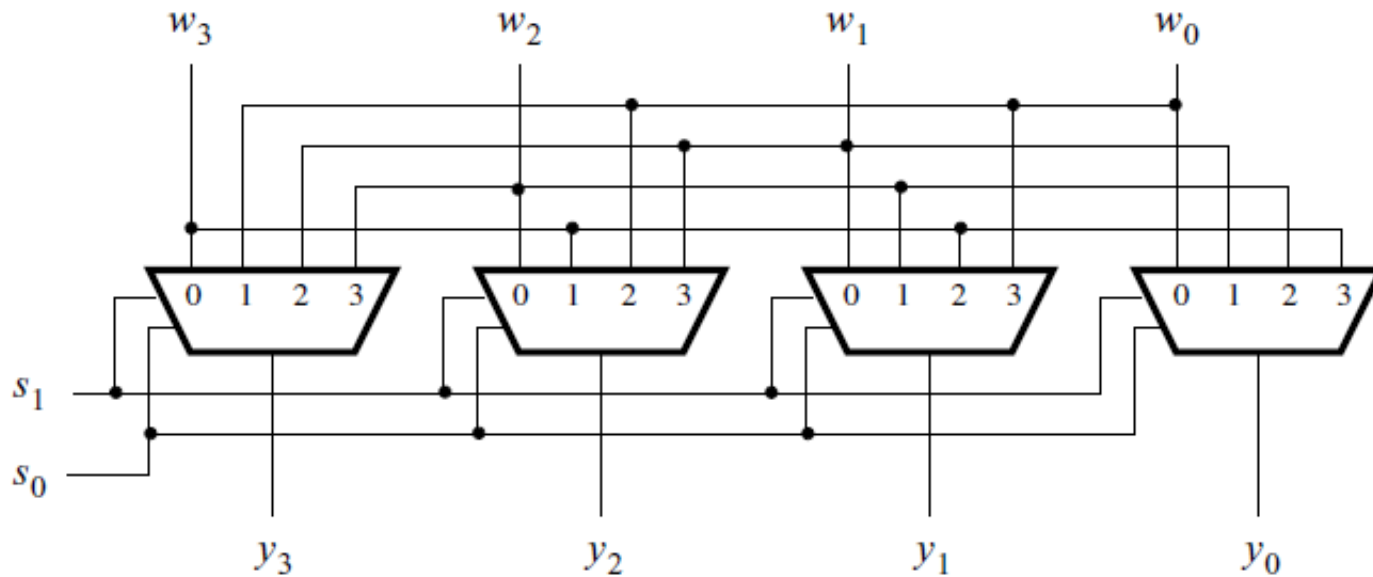


(b) Circuit

# A barrel shifter circuit

$s_1$	$s_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	$w_3$	$w_2$	$w_1$	$w_0$
0	1	$w_0$	$w_3$	$w_2$	$w_1$
1	0	$w_1$	$w_0$	$w_3$	$w_2$
1	1	$w_2$	$w_1$	$w_0$	$w_3$

(a) Truth table

 


(b) Circuit

# A barrel shifter circuit

$s_1$	$s_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	$w_3$	$w_2$	$w_1$	$w_0$
0	1	$w_0$	$w_3$	$w_2$	$w_1$
1	0	$w_1$	$w_0$	$w_3$	$w_2$
1	1	$w_2$	$w_1$	$w_0$	$w_3$

(a) Truth table

 

(b) Circuit

**Questions?**



**THE END**