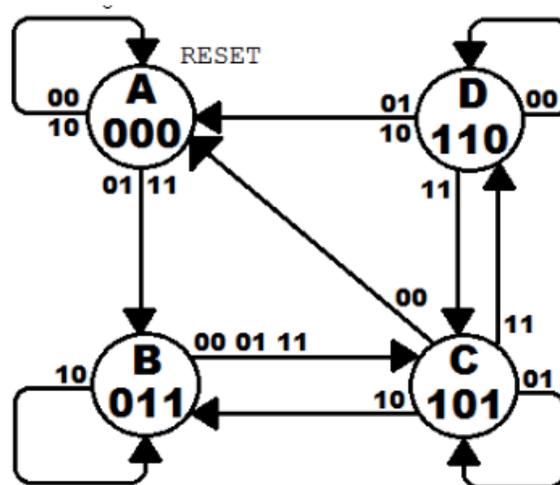



**Basic Design Steps, State-Assignment
 Problems, Moore & Mealy Machines**
Assigned Date: Eleventh Week
Finish by Nov. 15, 2021

P1 (20 points): Design and implement a Moore machine that detects the pattern 011 in its 1-bit serial input stream. Explain the logic behind your solution. Show your work for all steps discussed during the lectures: graph, state table, state-assigned table, truth tables, k-maps, expressions, circuit diagram.

P2 (15 points): Look at the state diagram below. The input variables are X and Y. The state variables are S1 and S0. The state encodings are as follows: A=00, B=01, C=10, and D=11. The output variables are Z2, Z1, and Z0.



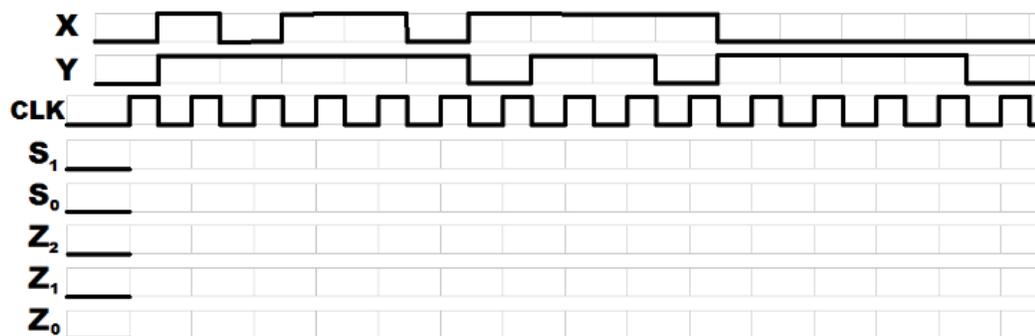- a. Fill in the timing diagram below given the state diagram for a circuit that implements this state diagram using Positive-Edge-Triggered DFFs.



Basic Design Steps, State-Assignment
Problems, Moore & Mealy Machines
Assigned Date: Eleventh Week
Finish by Nov. 15, 2021

b. Fill in the state table with state assignments

	X=0, Y=0	X=0, Y=1	X=1, Y=0	X=1, Y=1	Z ₂ Z ₁ Z ₀
A					
B					
C					
D					

c. Draw the truth table and show that the next-state expressions can be expressed as follows:

$$S_0^{new} = \bar{S}_1 \bar{S}_0 (Y) + \bar{S}_1 S_0 (X\bar{Y}) + S_1 \bar{S}_0 (X) + S_1 S_0 (\bar{X}\bar{Y})$$

$$S_1^{new} = \bar{S}_1 \bar{S}_0 (0) + \bar{S}_1 S_0 (\bar{X} + Y) + S_1 \bar{S}_0 (Y) + S_1 S_0 (XY + \bar{X}\bar{Y})$$

d. Derive expressions for the output variables Z₂, Z₁, and Z₀ in terms of S₁ and S₀


P3 (15 points): Draw a state diagram for a state machine that reads in a sequence of bits, one bit at a time, and stops when it has read in five 1s. (The five 1s can be non-consecutive.) The machine outputs a 1 when it has read at least five 1's. It outputs a 0 otherwise.

P4 (20 points): Draw a state diagram for a state machine that reads in a sequence of bits, one bit at a time, and outputs a 1 whenever the sequence 1110 is detected. It outputs a 0 otherwise. The machine keeps detecting the sequence and never stops.


- Using a Moore machine
- Using a Mealy machine

P5 (15 points): perform state minimization on the following state diagrams:

a.

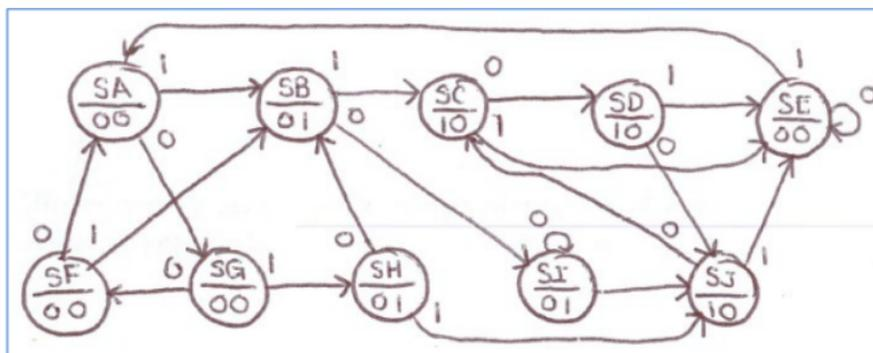

b.

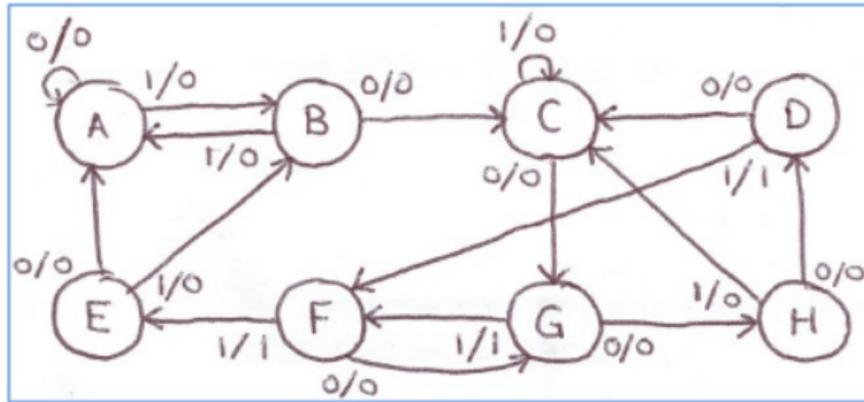

P6 (15 points): Reduce the state diagram below to use only 5 states:

