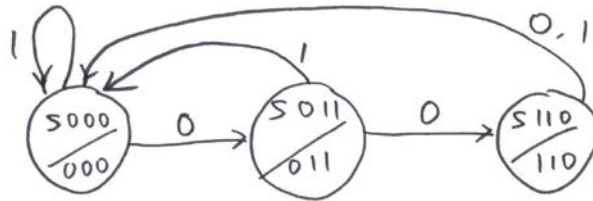


# Recitation #10 Solutions

1. a. State diagram:



b. State assignment:

State	q1	q0
S000	0	0
S011	0	1
S110	1	0

State table:


R	q1	q0	Q1	Q0
0	0	0	0	1
0	0	1	1	0
0	1	0	0	0
0	1	1	d	d
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	d	d

Output table:

q1	q0	D2	D1	D0
0	0	0	0	0
0	1	0	1	1
1	0	1	1	0
1	1	d	d	d

- c.  $Q1 = R'.q0$
- $Q0 = R'.q1'.q0$
- $D2 = q1$
- $D1 = q1+q0$
- $D0 = q0$

Sequence circuit:

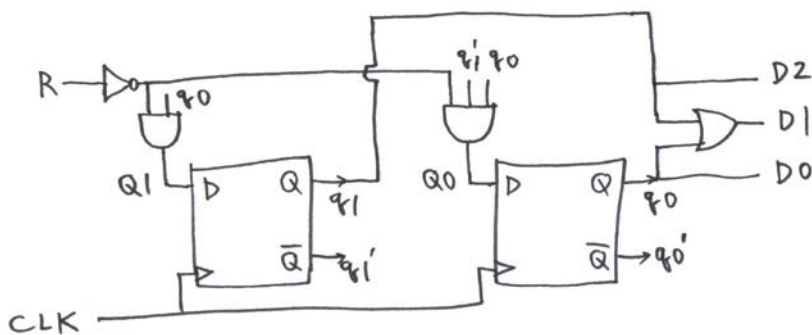

2. We design a Moore machine with 4 states:


S – Before the lock enters a state in which both  $S_1$  and  $S_2$  are open.

S00 – Both  $S_1$  and  $S_2$  are open.

S10 –  $S_1$  is closed while  $S_2$  is open.

S11 – Both  $S_1$  and  $S_2$  are closed.

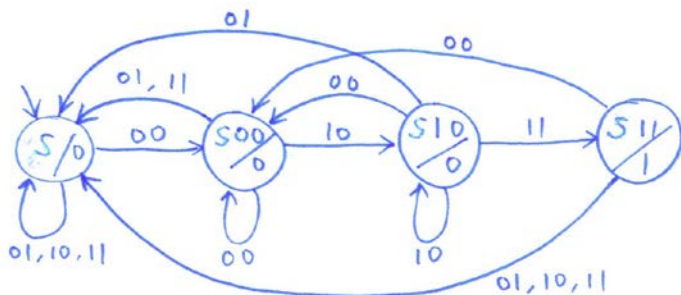State diagram (the label on each transition is “ $S_1S_2$ ”):



Assume the following state assignment:  $S \rightarrow 01$ ,  $S00 \rightarrow 00$ ,  $S10 \rightarrow 10$ ,  $S11 \rightarrow 11$ .

State table:

q1	q0	$S_1$	$S_2$	Q1	Q0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	1
0	1	0	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	1	0
1	0	1	1	1	1
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	0	1

$$Q1 = q1 \cdot q0' \cdot S_1 + q0' \cdot S_1 \cdot S_2'$$


$$Q0 = S_2 + q0 \cdot S_1$$

Output table:

q1	q0	Z
0	0	0
0	1	0
1	0	0
1	1	1

$$Z = q1 \cdot q0$$

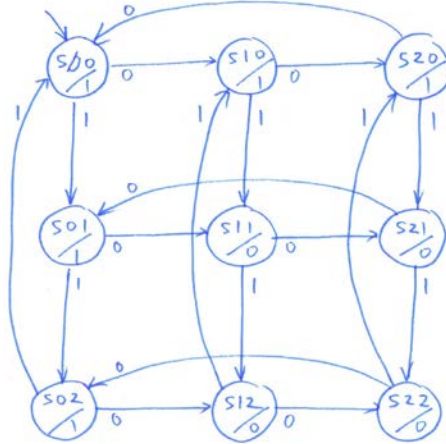3. Nine states are required. Each state is named SXY such that X is the remainder when number of 0's is divided by 3 and Y is the remainder when number of 1's is divided by 3. The state diagram:



4. We design a Moore machine with 4 states. The output will be the same as the state. The state table is as follows:

S	Q1	Q0	q1	q0	J1	K1	J0	K0
0	0	0	0	1	0	d	1	d
0	0	1	1	0	1	d	d	1
0	1	0	1	1	d	0	1	d
0	1	1	0	0	d	1	d	1
1	0	0	1	1	1	d	1	d
1	0	1	0	0	0	d	d	1
1	1	0	0	1	d	1	1	d
1	1	1	1	0	d	0	d	1

$J1=K1=S \oplus Q0, J0=K0=1$

