



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Decoders and Encoders


CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev

Administrative Stuff


- **HW6 is due today**
- **HW7 is out. It is due on Monday Oct 18 @ 4pm.**

Quick Review


Graphical Symbol for a 2-1 Multiplexer

 

Circuit for 2-1 Multiplexer

 


(b) Circuit

 


(c) Graphical symbol

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$


The Three Basic Logic Gates

 

NOT gate

 


AND gate

 


OR gate

Building an AND Gate with 2-to-1 Mux

 


x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

 Red annotations: A vertical red line is drawn between the x_1 and x_2 columns. A horizontal red line is drawn between the second and third rows. Red curly braces group the output values: the first two rows are grouped and labeled 0 , and the last two rows are grouped and labeled x_2 .




Building an OR Gate with 2-to-1 Mux

 


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 
Red annotations: A vertical red line is between the x_1 and x_2 columns. A horizontal red line is between the second and third rows. Red curly braces on the right group the output values: the first two rows are grouped and labeled x_2 , and the last two rows are grouped and labeled 1 .



Building a NOT Gate with 2-to-1 Mux

 


x	\bar{x}
0	1
1	0

 

Implications

**Any Boolean function can be implemented
using only 2-to-1 multiplexers!**

 4-to-1 Multiplexer: Graphical Symbol and Truth Table




(a) Graphic symbol


s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table


The Three Basic Logic Gates

 

NOT gate

 


AND gate

 


OR gate


Building an AND Gate with 4-to-1 Mux

 


x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

 


Building an OR Gate with 4-to-1 Mux

 



x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 

Building a NOT Gate with 4-to-1 Mux

 

x	\bar{x}
0	1
1	0

  


Two alternative solutions.


Implications

**Any Boolean function can be implemented
using only 4-to-1 multiplexers!**

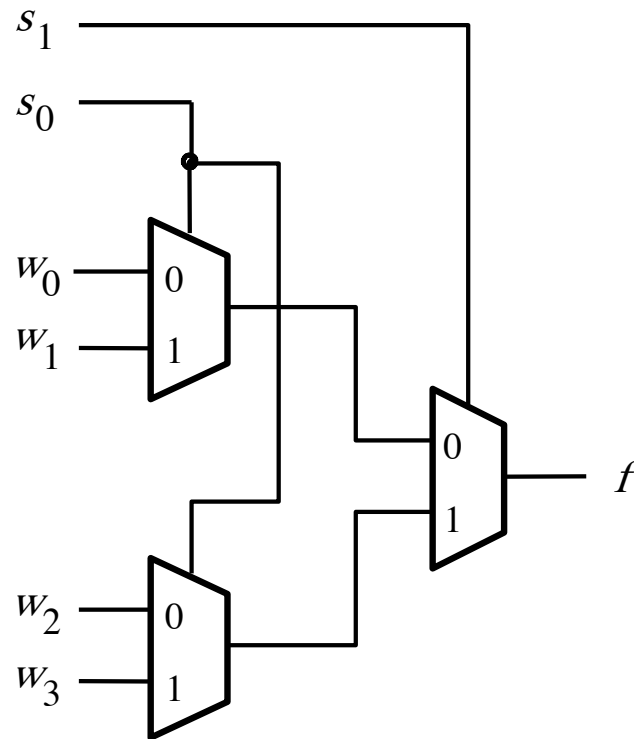Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



16-1 Multiplexer

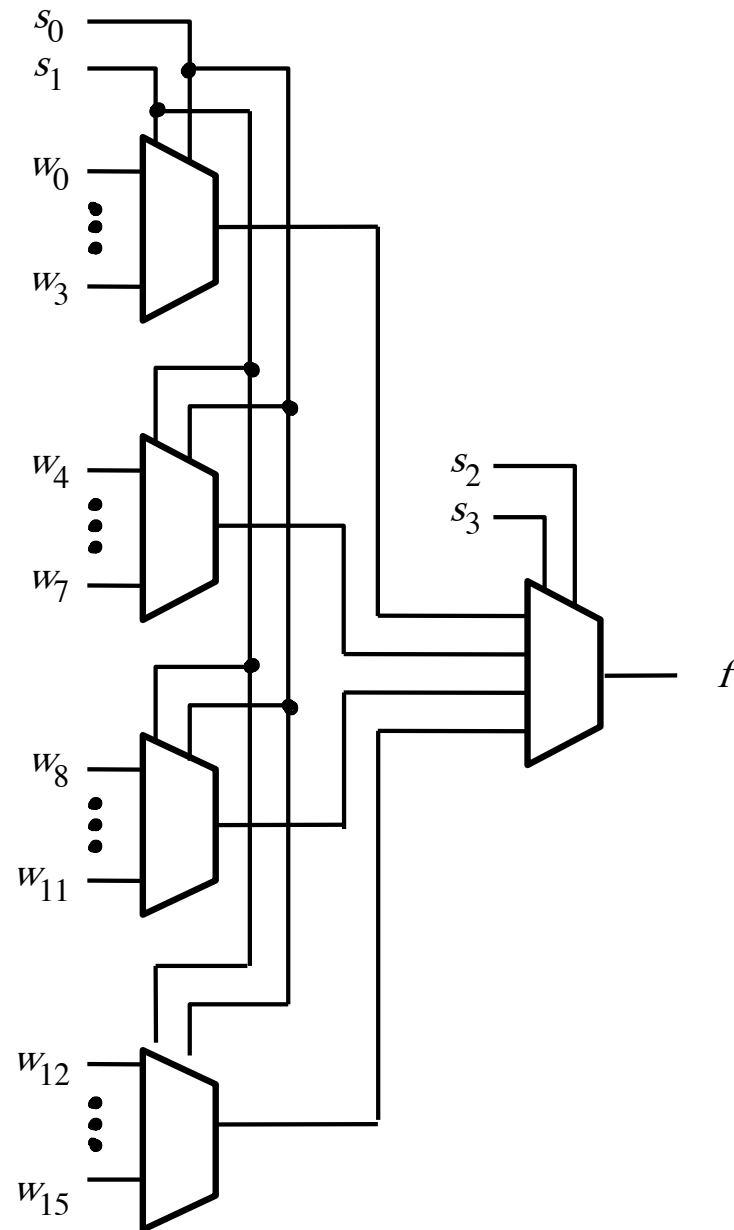

[Figure 4.4 from the textbook]


Synthesis of Logic Circuits Using Multiplexers

Synthesis of Logic Circuits Using Multiplexers

**Note: This method is NOT the same as simply replacing each logic gate with a multiplexer!
It is a lot more efficient.**

Implementation of a logic function with a 4x1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 


Implementation of the same logic function with a 2x1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0


w_1	f
0	w_2
1	\bar{w}_2

(b) Modified truth table

 

(c) Circuit

The XOR Logic Gate

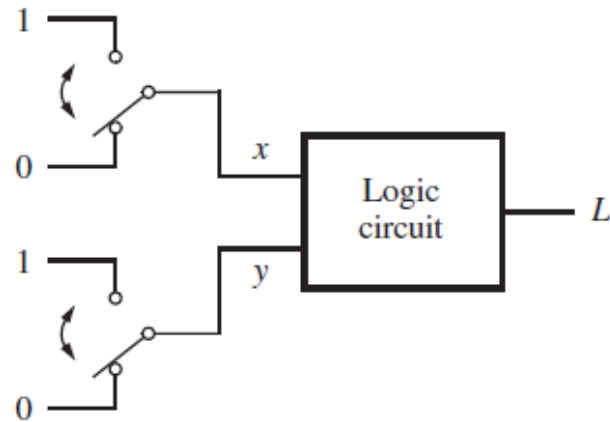


(a) Two switches that control a light

x	y	L
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table


The XOR Logic Gate

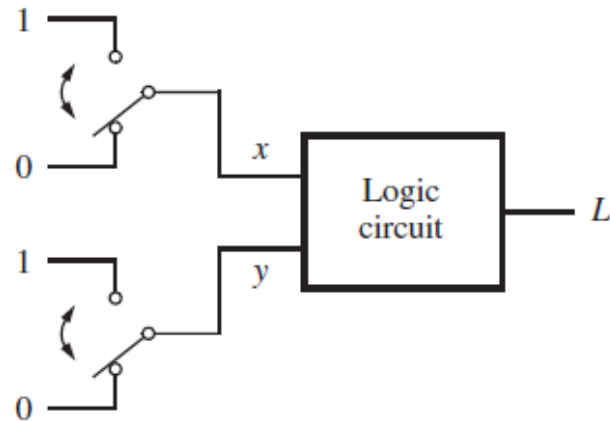

(a) Two switches that control a light

x	y	L
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table

 


(c) Logic network




 (d) XOR gate symbol


Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



 
Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT





 
Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



 These two circuits are equivalent
(the wires of the bottom AND gate are flipped)



   **In other words,
all four of these are equivalent!**



Another Example (3-input XOR)

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


Red annotations in the table:

- A vertical red line is drawn between the w_1 and w_2 columns.
- A horizontal red line is drawn between the w_3 and f columns.
- Red curly braces group the f values for $w_1 = 0$ and $w_1 = 1$.
- Red text $w_2 \oplus w_3$ is placed to the right of the first brace.
- Red text $\overline{w_2 \oplus w_3}$ is placed to the right of the second brace.

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

 


(b) Circuit

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

 

(b) Circuit

Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

 

(b) Circuit

Multiplexor Synthesis Using Shannon's Expansion

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

The diagram illustrates the mapping of the three-input majority function truth table to a two-input truth table. The first table shows the function f for all combinations of inputs w_1, w_2, w_3 . The second table shows the function f for inputs w_1 and f . Red arrows and brackets indicate the mapping: the output f of the first table is mapped to the input f of the second table. The output f of the second table is mapped to the output f of the first table.

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

(b) Truth table

 


(b) Circuit

Three-input majority function

$$f = \bar{w}_1 w_2 w_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 \bar{w}_3 + w_1 w_2 w_3$$
 
$$\begin{aligned} f &= \bar{w}_1 (w_2 w_3) + w_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3 + w_2 w_3) \\ &= \bar{w}_1 (w_2 w_3) + w_1 (w_2 + w_3) \end{aligned}$$



Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

cofactor

cofactor

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3 (\overline{w_1} + w_1)$$

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3 (\bar{w}_1 + w_1)$$

$$\begin{aligned} f &= \bar{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$

Shannon's Expansion Theorem (In terms of more than one variable)

$$f(w_1, \dots, w_n) = \bar{w}_1 \bar{w}_2 \cdot f(0, 0, w_3, \dots, w_n) + \bar{w}_1 w_2 \cdot f(0, 1, w_3, \dots, w_n) \\ + w_1 \bar{w}_2 \cdot f(1, 0, w_3, \dots, w_n) + w_1 w_2 \cdot f(1, 1, w_3, \dots, w_n)$$

This form is suitable for implementation with a 4x1 multiplexer.

Another Example

Factor and implement the following function with a 2-to-1 multiplexer


$$f = \bar{w}_1\bar{w}_3 + w_1w_2 + w_1w_3$$

Factor and implement the following function with a 2-to-1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$

 Factor and implement the following function with a 2-to-1 multiplexer



$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$
$$= \bar{w}_1 (\bar{w}_2 + w_2) \bar{w}_3 + w_1 w_2 + w_1 (\bar{w}_2 + w_2) w_3$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

$$= \bar{w}_1 (\bar{w}_2 + w_2) \bar{w}_3 + w_1 w_2 + w_1 (\bar{w}_2 + w_2) w_3$$

$$= \bar{w}_1 \bar{w}_2 \bar{w}_3 + \bar{w}_1 w_2 \bar{w}_3 + w_1 w_2 + w_1 \bar{w}_2 w_3 + w_1 w_2 w_3$$

$$= \bar{w}_1 \bar{w}_2 \bar{w}_3 + \bar{w}_1 w_2 \bar{w}_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 (1 + w_3)$$

$$= \bar{w}_1 \bar{w}_2 (\bar{w}_3) + \bar{w}_1 w_2 (\bar{w}_3) + w_1 \bar{w}_2 (w_3) + w_1 w_2 (1)$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

$$= \bar{w}_1 (\bar{w}_2 + w_2) \bar{w}_3 + w_1 w_2 + w_1 (\bar{w}_2 + w_2) w_3$$

$$= \bar{w}_1 \bar{w}_2 \bar{w}_3 + \bar{w}_1 w_2 \bar{w}_3 + w_1 w_2 + w_1 \bar{w}_2 w_3 + w_1 w_2 w_3$$

$$= \bar{w}_1 \bar{w}_2 \bar{w}_3 + \bar{w}_1 w_2 \bar{w}_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 (1 + w_3)$$

$$= \bar{w}_1 \bar{w}_2 (\bar{w}_3) + \bar{w}_1 w_2 (\bar{w}_3) + w_1 \bar{w}_2 (w_3) + w_1 w_2 (1)$$


these are the 4 cofactors

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \bar{w}_1\bar{w}_3 + w_1w_2 + w_1w_3$$

$$\begin{aligned} f &= \bar{w}_1\bar{w}_2f_{\bar{w}_1\bar{w}_2} + \bar{w}_1w_2f_{\bar{w}_1w_2} + w_1\bar{w}_2f_{w_1\bar{w}_2} + w_1w_2f_{w_1w_2} \\ &= \bar{w}_1\bar{w}_2(\bar{w}_3) + \bar{w}_1w_2(\bar{w}_3) + w_1\bar{w}_2(w_3) + w_1w_2(1) \end{aligned}$$

 Factor and implement the following function with a 4-to-1 multiplexer



$$\begin{aligned} f &= \overline{w_1}\overline{w_2}f_{\overline{w_1}\overline{w_2}} + \overline{w_1}w_2f_{\overline{w_1}w_2} + w_1\overline{w_2}f_{w_1\overline{w_2}} + w_1w_2f_{w_1w_2} \\ &= \overline{w_1}\overline{w_2}(\overline{w_3}) + \overline{w_1}w_2(\overline{w_3}) + w_1\overline{w_2}(w_3) + w_1w_2(1) \end{aligned}$$

Yet Another Example

Factor and implement the following function using only 2x1 multiplexers

$$f = w_1w_2 + w_1w_3 + w_2w_3$$

Factor and implement the following function using only 2x1 multiplexers

$$f = w_1w_2 + w_1w_3 + w_2w_3$$

$$\begin{aligned} f &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$

Factor and implement the following function using only 2x1 multiplexers


$$f = w_1w_2 + w_1w_3 + w_2w_3$$

$$f = \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3)$$

$$= \bar{w}_1(\underbrace{w_2w_3}) + w_1(\underbrace{w_2 + w_3})$$

$$g = w_2w_3 \quad h = w_2 + w_3$$

 Factor and implement the following function using only 2x1 multiplexers



$$f = \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3)$$

$$= \bar{w}_1(\underbrace{w_2w_3}) + w_1(\underbrace{w_2 + w_3})$$

$$g = w_2w_3 \quad h = w_2 + w_3$$

Factor and implement the following function using only 2x1 multiplexers

$$g = w_2 w_3$$

$$h = w_2 + w_3$$

Factor and implement the following function using only 2x1 multiplexers

$$g = w_2 w_3$$





$$g = \bar{w}_2(0) + w_2(w_3)$$

$$h = w_2 + w_3$$



$$h = \bar{w}_2(w_3) + w_2(1)$$

  
Factor and implement the following function using only 2x1 multiplexers




$$g = \bar{w}_2(0) + w_2(w_3)$$

$$h = \bar{w}_2(w_3) + w_2(1)$$

 
Finally, we are ready to draw the circuit



 Finally, we are ready to draw the circuit



 Finally, we are ready to draw the circuit



Decoders


2-to-4 Decoder (Definition)

- Has two inputs: w_1 and w_0
- Has four outputs: y_0 , y_1 , y_2 , and y_3
- If $w_1=0$ and $w_0=0$, then the output y_0 is set to 1
- If $w_1=0$ and $w_0=1$, then the output y_1 is set to 1
- If $w_1=1$ and $w_0=0$, then the output y_2 is set to 1
- If $w_1=1$ and $w_0=1$, then the output y_3 is set to 1
- Only one output is set to 1. All others are set to 0.

Truth Table and Graphical Symbol for a 2-to-4 Decoder

w_1	w_0	y_0	y_1	y_2	y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a) Truth table

 


(b) Graphical symbol

Truth Table and Graphical Symbol for a 2-to-4 Decoder

w_1	w_0	y_0	y_1	y_2	y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


The outputs are “one-hot” encoded

(a) Truth table

 


(b) Graphical symbol

The Logic Circuit for a 2-to-4 Decoder

 


[Figure 4.13c from the textbook]

The Logic Circuit for a 2-to-4 Decoder

 


[Figure 4.13c from the textbook]

The Logic Circuit for a 2-to-4 Decoder

 


[Figure 4.13c from the textbook]

The Logic Circuit for a 2-to-4 Decoder

 


[Figure 4.13c from the textbook]

The Logic Circuit for a 2-to-4 Decoder

 


[Figure 4.13c from the textbook]

The Logic Circuit for a 2-to-4 Decoder

 


[Figure 4.13c from the textbook]

The Logic Circuit for a 2-to-4 Decoder

 


[Figure 4.13c from the textbook]

Adding an Enable Input

 


[Figure 4.13c from the textbook]

Adding an Enable Input

 


[Figure 4.14c from the textbook]

Adding an Enable Input

 

When $En=1$ this circuit behaves like the one without enable.

Adding an Enable Input

 


When $En=0$ all outputs are set to 0 and the decoder is disabled.

Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphical symbol

Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphical symbol

x indicates that it does not matter what the value of this variable is for this row of the truth table

Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input


En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0

 

(b) Graphical symbol


Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

En	w_1	w_0	y_0	y_1	y_2	y_3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

 (b) Graphical symbol

Graphical Symbol for a Binary n -to- 2^n Decoder with an Enable Input



(d) An n -to- 2^n decoder


A binary decoder with n inputs has 2^n outputs

The outputs of an enabled binary decoder are “one-hot” encoded, meaning that only a single bit is set to 1, i.e., it is *hot*.

How can we build larger decoders?


- 3-to-8 ?
- 4-to-16?
- 5-to-??

Hint: How did we build a 16-1 Multiplexer

 


[Figure 4.4 from the textbook]

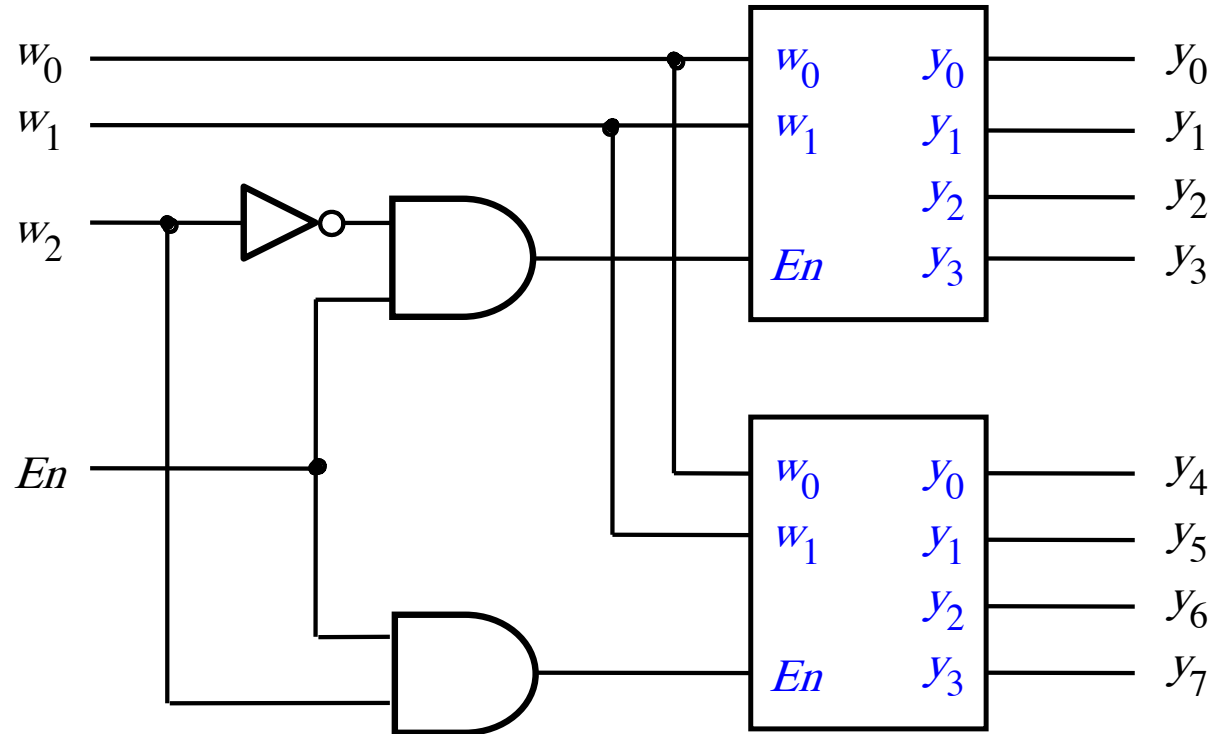A 3-to-8 decoder using two 2-to-4 decoders




 A 3-to-8 decoder using two 2-to-4 decoders




What is this?

What is this?

 


What is this?

 


This is a 1-to-2 decoder with an enable input.

 A 3-to-8 decoder using two 2-to-4 decoders




A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

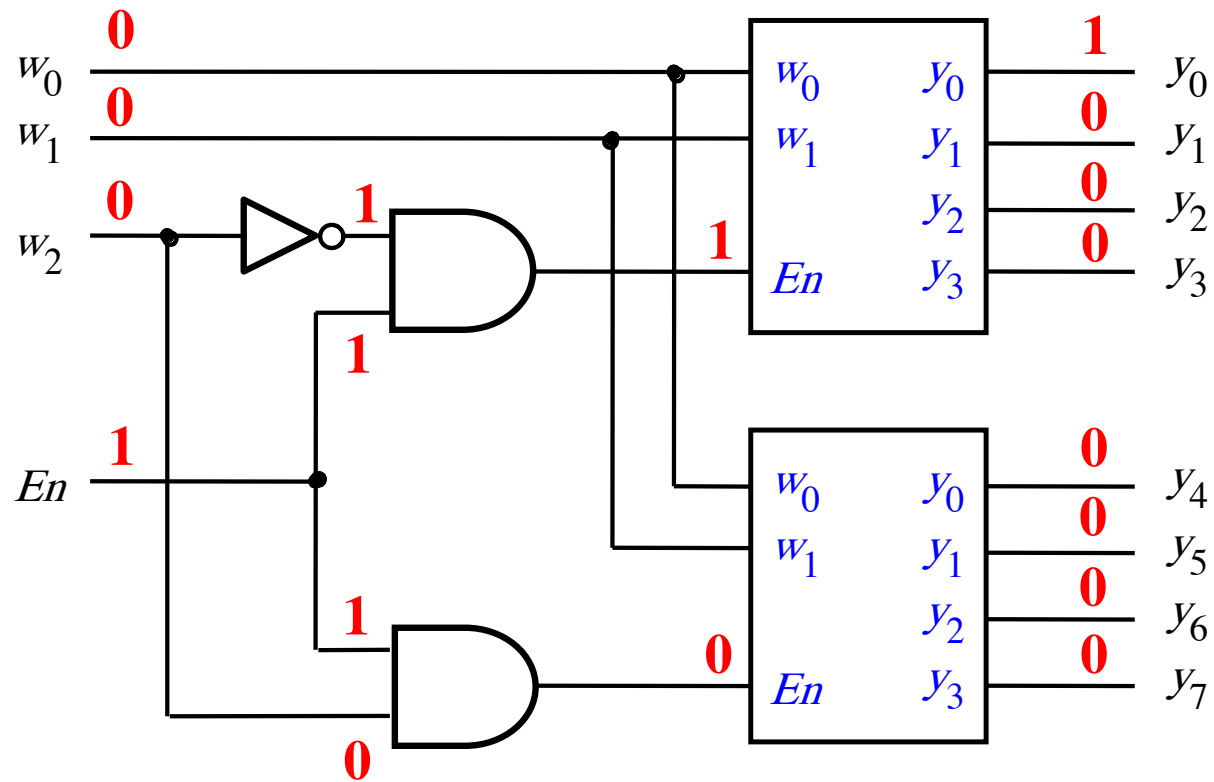
A 3-to-8 decoder using two 2-to-4 decoders



 
A 3-to-8 decoder using two 2-to-4 decoders



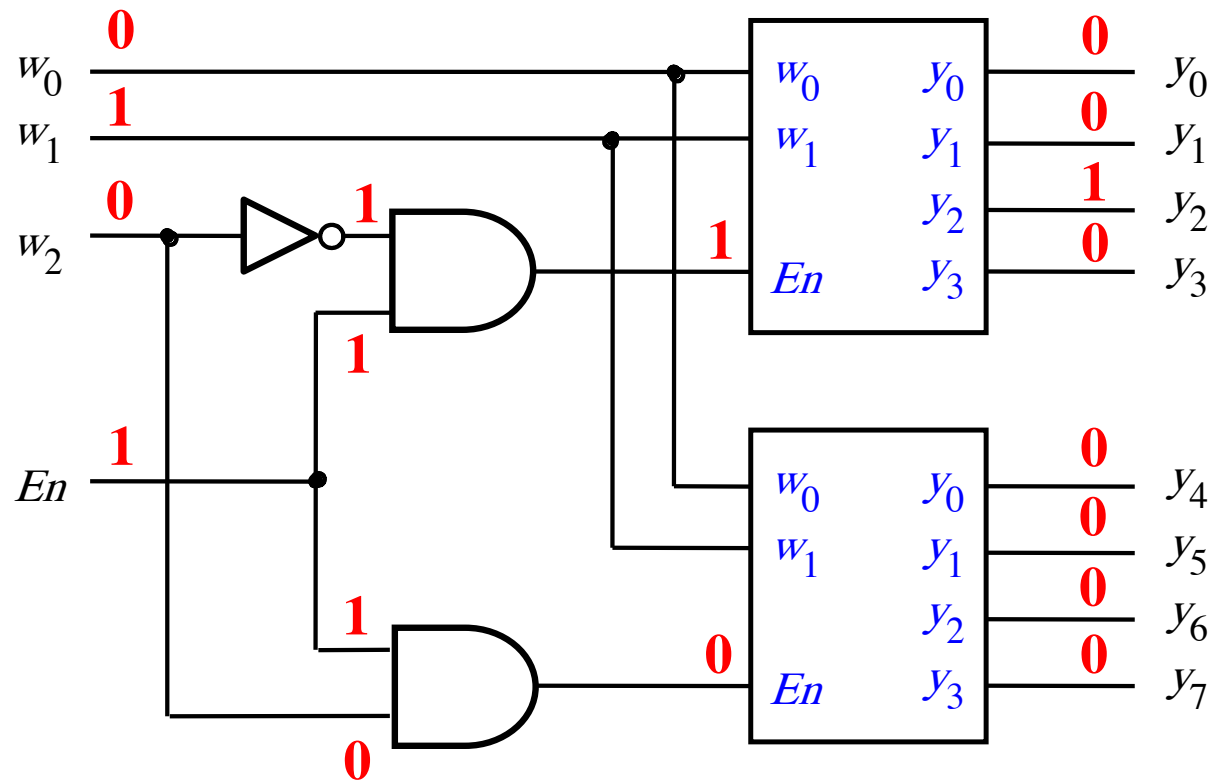
A 3-to-8 decoder using two 2-to-4 decoders



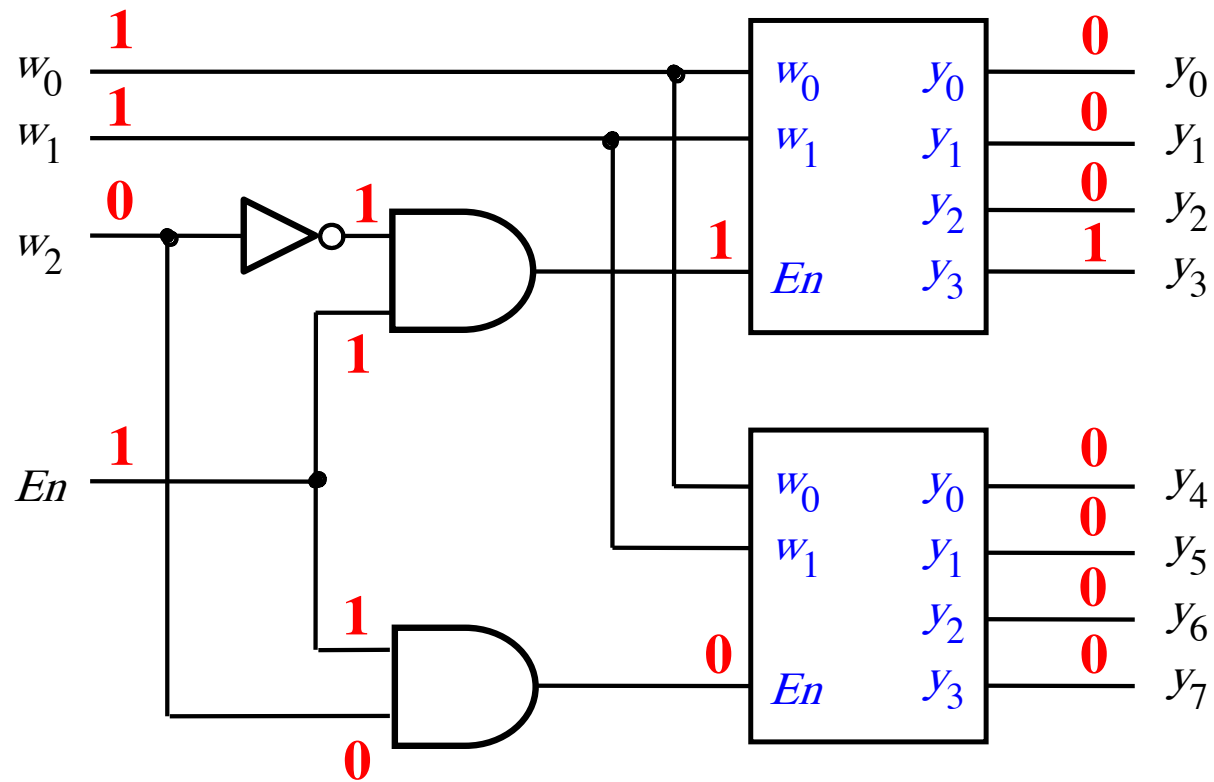A 3-to-8 decoder using two 2-to-4 decoders




A 3-to-8 decoder using two 2-to-4 decoders

 


[Figure 4.15 from the textbook]

A 3-to-8 decoder using two 2-to-4 decoders

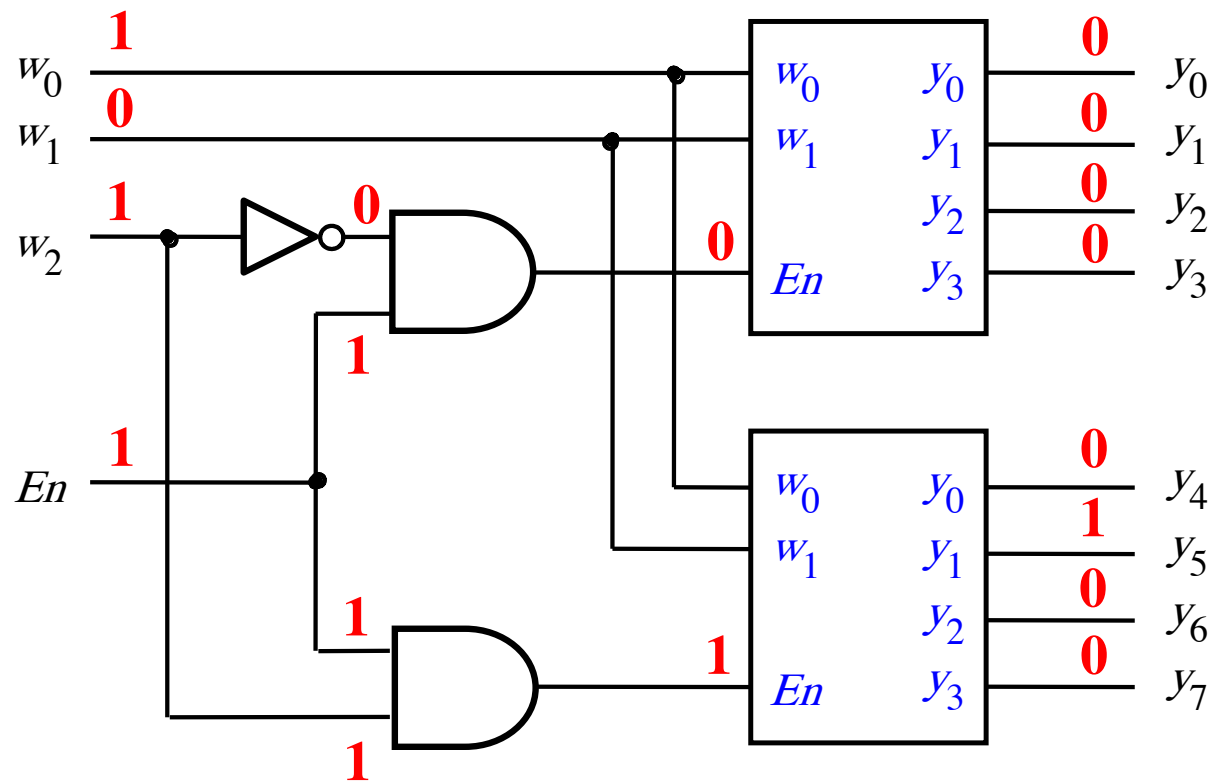


[Figure 4.15 from the textbook]

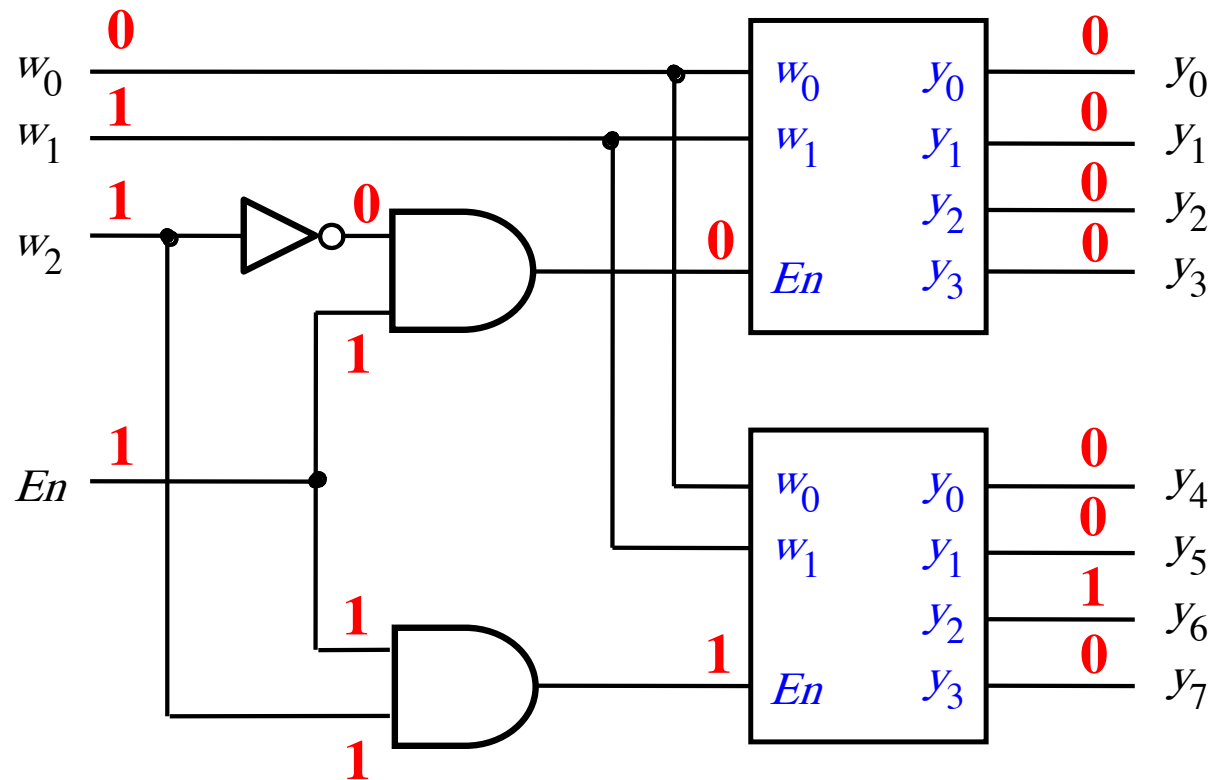
A 3-to-8 decoder using two 2-to-4 decoders



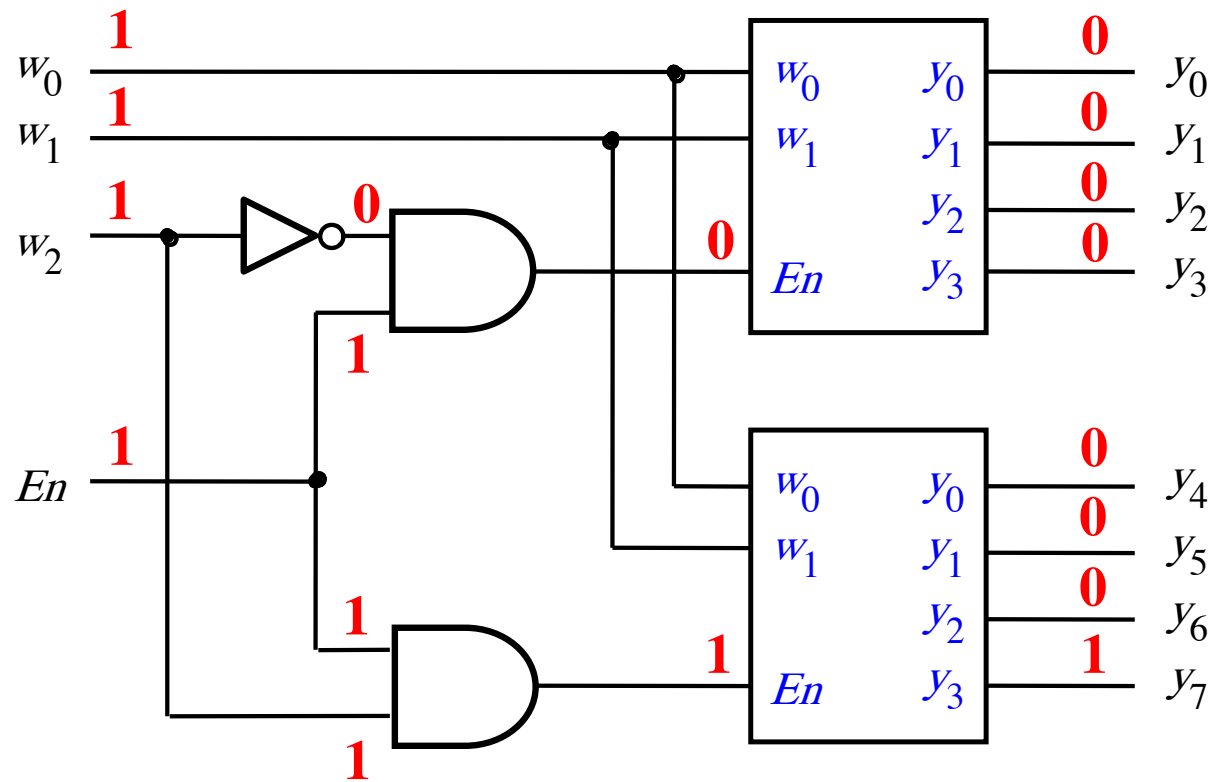A 3-to-8 decoder using two 2-to-4 decoders





4-to-16 decoder built using a decoder tree

 


[Figure 4.16 from the textbook]


Let's build a 5-to-32 decoder

  

Let's build a 5-to-32 decoder

 

Let's build a 5-to-32 decoder

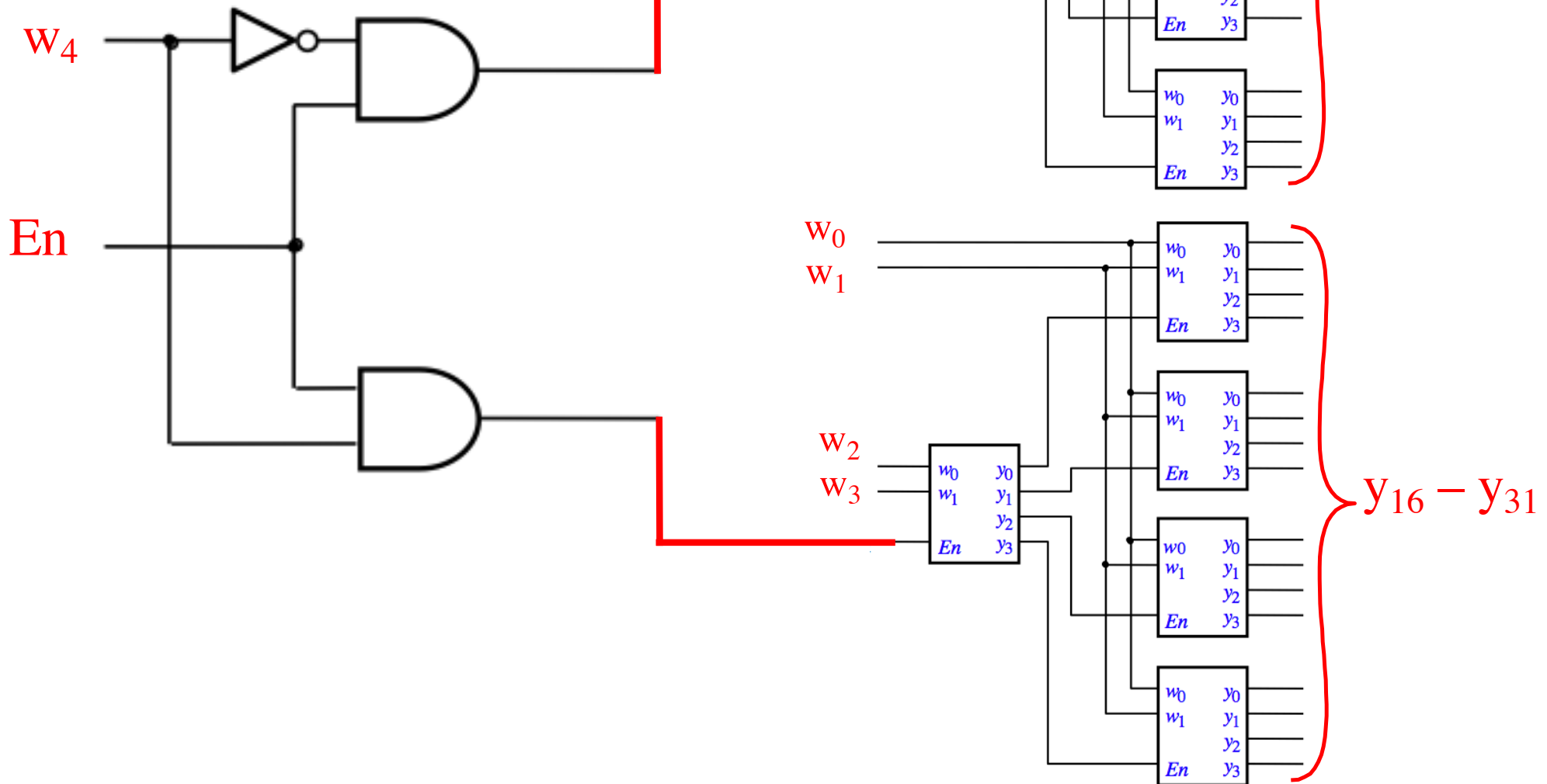


Demultiplexers

1-to-4 Demultiplexer (Definition)


- Has one data input line: D
- Has two output select lines: w_1 and w_0
- Has four outputs: y_0 , y_1 , y_2 , and y_3
- If $w_1=0$ and $w_0=0$, then the output y_0 is set to D
- If $w_1=0$ and $w_0=1$, then the output y_1 is set to D
- If $w_1=1$ and $w_0=0$, then the output y_2 is set to D
- If $w_1=1$ and $w_0=1$, then the output y_3 is set to D
- Only one output is set to D . All others are set to 0.

 A 1-to-4 demultiplexer built with a 2-to-4 decoder



A 1-to-4 demultiplexer built with a 2-to-4 decoder

output
select
lines

 


the
four
output
lines


data
input
line

Multiplexers (Implemented with Decoders)

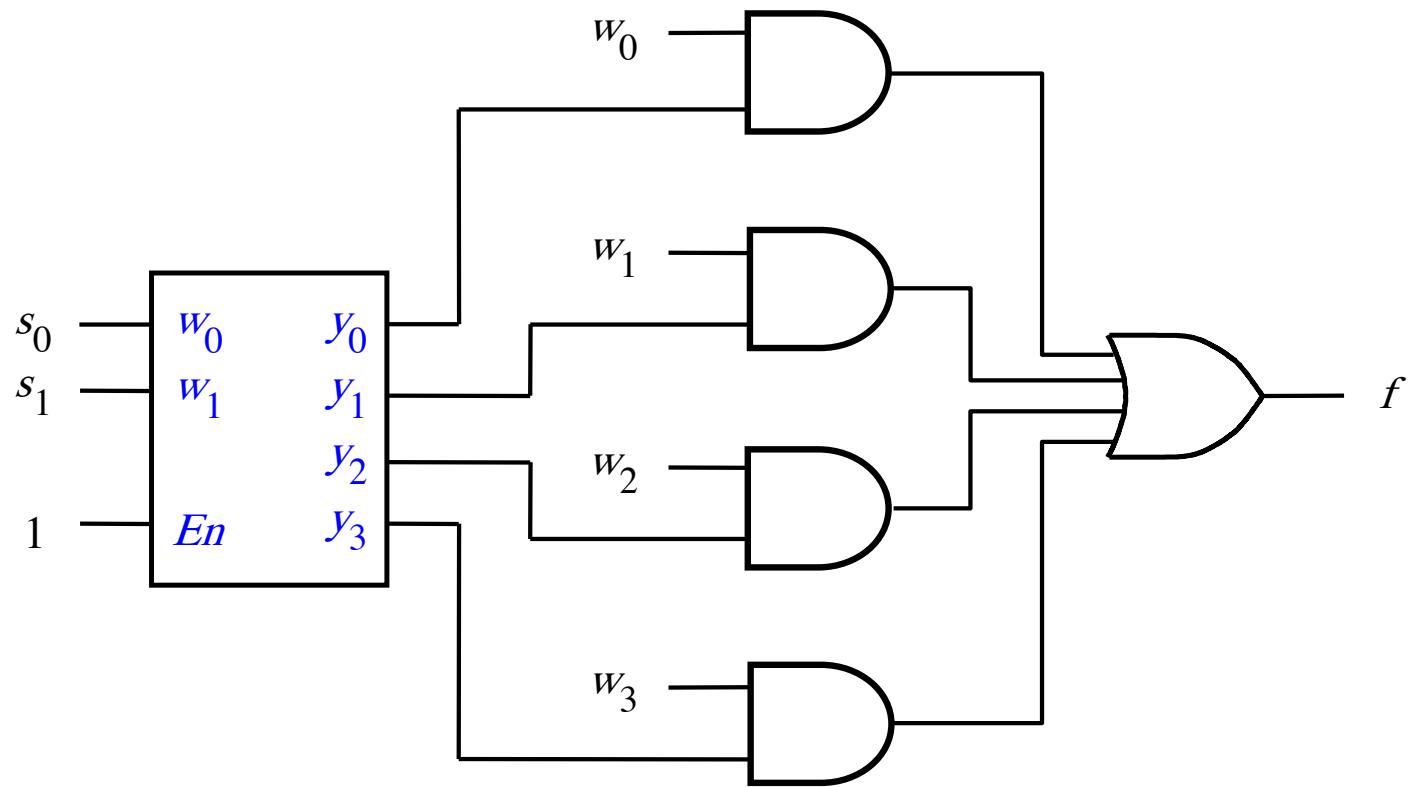
A 4-to-1 multiplexer built using a 2-to-4 decoder



 
A 4-to-1 multiplexer built using a 2-to-4 decoder



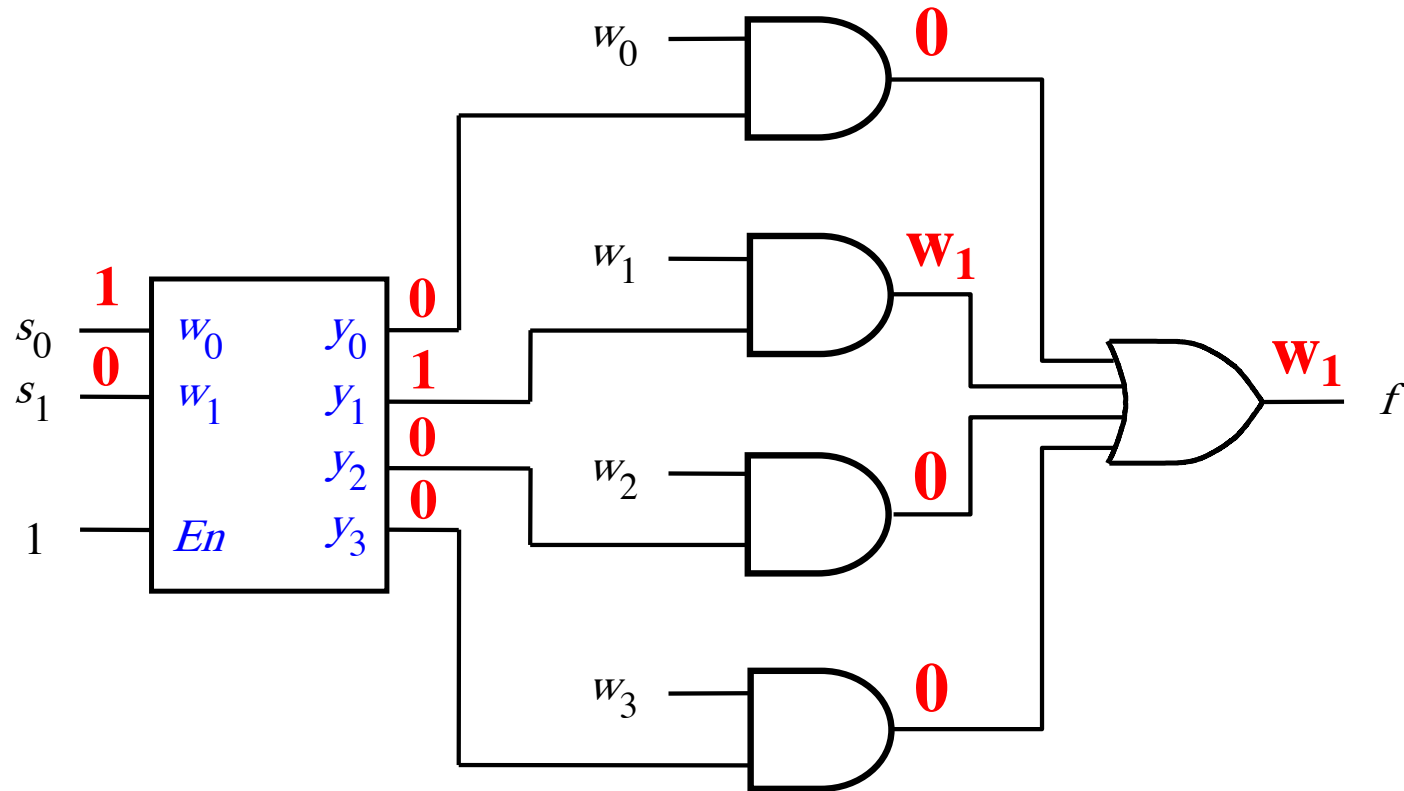
A 4-to-1 multiplexer built using a 2-to-4 decoder



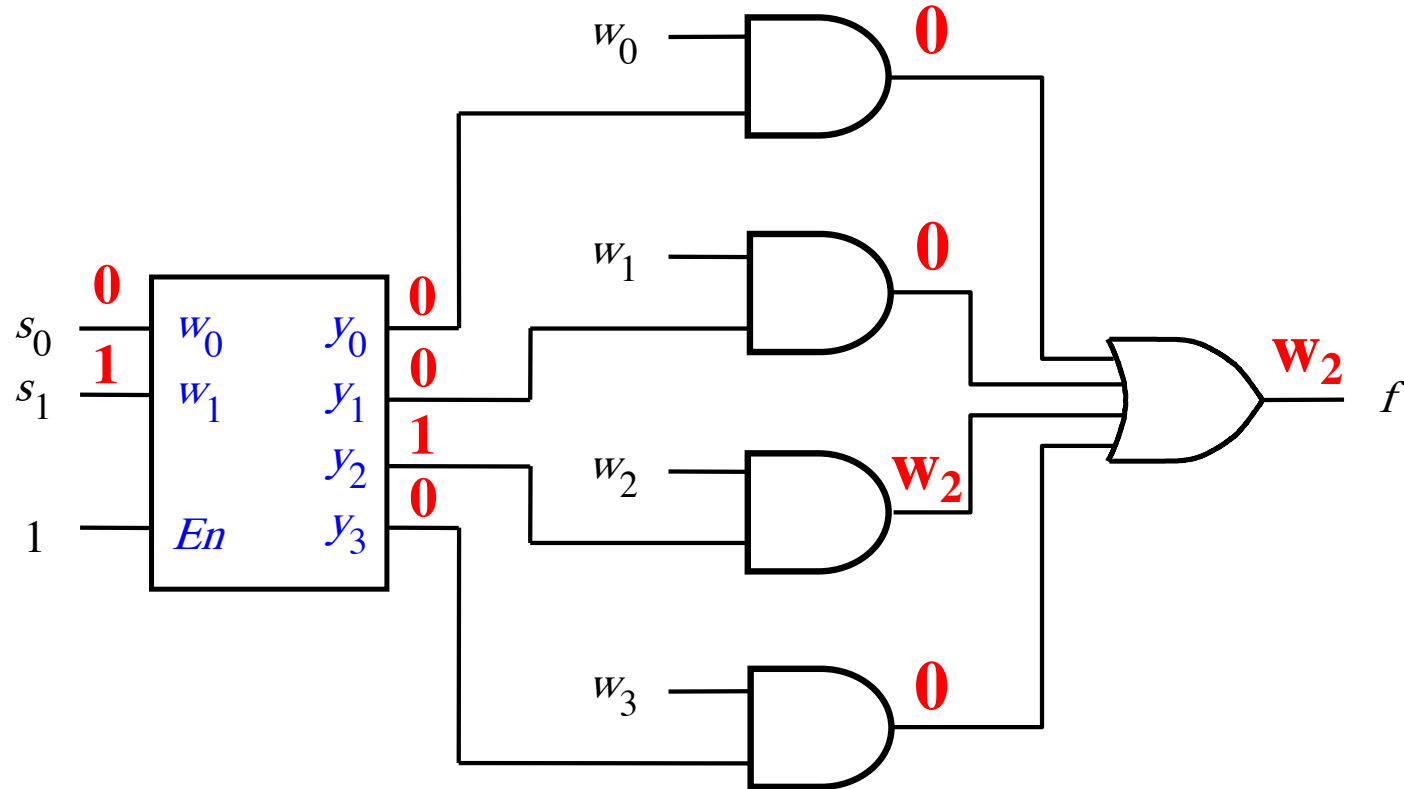
A 4-to-1 multiplexer built using a 2-to-4 decoder



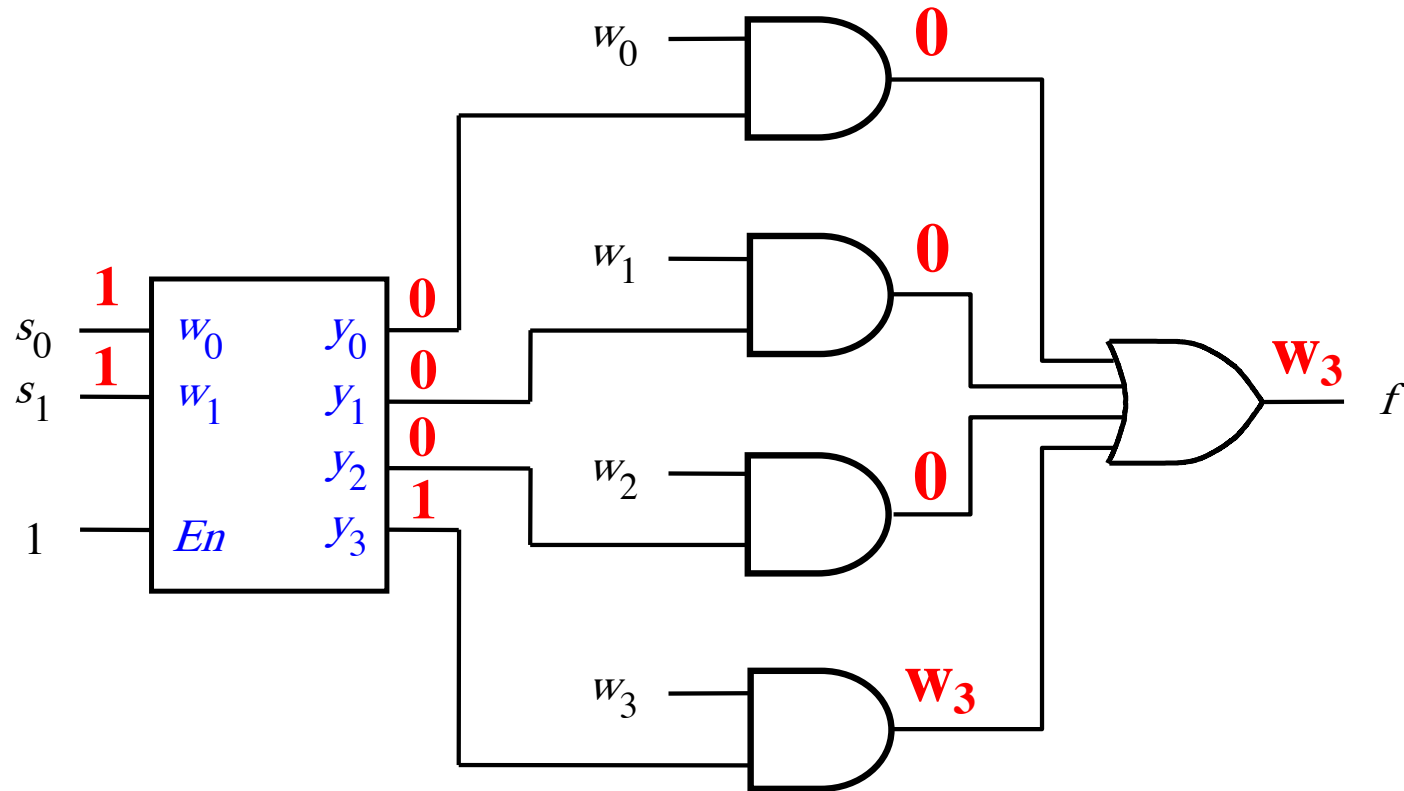A 4-to-1 multiplexer built using a 2-to-4 decoder



4-to-1 Multiplexer (SOP circuit)

 

$$f = \overline{s_1} \overline{s_0} w_0 + \overline{s_1} s_0 w_1 + s_1 \overline{s_0} w_2 + s_1 s_0 w_3$$

Encoders

Encoders
(there are several types)

Binary Encoders

4-to-2 Binary Encoder (Definition)

- Has four inputs: w_3 , w_2 , w_1 , and w_0
- Has two outputs: y_1 and y_0
- Only one input is set to 1 (“one-hot” encoded).
All others are set to 0.
- If $w_0=1$ then $y_1=0$ and $y_0=0$
- If $w_1=1$ then $y_1=0$ and $y_0=1$
- If $w_2=1$ then $y_1=1$ and $y_0=0$
- If $w_3=1$ then $y_1=1$ and $y_0=1$

Truth table for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


Truth table for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

The inputs are “one-hot” encoded


Circuit for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


Circuit for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


Circuit for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

Circuit for a 4-to-2 binary encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

Circuit for a 4-to-2 binary encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 As this level of abstraction we need that w_0 input for this to be a proper 4-to-2 binary encoder.




Circuit for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


Circuit for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


Circuit for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

Circuit for a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

Expressions for 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	0		
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1		
0	1	0	0	1	0
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0	1	1
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Expressions for 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	0	d	d
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	d	d
0	1	0	0	1	0
0	1	0	1	d	d
0	1	1	0	d	d
0	1	1	1	d	d
1	0	0	0	1	1
1	0	0	1	d	d
1	0	1	0	d	d
1	0	1	1	d	d
1	1	0	0	d	d
1	1	0	1	d	d
1	1	1	0	d	d
1	1	1	1	d	d


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Expressions for 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	0	d	d
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	d	d
0	1	0	0	1	0
0	1	0	1	d	d
0	1	1	0	d	d
0	1	1	1	d	d
1	0	0	0	1	1
1	0	0	1	d	d
1	0	1	0	d	d
1	0	1	1	d	d
1	1	0	0	d	d
1	1	0	1	d	d
1	1	1	0	d	d
1	1	1	1	d	d

		$w_3 w_2$	00	01	11	10
$w_1 w_0$	00	d	0	d	1	
01	0	d	d	d		
11	d	d	d	d		
10	1	d	d	d		

$$y_0 = (w_1 + w_3)$$

 


Expressions for 4-to-2 binary encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	0	d	d
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	d	d
0	1	0	0	1	0
0	1	0	1	d	d
0	1	1	0	d	d
0	1	1	1	d	d
1	0	0	0	1	1
1	0	0	1	d	d
1	0	1	0	d	d
1	0	1	1	d	d
1	1	0	0	d	d
1	1	0	1	d	d
1	1	1	0	d	d
1	1	1	1	d	d

$w_3 w_2$	$w_1 w_0$	00	01	11	10
00	00	d	1	d	1
01	00	0	d	d	d
11	00	d	d	d	d
10	00	0	d	d	d

$$y_1 = (w_3 + w_2)$$

 

 The Most General Case: 2^n -to- n binary encoder



Priority Encoders

4-to-2 Priority Encoder (Definition)

- Has four inputs: w_3 , w_2 , w_1 , and w_0
- Has two primary outputs: y_1 and y_0
- Has one other output: z
- The inputs are NOT “one-hot” encoded.
- More than one input can be set to 1 but they have priorities associated with them: w_3 – highest priority and w_0 – lowest priority.
- $y_1=0$ and $y_0=0$ (if $w_0=1$ and $w_3=w_2=w_1=0$)
- $y_1=0$ and $y_0=1$ (if $w_1=1$ and $w_3=w_2=0$)
- $y_1=1$ and $y_0=0$ (if $w_2=1$ and $w_3=0$)
- $y_1=1$ and $y_0=1$ (if $w_3=1$)

4-to-2 Priority Encoder (Definition)

- Has four inputs: w_3 , w_2 , w_1 , and w_0
- Has two primary outputs: y_1 and y_0
- Has one other output: z
- The inputs are NOT “one-hot” encoded.
- More than one input can be set to 1 but they have priorities associated with them: w_3 – highest priority and w_0 – lowest priority.
- $y_1=0$ and $y_0=0$ (if $w_0=1$ and $w_3=w_2=w_1=0$)
- $y_1=0$ and $y_0=1$ (if $w_1=1$ and $w_3=w_2=0$) **w_0**
- $y_1=1$ and $y_0=0$ (if $w_2=1$ and $w_3=0$) **w_0 , w_1**
- $y_1=1$ and $y_0=1$ (if $w_3=1$) **w_0 , w_1 , w_2**

these have lower priorities
and can be either 0 or 1.

4-to-2 Priority Encoder (Definition)

- Has four inputs: w_3 , w_2 , w_1 , and w_0
- Has two primary outputs: y_1 and y_0
- Has one other output: z
- The inputs are NOT “one-hot” encoded.
- More than one input can be set to 1 but they have priorities associated with them: w_3 – highest priority and w_0 – lowest priority.
- $y_1=0$ and $y_0=0$ (if $w_0=1$ and $w_3=w_2=w_1=0$)
- $y_1=0$ and $y_0=1$ (if $w_1=1$ and $w_3=w_2=0$)
- $y_1=1$ and $y_0=0$ (if $w_2=1$ and $w_3=0$)
- $y_1=1$ and $y_0=1$ (if $w_3=1$)
- $z = 0$ if $w_3=w_2=w_1=w_0=0$; otherwise $z=1$.

Truth table for a 4-to-2 priority encoder (abbreviated version)

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

Truth table for a 4-to-2 priority encoder (abbreviated version)

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

Truth table for a 4-to-2 priority encoder

	w_3	w_2	w_1	w_0	y_1	y_0	z
0 0 0 0	0	0	0	0	d	d	0
0 0 0 1	0	0	0	1	0	0	1
0 0 1 x	0	0	1	0	0	1	1
	0	0	1	1	0	1	1
0 1 x x	0	1	0	0	1	0	1
	0	1	0	1	1	0	1
	0	1	1	0	1	0	1
	0	1	1	1	1	0	1
1 x x x	1	0	0	0	1	1	1
	1	0	0	1	1	1	1
	1	0	1	0	1	1	1
	1	0	1	1	1	1	1
	1	1	0	0	1	1	1
	1	1	0	1	1	1	1
	1	1	1	0	1	1	1
	1	1	1	1	1	1	1

Expressions for 4-to-2 priority encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

		$w_3 w_2$			
$w_1 w_0$		00	01	11	10
	00	d	1	1	1
01	0	1	1	1	
11	0	1	1	1	
10	0	1	1	1	

$$y_1 = w_3 + w_2$$

Expressions for 4-to-2 priority encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

		$w_3 w_2$			
$w_1 w_0$		00	01	11	10
00		d	0	1	1
01		0	0	1	1
11		1	0	1	1
10		1	0	1	1

$$y_0 = w_3 + w_1 \overline{w_2}$$


Expressions for 4-to-2 priority encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

		$w_3 w_2$			
$w_1 w_0$		00	01	11	10
	00	0	1	1	1
01	1	1	1	1	
11	1	1	1	1	
10	1	1	1	1	

$$Z = w_3 + w_2 + w_1 + w_0$$

Circuit for the 4-to-2 priority encoder

 

The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

 

The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

 

The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

 

Try to prove that this is equivalent to the circuit that was derived above.

Let's prove this for z

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

		$w_3 w_2$			
		00	01	11	10
$w_1 w_0$	00	0	1	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$z = ?$

Let's prove this for z

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

		$w_3 w_2$			
		00	01	11	10
$w_1 w_0$	00	0	1	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$$z = (w_0 + w_1 + w_2 + w_3)$$

Let's prove this for y_0

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

		w_3	w_2		
w_1	w_0	00	01	11	10
	00	0	0	1	1
	01	0	0	1	1
	11	1	0	1	1
	10	1	0	1	1

$$y_0 = ?$$

Let's prove this for y_0

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

		$w_3 w_2$			
		00	01	11	10
$w_1 w_0$	00	0	0	1	1
	01	0	0	1	1
11	1	0	1	1	
10	1	0	1	1	

$$y_0 = w_3 + w_1 \bar{w}_2$$

Let's prove this for y_1

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

		w_3	w_2		
w_1	w_0	00	01	11	10
	00	0	1	1	1
	01	0	1	1	1
	11	0	1	1	1
	10	0	1	1	1

$y_1 = ?$

Let's prove this for y_1

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

		$w_3 w_2$			
		00	01	11	10
$w_1 w_0$	00	0	1	1	1
	01	0	1	1	1
	11	0	1	1	1
	10	0	1	1	1

$$y_1 = w_3 + w_2$$

Therefore, this circuit for the 4-to-2 priority encoder is equivalent to ..

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$


$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

 

 ... this circuit for the 4-to-2 priority encoder



Questions?

THE END