


# **CprE 281: Digital Logic**


**Instructor: Alexander Stoytchev**


**<http://www.ece.iastate.edu/~alexs/classes/>**
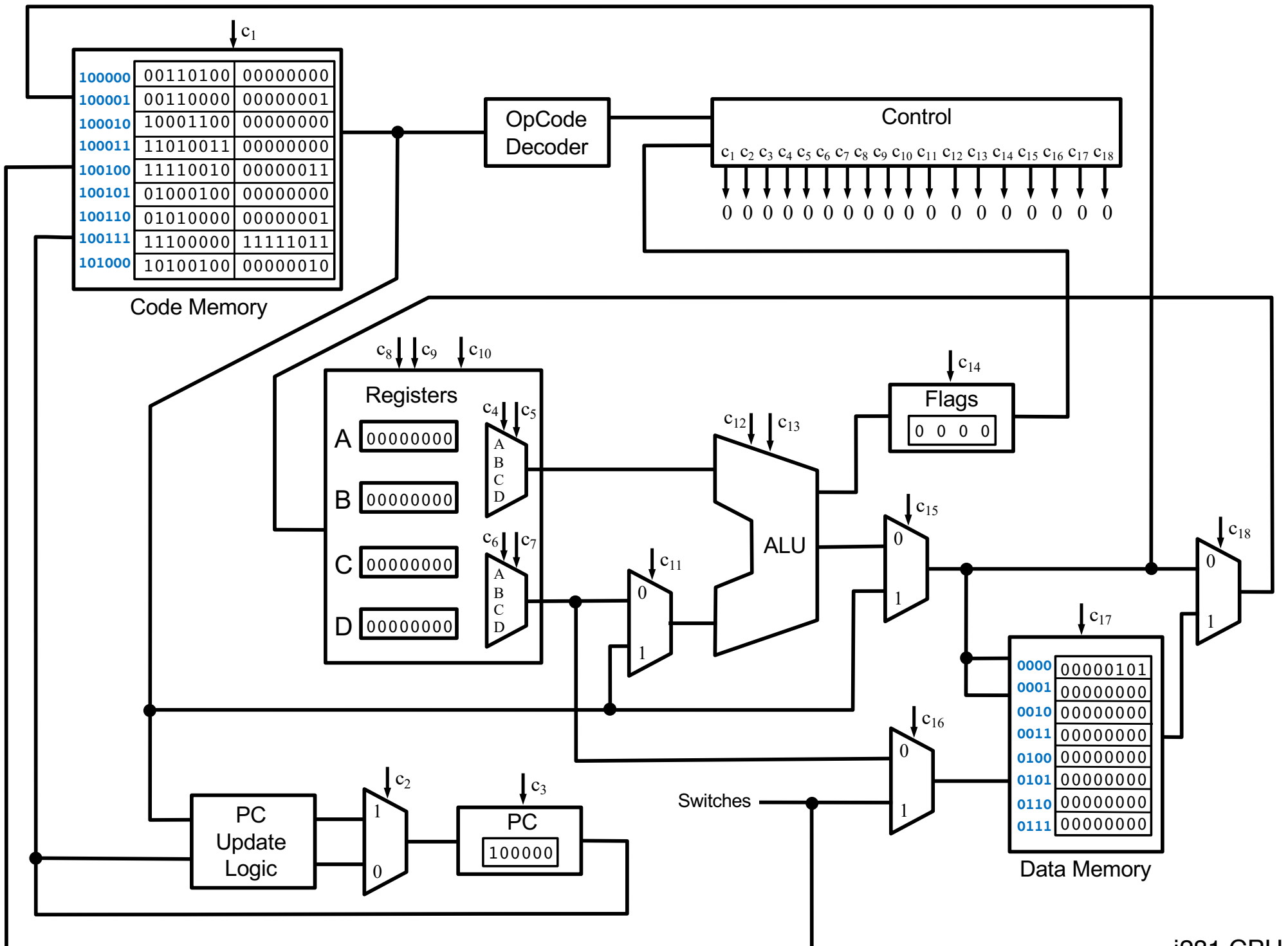
# **i281 CPU Architecture**

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*



 

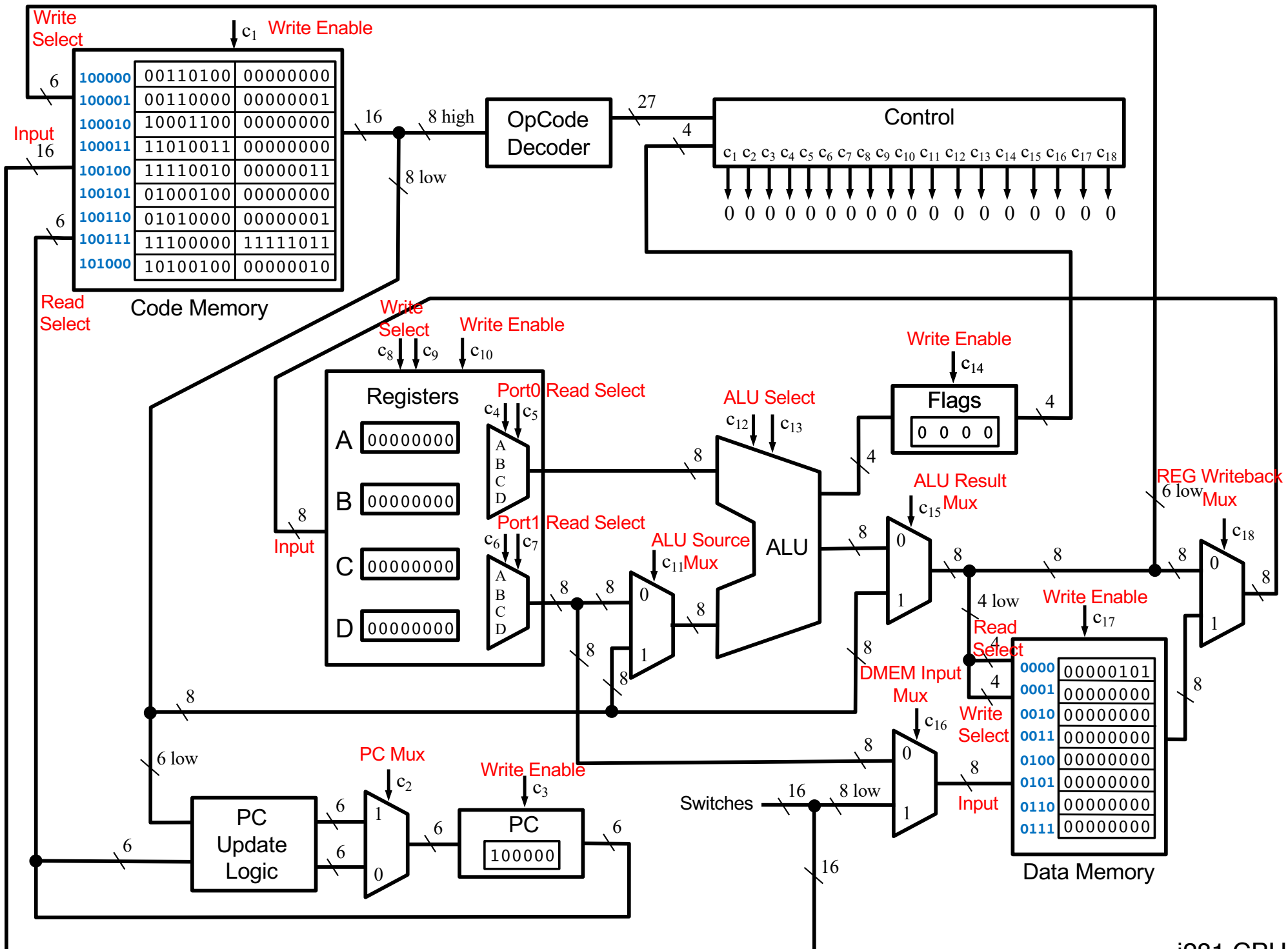

# Drawing Convention

- **Inputs enter from the left (for each box)**
- **Outputs exit from the right (for each box)**
- **Control lines are vertical arrows (come from the top)**

# i281 CPU

- **The CPU was designed specifically for this class 😊**

# i281 CPU

- **The CPU was designed specifically for this class 😊**
- **It was designed by:**  
**Kyung-Tae Kim and Alexander Stoytchev**




# **The CPU Components**

## The Code Memory (or Instruction Memory)


100000	00110100	00000000
100001	00110000	00000001
100010	10001100	00000000
100011	11010011	00000000
100100	11110010	00000011
100101	01000100	00000000
100110	01010000	00000001
100111	11110000	11111011
101000	10100100	00000010

Code Memory

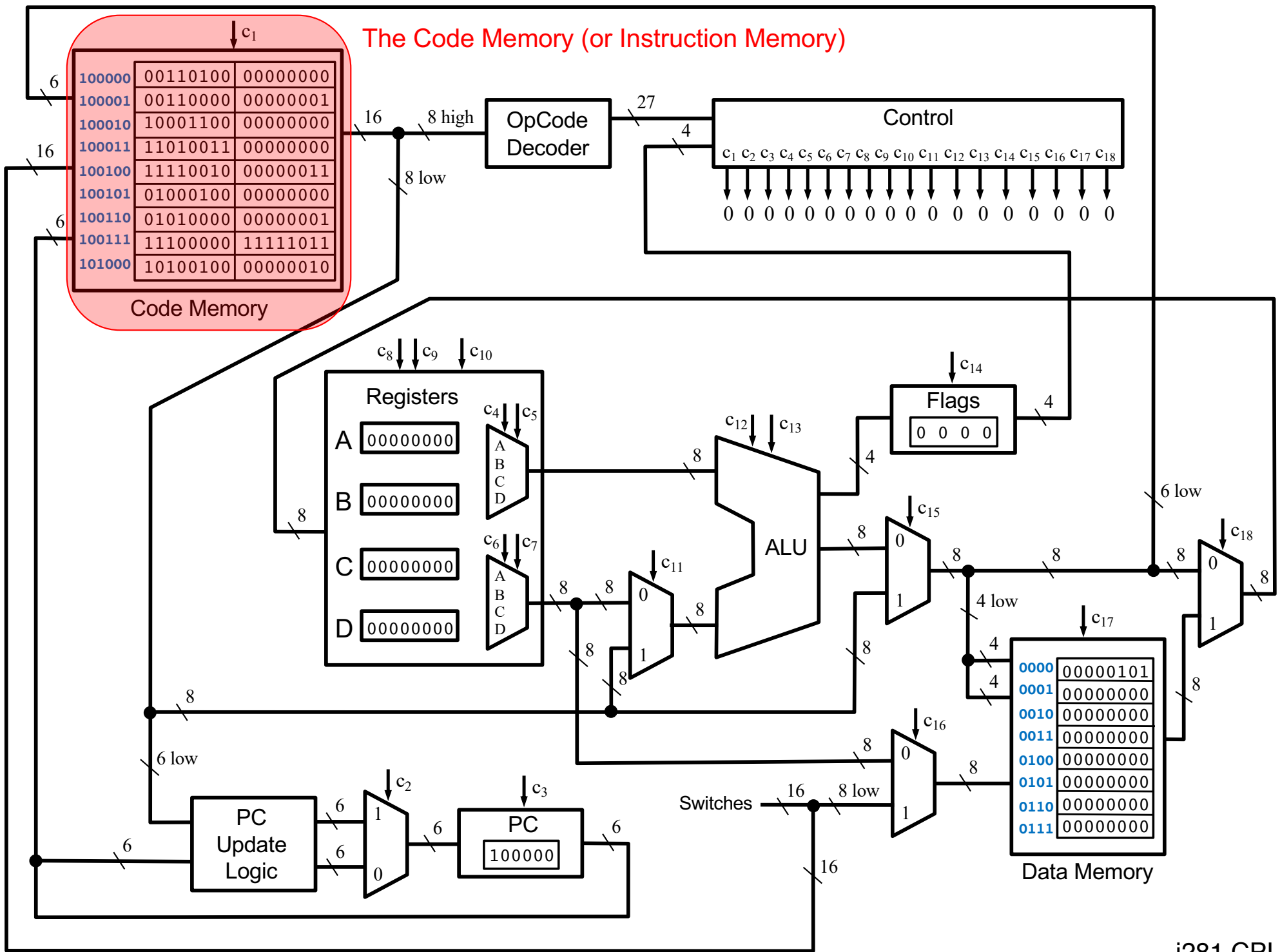



0000	00000101
0001	00000000
0010	00000000
0011	00000000
0100	00000000
0101	00000000
0110	00000000
0111	00000000


Data Memory

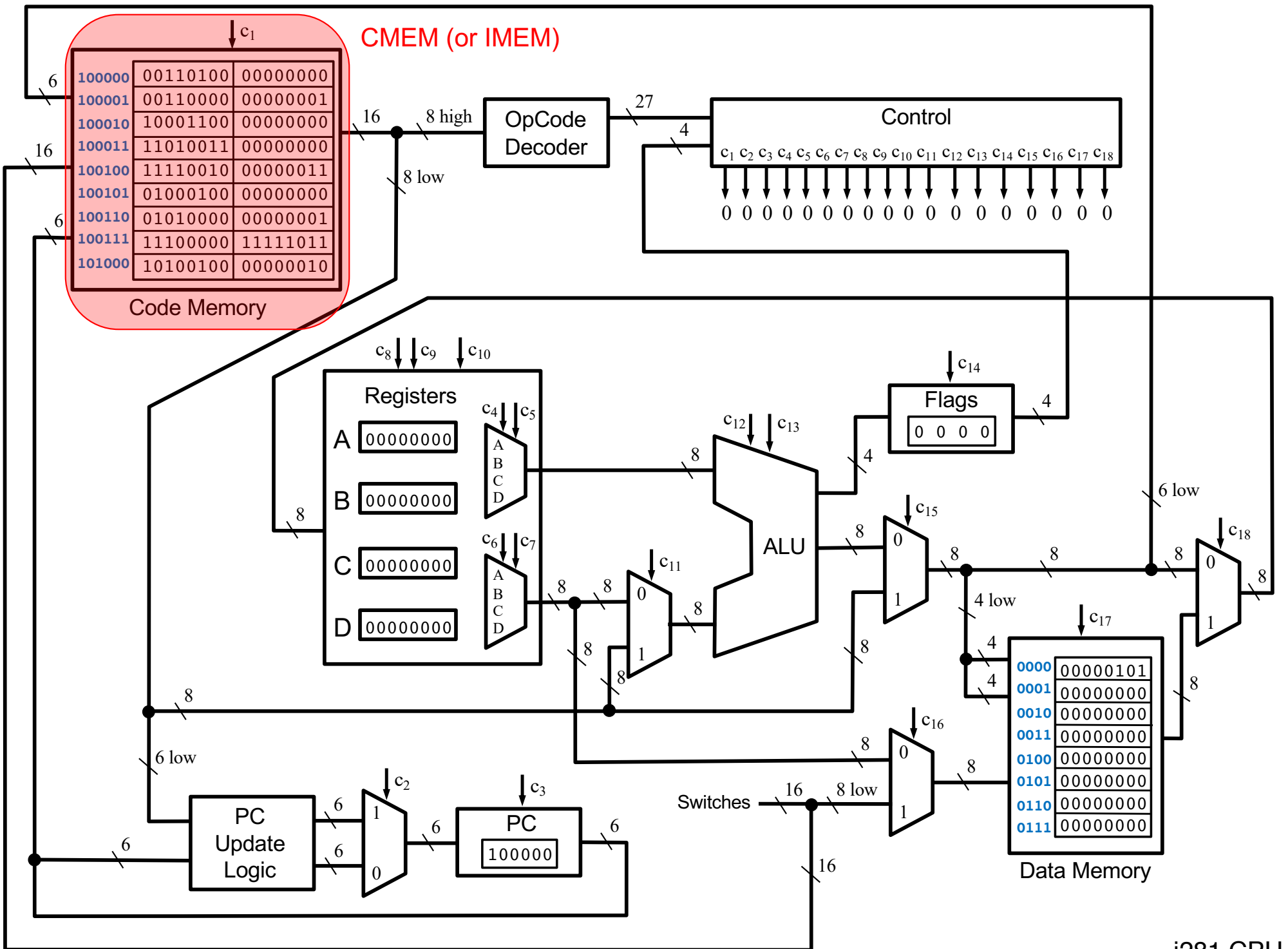



## The OpCode Decoder

 

 


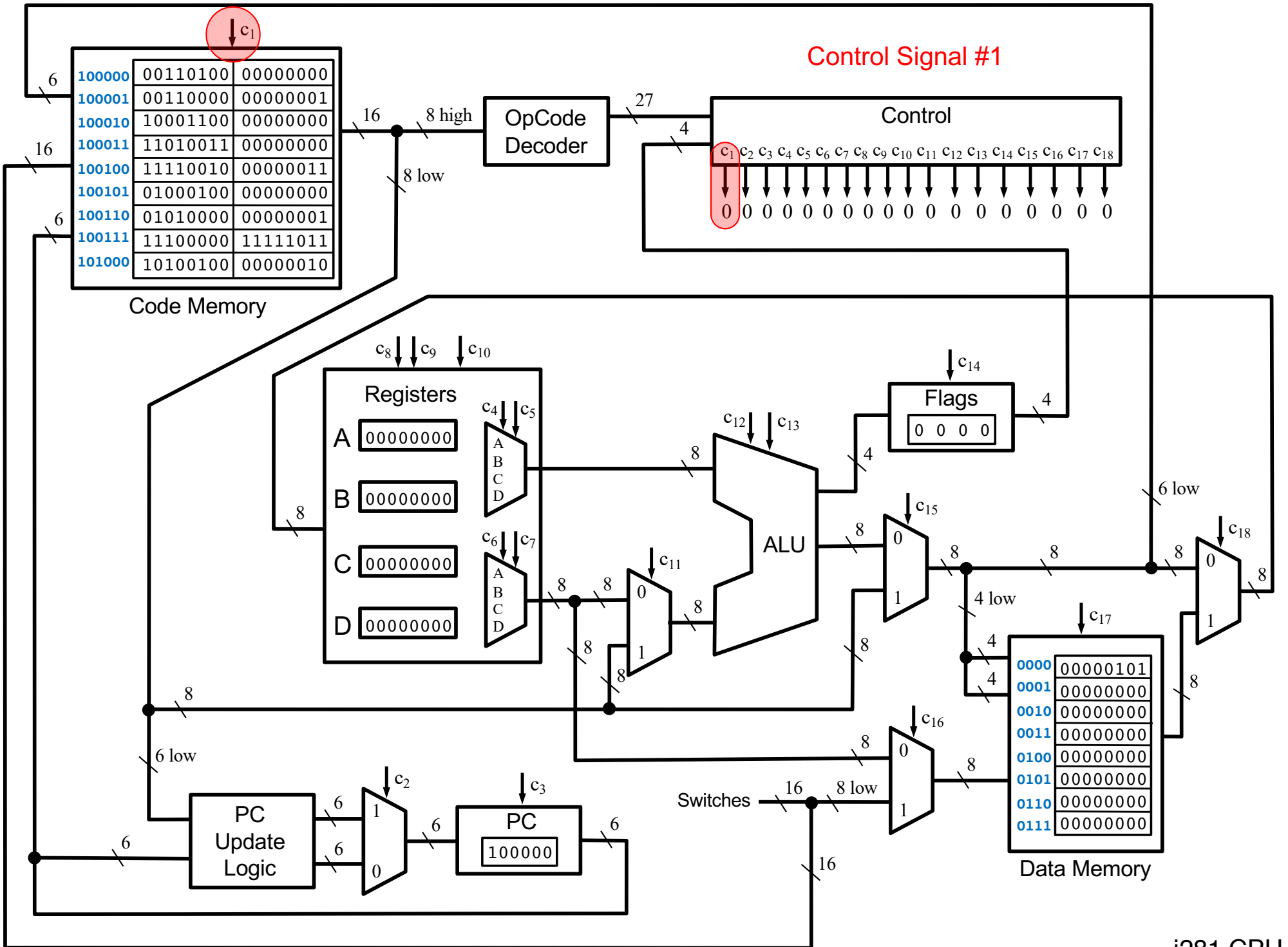


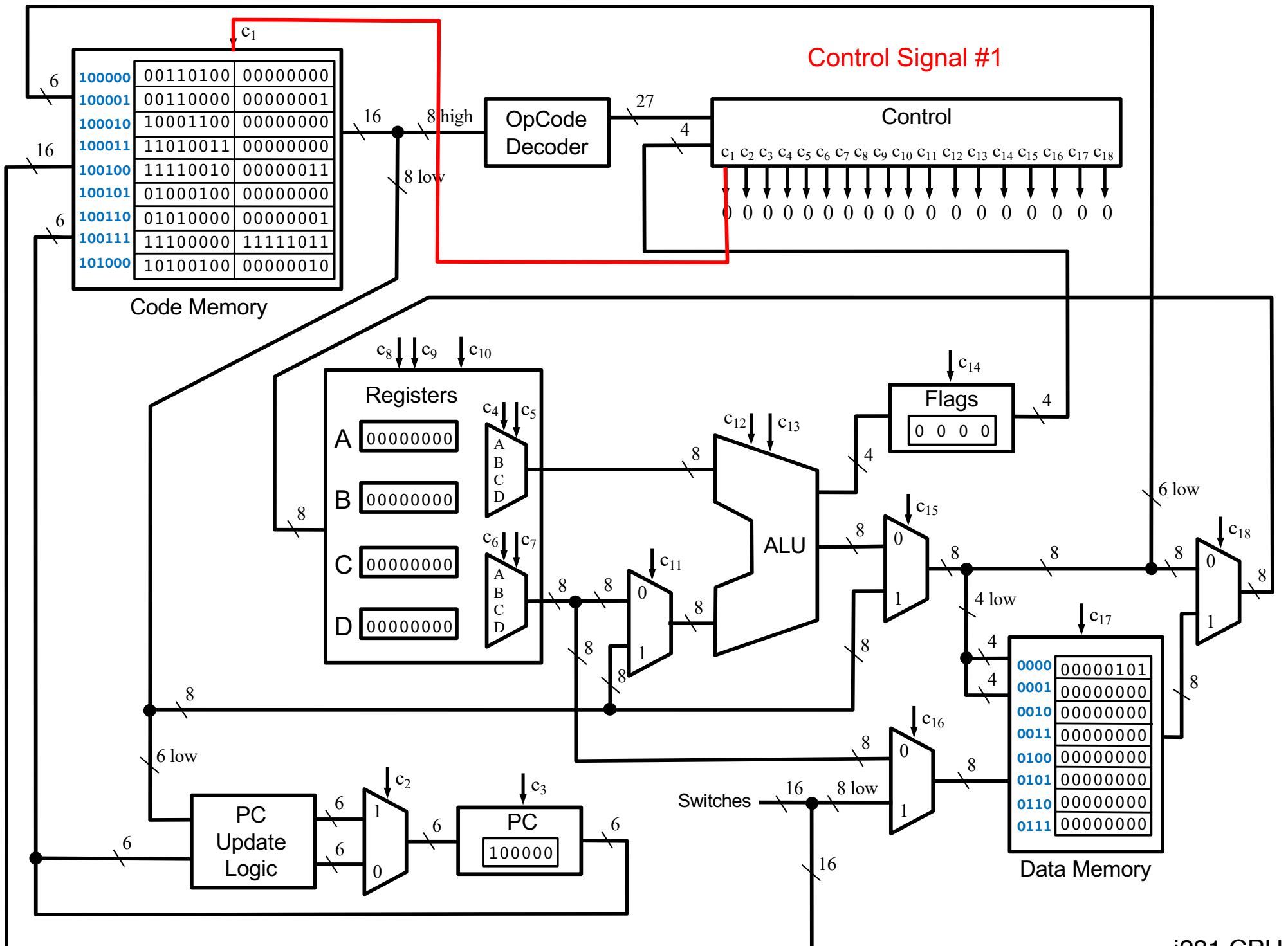


 





 

 


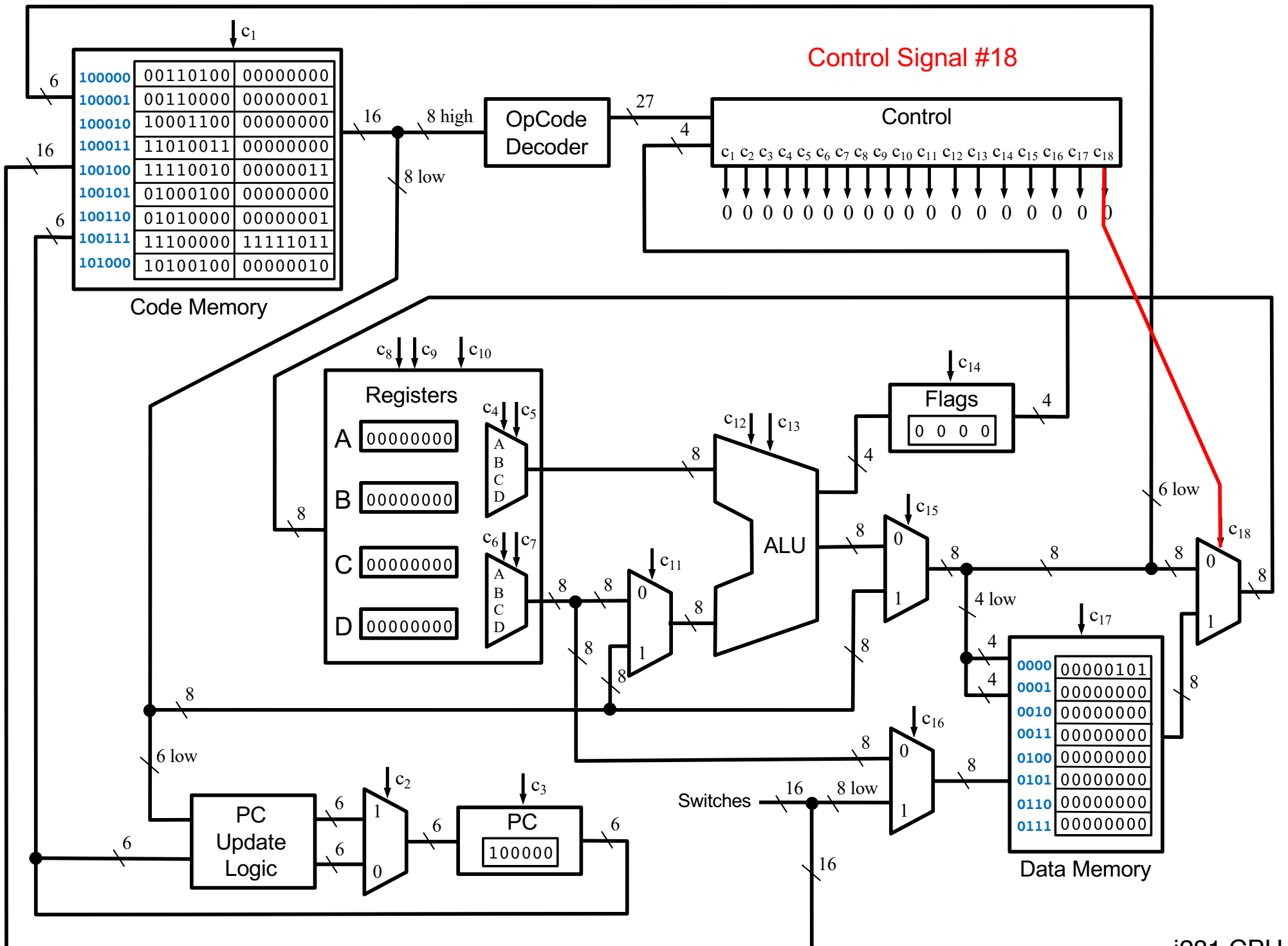


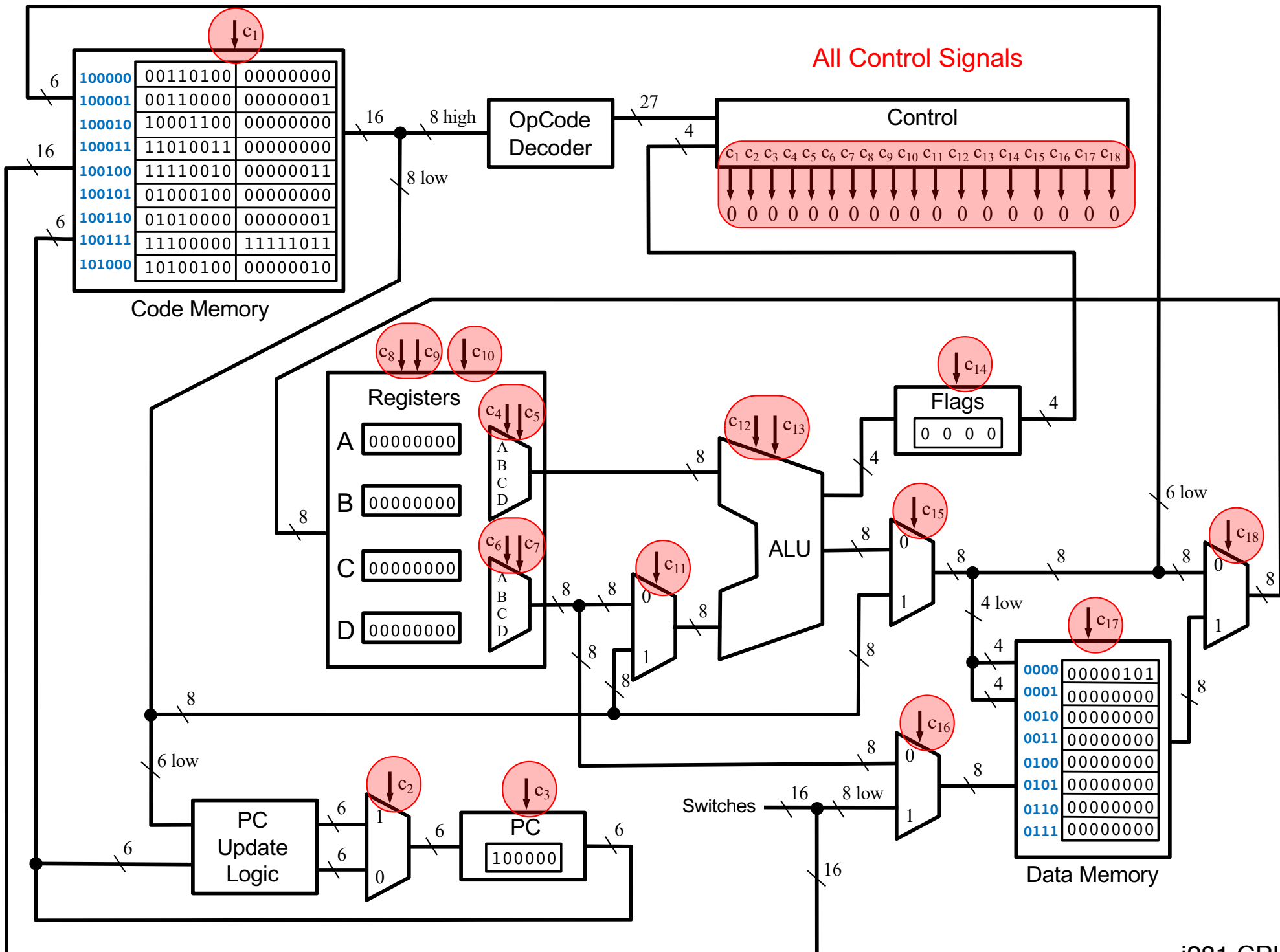


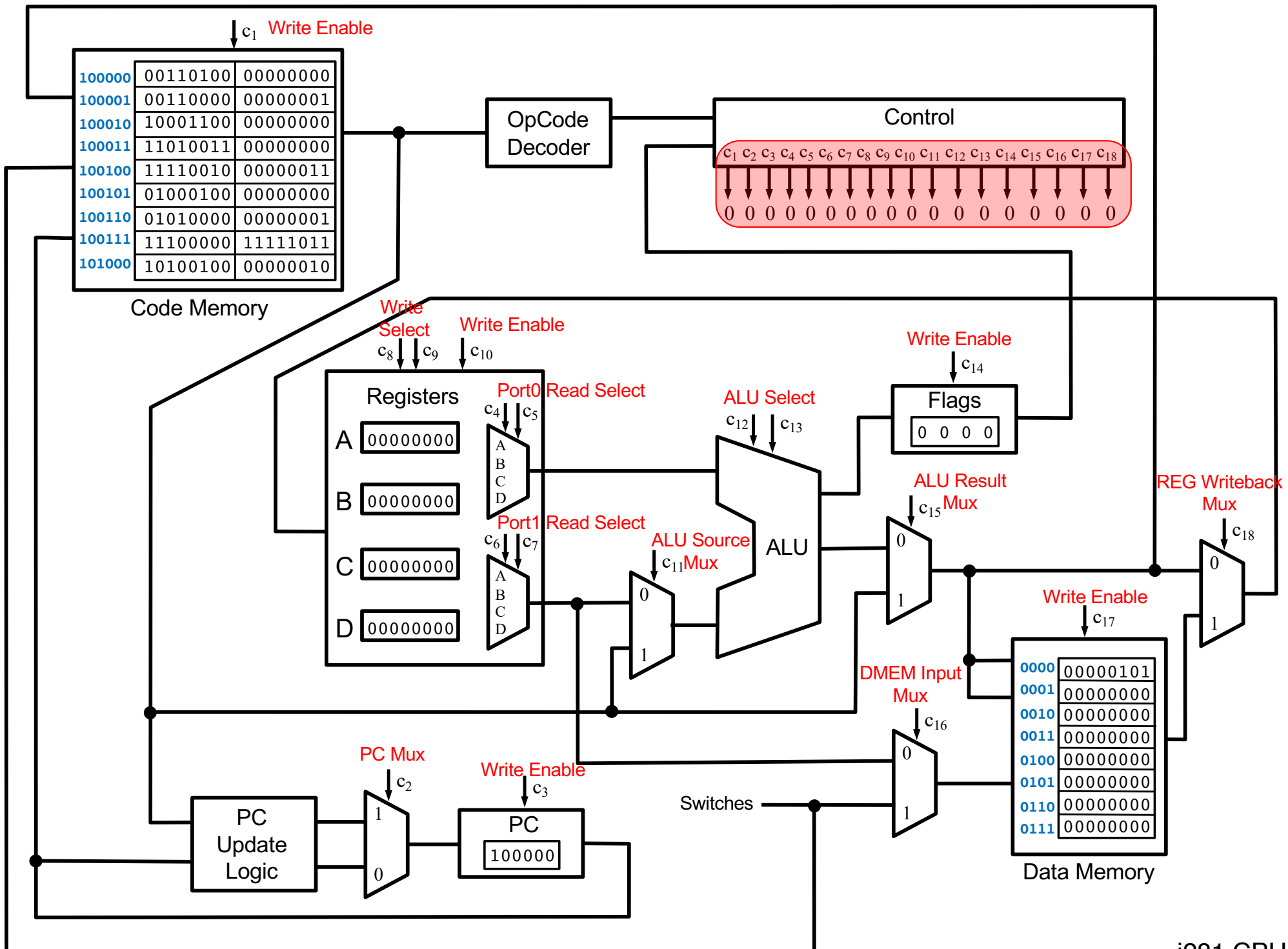

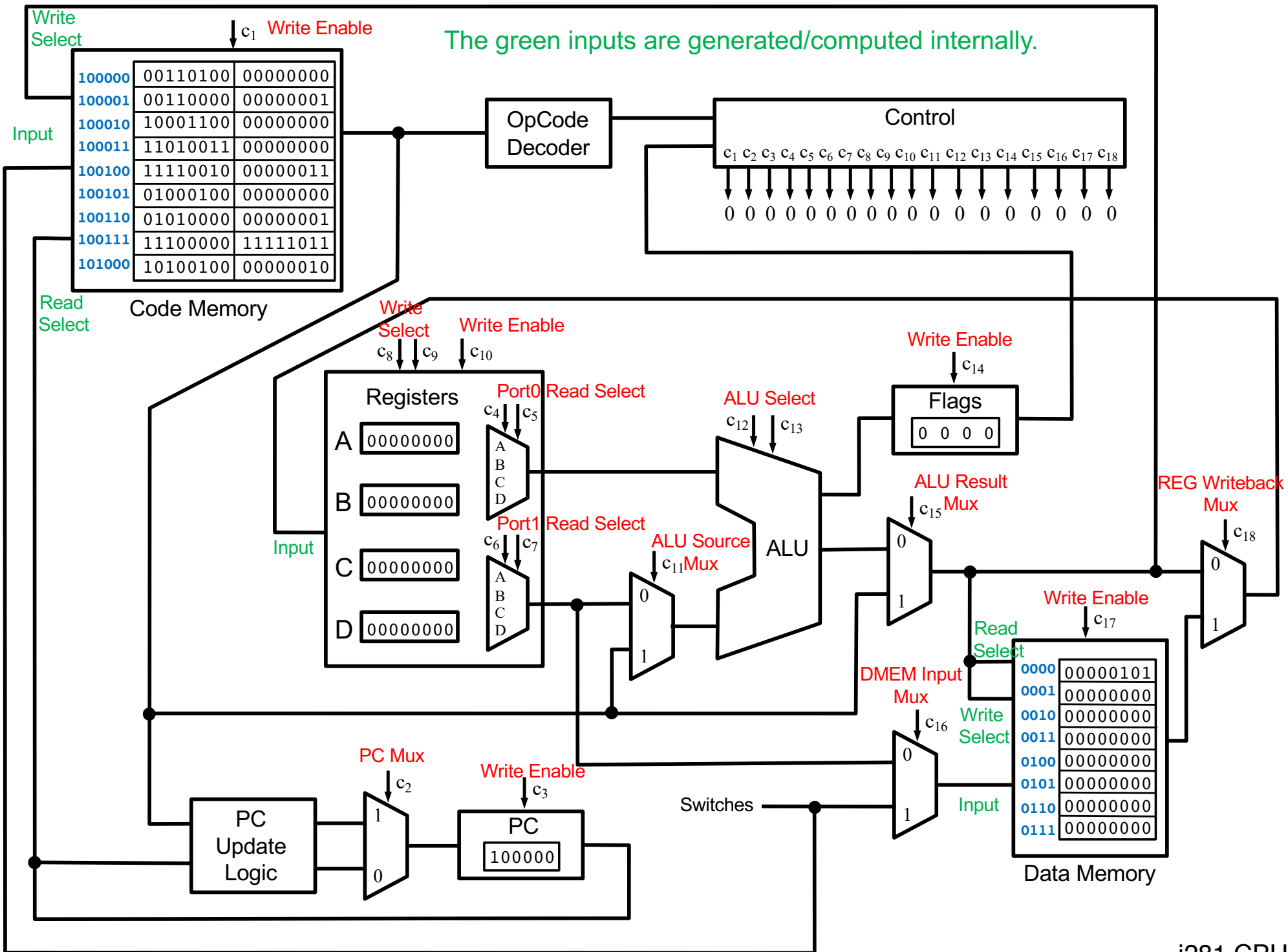
The green inputs are generated/computed internally.




 


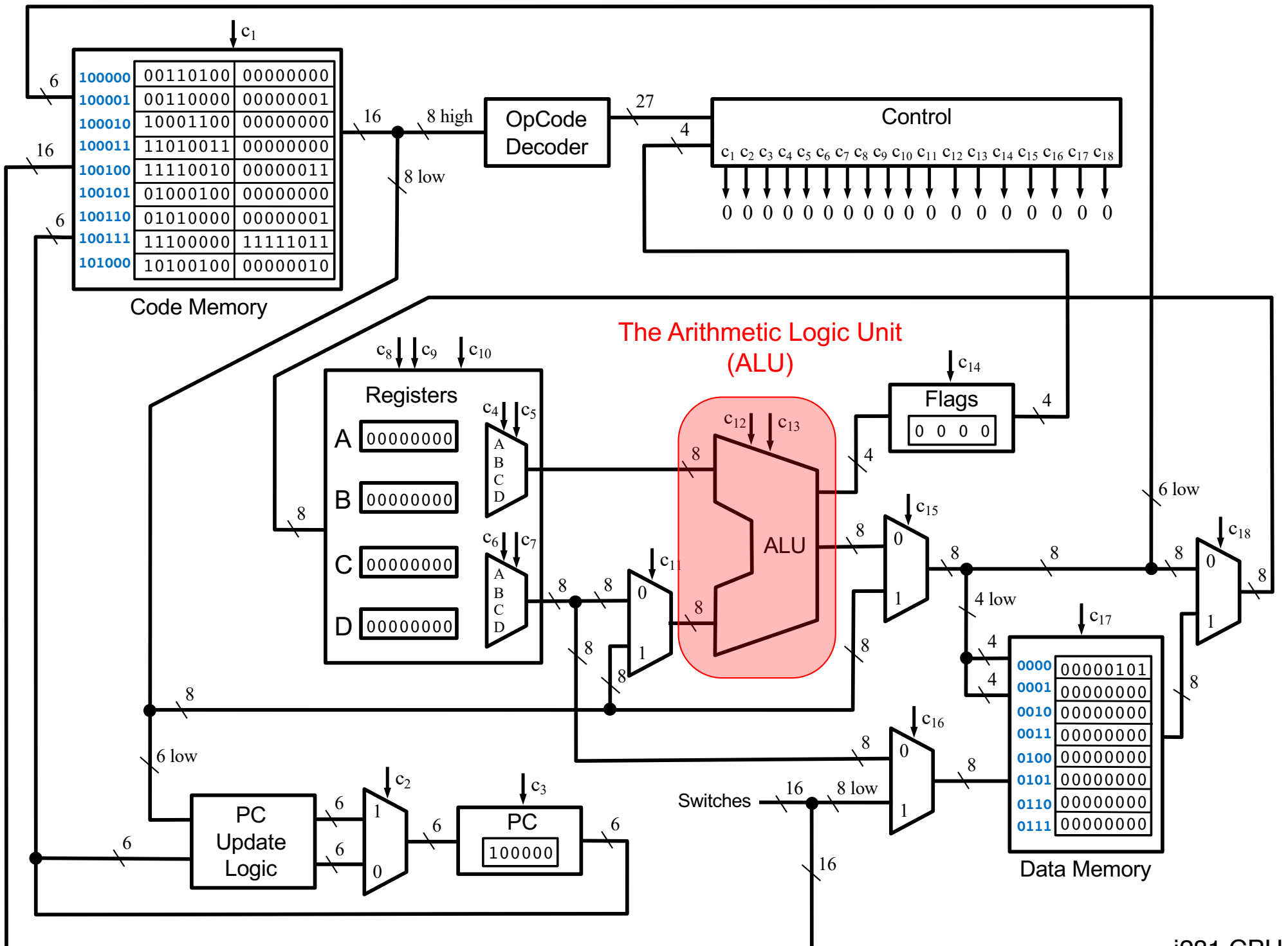





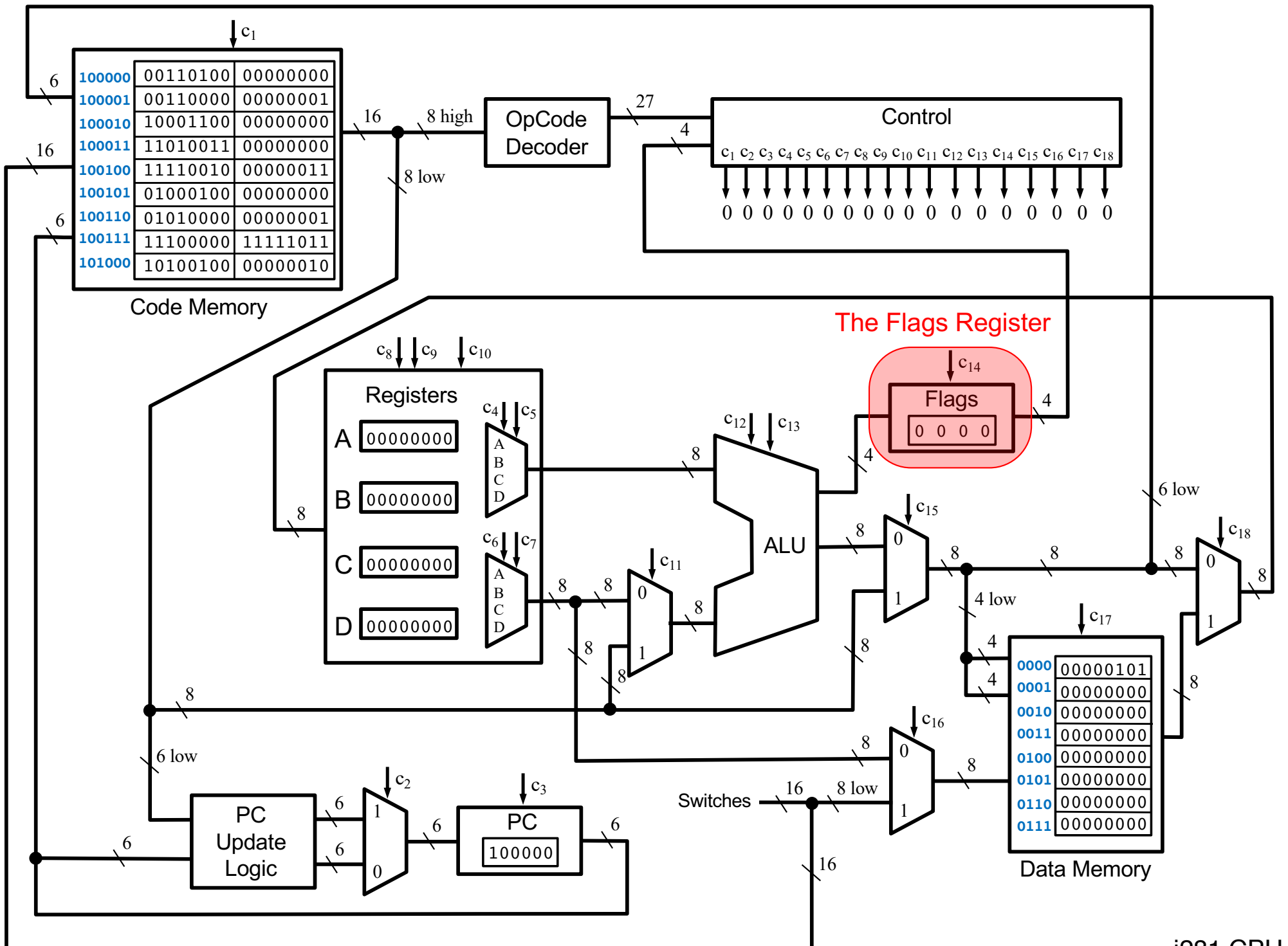

 


 

 


 

The Switches  
for User Input

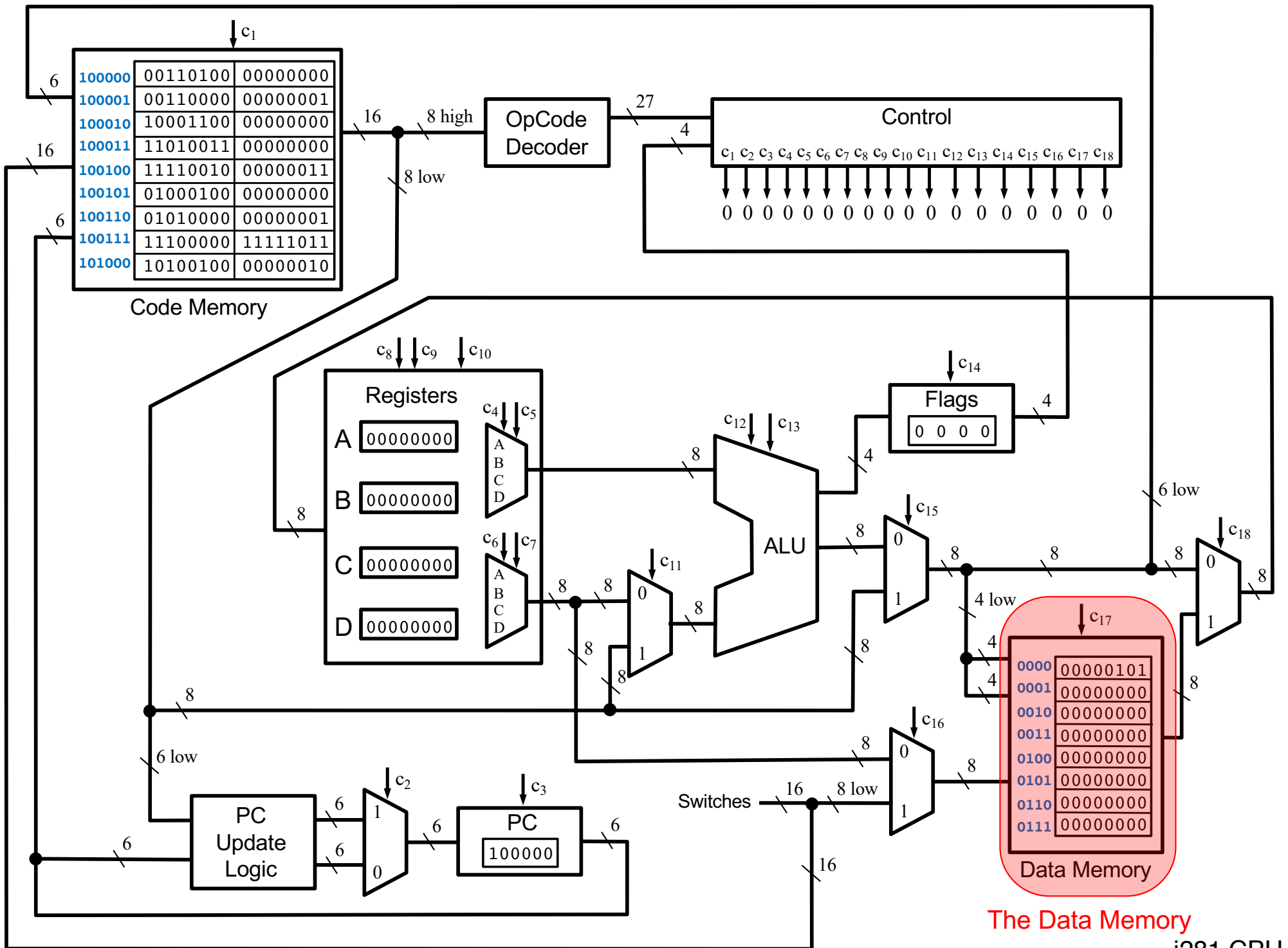

The Data Memory

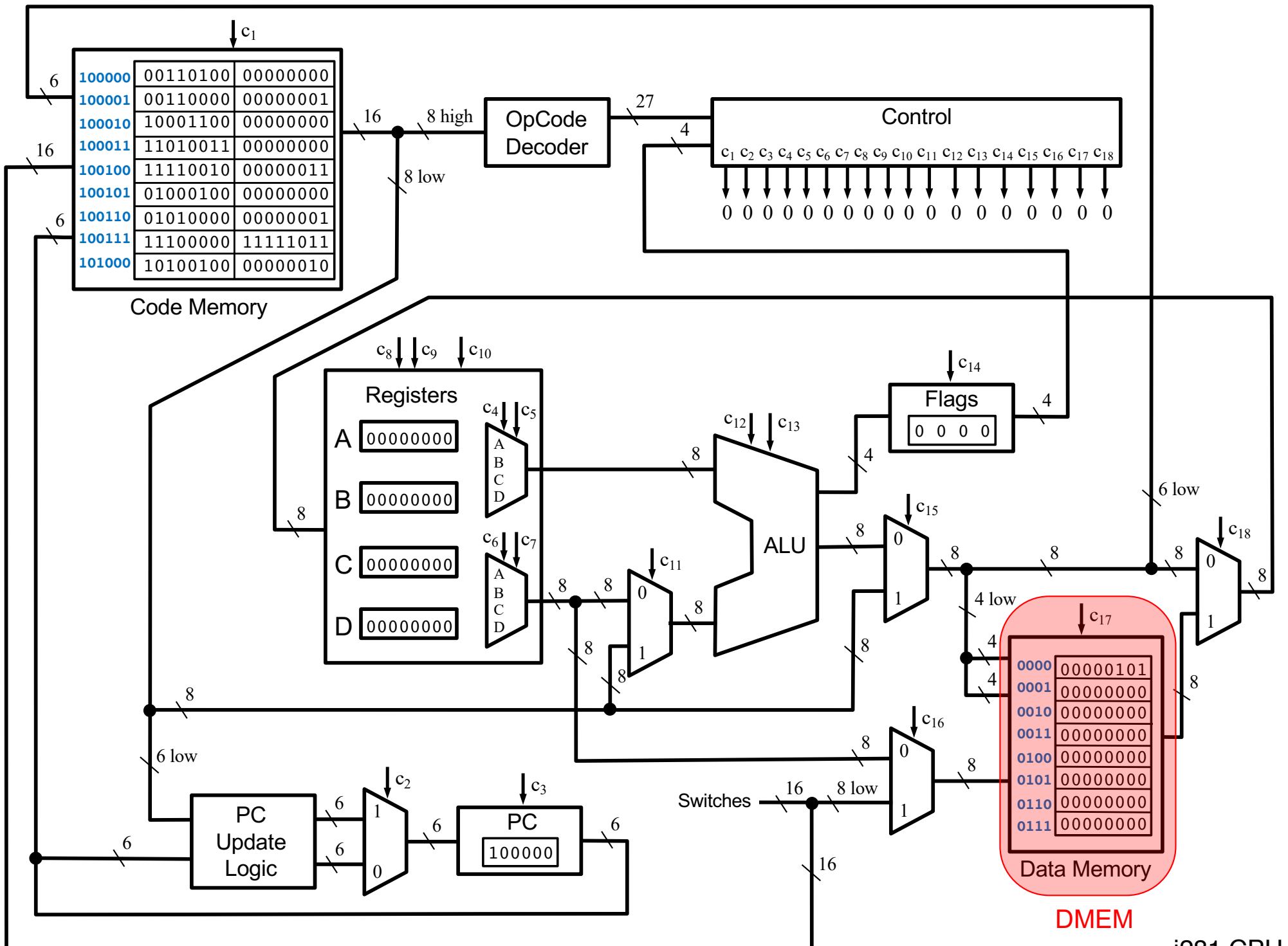


# **The Memory Layout**


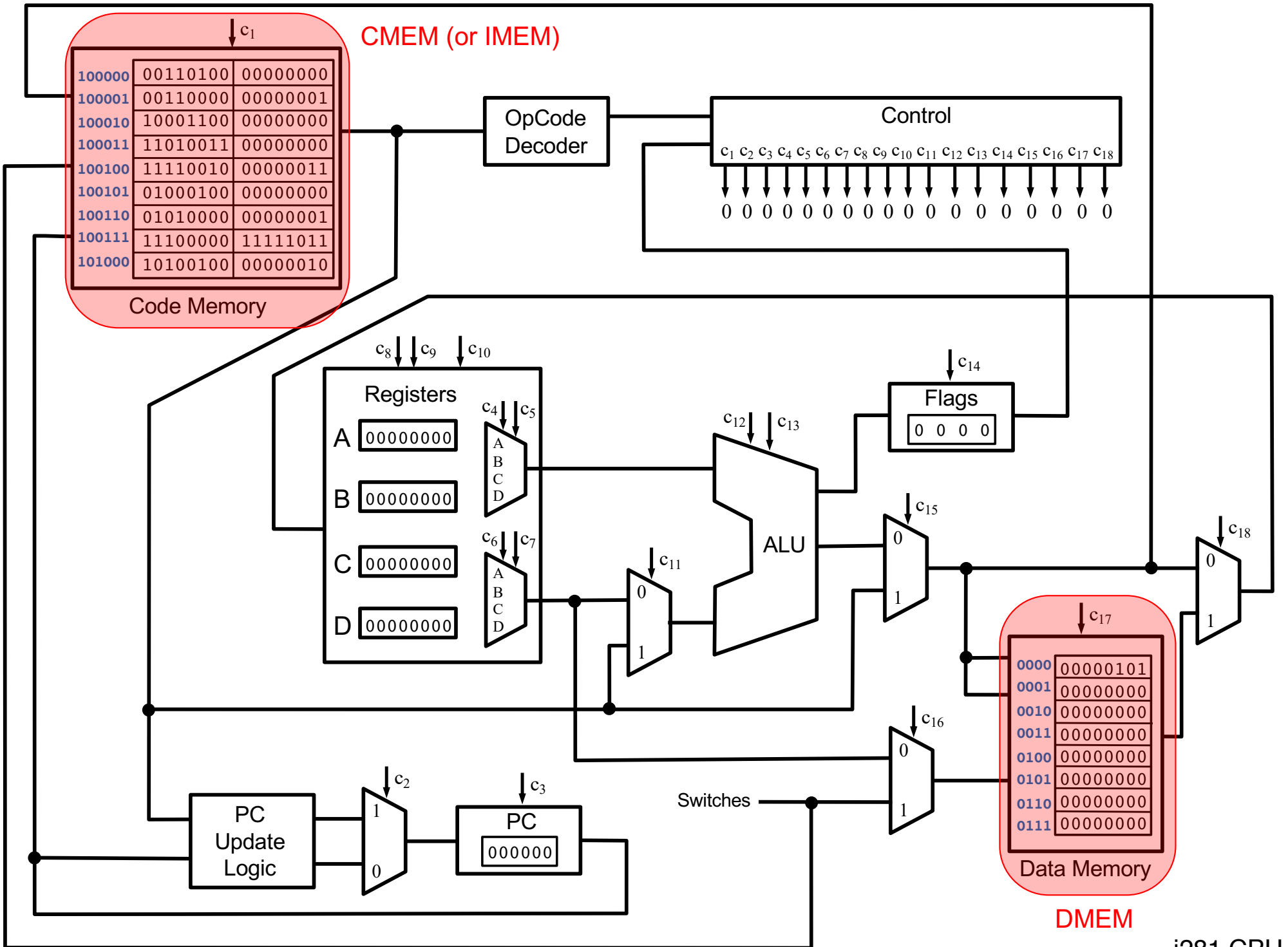
# Memory Layout

- **The i281 CPU uses two different memories**



i281 CPU

# Memory Layout

- **The i281 CPU uses two different memories**
- **Data Memory**
  - 16 x 8 bits
- **Code Memory**
  - 64 x 16 bits

# Memory Layout

- The i281 CPU uses two different memories
- Data Memory
  - 16 x 8 bits
- Code Memory
  - 64 x 16 bits
- Note that they have different number of bits

# Memory Layout

- The i281 CPU uses two different memories
- Data Memory
  - 16 x 8 bits ( only 16 bytes! )
- Code Memory
  - 64 x 16 bits ( only 128 bytes! )
- This is a combined total of 144 bytes!

# Memory Layout

- The i281 CPU uses two different memories
- Data Memory
  - 16 x 8 bits ( only 16 bytes! )
- Code Memory
  - 64 x 16 bits ( only 128 bytes! )
- This is a combined total of 144 bytes!
- Which is enough to represent 48 pixels on this slide!

# Data Memory Layout

- **Organized as one contiguous block**
- **Data Memory**
  - **Random access**
  - **Read/write memory**
  - **16 x 8 bits**
  - **Only 16 bytes!**

# Data Memory Layout

- **Organized as one contiguous block**
- **Data Memory**
  - **Random access**
  - **Read/write memory**
  - **16 x 8 bits**
  - **Only 16 bytes!**
- **Implemented as a register file with 16 registers, each of which is 8-bits wide.**
- **The register file has one read port and one write port. It also has a write enable input.**



# Video Card

- **Memory-mapped video memory**
- **The first 8 bytes of the data memory are connected to the 7-segment displays on the Altera board**
- **Writing to these memory cells automatically lights up the displays, which use only the 4 least significant bits**
- **In video game mode each LED is controlled separately using a different set of 7-segment decoders & all 8 bits**
- **The contents of the second 8 bytes of the data memory cannot be visualized, but programs can still use them**

# Data Memory Contents for the Bubble Sort Program

```
00000111
00000011
00000010
00000001
00000110
00000100
00000101
00001000
00000111
00000000
00000000
00000000
00000000
00000000
00000000
00000000
```

# Data Memory Contents for the Bubble Sort Program

Address	Data
0000	00000111
0001	00000011
0010	00000010
0011	00000001
0100	00000110
0101	00000100
0110	00000101
0111	00001000
1000	00000111
1001	00000000
1010	00000000
1011	00000000
1100	00000000
1101	00000000
1110	00000000
1111	00000000

# Data Memory Contents for the Bubble Sort Program

Address	Data	Comment
0000	00000111	//array[0]
0001	00000011	//array[1]
0010	00000010	//array[2]
0011	00000001	//array[3]
0100	00000110	//array[4]
0101	00000100	//array[5]
0110	00000101	//array[6]
0111	00001000	//array[7]
1000	00000111	//last
1001	00000000	//temp
1010	00000000	
1011	00000000	
1100	00000000	
1101	00000000	
1110	00000000	
1111	00000000	

# Memory-Mapped Video Memory

Address	Data
0000	00000111
0001	00000011
0010	00000010
0011	00000001
0100	00000110
0101	00000100
0110	00000101
0111	00001000
1000	00000111
1001	00000000
1010	00000000
1011	00000000
1100	00000000
1101	00000000
1110	00000000
1111	00000000

# Memory-Mapped Video Memory

Address	Data	
0000	00000111	→ 7
0001	00000011	→ 3
0010	00000010	→ 2
0011	00000001	→ 1
0100	00000110	→ 6
0101	00000100	→ 4
0110	00000101	→ 5
0111	00001000	→ 8
1000	00000111	
1001	00000000	
1010	00000000	
1011	00000000	
1100	00000000	
1101	00000000	
1110	00000000	
1111	00000000	


# Memory-Mapped Video Memory

Address	Data
0000	00000111 → 3
0001	00000011 → 3
0010	00000010 → 2
0011	00000001 → 1
0100	00000110 → 6
0101	00000100 → 4
0110	01100101 → 5
0111	00001000 → 8
1000	00000111
1001	00000000
1010	00000000
1011	00000000
1100	00000000
1101	00000000
1110	00000000
1111	00000000

Changing these bits will not affect what is displayed, but it will affect the program.

# Memory-Mapped Video Memory

Address	Data
0000	0 <b>1</b> 000111
0001	000 <b>1</b> 0011
0010	<b>1</b> 0000010
0011	0 <b>1</b> 000001
0100	000 <b>1</b> 0110
0101	<b>1</b> 0000100
0110	0 <b>1</b> 100101
0111	0 <b>1</b> 001000
1000	00000111
1001	00000000
1010	00000000
1011	00000000
1100	00000000
1101	00000000
1110	00000000
1111	00000000

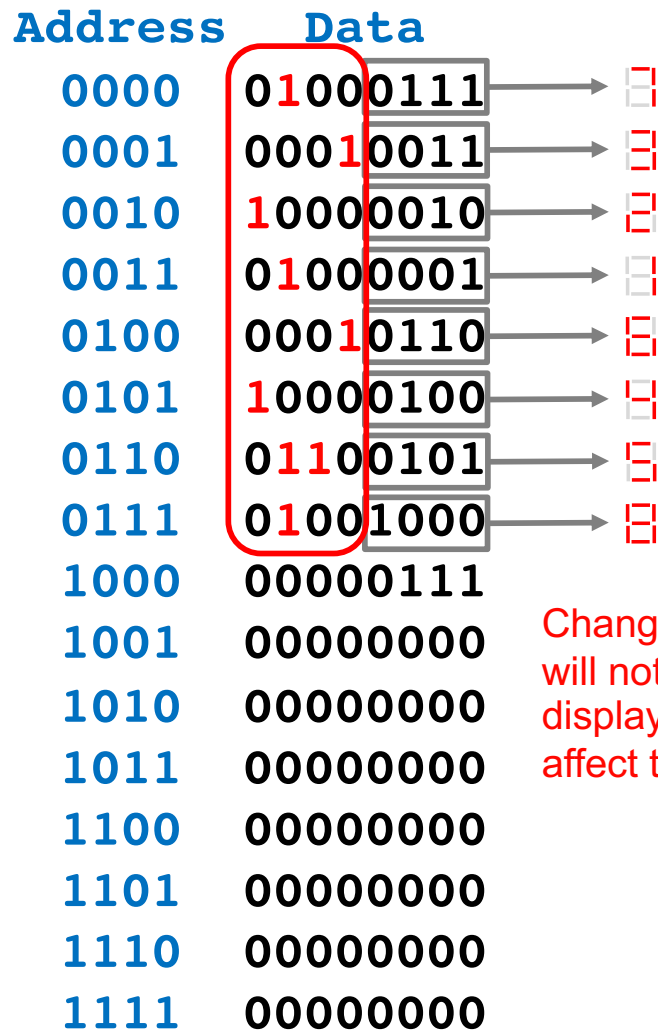

Changing these bits will not affect what is displayed, but it will affect the program.



# Memory-Mapped Video Memory

Address	Data	
0000	00000111	→ 1
0001	00000011	→ 3
0010	00000010	→ 2
0011	00000001	→ 1
0100	00000110	→ 3
0101	00000100	→ 4
0110	00000101	→ 5
0111	00001000	→ 8
1000	00000111	
1001	00000000	
1010	00000000	
1011	00000000	
1100	00000000	
1101	00000000	
1110	00000000	
1111	00000000	

This memory cell is used by the program, but it cannot be visualized on the 7-segment displays.

# Memory-Mapped Video Memory









Address	Data	
0000	00000111	→ 1
0001	00000011	→ 3
0010	00000010	→ 2
0011	00000001	→ 1
0100	00000110	→ 6
0101	00000100	→ 4
0110	00000101	→ 5
0111	00001000	→ 8
1000	00000111	
1001	00000000	
1010	00000000	
1011	00000000	
1100	00000000	
1101	00000000	
1110	00000000	
1111	00000000	

All of these cannot be visualized on the 7-segment displays.









# Memory-Mapped Video Memory in Video Game Mode


Address	Data
0000	00000000
0001	00000000
0010	00000000
0011	00000000
0100	01111001
0101	01010100
0110	01011110
0111	00000000
1000	00000000
1001	00000000
1010	00000000
1011	00000000
1100	00000000
1101	00000000
1110	00000000
1111	00000000

# Memory-Mapped Video Memory in Video Game Mode

Address	Data
0000	00000000 → 
0001	00000000 → 
0010	00000000 → 
0011	00000000 → 
0100	01111001 → 
0101	01010100 → 
0110	01011110 → 
0111	00000000 → 
1000	00000000
1001	00000000
1010	00000000
1011	00000000
1100	00000000
1101	00000000
1110	00000000
1111	00000000

# Memory-Mapped Video Memory in Video Game Mode


Address	Data
0000	00000000 → 
0001	00000000 → 
0010	00000000 → 
0011	00000000 → 
0100	01111001 → 
0101	01010100 → 
0110	01011110 → 
0111	00000000 → 
1000	00000000
1001	00000000
1010	00000000
1011	00000000
1100	00000000
1101	00000000
1110	00000000
1111	00000000

 


In this case the last 7 bits are used and each controls one of the 7 LEDs.
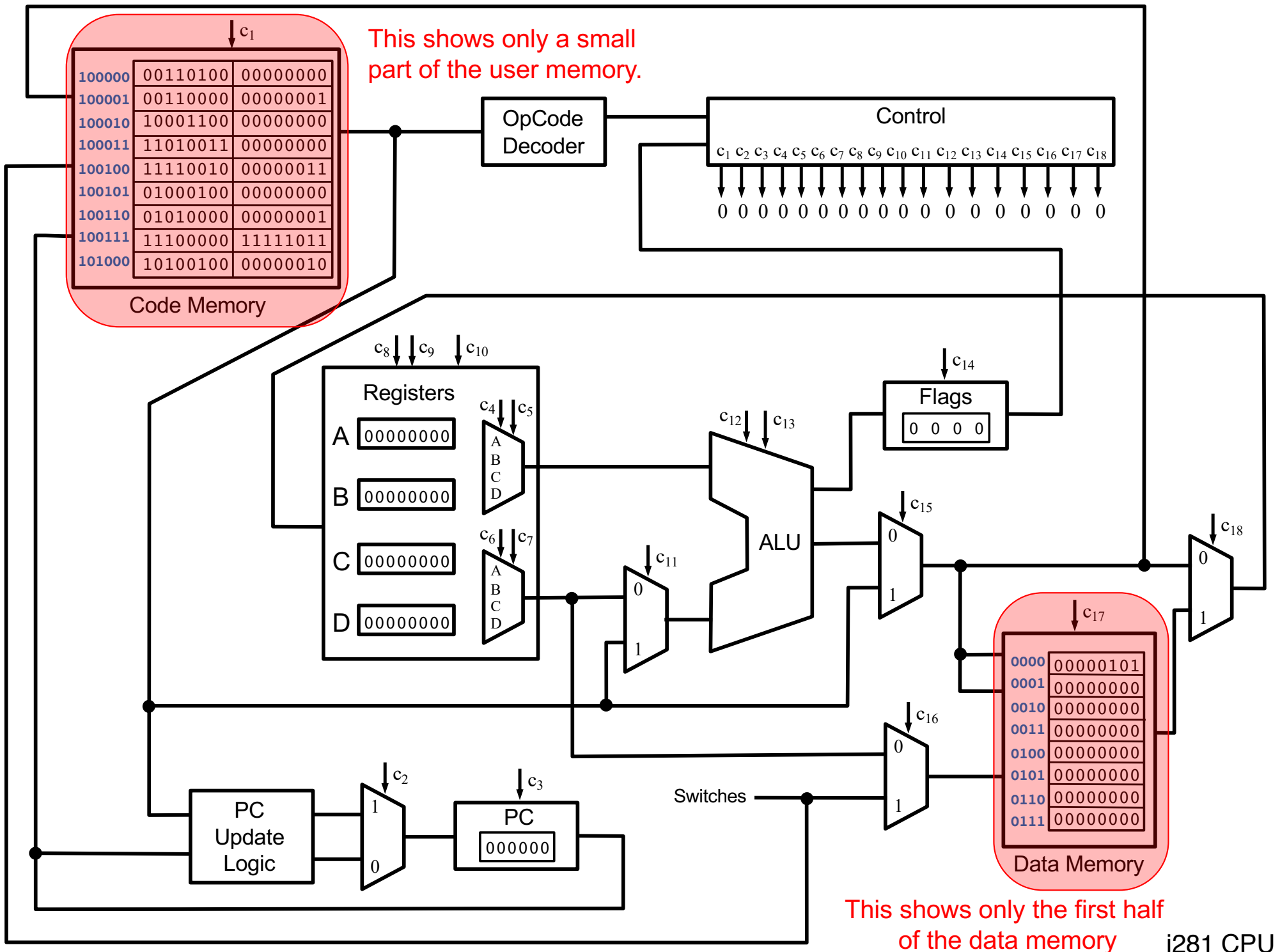
# Code Memory Layout


- **Split into two parts**
- **BIOS Code Memory (addresses 0 to 31)**
  - Read only memory
  - 32 x 16 bits
- **User Code Memory (addresses 32 to 63)**
  - Read only memory (in User mode)
  - Read/Write memory (in BIOS mode)
  - 32 x 16 bits




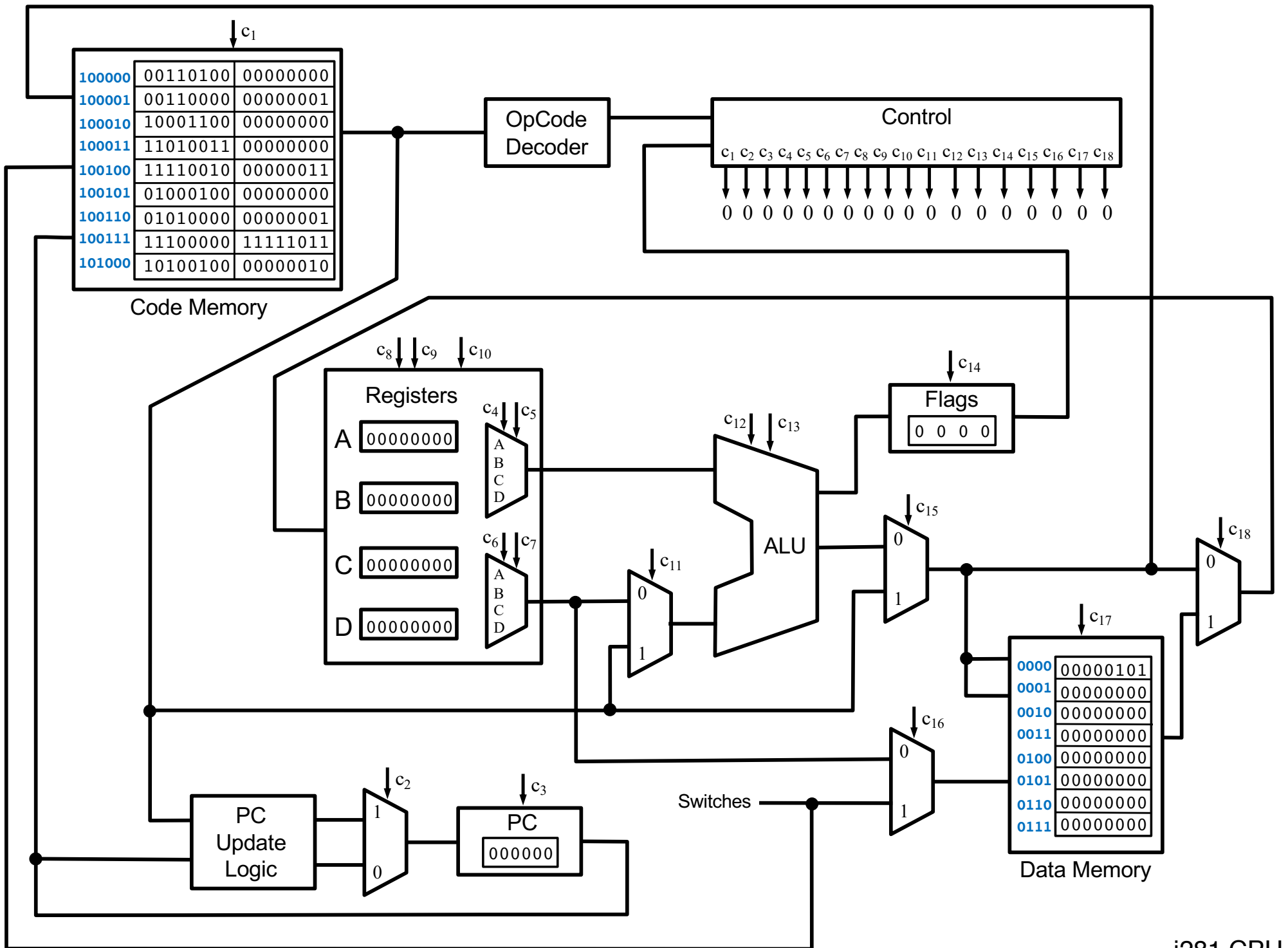






# **The OPCODE Decoder**

 


 

 


 

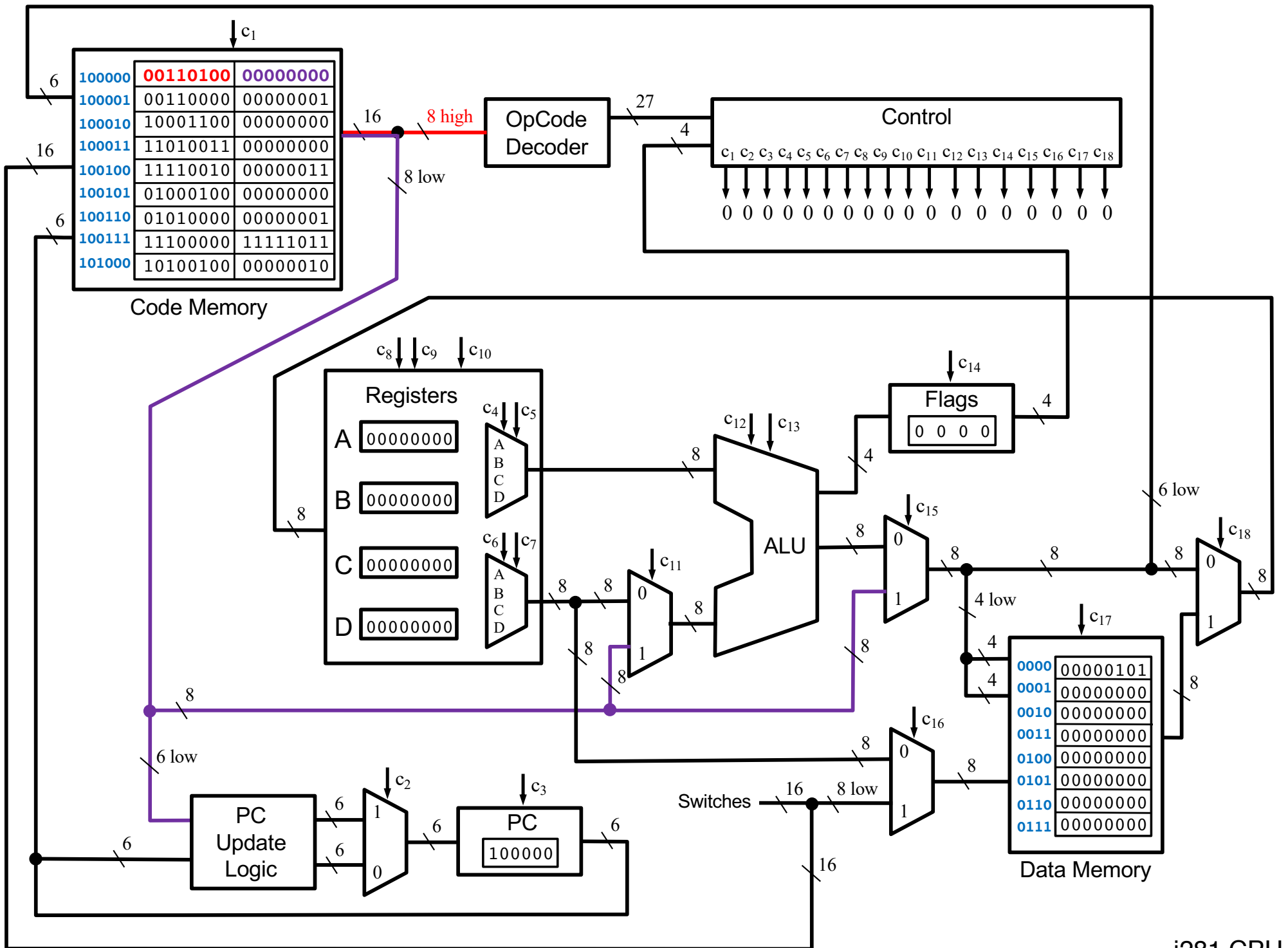


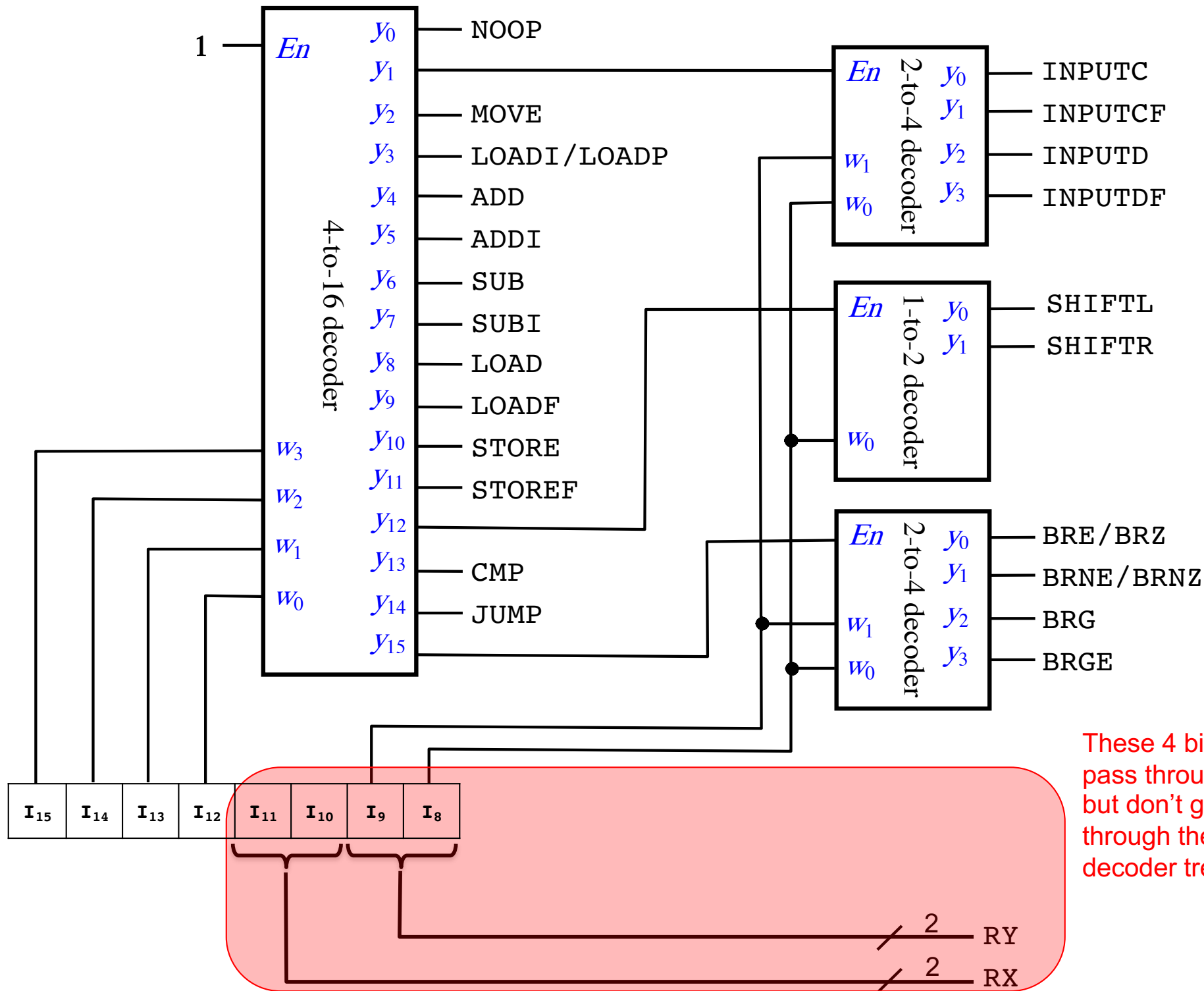

 These 4 bits pass through, but don't go through the decoder tree.







 



These are their names used in the hardware design.

<b>I<sub>15</sub></b>	<b>I<sub>14</sub></b>	<b>I<sub>13</sub></b>	<b>I<sub>12</sub></b>	<b>I<sub>11</sub></b>	<b>I<sub>10</sub></b>	<b>I<sub>9</sub></b>	<b>I<sub>8</sub></b>
-----------------------	-----------------------	-----------------------	-----------------------	-----------------------	-----------------------	----------------------	----------------------

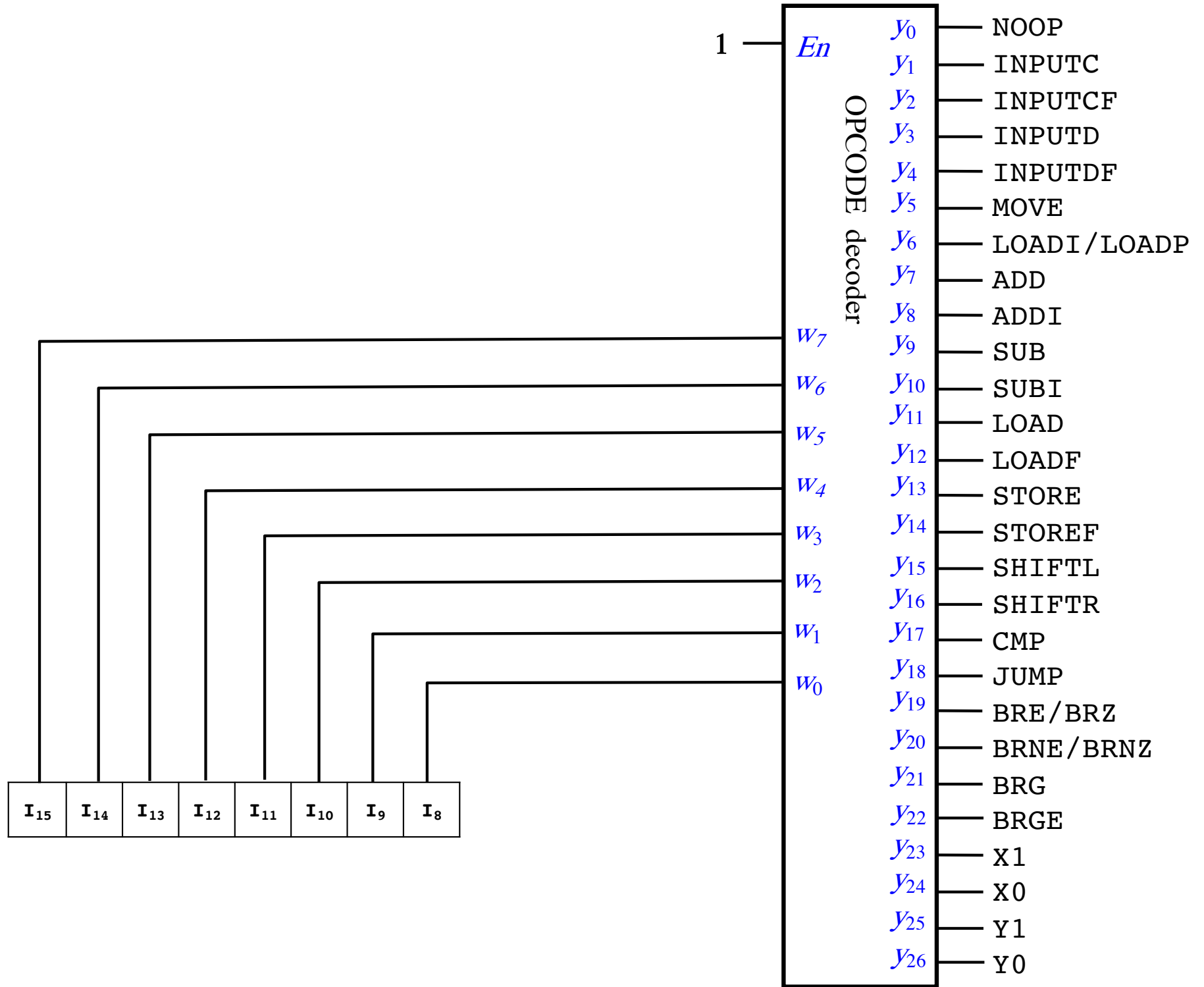


 

 

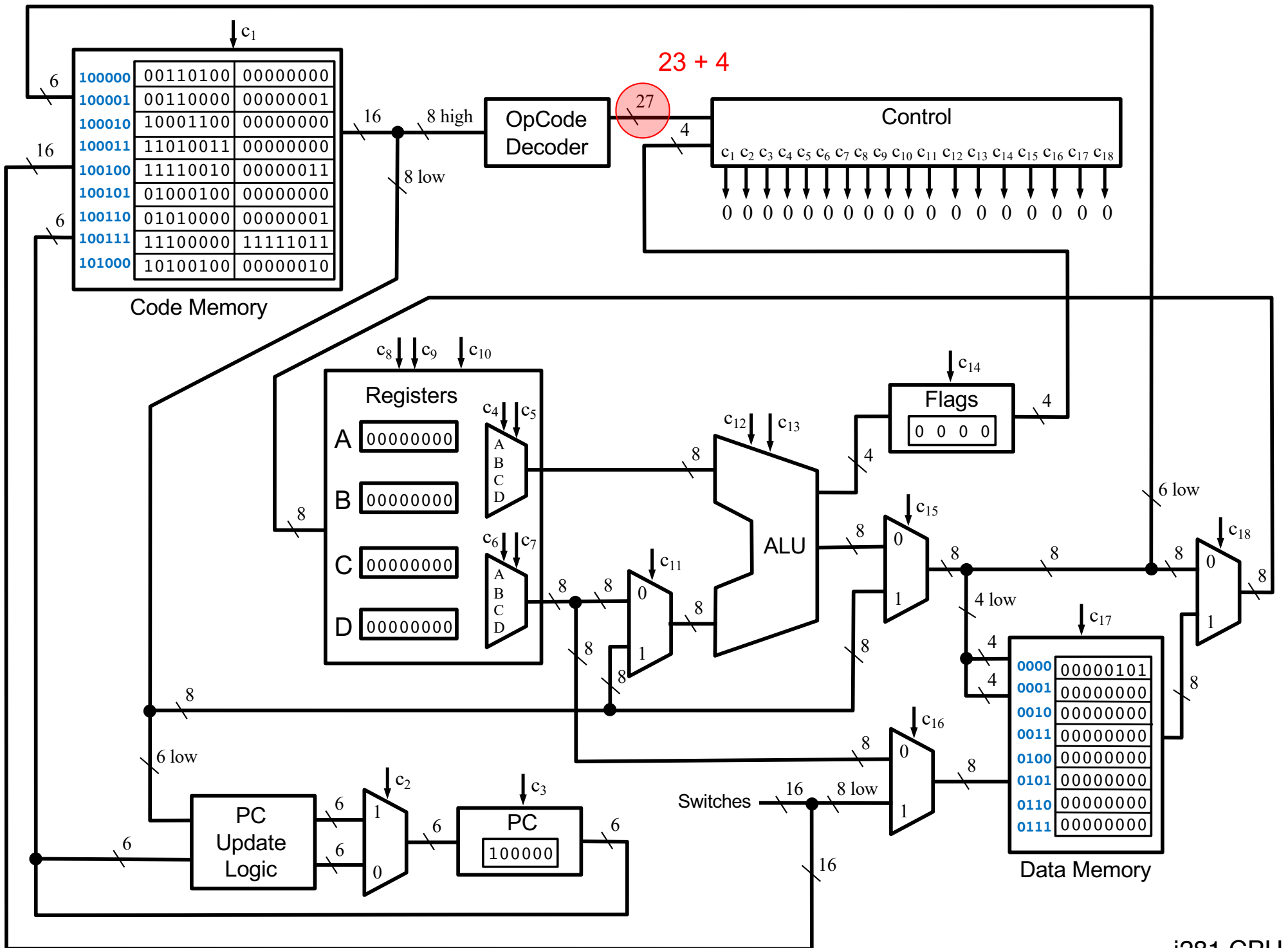

# **The Control Logic**

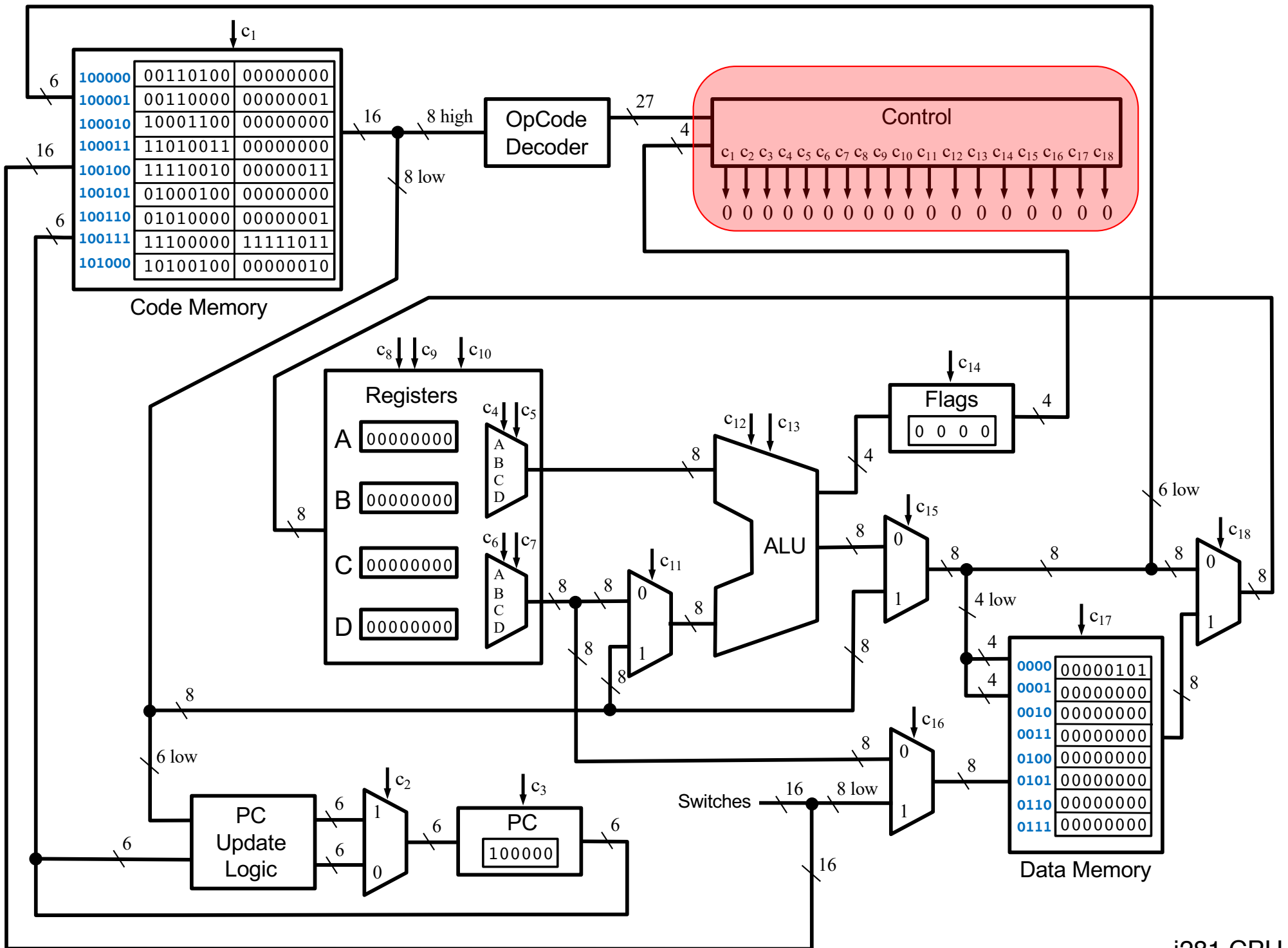













	C <sub>1</sub>	C <sub>2</sub>	C <sub>3</sub>	C <sub>4</sub>	C <sub>5</sub>	C <sub>6</sub>	C <sub>7</sub>	C <sub>8</sub>	C <sub>9</sub>	C <sub>10</sub>	C <sub>11</sub>	C <sub>12</sub>	C <sub>13</sub>	C <sub>14</sub>	C <sub>15</sub>	C <sub>16</sub>	C <sub>17</sub>	C <sub>18</sub>
	IMEM_WRITE_ENABLE	PROGRAM_COUNTER_MUX	PROGRAM_COUNTER_WRITE_EN	REGISTERS_PORT0_SELECT1	REGISTERS_PORT0_SELECT0	REGISTERS_PORT1_SELECT1	REGISTERS_PORT1_SELECT0	REGISTERS_WRITE_SELECT1	REGISTERS_WRITE_SELECT0	REGISTERS_WRITE_ENABLE	ALU_SOURCE_MUX	ALU_SELECT1	ALU_SELECT0	FLAGS_WRITE_ENABLE	ALU_RESUT_MUX	DMEM_INPUT_MUX	DMEM_WRITE_ENABLE	REG_WRITEBACK_MUX
NOOP			1															
INPUTC	1		1												1			
INPUTCF	1		1	X1	X0						1	1						
INPUTD			1												1	1	1	
INPUTDF			1	X1	X0						1	1				1	1	
MOVE			1	Y1	Y0			X1	X0	1	1	1						
LOADI/LOADP			1					X1	X0	1					1			
ADD			1	X1	X0	Y1	Y0	X1	X0	1		1		1				
ADDI			1	X1	X0			X1	X0	1	1	1		1				
SUB			1	X1	X0	Y1	Y0	X1	X0	1		1	1	1				
SUBI			1	X1	X0			X1	X0	1	1	1	1	1				
LOAD			1					X1	X0	1					1			1
LOADF			1	Y1	Y0			X1	X0	1	1	1						1
STORE			1			X1	X0								1		1	
STOREF			1	Y1	Y0	X1	X0				1	1					1	
SHIFTL			1	X1	X0			X1	X0	1				1				
SHIFTR			1	X1	X0			X1	X0	1			1	1				
CMP			1	X1	X0	Y1	Y0					1	1	1				
JUMP		1	1															
BRE/BRZ		B1	1															
BRNE/BRNZ		B2	1															
BRG		B3	1															
BRGE		B4	1															

Taken from these bits of the instruction

I <sub>15</sub>	I <sub>14</sub>	I <sub>13</sub>	I <sub>12</sub>	I <sub>11</sub>	I <sub>10</sub>	I <sub>9</sub>	I <sub>8</sub>	I <sub>7</sub>	I <sub>6</sub>	I <sub>5</sub>	I <sub>4</sub>	I <sub>3</sub>	I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>
						Y <sub>1</sub>	Y <sub>0</sub>								

	C <sub>1</sub>	C <sub>2</sub>	C <sub>3</sub>	C <sub>4</sub>	C <sub>5</sub>	C <sub>6</sub>	C <sub>7</sub>	C <sub>8</sub>	C <sub>9</sub>	C <sub>10</sub>	C <sub>11</sub>	C <sub>12</sub>	C <sub>13</sub>	C <sub>14</sub>	C <sub>15</sub>	C <sub>16</sub>	C <sub>17</sub>	C <sub>18</sub>
	IMEM_WRITE_ENABLE	PROGRAM_COUNTER_MUX	PROGRAM_COUNTER_WRITE_EN	REGISTERS_PORT0_SELECT1	REGISTERS_PORT0_SELECT0	REGISTERS_PORT1_SELECT1	REGISTERS_PORT1_SELECT0	REGISTERS_WRITE_SELECT1	REGISTERS_WRITE_SELECT0	REGISTERS_WRITE_ENABLE	ALU_SOURCE_MUX	ALU_SELECT1	ALU_SELECT0	FLAGS_WRITE_ENABLE	ALU_RESUT_MUX	DMEM_INPUT_MUX	DMEM_WRITE_ENABLE	REG_WRITEBACK_MUX
NOOP			1															
INPUTC	1		1												1			
INPUTCF	1		1	X1	X0						1	1						
INPUTD			1											1	1	1		
INPUTDF			1	X1	X0						1	1				1	1	
MOVE			1	Y1	Y0			X1	X0	1	1	1						
LOADI/LOADP			1					X1	X0	1					1			
ADD			1	X1	X0	Y1	Y0	X1	X0	1		1		1				
ADDI			1	X1	X0			X1	X0	1	1	1		1				
SUB			1	X1	X0	Y1	Y0	X1	X0	1		1	1	1				
SUBI			1	X1	X0			X1	X0	1	1	1	1	1				
LOAD			1					X1	X0	1					1			1
LOADF			1	Y1	Y0			X1	X0	1	1	1						1
STORE			1			X1	X0								1		1	
STOREF			1	Y1	Y0	X1	X0				1	1					1	
SHIFTL			1	X1	X0			X1	X0	1				1				
SHIFTR			1	X1	X0			X1	X0	1			1	1				
CMP			1	X1	X0	Y1	Y0					1	1	1				
JUMP		1	1															
BRE/BRZ		B1	1															
BRNE/BRNZ		B2	1															
BRG		B3	1															
BRGE		B4	1															

Taken from these bits of the instruction

I <sub>15</sub>	I <sub>14</sub>	I <sub>13</sub>	I <sub>12</sub>	I <sub>11</sub>	I <sub>10</sub>	I <sub>9</sub>	I <sub>8</sub>	I <sub>7</sub>	I <sub>6</sub>	I <sub>5</sub>	I <sub>4</sub>	I <sub>3</sub>	I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>
						Y <sub>1</sub>	Y <sub>0</sub>								






	C <sub>1</sub>	C <sub>2</sub>	C <sub>3</sub>	C <sub>4</sub>	C <sub>5</sub>	C <sub>6</sub>	C <sub>7</sub>	C <sub>8</sub>	C <sub>9</sub>	C <sub>10</sub>	C <sub>11</sub>	C <sub>12</sub>	C <sub>13</sub>	C <sub>14</sub>	C <sub>15</sub>	C <sub>16</sub>	C <sub>17</sub>	C <sub>18</sub>
	IMEM_WRITE_ENABLE	PROGRAM_COUNTER_MUX	PROGRAM_COUNTER_WRITE_EN	REGISTERS_PORT0_SELECT1	REGISTERS_PORT0_SELECT0	REGISTERS_PORT1_SELECT1	REGISTERS_PORT1_SELECT0	REGISTERS_WRITE_SELECT1	REGISTERS_WRITE_SELECT0	REGISTERS_WRITE_ENABLE	ALU_SOURCE_MUX	ALU_SELECT1	ALU_SELECT0	FLAGS_WRITE_ENABLE	ALU_RESUT_MUX	DMEM_INPUT_MUX	DMEM_WRITE_ENABLE	REG_WRITEBACK_MUX
NOOP			1															
INPUTC	1		1												1			
INPUTCF	1		1	X1	X0						1	1						
INPUTD			1											1	1	1		
INPUTDF			1	X1	X0						1	1				1	1	
MOVE			1	Y1	Y0			X1	X0	1	1	1						
LOADI/LOADP			1					X1	X0	1					1			
ADD			1	X1	X0	Y1	Y0	X1	X0	1		1		1				
ADDI			1	X1	X0			X1	X0	1	1	1		1				
SUB			1	X1	X0	Y1	Y0	X1	X0	1		1	1	1				
SUBI			1	X1	X0			X1	X0	1	1	1	1	1				
LOAD			1					X1	X0	1					1			1
LOADF			1	Y1	Y0			X1	X0	1	1	1						1
STORE			1			X1	X0								1		1	
STOREF			1	Y1	Y0	X1	X0				1	1					1	
SHIFTL			1	X1	X0			X1	X0	1				1				
SHIFTR			1	X1	X0			X1	X0	1			1	1				
CMP			1	X1	X0	Y1	Y0					1	1	1				
JUMP		1	1															
BRE/BRZ		B1	1															
BRNE/BRNZ		B2	1															
BRG		B3	1															
BRGE		B4	1															


computed using  
the flags register


- B1= ZF
- B2= ~ZF
- B3= AND (~ZF, XNOR(NF, OF))
- B4= XNOR(NF, OF)


- Zero Flag (ZF)
- Negative Flag (NF)
- Overflow Flag (OF)


# **The Control Signals**

 


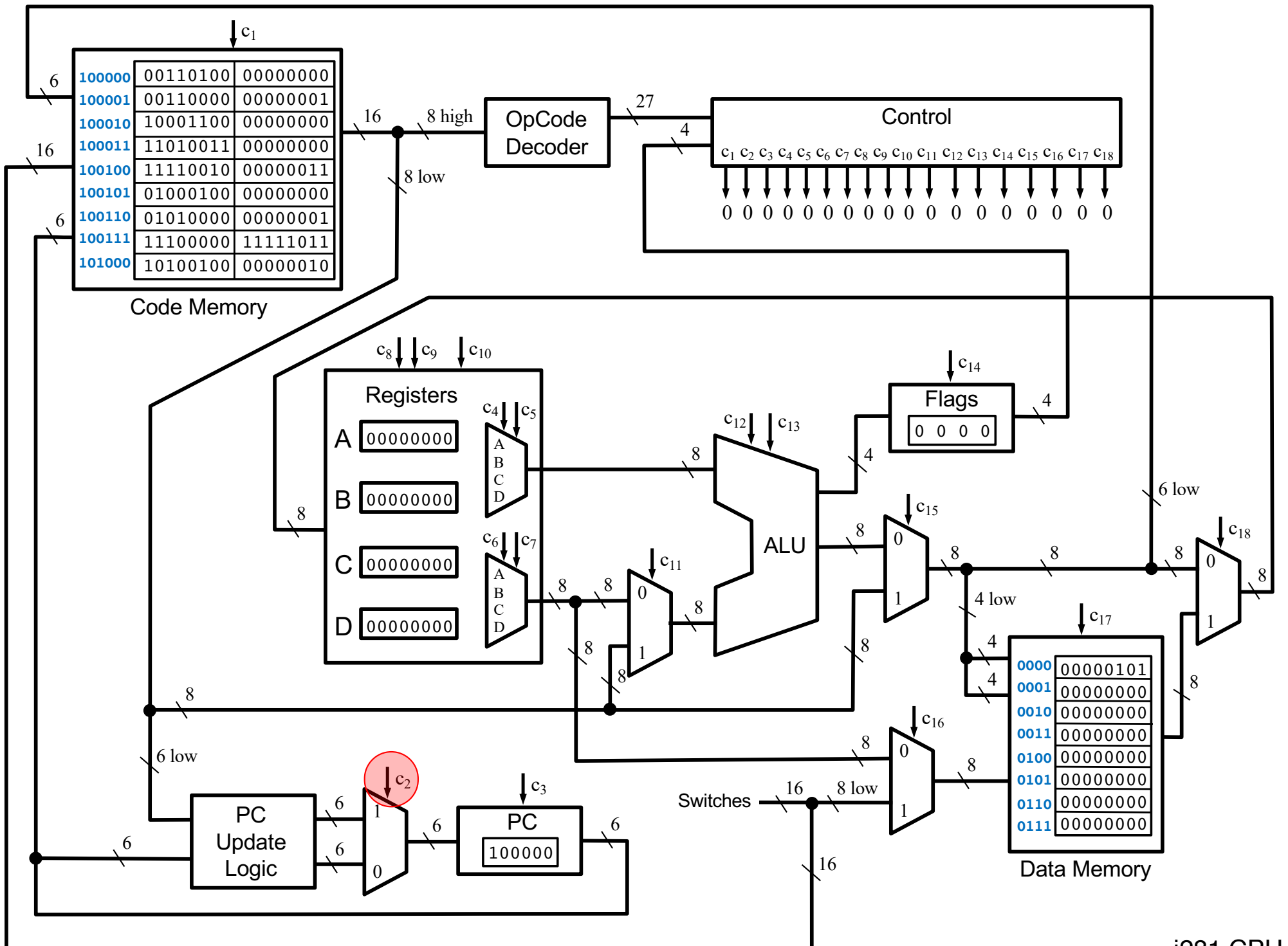

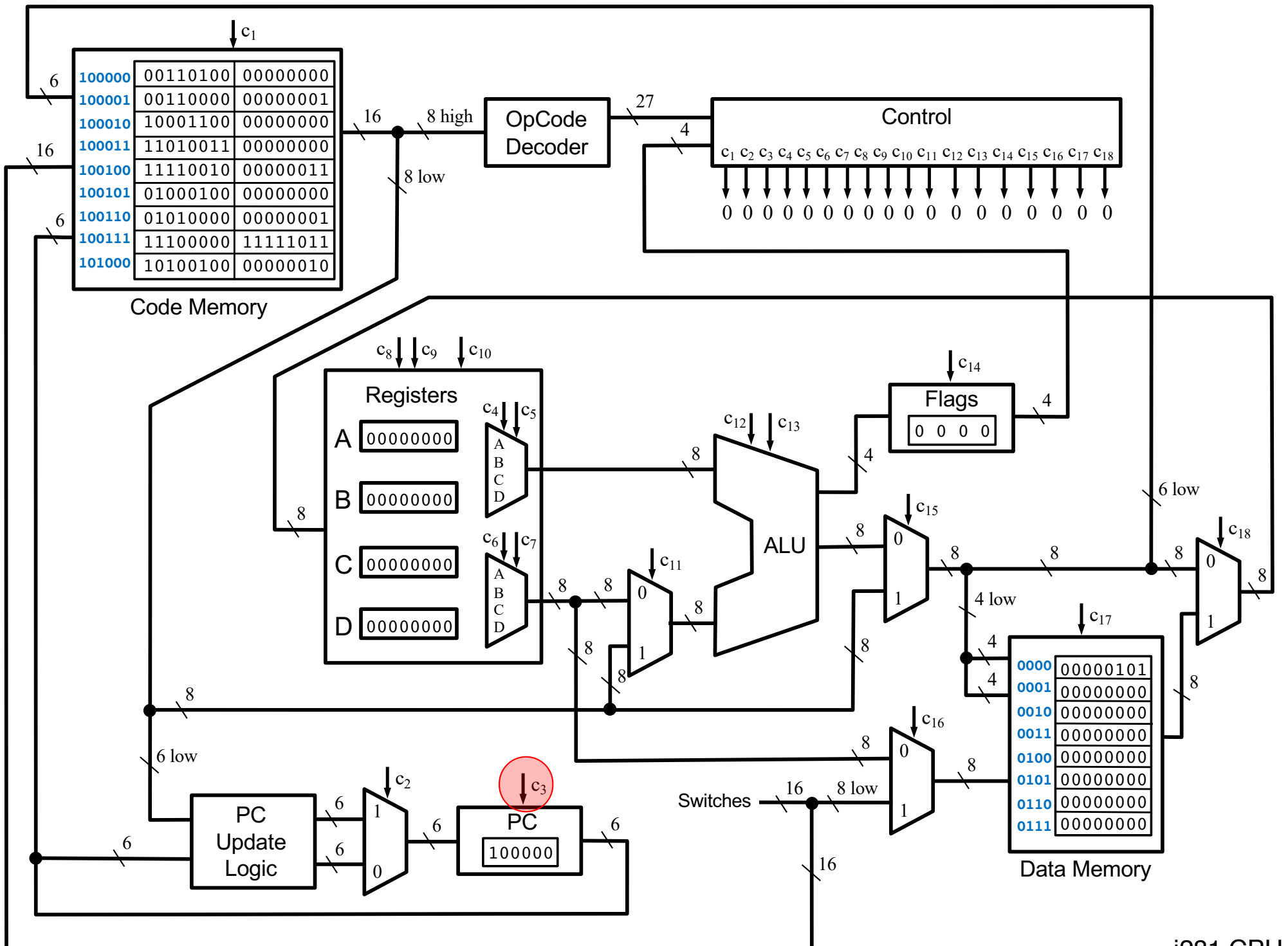


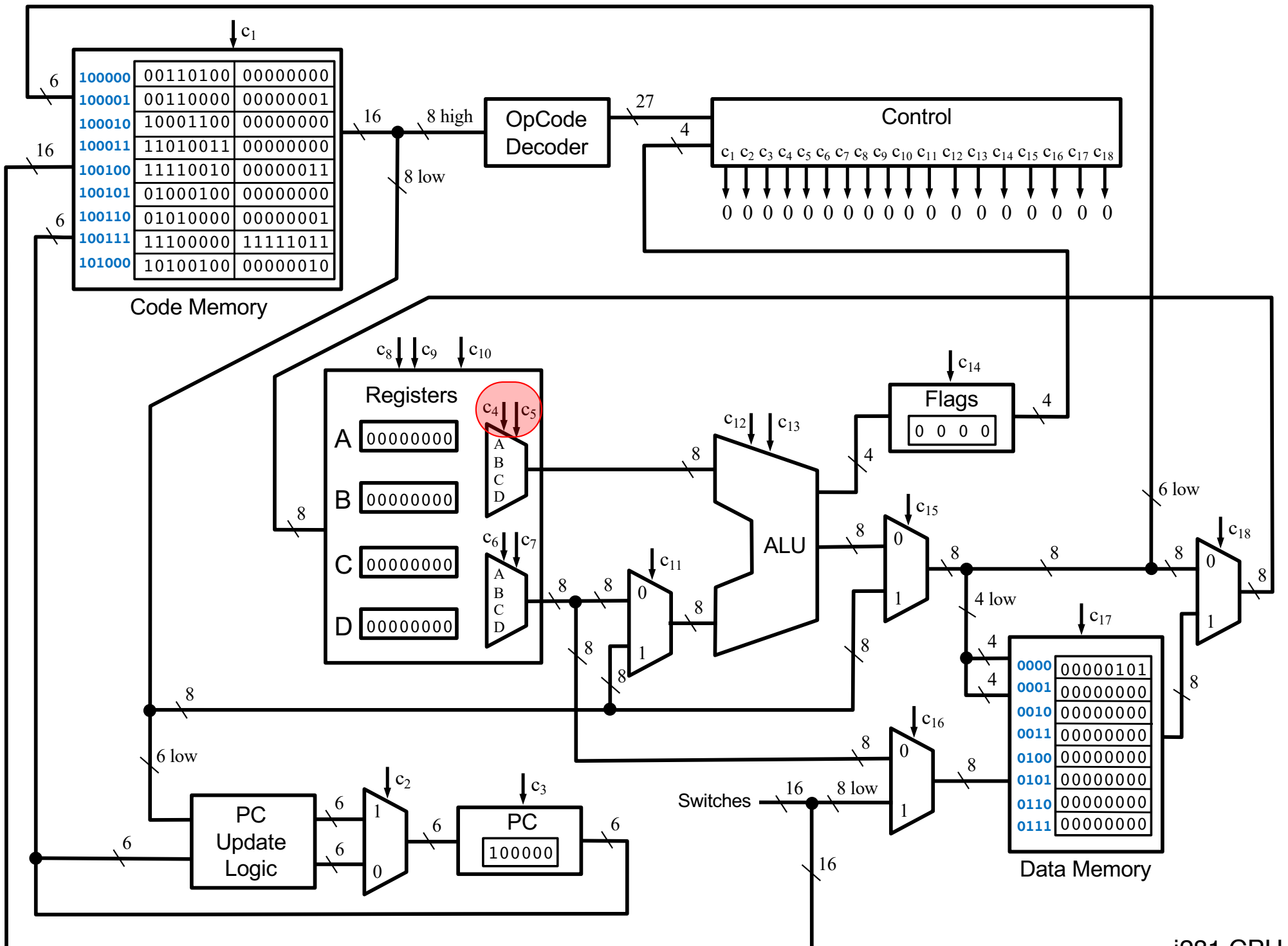


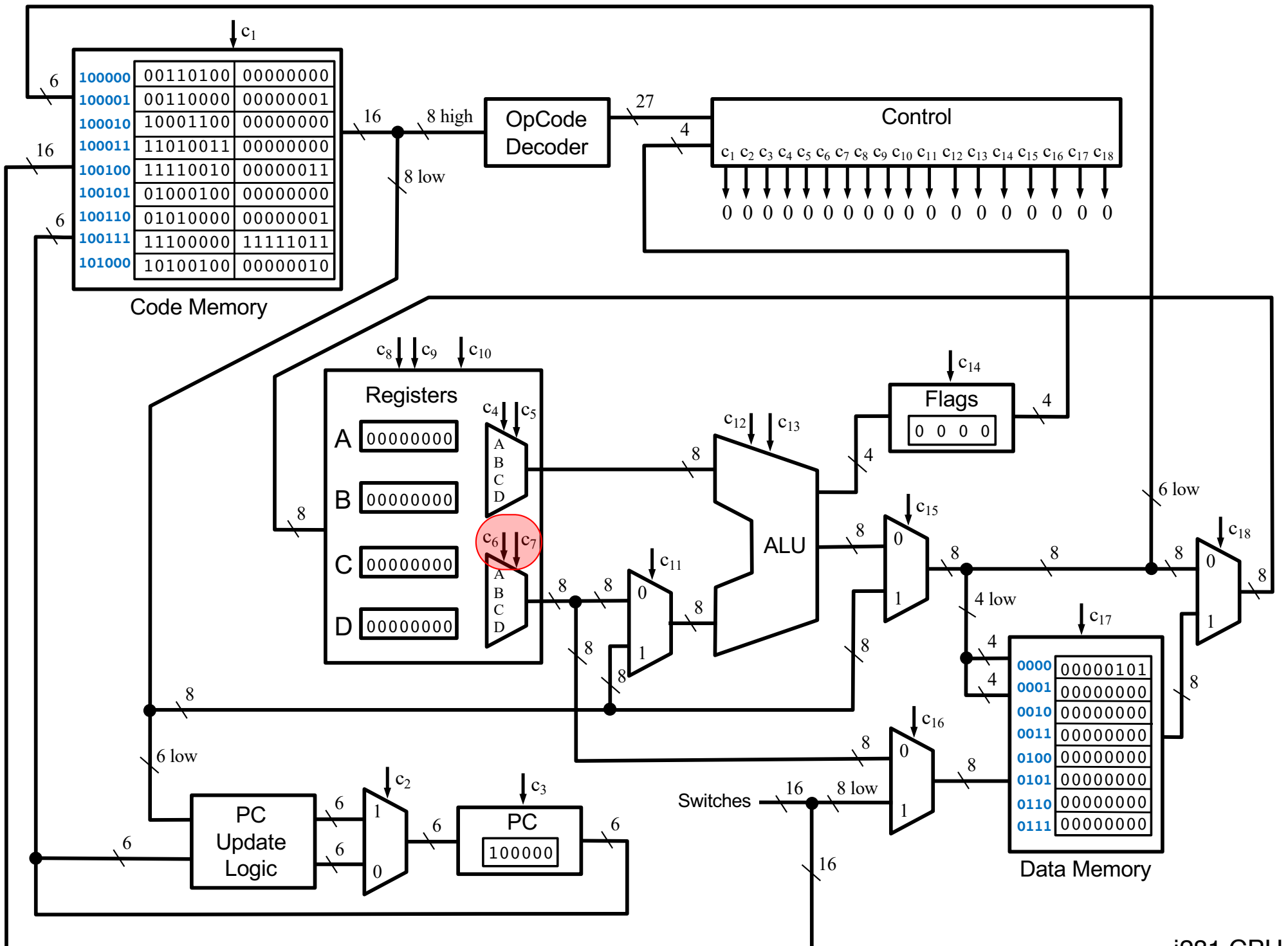


 





 


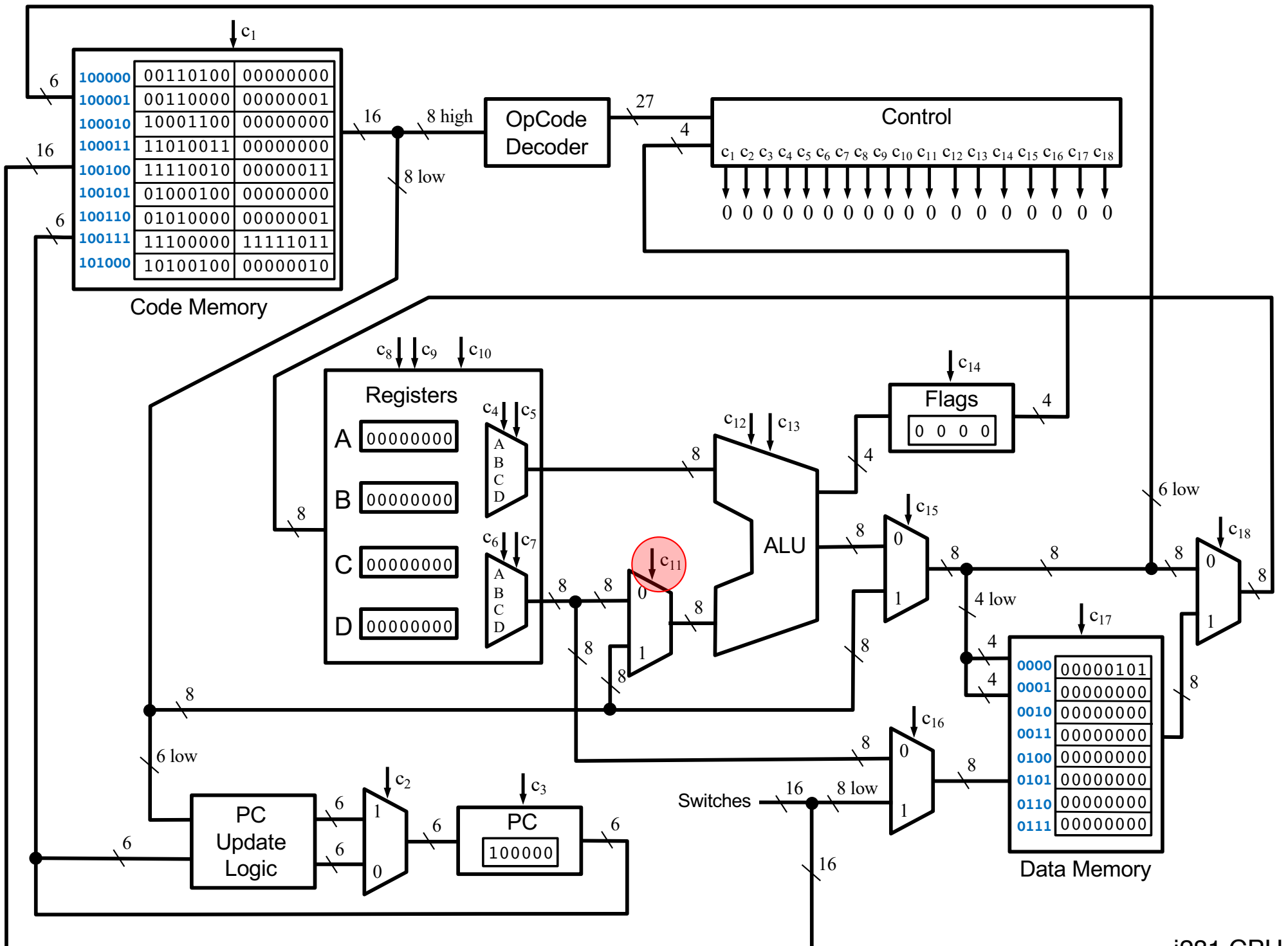


 


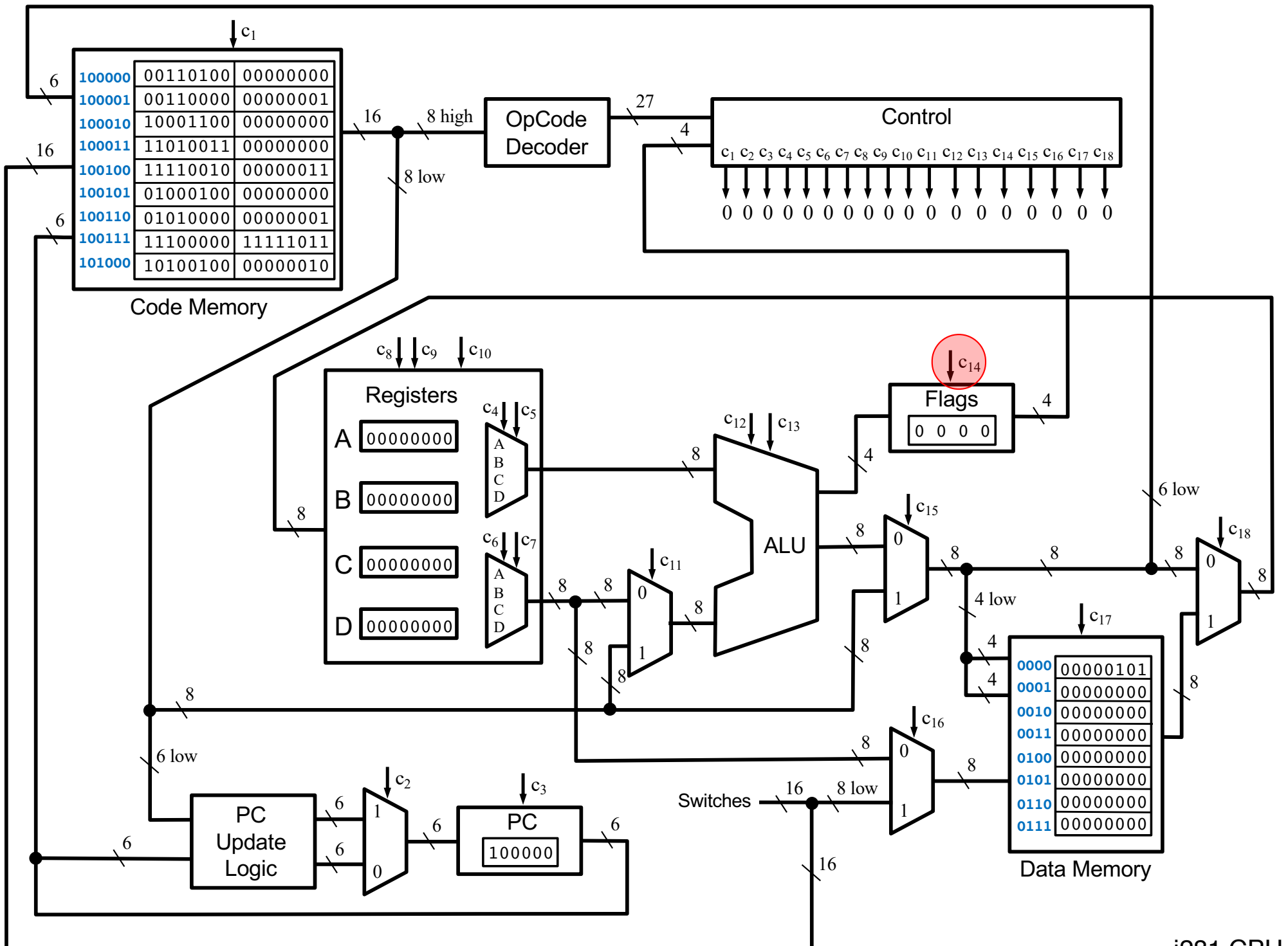

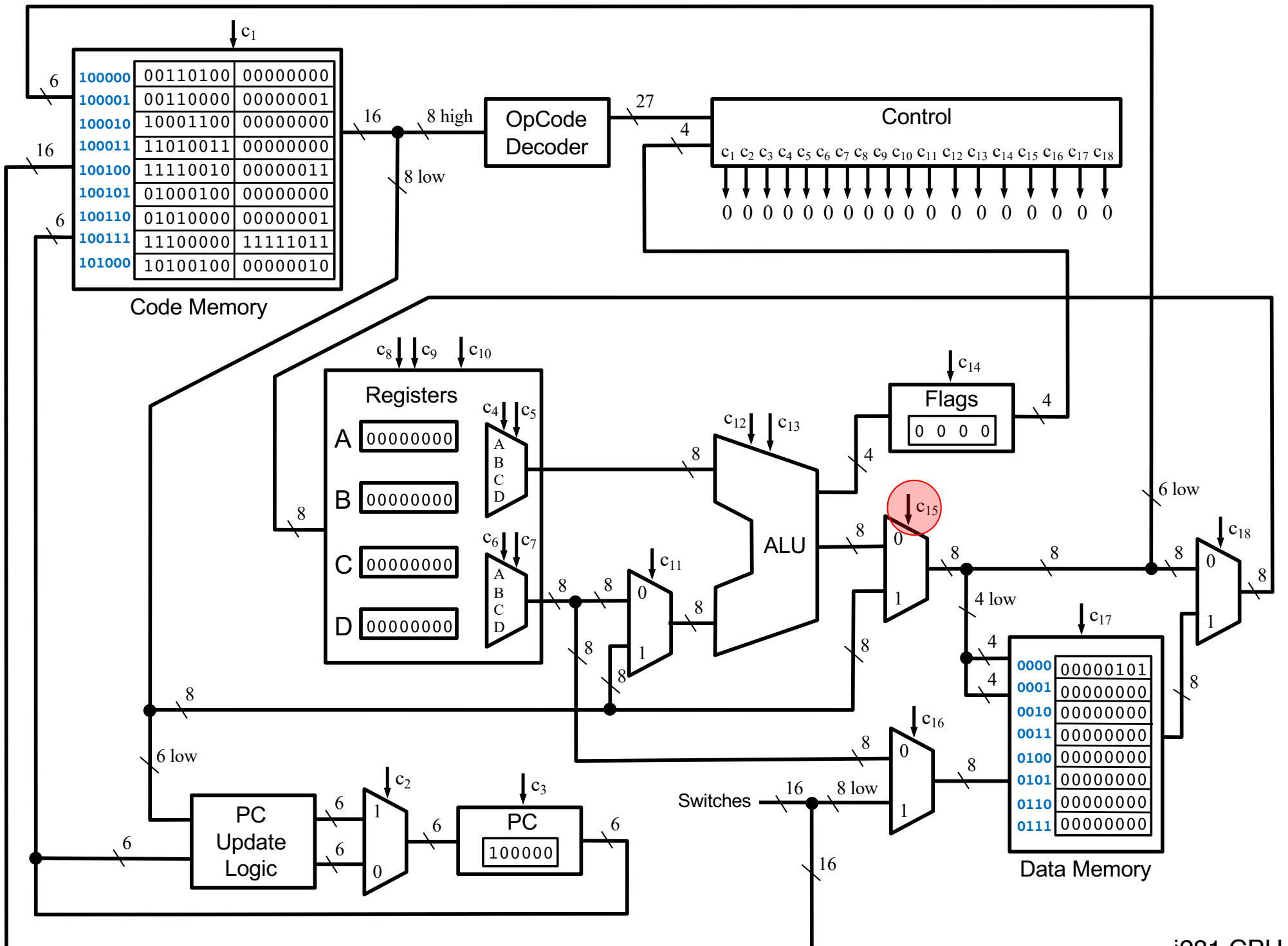


 


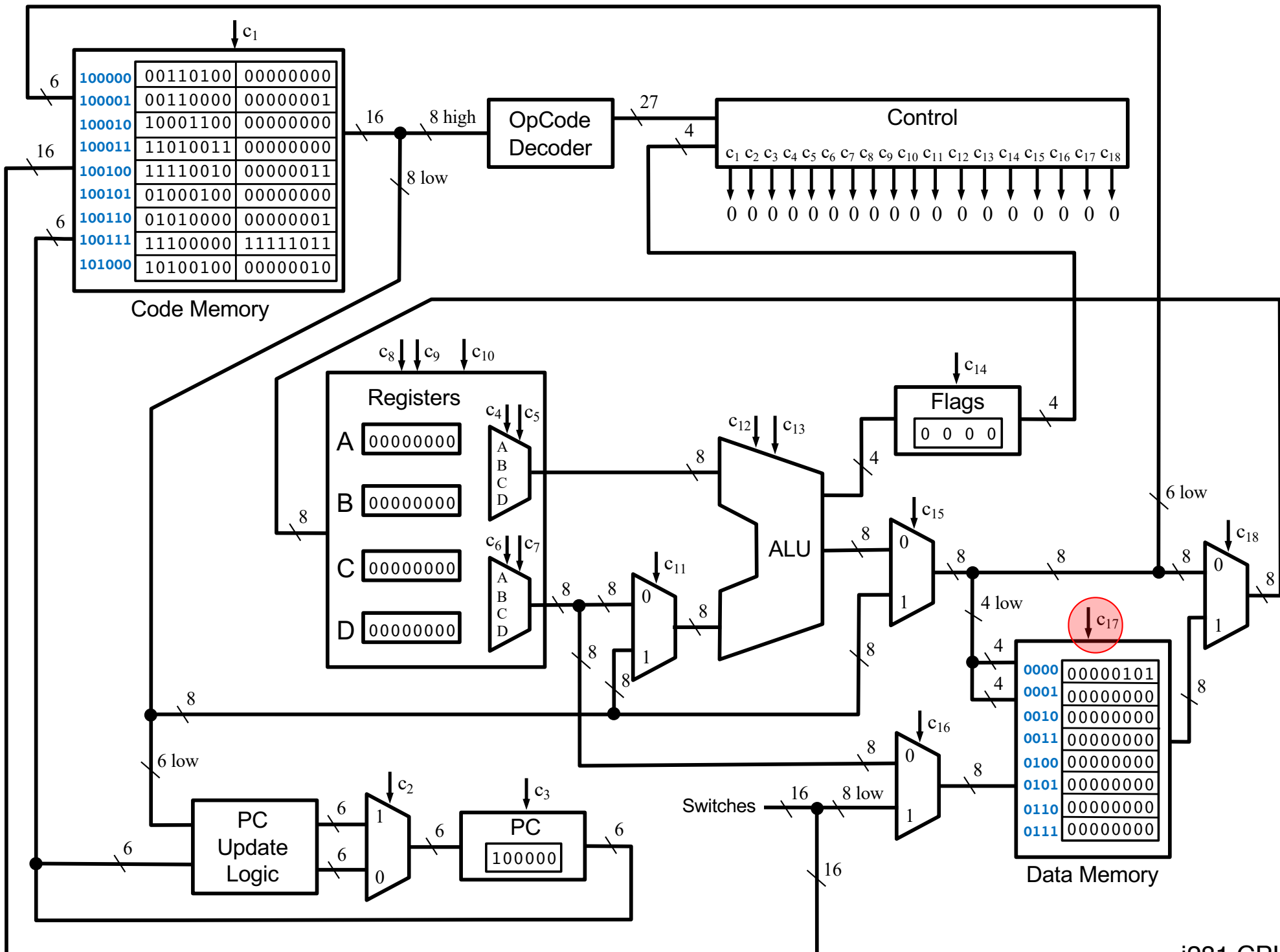

 





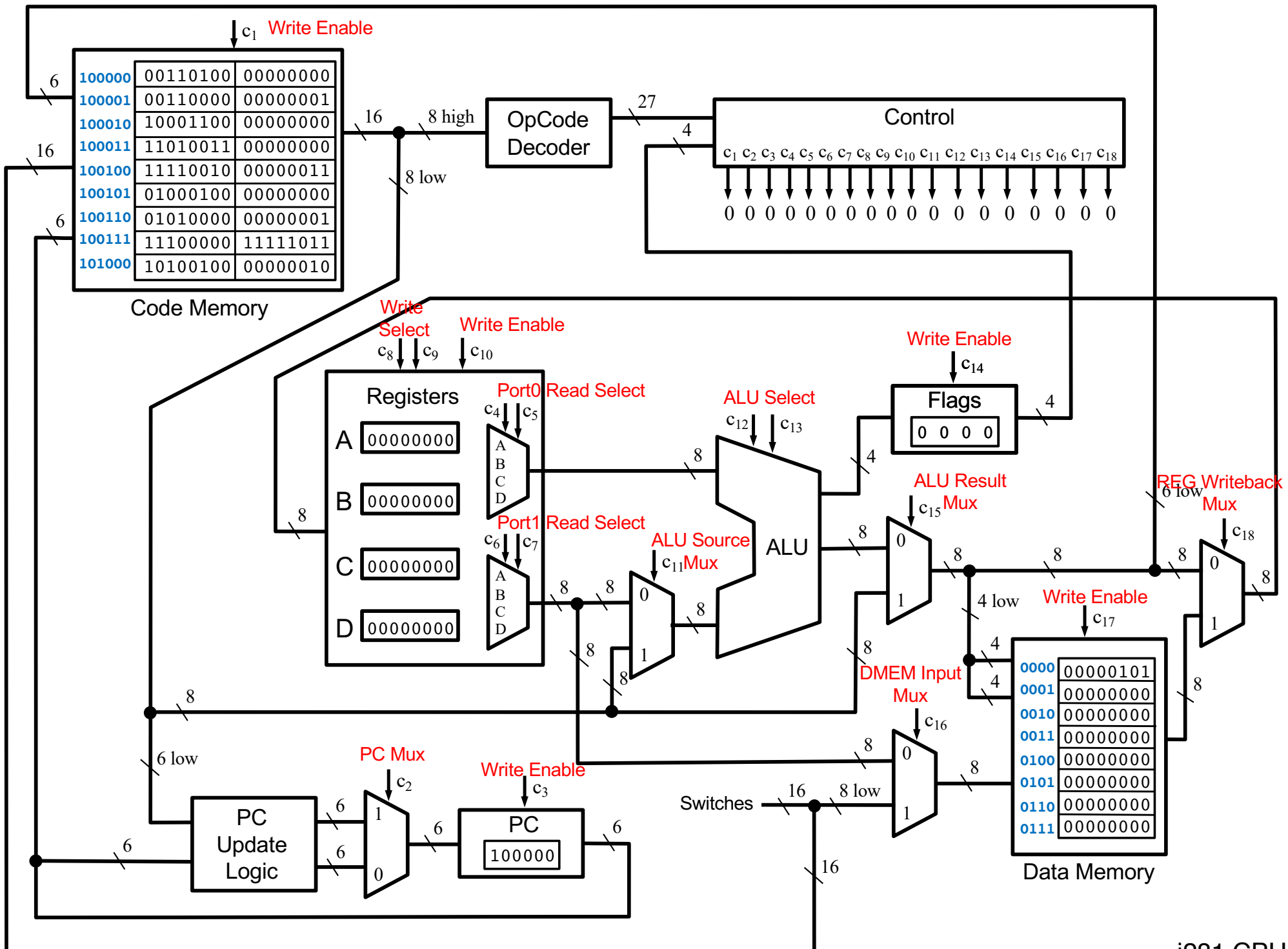

 



# **The Five Bus Multiplexers**

 


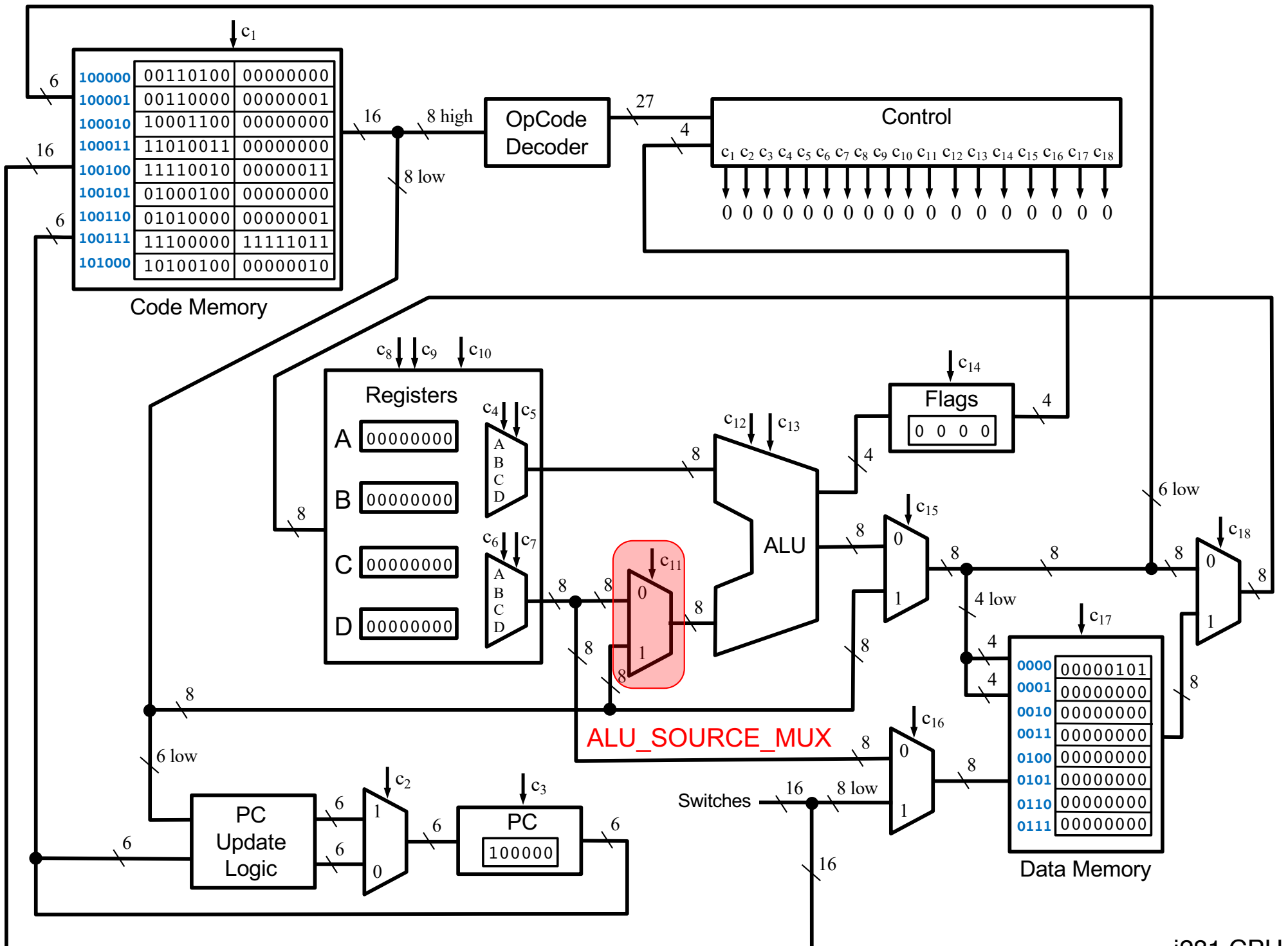

 
# 2-to-1 Bus Multiplexer (with 8-bit lines)




 


 





 


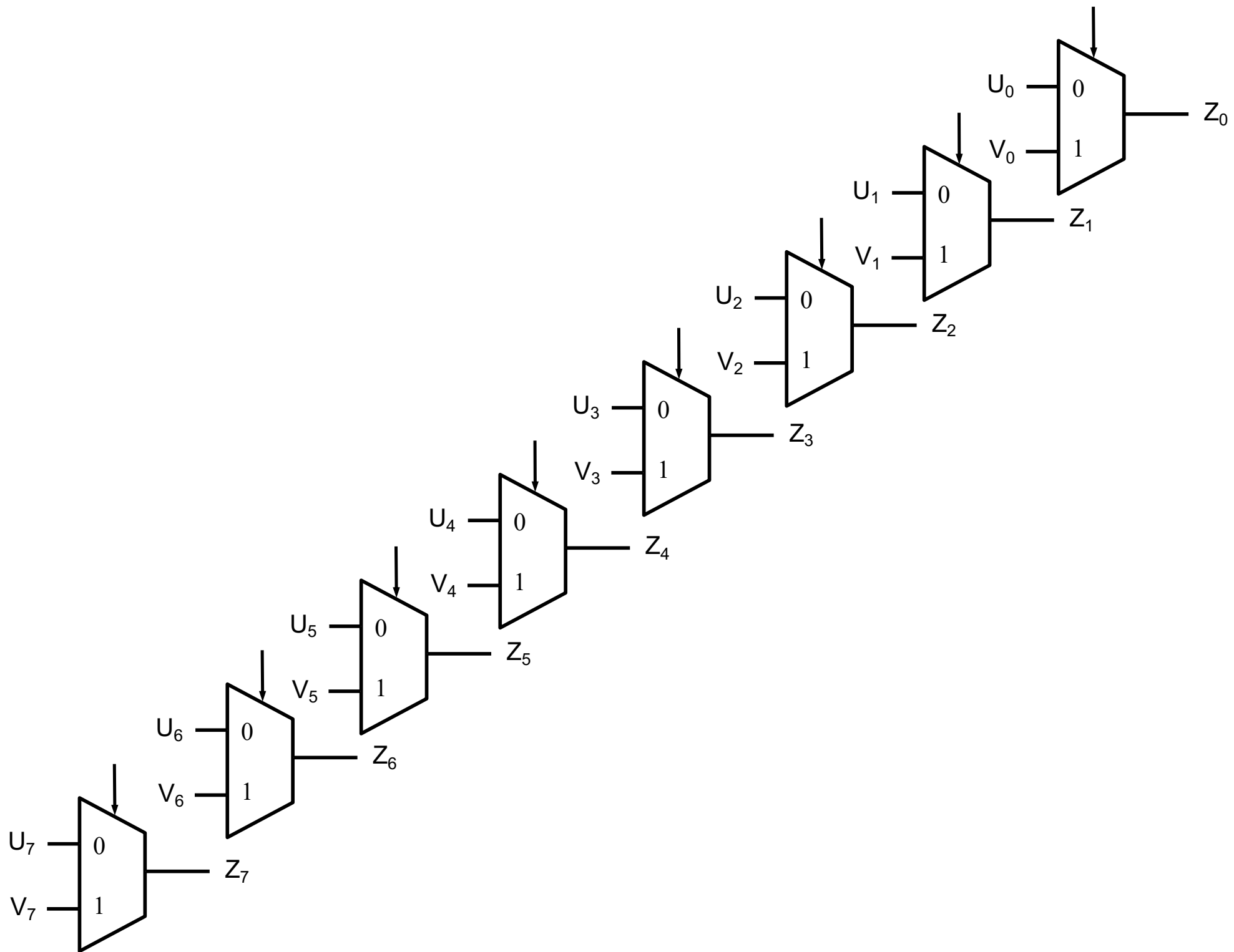


 


 

 


 


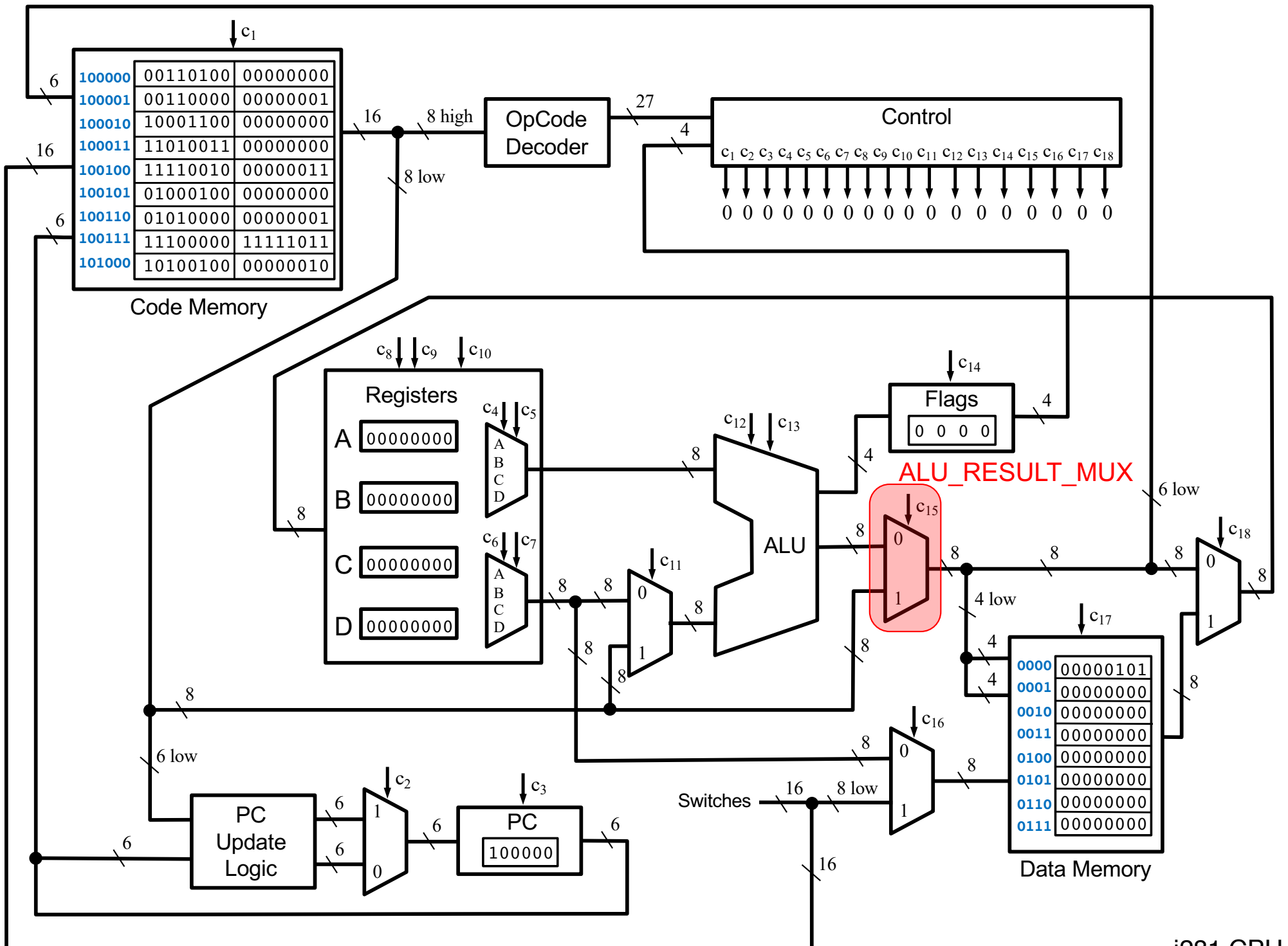


 





 


 

 


 

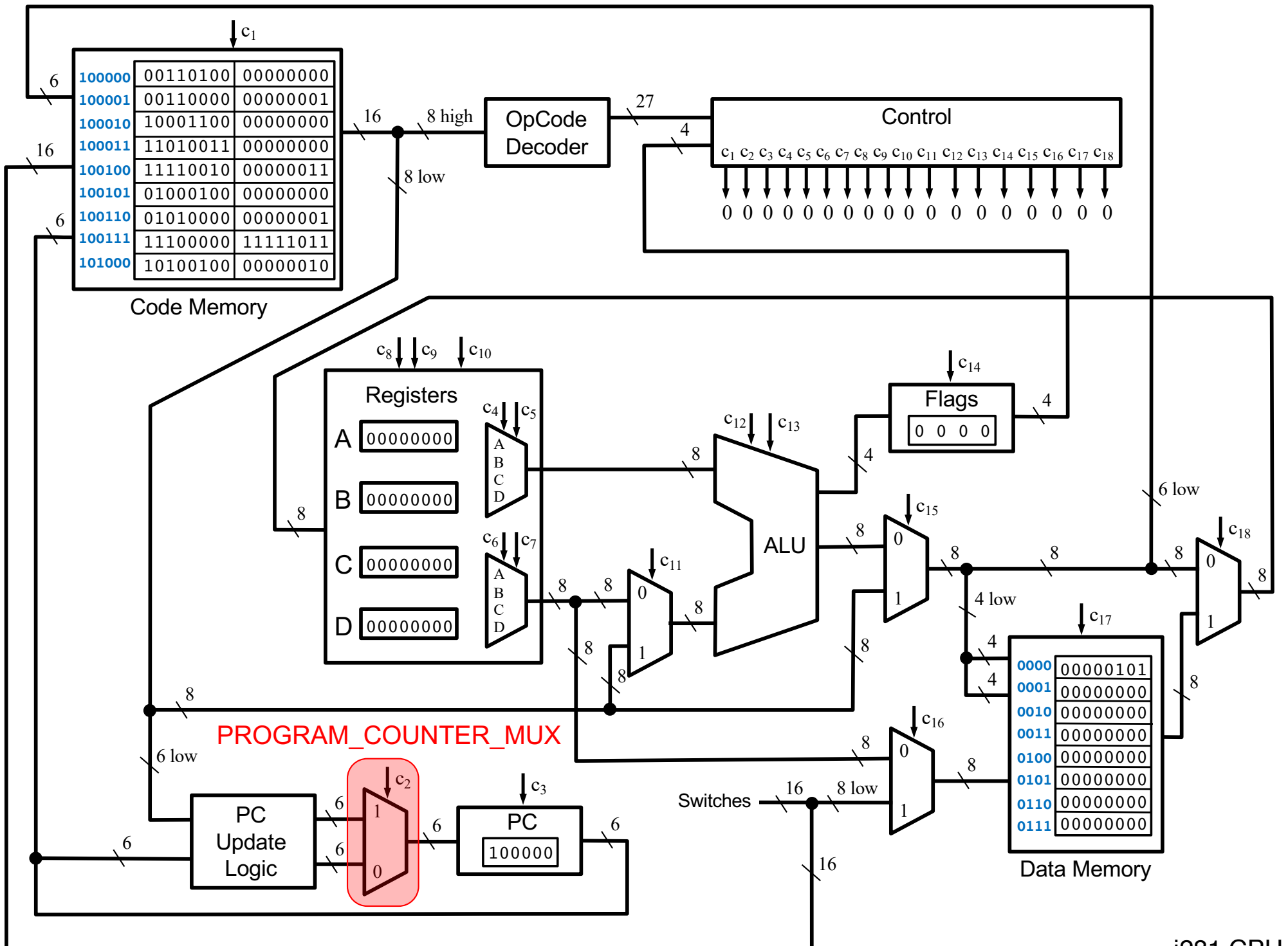


 
 
# 2-to-1 Bus Multiplexer (with **6-bit** lines)




 
# 2-to-1 Bus Multiplexer (with **6-bit** lines)




 Note that the 0 and the 1 are swapped  
(in order to simplify the large diagram).







 


 


# **The Four Registers**

 


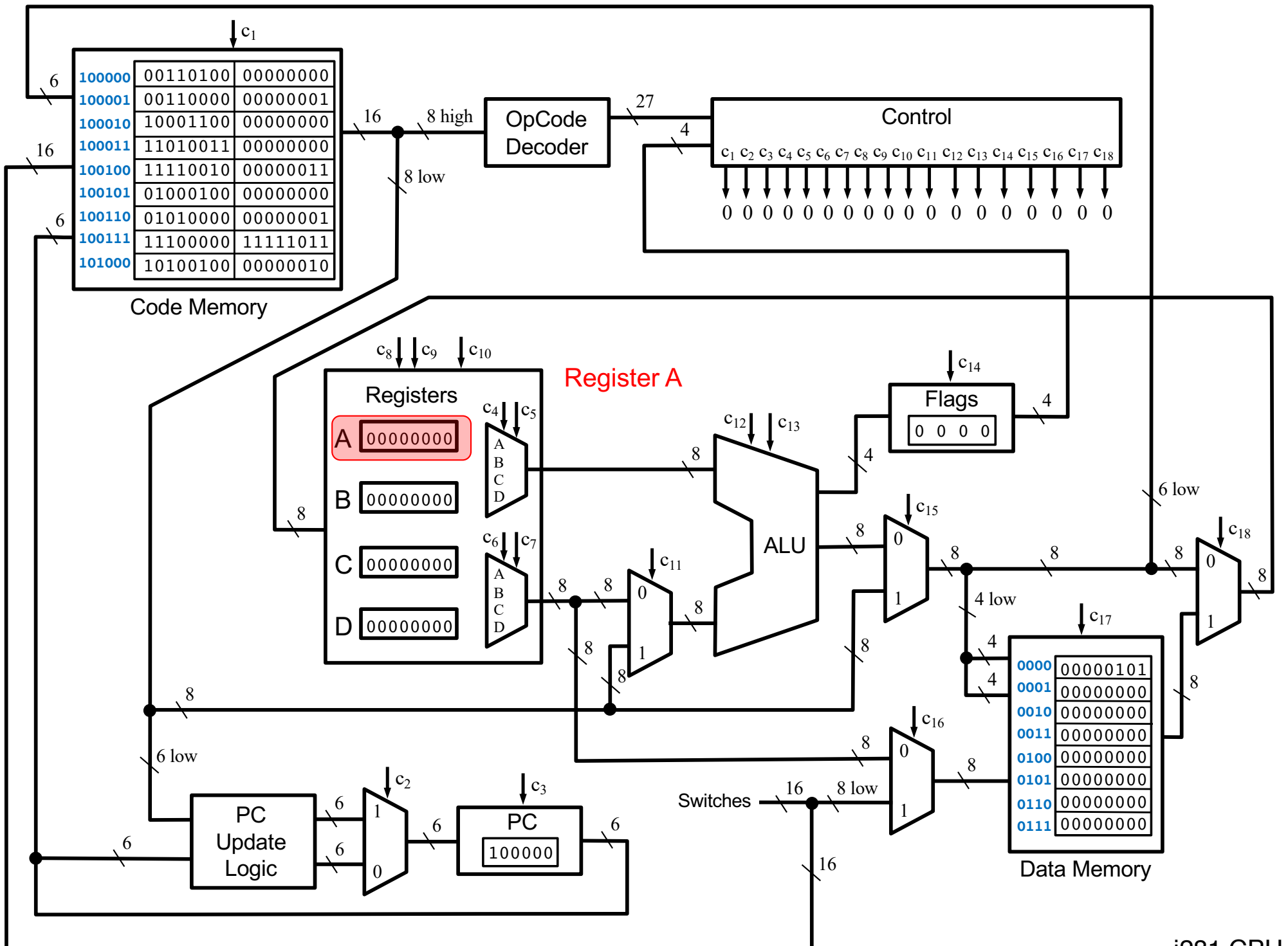

 


 



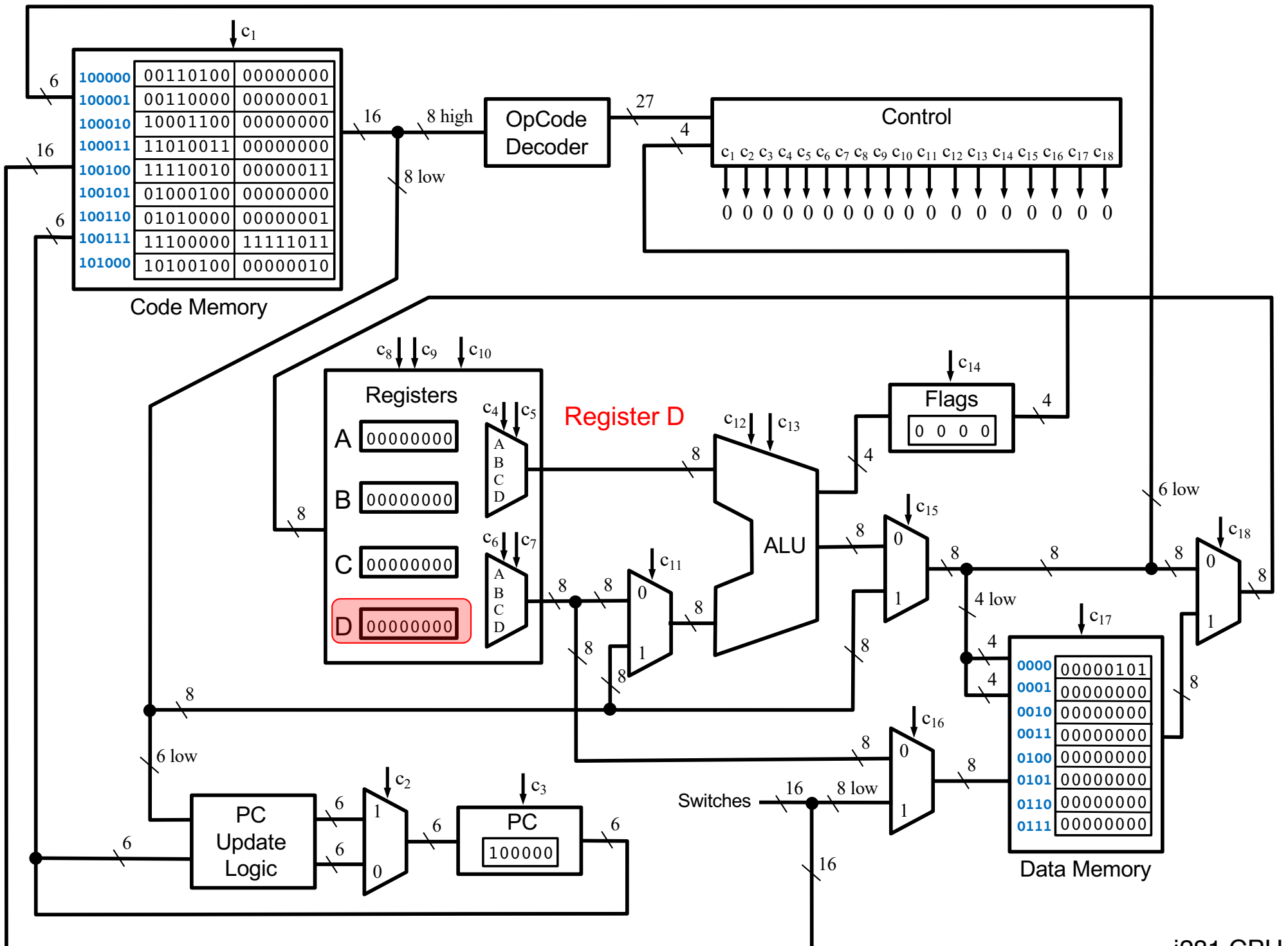


# Register A

 


8-Bit Parallel-Access Register

# Register A

 


# Register A

 


8-Bit Parallel-Access Register

# Register B

 


8-Bit Parallel-Access Register

# Register C

 


8-Bit Parallel-Access Register

# Register D

 



8-Bit Parallel-Access Register

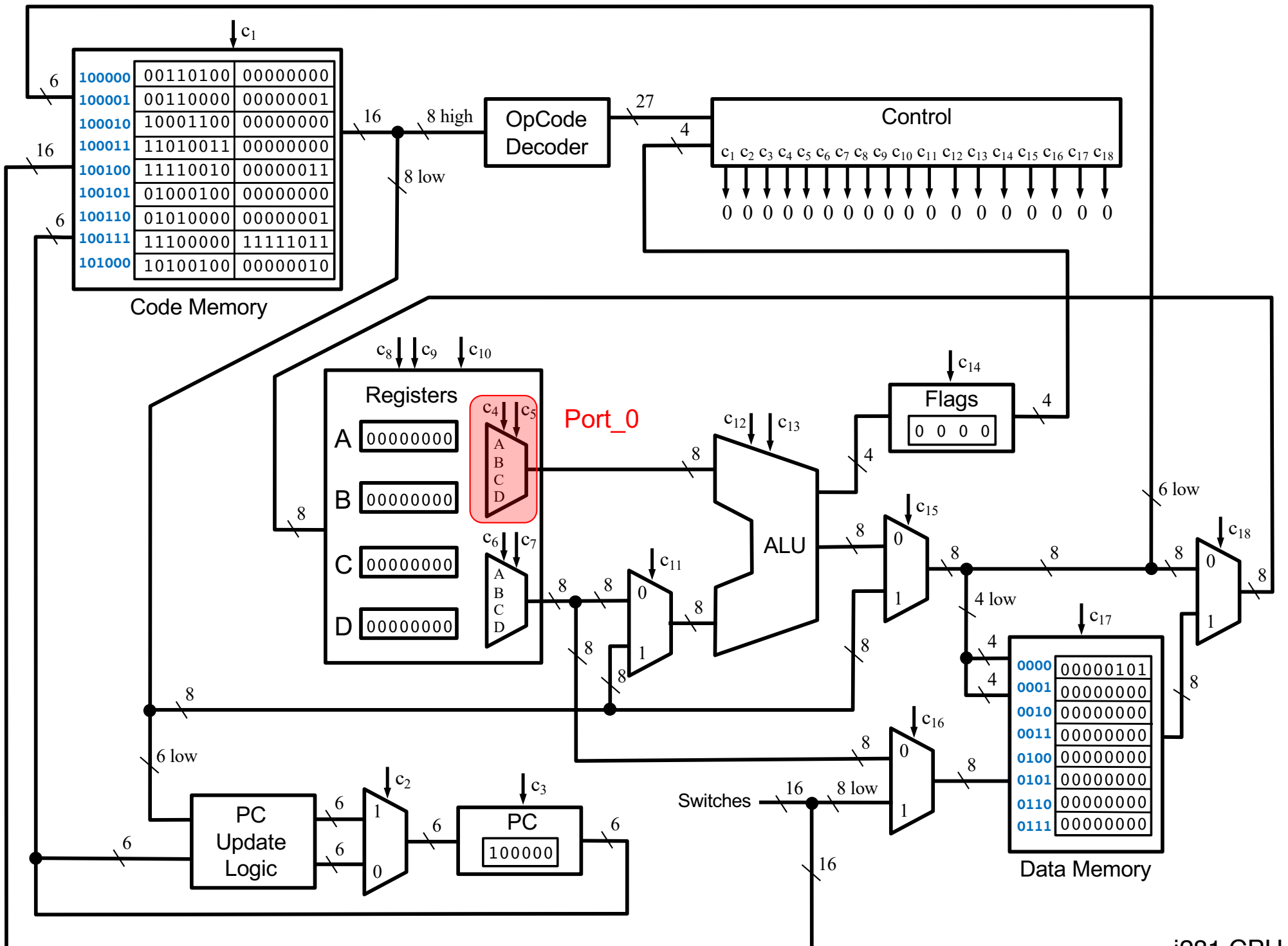





 
# 4-to-1 Bus Multiplexer (with 8-bit lines)




 


 


 

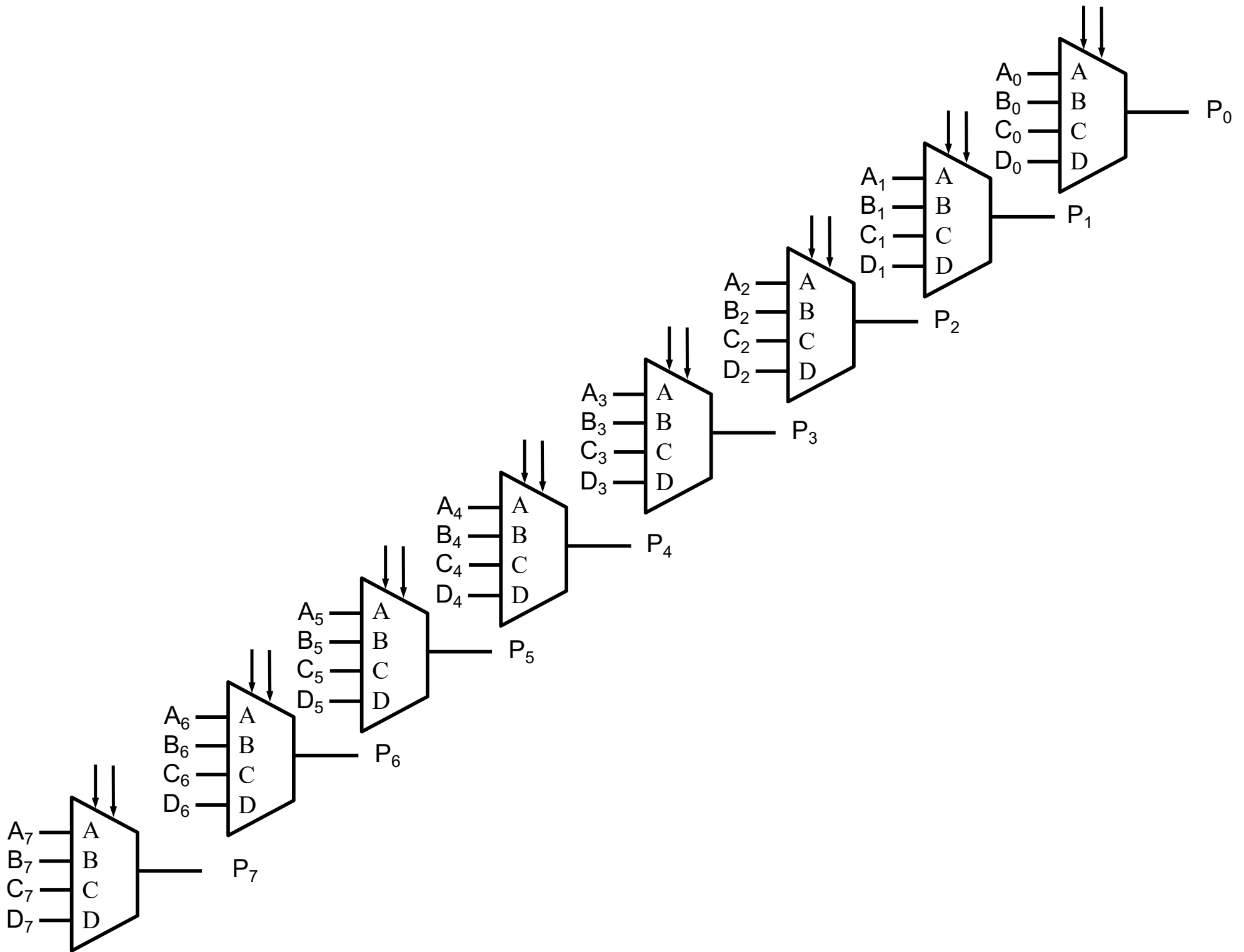


 


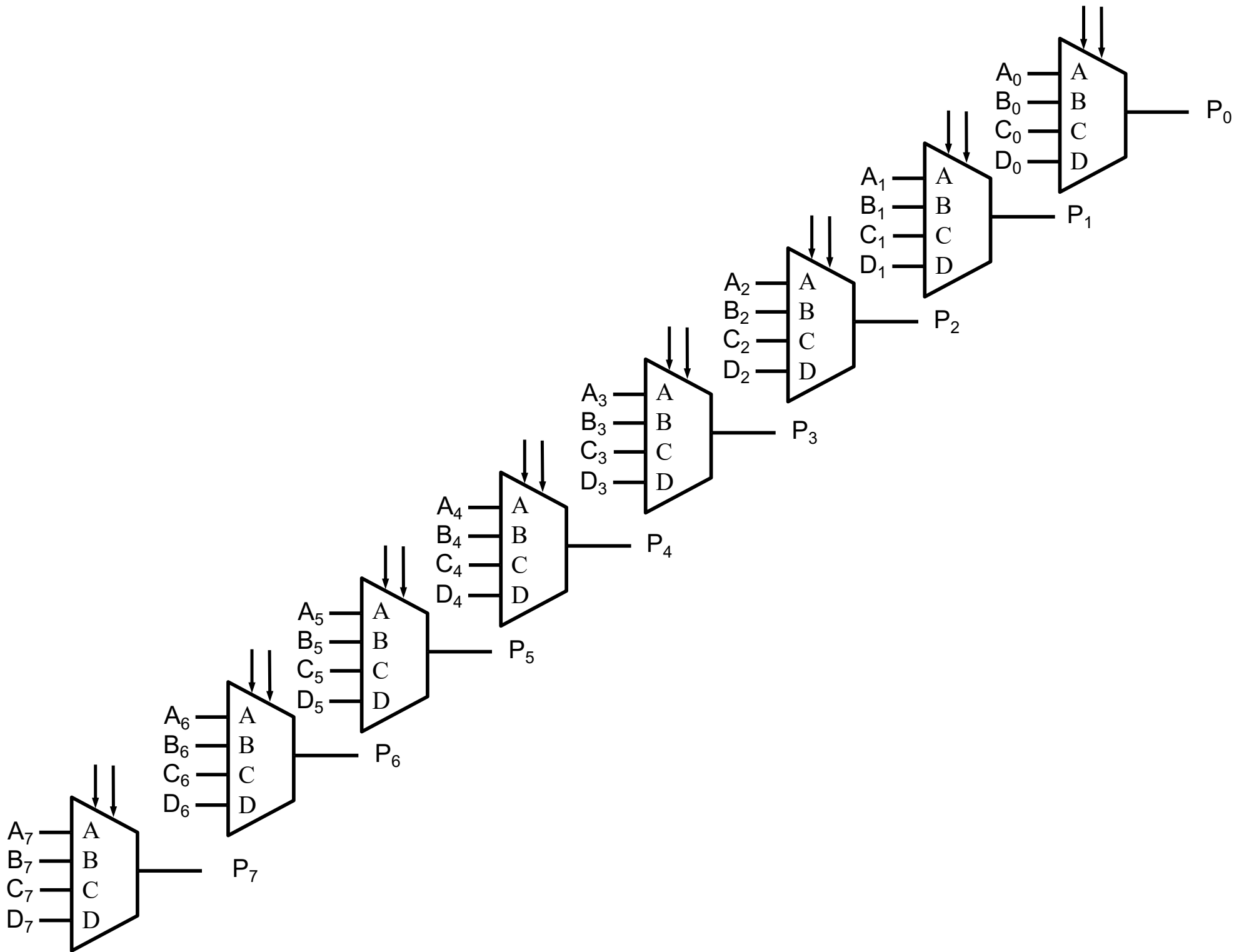


 





 


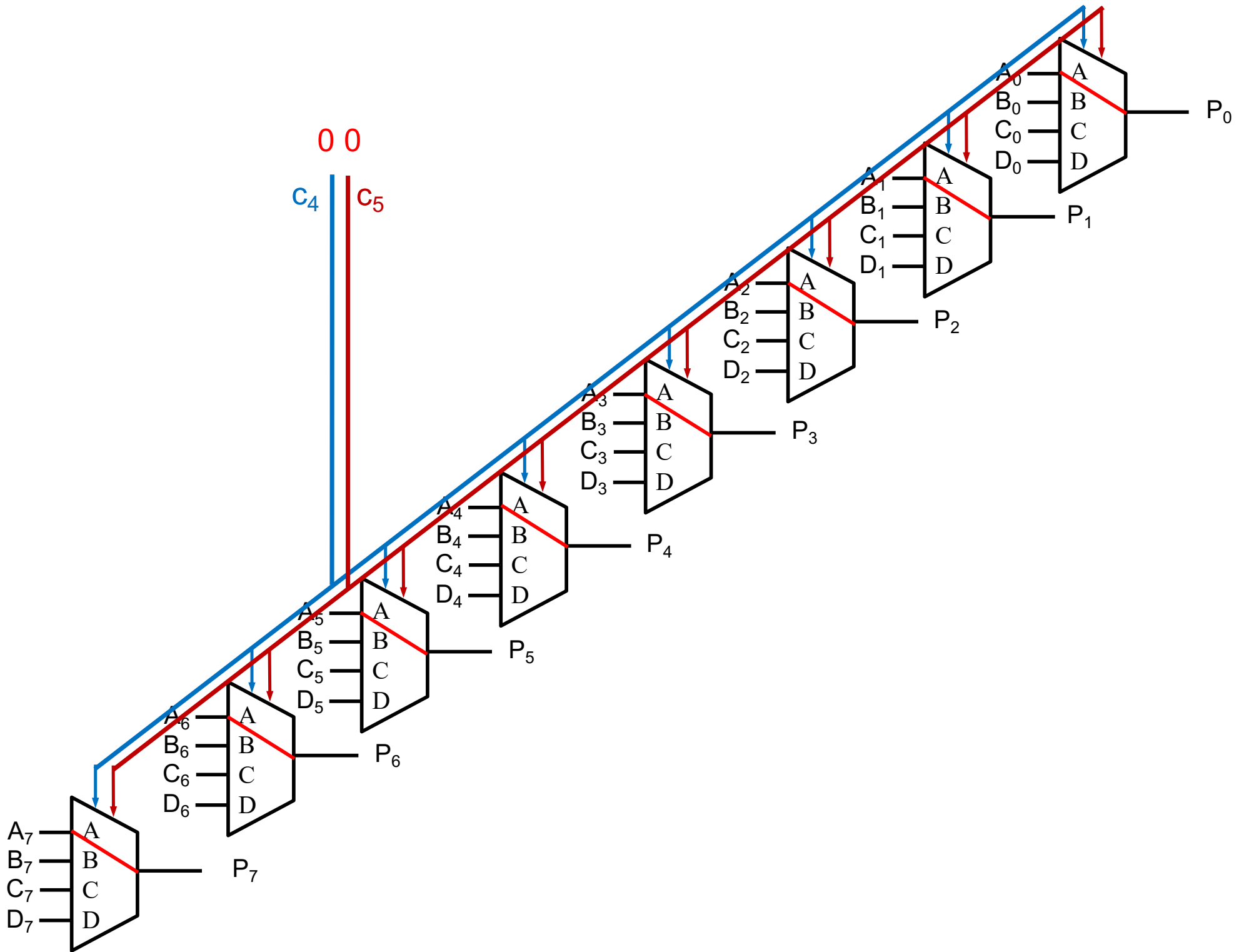

 


 


 

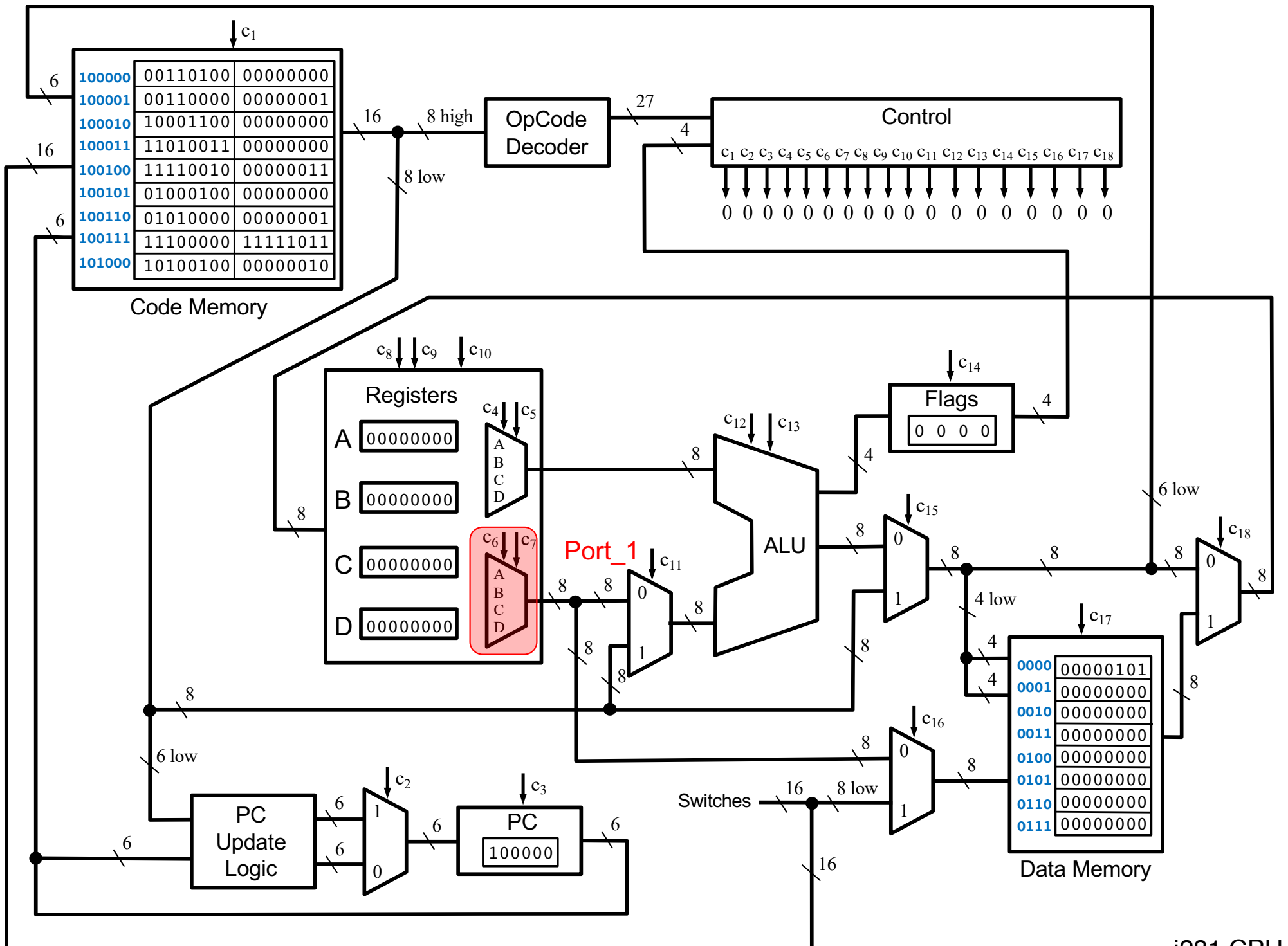


 
# 4-to-1 Bus Multiplexer (with 8-bit lines)




 





 


 


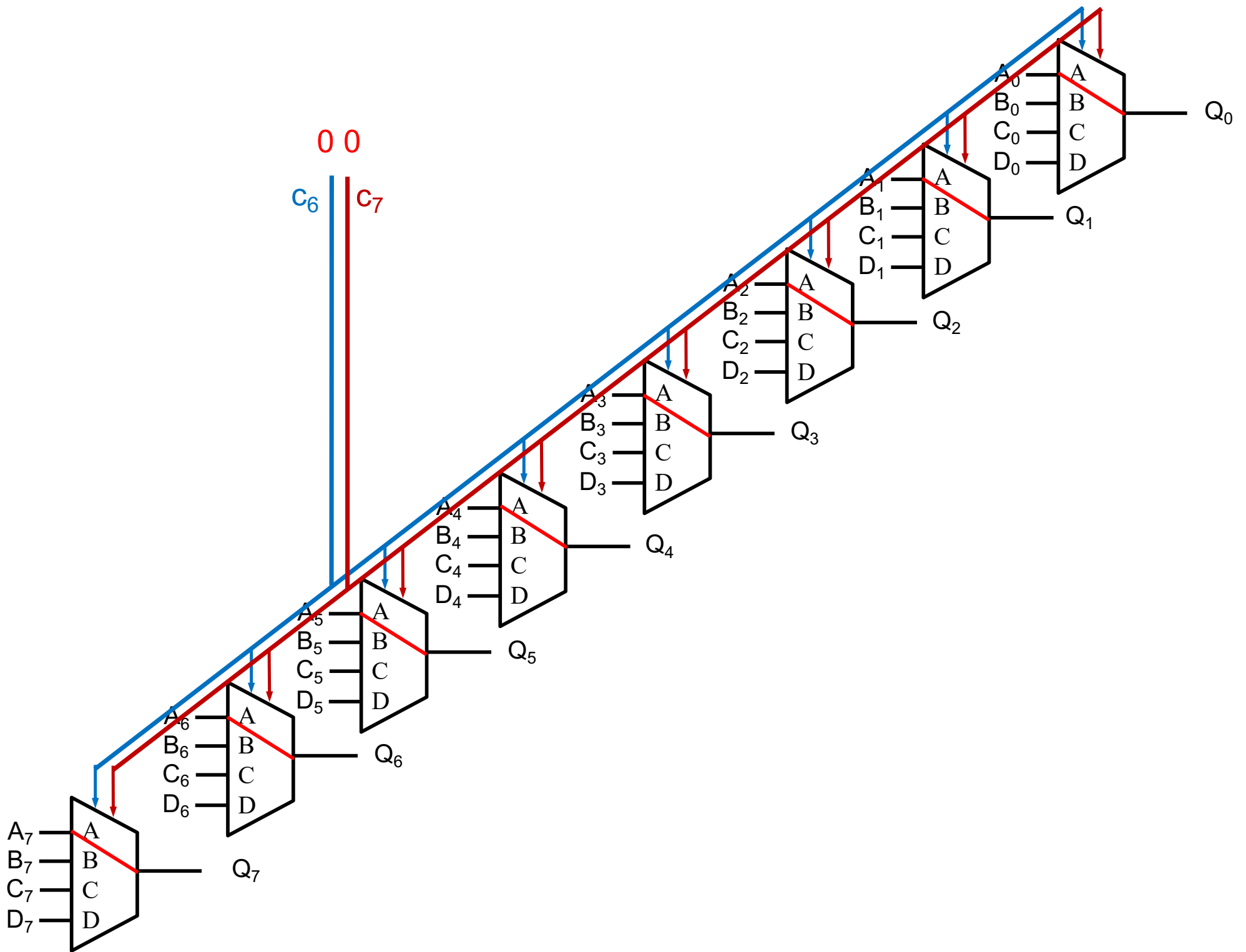

 

 


 

 


# **The Data Memory**




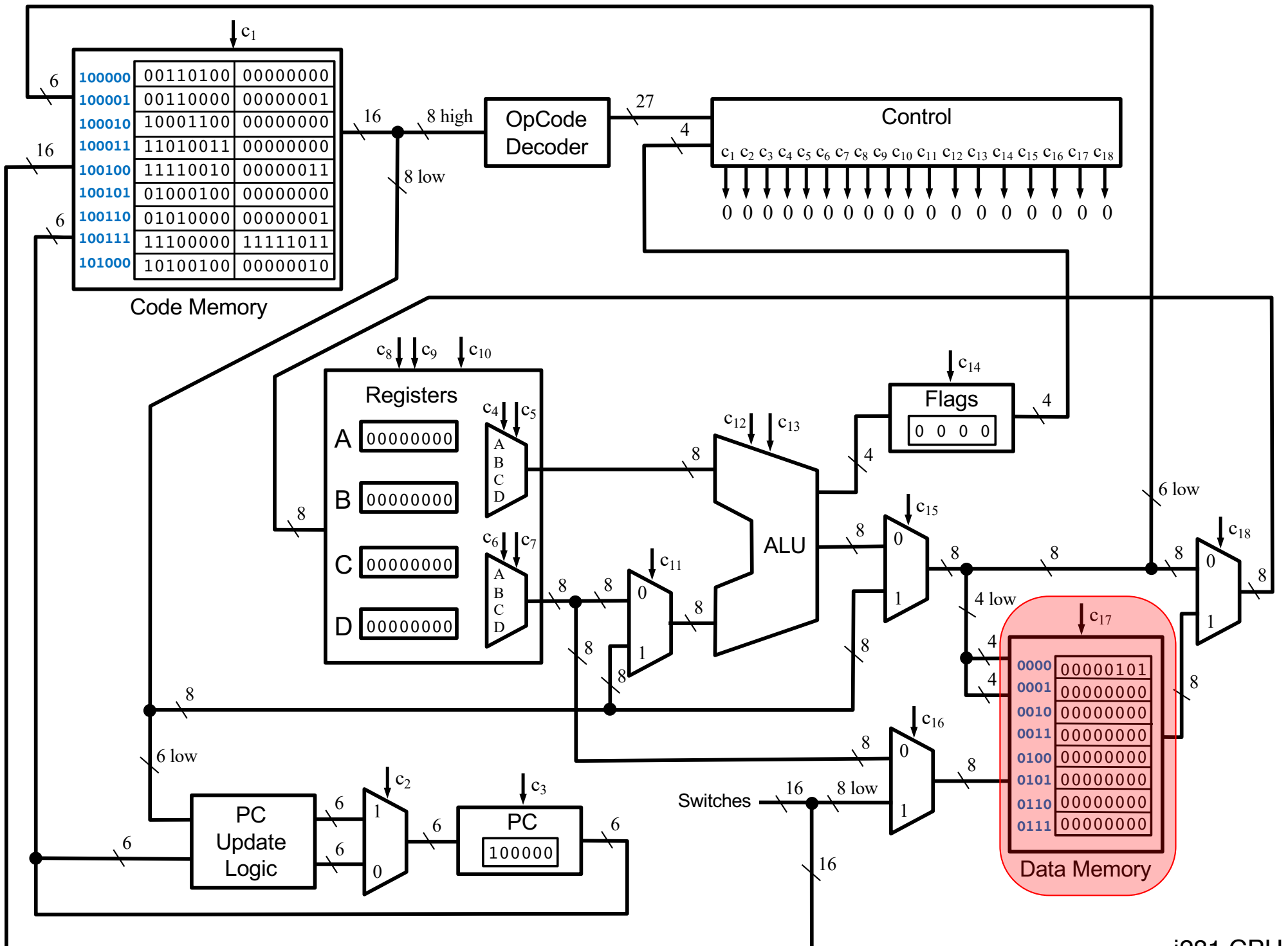


i281 CPU

 


# 8-Bit Parallel-Access Register

 


# **The Code Memory**

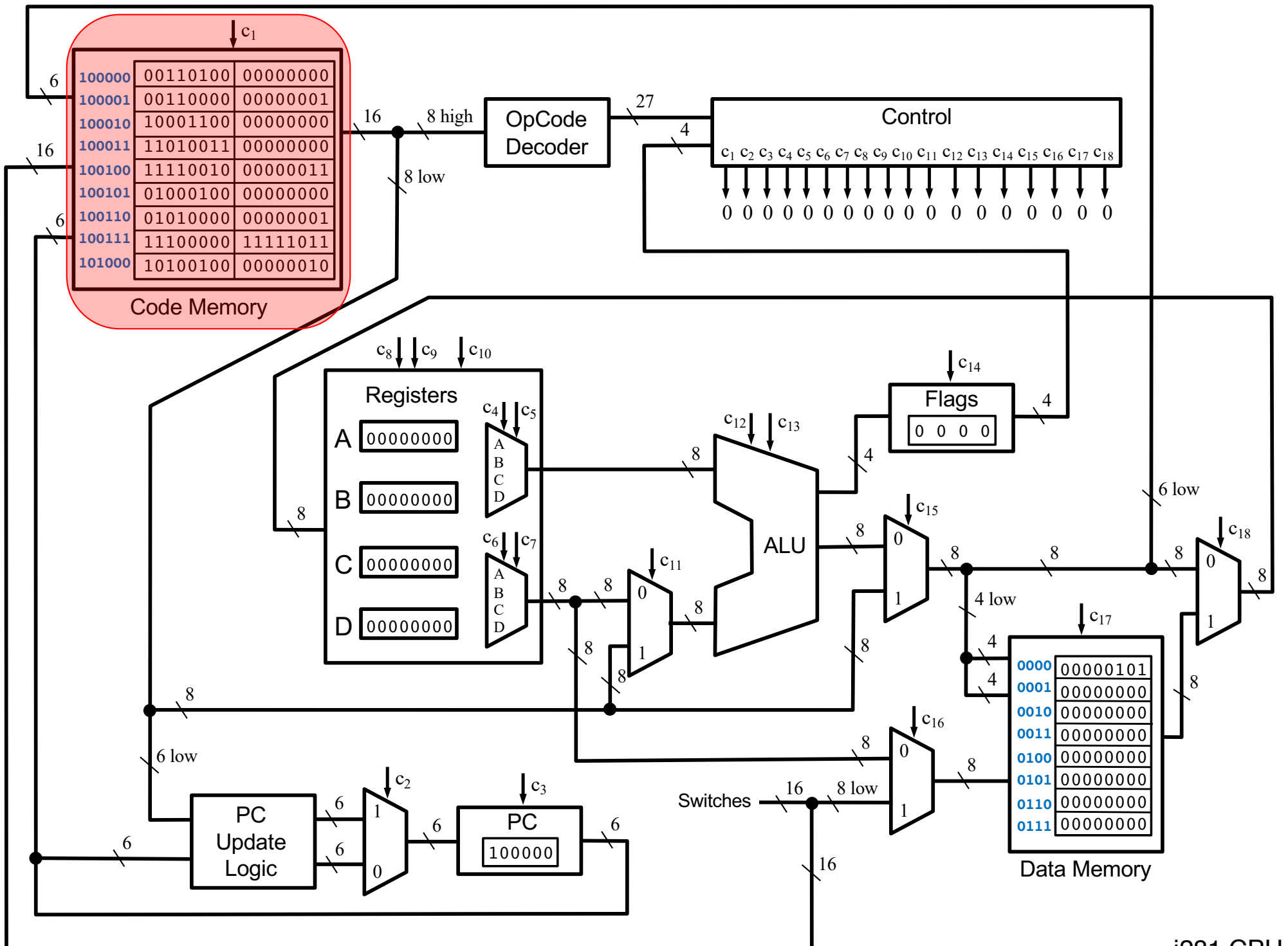

 



# 16-Bit Parallel-Access Register

 


# **The Input Switches**




 

 


 

 
These 16 switches are used for input into the Code Memory.




0 0 0 0 0 0 0 0 0 0 1 0 0 0 0 0

 

 These 8 switches are used for input into the Data Memory.



0 1 0 0 0 0 0 0

 



0 1 0 0 0 0 0 0


This switch controls the paddle in PONG


**To Be Covered  
Next Time**



 

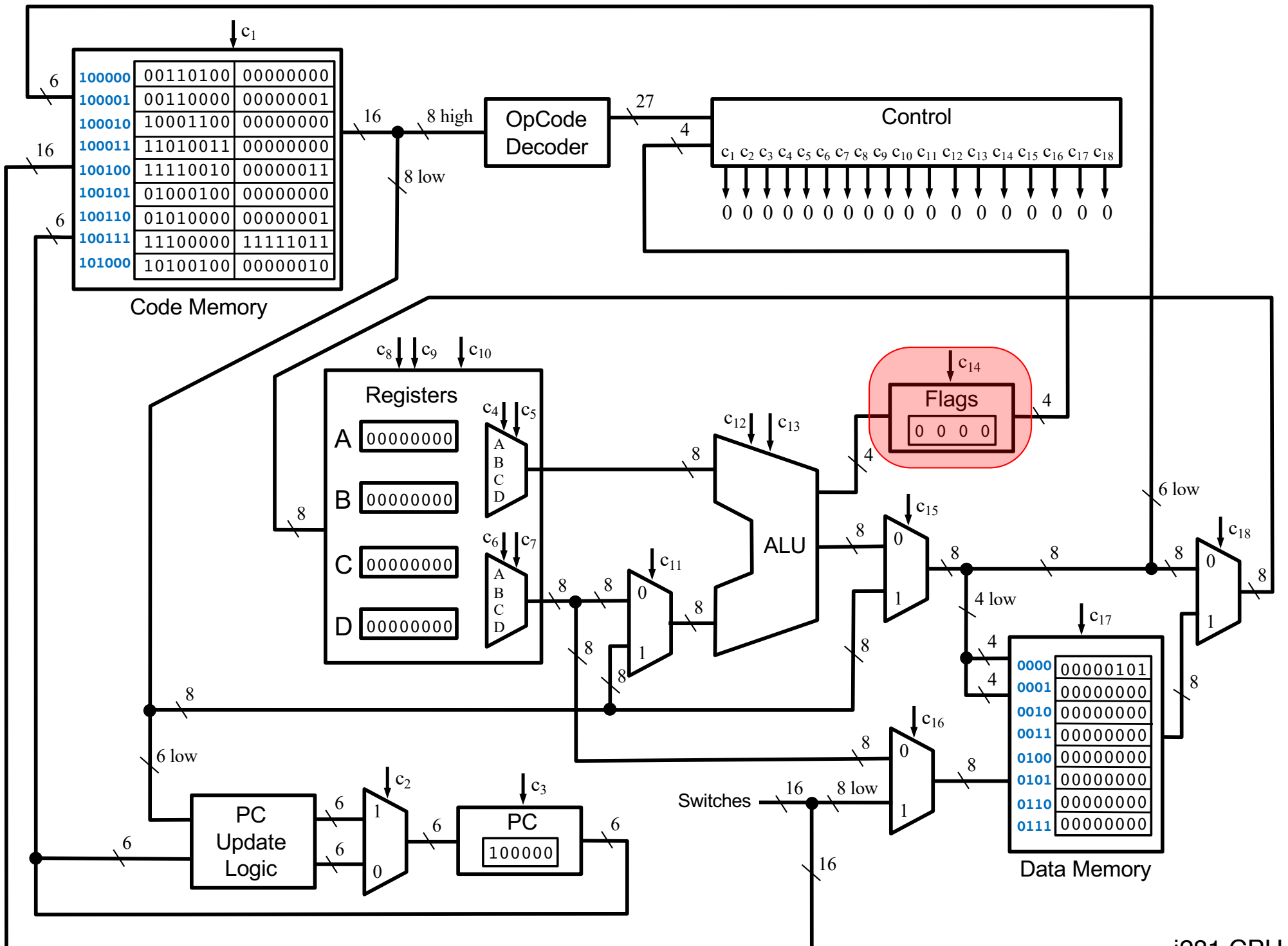

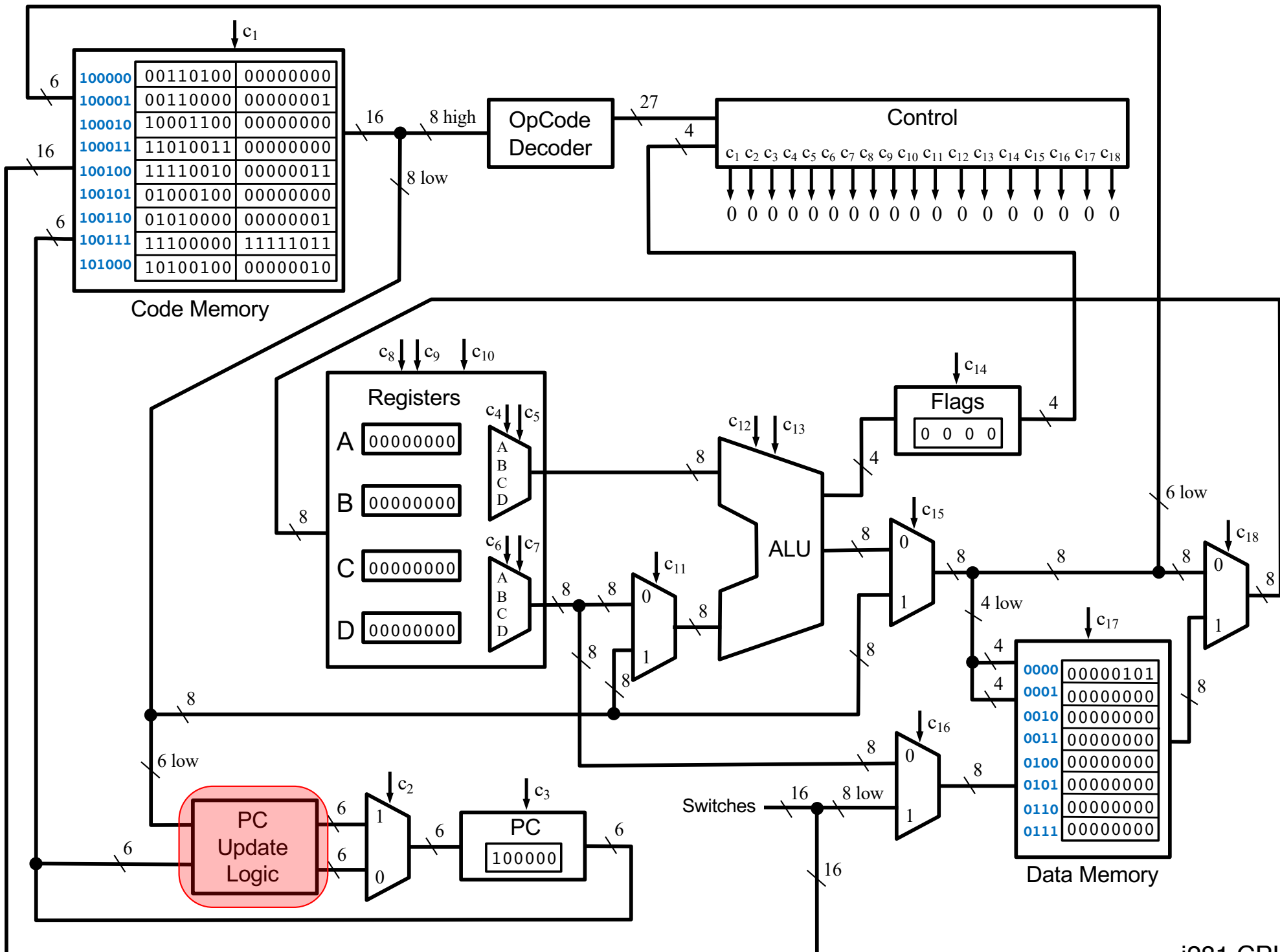


 

# **Some Additional Topics**

# **Examples of Some Famous Microprocessors**

# Intel's 4004 Chip

 


# Technical specifications

- **Maximum clock speed was 740 kHz**
- **Instruction cycle time: 10.8  $\mu$ s  
(8 clock cycles / instruction cycle)**
- **Instruction execution time 1 or 2 instruction cycles  
(10.8 or 21.6  $\mu$ s), 46300 to 92600 instructions per  
second**
- **Built using 2,300 transistors**


 
# Technical specifications

- **Separate program and data storage.**
- **The 4004, with its need to keep pin count down, used a single multiplexed 4-bit bus for transferring:**
  - **12-bit addresses**
  - **8-bit instructions**
  - **4-bit data words**
- **Instruction set contained 46 instructions (of which 41 were 8 bits wide and 5 were 16 bits wide)**
- **Register set contained 16 registers of 4 bits each**
- **Internal subroutine stack, 3 levels deep.**



## Intel 4004 registers

1 1 0 0 0 0 7 0 0 5 0 0 3 0 2 0 1 0 0 (bit position)

### Main registers

		<b>A</b>	<b>Accumulator</b>
	<b>R0</b>	<b>R1</b>	
	<b>R2</b>	<b>R3</b>	
	<b>R4</b>	<b>R5</b>	
	<b>R6</b>	<b>R7</b>	
	<b>R8</b>	<b>R9</b>	
	<b>R10</b>	<b>R11</b>	
	<b>R12</b>	<b>R13</b>	
	<b>R14</b>	<b>R15</b>	

### Program counter

<b>PC</b>	<b>Program Counter</b>
-----------	------------------------


### Push-down address call stack

<b>PC1</b>	<b>Call level 1</b>
<b>PC2</b>	<b>Call level 2</b>
<b>PC3</b>	<b>Call level 3</b>

### Status register

	<b>C</b>	<b>P</b>	<b>Z</b>	<b>S</b>	<b>Flags</b>
--	----------	----------	----------	----------	--------------

# Intel's 8086 Chip

 

## Intel 8086 registers

1<sub>9</sub> 1<sub>8</sub> 1<sub>7</sub> 1<sub>6</sub> 1<sub>5</sub> 1<sub>4</sub> 1<sub>3</sub> 1<sub>2</sub> 1<sub>1</sub> 1<sub>0</sub> 0<sub>9</sub> 0<sub>8</sub> 0<sub>7</sub> 0<sub>6</sub> 0<sub>5</sub> 0<sub>4</sub> 0<sub>3</sub> 0<sub>2</sub> 0<sub>1</sub> 0<sub>0</sub> (bit position)

### Main registers

	AH	AL	<b>AX</b> (primary accumulator)
	BH	BL	<b>BX</b> (base, accumulator)
	CH	CL	<b>CX</b> (counter, accumulator)
	DH	DL	<b>DX</b> (accumulator, other functions)

### Index registers

0000	SI	<b>Source Index</b>
0000	DI	<b>Destination Index</b>
0000	BP	<b>Base Pointer</b>
0000	SP	<b>Stack Pointer</b>

### Program counter


0000	IP	<b>Instruction Pointer</b>
------	----	----------------------------

### Segment registers

CS	0000	<b>Code Segment</b>
DS	0000	<b>Data Segment</b>
ES	0000	<b>ExtraSegment</b>
SS	0000	<b>Stack Segment</b>

### Status register

- - - - O D I T S Z - A - P - C	Flags
---------------------------------	-------

 

**Simplified block diagram of Intel 8088 (a variant of 8086);**

- 1=main registers;
- 2=segment registers and IP;
- 3=address adder;
- 4=internal address bus;
- 5=instruction queue;
- 6=control unit (very simplified!);
- 7=bus interface;
- 8=internal databus;
- 9=ALU;
- 10/11/12=external address/  
data/control bus.

**Questions?**

**THE END**