
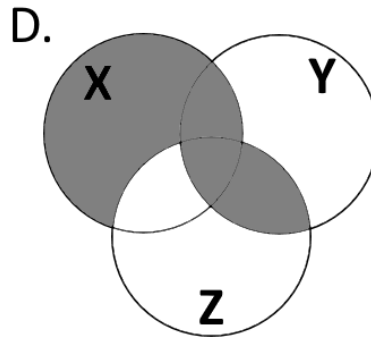
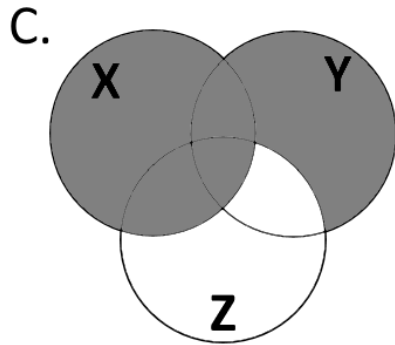
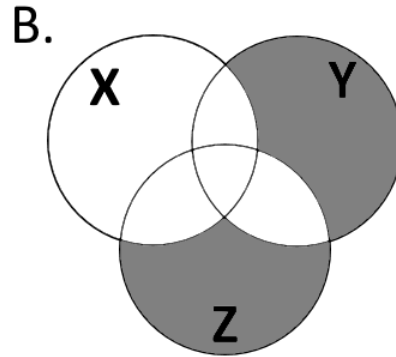


P1. (10 points): Given the Venn diagrams below:

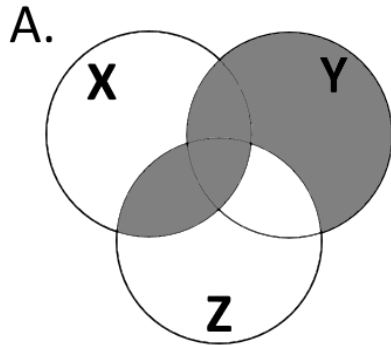
A. Which of the following can be used to represent the function,
 $f(X, Y, Z) = Y\bar{Z} + XZ$



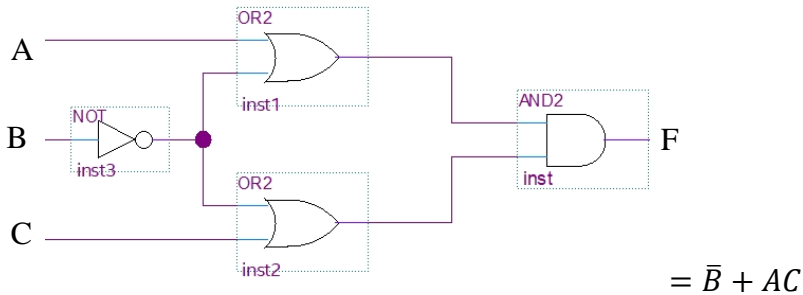B. Write the Boolean expressions for the other Venn Diagrams

P2. (15 points): For the circuit below,

- Find the boolean expression describing the circuit below
- Prove that the equation found in part A. matches the simplified equation below



P3. (15 points): Given truth table below:

a	b	c	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Write the boolean expression for F
- Draw the function using only NAND gates
- Draw the function using only NOR gates

P4. (10 points): Find \bar{f} by first negating the right-hand side and then applying DeMorgan's theorem to simplify the expression.

- $f = xz + \bar{w}y + \bar{x}\bar{x}$
- $f = (a + b)(\bar{a}\bar{b} + c)(a + \bar{b}c)$

P5. (10 points): Given the following functions, write the canonical Sum-of-Products expressions:

- $f(x_1, x_2, x_3) = \sum m(0,1,6)$
- $f(x_1, x_2, x_3) = \sum m(2,4,5,7)$

Boolean algebra,
AND/OR/NAND/NOR gates
Assigned Date: Second Week
Finish by Sep. 7, 2022

P6. (10 points): Given the following functions, write the canonical Products-of-Sums expressions:

- A. $f(x_1, x_2, x_3) = \prod M(0,6,7)$
- B. $f(x_1, x_2, x_3) = \prod M(0,1,4,7)$

P7. (10 points): Use Boolean Algebra to prove the following expressions as equivalent. Show each rule of Boolean Algebra used to perform each step:

- A. $B + BCD + \bar{B}CD + AB + \bar{A}B + \bar{B}C = B + C$
- B. $B\bar{C}(C + A\bar{C}) + (\bar{A} + \bar{C})(\bar{A}B + \bar{A}C) = B\bar{C} + \bar{A}C$

P8. (20 points) Consider the logic function $f(A, B, C) = (\bar{A}BC + A\bar{B}\bar{C} + ABC\bar{C} + \bar{A}\bar{B})$

- A. Draw the logic circuit for the function given above.
- B. Let the cost of a logic circuit be the total number of gates plus the total number of inputs to all gates in the circuit. What is the cost of the circuit in A?
- C. Simplify f using Boolean algebra as much as possible.
- D. Draw the logic circuit for the simplified version of f in C.
- E. What is the cost of the circuit in D?