

P1 (20 points): This problem concerns the algorithmic state machine (ASM) chart shown below:



- A: What are the inputs and the outputs of this state machine?
- B: Draw the state diagram that represents this state machine.
- C: Make state assignments as follows: A=00, B=01, C=10, and D=11. Derive output expressions for this ASM chart using DFFs, AND gates, OR gates, and NOT gates.
- D: Show that the next state expressions can be written as: $S_1^{new} = (\overline{Z} + S_0)(\overline{ZS_1}), S_0^{new} = (\overline{Z} + \overline{S_0})(\overline{ZS_1})$



P2. (20 points): Use synchronous sequential circuit (SSC) analysis to reverse engineer the operation of the circuit shown below.



- A. Is this a Mealy or Moore Machine?
- B. Write expressions for Next State and Output logic
- C. Write the State-Assigned Table for the circuit
- D. Draw the state transition diagram



P3: (10 points): Perform state minimization on the following state diagrams:









P4. (15 points) A sequential circuit has 2 rising edge triggered flip-flops (outputs A and B), two inputs (X and Y) and one output Z. One of the flip-flops is D the other is JK. The logic expressions for this circuit are:

$$D_a = X' \cdot Y + X \cdot A$$
$$J_b = X' \cdot B + X' \cdot A$$
$$K_b = Y \cdot B$$
$$Z = X \cdot B$$

- A. Sketch the circuit diagram
- B. Construct the transition table
- C. Construct the state diagram

P5. (**25 points**) Consider a counter that has a special counting sequence: 0,4,5,1,0,4,5,1, and so on. Draw this counter with minimal number of states.

- A. Draw the state diagram for the counter
- B. Construct the state-assigned table including the next state and output
- C. Draw the circuit diagram for the counter using D flip-flops
- D. Draw the circuit diagram using T flip-flops
- E. Draw the circuit diagram using JK flip-flops

P6. (10 points) Consider a register machine with four registers R0, R1, R2, and R3. Write a complete register machine program (in the table format shown in the lectures) that copies the contents of register 3 into register 2 using register 1 as a temporary storage. The value of R3 at the end of the program must be the same as its value at the beginning of the program. Hint: First, you may have to clear R2 and R1 to zero them. Write a comment for each line/block of your program.