

Name: _____ ID Number: _____

Lab Section: (circle one)	Tue 2-5 (#9)	Wed 7-10 (# 6)	Thur 8-11 (#15)
		Wed 11-2 (#13)	Thur 11-2 (#11)
		Wed 6-9 (#12)	Thur 2-5 (# 8)


Thur 5-8 (# 7)

1. True/False Questions (10 x 1p each = 10p)

- (a) I forgot to write down my name, student ID number, and lab section. TRUE / FALSE
- (b) The circuit in the CprE 281 class logo is called a "half-adder." TRUE / FALSE
- (c) For the same function, the SOP expression is shorter than the POS. TRUE / FALSE
- (d) A POS expression is easily implementable with NOR-NOR logic. TRUE / FALSE
- (e) When converting from base 6 to base 3, each digit in base 6 can be directly mapped to two digits in base 3. TRUE / FALSE
- (f) The shape of a K-Map with 8 input variables will be 8x8. TRUE / FALSE
- (g) For 2-variable functions it is always true that $\Sigma m(1, 3) = \Pi M(0, 2)$. TRUE / FALSE
- (h) These are ordered from small to large: Bantha, Rancor, Sarlacc. TRUE / FALSE
- (i) $A \overline{B} \overline{C} + A B C = A$. TRUE / FALSE
- (j) Behavioral-Procedural Verilog uses assign statements in the modules. TRUE / FALSE

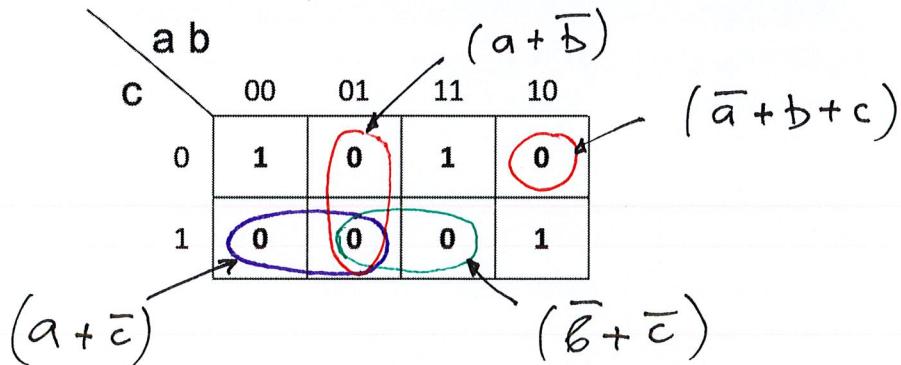2. Three-Variable K-map (5p)

Derive the minimum-cost POS expression for $F(a,b,c)$ that is specified with this K-map.



$$F = (a + \bar{b}) \cdot (\bar{a} + b + c) \cdot (a + \bar{c}) \cdot (\bar{b}' + \bar{c})$$

3.Truth Table and Venn Diagram (5p + 5p = 10p)


(a) Draw the truth table for the following Boolean function:

$$f(x, y, z) = \bar{x} (yz + \bar{y})$$

x	y	z	\bar{x}	$yz + \bar{y}$	f
0	0	0	1	0 1 1	1
0	0	1	1	0 1 1	1
0	1	0	1	0 0 0	0
0	1	1	1	1 1 0	1
1	0	0	0	0 1 1	0
1	0	1	0	0 1 1	0
1	1	0	0	0 0 0	0
1	1	1	0	1 1 0	0

(b) Draw the Venn diagram that corresponds to this K-map:

		y	z		
		00	01	11	10
		0	0	0	1
x	0	1	1	1	0

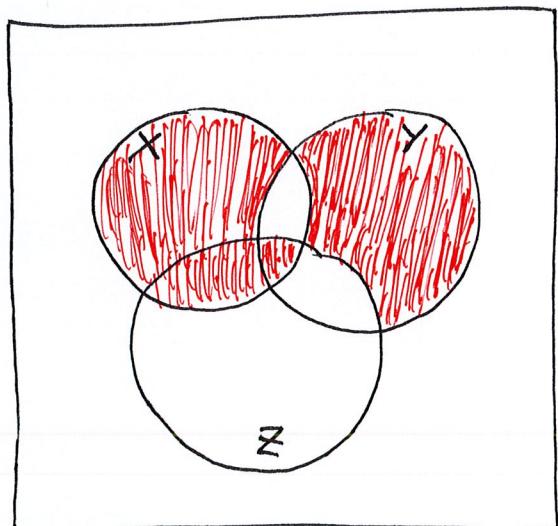

4. Number Conversions (5 x 4p each = 20p)

(a) Convert 10101101_2 to decimal

$$1 \times 2^7 + \cancel{0 \times 2^6} + 1 \times 2^5 + \cancel{0 \times 2^4} + 1 \times 2^3 + 1 \times 2^2 + \cancel{0 \times 2^1} + 1 \times 2^0 = \\ = 128 + 32 + 8 + 4 + 1 = 128 + 40 + 5 = 168 + 5 \\ = \boxed{173_{10}}$$

(b) Convert 91_{10} to binary

$\boxed{1011011_2}$

$$\begin{array}{r|l} 91/2 & 45 \quad 1 \\ 45/2 & 22 \quad 1 \\ 22/2 & 11 \quad 0 \\ 11/2 & 5 \quad 1 \\ 5/2 & 2 \quad 1 \\ 2/2 & 1 \quad 0 \\ 1/2 & 0 \quad 1 \end{array}$$

(c) Convert 165_{10} to hexadecimal

$$\begin{array}{r|l} 165/16 & 10 \quad 5 \\ 10/16 & 0 \quad 10 = A \end{array}$$

$\boxed{A5_{16}}$

(d) Convert 312_4 to octal

$\begin{array}{r} \swarrow \downarrow \searrow \\ 11 \quad 01 \quad 10 \end{array}$

$\begin{array}{r} \overbrace{11}^6 \quad \overbrace{01}^6 \quad \overbrace{10}^6 \\ | \quad | \quad | \\ 6 \quad 6 \end{array}$

Convert to binary, then to octal.

$312_4 = \boxed{66_8}$

(e) Find the value of X that satisfies: $10_5 + 10_6 + 10_7 = X_8$

$$\begin{array}{r} 18/8 = 2 \quad 2 \\ 2/8 = 0 \quad 2 \end{array}$$


$$\underbrace{5_{10}}_{18_{10}} + \underbrace{6_{10}}_{\text{+}} + \underbrace{7_{10}}_{= 228} = 228$$

$\Rightarrow X = 22$

5. Verilog Code (10p)

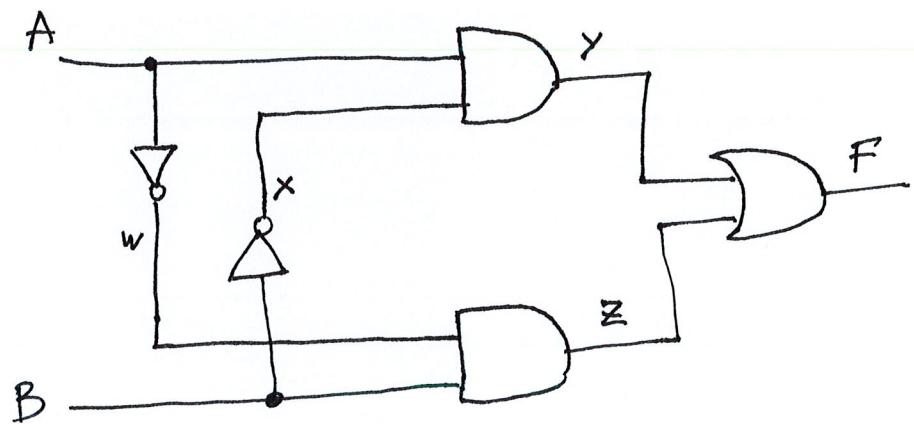a) Draw the circuit diagram that corresponds to the Structural Verilog module shown below. Clearly label all inputs, outputs and wires of your circuit

```
module mystery(A, B, F);
    input A, B;
    output F;
    not(W, A);
    not(X, B);
    and(Y, A, X);
    and(Z, W, B);
    or(F, Y, Z);
endmodule
```



$$F = A\bar{B} + \bar{A}B$$

This is an XOR.

b) Now write the Behavioral-Continuous Verilog code for the circuit above.

```
module mystery(A, B, F);
    input A, B;
    output F;
    assign F = (~A & B) | (A & ~B);
endmodule
```



$$\text{assign } F = (\sim A \& B) | (A \& \sim B);$$

also ok

Note: $\text{assign } F = A \wedge B;$

6. Waveform (3 x 5p = 15p)

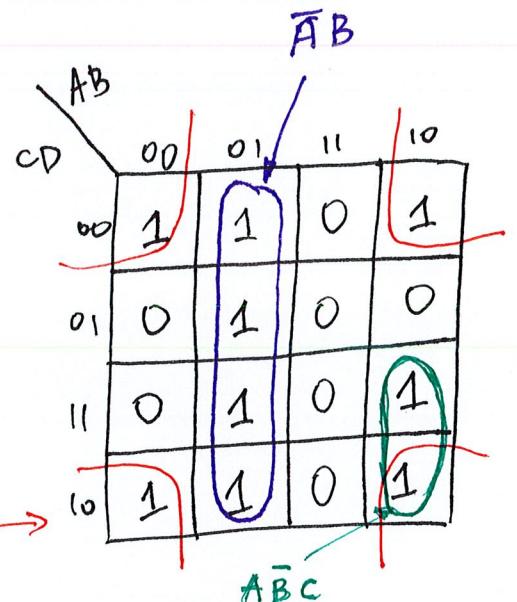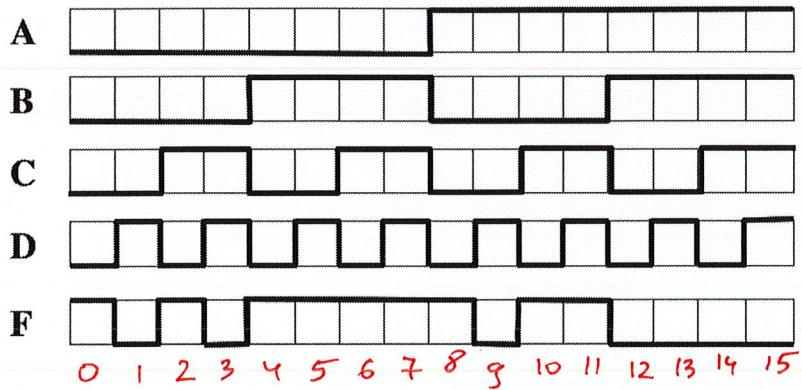
(a) Given this Questa Sim waveform, draw the corresponding K-map for $F(A, B, C, D)$.



(b) Use the K-map from (a) to derive the minimum-cost Sum-of-Products (SOP) expression for F .


$$F = \bar{A}\bar{B} + \bar{B}\bar{D} + A\bar{B}C$$

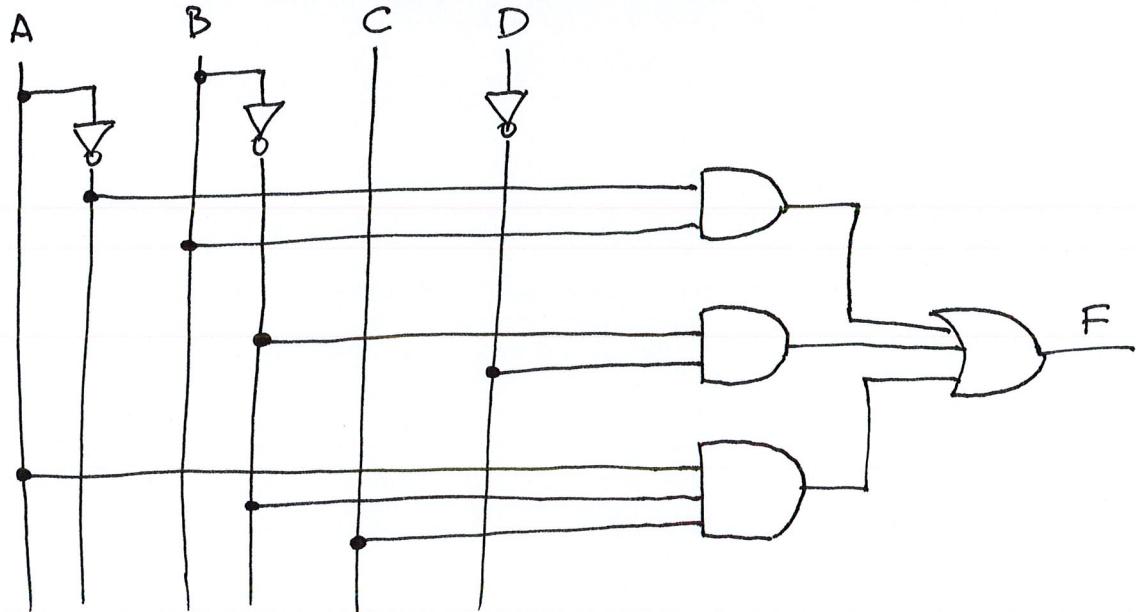(c) Draw the circuit for the minimum SOP expression. Label all inputs and outputs.




7. Derive the minimum POS expression using a K-map (10p + 5p = 15p)

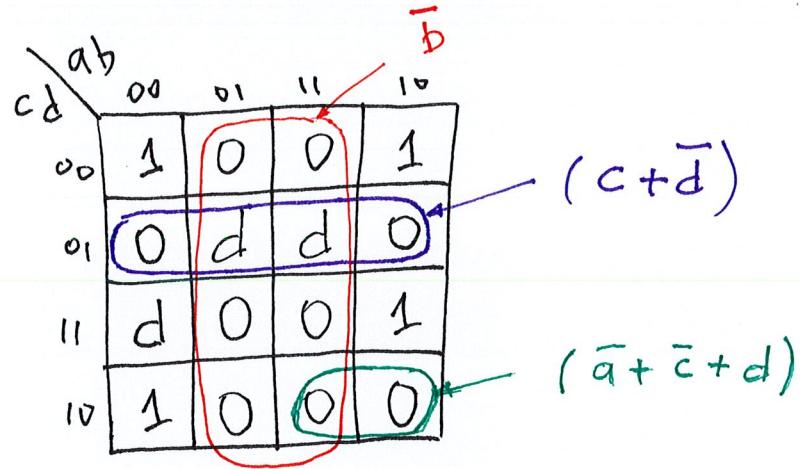(a) Use a K-map to derive the minimum-cost POS expression for the following function
 $f(a,b,c,d) = \prod M(1, 4, 6, 7, 9, 10, 12, 14, 15) + D(3, 5, 13).$




$$f = (\bar{a} + \bar{c} + d) \cdot (c + \bar{d}) \cdot \bar{b}$$

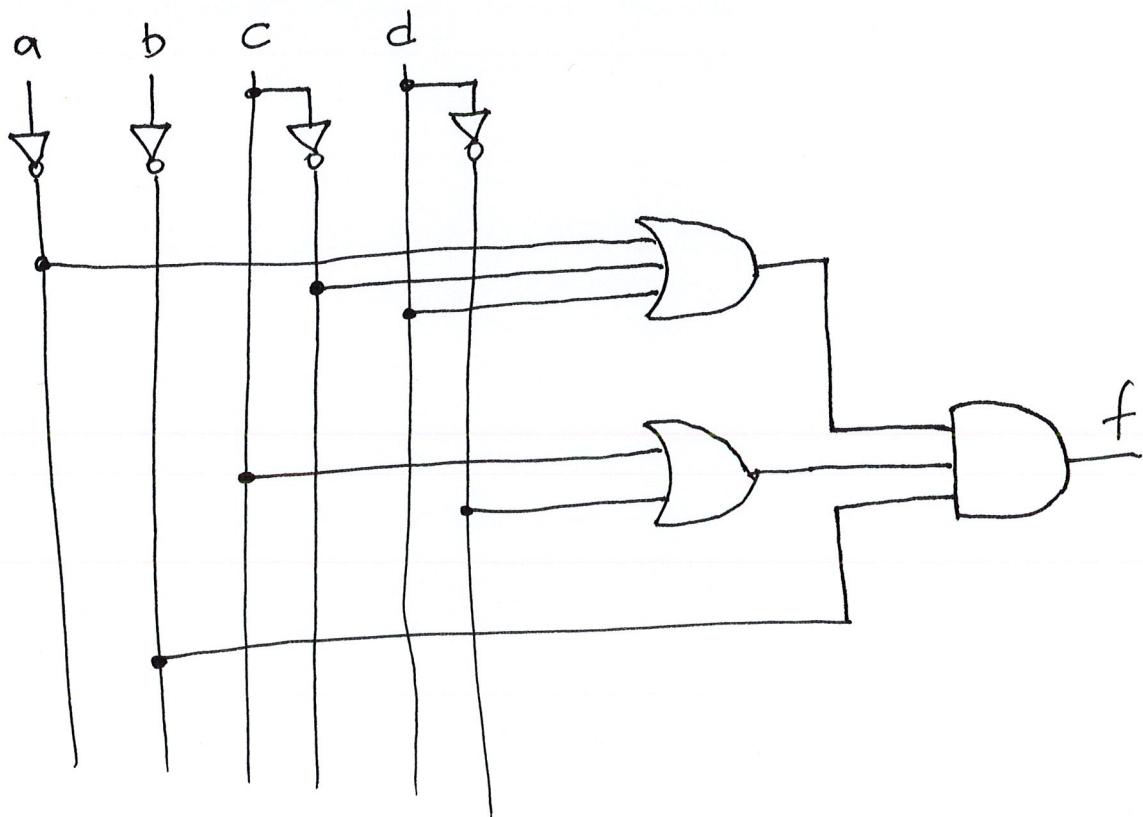(b) Draw the circuit diagram for the minimum-cost Product-Of-Sums (POS) expression. Clearly label all inputs and outputs.



8. Redraw the Circuit ($3 \times 5p = 15p$)

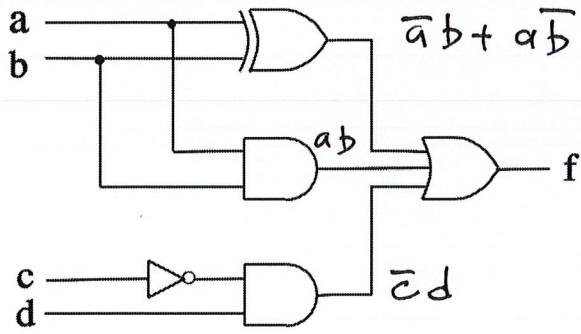(a) Write the Boolean expression that corresponds to this circuit (do not simplify it yet).




$$f = \bar{a}b + a\bar{b} + ab + \bar{c}d$$

(b) Use the theorems and axioms of Boolean algebra to simplify the expression that corresponds to the circuit form (a) into a minimum-cost SOP expression.

$$\begin{aligned} f &= \bar{a}b + a\bar{b} + ab + \bar{c}d \\ &= \bar{a}b + a(\bar{b} + b) + \bar{c}d && // \text{Theorem 8b} \\ &= \bar{a}b + a + \bar{c}d && // \text{Theorem 16a} \\ &= a + b + \bar{c}d. \end{aligned}$$

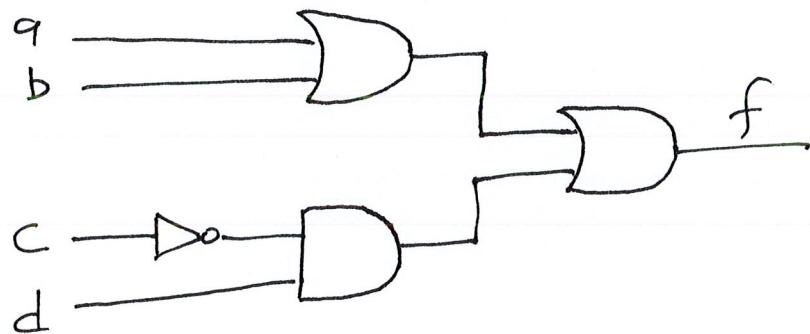
(c) Use the minimum-cost SOP expression to redraw the circuit using only basic logic gates with at most 2-inputs each (i.e., only AND, OR, NOT gates).



9. Minimization and NAND implementation (3 x 5p = 15p)

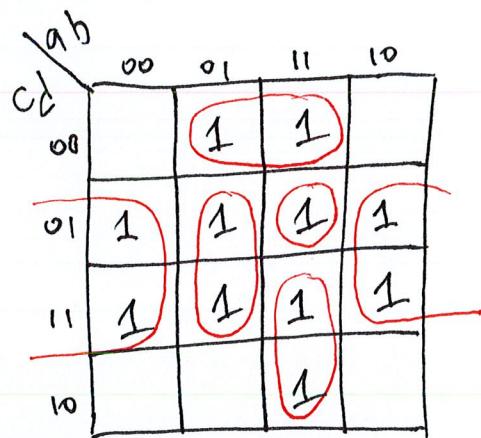
(a) Draw the K-map that corresponds to the following Boolean function:

$$f = \overline{a}b\overline{d} + a\overline{b}\overline{c}\overline{d} + b\overline{c}\overline{d} + ab\overline{c} + \overline{b}d$$




(b) Redraw the K-map from (a) and derive the minimum-cost SOP expression for f.

$$f = ab + b\overline{c} + d$$

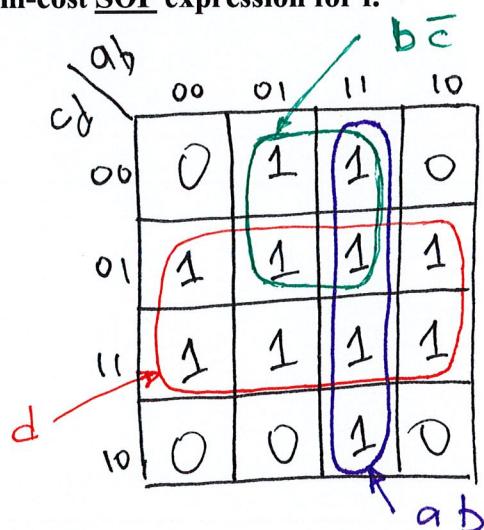

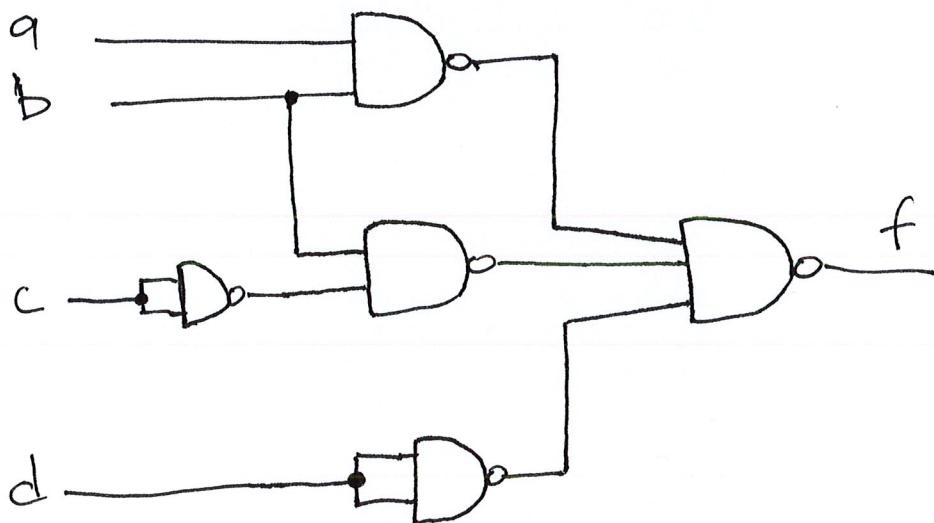(c) Draw the circuit for the minimum-cost SOP expression using only NAND gates.
Clearly label all inputs and outputs.



10. Boolean Algebra (15p)

Use the theorems and axioms of Boolean algebra to simplify the following expression:

$$F = \overline{AB}(\overline{B} + ABC) + \overline{\overline{C}\overline{B}\overline{A}} + \overline{\overline{ABC}} + \overline{C}(\overline{AB} + \overline{AB} + A) = \overline{\lambda + \beta + \gamma + \delta},$$

where

$$\lambda = \overline{AB}(\overline{B} + ABC) = \overline{AB}\overline{B} + \overline{AB}ABC = 0,$$

$$\beta = \overline{C}\overline{B}\overline{A} = (\overline{C} + \overline{B})\overline{A} = \overline{CA} + \overline{AB},$$

$$\gamma = \overline{\overline{ABC}} = \overline{\overline{AB}} + \overline{C} = AB + \overline{C},$$

$$\delta = \overline{C}(\overline{AB} + \overline{AB} + A) = \overline{C}(\overline{A}(\overline{B} + B) + A) = \overline{C}(\overline{A} + A) = \overline{C}.$$

$$F = \overline{\lambda + \beta + \gamma + \delta}$$

$$= \overline{0 + \overline{C}A + \overline{AB} + AB + \overline{C} + \overline{C}}$$

$$= \overline{\overline{C}A + (\overline{A} + A)B + \overline{C}}$$

$$= \overline{\overline{C}(A + 1) + B}$$

$$= \overline{\overline{C} + B}$$

$$= \overline{\overline{C} \cdot \overline{B}}$$

$$= \overline{B}C.$$

Question	Max	Score
1. True/False	10	
2. Three-variable K-map	5	
3. Truth Table & Venn D.	10	
4. Number Conversions	20	
5. Verilog Code	10	
6. Waveform	15	
7. POS with K-map	15	
8. Redraw the Circuit	15	
9. Minimization & NAND	15	
10. Boolean Algebra	15	
TOTAL:	130	