


Sample Solutions

Name: _____

ID Number: _____

Lab Section: Tue 2-5 (#9) Wed 7-10 (#6) Thur 8-11 (#15)
 (circle one) Wed 11-2 (#13) Thur 11-2 (#11)
Wed 6-9 (#12) Thur 2-5 (#8)
Thur 5-8 (#7)

 
1. True/False Questions (10 x 1p each = 10p)



- (a) I forgot to write down my name, lab section, and student ID number. TRUE / FALSE
- (b) Any Boolean function can be implemented using only 2-to-4 decoders. TRUE / FALSE
- (c) A full-adder can be constructed using two half-adders and one XOR gate. TRUE / FALSE *OR*
- (d) The phrase "This is the way" refers to a code. TRUE / FALSE
- (e) A JK flip-flop has 2 inputs, 2 outputs, and can store 2 bits of information. TRUE / FALSE
- (f) The characteristic tables of the SR latch and the $\overline{S} \overline{R}$ latch are the same. TRUE / FALSE
- (g) A demultiplexer changes its outputs on the positive edge of the clock. TRUE / FALSE
- (h) A 32-bit hierarchical carry-lookahead adder sets the carries in 7 gate delays. TRUE / FALSE
- (i) In 1's complement, the magnitude of a number with all bits set to 1 is 0. TRUE / FALSE
- (j) The ALU of the i281 CPU has one 8-bit ripple-carry adder. TRUE / FALSE

 2. Decoder Expressions (5p)

Draw the truth table for the 1-to-2 decoder with enable that is shown below. Then, write the Boolean expressions for the outputs Z_0 and Z_1 in terms of the inputs X and Y.



X	Y	z_0	z_1
0	0	0	0
0	1	1	0
1	0	0	0
1	1	0	1

$z_0 = \overline{X} Y$



$z_1 = X Y$

3. Computations with Adders (5 x 3p each = 15p)

In all problems below, the binary numbers are stored in 2's complement representation. For each of the following, assign either a 0 or a 1 to each input and output of the 5-bit adder such that it computes the given expression. The problem in a) is already solved.

a) $(+5) + (+6) = +11$



b) $(+3) + (+8) = +11$

  

$$\begin{array}{r} + 00011 \\ + 01000 \\ \hline 01011 \end{array}$$



c) $(+14) + (-6) = +8$

d) $(-4) + (-5) = -9$

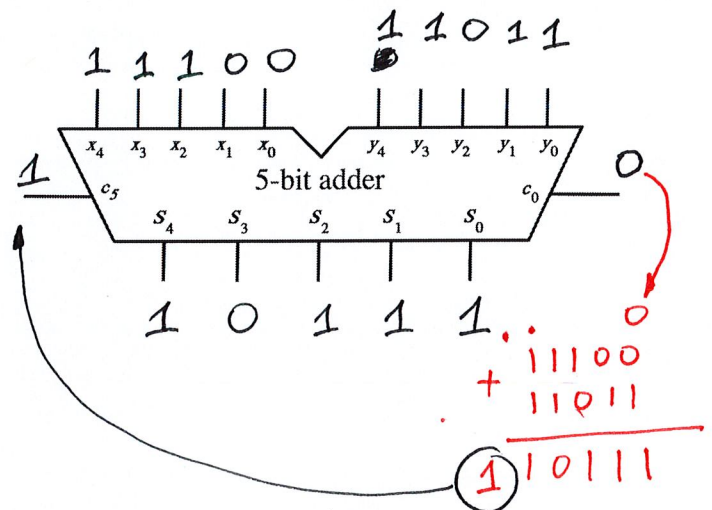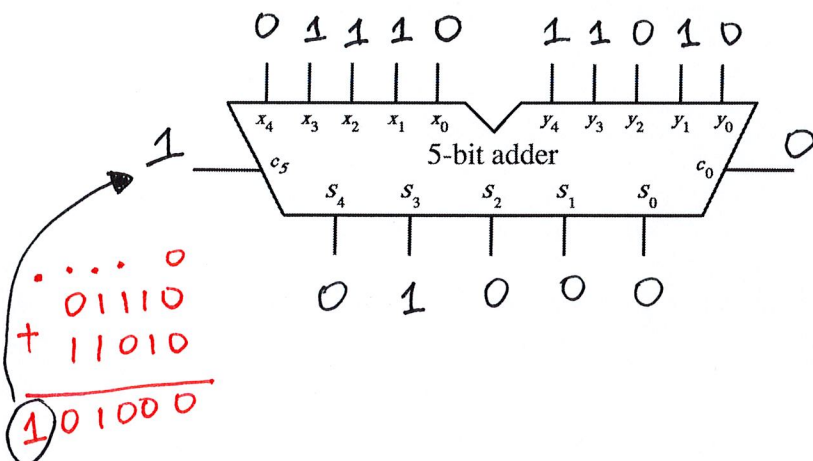


e) $(-7) - (+9) = -16$

f) $(-11) - (-2) = -9$

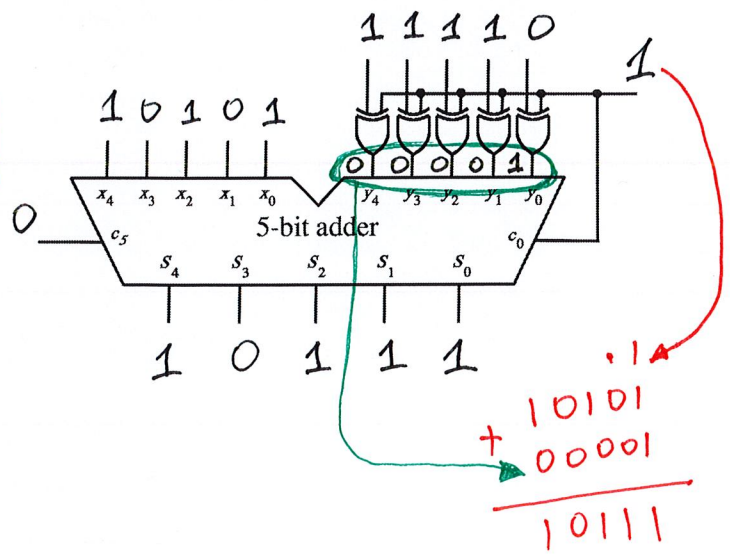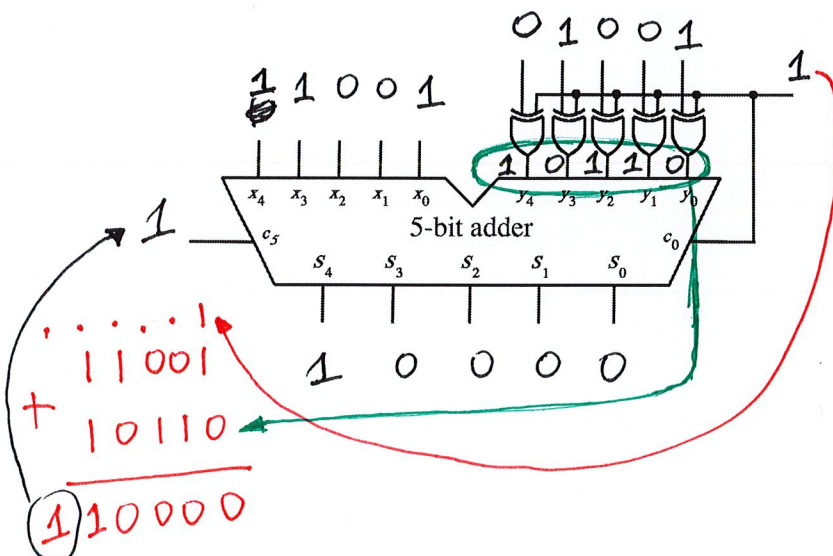


4. Basic Circuits (3 x 5p each = 15p).

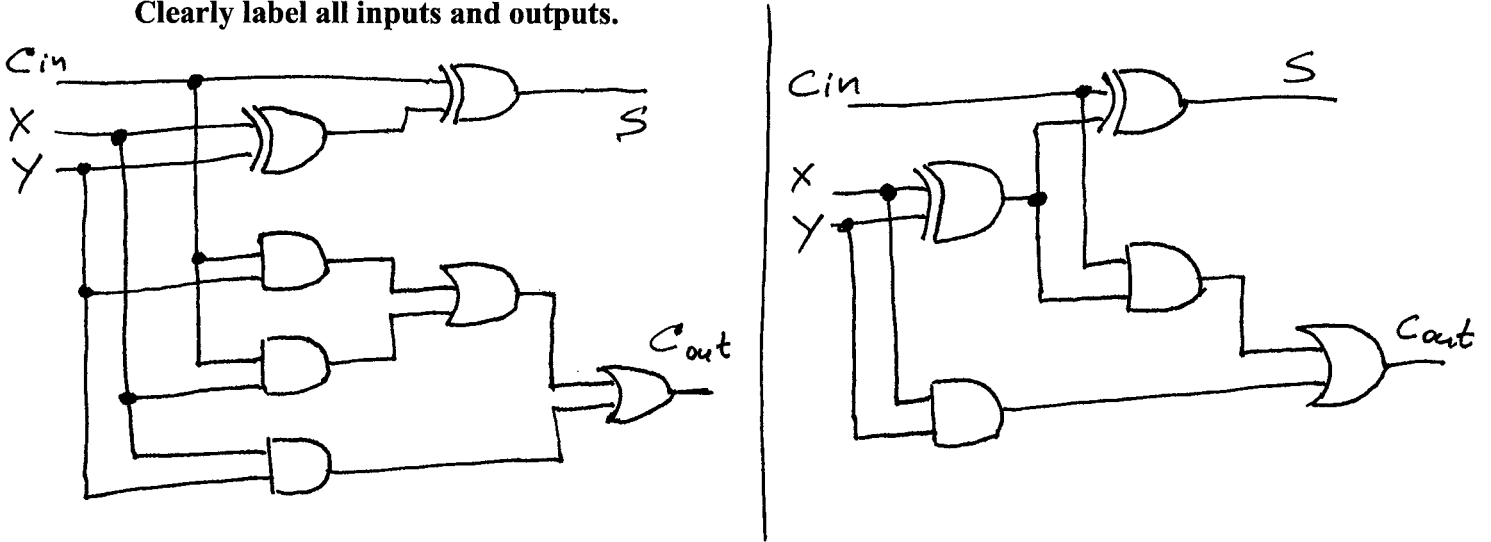
(a) Draw the complete wiring diagram for a full-adder using only 2-input logic gates. Clearly label all inputs and outputs.



 (b) Draw the complete wiring diagram for a gated D latch (with NOR gates for the latch). Clearly label all inputs and outputs.



 (c) Draw the complete wiring diagram for a 1-to-2 demultiplexer using only NAND gates. Clearly label all inputs and outputs.



5. Number Conversions (3p + 4p + 4p + 4p = 15p)

(a) Convert 191_{10} to hexadecimal.

$$\begin{array}{r} 191 / 16 = 11 \quad 15 \\ \hline 16 \\ \hline 31 \\ \hline -16 \\ \hline 15 \end{array}$$

$191_{10} = BF_{16}$

11 = B 15 = F

(b) Convert -65_{10} to an 8-bit binary number in 2's complement representation.

$$\begin{array}{r} 65 / 2 = 32 \quad 1 \\ 32 / 2 = 16 \quad 0 \\ 16 / 2 = 8 \quad 0 \\ 8 / 2 = 4 \quad 0 \\ 4 / 2 = 2 \quad 0 \\ 2 / 2 = 1 \quad 0 \\ 1 / 2 = 0 \quad 1 \end{array}$$

7-bit
pad
negate

$$\begin{array}{r} 1000001 \\ 01000001 \\ \hline 10111111 \end{array}$$

result in 2's complement.

(c) Convert the following 32-bit float number (in IEEE 754 format) to decimal.

negative →

$$1 \mid \underbrace{10000010}_{130} \mid \underbrace{011100000000000000000000}_{\substack{\uparrow \frac{1}{4} \\ \uparrow \frac{1}{8} \\ \uparrow \frac{1}{16}}}$$

$$(-1)^1 \times 2^{130-127} \times \left(1 + \frac{1}{4} + \frac{1}{8} + \frac{1}{16}\right) = -2^3 \times \left(\frac{16+4+2+1}{16}\right) = -\frac{23}{2} = -11.5$$

(d) Write down the 32-bit floating point representation (in IEEE 754 format) for -42.0

$$42 / 32 = 1.3125$$

$$\begin{array}{r} 42 \\ -32 \\ \hline 100 \\ -96 \\ \hline 40 \\ -32 \\ \hline 80 \\ -64 \\ \hline 160 \\ -160 \\ \hline 0 \end{array}$$

32 = 2⁵
132 - 127 = 5

$$\begin{array}{r} 0.3125 \\ -0.25 \\ \hline 0.0625 \end{array}$$

0.5
0.25 ✓
0.125
0.0625 ✓


$$1 \mid 10000100 \mid 010100 \dots 0$$

19 zeros


6. Flip-Flops and Timing Diagrams (3 x 5p = 15p)

Complete the timing diagram for the specified flip-flop such that the output Q will be as indicated. Assume that the input signal can change only on the vertical lines. Also, assume that the setup time t_{su} and the hold time t_h are each equal to the width of one square.

 
a) Complete the timing diagram for the D input to a positive-edge triggered D flip-flop.



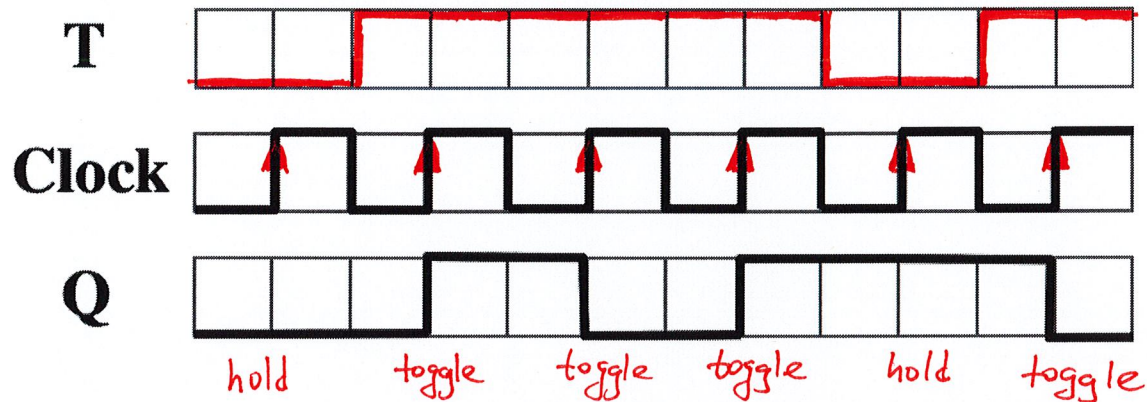
b) Complete the timing diagram for the T input to a positive-edge triggered T flip-flop.



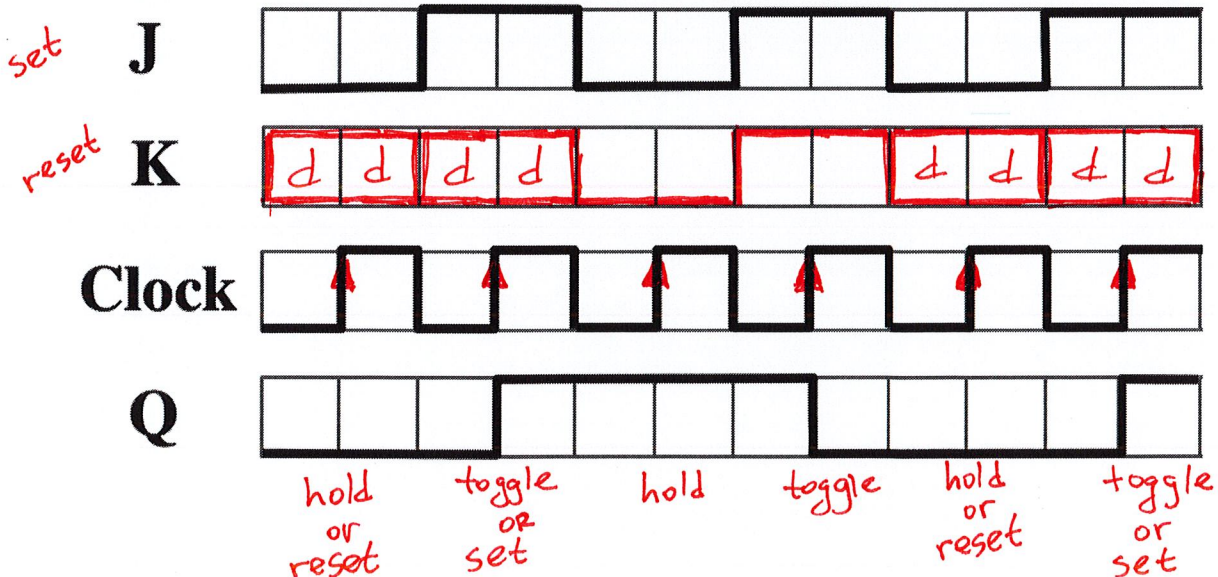c) Complete the timing diagram for the K input to a positive-edge triggered JK flip-flop. If more than one value is possible for J at any time, indicate that with a don't care (d).



7. Mystery Circuit (3 x 5p = 15p)

 

a) Draw the truth table for the outputs P and Q as functions of A, B, and C. (5p)

A	B	C	P	Q
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

b) Use K-maps to find the minimum-cost SOP expressions for P and Q. (5p)

C	AB			
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

C	AB			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$P = AB + BC + AC$$

$$Q = A \oplus B \oplus C$$

c) What type of familiar circuit is this equivalent to? Explain. (5p)

This is a full-adder with $Q = \text{Sum}$ and $P = \text{Carry}$. The inputs A, B, and C are the inputs to the full-adder.

8. Implement a JK flip-flop using a T flip-flop. (3p +4p +4p = 10p)

You need to implement a JK flip-flop, but you only have a T flip-flop and some extra logic gates (ANDs, ORs, NOTs, and XORs). You also know the effects of the J and K inputs on the output Q. Hopefully, that is all you need to get the job done.


- a) Draw the truth table for a positive-edge-triggered JK flip-flop. Hint: the inputs are J, K, and Q(t); the output is Q(t+1). (3p)
- b) Add a column T to the truth table and infer the value of T that will cause the transition from Q(t) to Q(t+1). Use a K-map to derive the minimum-cost SOP expression for T. (4p)
- c) Draw the circuit for the JK flip-flop, using the graphical symbol for a T flip-flop and any other necessary logic gates. Clearly label all inputs, outputs, and pins. (4p)

a)

	J	K	Q_t	Q_{t+1}
hold	0	0	0	0
	0	0	1	1
reset	0	1	0	0
	0	1	1	0
set	1	0	0	1
	1	0	1	1
toggle	1	1	0	1
	1	1	1	0


b)

T
0
0
0
1
1
1
1
1

 

$$T = J\bar{Q}_t + KQ_t$$

c)

 

9. Alternative Implementation (3 x 5p each = 15p)

a) Draw the truth table for the function $f(a, b, c) = \overline{a+b} + \overline{c}(\overline{a+b})$.

a	b	c	$\overline{a+b} + ab\overline{c}$	f
0	0	0	1	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	1
1	1	1	0	0


$$f(a, b, c) = \overline{a+b} + \overline{c}(\overline{a+b})$$

$$= \overline{a+b} + \overline{c}(\overline{a \cdot b})$$

$$= \overline{a+b} + ab\overline{c}$$


b) Implement this function using a minimal number of 2-to-1 multiplexers. You must use only 2-to-1 multiplexers and no other logic gates. Assume that the signals a, b, and c are available only in their non-inverted form. You can also use the constants 0 and 1. Clearly label all inputs, outputs, and pins.

a	b	c	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

 

c) Implement this function using one 4-to-1 multiplexer and one XOR gate. Clearly label all inputs, outputs, and pins.



a	b	c	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

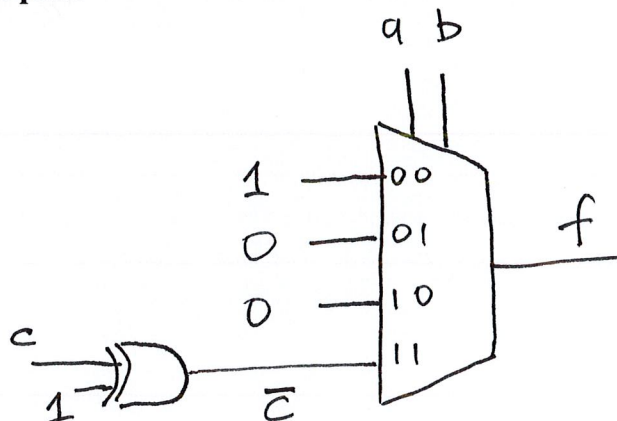



10. Error-Correcting Code (7p + 8p = 15p) [Use the space on the next page if needed.]

(a) The Hamming (7, 4) code is a popular error-correcting code that is used to store or transfer data that can be corrupted by noise. Given four data bits (d_4, d_3, d_2, d_1) this code computes three parity bits (p_3, p_2, p_1) and interleaves them to construct a 7-bit message $m_7, m_6, m_5, m_4, m_3, m_2, m_1$ from $d_4, d_3, d_2, d_1, p_2, p_1, p_3$. Parity bit p_1 is computed from d_1, d_2, d_3, d_4 . Parity bit p_2 from d_1, d_3, d_2, d_4 . And parity bit p_3 from d_2, d_3, d_2, d_4 . In all cases, what is computed is even parity. That is, the parity bit is set to 0 if the number of 1's in the three corresponding data bits is even. Otherwise, it is set to 1. Draw a circuit that encodes a 7-bit message given 4-bit input data. Explain your solution.

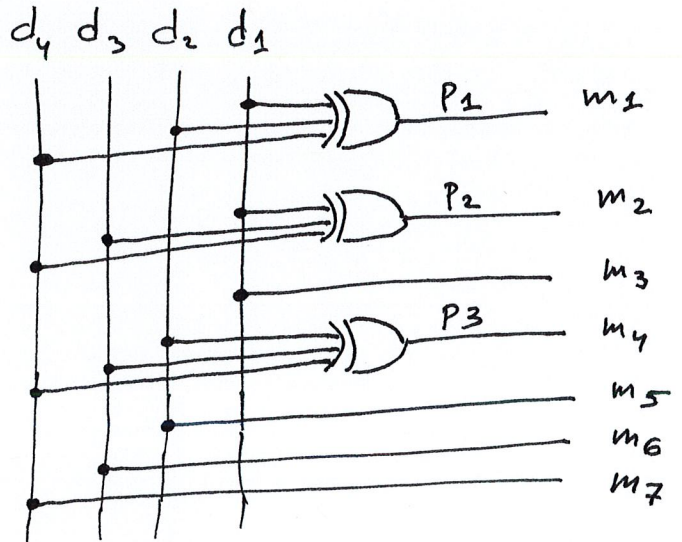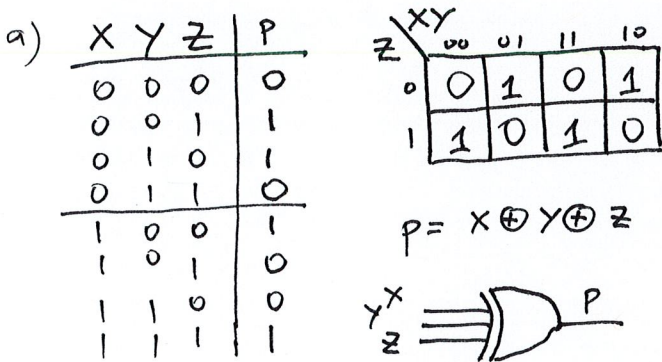(b) When the message is received the code has the ability to detect and correct 1-bit errors. Three new parity bits are computed: P_3, P_2, P_1 (note the capital letter). P_1 is 0 if the number of 1's in m_7, m_5, m_3, m_1 is even. Otherwise, it is 1. Similarly for P_2 , which depends on m_7, m_6, m_3, m_2 . And P_3 , which is computed from m_7, m_6, m_5, m_4 . If $P_3=P_2=P_1=0$, then the message was not corrupted. When P_3, P_2, P_1 is interpreted as a binary number it points to the 1-based index of the bit in $m_7, m_6, m_5, m_4, m_3, m_2, m_1$ that is wrong. This bit can be corrected by simply flipping its value (from 1 to 0 or from 0 to 1). Draw a circuit that uses this method to detect and correct 1-bit errors. Explain.



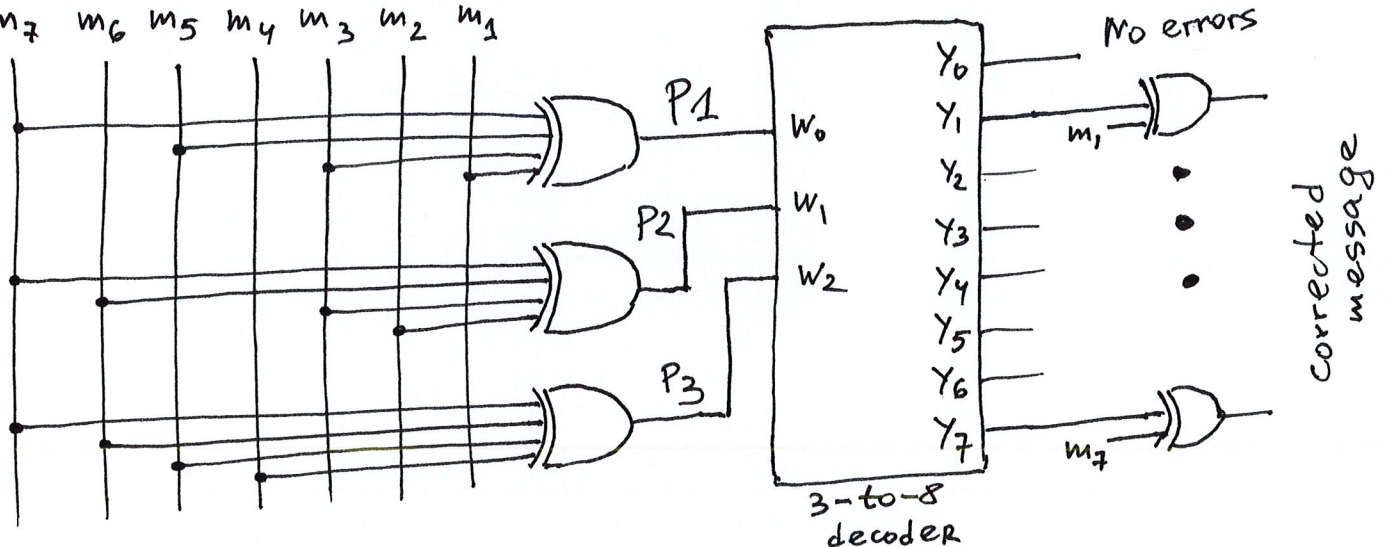 The XOR is used to compute the parity in all 3 cases. Just its three inputs are different.



The parity bits are now computed with 4-input XORs. They go as inputs to the 3-to-8 decoder. If $P_1=P_2=P_3=1$, then only Y_0 is set to 1 to indicate that the message is OK. All other Y 's will be 0's and the XORs will output the m 's. In all other cases the decoder will have a 1 on the index of the wrong/corrupted bit. That one will make the XOR work like NOT which will correct the wrong bit!

Question	Max	Score
1. True/False	10	
2. Decoder Expressions	5	
3. Computations with Adders	15	
4. Basic Circuits	15	
5. Number Conversions	15	
6. Flip-Flops	15	
7. Mystery Circuit	15	
8. JK flip-flop with T flip-flop	10	
9. Alternative Implementation	15	
10. Error-Correcting Code	15	
TOTAL:	130	