

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Examples of Solved Problems

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW4 is due today**

Administrative Stuff

- **HW5 is out**
- **It is due on Monday Sep 26 @ 10pm.**
- **It is posted on the class web page**
- **I also sent you an e-mail with the link.**
- **You can use this as a preparation for the exam.**

Administrative Stuff

- **Midterm Exam #1**
- **When: Friday Sep 23.**
- **What: Chapter 1 and Chapter 2 plus number systems**
- **The exam will be closed book but open notes
(you can bring up to 3 pages of handwritten notes).**
- **It will be in this room.**
- **Review session: This Wednesday during lecture**

Topics for the Midterm Exam

- **Binary Numbers**
- **Octal Numbers**
- **Hexadecimal Numbers**
- **Conversion between the different number systems**
- **Truth Tables**
- **Boolean Algebra**
- **Logic Gates**
- **Circuit Synthesis with AND, OR, NOT**
- **Circuit Synthesis with NAND, NOR**
- **Converting an AND/OR/NOT circuit to NAND circuit**
- **Converting an AND/OR/NOT circuit to NOR circuit**
- **SOP and POS expressions**

Topics for the Midterm Exam


- Mapping a Circuit to Verilog code
- Mapping Verilog code to a circuit
- Multiplexers
- Venn Diagrams
- K-maps for 2, 3, and 4 variables
- Minimization of Boolean expressions using theorems
- Minimization of Boolean expressions with K-maps
- Incompletely specified functions (with don't cares)
- Functions with multiple outputs
- Something from Star Wars

**All possible Boolean functions
with two input variables**

**There are 16 possible Boolean functions
with two input variables**

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

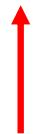

constant 0



constant 1

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1



NOR(x, y)



OR(x, y)

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1



$$m_1 = \bar{x} y$$



$$M_1 = x + \bar{y}$$

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1



NOT(x)



x

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1



$$m_2 = x \bar{y}$$



$$M_2 = \bar{x} + y$$

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1



NOT(y)



y

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1




XOR(x, y)

XNOR(x, y)

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

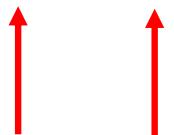

NAND(x, y) AND(x, y)

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

0 NOR m_1 \bar{x} m_2 \bar{y} XOR NAND AND XNOR y M_2 x M_1 OR 1

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

0 m_0 m_1 \bar{x} m_2 \bar{y} XOR M_3 m_3 XNOR y M_2 \bar{x} M_1 M_0 1

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

0 m_0 m_1 \bar{x} m_2 \bar{y} $m_1 + m_2$ M_3 m_3 $M_1 \bullet M_2$ y M_2 x M_1 M_0 1

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

0 m_0 m_1 m_2 $m_0 + m_2$ $m_1 + m_2$ M_3 m_3 $M_1 \bullet M_2$ $M_0 \bullet M_2$ M_2 $M_0 \bullet M_1$ M_1 M_0 1

These are all valid groupings

	x	0	1
0	y	1	0
1		0	0

	x	0	1
0	y	0	0
1		1	0

	x	0	1
0	y	0	1
1		0	0

	x	0	1
0	y	0	0
1		0	1

$\bar{x} \quad \bar{y}$

$\bar{x} \ y$

$x \bar{y}$

$x \ y$

These are all valid groupings

	x	
y	0	1
0	1	0
1	1	0

	x	
y	0	1
0	0	1
1	0	1

	x	
y	0	1
0	1	1
1	0	0

	x	
y	0	1
0	0	0
1	1	1

\bar{x}

x

\bar{y}

y

These are all valid groupings

	x	0	1
0	y	1	1
1		1	0

$$\bar{x} + \bar{y}$$

	x	0	1
0	y	1	0
1		1	1

$$\bar{x} + y$$


	x	0	1
0	y	1	1
1		0	1

$$x + \bar{y}$$


	x	0	1
0	y	0	1
1		1	1

$$x + y$$

These are valid too

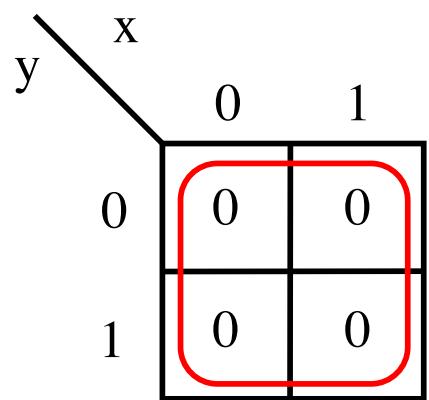

constant 0

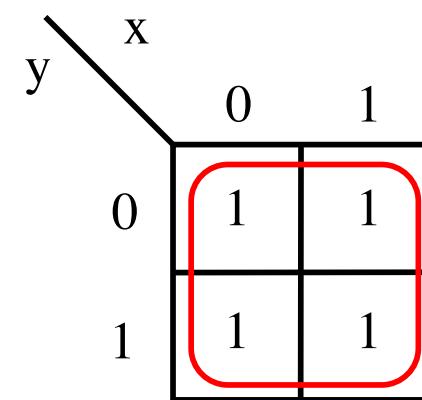

constant 1

**These are not valid groupings,
but they correspond to XOR and XNOR**

A truth table for the XOR function. The horizontal axis is labeled 'x' and the vertical axis is labeled 'y', both with values 0 and 1. The table shows the output 'z' for each input pair: (0,0) is 0, (0,1) is 1, (1,0) is 1, and (1,1) is 0. A red diagonal line highlights the path from (0,0) to (1,1), indicating an invalid grouping of terms.

	x	0	1
y	0	0	1
0	0	1	
1	1		0

A truth table for the XNOR function. The horizontal axis is labeled 'x' and the vertical axis is labeled 'y', both with values 0 and 1. The table shows the output 'z' for each input pair: (0,0) is 1, (0,1) is 0, (1,0) is 0, and (1,1) is 1. A red diagonal line highlights the path from (0,0) to (1,1), indicating an invalid grouping of terms.

	x	0	1
y	0	1	
0	1	0	
1	0		1

**These are not valid groupings,
but they correspond to XOR and XNOR**

A truth table for the XOR function. The horizontal axis is labeled 'x' and the vertical axis is labeled 'y', both with values 0 and 1. The table shows the result of the XOR operation for all combinations of x and y. The result is 0 when both inputs are the same (0,0 or 1,1) and 1 when the inputs are different (0,1 or 1,0). The cells where the result is 1 are highlighted with red boxes.

		x	y
		0	1
x	0	0	1
	1	1	0

XOR(x, y)

A truth table for the XNOR function. The horizontal axis is labeled 'x' and the vertical axis is labeled 'y', both with values 0 and 1. The table shows the result of the XNOR operation for all combinations of x and y. The result is 1 when both inputs are the same (0,0 or 1,1) and 0 when the inputs are different (0,1 or 1,0). The cells where the result is 1 are highlighted with red boxes.


		x	y
		0	1
x	0	1	0
	1	0	1

XNOR(x, y)

The Link Between Truth Tables and Venn Diagrams


Place the minterms on the Venn diagram

A	B	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

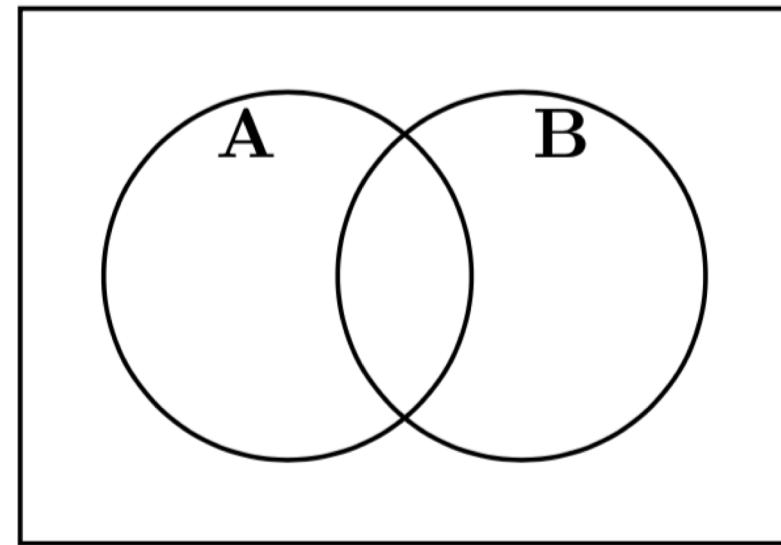


Place the minterms on the Venn diagram

A	B	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

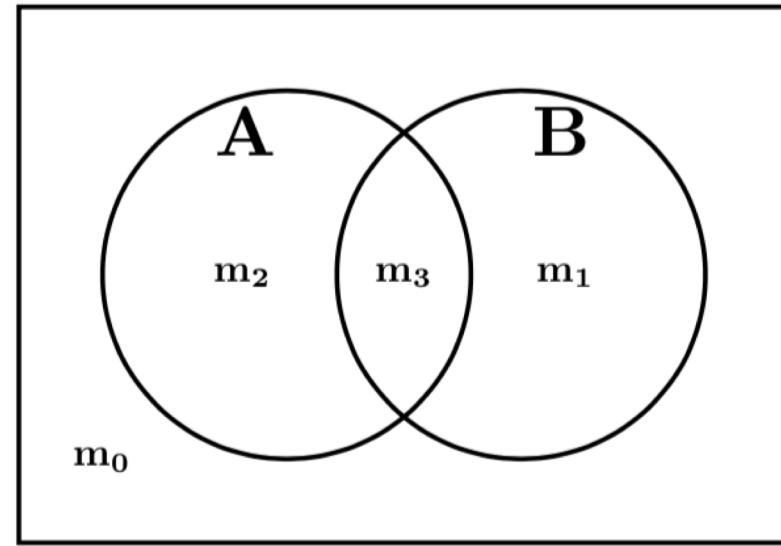


Color the Venn diagram for XOR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

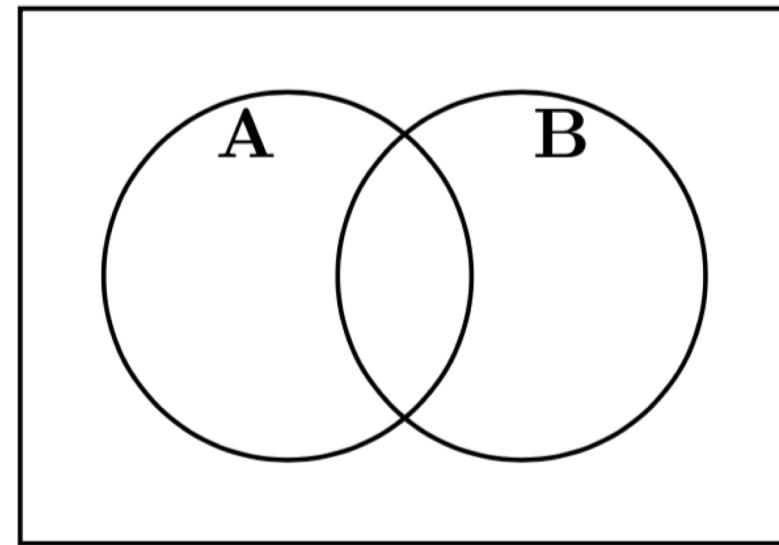


Color the Venn diagram for XOR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

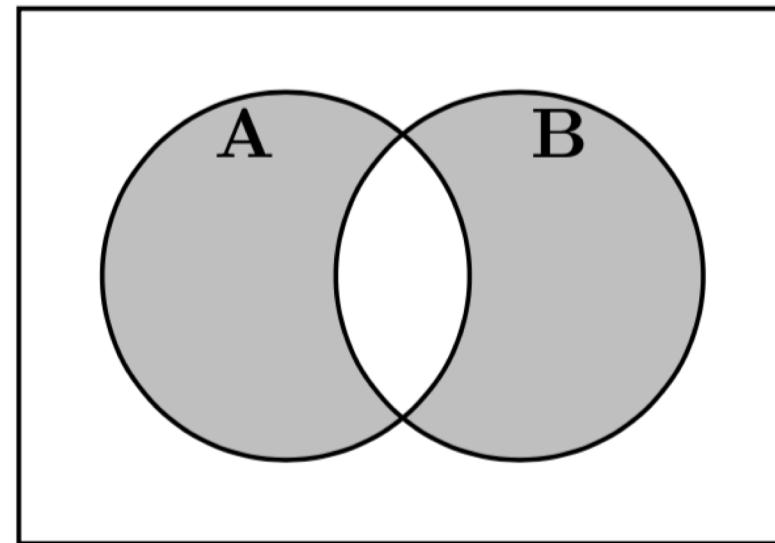

Color the Venn diagram for XOR


	A	B	F
m ₀	0	0	0
m ₁	0	1	1
m ₂	1	0	1
m ₃	1	1	0

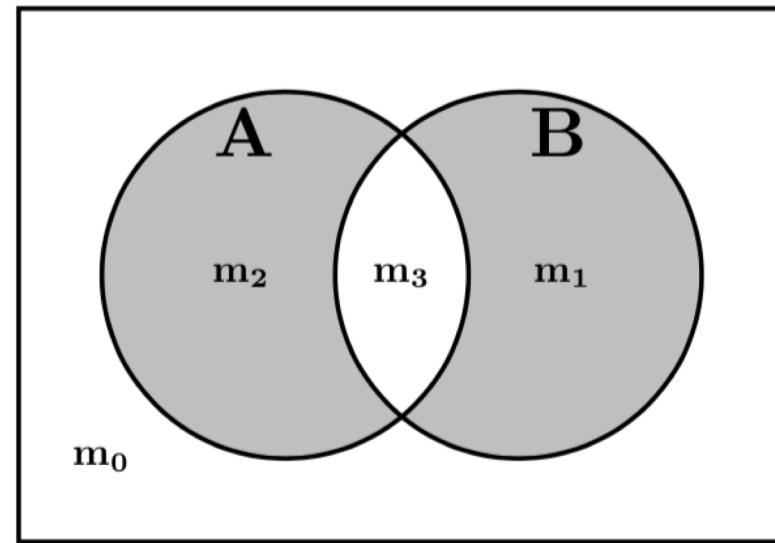

$$F = \overline{A}B + A\overline{B}$$


Place the minterms on the Venn diagram

A	B	C	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

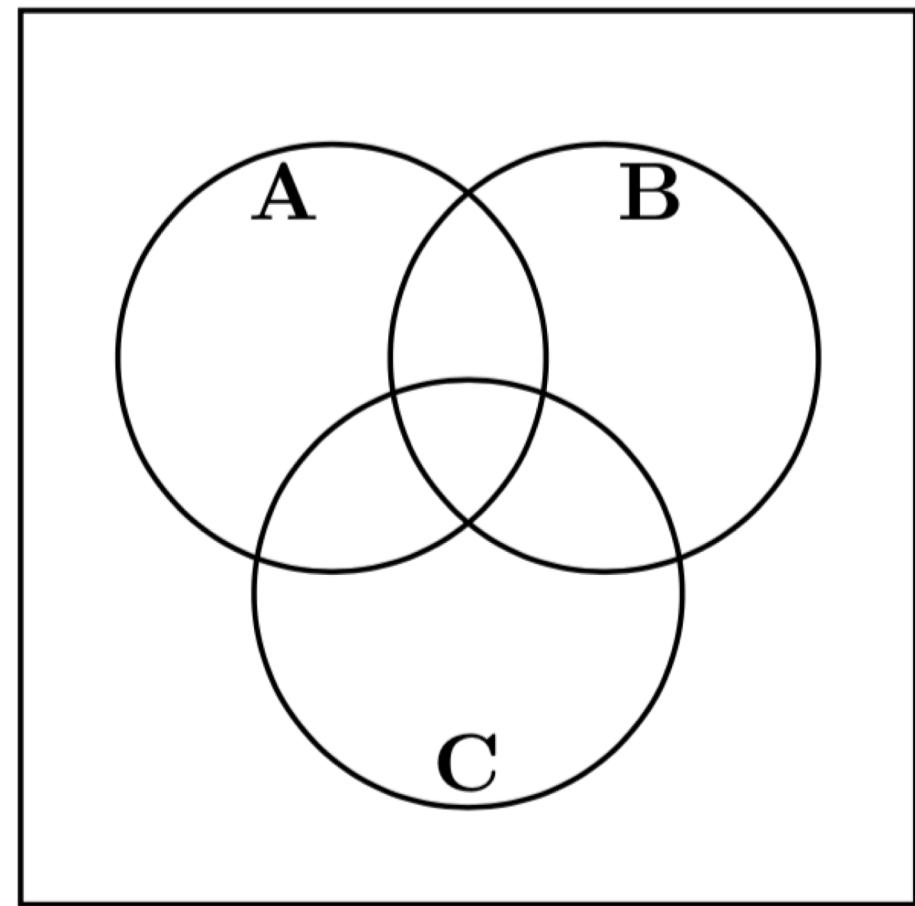


Place the minterms on the Venn diagram

A	B	C	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

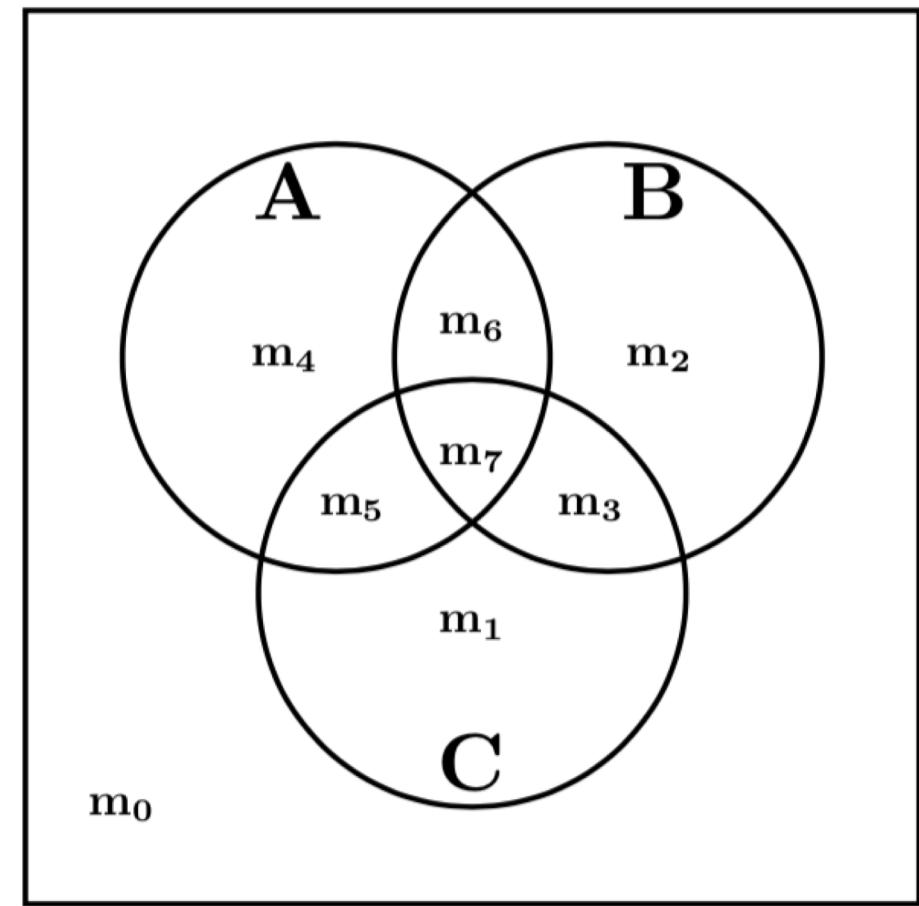


Color the Venn diagram for this function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

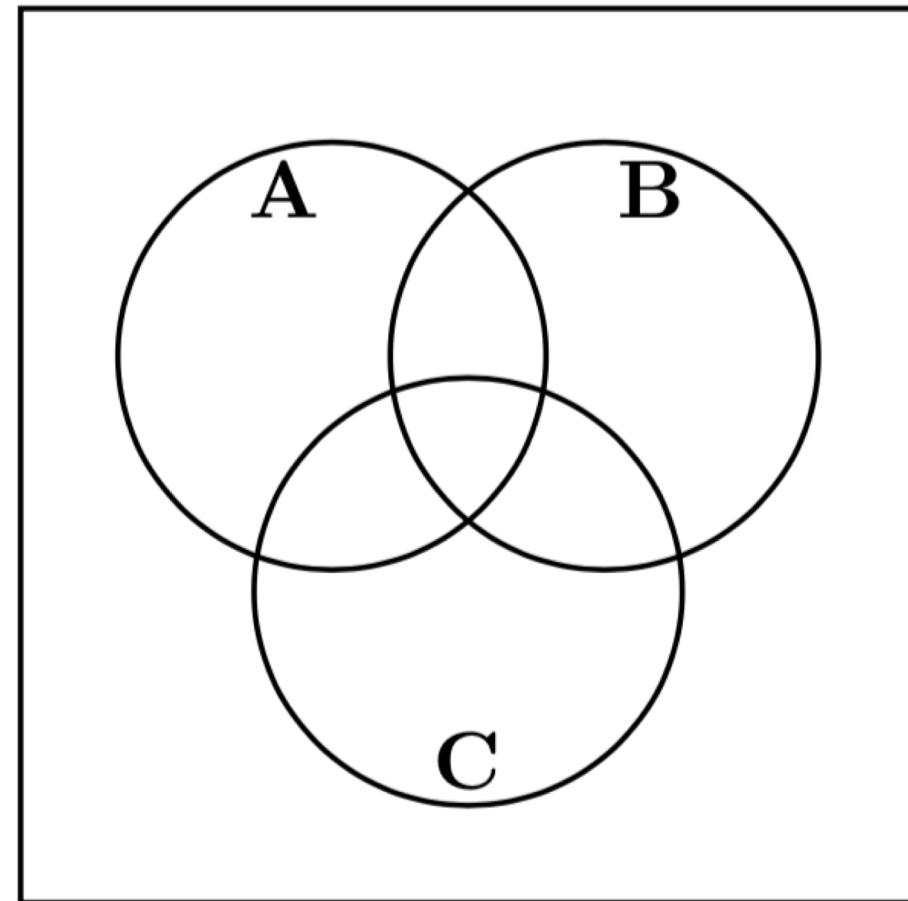


Color the Venn diagram for this function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

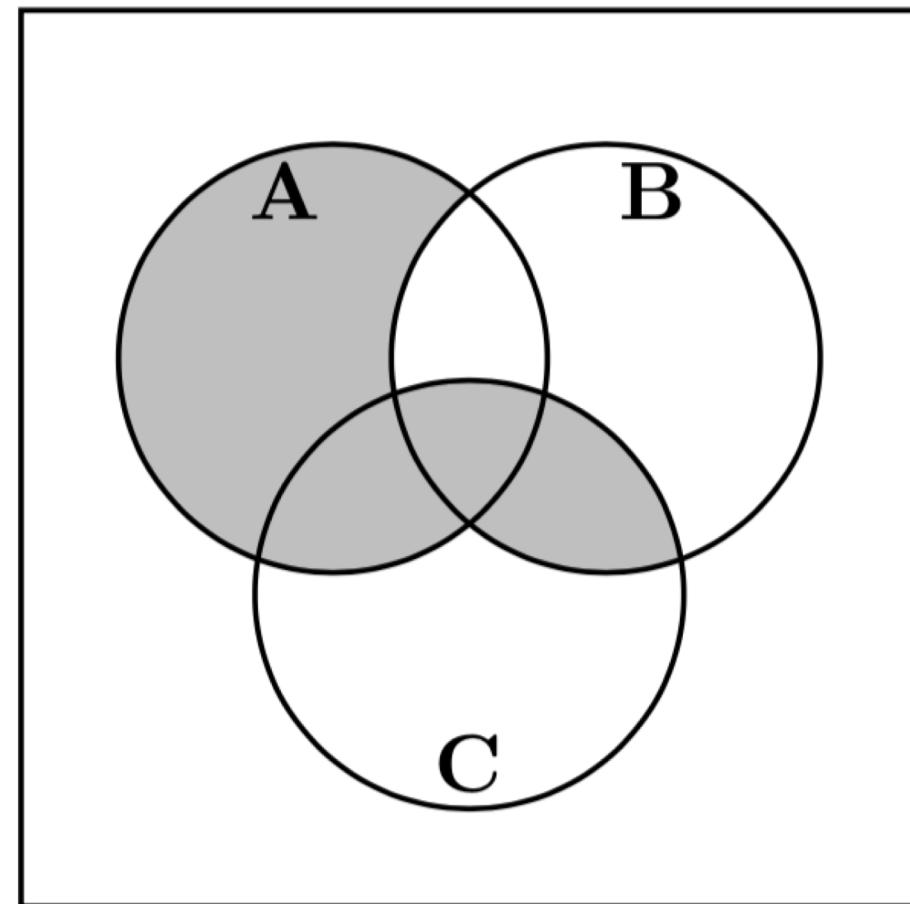


Place the minterms on the Venn diagram

	A	B	C	F
m ₀	0	0	0	0
m ₁	0	0	1	0
m ₂	0	1	0	0
m ₃	0	1	1	1
m ₄	1	0	0	1
m ₅	1	0	1	1
m ₆	1	1	0	0
m ₇	1	1	1	1

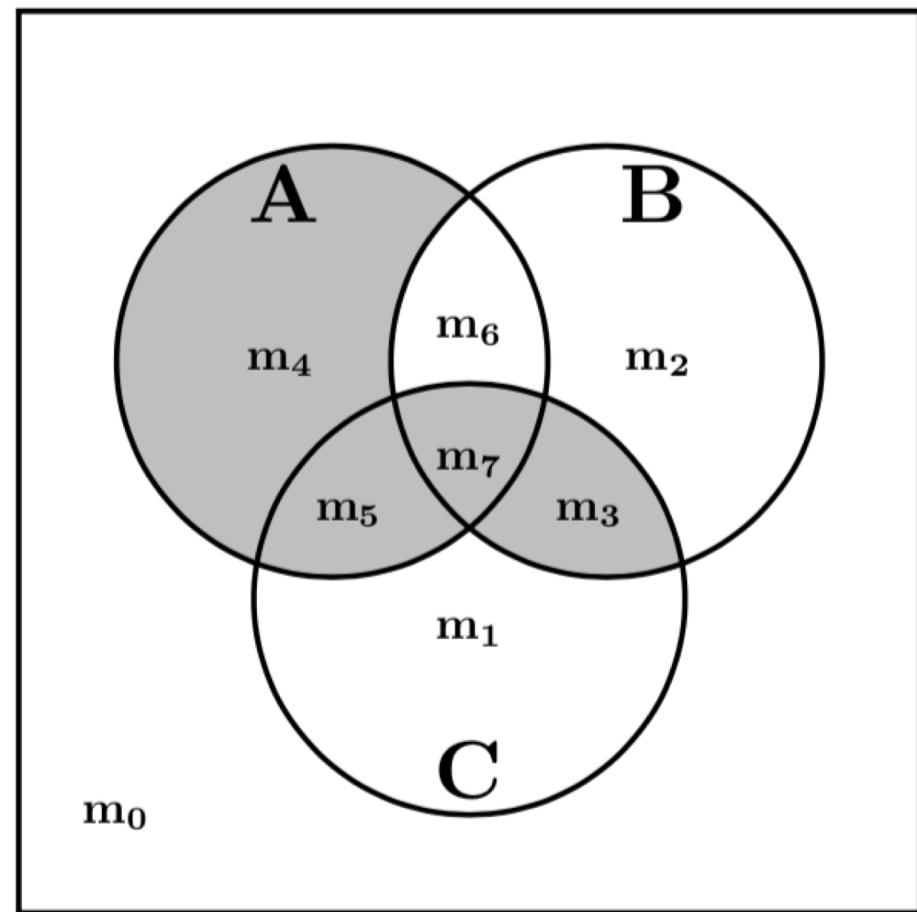


Color the Venn diagram for this function

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

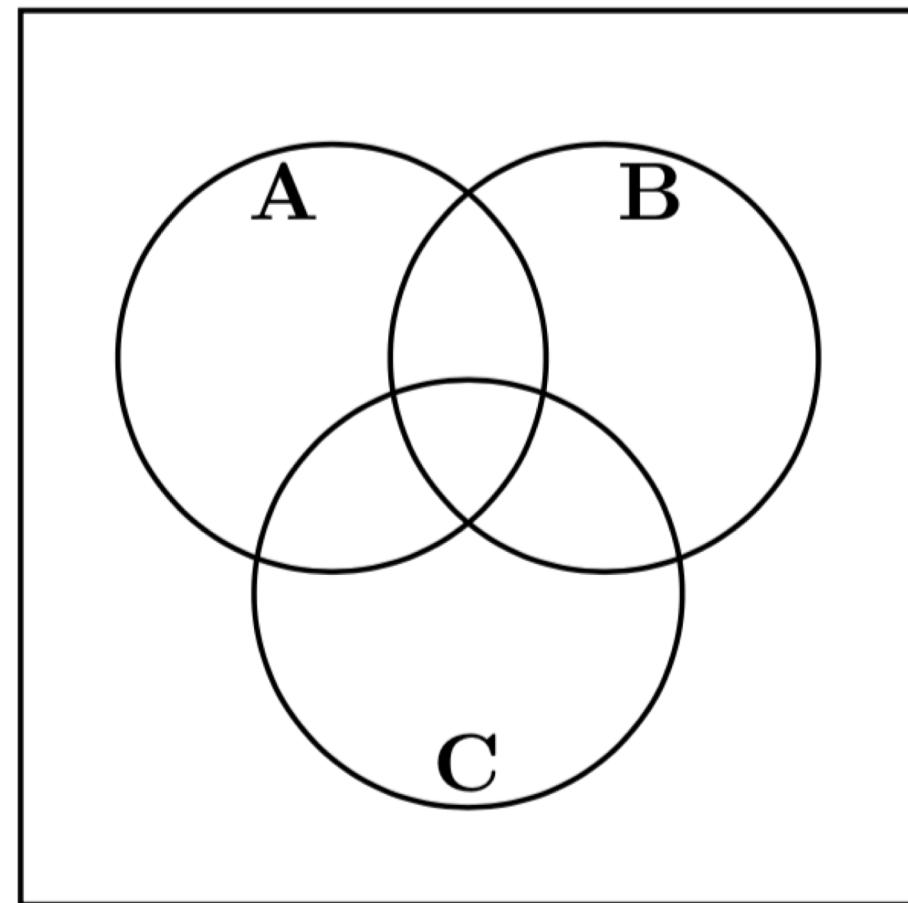


Color the Venn diagram for this function

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

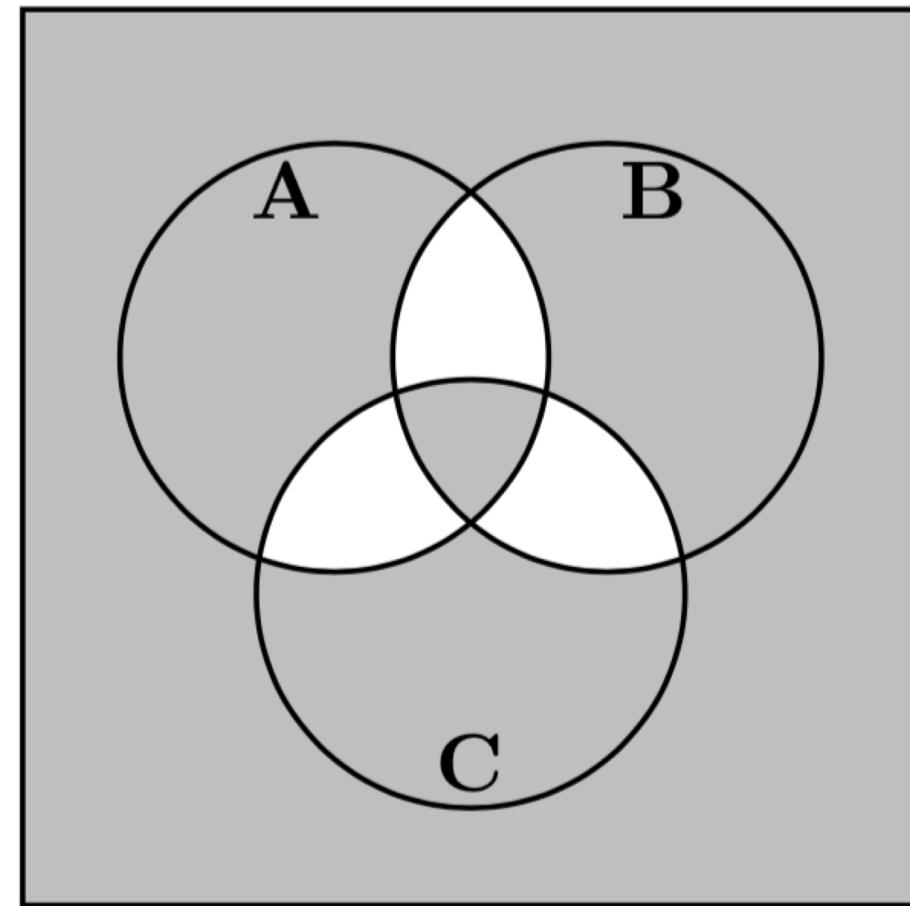


Place the minterms on the Venn diagram


	A	B	C	F
m_0	0	0	0	1
m_1	0	0	1	1
m_2	0	1	0	1
m_3	0	1	1	0
m_4	1	0	0	1
m_5	1	0	1	0
m_6	1	1	0	0
m_7	1	1	1	1

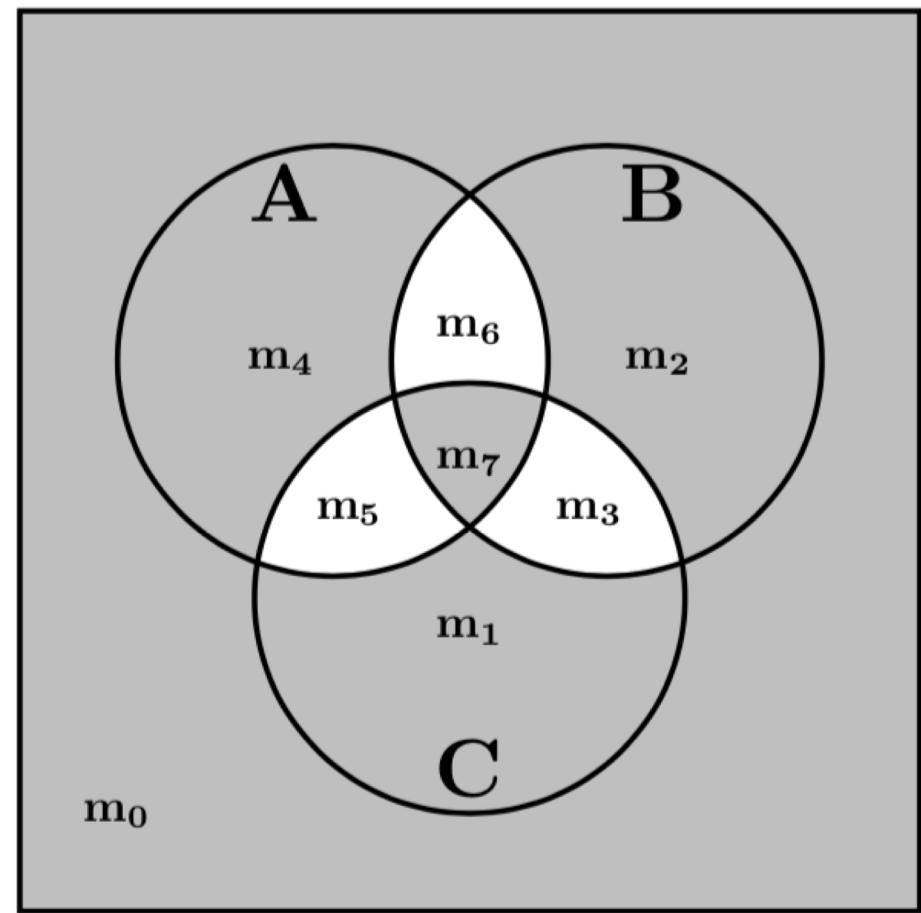

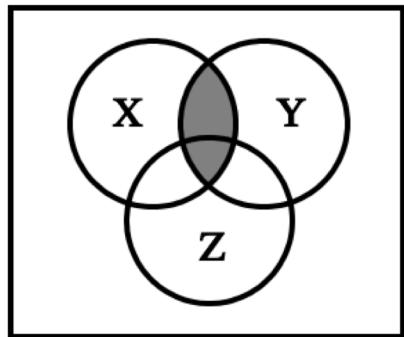
Write the expression that is represented by each of the three Venn diagrams:



(A)

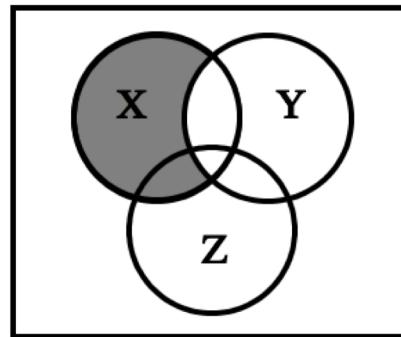


(B)

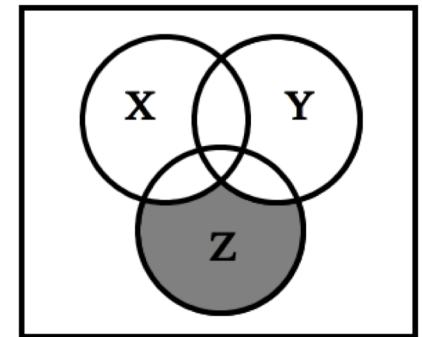


(C)

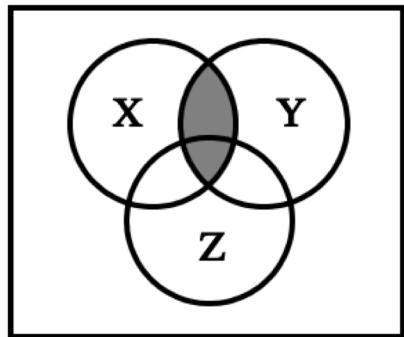
Write the expression that is represented by each of the three Venn diagrams:



(A)

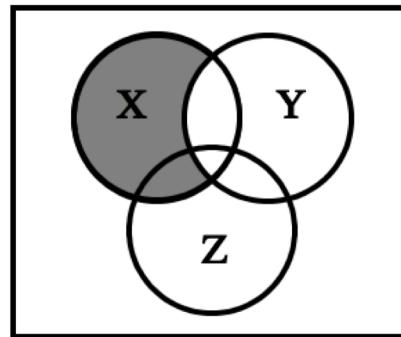

(B)

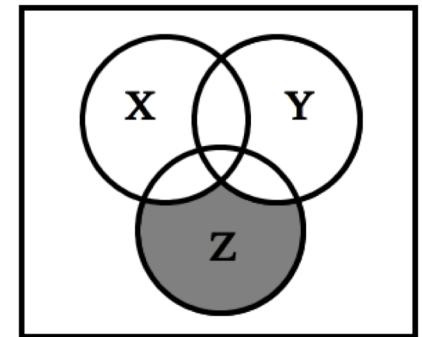

(C)

$$XY$$

$$\bar{X}\bar{Y}$$

$$\overline{\bar{X}\bar{Y}Z}$$

Example 1

Determine if the following equation is valid

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 = \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 = \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\overline{x_1} \overline{x_3}$	$x_2 \overline{x_3}$	$\overline{x_1} \overline{x_2}$	f
0	0	0	0				
1	0	0	1				
2	0	1	0				
3	0	1	1				
4	1	0	0				
5	1	0	1				
6	1	1	0				
7	1	1	1				

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_3$	$\bar{x}_2 \bar{x}_3$	$\bar{x}_1 \bar{x}_2$	f
0	0	0	0	1	0	0	
1	0	0	1	0	0	0	
2	0	1	0	1	0	0	
3	0	1	1	0	1	0	
4	1	0	0	0	0	1	
5	1	0	1	0	0	1	
6	1	1	0	0	0	0	
7	1	1	1	0	1	0	

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_3$	$x_2 \bar{x}_3$	$\bar{x}_1 \bar{x}_2$	f
0	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	0	1	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	0	1	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_2$	$x_1 x_3$	$\bar{x}_2 \bar{x}_3$	f
0	0	0	0				
1	0	0	1				
2	0	1	0				
3	0	1	1				
4	1	0	0				
5	1	0	1				
6	1	1	0				
7	1	1	1				

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_2$	$x_1 x_3$	$\bar{x}_2 \bar{x}_3$	f
0	0	0	0	0	0	1	
1	0	0	1	0	0	0	
2	0	1	0	1	0	0	
3	0	1	1	1	0	0	
4	1	0	0	0	0	1	
5	1	0	1	0	1	0	
6	1	1	0	0	0	0	
7	1	1	1	0	1	0	

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_2$	$x_1 x_3$	$\bar{x}_2 \bar{x}_3$	f
0	0	0	0	0	0	1	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	1	0	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	1	0	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 = \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

?



LHS RHS

$$\frac{f}{\rule{0pt}{1.5ex}}$$

1

0

1

1

1

1

0

1

$$\frac{f}{\rule{0pt}{1.5ex}}$$

1

0

1

1

1

1

0

1

They are equal.

Example 2

Design the minimum-cost product-of-sums expression for the function

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

[Figure 2.22 from the textbook]

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

The function is
1 for these rows

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

The function is
1 for these rows

The function is
0 for these rows

Two different ways to specify the same function f of three variables

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

$$f(x_1, x_2, x_3) = \prod M(1, 3)$$

Two different ways to specify the same function f of three variables

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

$$f(x_1, x_2, x_3) = \prod M(1, 3)$$

$$= M_1 \bullet M_3$$

$$= (x_1 + x_2 + \bar{x}_3) \bullet (x_1 + \bar{x}_2 + \bar{x}_3)$$

The Minimum POS Expression

$$\begin{aligned}f(x_1, x_2, x_3) &= (x_1 + x_2 + \overline{x}_3) \bullet (x_1 + \overline{x}_2 + \overline{x}_3) \\&= (x_1 + \overline{x}_3 + x_2) \bullet (x_1 + \overline{x}_3 + \overline{x}_2) \\&= (x_1 + \overline{x}_3)\end{aligned}$$


Hint: Use the following Boolean Algebra theorem

14b. $(x + y) \bullet (x + \overline{y}) = x$

Alternative Solution Using K-Maps

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

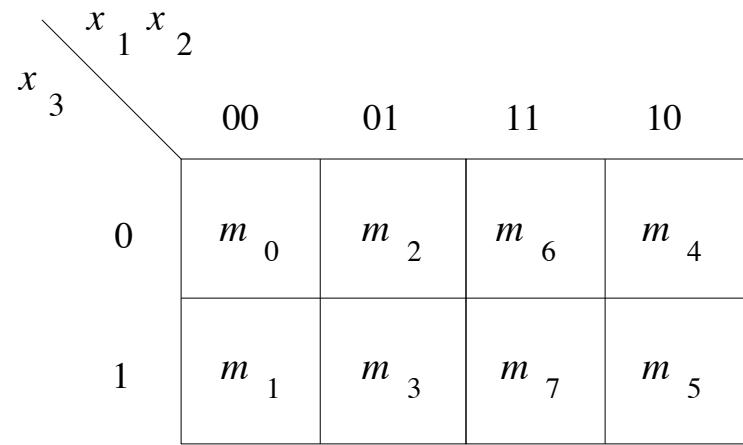


(b) Karnaugh map

Alternative Solution Using K-Maps

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

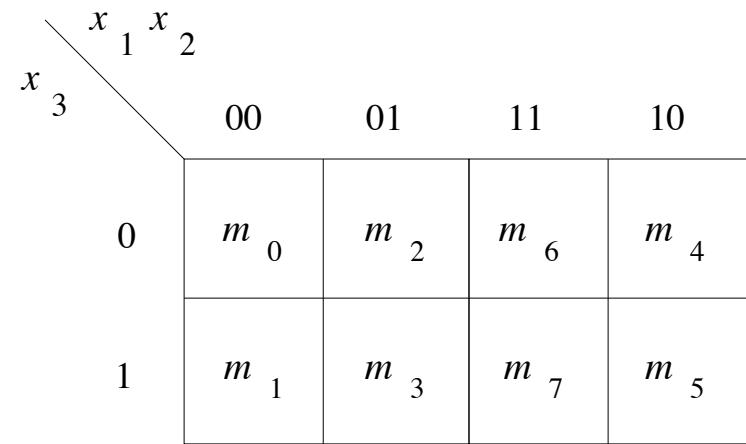


(b) Karnaugh map

Alternative Solution Using K-Maps


x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

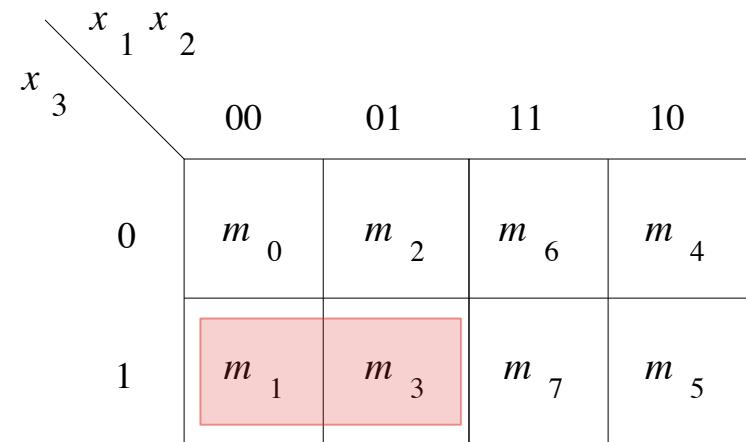


(b) Karnaugh map

Alternative Solution Using K-Maps

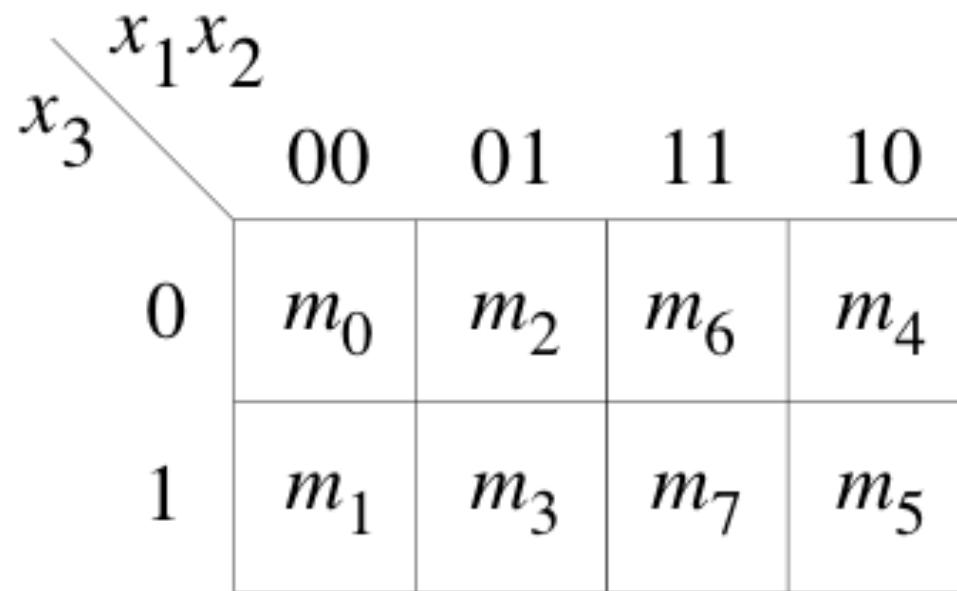


Alternative Solution Using K-Maps

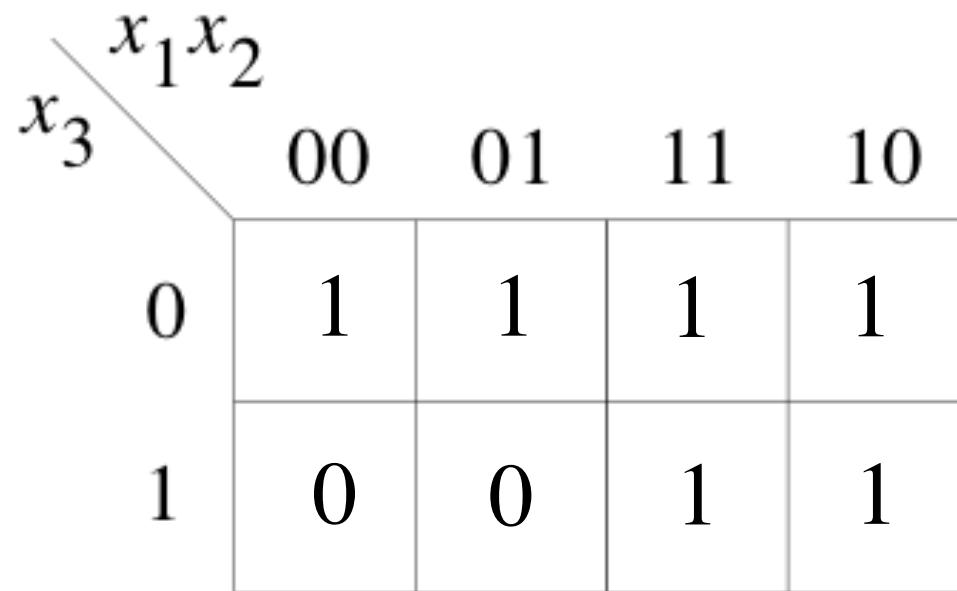

		x_1x_2	00	01	11	10
		x_3	00	01	11	10
x_3	0	1	1	1	1	
	1	0	0	1	1	

Alternative Solution Using K-Maps

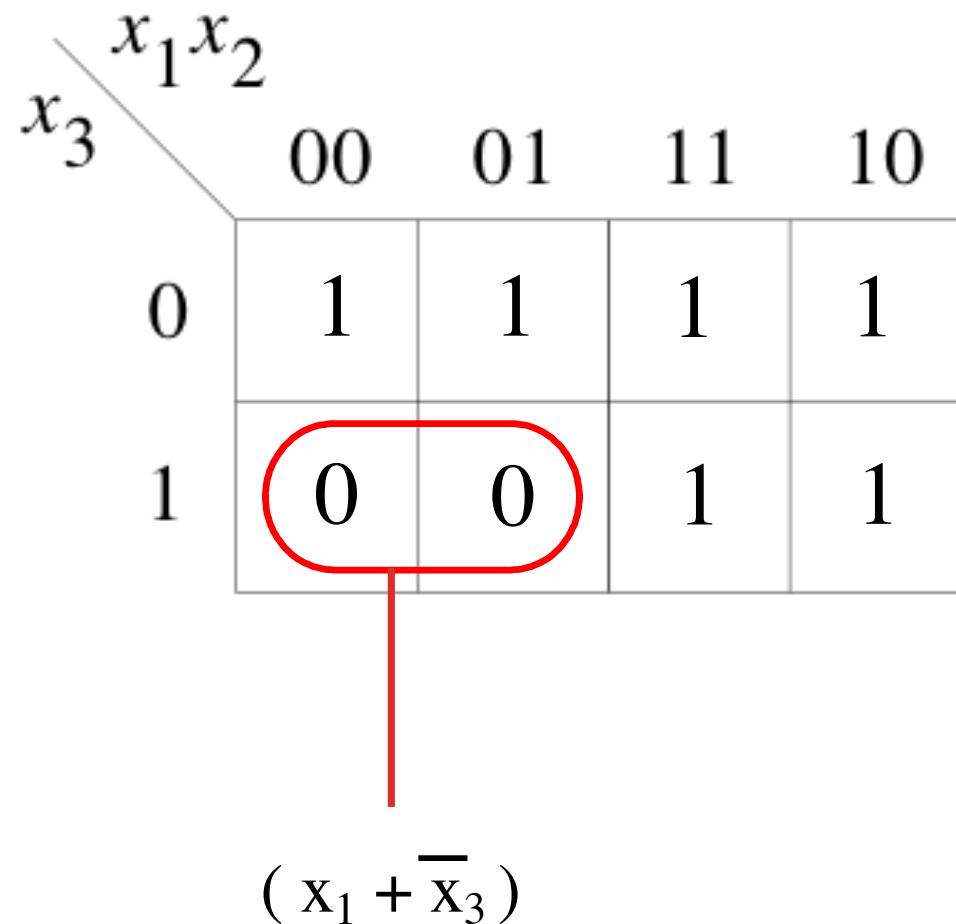

Example 3

Problem: A circuit that controls a given digital system has three inputs: x_1 , x_2 , and x_3 . It has to recognize three different conditions:

- Condition *A* is true if x_3 is true and either x_1 is true or x_2 is false
- Condition *B* is true if x_1 is true and either x_2 or x_3 is false
- Condition *C* is true if x_2 is true and either x_1 is true or x_3 is false

The control circuit must produce an output of 1 if at least two of the conditions *A*, *B*, and *C* are true. Design the simplest circuit that can be used for this purpose.

Condition A

Condition *A* is true if x_3 is true and either x_1 is true or x_2 is false

Condition A

Condition A is true if x_3 is true and either x_1 is true or x_2 is false

$$A = x_3(x_1 + \bar{x}_2) = x_3x_1 + x_3\bar{x}_2$$

Condition B

Condition *B* is true if x_1 is true and either x_2 or x_3 is false

Condition B

Condition B is true if x_1 is true and either x_2 or x_3 is false

$$B = x_1(\bar{x}_2 + \bar{x}_3) = x_1\bar{x}_2 + x_1\bar{x}_3$$

Condition C

Condition C is true if x_2 is true and either x_1 is true or x_3 is false

Condition C

Condition C is true if x_2 is true and either x_1 is true or x_3 is false

$$C = x_2(x_1 + \bar{x}_3) = x_2x_1 + x_2\bar{x}_3$$

The output of the circuit can be expressed as

$$f = \boxed{AB} + AC + BC$$

$$AB = (x_3x_1 + x_3\bar{x}_2)(x_1\bar{x}_2 + x_1\bar{x}_3)$$

$$= x_3x_1x_1\bar{x}_2 + x_3x_1x_1\bar{x}_3 + x_3\bar{x}_2x_1\bar{x}_2 + x_3\bar{x}_2x_1\bar{x}_3$$

$$= x_3x_1\bar{x}_2 + 0 + x_3\bar{x}_2x_1 + 0$$

$$= x_1\bar{x}_2x_3$$

The output of the circuit can be expressed as

$$f = AB + \boxed{AC} + BC$$

$$\begin{aligned} AC &= (x_3x_1 + x_3\bar{x}_2)(x_2x_1 + x_2\bar{x}_3) \\ &= x_3x_1x_2x_1 + x_3x_1x_2\bar{x}_3 + x_3\bar{x}_2x_2x_1 + x_3\bar{x}_2x_2\bar{x}_3 \\ &= x_3x_1x_2 + 0 + 0 + 0 \\ &= x_1x_2x_3 \end{aligned}$$

The output of the circuit can be expressed as

$$f = AB + AC + BC$$

$$BC = (x_1\bar{x}_2 + x_1\bar{x}_3)(x_2x_1 + x_2\bar{x}_3)$$

$$= x_1\bar{x}_2x_2x_1 + x_1\bar{x}_2x_2\bar{x}_3 + x_1\bar{x}_3x_2x_1 + x_1\bar{x}_3x_2\bar{x}_3$$

$$= 0 + 0 + x_1\bar{x}_3x_2 + x_1\bar{x}_3x_2$$

$$= x_1x_2\bar{x}_3$$

Finally, we get


$$\begin{aligned}f &= x_1\bar{x}_2x_3 + x_1x_2x_3 + x_1x_2\bar{x}_3 \\&= x_1(\bar{x}_2 + x_2)x_3 + x_1x_2(x_3 + \bar{x}_3) \\&= x_1x_3 + x_1x_2 \\&= x_1(x_3 + x_2)\end{aligned}$$

Example 4

Solve the previous problem using Venn diagrams.


Venn Diagrams

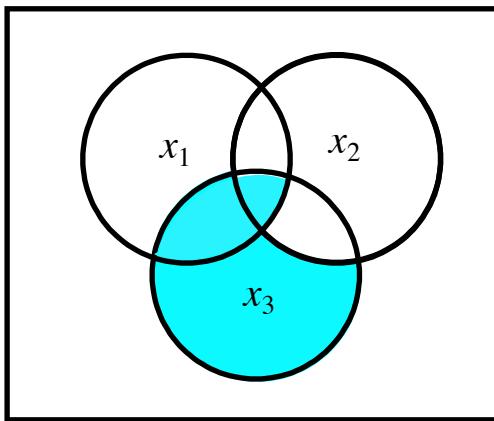(find the areas that are shaded at least two times)




(a) Function A :

$$x_3x_1 + x_3\bar{x}_2$$

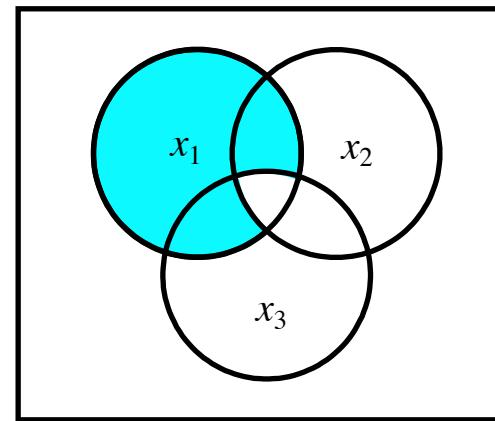


(b) Function B

$$x_1\bar{x}_2 + x_1\bar{x}_3$$

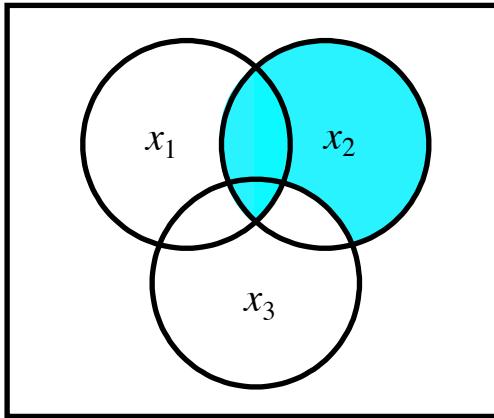

(c) Function C

$$x_2x_1 + x_2\bar{x}_3$$

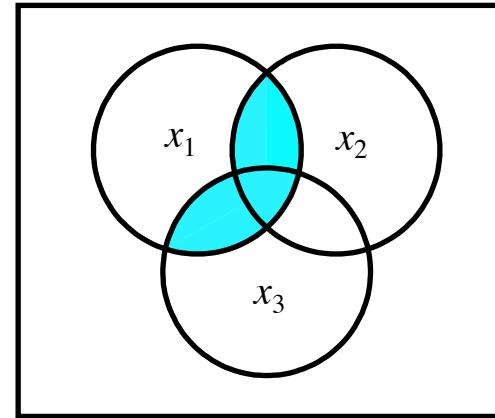

(d) Function f

$$x_1(x_3 + x_2)$$

[Figure 2.66 from the textbook]


Example 5

**Design the minimum-cost SOP and POS
expression for the function**

$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$


Let's Use a K-Map
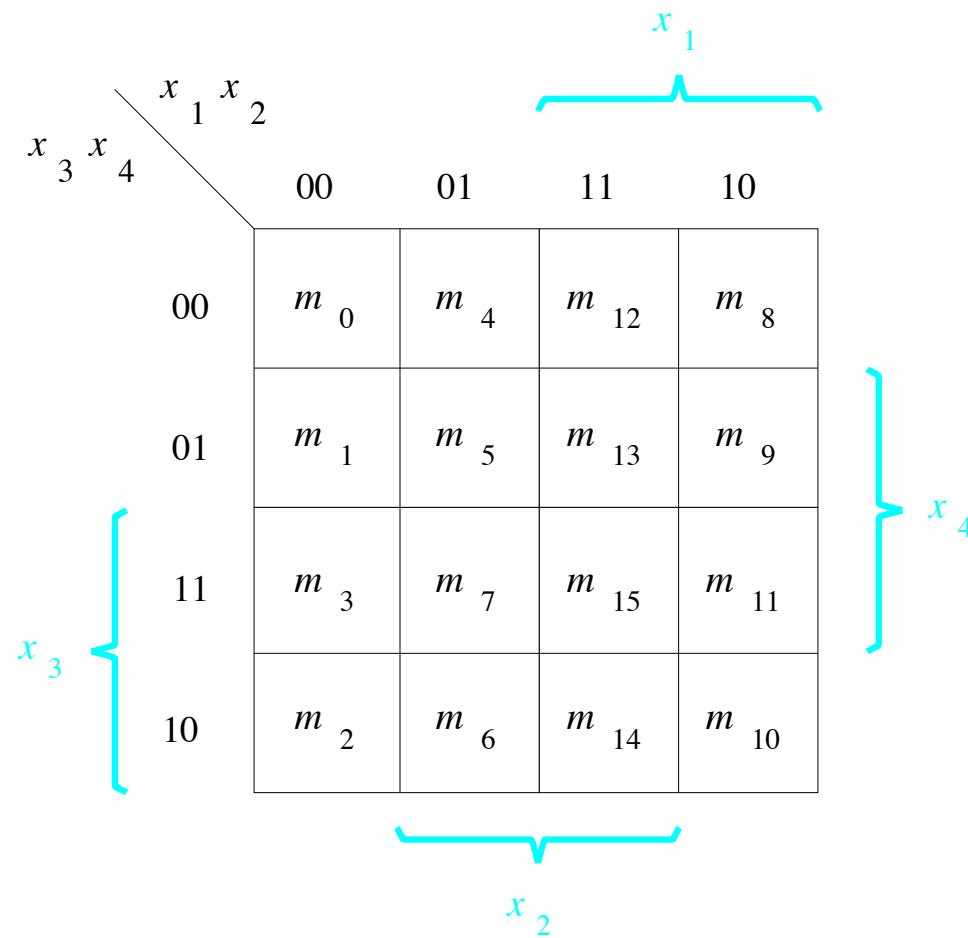
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




Let's Use a K-Map
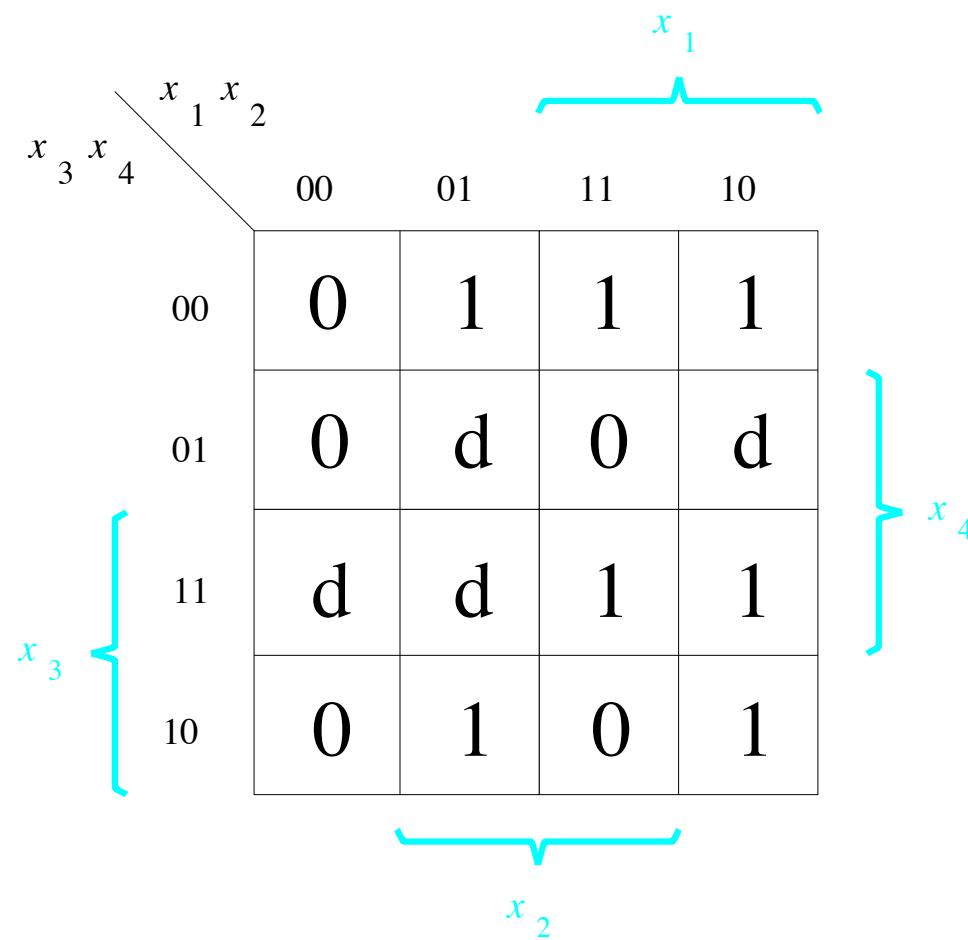
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




Let's Use a K-Map
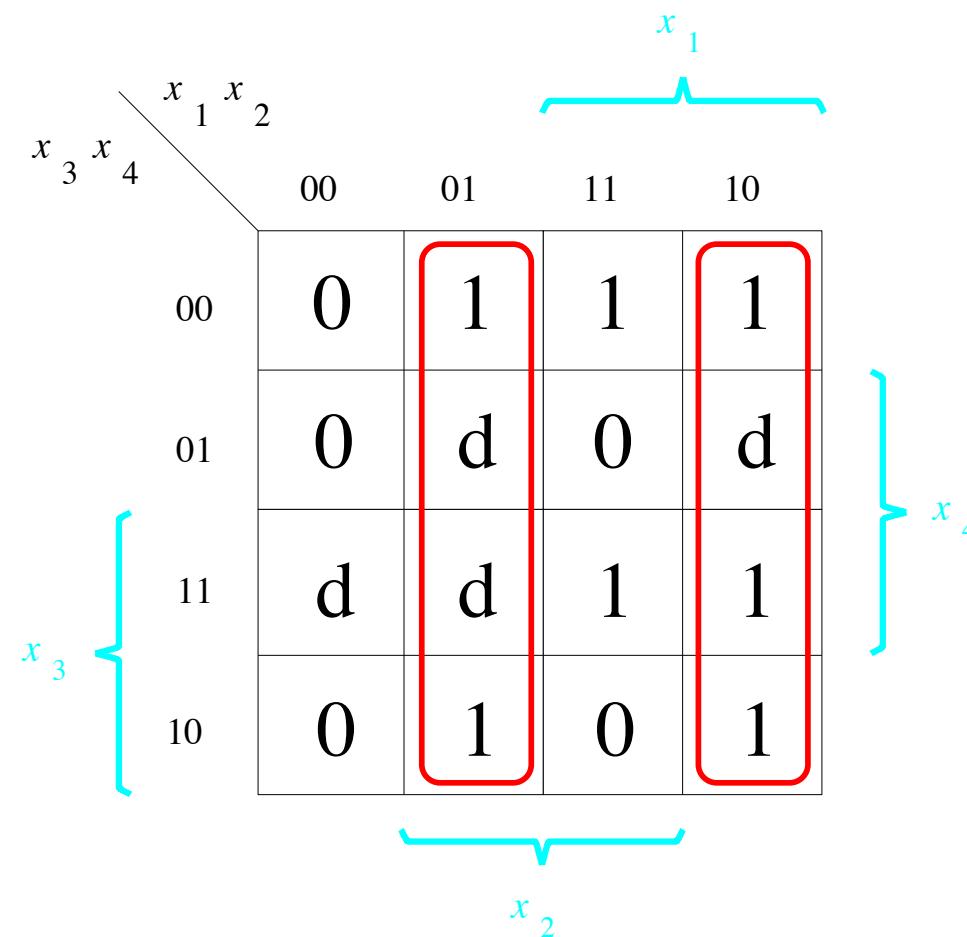
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




Let's Use a K-Map
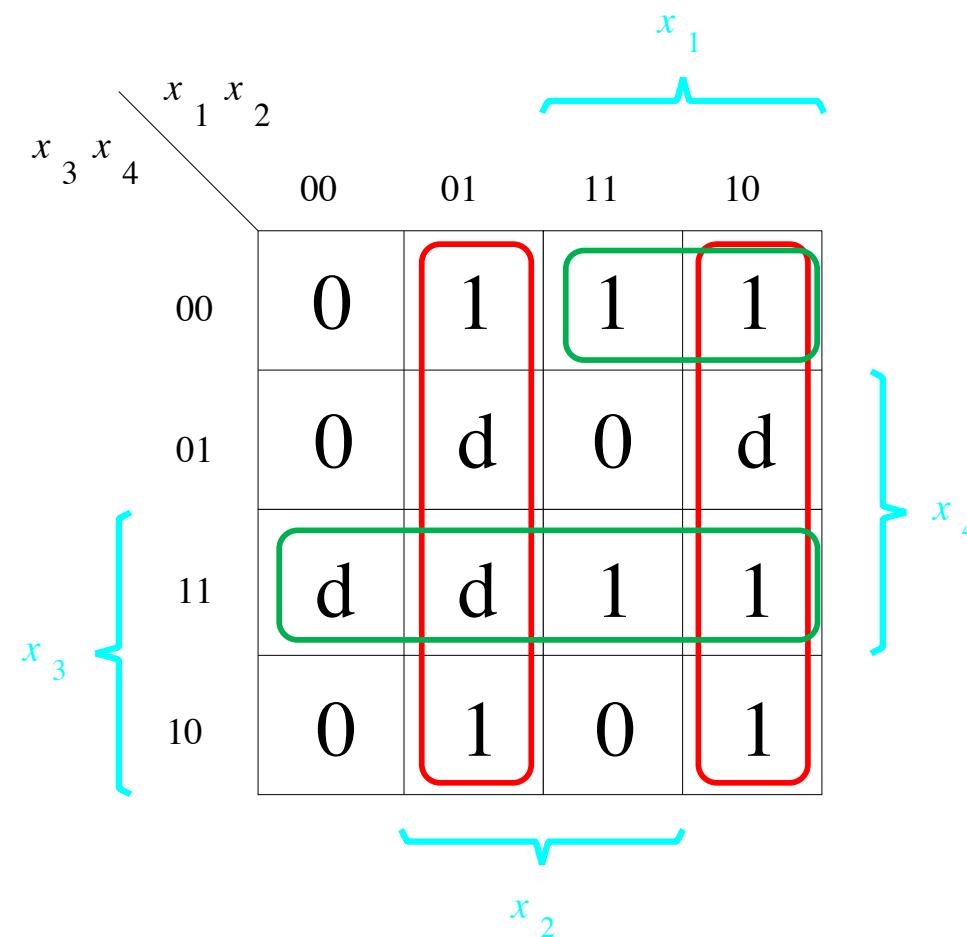
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$





Let's Use a K-Map
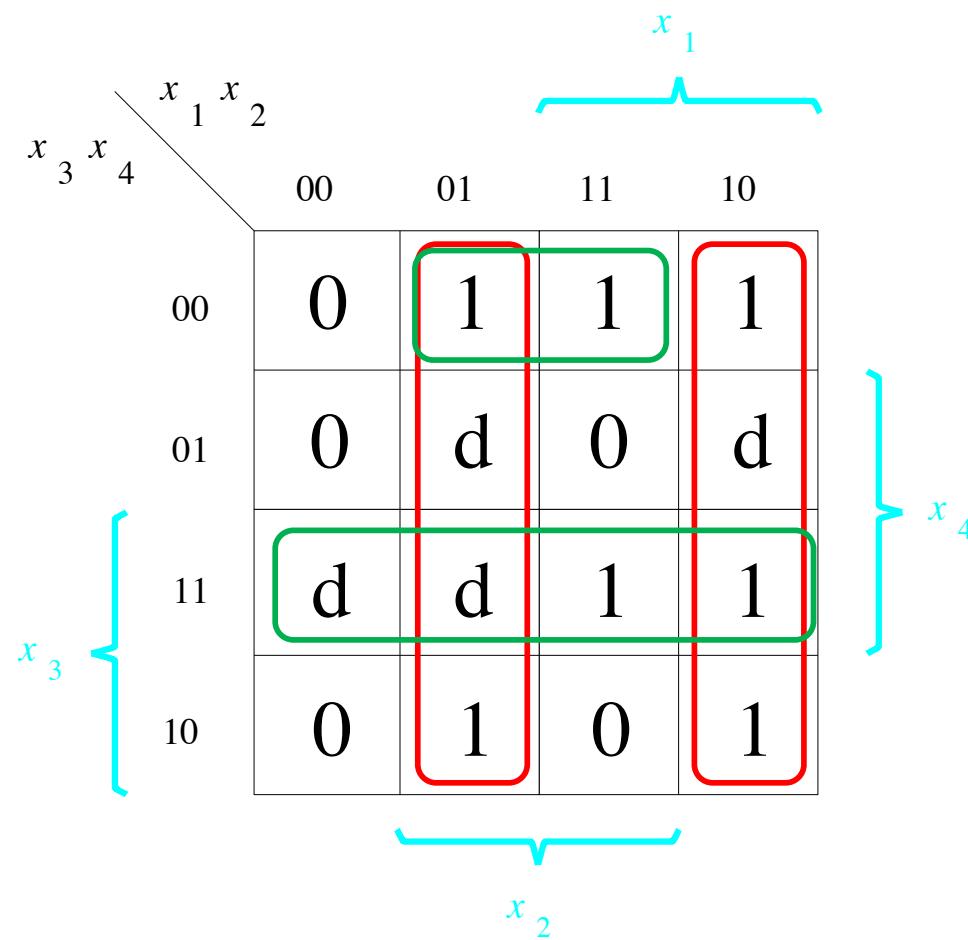
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




Two Alternative Solutions
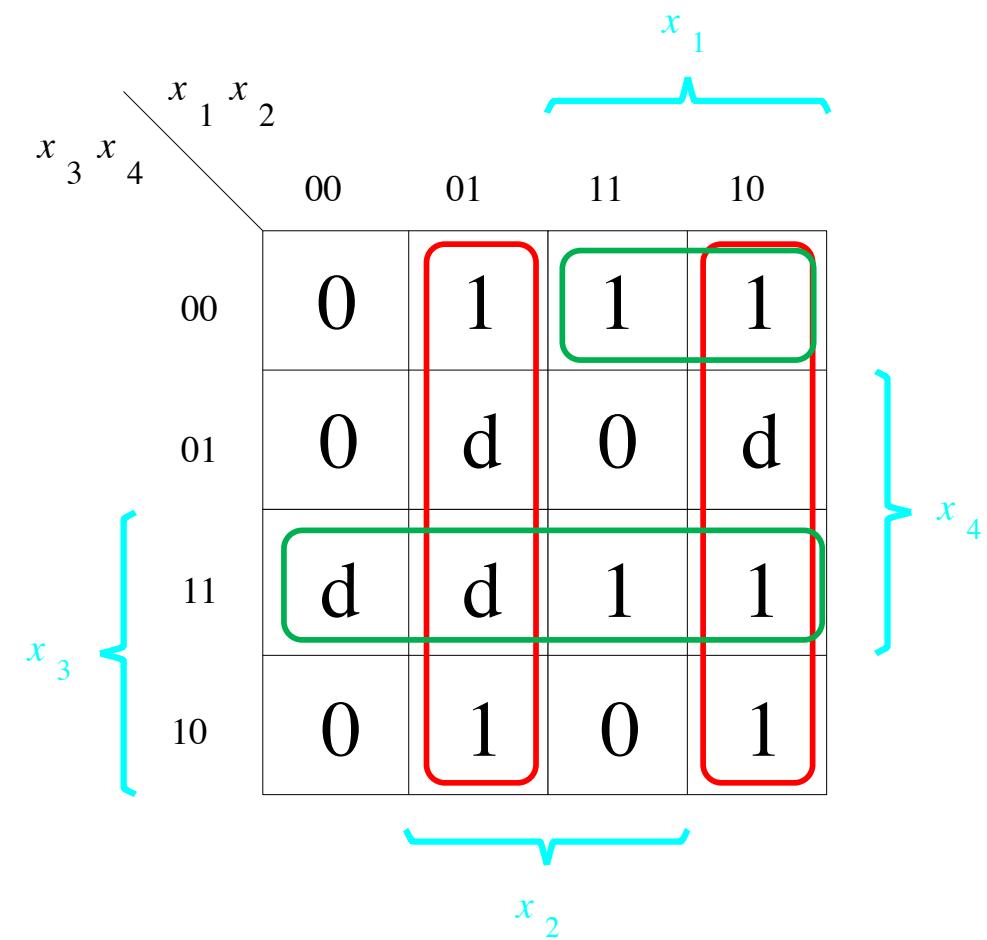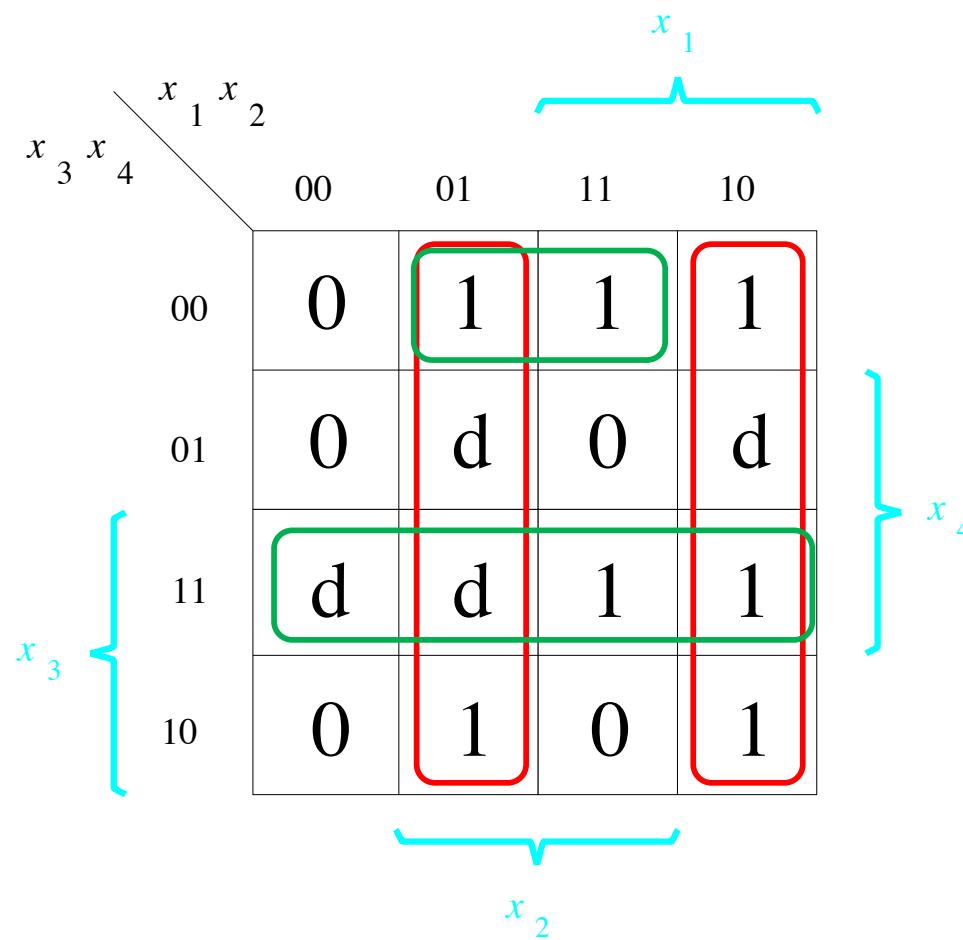
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$



The SOP Expression

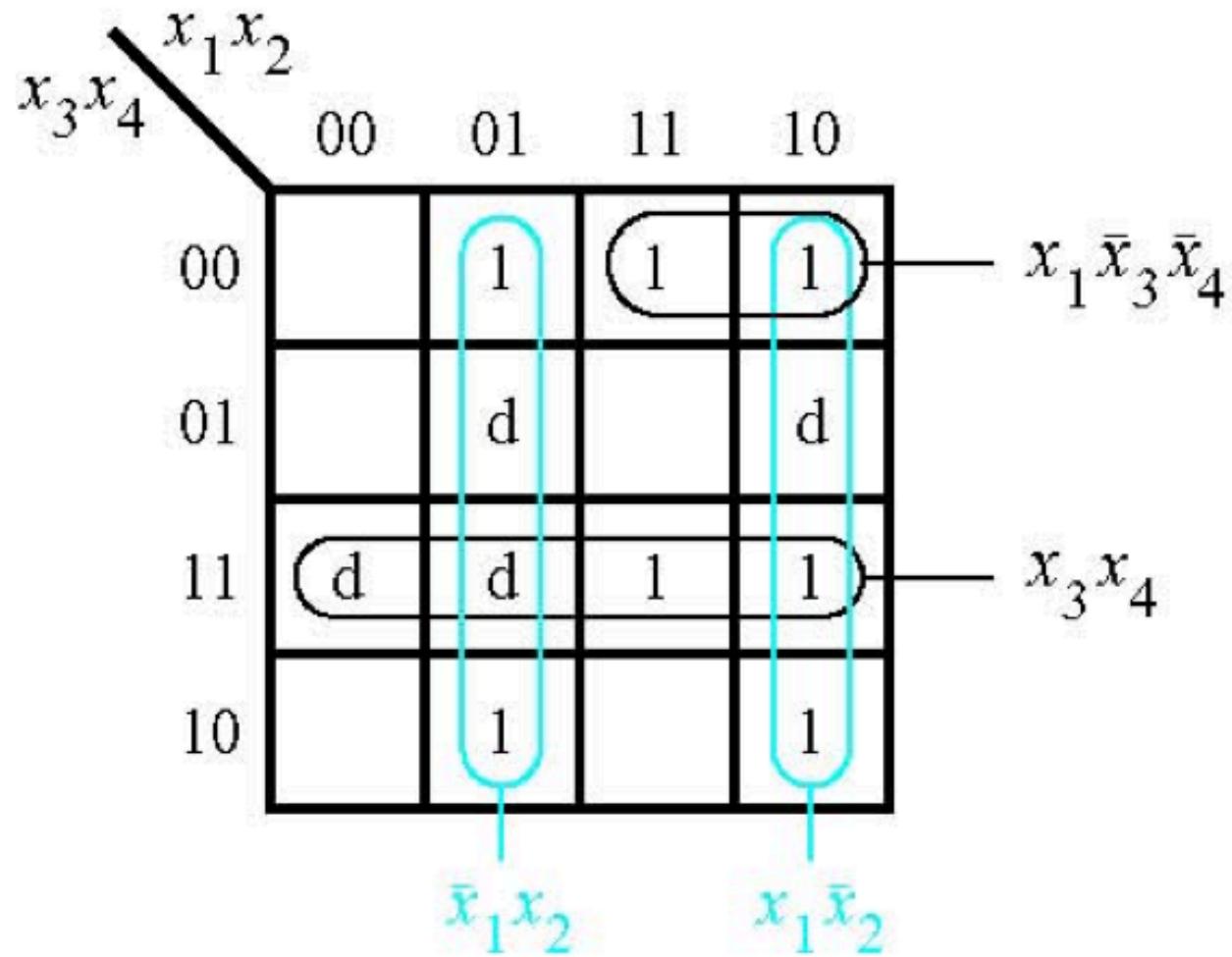


$$f = \overline{x_1} \ x_2 + x_1 \ \overline{x_2} + x_1 \ \overline{x_3} \ \overline{x_4} + x_3 \ x_4$$

[Figure 2.67a from the textbook]


What about the POS Expression?
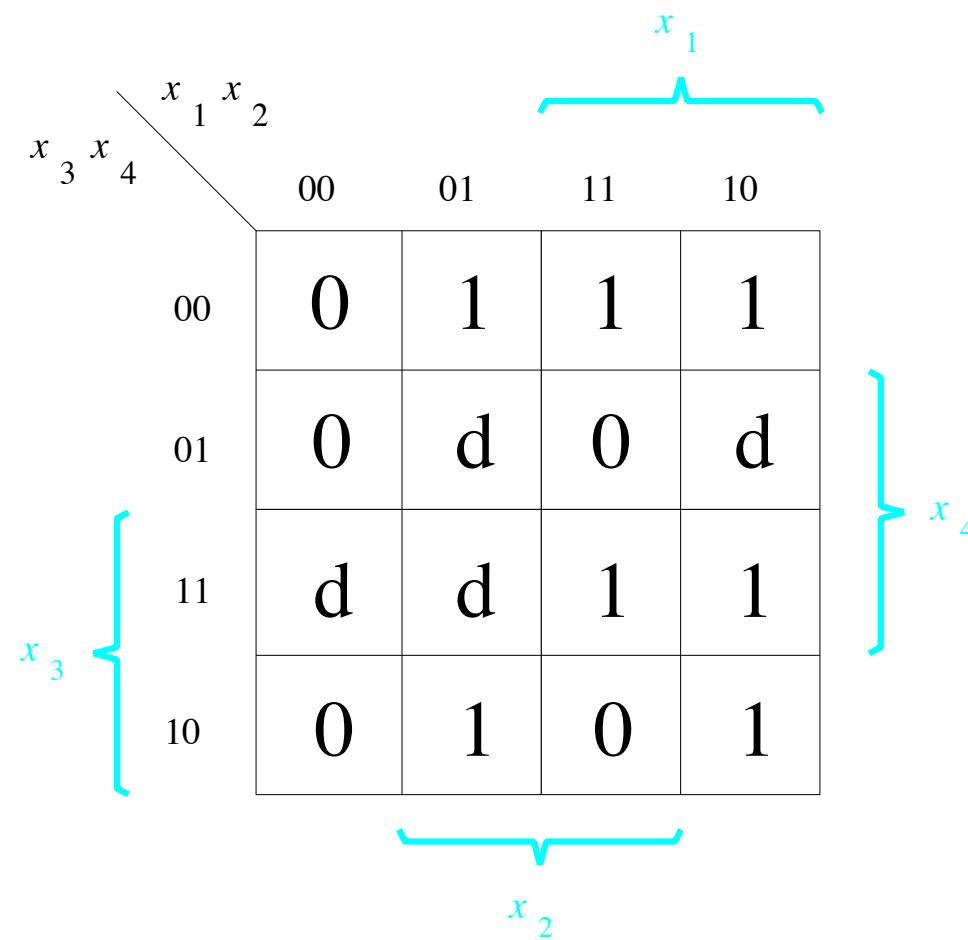
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




What about the POS Expression?
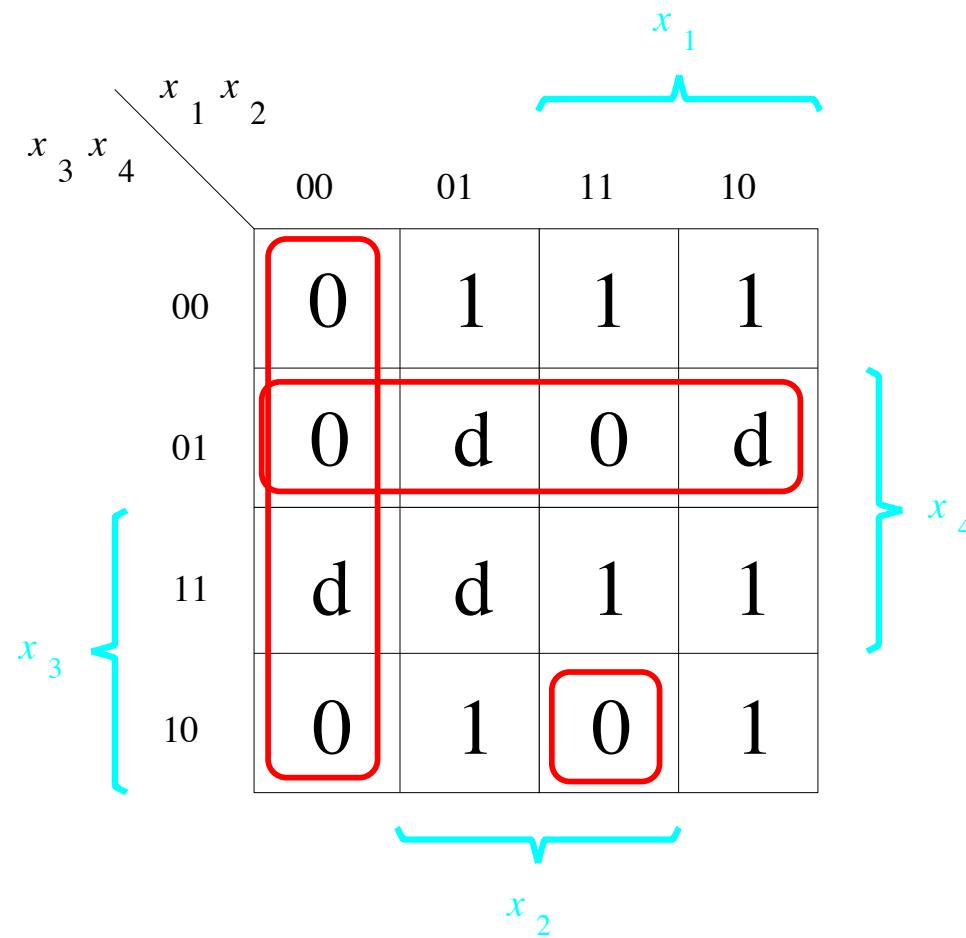
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$



The POS Expression

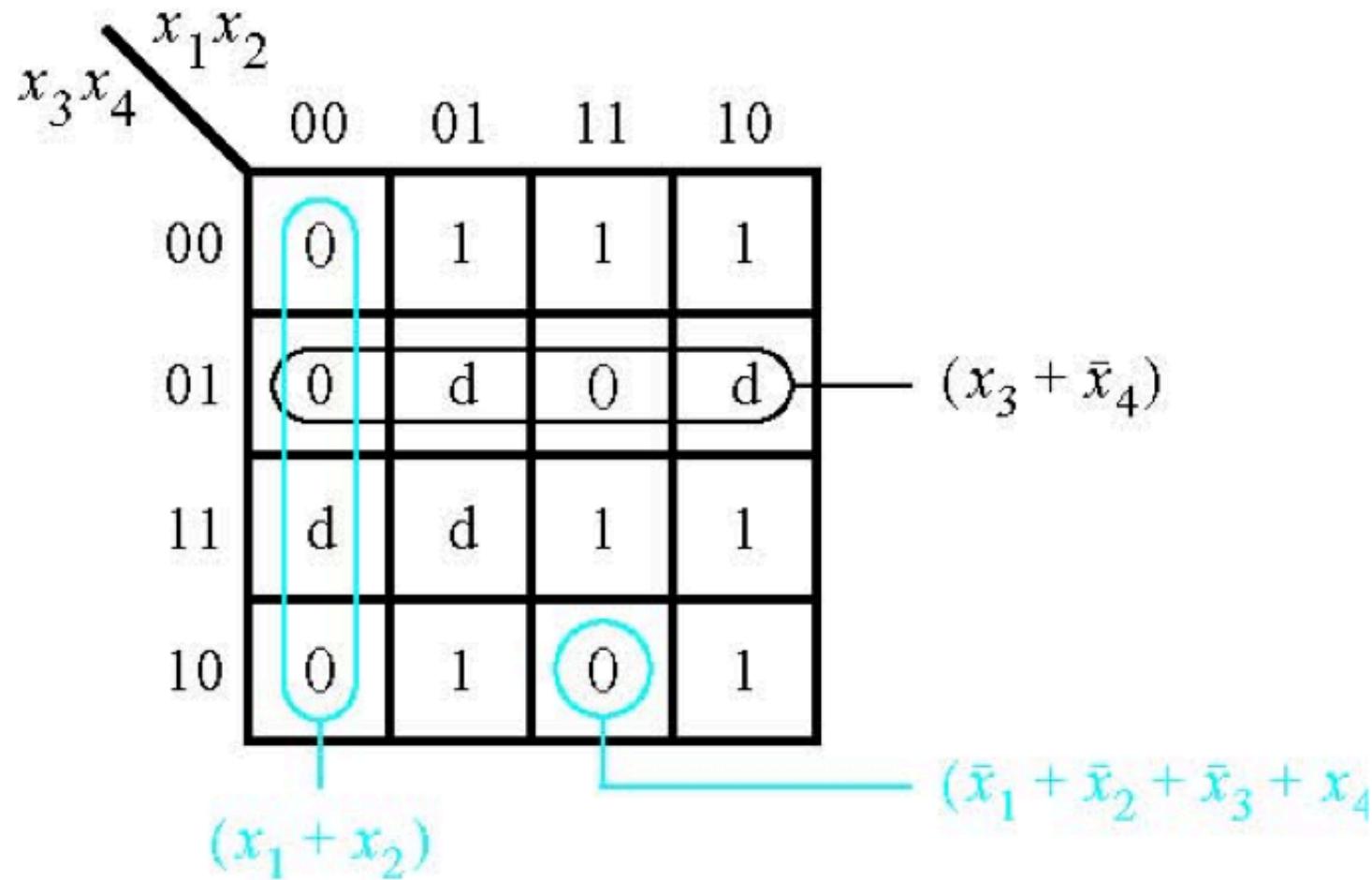

$$f = (x_1 + x_2) \bullet (x_3 + \bar{x}_4) \bullet (\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + x_4)$$

[Figure 2.67b from the textbook]

Example 6

Use K-maps to find the minimum-cost SOP and POS expression for the function


$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$

assuming that there are also don't-cares defined as $D = \sum(9, 12, 14)$.

Let's map the expression to the K-Map

$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$


$$D = \sum(9, 12, 14).$$

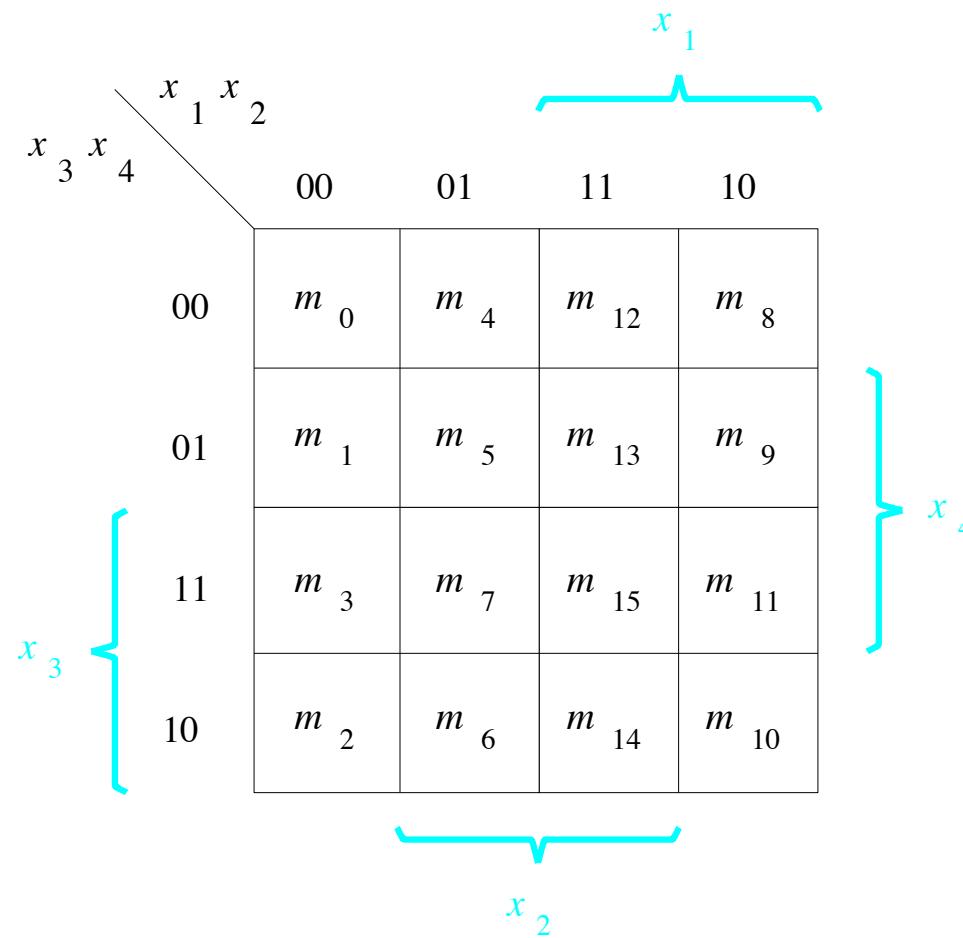

Let's map the expression to the K-Map


$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$

$$D = \sum(9, 12, 14).$$

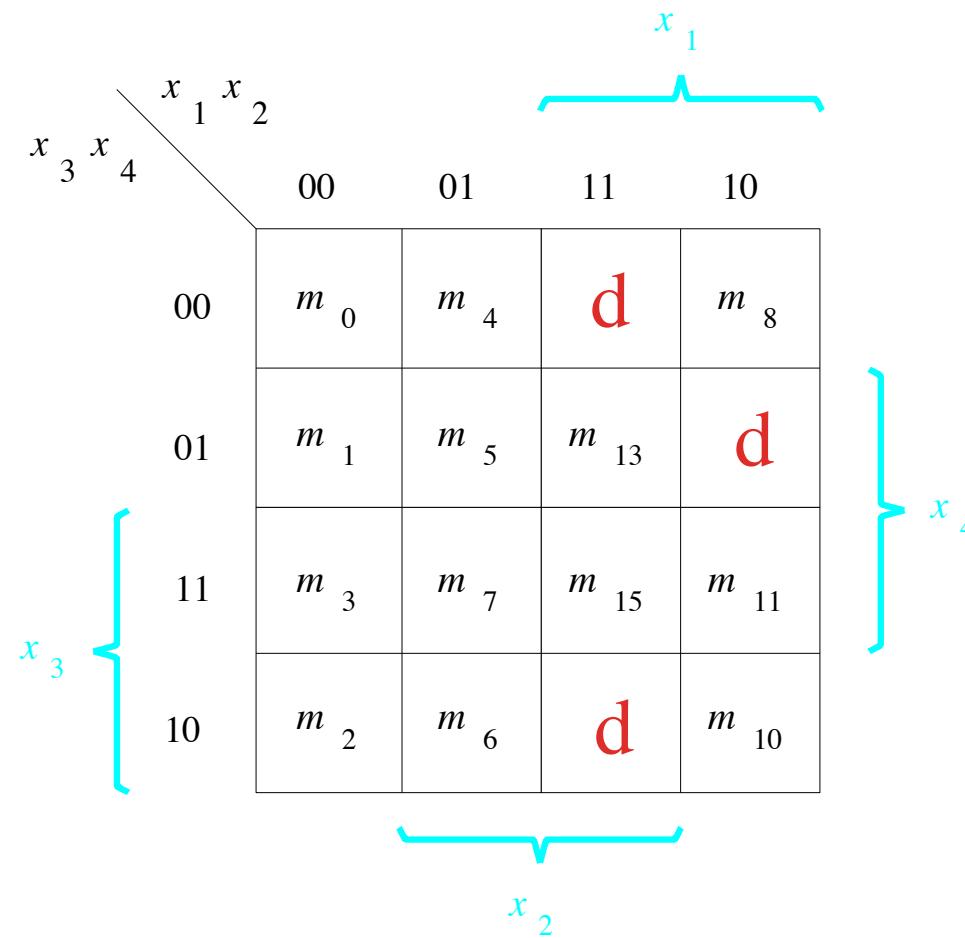


Let's map the expression to the K-Map
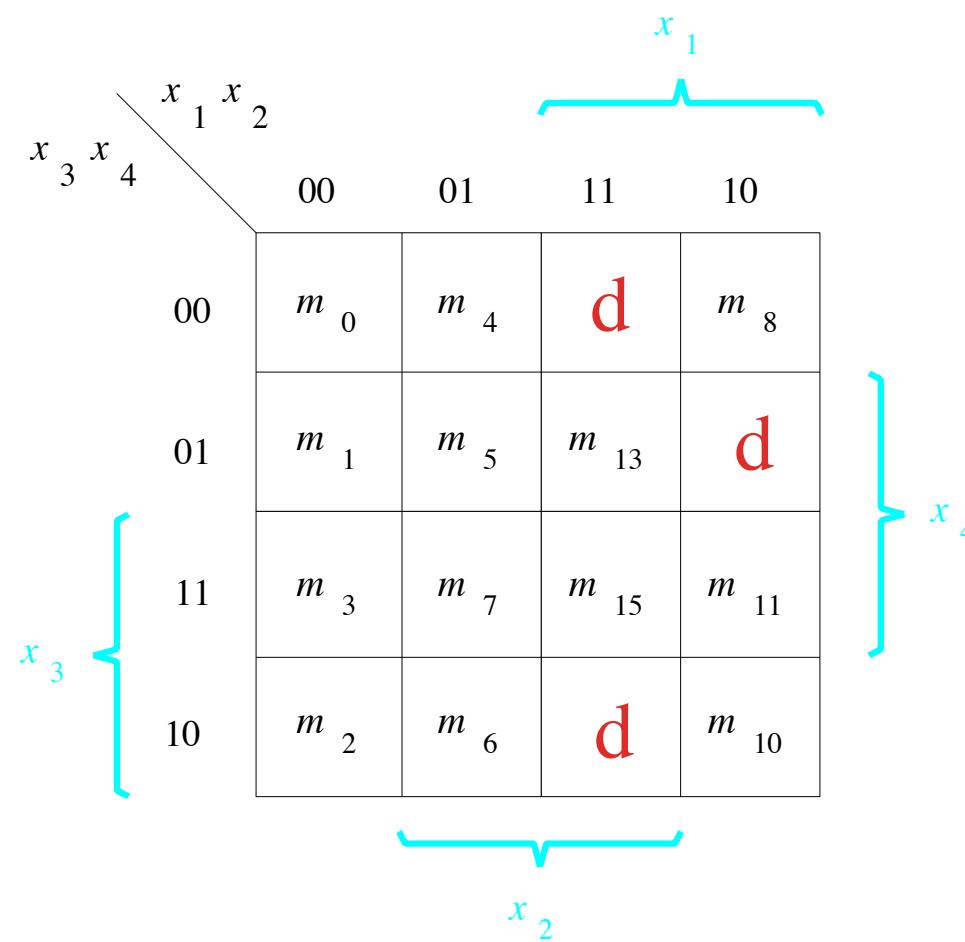
$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$




Let's map the expression to the K-Map
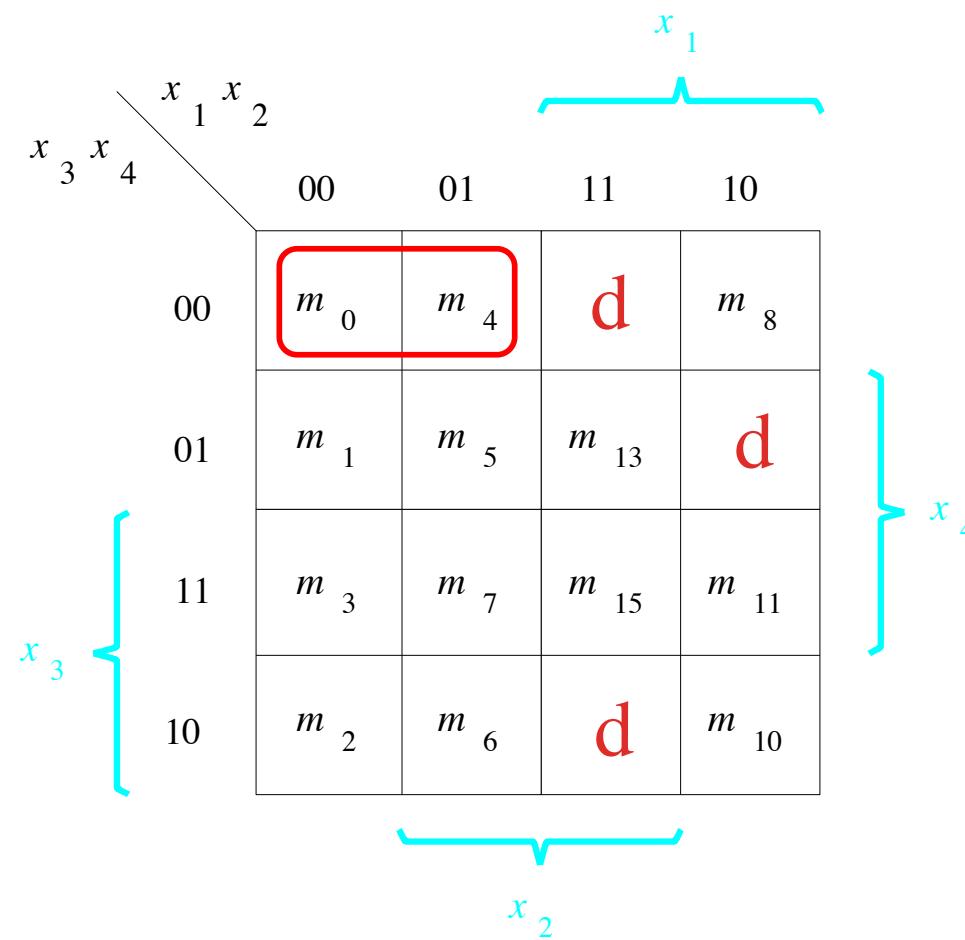
$$f(x_1, \dots, x_4) = \boxed{\bar{x}_1 \bar{x}_3 \bar{x}_4} + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$




Let's map the expression to the K-Map
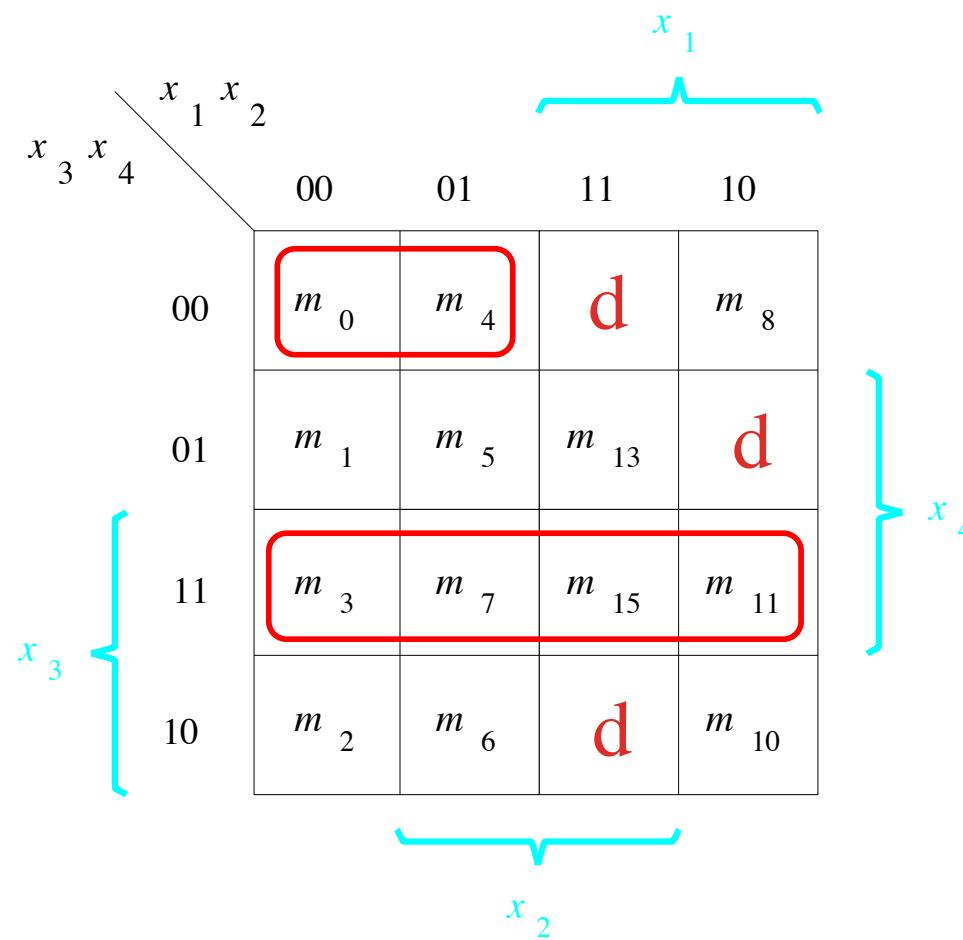
$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + \boxed{x_3 x_4} + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$




Let's map the expression to the K-Map
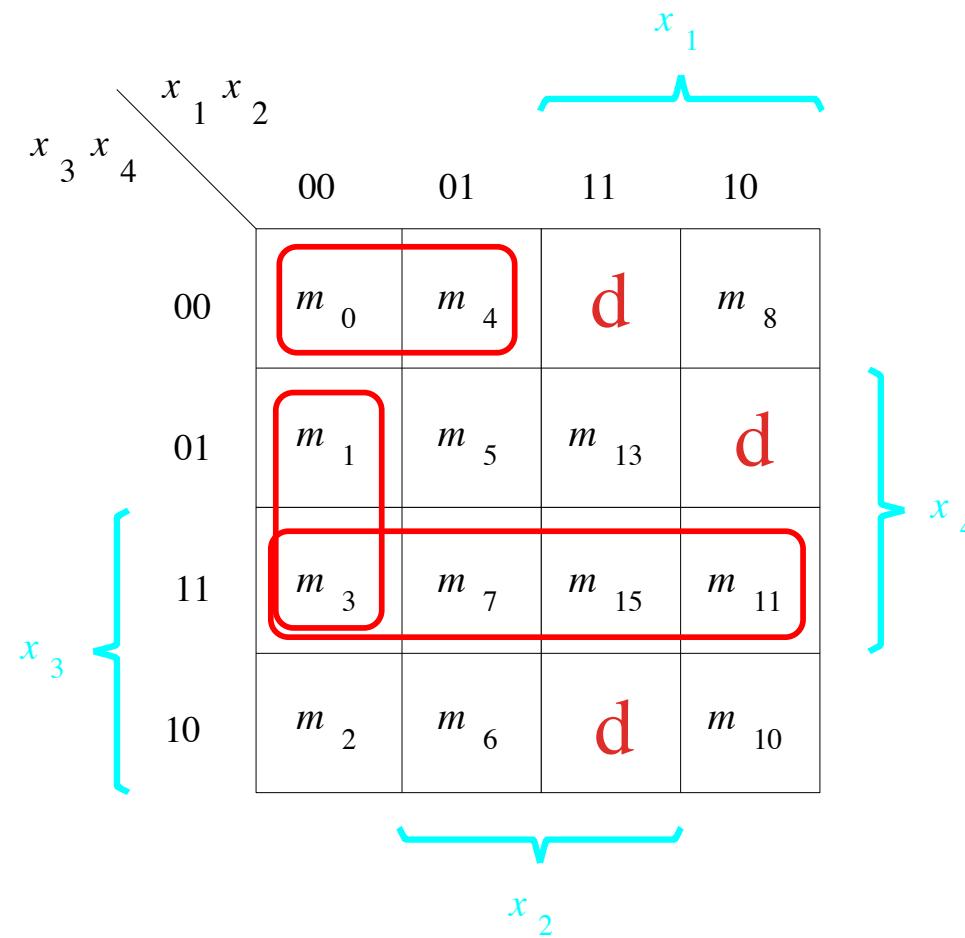
$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \boxed{\bar{x}_1 \bar{x}_2 x_4} + x_1 x_2 \bar{x}_3 x_4$$




Let's map the expression to the K-Map
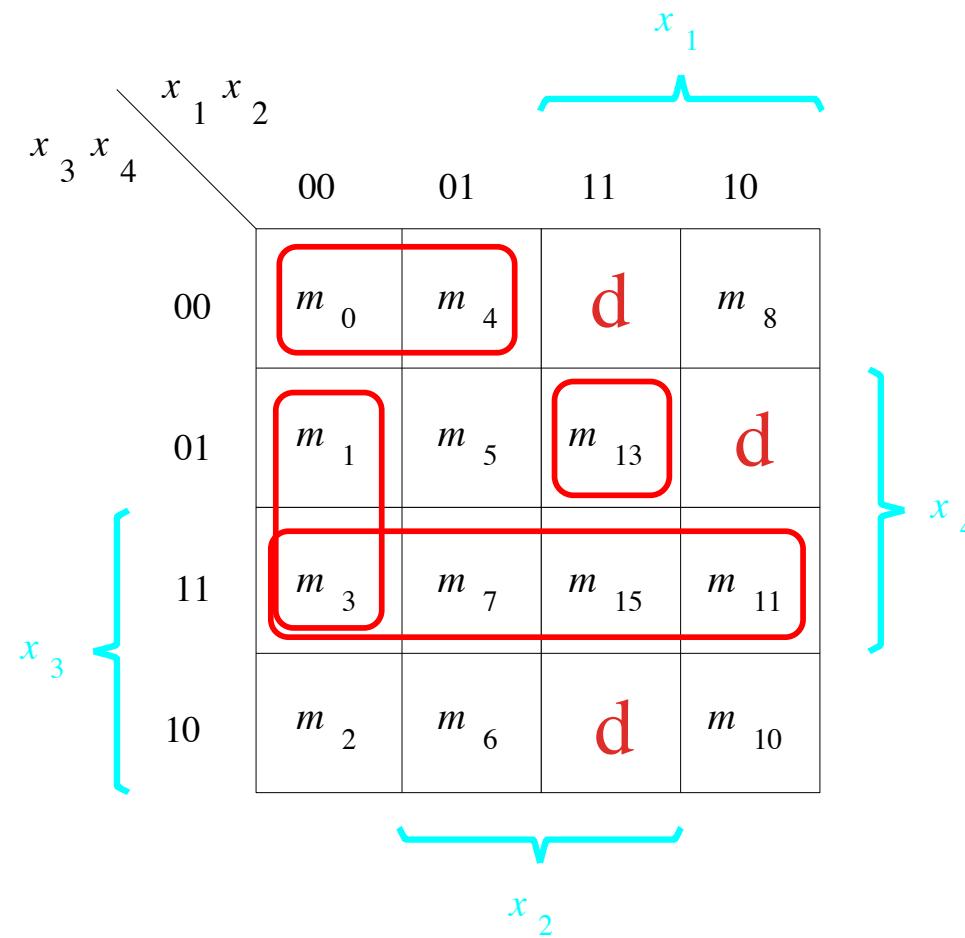
$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + \boxed{x_1 x_2 \bar{x}_3 x_4}$$




Let's map the expression to the K-Map
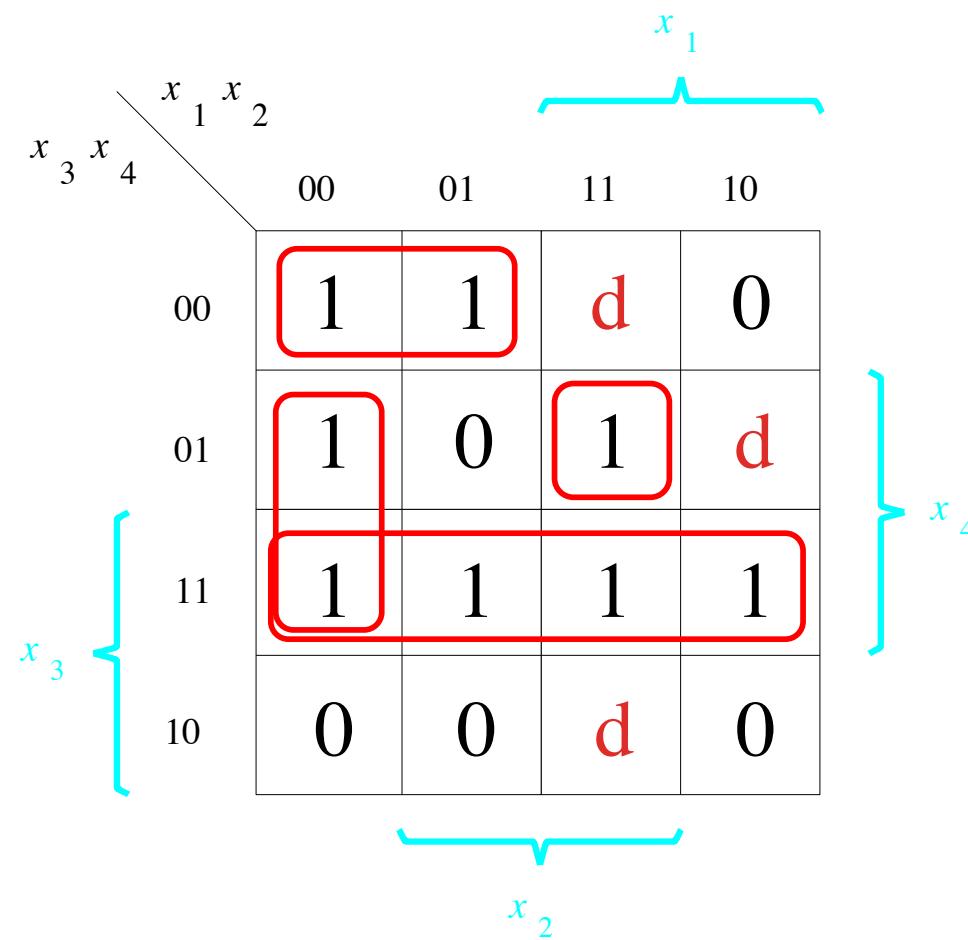
$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$




Let's map the expression to the K-Map
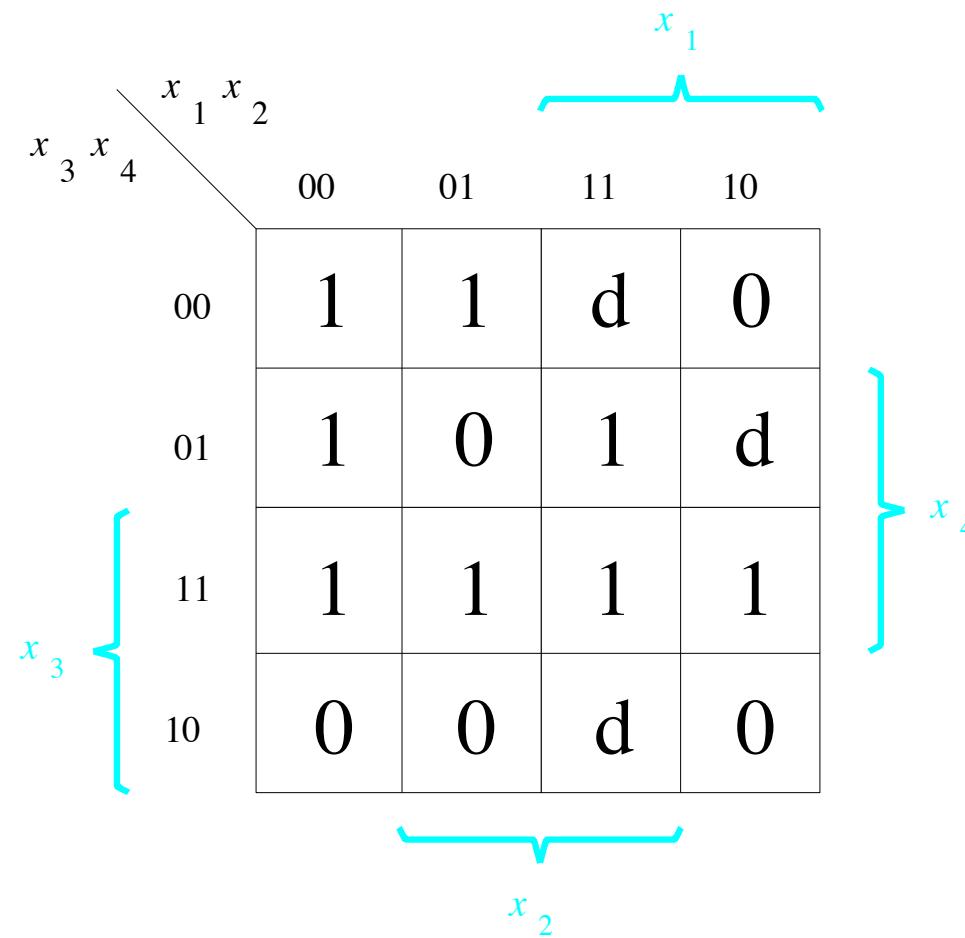
$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$




Let's map the expression to the K-Map
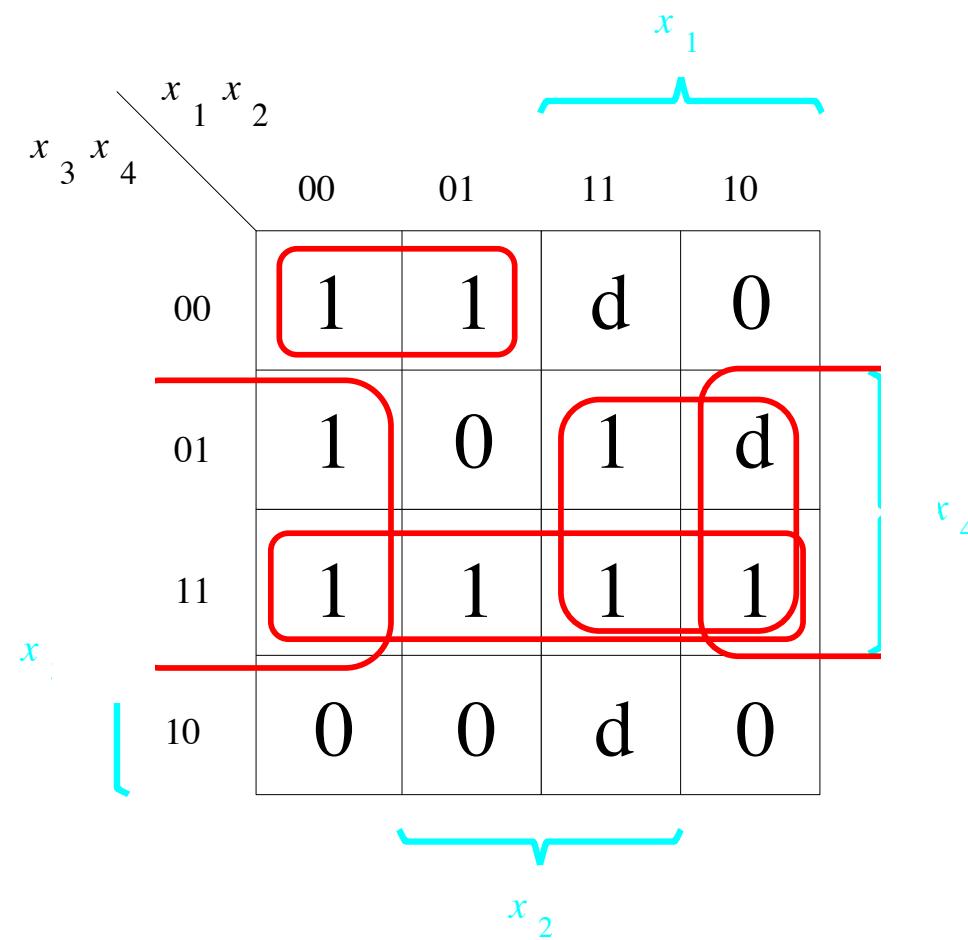
$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$



The SOP Expression

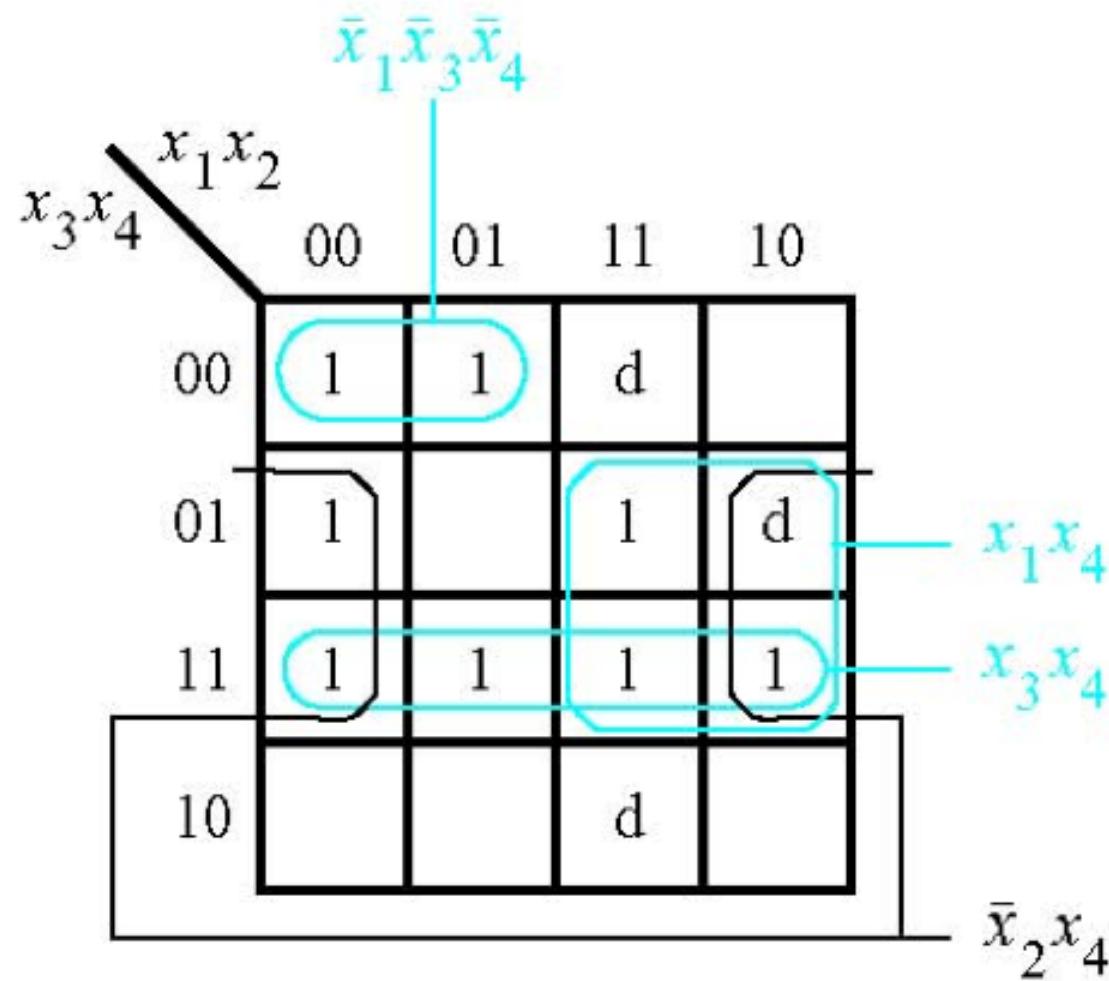
$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$




$$f = x_3 x_4 + \bar{x}_1 \bar{x}_3 \bar{x}_4 + \bar{x}_2 x_4 + x_1 x_2$$

[Figure 2.68a from the textbook]


What about the POS Expression?

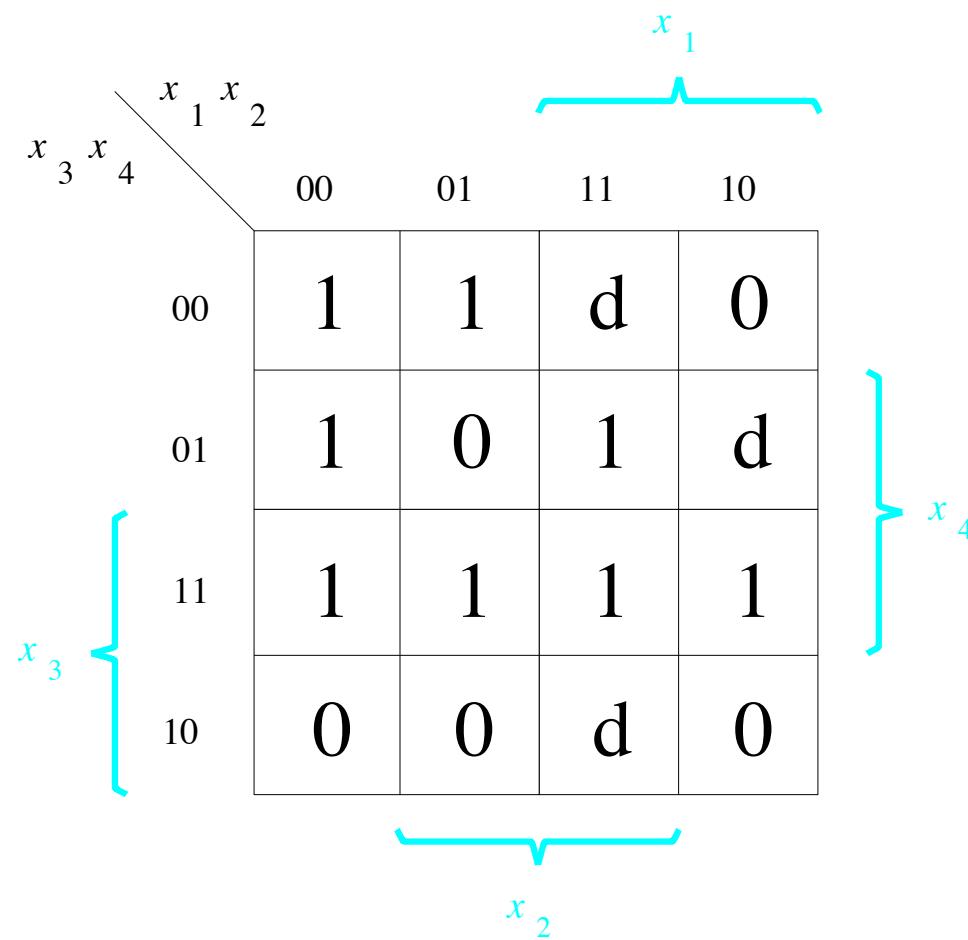

What about the POS Expression?

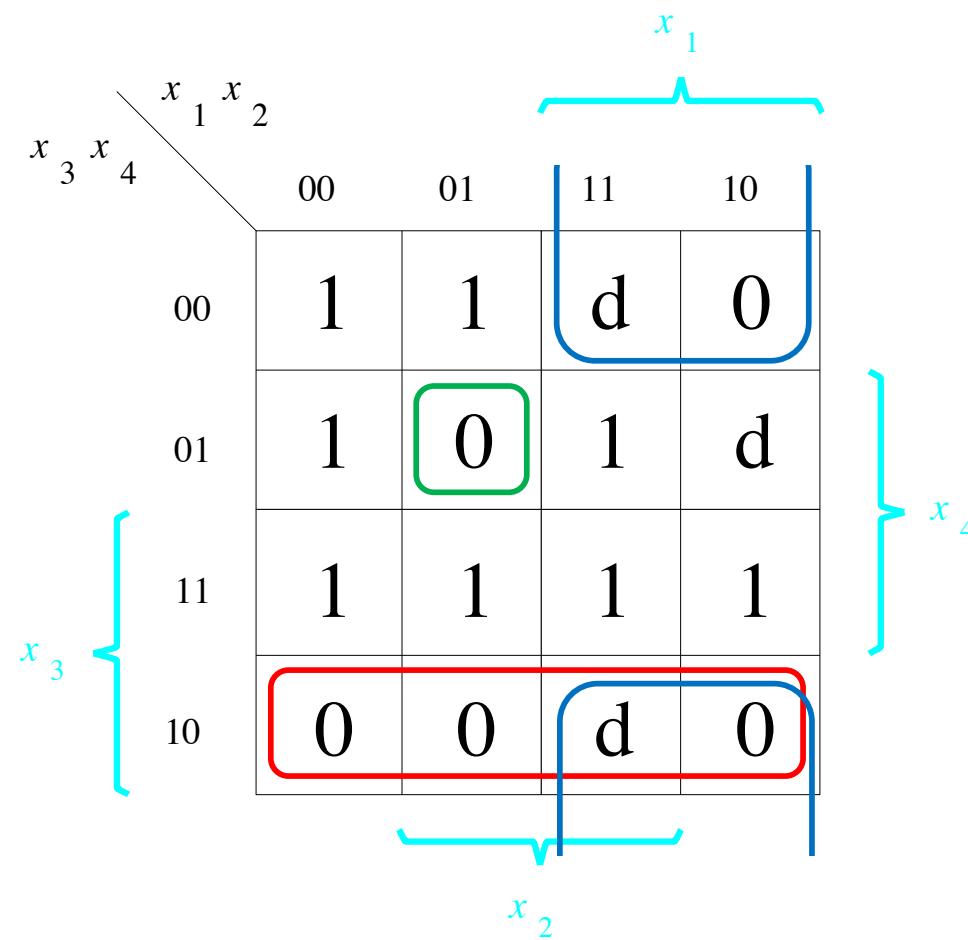

The POS Expression

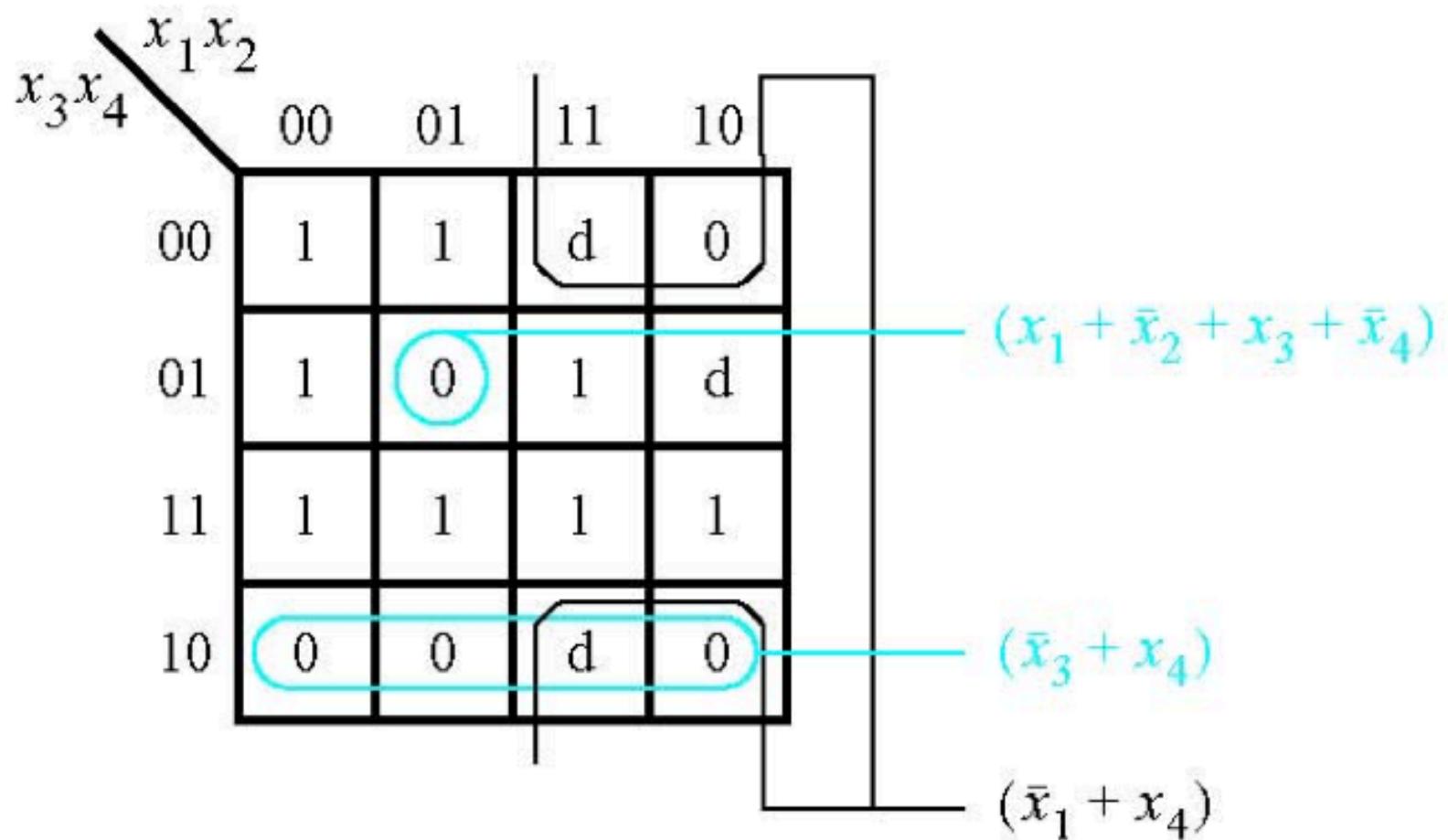

$$f = (\bar{x}_3 + x_4)(\bar{x}_1 + x_4)(x_1 + \bar{x}_2 + x_3 + \bar{x}_4)$$

[Figure 2.68b from the textbook]

Example 7

Derive the minimum-cost SOP expression for

$$f = s_3(\bar{s}_1 + \bar{s}_2) + s_1s_2$$

**First, expand the expression
using property 12a**

$$f = s_3(\bar{s}_1 + \bar{s}_2) + s_1s_2$$


$$f = \bar{s}_1s_3 + \bar{s}_2s_3 + s_1s_2$$

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

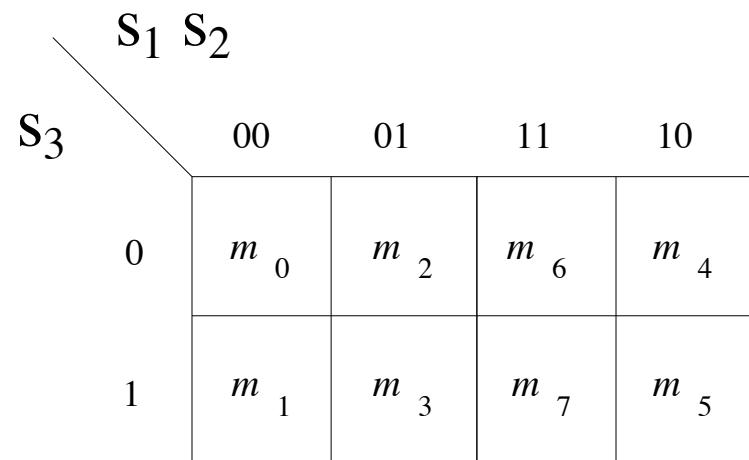


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

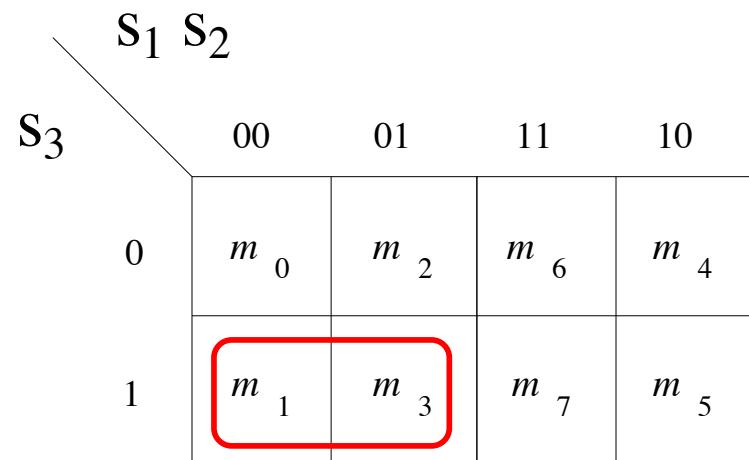


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \boxed{\bar{s}_2 s_3} + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

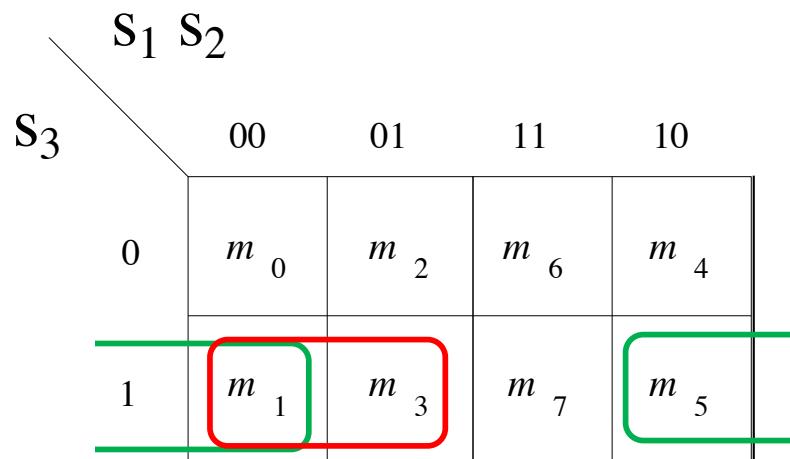


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + \boxed{s_1 s_2}$$

s_1	s_2	s_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

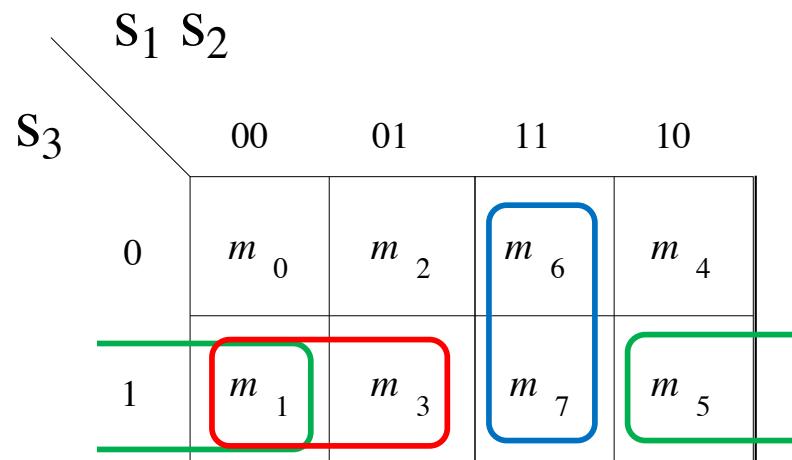


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(a) Truth table

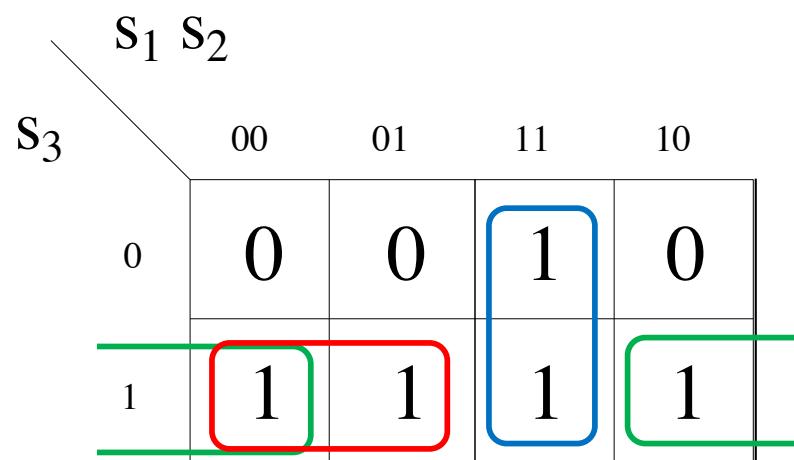


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(a) Truth table

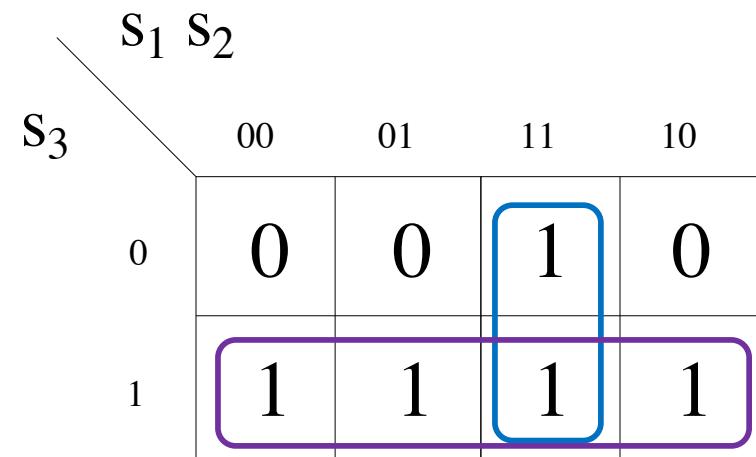


(b) Karnaugh map

Simplified Expression: $f = s_3 + s_1 s_2$

Construct the K-Map for this expression


$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

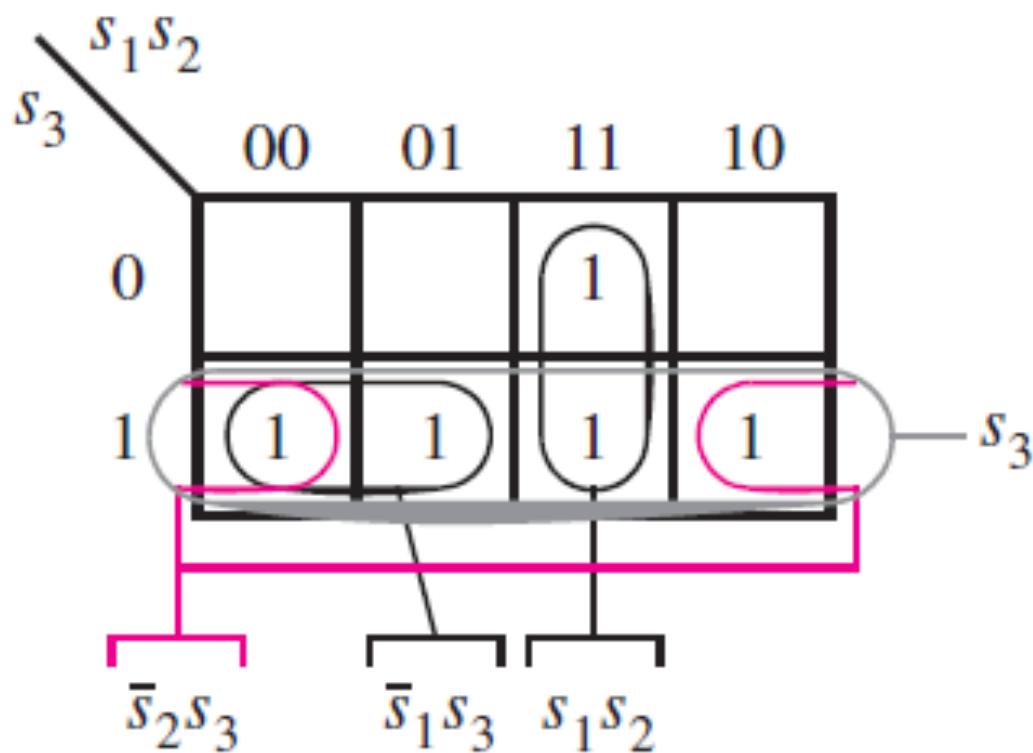

[Figure 2.69 from the textbook]

Construct the K-Map for this expression
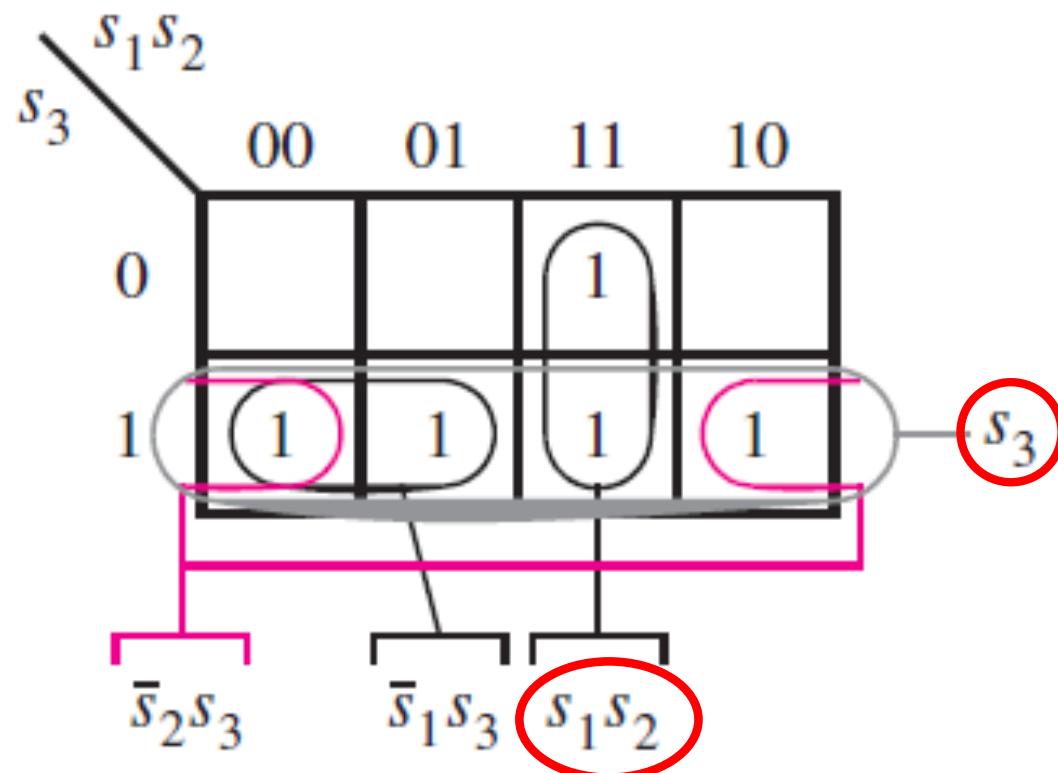
$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$




Simplified Expression: $f = s_3 + s_1 s_2$

[Figure 2.69 from the textbook]

Example 8


Write the Verilog code for the following circuit ...

Logic Circuit

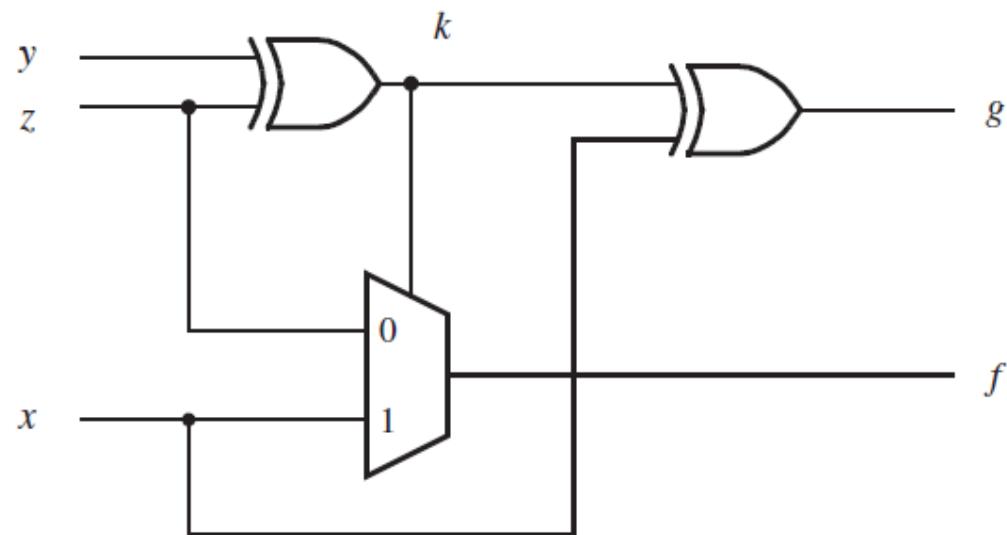


[Figure 2.70 from the textbook]

Circuit for 2-1 Multiplexer

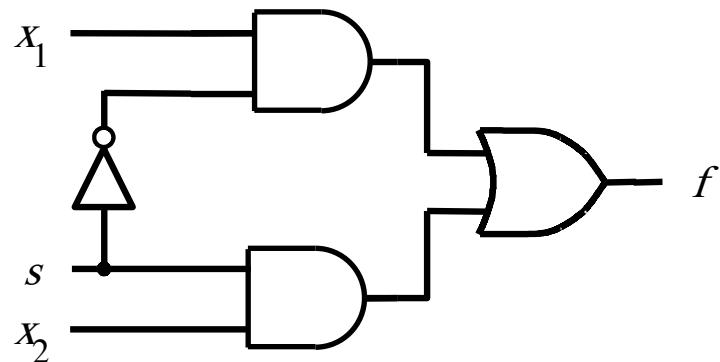

(b) Circuit

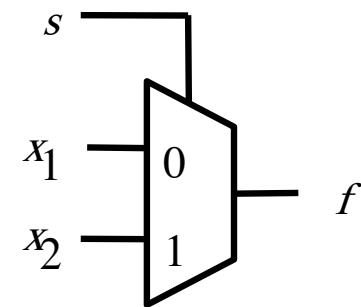


(c) Graphical symbol

$$f(s, x_1, x_2) = \bar{s}x_1 + s x_2$$

[Figure 2.33b-c from the textbook]

Logic Circuit vs Verilog Code

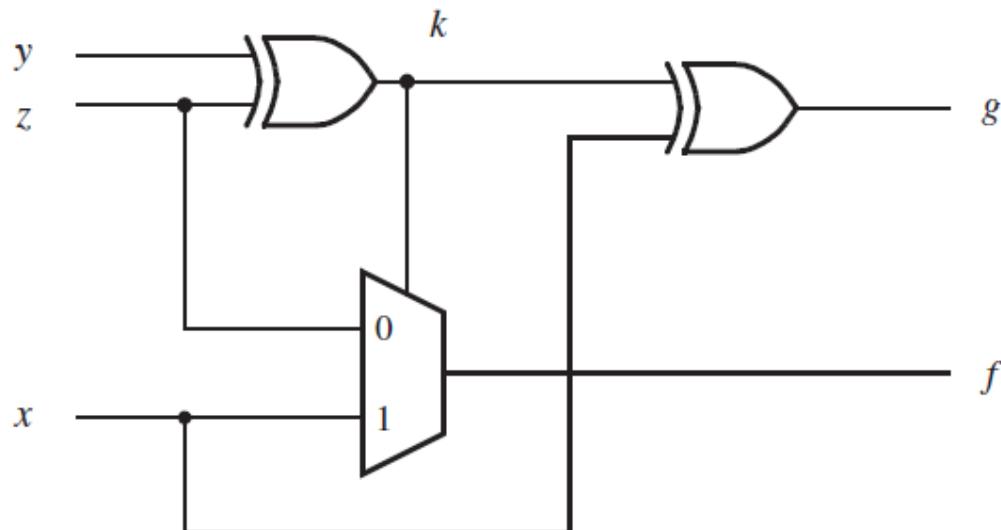

```
module f_g (x, y, z, f, g);
  input x, y, z;
  output f, g;
  wire k;


  assign k = y ^ z;
  assign g = k ^ x;
  assign f = (~k & z) | (k & x);

endmodule
```

Example 9


Write the Verilog code for the following circuit ...

The Logic Circuit for this Example

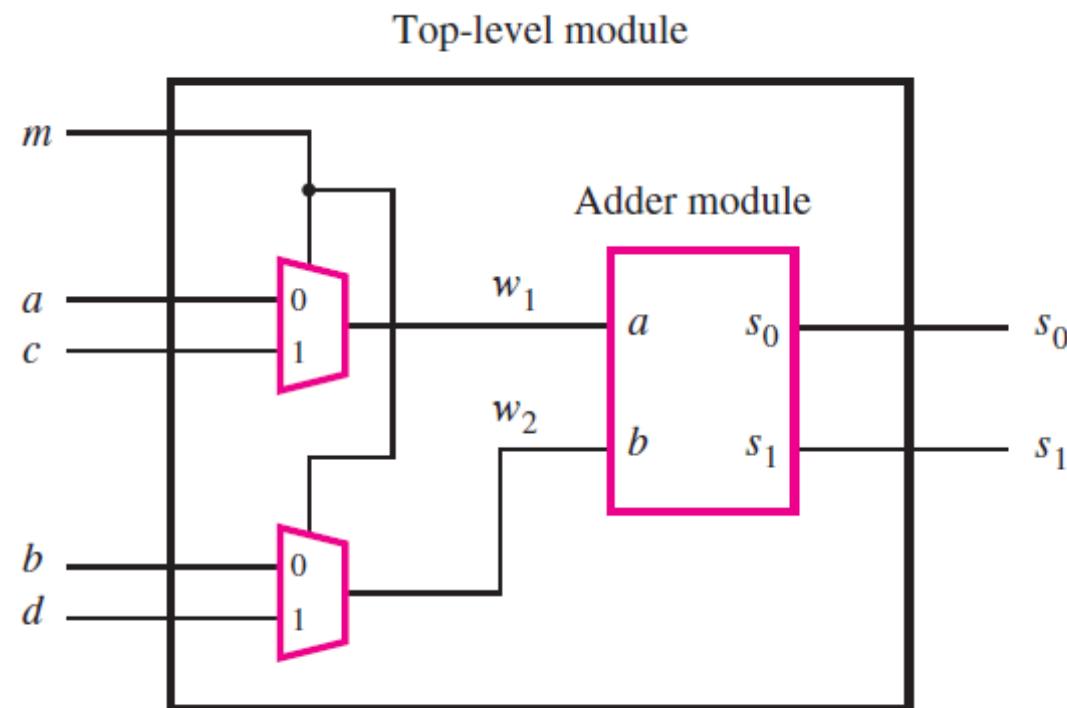


[Figure 2.72 from the textbook]

Circuit for 2-1 Multiplexer

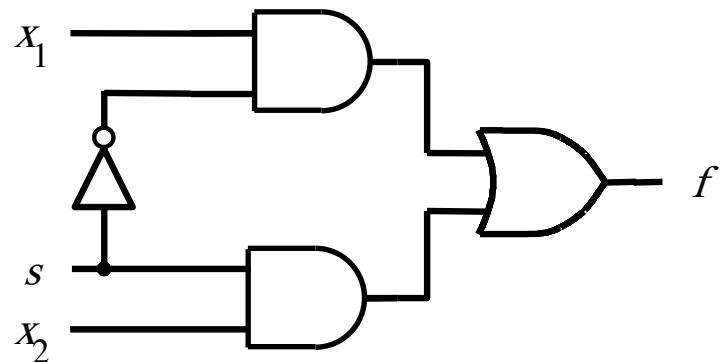

(b) Circuit

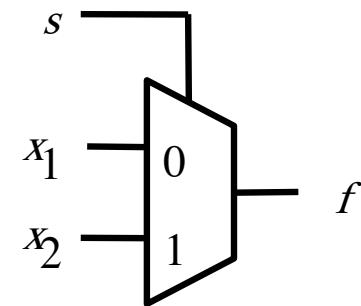


(c) Graphical symbol

$$f(s, x_1, x_2) = \bar{s}x_1 + s x_2$$


[Figure 2.33b-c from the textbook]

Addition of Binary Numbers

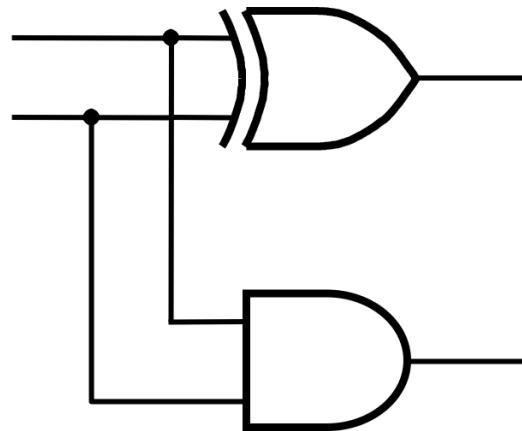

a	b	s_1	s_0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Logic Circuit vs Verilog Code

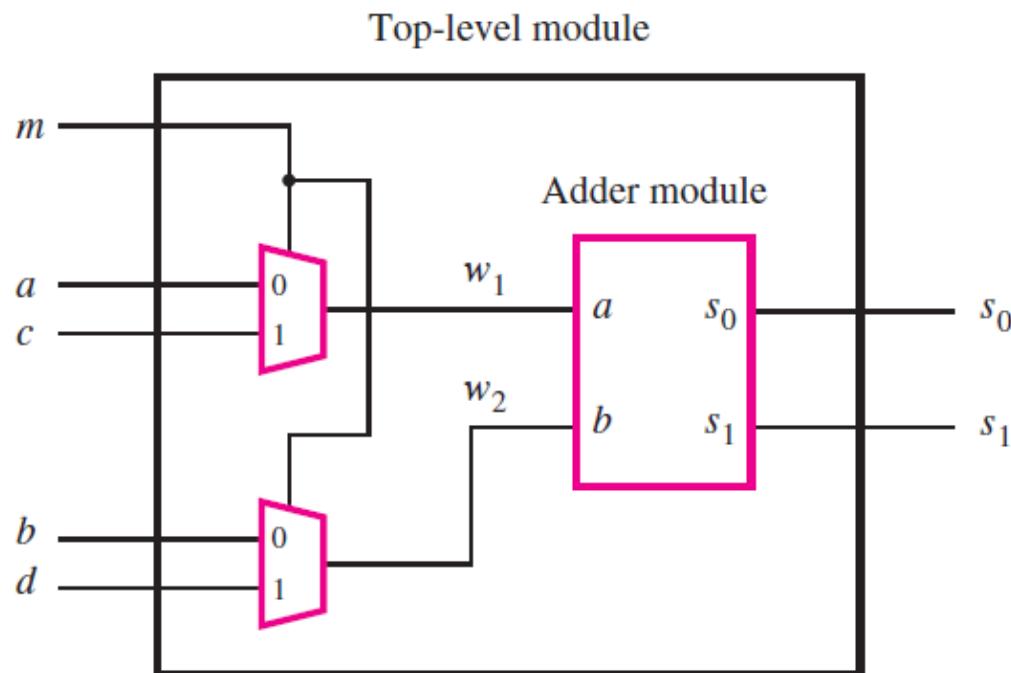


```
module shared (a, b, c, d, m, s1, s0);
    input a, b, c, d, m;
    output s1, s0;
    wire w1, w2;
    mux2to1 U1 (a, c, m, w1);
    mux2to1 U2 (b, d, m, w2);
    adder U3 (w1, w2, s1, s0);
endmodule
```

```
module mux2to1 (x1, x2, s, f);
    input x1, x2, s;
    output f;
    assign f = (~s & x1) | (s & x2);
endmodule
```

```
module adder (a, b, s1, s0);
    input a, b;
    output s1, s0;
    assign s1 = a & b;
    assign s0 = a ^ b;
endmodule
```


Some material form Appendix B

Programmable Logic Array (PLA)

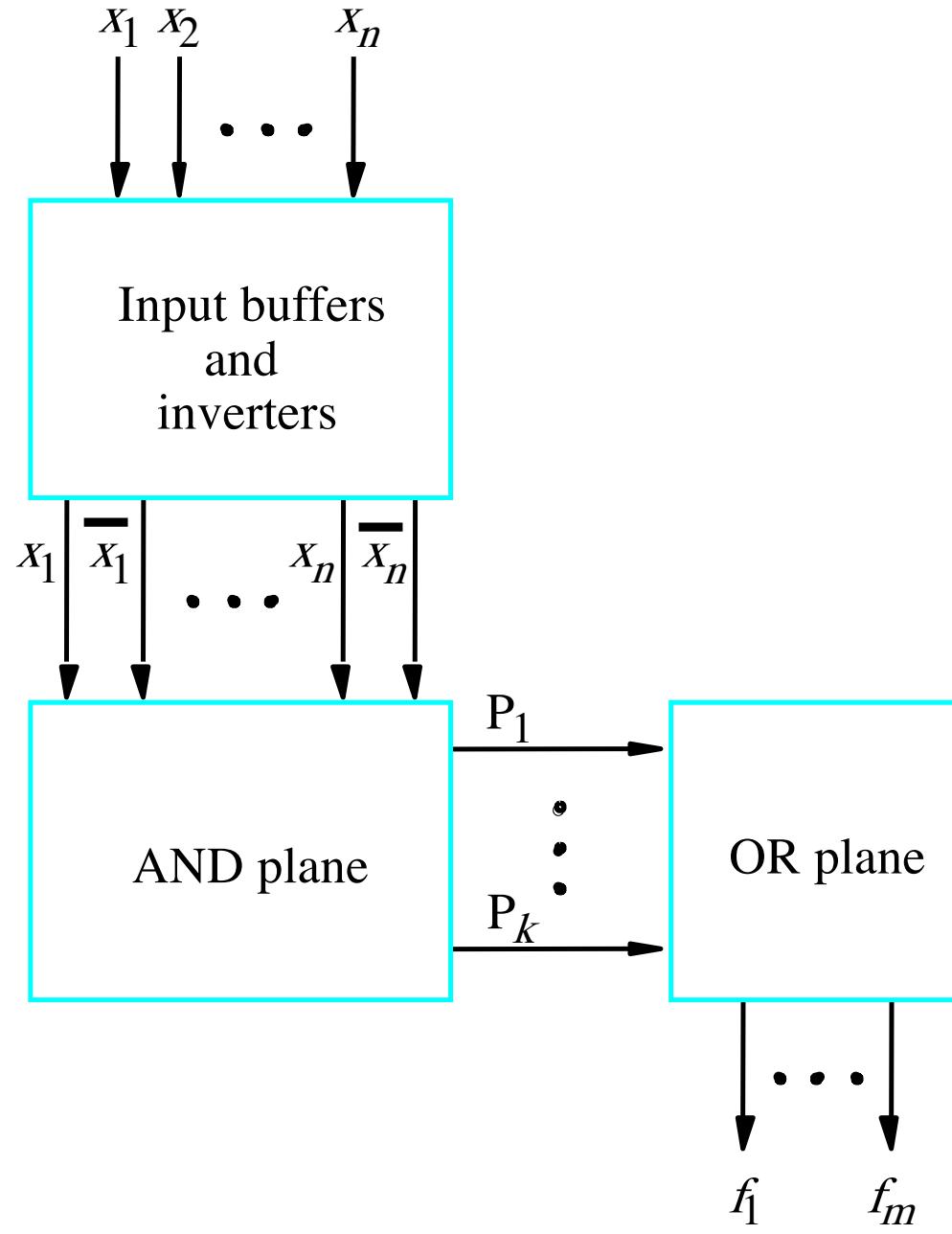


[Figure B.25 from textbook]

Gate-Level Diagram of a PLA

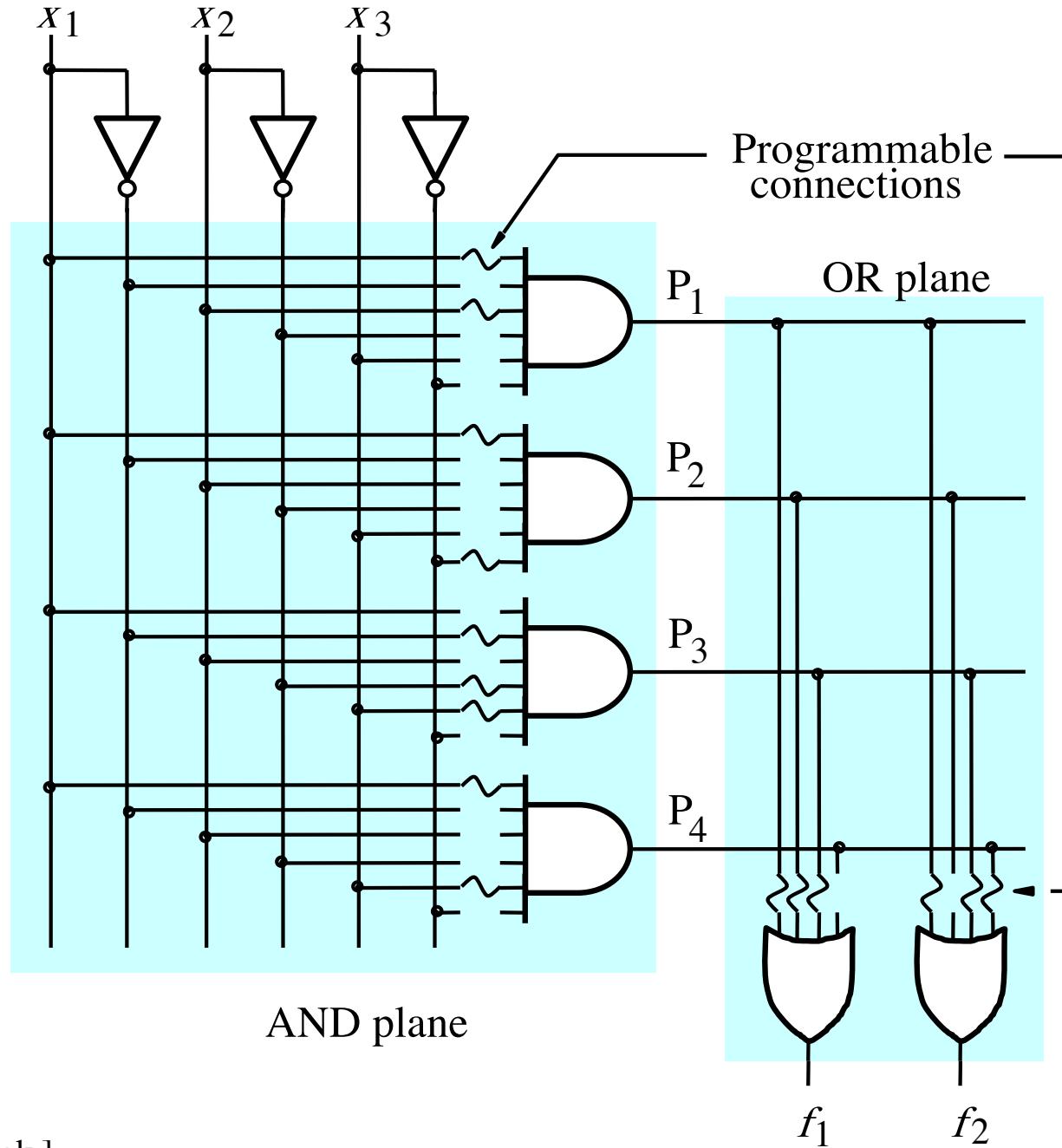


[Figure B.26 from textbook]

Customary Schematic for PLA

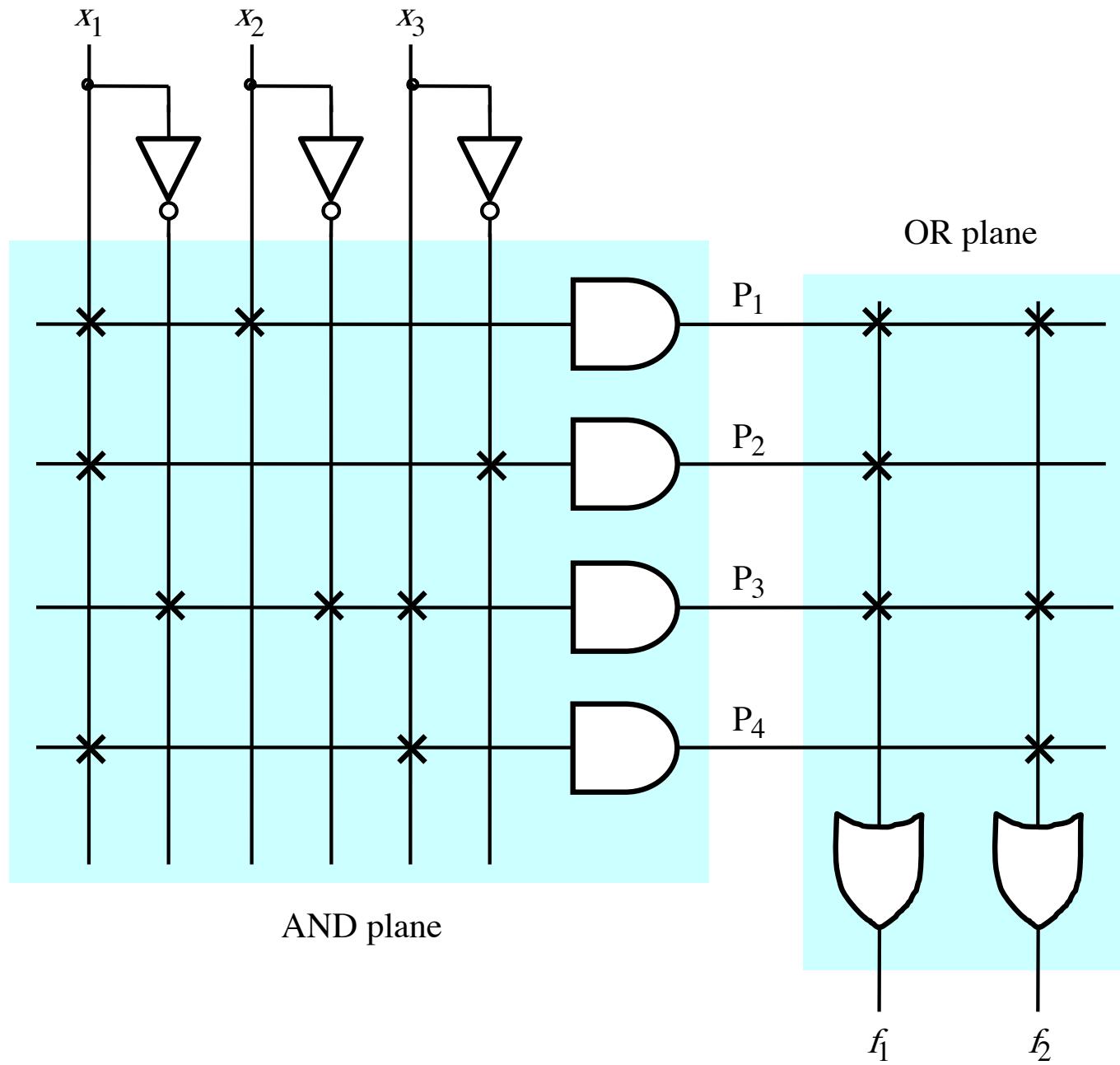


[Figure B.27 from textbook]

Programmable Array Logic (PAL)

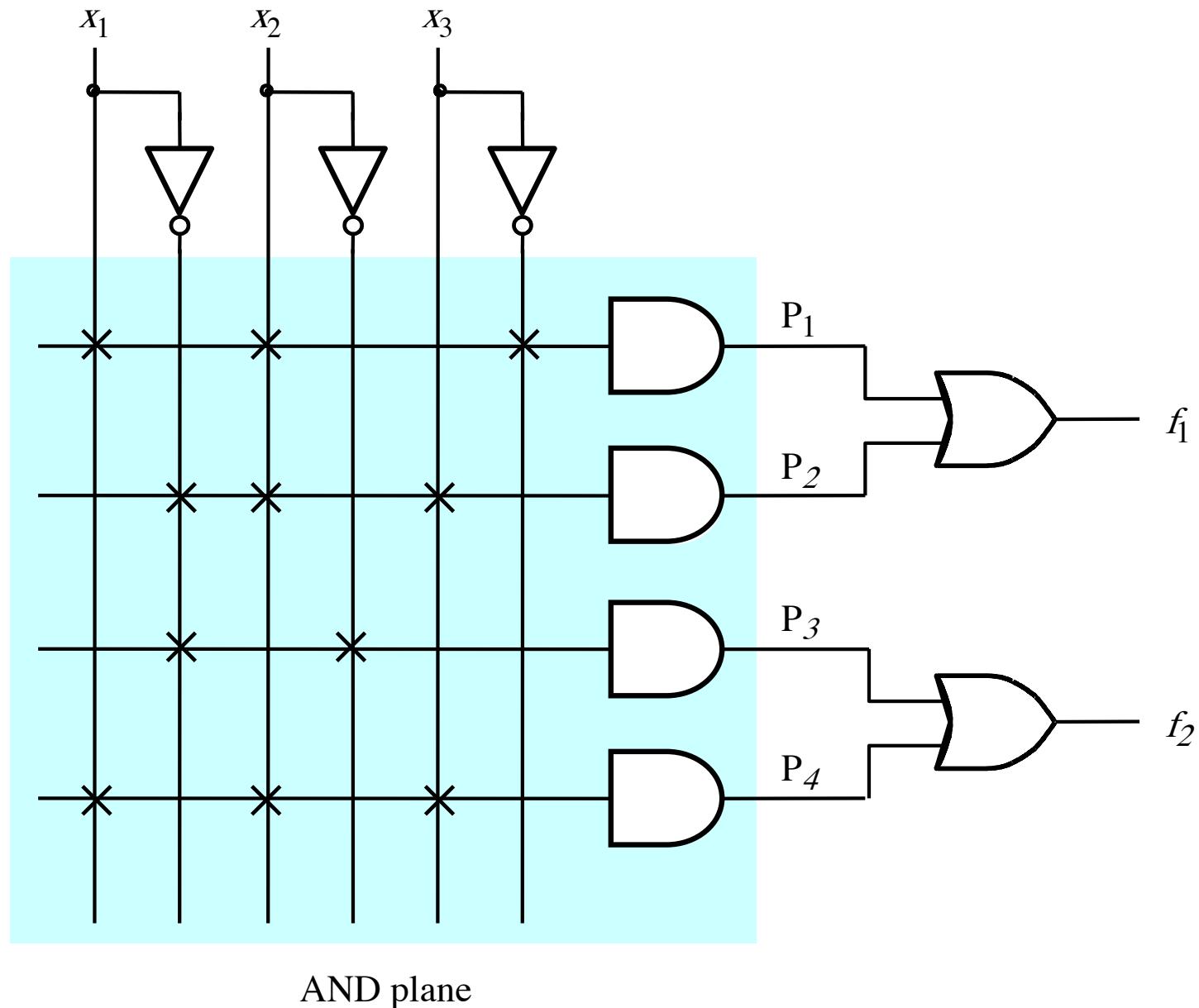

[Figure B.28 from textbook]

Programmable Array Logic (PAL)

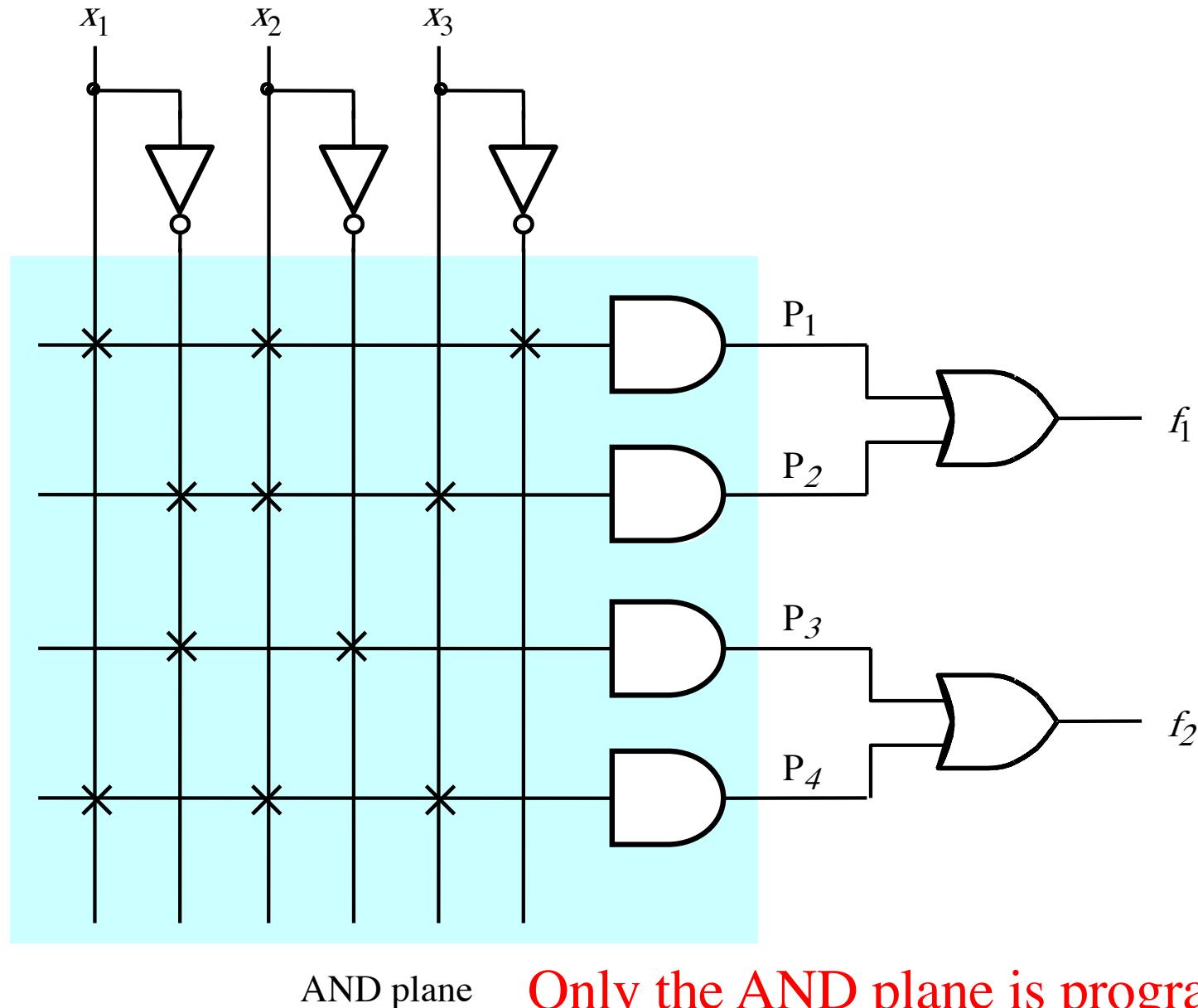

[Figure B.28 from textbook]

Questions?

THE END