



# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Fast Adders

*CprE 281: Digital Logic*  
*Iowa State University, Ames, IA*  
*Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **No HW is due next Monday**
- **HW 6 will be due on Monday Oct. 10.**

# Administrative Stuff

- **Labs next week**
- **Mini-Project**
- **This is worth 3% of your grade (x2 labs)**
- **[https://www.ece.iastate.edu/~alexs/classes/2022\\_Fall\\_281/labs/Project-Mini/](https://www.ece.iastate.edu/~alexs/classes/2022_Fall_281/labs/Project-Mini/)**

# Quick Review

The problems in which row are easier to calculate?

$$\begin{array}{r} \phantom{-} 82 \\ - \phantom{0} 61 \\ \hline \phantom{00} ?? \end{array}$$

$$\begin{array}{r} \phantom{-} 48 \\ - \phantom{0} 26 \\ \hline \phantom{00} ?? \end{array}$$

$$\begin{array}{r} \phantom{-} 32 \\ - \phantom{0} 11 \\ \hline \phantom{00} ?? \end{array}$$

$$\begin{array}{r} \phantom{-} 82 \\ - \phantom{0} 64 \\ \hline \phantom{00} ?? \end{array}$$

$$\begin{array}{r} \phantom{-} 48 \\ - \phantom{0} 29 \\ \hline \phantom{00} ?? \end{array}$$

$$\begin{array}{r} \phantom{-} 32 \\ - \phantom{0} 13 \\ \hline \phantom{00} ?? \end{array}$$

The problems in which row are easier to calculate?

$$\begin{array}{r} \phantom{-} 82 \\ - 61 \\ \hline 21 \end{array}$$

$$\begin{array}{r} \phantom{-} 48 \\ - 26 \\ \hline 22 \end{array}$$

$$\begin{array}{r} \phantom{-} 32 \\ - 11 \\ \hline 21 \end{array}$$

Why?

$$\begin{array}{r} \phantom{-} 82 \\ - 64 \\ \hline 18 \end{array}$$

$$\begin{array}{r} \phantom{-} 48 \\ - 29 \\ \hline 19 \end{array}$$

$$\begin{array}{r} \phantom{-} 32 \\ - 13 \\ \hline 19 \end{array}$$

# Another Way to Do Subtraction

$$82 - 64 = 82 + 100 - 100 - 64$$



# Another Way to Do Subtraction

$$\begin{aligned}82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100\end{aligned}$$

## Another Way to Do Subtraction

$$\begin{aligned}82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100 \\ &= 82 + (99 + 1 - 64) - 100\end{aligned}$$

# Another Way to Do Subtraction

$$\begin{aligned}82 - 64 &= 82 + 100 - 100 - 64 \\&= 82 + (100 - 64) - 100 \\&= 82 + (99 + 1 - 64) - 100 \\&= 82 + (99 - 64) + 1 - 100\end{aligned}$$

# Another Way to Do Subtraction

$$82 - 64 = 82 + 100 - 100 - 64$$

$$= 82 + (100 - 64) - 100$$

$$= 82 + (99 + 1 - 64) - 100$$

Does not require borrows

$$= 82 + (99 - 64) + 1 - 100$$

# 9's Complement (subtract each digit from 9)

$$\begin{array}{r} 99 \\ - 64 \\ \hline 35 \end{array}$$

# 10's Complement

(subtract each digit from 9 and add 1 to the result)

$$\begin{array}{r} \phantom{-} 99 \\ - 64 \\ \hline 35 + 1 = 36 \end{array}$$

# Another Way to Do Subtraction

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$



# Another Way to Do Subtraction

9's complement

$$\begin{aligned}82 - 64 &= 82 + (99 - 64) + 1 - 100 \\ &= 82 + 35 + 1 - 100\end{aligned}$$

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

$$= 82 + (35 + 1) - 100$$

10's complement

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

$$= 82 + (35 + 1) - 100$$

10's complement

$$= 82 + 36 - 100$$

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

10's complement

$$= 82 + (35 + 1) - 100$$

$$= (82 + 36) - 100 \quad // \text{ Add the first two.}$$

$$= 118 - 100$$

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

10's complement

$$= 82 + (35 + 1) - 100$$

$$= 82 + 36 - 100 \quad // \text{ Add the first two.}$$

$$= 118 - 100 \quad // \text{ Just delete the leading 1.}$$

// No need to subtract 100.

$$= 18$$

# 1's Complement

# **1' s complement (subtract each digit from 1)**

Let  $K$  be the negative equivalent of an  $n$ -bit positive number  $P$ .

Then, in 1' s complement representation  $K$  is obtained by subtracting  $P$  from  $2^n - 1$ , namely

$$K = (2^n - 1) - P$$

This means that  $K$  can be obtained by inverting all bits of  $P$ .

# 1' s complement (subtract each digit from 1)

Let  $K$  be the negative equivalent of an 8-bit positive number  $P$ .

Then, in 1' s complement representation  $K$  is obtained by subtracting  $P$  from  $2^8 - 1$ , namely

$$K = (2^8 - 1) - P = 255 - P$$

This means that  $K$  can be obtained by inverting all bits of  $P$ .


Provided that  $P$  is between 0 and 127, because the most significant bit must be zero to indicate that it is positive.




# 1's complement (subtract each digit from 1)

$$\begin{array}{r} \phantom{-} 1 \phantom{0} 1 \phantom{0} 1 \phantom{0} 1 \phantom{0} 1 \phantom{0} 1 \phantom{0} 1 \\ - 0 \phantom{0} 0 \phantom{0} 1 \phantom{0} 0 \phantom{0} 1 \phantom{0} 1 \phantom{0} 0 \phantom{0} 0 \\ \hline 1 \phantom{0} 1 \phantom{0} 0 \phantom{0} 1 \phantom{0} 0 \phantom{0} 0 \phantom{0} 1 \phantom{0} 1 \end{array}$$
 
# Circuit for negating a number stored in 1's complement representation


 
# Circuit for negating a number stored in 1's complement representation



# **2's Complement**

# 2' s complement

Let  $K$  be the negative equivalent of an  $n$ -bit positive number  $P$ .

Then, in 2' s complement representation  $K$  is obtained by subtracting  $P$  from  $2^n$ , namely

$$K = 2^n - P$$

# Deriving 2' s complement

For a positive n-bit number P, let  $K_1$  and  $K_2$  denote its 1' s and 2' s complements, respectively.

$$K_1 = (2^n - 1) - P$$

$$K_2 = 2^n - P$$

Since  $K_2 = K_1 + 1$ , it is evident that in a logic circuit the 2' s complement can be computed by inverting all bits of P and then adding 1 to the resulting 1' s-complement number.

# Deriving 2' s complement

For a positive 8-bit number  $P$ , let  $K_1$  and  $K_2$  denote its 1' s and 2' s complements, respectively.

$$K_1 = (2^n - 1) - P = 255 - P$$

$$K_2 = 2^n - P = 256 - P$$

Since  $K_2 = K_1 + 1$ , it is evident that in a logic circuit the 2' s complement can be computed by inverting all bits of  $P$  and then adding 1 to the resulting 1' s-complement number.

# Negate these numbers stored in 2's complement representation

0 1 0 1

1 1 1 0

1 1 0 0

0 1 1 1



# Negate these numbers stored in 2's complement representation

0 1 0 1

1 0 1 0

1 1 1 0

0 0 0 1

1 1 0 0

0 0 1 1

0 1 1 1

1 0 0 0

Invert all bits...

# Negate these numbers stored in 2's complement representation

$$\begin{array}{r} 0101 \\ + 1010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 1110 \\ + 0001 \\ \hline 0010 \end{array}$$

$$\begin{array}{r} 1100 \\ + 0011 \\ \hline 0100 \end{array}$$

$$\begin{array}{r} 0111 \\ + 1000 \\ \hline 1001 \end{array}$$

.. then add 1.

# Negate these numbers stored in 2's complement representation


$$\begin{array}{r} 0101 = +5 \\ + 1010 \\ \hline 1011 = -5 \end{array}$$

$$\begin{array}{r} 1110 = -2 \\ + 0001 \\ \hline 0010 = +2 \end{array}$$


$$\begin{array}{r} 1100 = -4 \\ + 0011 \\ \hline 0100 = +4 \end{array}$$

$$\begin{array}{r} 0111 = +7 \\ + 1000 \\ \hline 1001 = -7 \end{array}$$
 
# Circuit #1 for negating a number stored in 2's complement representation


 
# Circuit #2 for negating a number stored in 2's complement representation



**Addition of two numbers stored  
in 2's complement representation**

# There are four cases to consider

- $(+5) + (+2)$

- $(-5) + (+2)$

- $(+5) + (-2)$

- $(-5) + (-2)$

# There are four cases to consider

- $(+5) + (+2)$       **positive plus positive**
- $(-5) + (+2)$       **negative plus positive**
- $(+5) + (-2)$       **positive plus negative**
- $(-5) + (-2)$       **negative plus negative**



# Positive plus positive

$$\begin{array}{r}
 (+5) \\
 + (+2) \\
 \hline
 (+7)
 \end{array}
 \qquad
 \begin{array}{r}
 0101 \\
 + 0010 \\
 \hline
 0111
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1


# Negative plus positive

$$\begin{array}{r}
 (-5) \\
 + (+2) \\
 \hline
 (-3)
 \end{array}
 \qquad
 \begin{array}{r}
 1011 \\
 + 0010 \\
 \hline
 1101
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

# Positive plus negative


$$\begin{array}{r}
 (+5) \\
 + (-2) \\
 \hline
 (+3)
 \end{array}
 \qquad
 \begin{array}{r}
 0101 \\
 + 1110 \\
 \hline
 10011
 \end{array}$$


  
 ignore

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

# Negative plus negative

$$\begin{array}{r}
 (-5) \\
 + (-2) \\
 \hline
 (-7)
 \end{array}
 \qquad
 \begin{array}{r}
 1011 \\
 + 1110 \\
 \hline
 11001
 \end{array}$$


  
 ignore

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

**Subtraction of two numbers stored  
in 2's complement representation**

# There are four cases to consider

- $(+5) - (+2)$

- $(-5) - (+2)$

- $(+5) - (-2)$

- $(-5) - (-2)$

# There are four cases to consider

- $(+5) - (+2)$       **positive minus positive**
- $(-5) - (+2)$       **negative minus positive**
- $(+5) - (-2)$       **positive minus negative**
- $(-5) - (-2)$       **negative minus negative**

# There are four cases to consider

- $(+5) - (+2)$
- $(-5) - (+2)$
- $(+5) - (-2)$
- $(-5) - (-2)$



# There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$

- $(-5) - (+2) = (-5) + (-2)$

- $(+5) - (-2) = (+5) + (+2)$

- $(-5) - (-2) = (-5) + (+2)$

# There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$

- $(-5) - (+2) = (-5) + (-2)$

- $(+5) - (-2) = (+5) + (+2)$

- $(-5) - (-2) = (-5) + (+2)$

We can change subtraction into addition ...

# There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$

- $(-5) - (+2) = (-5) + (-2)$

- $(+5) - (-2) = (+5) + (+2)$

- $(-5) - (-2) = (-5) + (+2)$

... if we negate the second number.

# There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$

- $(-5) - (+2) = (-5) + (-2)$

- $(+5) - (-2) = (+5) + (+2)$

- $(-5) - (-2) = (-5) + (+2)$

These are the four addition cases  
(arranged in a shuffled order)

# Start with: Positive minus positive


$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 \underline{0101} \\
 - \underline{0010} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]


# Convert to: Positive plus negative

$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 \color{red}{0101} \\
 - \color{yellow}{0010} \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 0101 \\
 + 1110 \\
 \hline
 10011
 \end{array}
 \quad
 \begin{array}{r}
 (+5) \\
 + (-2) \\
 \hline
 (+3)
 \end{array}$$



$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1


# Convert to: Positive plus negative

 

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]
 
# Graphical interpretation of four-bit 2's complement numbers



(a) The number circle

(b) Subtracting 2 by adding its 2's complement




# Start with: Negative minus positive

$$\begin{array}{r}
 (-5) \\
 - (+2) \\
 \hline
 (-7)
 \end{array}
 \qquad
 \begin{array}{r}
 \color{red}{1011} \\
 - \color{yellow}{0010} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]

# Convert to: Negative plus negative

 

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]



# Start with: Positive minus negative

$$\begin{array}{r}
 (+5) \\
 - (-2) \\
 \hline
 (+7)
 \end{array}
 \qquad
 \begin{array}{r}
 \underline{0101} \\
 - \underline{1110} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]

# Convert to: Positive plus positive

$$\begin{array}{r}
 (+5) \\
 - (-2) \\
 \hline
 (+7)
 \end{array}
 \quad
 \begin{array}{r}
 \text{0101} \\
 - \text{1110} \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 \text{0101} \\
 + \text{0010} \\
 \hline
 \text{0111}
 \end{array}
 \quad
 \begin{array}{r}
 (+5) \\
 + (+2) \\
 \hline
 (+7)
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]



# Start with: Negative minus negative

$$\begin{array}{r}
 (-5) \\
 - (-2) \\
 \hline
 (-3)
 \end{array}
 \qquad
 \begin{array}{r}
 \underline{1011} \\
 - \underline{1110} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]

# Convert to: Negative plus positive

$$\begin{array}{r}
 (-5) \\
 - (-2) \\
 \hline
 (-3)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{1011} \\
 - \boxed{1110} \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 \boxed{1011} \\
 + \boxed{0010} \\
 \hline
 \boxed{1101}
 \end{array}
 \quad
 \begin{array}{r}
 (-5) \\
 + (+2) \\
 \hline
 (-3)
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1


[ Figure 3.10 from the textbook ]



# Take Home Message

- **Subtraction can be performed by simply negating the second number and adding it to the first, regardless of the signs of the two numbers.**
- **Thus, the same adder circuit can be used to perform both addition and subtraction !!!**


# Adder/subtractor unit

 

[ Figure 3.12 from the textbook ]



# XOR Tricks

control	$y$	out
0	0	0
0	1	1
1	0	1
1	1	0

  


# XOR as a repeater

control	$y$	out
0	0	0
0	1	1




# XOR as a repeater

control	$y$	out
0	0	0
0	1	1




# XOR as an inverter

control	$y$	out
1	0	1
1	1	0

 


# XOR as an inverter

control	$y$	out
1	0	1
1	1	0

 


# Addition: when control = 0

 

[ Figure 3.12 from the textbook ]




# Addition: when control = 0

 


[ Figure 3.12 from the textbook ]

# Addition: when control = 0

 


[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

 


[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

 


[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

 

[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

 


[ Figure 3.12 from the textbook ]

## **Addition Examples:**


**all inputs and outputs are given in  
2's complement representation**

# Addition: $5 + 6 = 11$

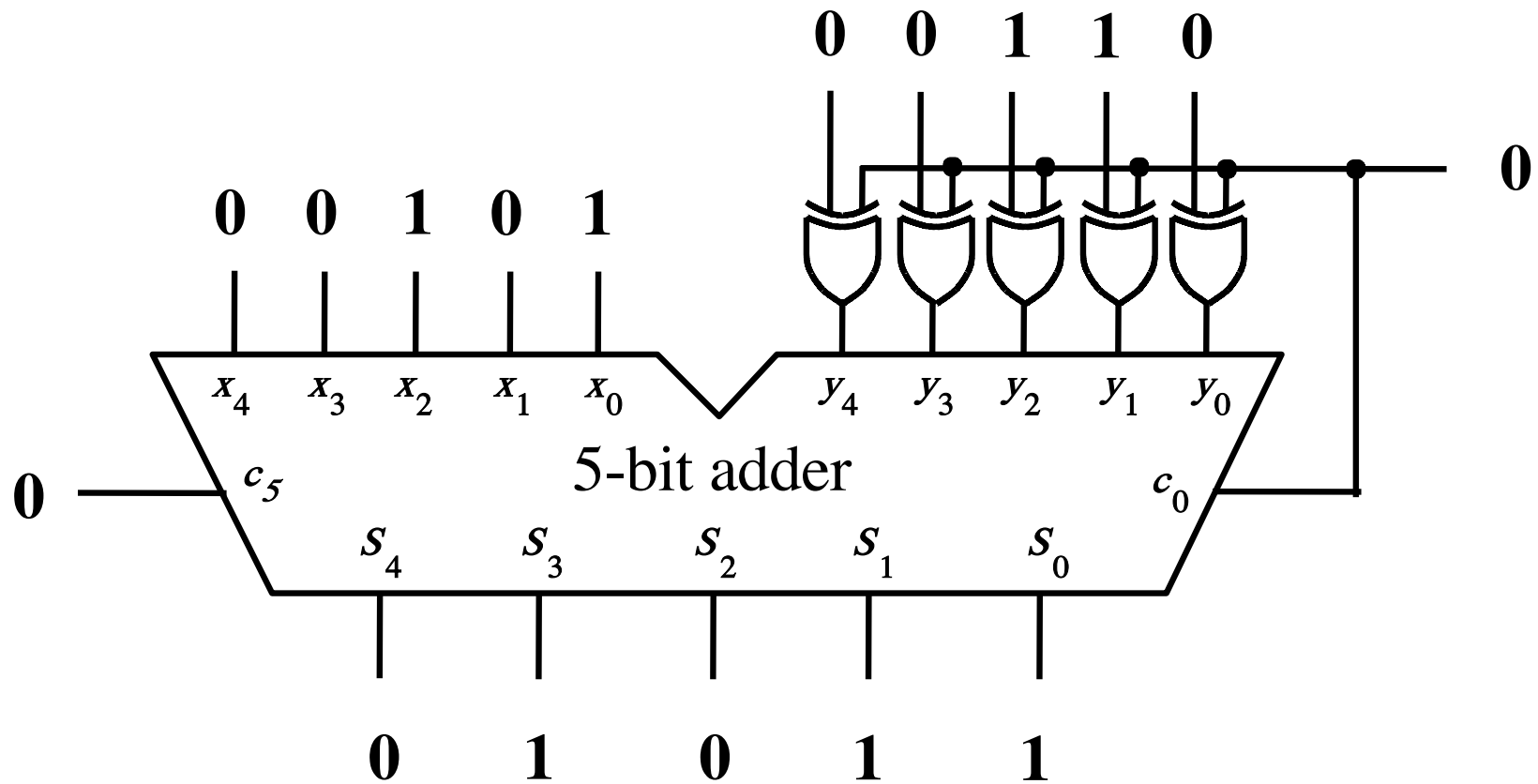





Addition: **5** + **6** = **11**

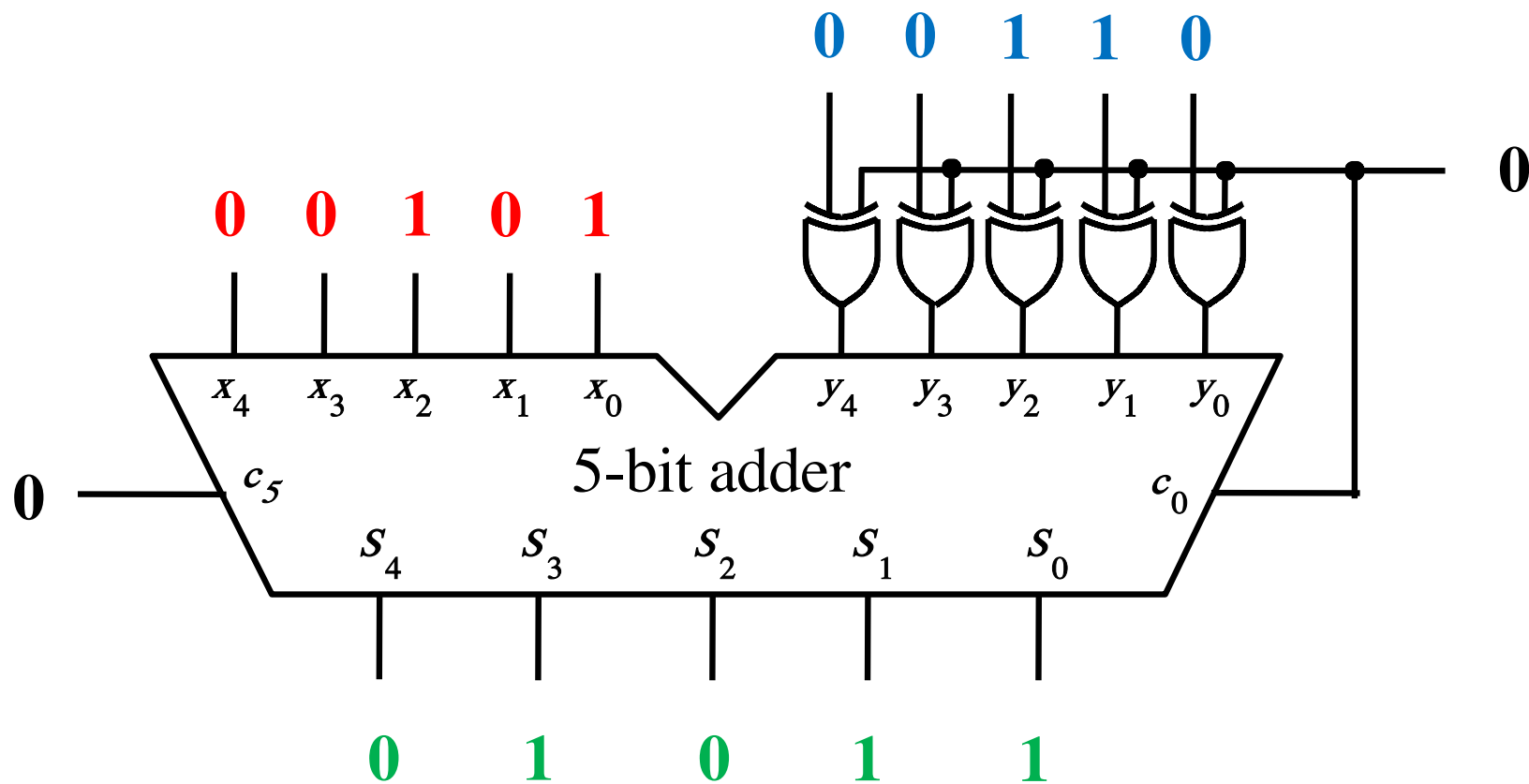


Addition: **5** + **6** = **11**

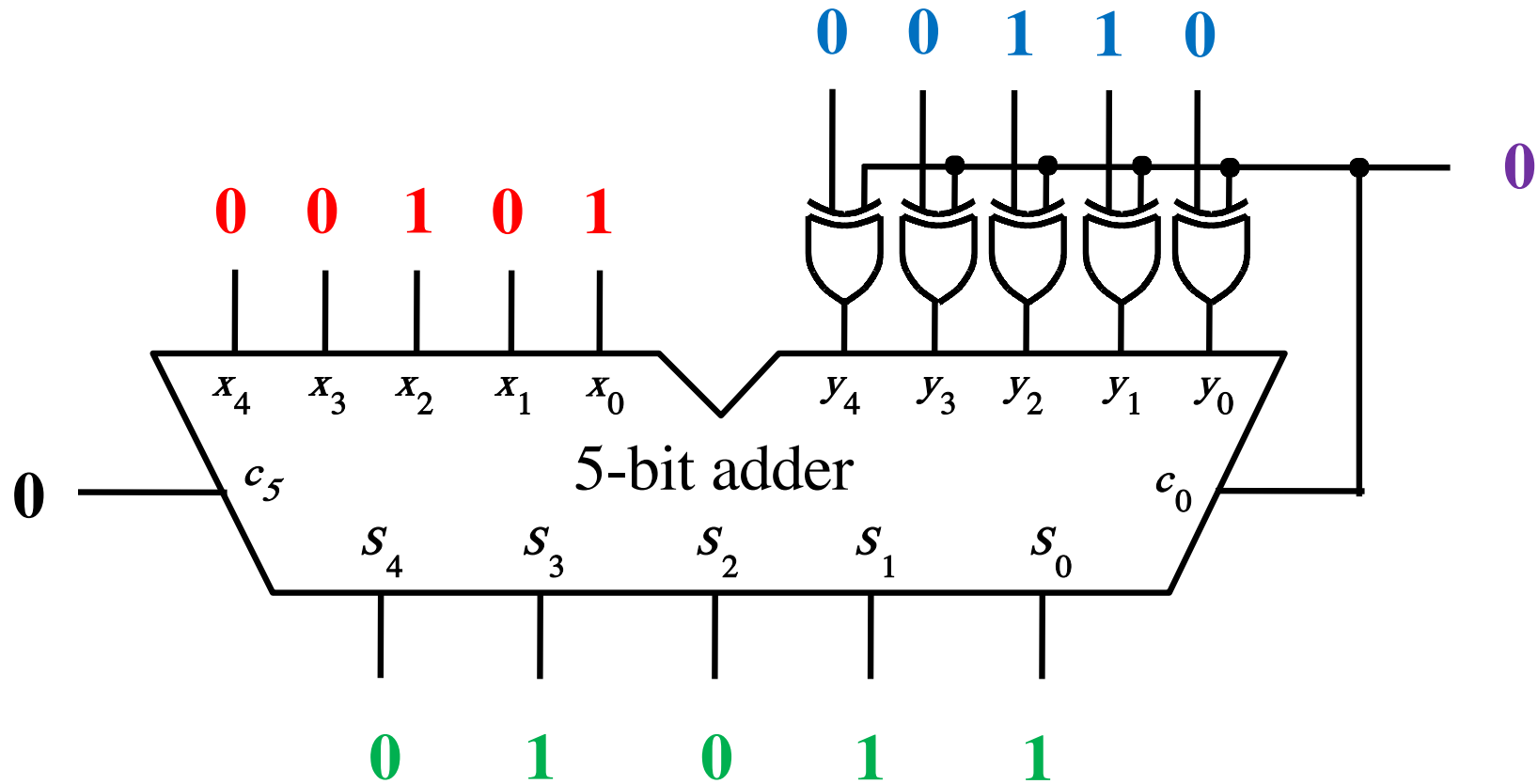

Addition: **5** + **6** = **11**

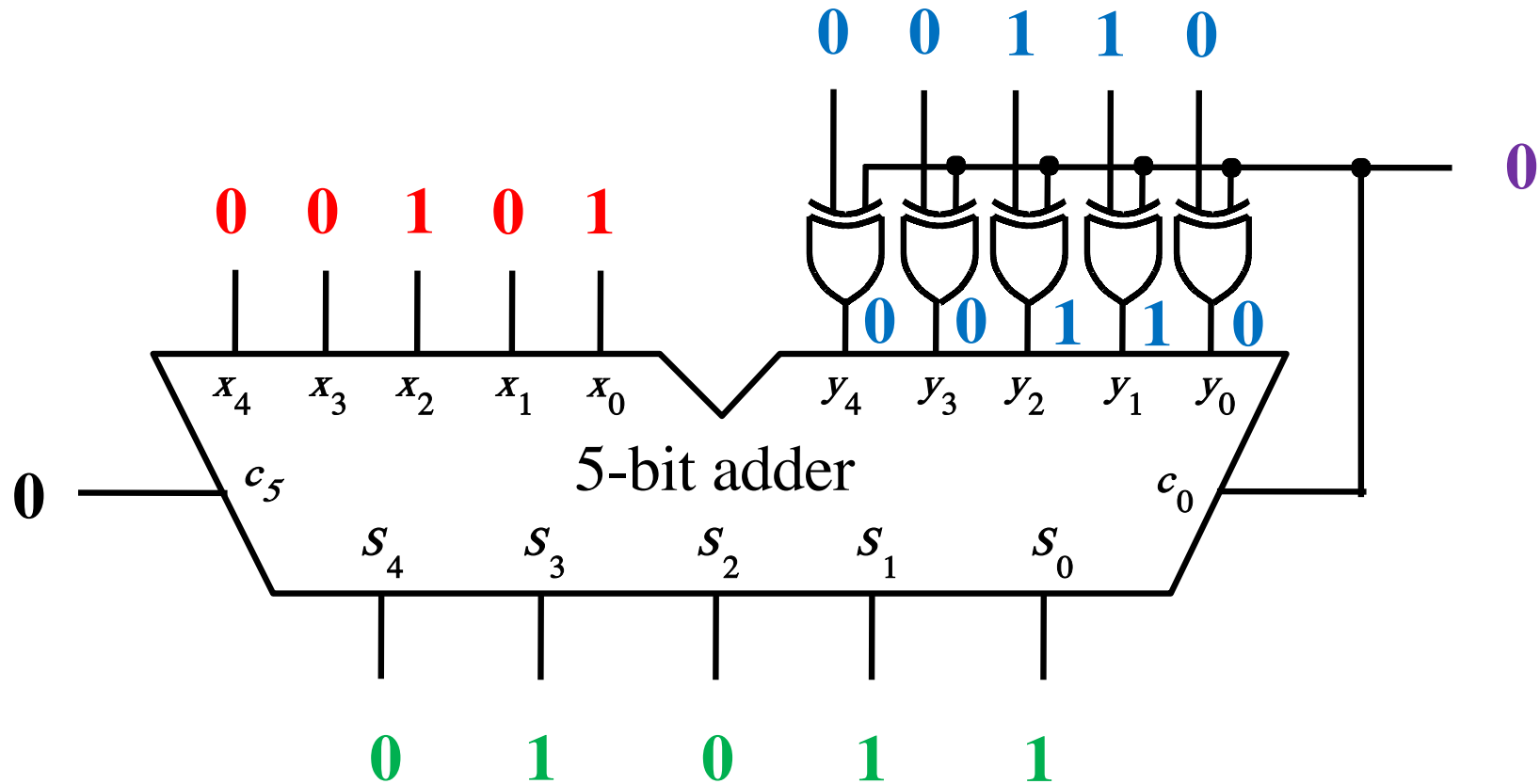


Addition: **5** + **6** = **11**

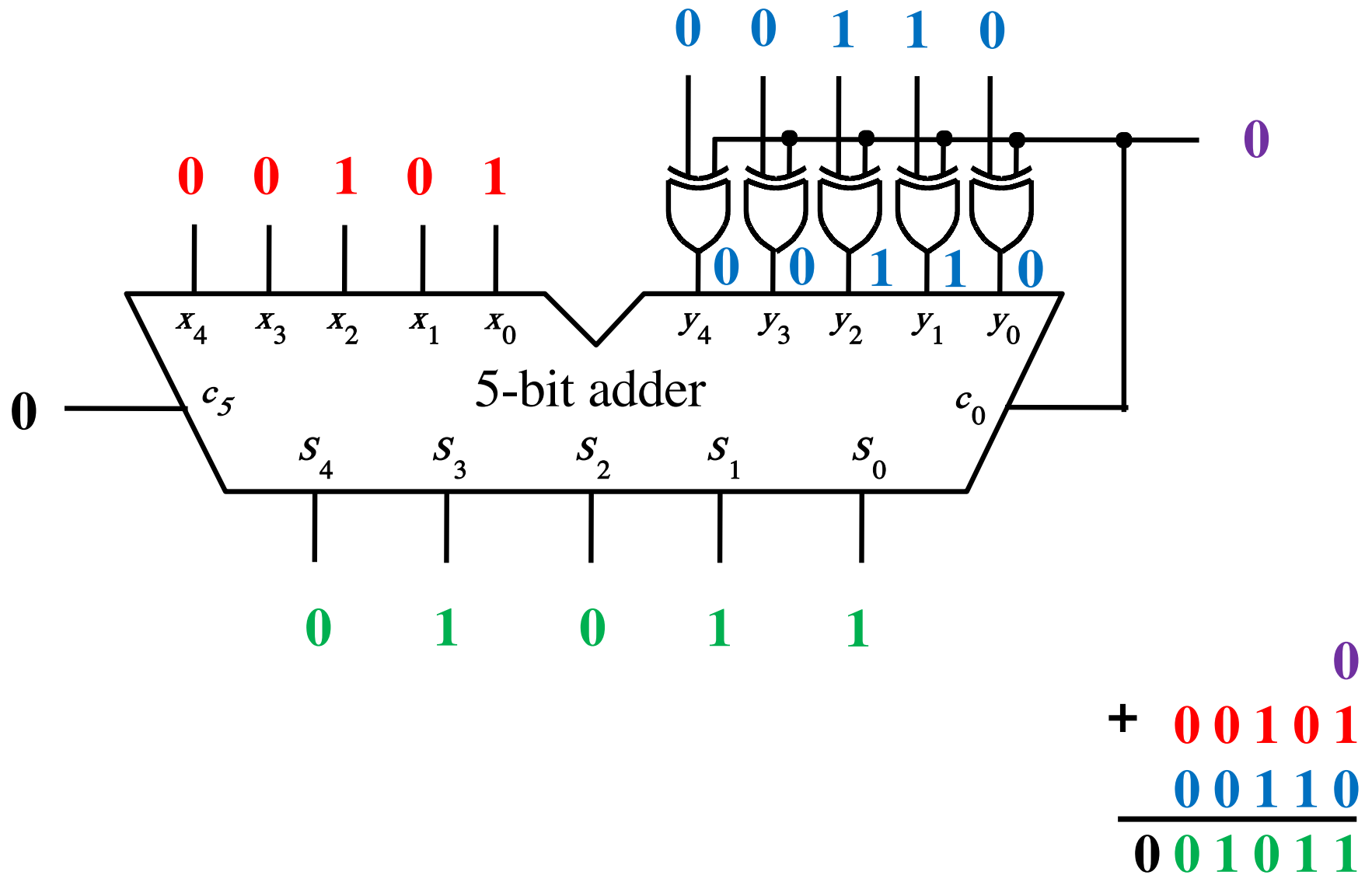





**Addition: 4 + (-7) = -3**

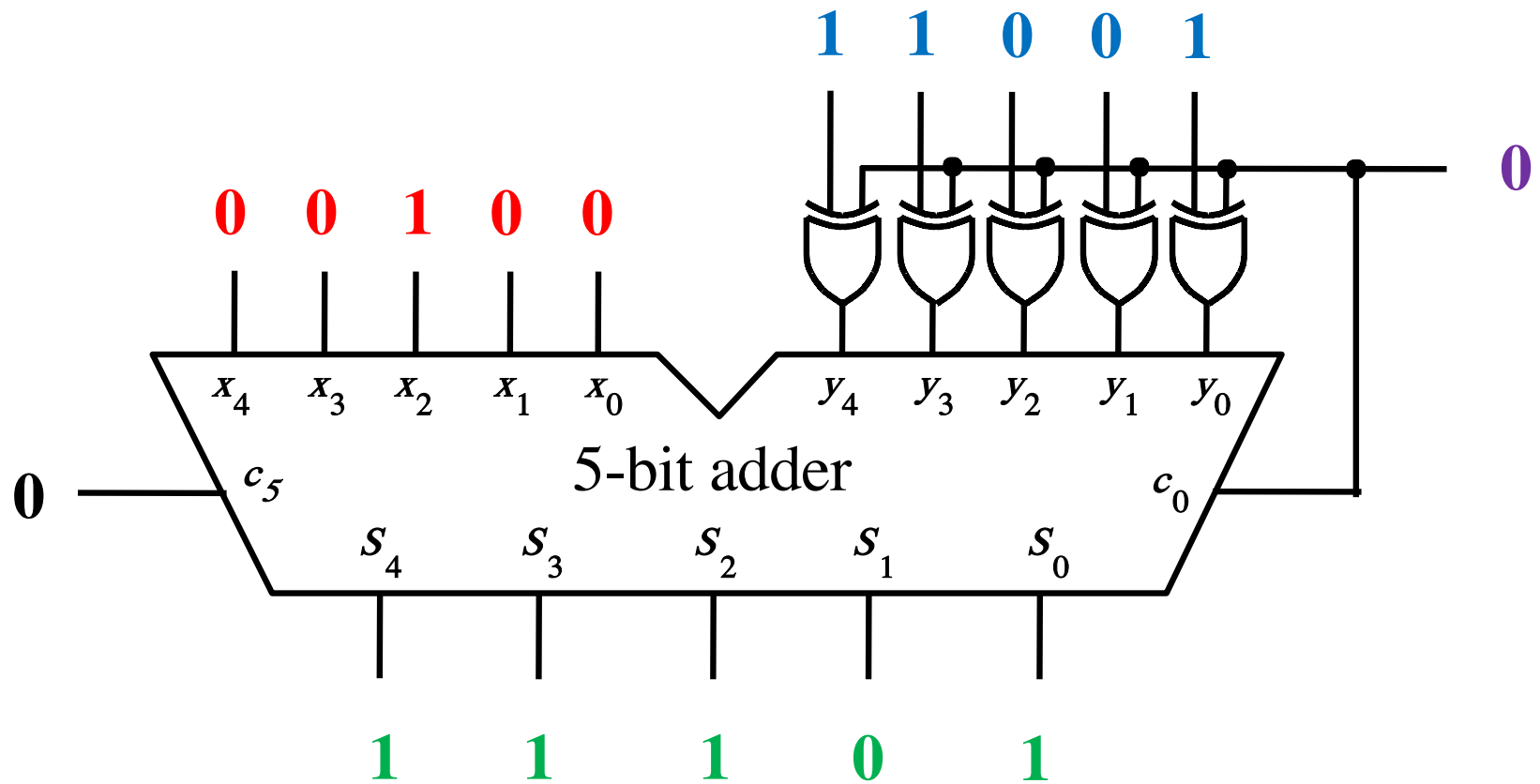

**Addition: 4 + (-7) = -3**

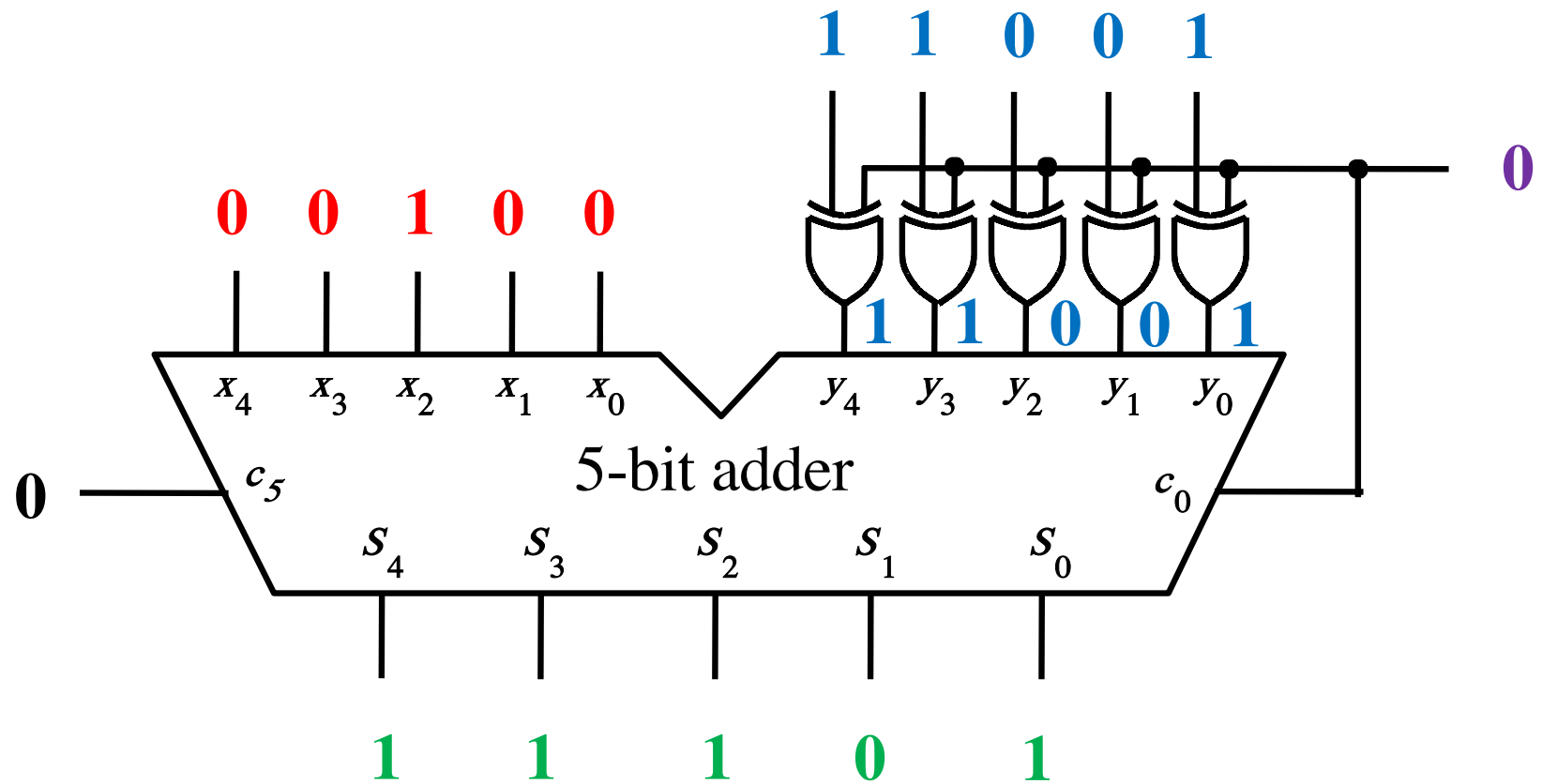

# Addition: $4 + (-7) = -3$

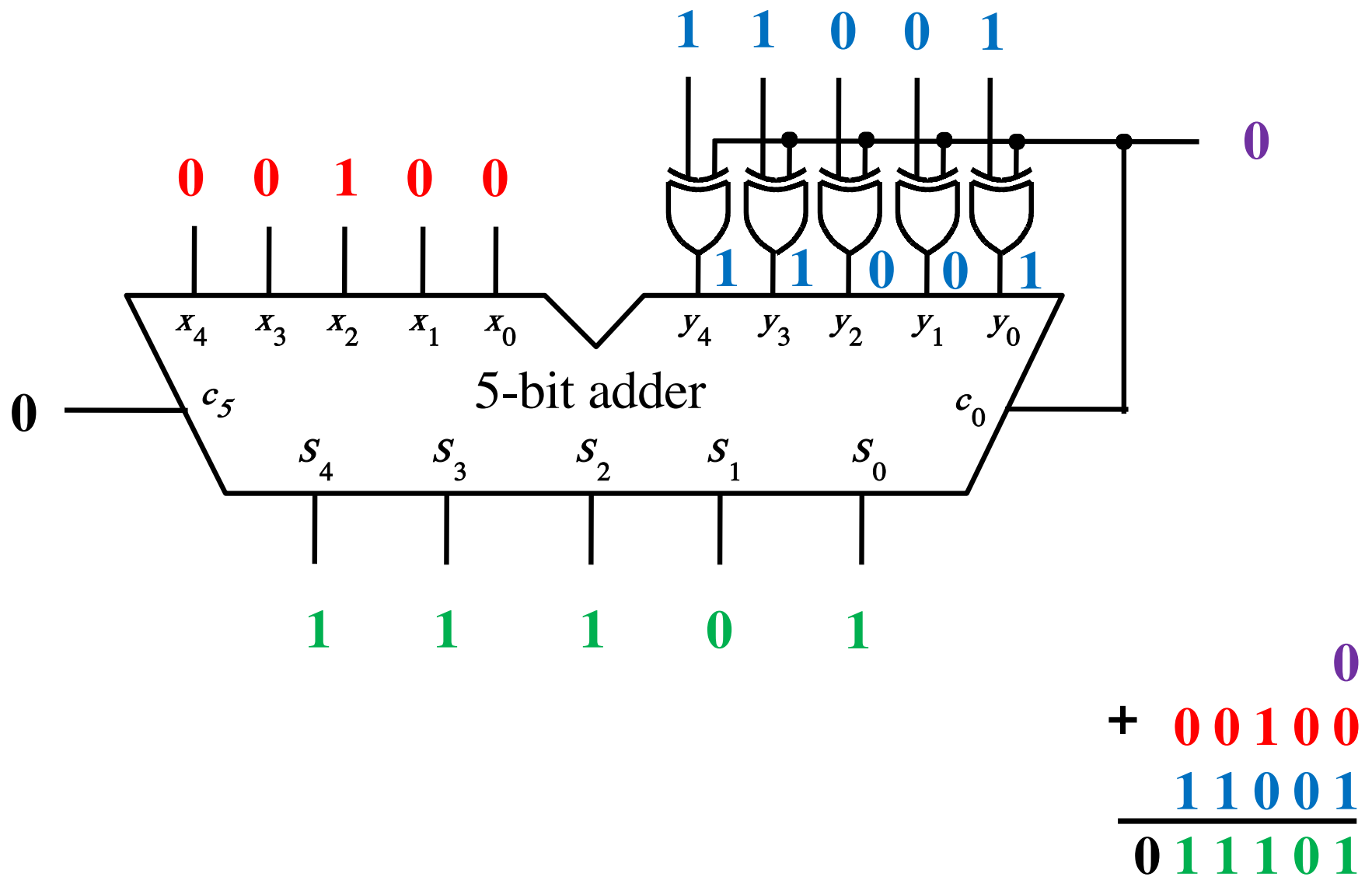





## **Subtraction Examples:**

**all inputs and outputs are given in  
2's complement representation**


Subtraction: **7** - **3** = **4**

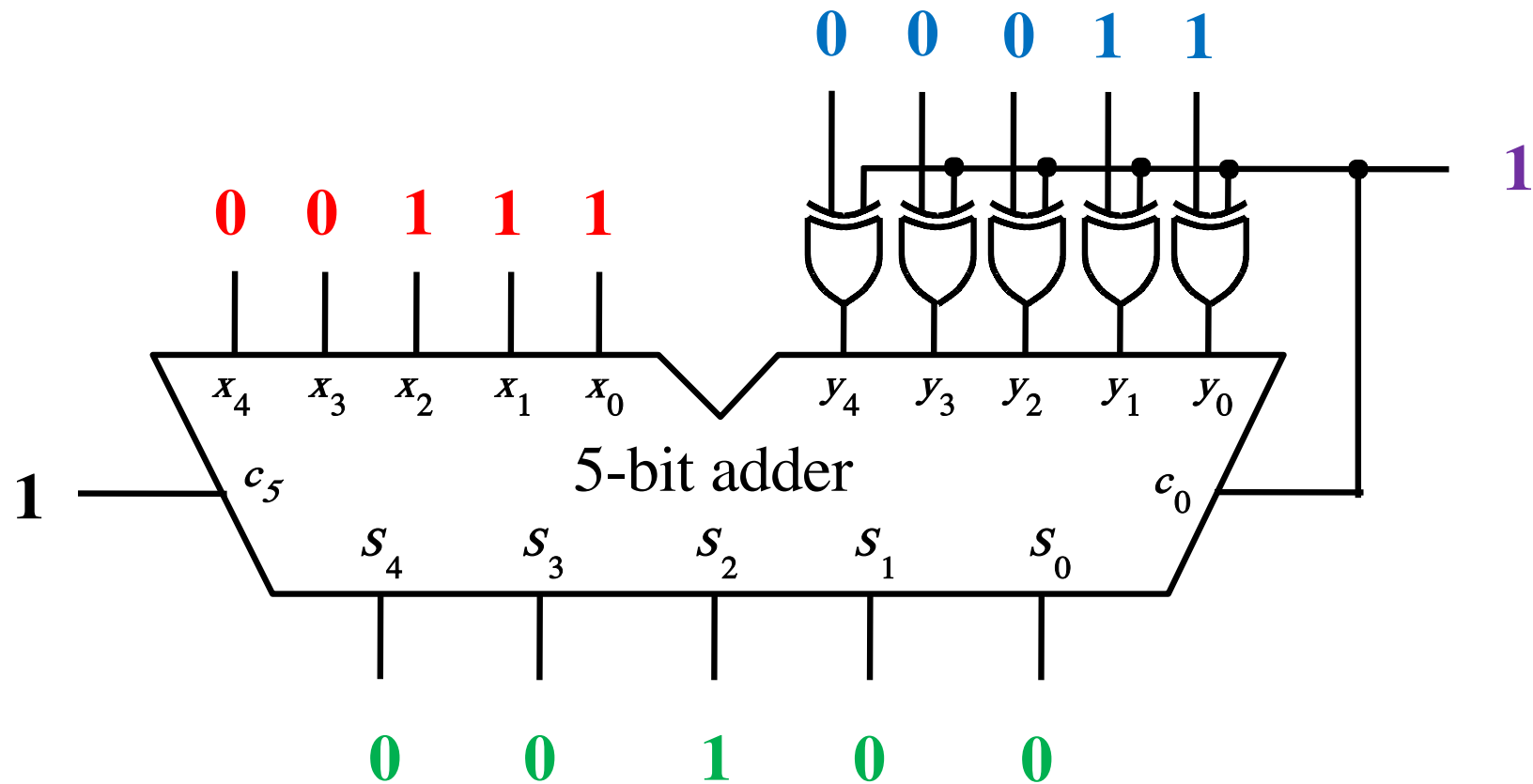

Subtraction: **7** - **3** = **4**

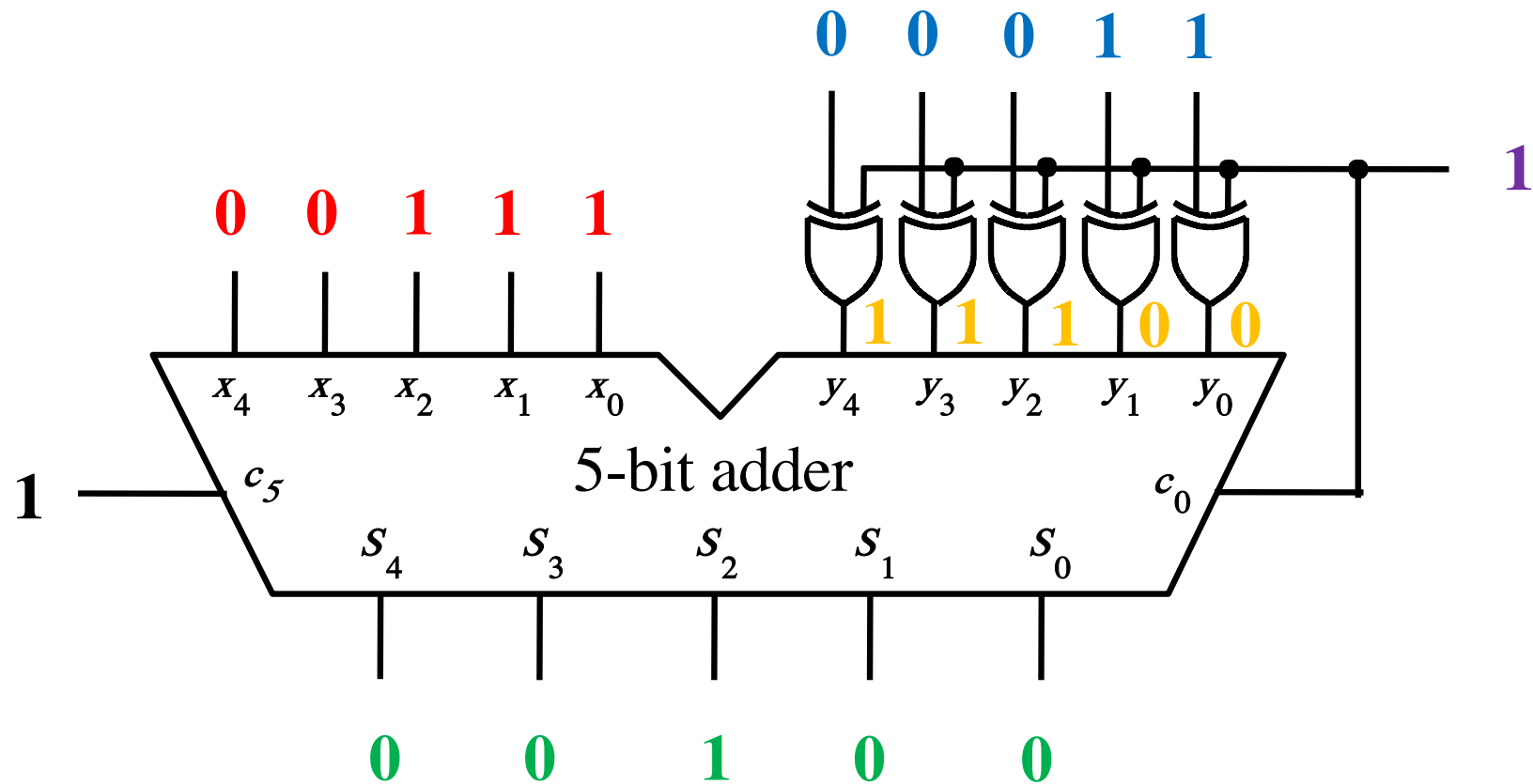


# Subtraction: $7 - 3 = 4$

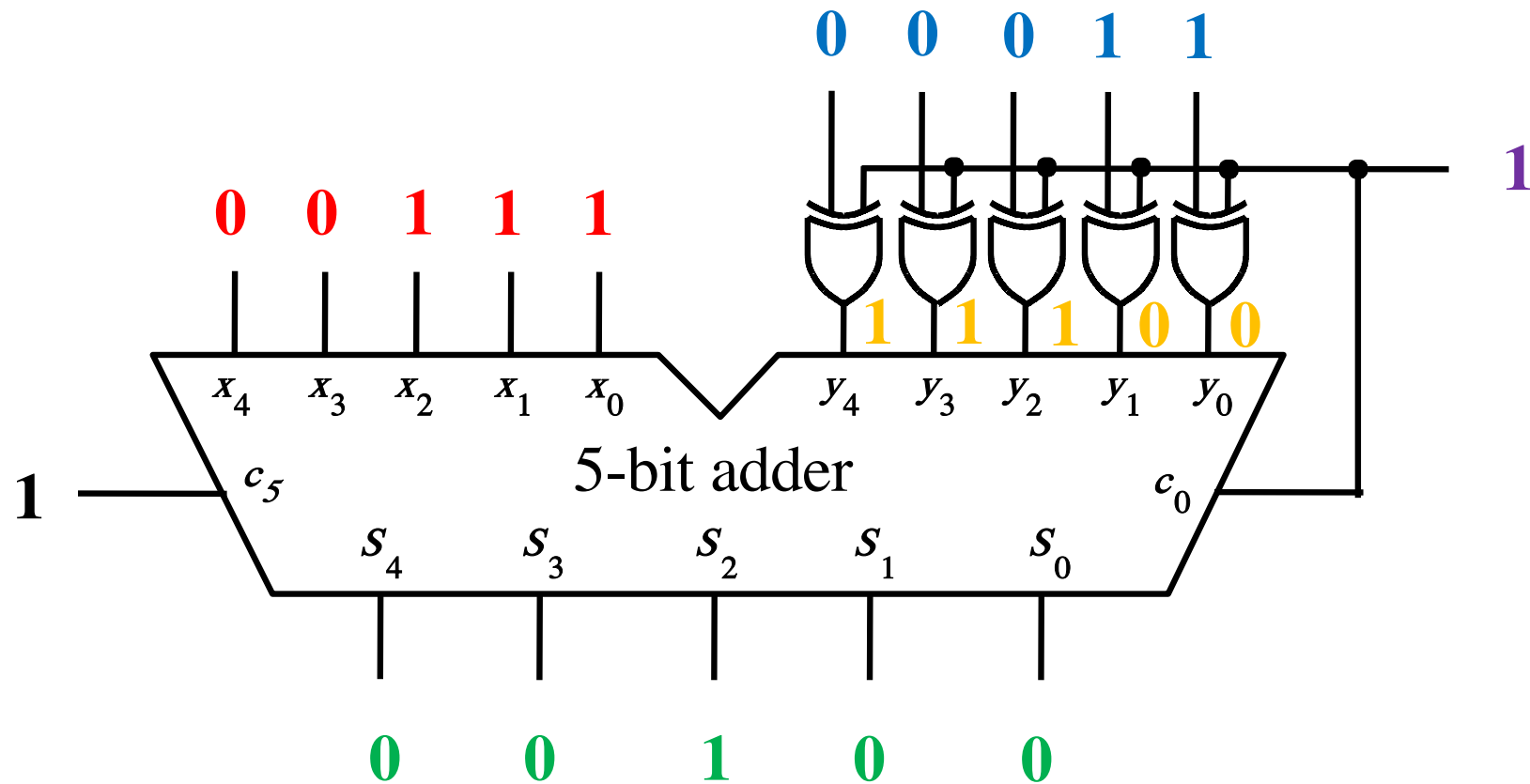


$$\begin{array}{r} & & & & & & & & & & & & & 1 \\ + & 0 & 0 & 1 & 1 & 1 & & & & & & & & \\ & 1 & 1 & 1 & 0 & 0 & & & & & & & & \\ \hline & 1 & 0 & 0 & 1 & 0 & 0 & & & & & & & \end{array}$$

# Subtraction: 7 - 3 = 4

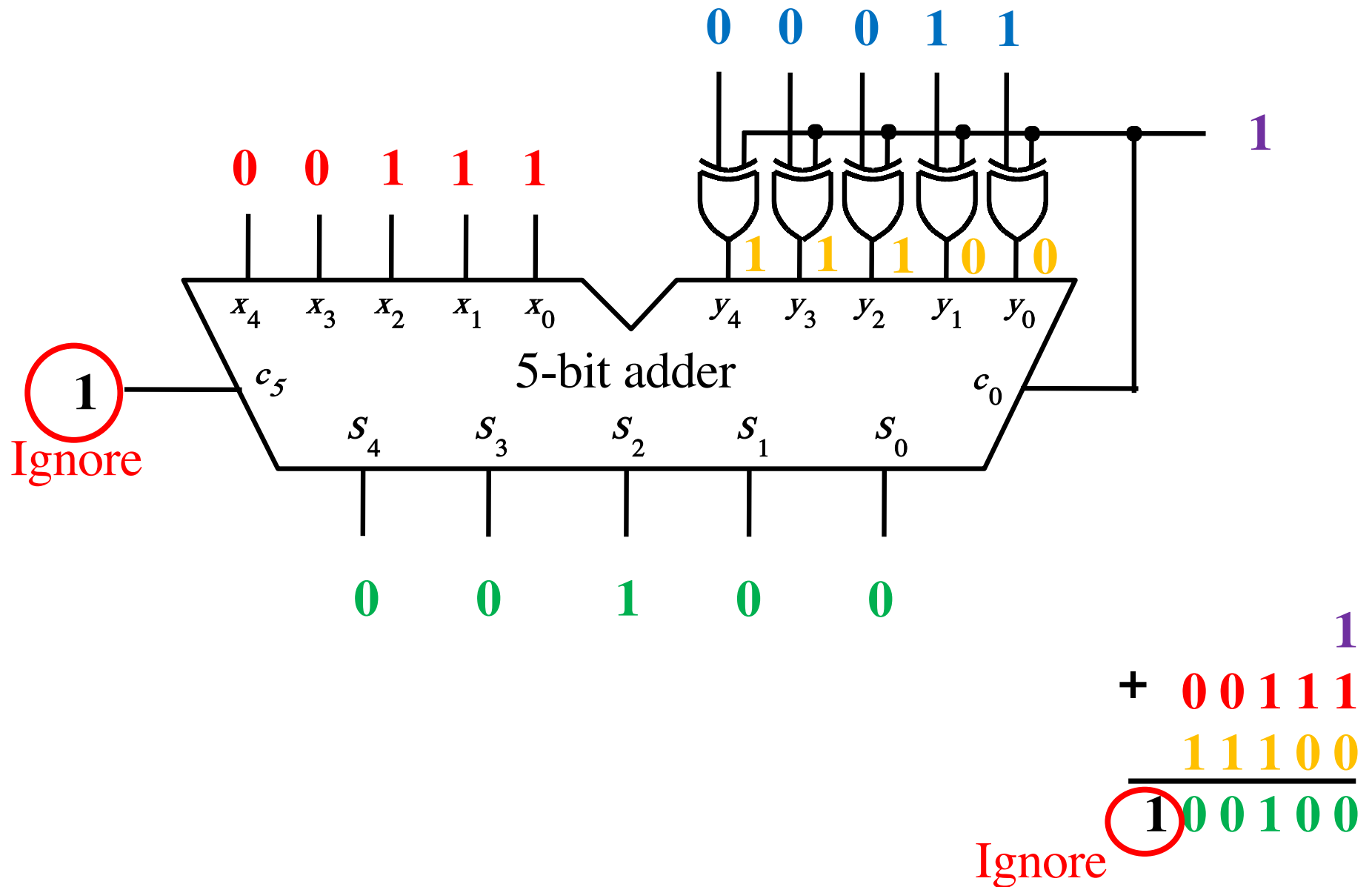




**Subtraction:  $(-2) - (-5) = 3$**

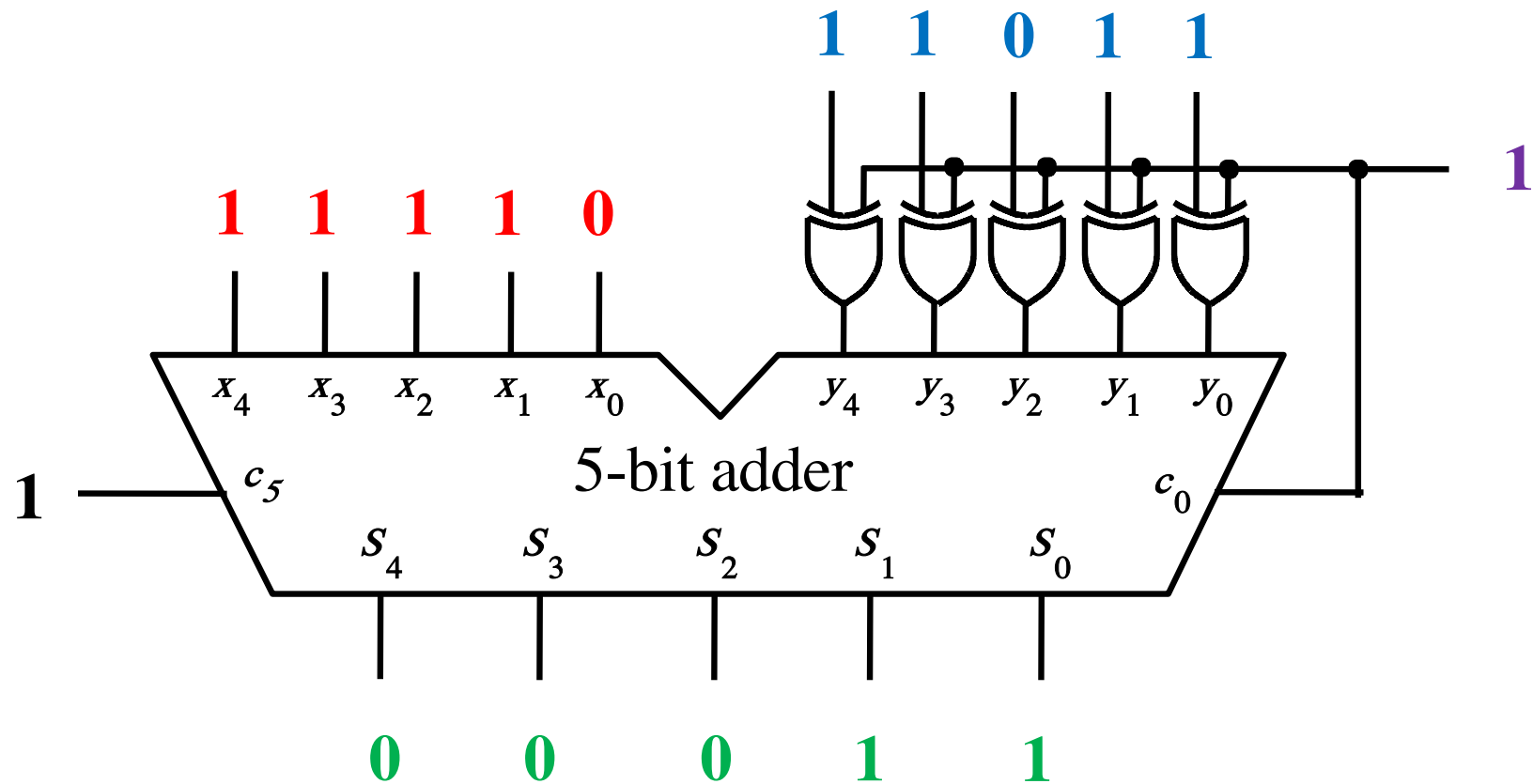


**Subtraction:  $(-2) - (-5) = 3$**

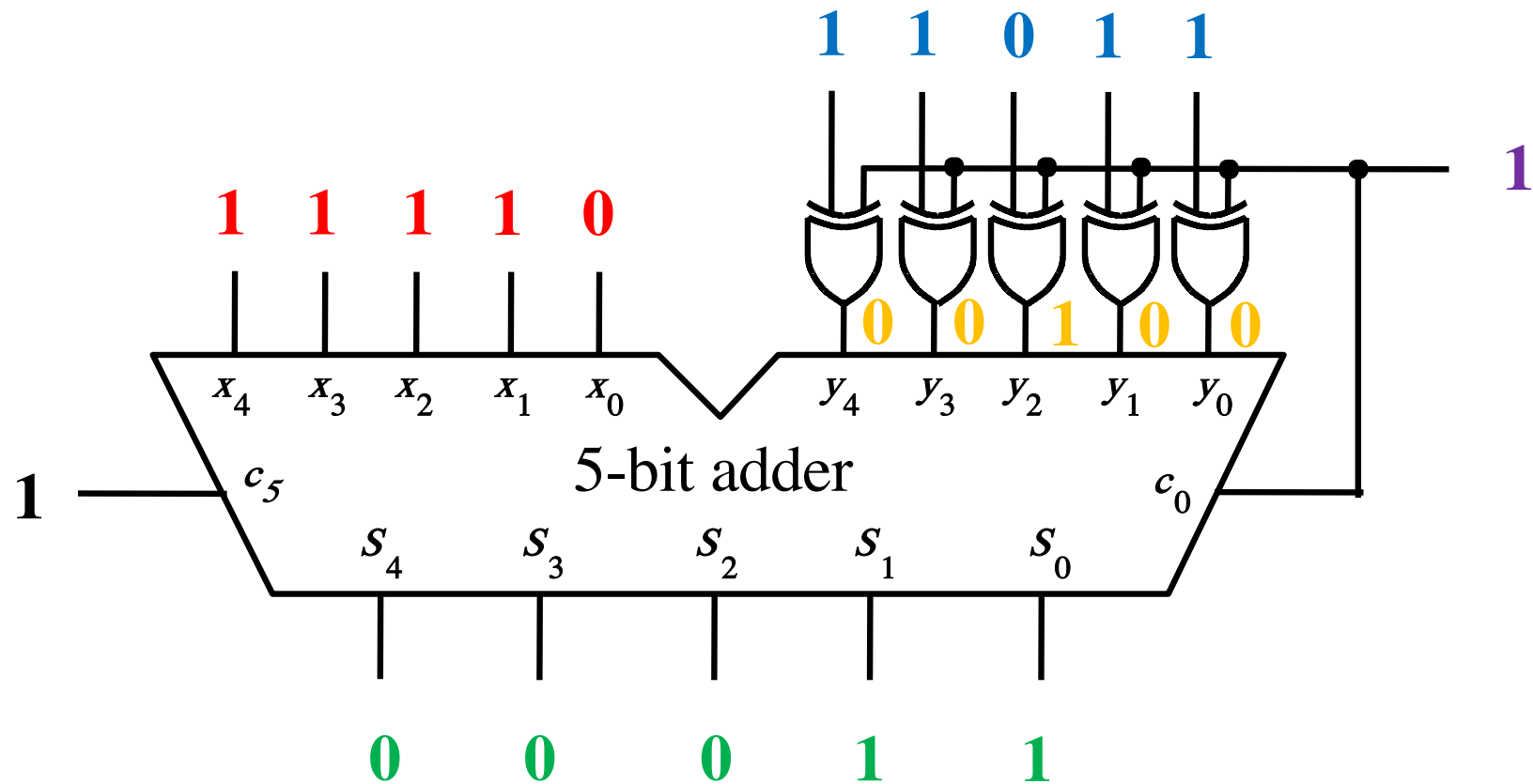




# Subtraction: $(-2) - (-5) = 3$

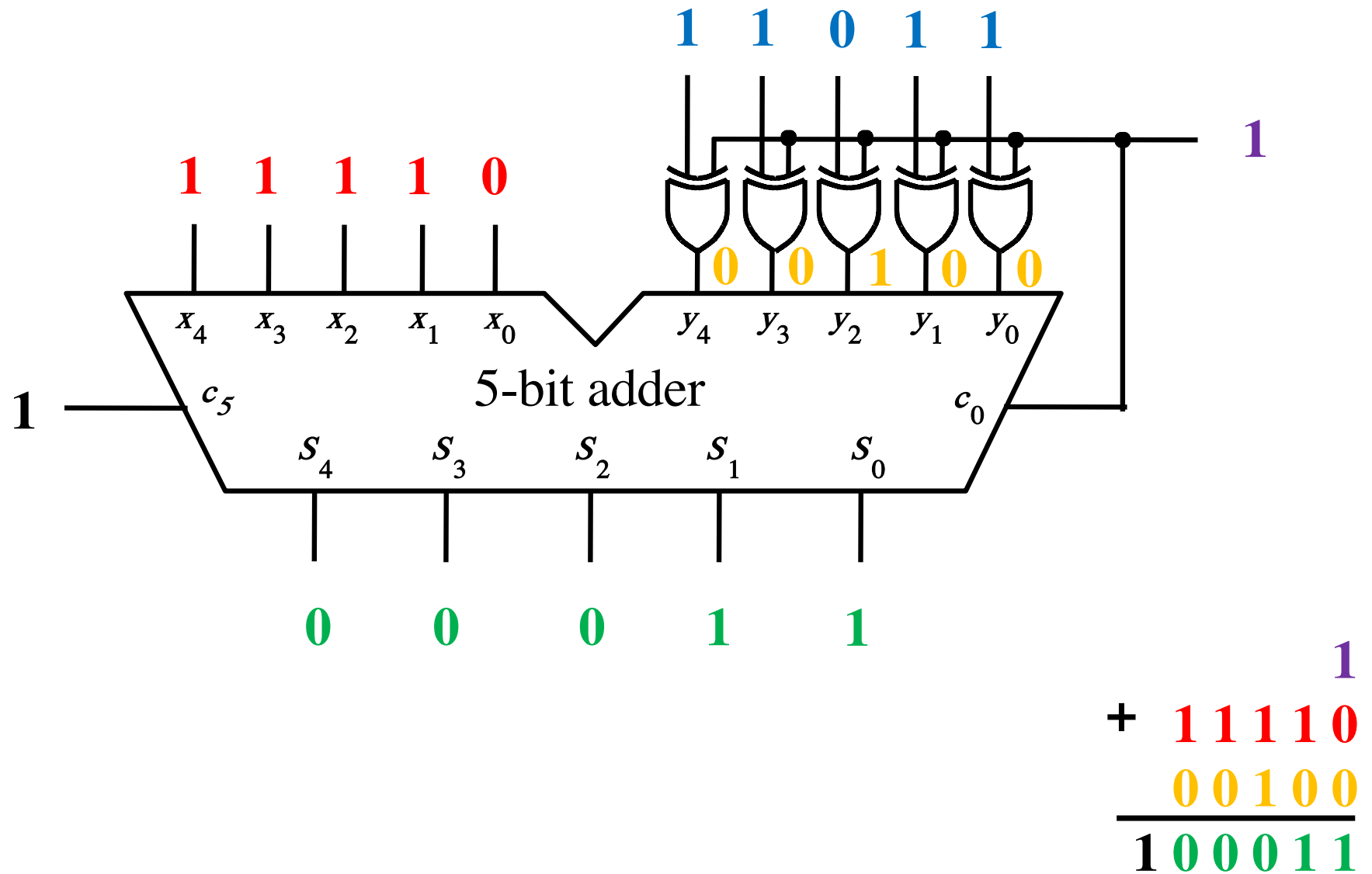

# Subtraction: $(-2) - (-5) = 3$

 

# Overflow Detection

# Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

# Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

In 2's complement, both +9 and -9 are not representable with 4 bits.

# Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad \begin{array}{r} 01100 \\ + 0111 \\ \hline 0010 \\ + 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad \begin{array}{r} 00000 \\ + 1001 \\ \hline 0010 \\ + 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad \begin{array}{r} 11100 \\ + 0111 \\ \hline 1110 \\ + 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad \begin{array}{r} 10000 \\ + 1001 \\ \hline 1110 \\ + 10111 \end{array}$$

Include the carry bits:  $c_4 c_3 c_2 c_1 c_0$

# Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{01}100 \\ 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{00}000 \\ 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{11}100 \\ 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{10}000 \\ 1001 \\ 1110 \\ \hline 10111 \end{array}$$

Include the carry bits:  $\boxed{c_4 c_3} c_2 c_1 c_0$

# Examples of determination of overflow

$$c_4 = 0$$

$$c_3 = 1$$

$$\begin{array}{r}
 (+7) \\
 + (+2) \\
 \hline
 (+9)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{01}100 \\
 + \quad 0111 \\
 \quad 0010 \\
 \hline
 1001
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (+2) \\
 \hline
 (-5)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{00}000 \\
 + \quad 1001 \\
 \quad 0010 \\
 \hline
 1011
 \end{array}
 \quad
 \begin{array}{l}
 c_4 = 0 \\
 c_3 = 0
 \end{array}$$

$$c_4 = 1$$

$$c_3 = 1$$

$$\begin{array}{r}
 (+7) \\
 + (-2) \\
 \hline
 (+5)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{11}100 \\
 + \quad 0111 \\
 \quad 1110 \\
 \hline
 10101
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (-2) \\
 \hline
 (-9)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{10}000 \\
 + \quad 1001 \\
 \quad 1110 \\
 \hline
 10111
 \end{array}
 \quad
 \begin{array}{l}
 c_4 = 1 \\
 c_3 = 0
 \end{array}$$

Include the carry bits:  $\boxed{c_4 c_3} c_2 c_1 c_0$



# Examples of determination of overflow

$$c_4 = 0$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{01}100 \\ 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{00}000 \\ 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$c_4 = 0$$

$$c_3 = 0$$

$$c_4 = 1$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{11}100 \\ 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{10}000 \\ 1001 \\ 1110 \\ \hline 10111 \end{array}$$

$$c_4 = 1$$

$$c_3 = 0$$

Overflow occurs only in these two cases.

# Examples of determination of overflow

$$c_4 = 0$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$\begin{array}{r} \boxed{01}100 \\ + 0111 \\ \hline 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} \boxed{00}000 \\ + 1001 \\ \hline 0010 \\ \hline 1011 \end{array}$$

$$c_4 = 0$$

$$c_3 = 0$$

$$c_4 = 1$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$\begin{array}{r} \boxed{11}100 \\ + 0111 \\ \hline 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} \boxed{10}000 \\ + 1001 \\ \hline 1110 \\ \hline 10111 \end{array}$$

$$c_4 = 1$$

$$c_3 = 0$$

$$\text{Overflow} = c_3 \bar{c}_4 + \bar{c}_3 c_4$$

# Examples of determination of overflow

$$c_4 = 0$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$\begin{array}{r} \boxed{01}100 \\ + 0111 \\ \hline 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} \boxed{00}000 \\ + 1001 \\ \hline 0010 \\ \hline 1011 \end{array}$$

$$c_4 = 0$$

$$c_3 = 0$$

$$c_4 = 1$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$\begin{array}{r} \boxed{11}100 \\ + 0111 \\ \hline 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} \boxed{10}000 \\ + 1001 \\ \hline 1110 \\ \hline 10111 \end{array}$$

$$c_4 = 1$$

$$c_3 = 0$$

$$\text{Overflow} = \underbrace{c_3 \bar{c}_4 + \bar{c}_3 c_4}_{\text{XOR}}$$


# Calculating overflow for 4-bit numbers with only three significant bits

$$\begin{aligned}\text{Overflow} &= c_3 \bar{c}_4 + \bar{c}_3 c_4 \\ &= c_3 \oplus c_4\end{aligned}$$


# Calculating overflow for n-bit numbers with only n-1 significant bits

$$\text{Overflow} = c_{n-1} \oplus c_n$$

# Detecting Overflow

 
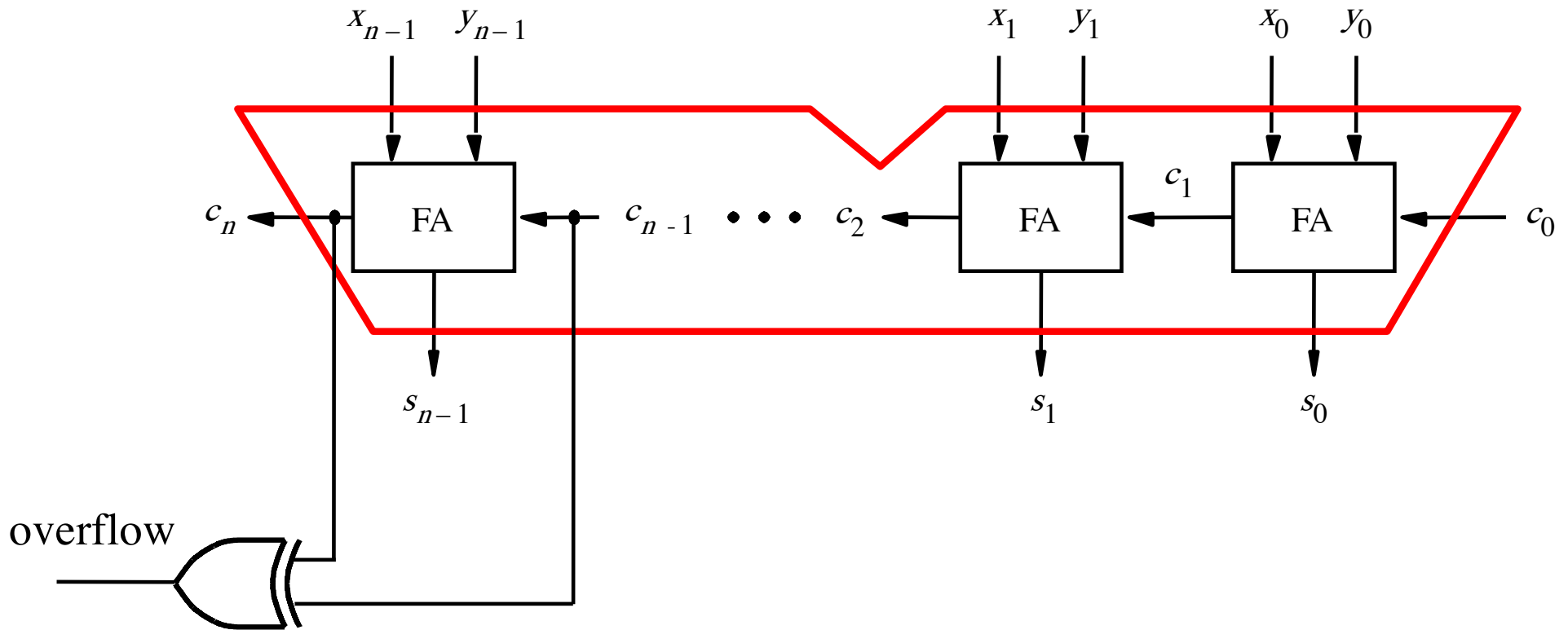
# Detecting Overflow (with one extra XOR)




# **Detecting Overflow**

## **(alternative method)**

Used if you don't have access to the internal carries of the adder.



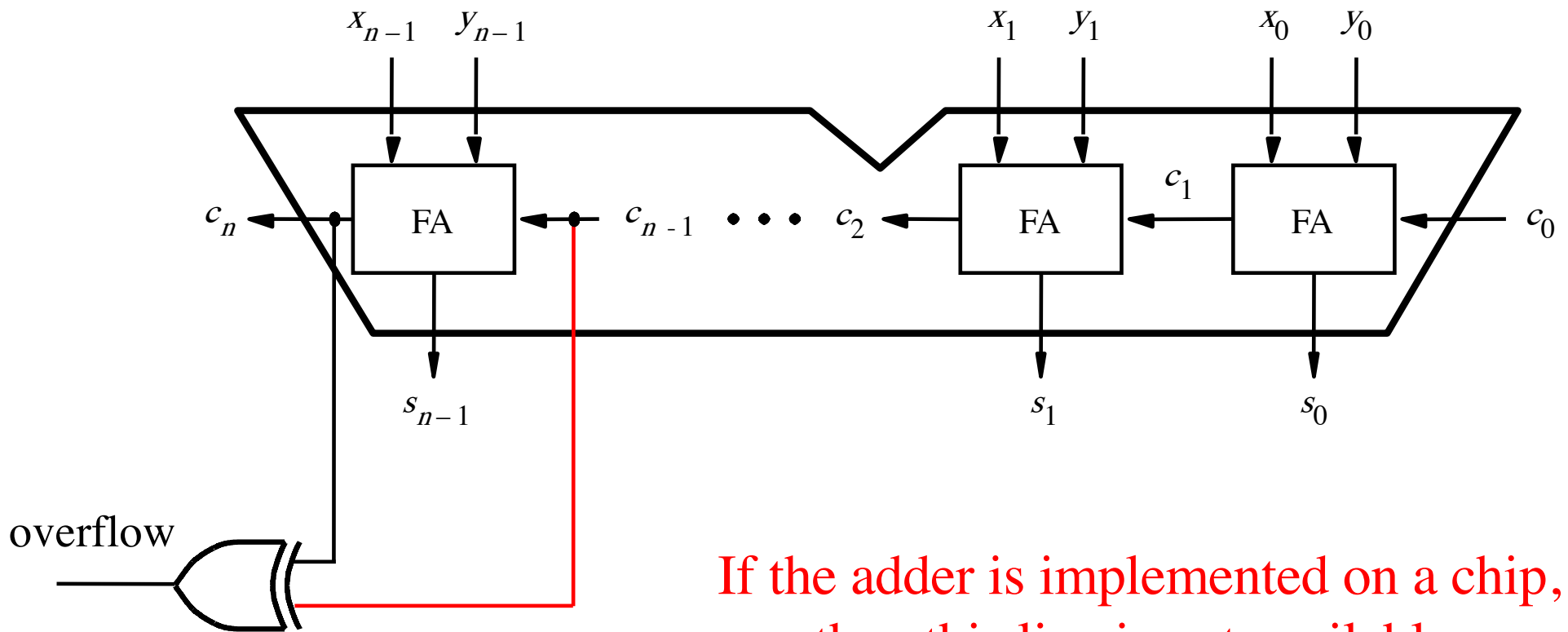
# Detecting Overflow (with one extra XOR)




If the adder is implemented on a chip,  
then this line is not available.  
So the first method can't be used.

# Overflow Detection: 4-bits

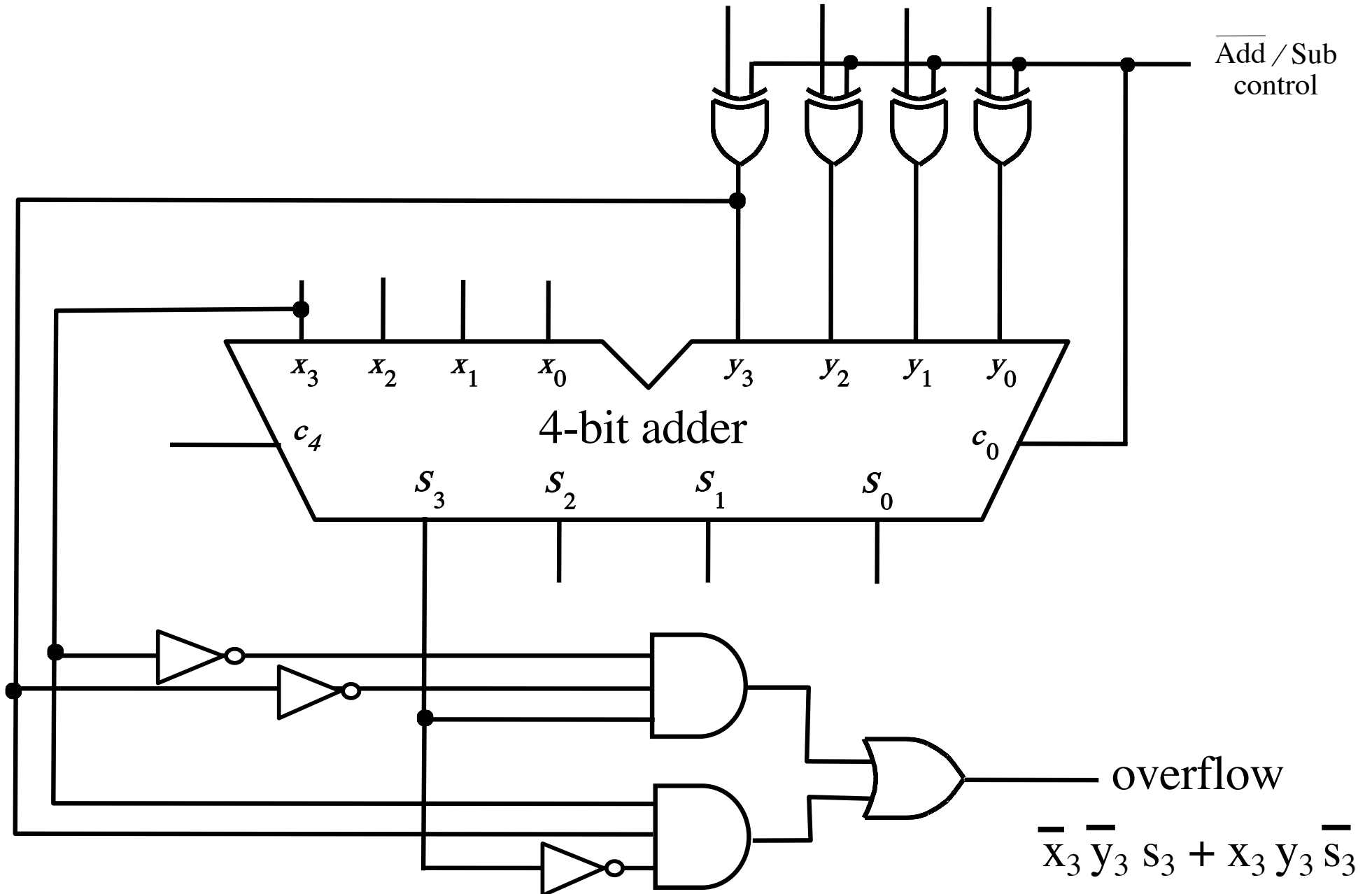


# Overflow Detection: 5-bits

 


# **A ripple-carry adder**

 
# How long does it take to compute all sum bits and all carry bits?


 
# Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 


(b) Detailed diagram
 
# Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 


(b) Detailed diagram
 
# Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 

(b) Detailed diagram



 
# How long does it take to compute all sum bits and all carry bits in this case?




It takes  $3n$  gate delays?

# Delays through the Full-Adder circuit

 


[ Figure 3.3c from the textbook ]

# Delays through the Full-Adder circuit

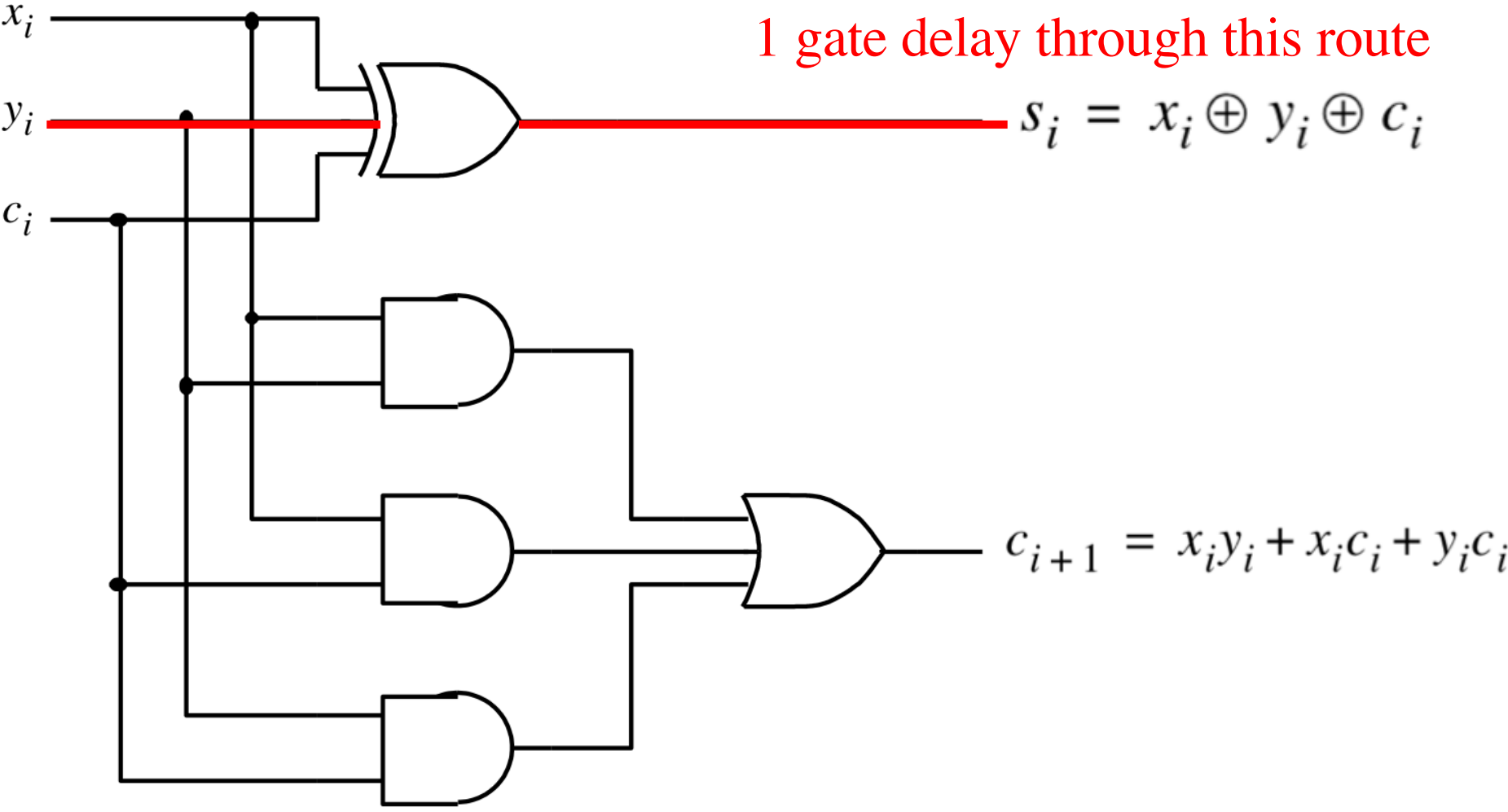


[ Figure 3.3c from the textbook ]

# Delays through the Full-Adder circuit

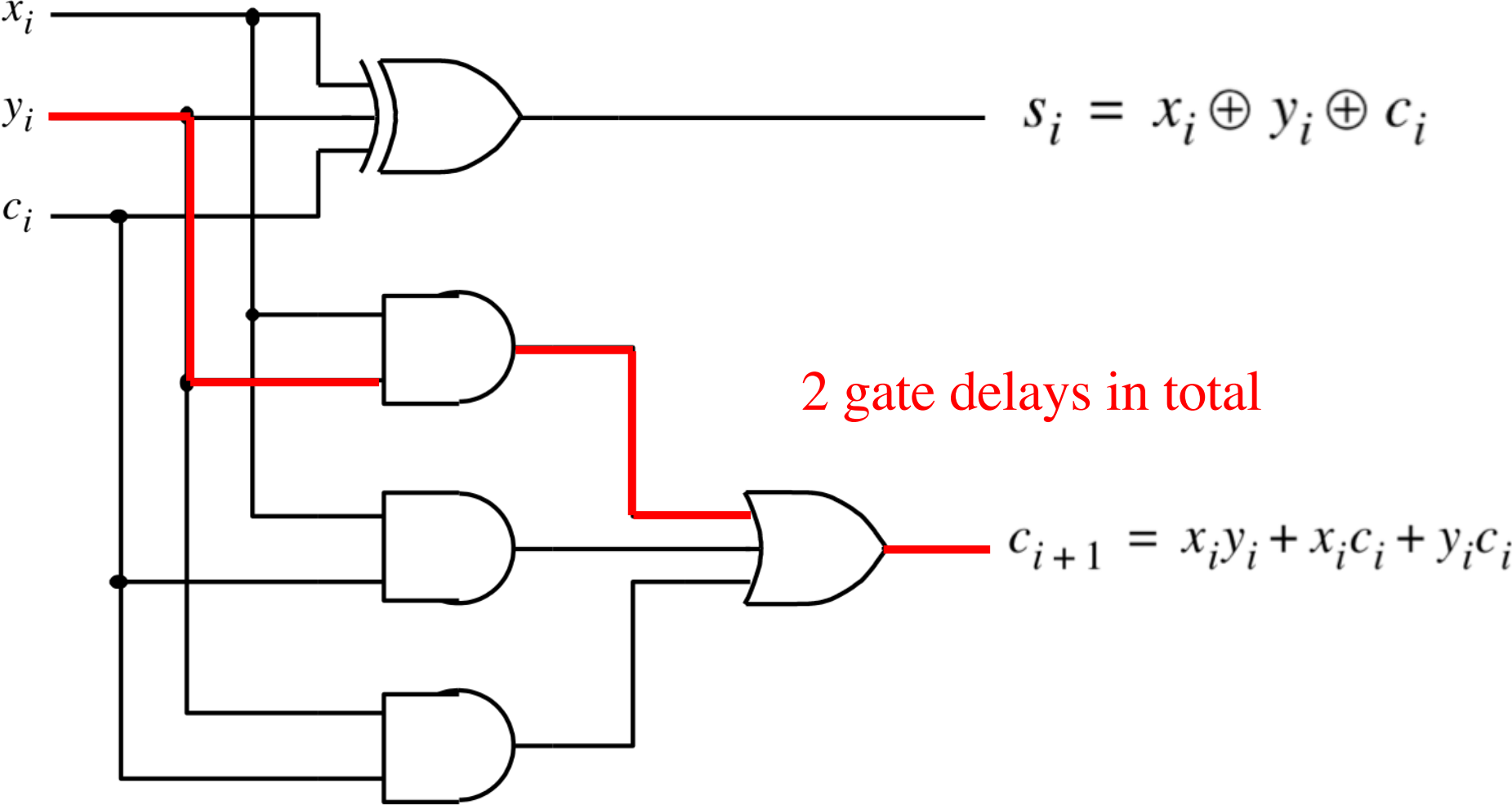

[ Figure 3.3c from the textbook ]
 
# How long does it take to compute all sum bits and all carry bits?



It takes  $2n$  gate delays?

# **Can we perform addition even faster?**


**The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.**

# **Can we perform addition even faster?**

**The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.**

**To accomplish this goal we will have to redesign the full-adder circuit yet again.**


# The Full-Adder Circuit

 

[ Figure 3.3c from the textbook ]



# The Full-Adder Circuit

 

# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

# Decomposing the Carry Expression


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

# Decomposing the Carry Expression

$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$C_{i+1} = x_i y_i + (x_i + y_i) c_i$$

 

# Another Way to Draw the Full-Adder Circuit


$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$C_{i+1} = x_i y_i + (x_i + y_i) c_i$$

 


# Another Way to Draw the Full-Adder Circuit

$$C_{i+1} = x_i y_i + (x_i + y_i)C_i$$

 
 
# Another Way to Draw the Full-Adder Circuit

$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} C_i$$




# Another Way to Draw the Full-Adder Circuit

g - generate


p - propagate
 
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} C_i$$





 
# Yet Another Way to Draw It (Just Rotate It)



# Now we can Build a Ripple-Carry Adder

 


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[ Figure 3.14 from the textbook ]

# Now we can Build a Ripple-Carry Adder

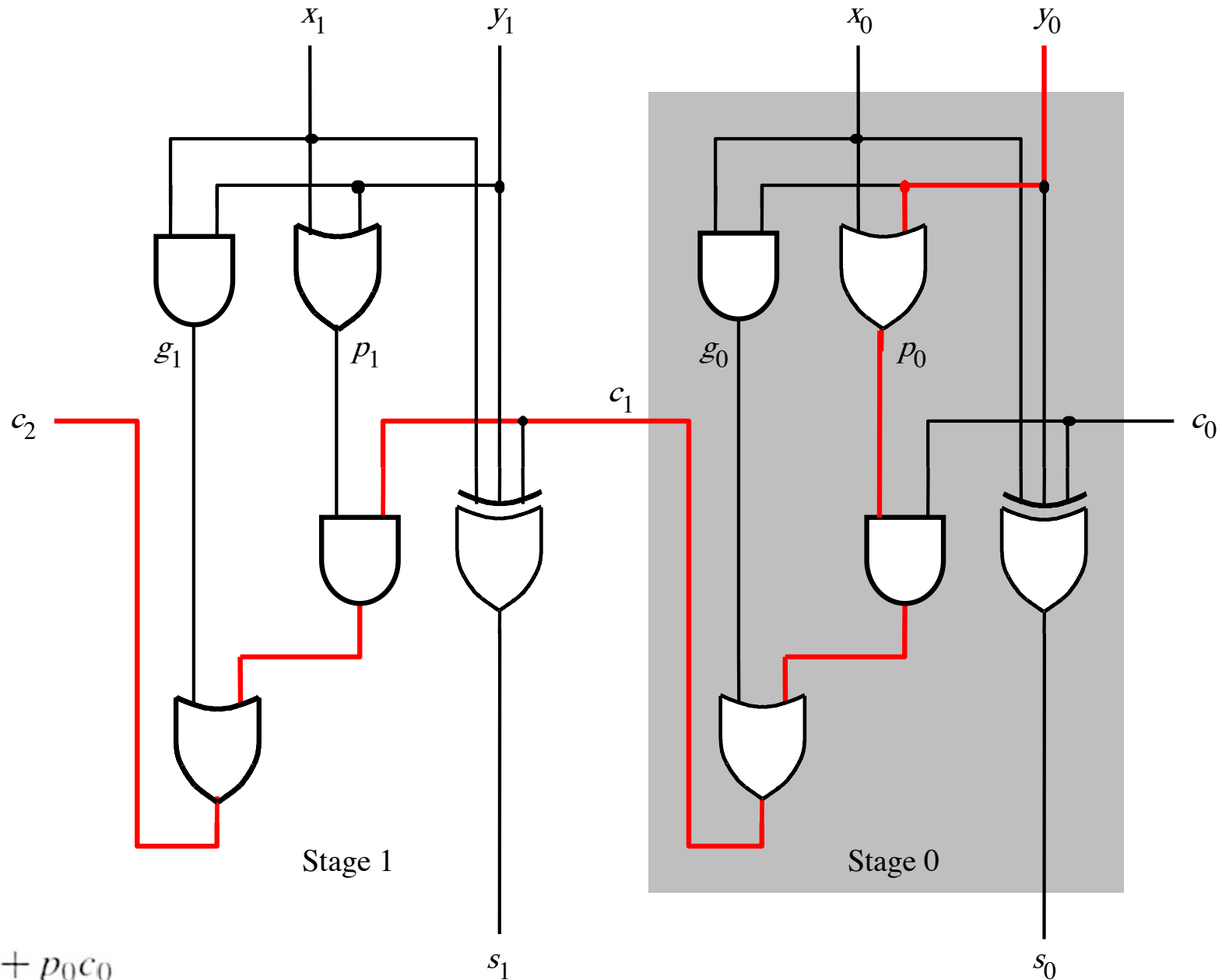


$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[ Figure 3.14 from the textbook ]
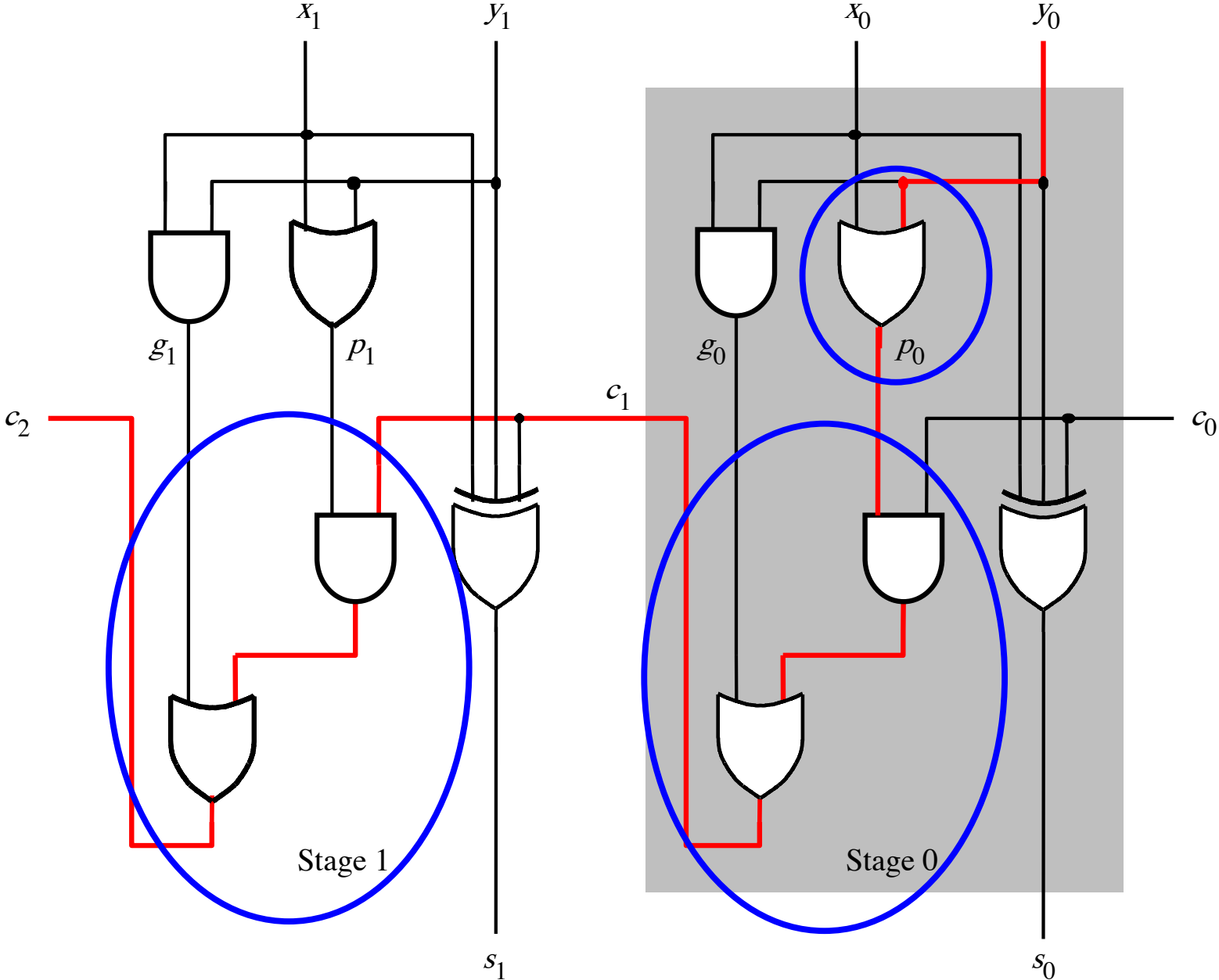
# 2-bit ripple-carry adder: 5 gate delays (1+2+2)


 
# n-bit ripple-carry adder: $2n+1$ gate delays



# **n-bit Ripple-Carry Adder**

- **It takes 1 gate delay to generate all  $g_i$  and  $p_i$  signals**
- **+2 more gate delays to generate carry 1**
- **+2 more gate delay to generate carry 2**
- **...**
- **+2 more gate delay to generate carry n**
- **Thus, the total delay through an n-bit ripple-carry adder is  $2n+1$  gate delays!**

# n-bit Ripple-Carry Adder

- It takes 1 gate delay to generate all  $g_i$  and  $p_i$  signals
- +2 more gate delays to generate carry 1
- +2 more gate delay to generate carry 2
- ...
- +2 more gate delay to generate carry n
- Thus, the total delay through an n-bit ripple-carry adder is  $2n+1$  gate delays!

This is slower by 1 than the original design?!

# **A carry-lookahead adder**



# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$


# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{P_i} c_i$$


(1 gate delay)    (1 gate delay)

# It takes 1 gate delay to compute all $p_i$ signals

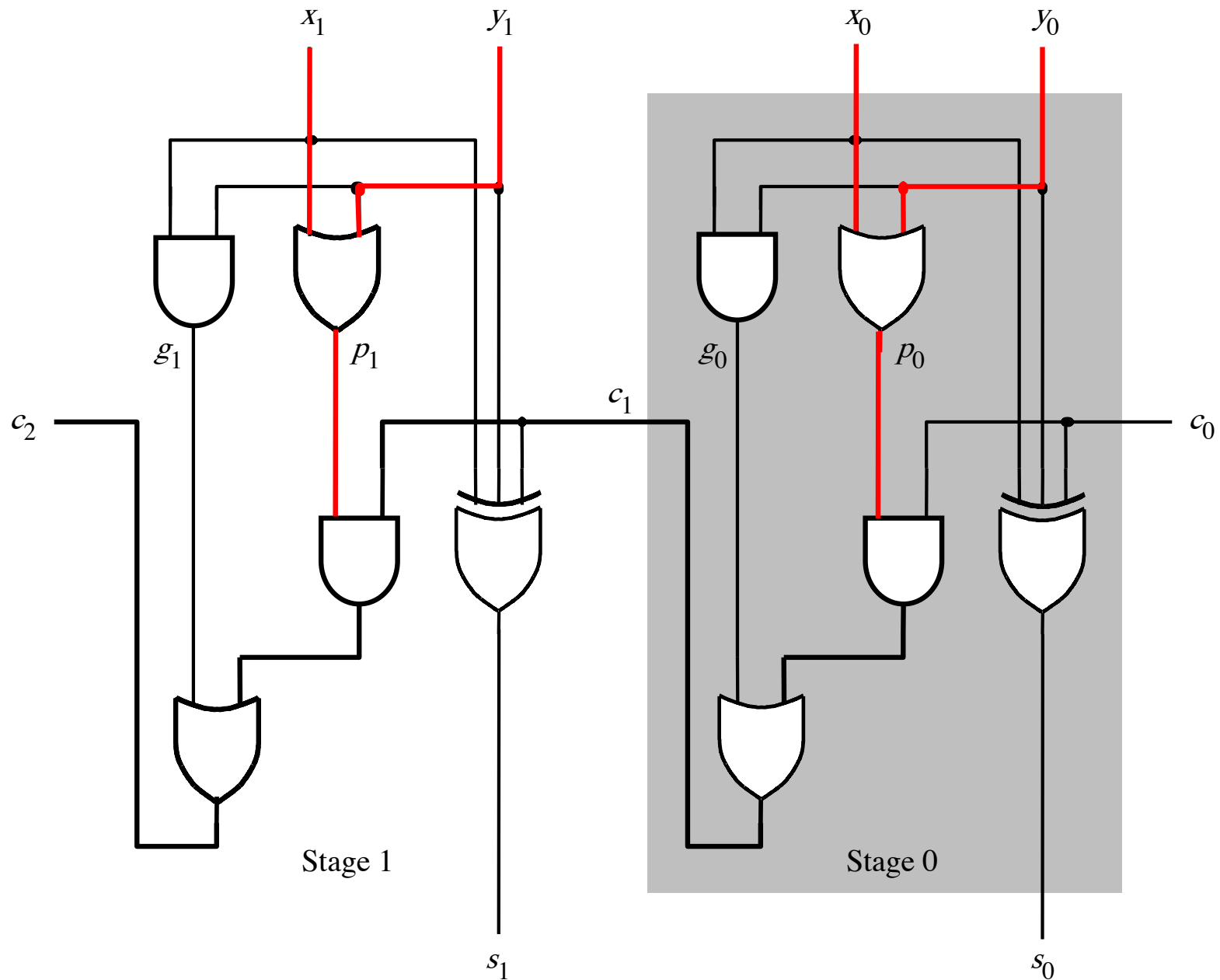

[ Figure 3.14 from the textbook ]

# It takes 1 gate delay to compute all $g_i$ signals

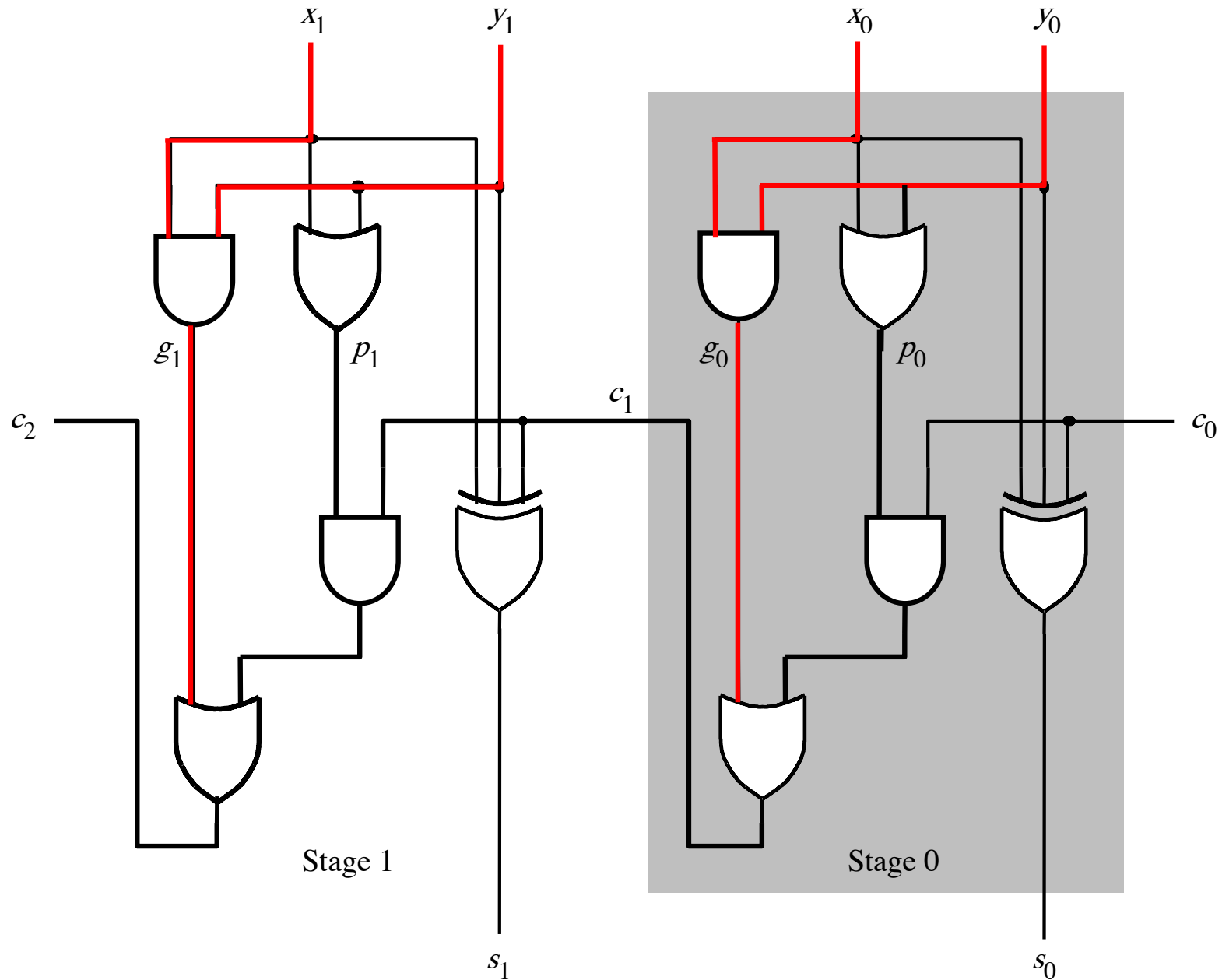

[ Figure 3.14 from the textbook ]

# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

recursive  
expansion of  
 $c_i$

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$



# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$


$$c_{i+1} = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1}$$

# Now we can Build a **Carry-Lookahead Adder**

 

[ Figure 3.15 from the textbook ]

# The first two stages of a carry-lookahead adder

 


[ Figure 3.15 from the textbook ]

# Carry for the first stage

$$c_1 = g_0 + p_0 c_0$$


# Carry for the first stage

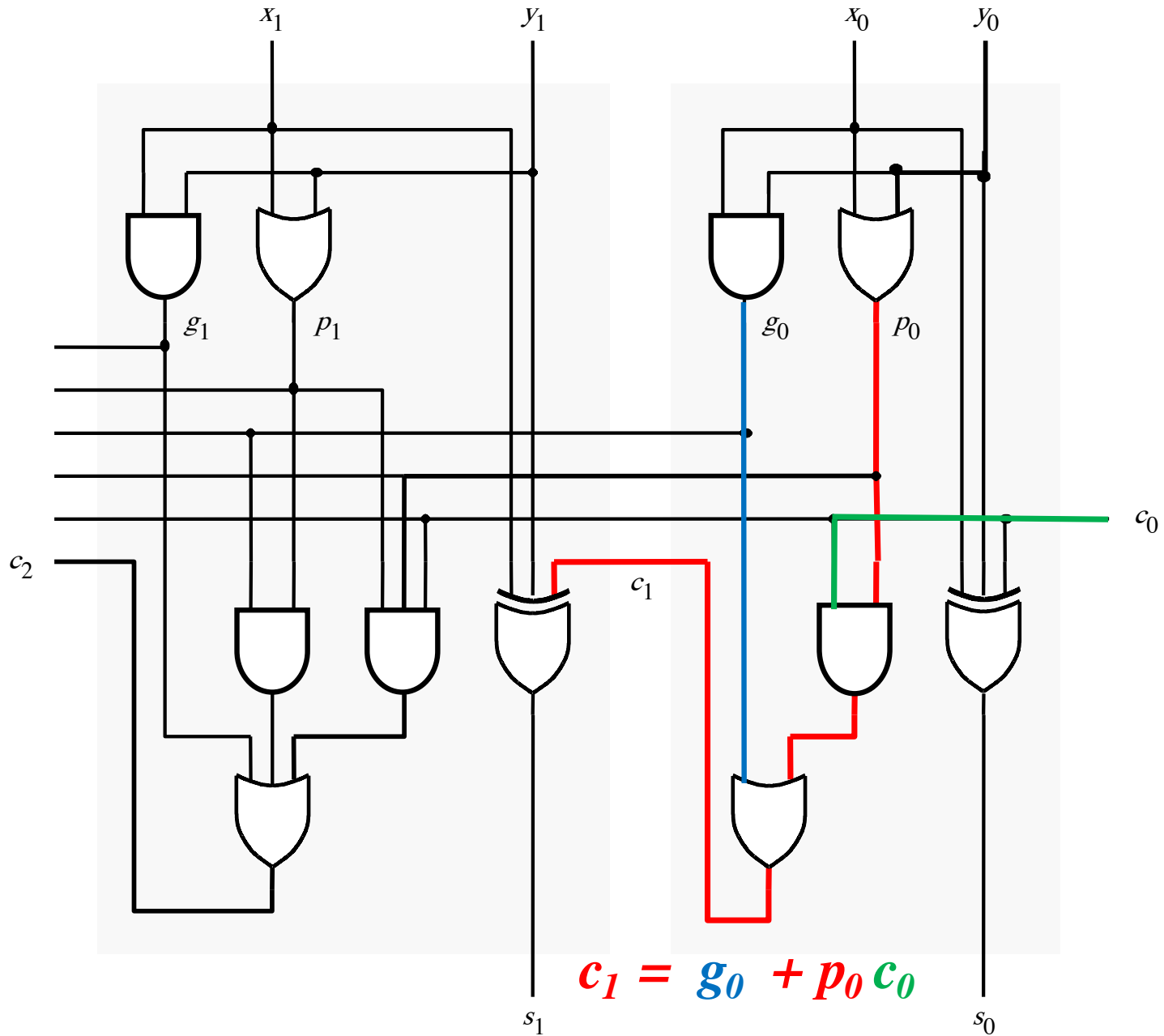

# Carry for the second stage

$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$

# Carry for the second stage

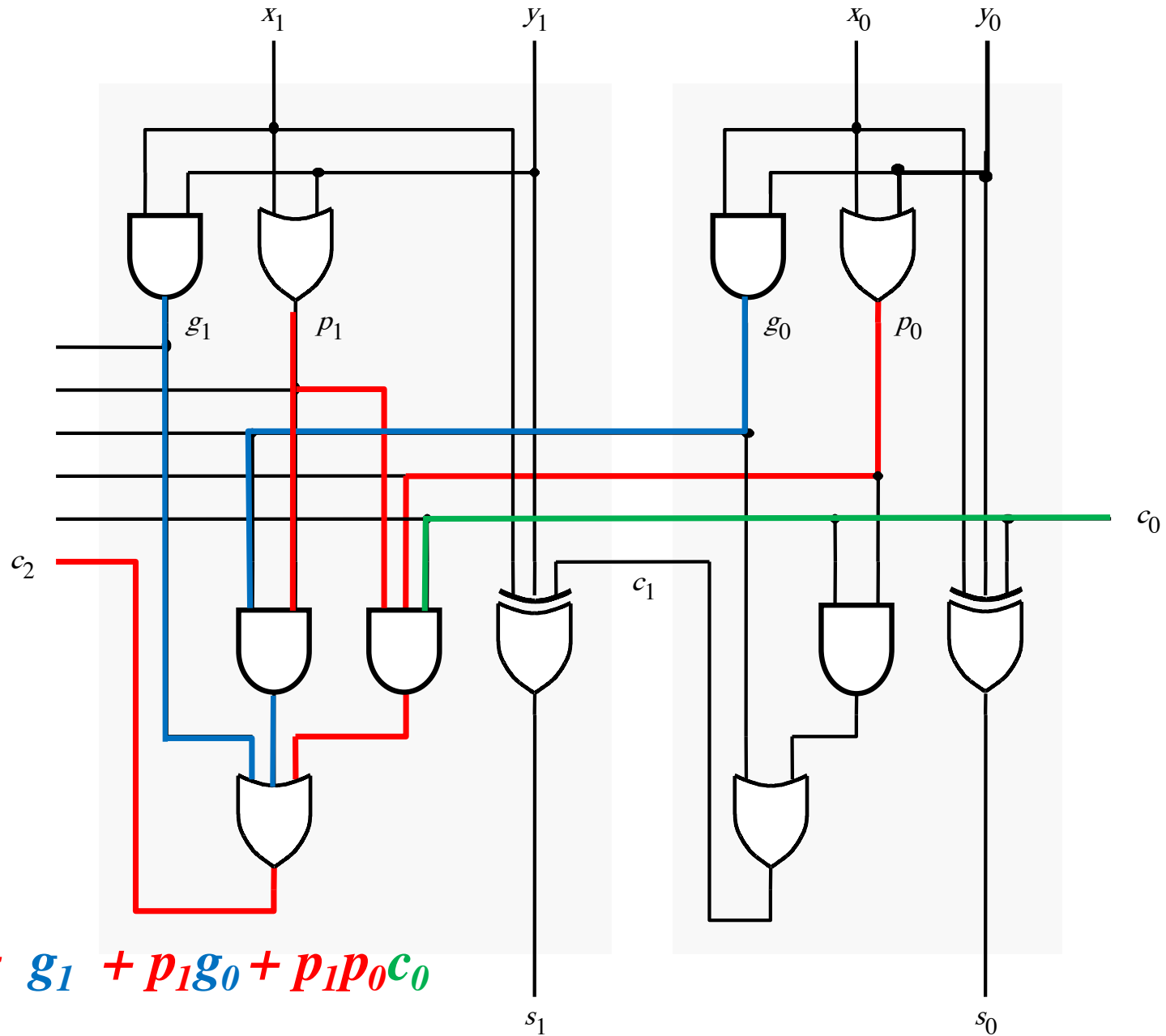

$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$

# Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$



# Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + \underline{p_1} g_0 + \underline{p_1 p_0} c_0$$

# Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + \underline{p_1 g_0} + \underline{p_1 p_0 c_0}$$

$$= g_1 + p_1 \underbrace{(g_0 + p_0 c_0)}_{c_1}$$

# Carry for the first two stages


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$= g_1 + p_1 \underbrace{(g_0 + p_0 c_0)}_{c_1}$$


$$= g_1 + p_1 c_1$$

# The first two stages of a carry-lookahead adder

 


[ Figure 3.15 from the textbook ]

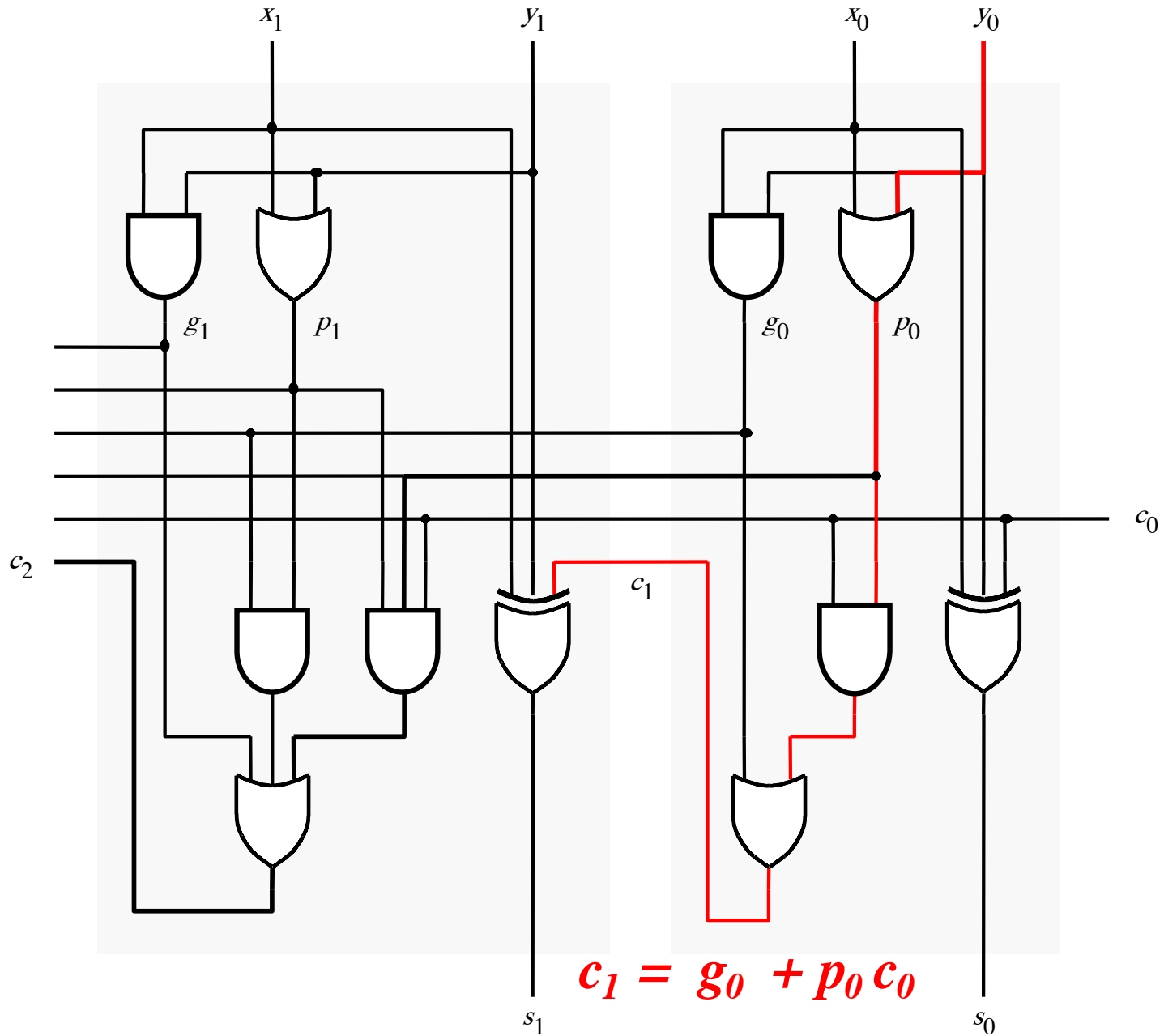**It takes 3 gate delays to generate  $c_1$**




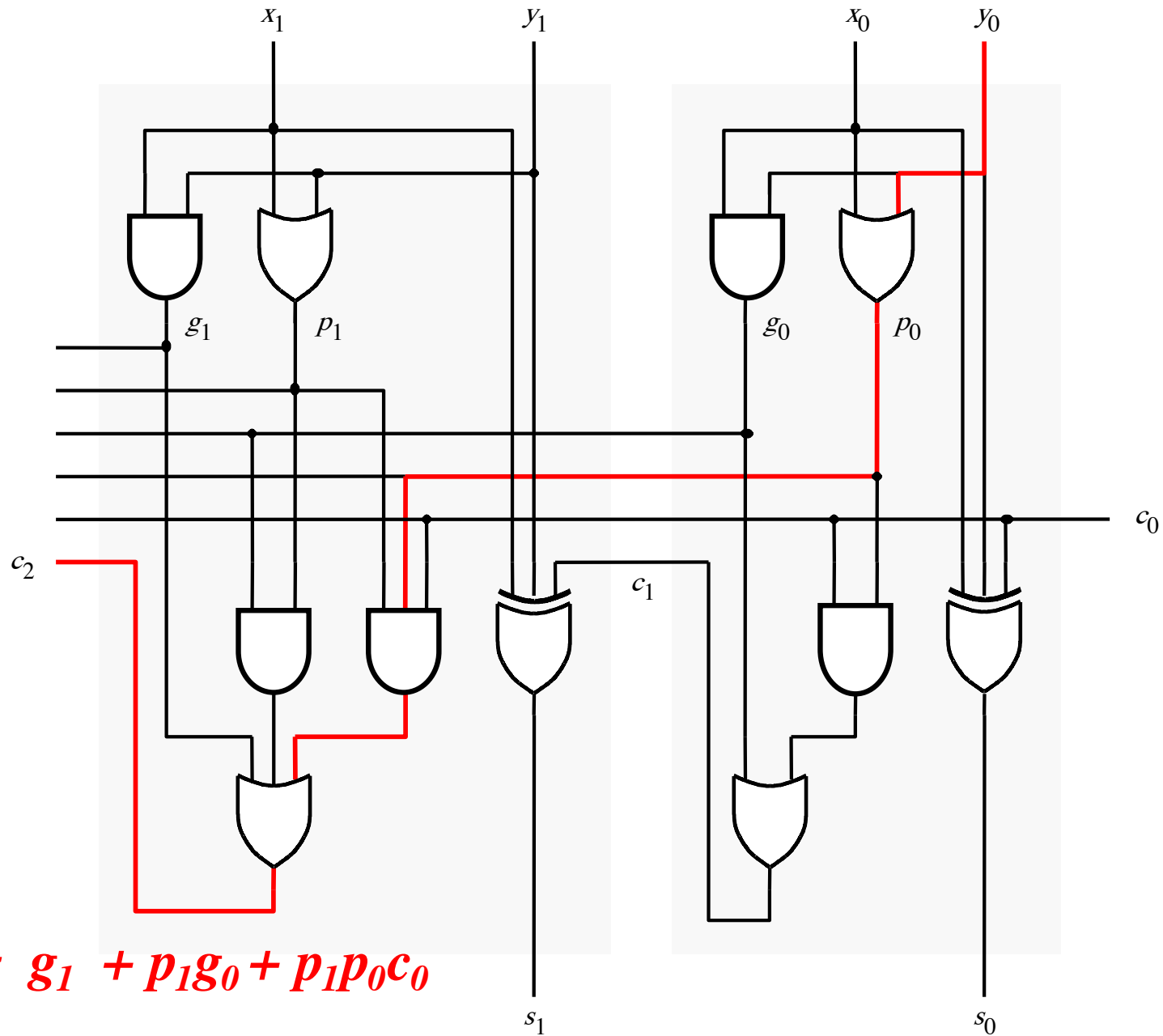It takes 3 gate delays to generate  $c_2$




$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$
 
# The first two stages of a carry-lookahead adder




 **It takes 4 gate delays to generate  $s_1$**





 It takes 4 gate delays to generate  $s_2$



# **N-bit Carry-Lookahead Adder**

- **It takes 1 gate delay to generate all  $g_i$  and  $p_i$  signals**
- **It takes 2 more gate delays to generate all carry signals**
- **It takes 1 more gate delay to generate all sum bits**
- **Thus, the total delay through an n-bit carry-lookahead adder is only 4 gate delays!**

# Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

# Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$

Even this takes  
only 3 gate delays


$$+ p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2$$

$$+ p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0$$


$$+ p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0$$

**A hierarchical carry-lookahead adder  
with ripple-carry between blocks**

 
# A hierarchical carry-lookahead adder with ripple-carry between blocks


 
# A hierarchical carry-lookahead adder with ripple-carry between blocks



 
# A hierarchical carry-lookahead adder with ripple-carry between blocks






# **A hierarchical carry-lookahead adder**

# A hierarchical carry-lookahead adder with ripple-carry between blocks

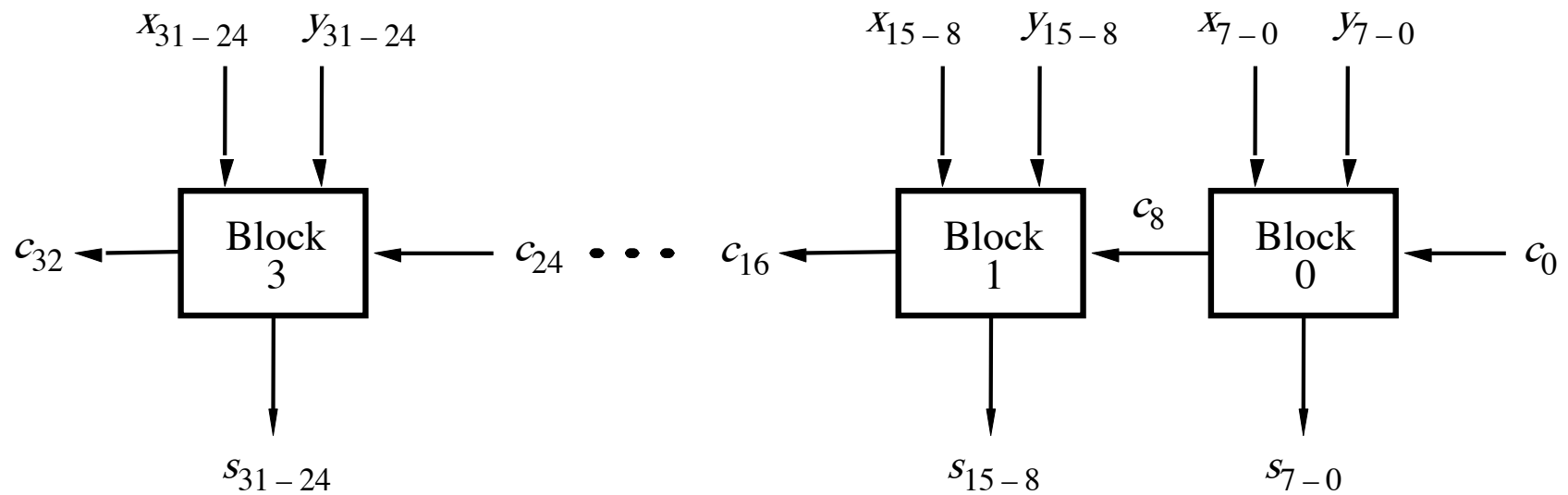


[ Figure 3.16 from the textbook ]

# A hierarchical carry-lookahead adder

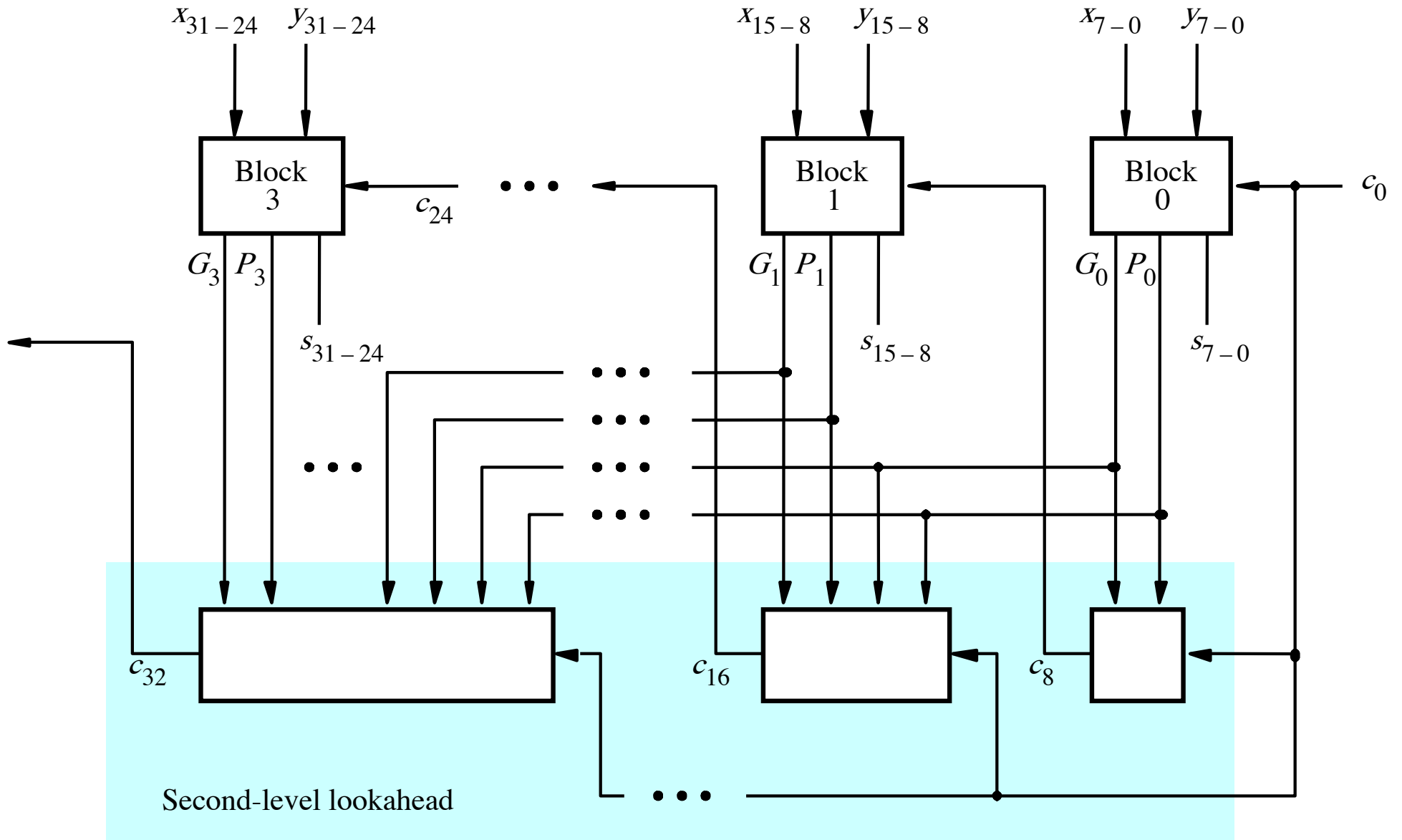


[ Figure 3.17 from the textbook ]

# A hierarchical carry-lookahead adder

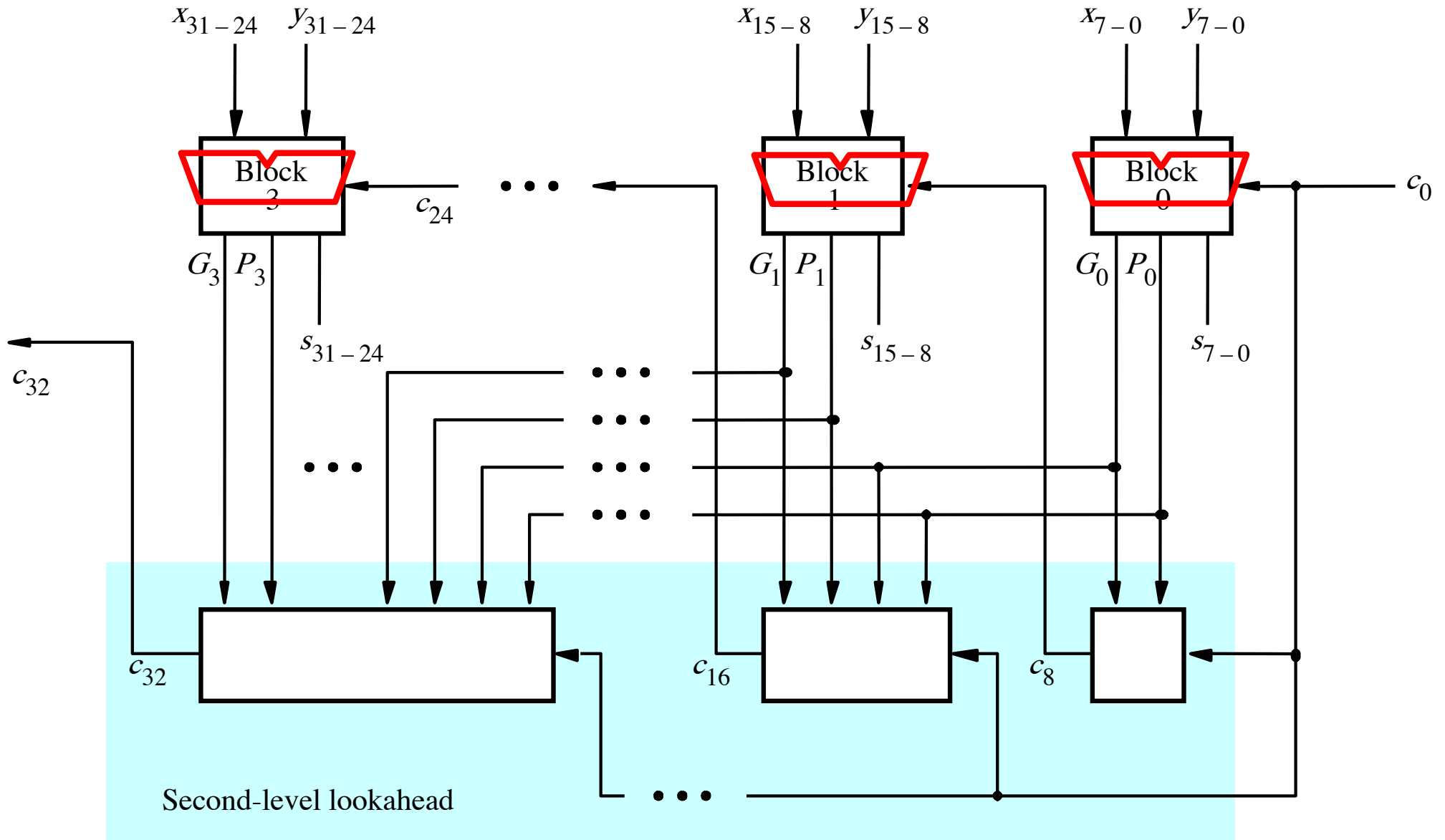

# A hierarchical carry-lookahead adder

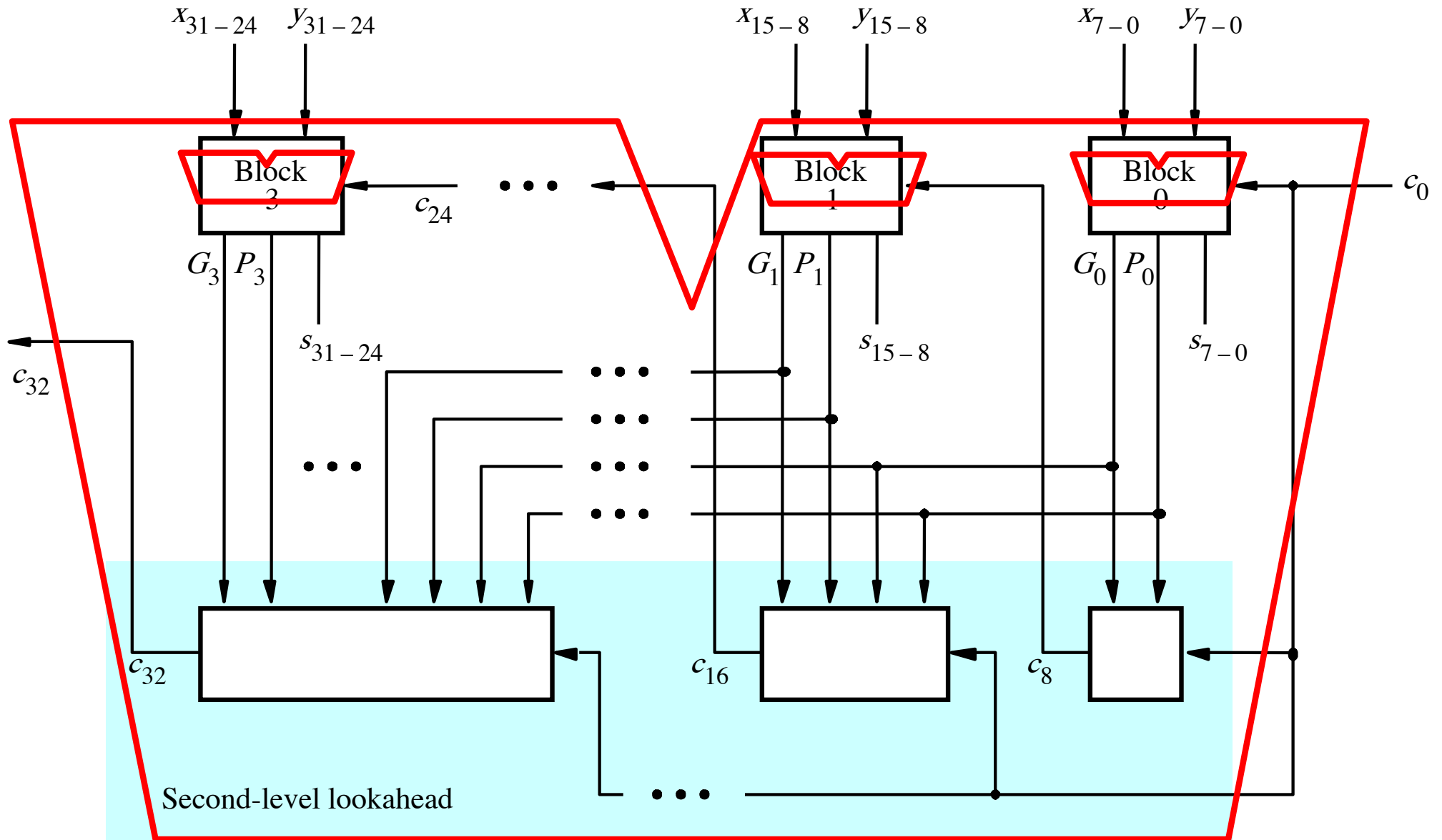



# The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

# The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$



# The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

$G_0$  →

$P_0$  →

# The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

$G_0$  →

$P_0$  →

$$c_8 = G_0 + P_0c_0$$

# The Hierarchical Carry Expression

3-gate delays

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

$G_0$  →

$P_0$  →

2-gate delays

$$c_8 = G_0 + P_0c_0$$

# The Hierarchical Carry Expression

3-gate delays

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

$G_0$  points to the first four terms of the expression.

$P_0$  points to the last term of the expression.

2-gate delays

$$c_8 = \underbrace{G_0}_{\substack{\text{3-gate} \\ \text{delays}}} + \underbrace{P_0}_{\substack{\text{2-gate} \\ \text{delays}}} c_0$$

# The Hierarchical Carry Expression

3-gate delays

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

$G_0$  → (points to the first four terms of the expression)  
 $P_0$  → (points to the last term of the expression)  
 2-gate delays (under the last term)

$$c_8 = \underbrace{G_0}_{\substack{\text{3-gate} \\ \text{delays}}} + \underbrace{P_0 c_0}_{\substack{\text{3-gate} \\ \text{delays}}}$$

# The Hierarchical Carry Expression

3-gate delays

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

$G_0$  →

$P_0$  →

2-gate delays

$$c_8 = G_0 + P_0c_0$$

4-gate  
delays

# The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\ & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$

# The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The same expression, just add 8 to all subscripts

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\ & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$



# The Hierarchical Carry Expression

3-gate delays

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

$G_0$  → (points to the first four terms of the equation)

$P_0$  → (points to the last term of the equation)

2-gate delays

$$\begin{aligned}
 c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\
 & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8
 \end{aligned}$$

# The Hierarchical Carry Expression

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

3-gate delays

$$\begin{aligned}
 c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\
 & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8
 \end{aligned}$$

$G_1$  →

$P_1$  →

2-gate delays

# The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

# The Hierarchical Carry Expression

$$c_8 = \textcircled{G_0} + P_0 c_0$$

3-gate delays

# The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

4-gate delays

# The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

# The Hierarchical Carry Expression

$$c_8 = \textcircled{G_0} + P_0 c_0$$

3-gate delays

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 \textcircled{G_0} + P_1 P_0 c_0 \end{aligned}$$

3-gate delays

# The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 \textcircled{G_0} + P_1 P_0 c_0 \end{aligned}$$

3-gate delays



# The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

4-gate delays

# The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

5-gate delays

# The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

# The Hierarchical Carry Expression


$$c_8 = G_0 + P_0 c_0 \quad \text{4-gate delays}$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 && \text{5-gate delays} \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0 \quad \text{5-gate delays}$$


$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0 \quad \text{5-gate delays}$$

# A hierarchical carry-lookahead adder

 

[ Figure 3.17 from the textbook ]

# A hierarchical carry-lookahead adder

 

[ Figure 3.17 from the textbook ]



# Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is 8 gates:
  - 3 to generate all  $G_i$  and  $P_i$  signals
  - +2 to generate  $c_8$ ,  $c_{16}$ ,  $c_{24}$ , and  $c_{32}$
  - +2 to generate internal carries in the blocks
  - +1 to generate the sum bits (one extra XOR)
  
# Hierarchical CLA Adder Carry Logic

SECOND  
LEVEL  
HIERARCHY

- C8 - 4 gate delays
- C16 - 5 gate delays
- C24 - 5 Gate delays
- C32 - 5 Gate delays





FIRST LEVEL HIERARCHY


  
# Hierarchical CLA Critical Path

SECOND  
LEVEL  
HIERARCHY

- C1 - 3 gate delays
- C9 - 6 gate delays
- C17 - 7 gate delays**
- C25 - 7 Gate delays




FIRST LEVEL HIERARCHY


# Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is 8 gates:
  - 3 to generate all  $G_i$  and  $P_i$  signals
  - +2 to generate  $c_8$ ,  $c_{16}$ ,  $c_{24}$ , and  $c_{32}$
  - **+2 to generate internal carries in the blocks**
  - +1 to generate the sum bits (one extra XOR)
 
## 2 more gate delays for the internal carries within a block


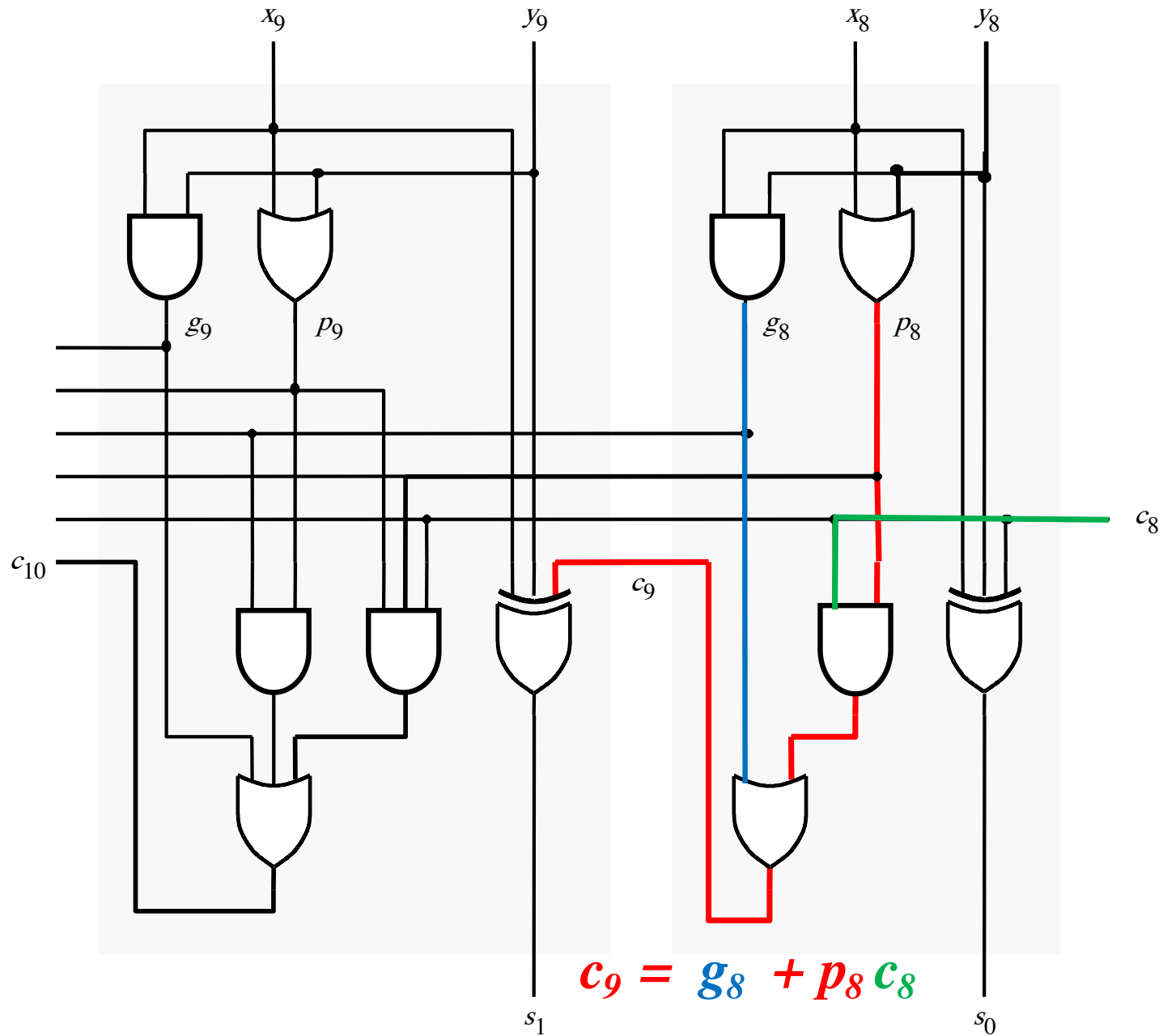
## 2 more gate delays for the internal carries within a block



# Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is **8 gates**:
  - 3 to generate all  $G_i$  and  $P_i$  signals
  - +2 to generate  $c_8$ ,  $c_{16}$ ,  $c_{24}$ , and  $c_{32}$
  - +2 to generate internal carries in the blocks
  - +1 to generate the sum bits (one extra XOR)

**Questions?**

**THE END**