



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

D Flip-Flops


*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff


- **Homework 7 is due today**
- **Homework 8 is due on Monday Oct 24 @ 10pm.**

Quick Review


A simple memory element with NOT Gates

 


A simple memory element with NOT Gates

 

A simple memory element with NOT Gates

 


A simple memory element with NOT Gates

 


The circuit will stay in this state indefinitely.


A simple memory element with NOT Gates

 

A simple memory element with NOT Gates


 


A simple memory element with NOT Gates

 


The circuit will stay in this state indefinitely.

  
This circuit can be in two possible states



 This circuit can be in two possible states




used to store a 1

 


used to store a 0

A simple memory element with NAND Gates

 


A simple memory element with NOR Gates

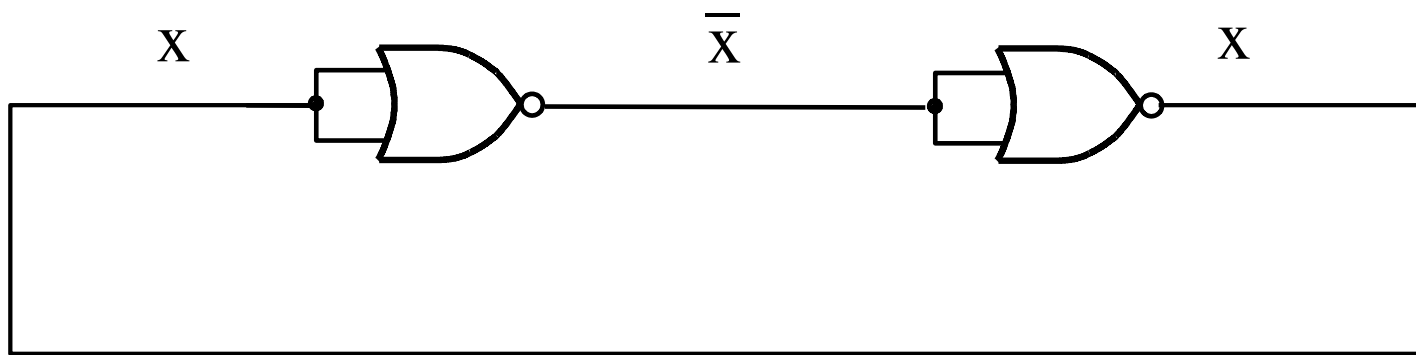


Basic Latch


A simple memory element with NOR Gates

 


A simple memory element with NOR Gates

 



A simple memory element with NOR Gates

 

A memory element with NOR gates

 


  Two Different Ways to Draw the Same Circuit



Circuit and Characteristic Table for the Basic Latch

 Note that Q_a and Q_b are inverses of each other!




(a) Circuit

| S | R | Q_a | Q_b | |
|---|---|-------|-------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

 (b) Characteristic table

SR Latch: Circuit and Characteristic Table




(a) Circuit

| S | R | Q_a | Q_b | |
|---|---|-------|-------|----------------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | (Undesirable) |

(b) Truth table

[Figure 5.4a,b from the textbook]

NOR Gate

 

NOR Gate Truth table

| x_1 | x_2 | f |
|-------|-------|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


Oscillations and Undesirable States

- **When $S=1$ and $R=1$ both outputs of the latch are equal to 0, i.e., $Q_a=0$ and $Q_b=0$.**
- **Thus, the two outputs are no longer complements of each other.**
- **This is undesirable as many of the circuits that we will build later with these latches rely on the assumption that the two outputs are always complements of each other.**
- **(This is obviously not the case for the basic latch, but we will patch it later to eliminate this problem).**

Oscillations and Undesirable States

- An even bigger problem occurs when we transition **from $S=R=1$ to $S=R=0$** .
- When $S=R=1$ we have $Q_a=Q_b=0$. After the transition to $S=R=0$, however, we get $Q_a=Q_b=1$, which would immediately cause $Q_a=Q_b=0$, and so on.
- If the gate delays and the wire lengths are identical, then this oscillation will continue forever.
- In practice, the oscillation dies down and the output settles into either $Q_a=1$ and $Q_b=0$ or $Q_a=0$ and $Q_b=1$.
- The problem is that **we can't predict** which one of these two it will settle into.

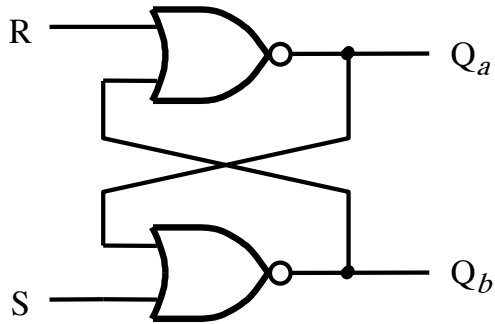
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q_a | Q_b |
|---|---|-------|-----------------|
| 0 | 0 | 0/1 | 1/0 (no change) |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |


(b) Characteristic table

 

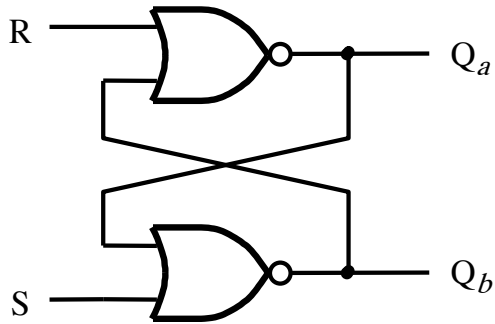(c) Timing diagram

[Figure 5.4 from the textbook]


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q_a | Q_b |
|---|---|-------|-----------------|
| 0 | 0 | 0/1 | 1/0 (no change) |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |


(b) Characteristic table

 

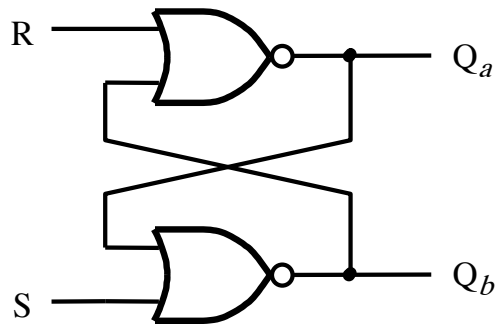(c) Timing diagram

[Figure 5.4 from the textbook]


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q_a | Q_b | |
|---|---|-------|-------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

 

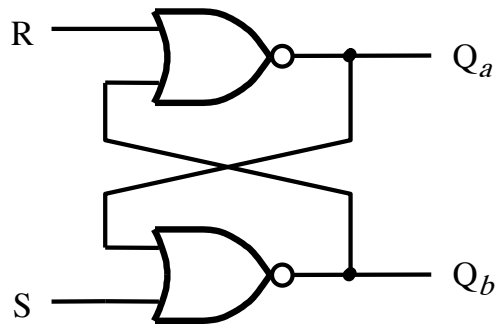(c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q_a | Q_b | |
|---|---|-------|-------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

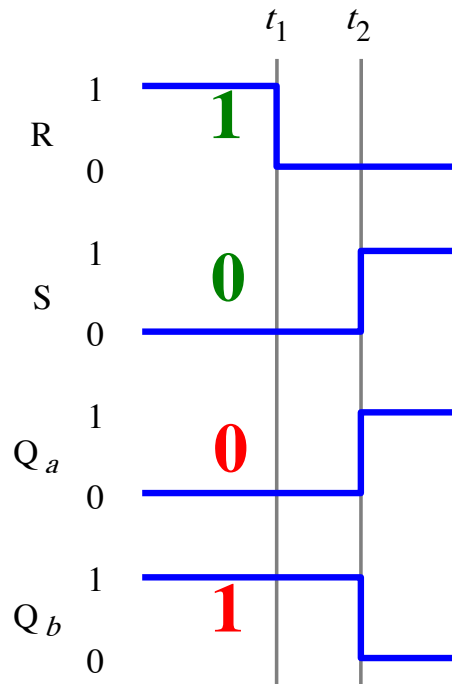

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

 

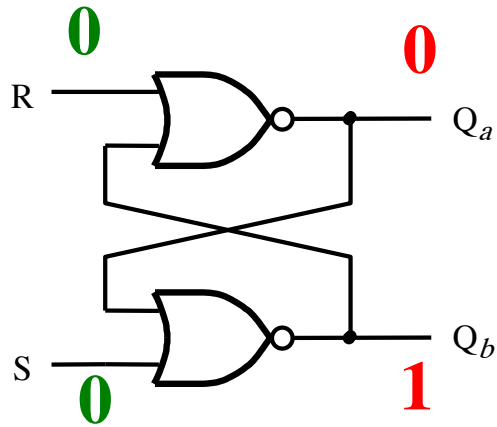(c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

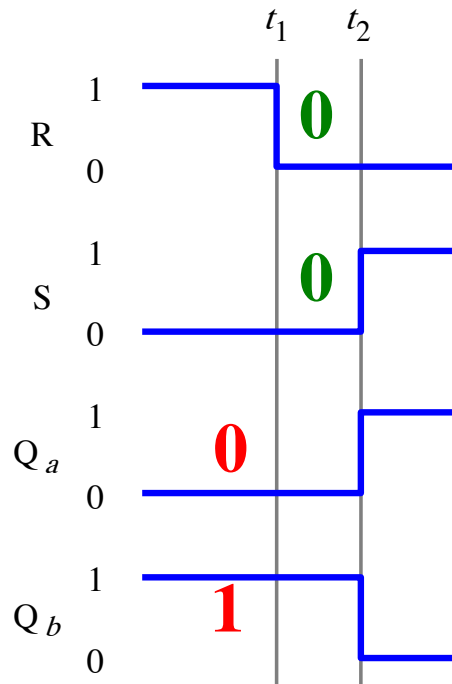

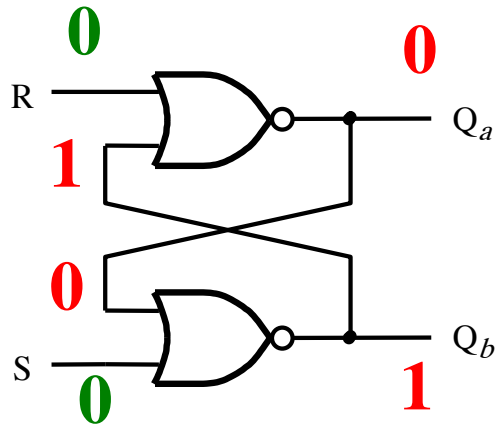(c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q_a | Q_b | |
|---|---|-------|-------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

 

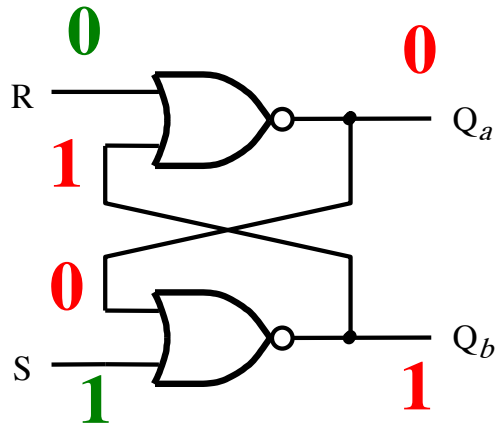(c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q_a | Q_b | |
|---|---|-------|-------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |


(b) Characteristic table

 

 (c) Timing diagram

For a brief moment the latch goes through the undesirable state $Q_a=0$ and $Q_b=0$.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |


(b) Characteristic table

 

 (c) Timing diagram

But these zeros loop around ...


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |


(b) Characteristic table

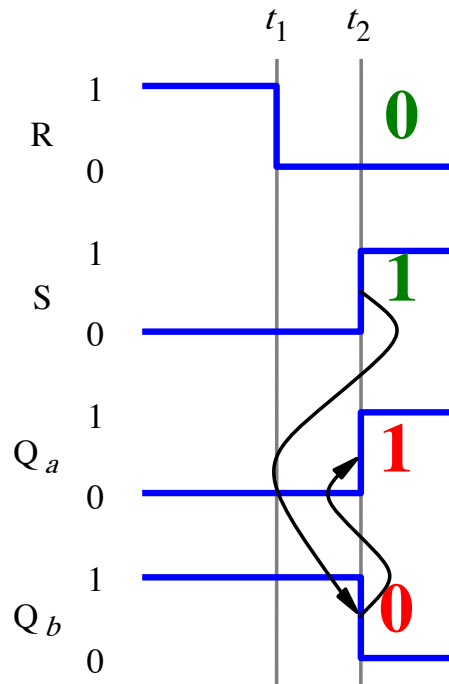

 (c) Timing diagram

... and set it to $Q_a=1$ and $Q_b=0$.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q _a | Q _b |
|---|---|----------------|-----------------|
| 0 | 0 | 0/1 | 1/0 (no change) |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |


(b) Characteristic table

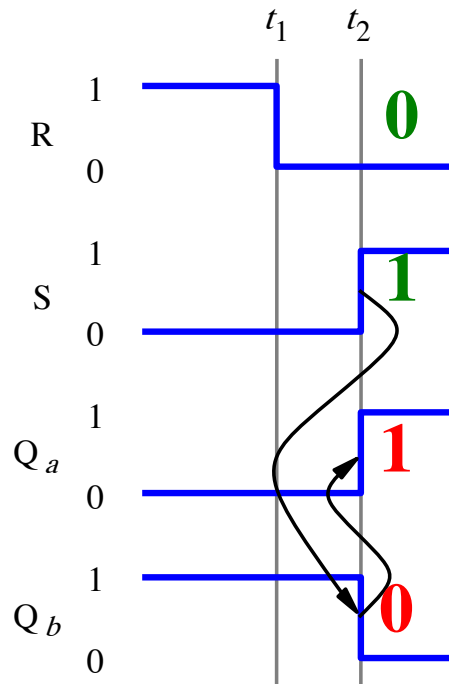

 (c) Timing diagram

The new values also loop around ...


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |


(b) Characteristic table

 

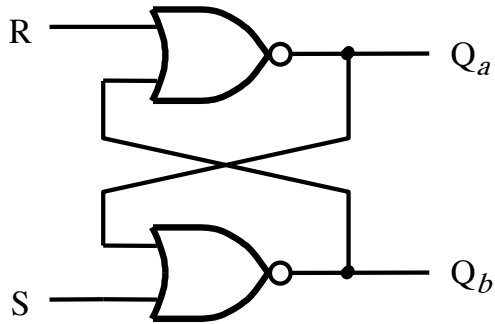(c) Timing diagram

... but they leave the outputs the same.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q_a | Q_b |
|---|---|-------|-----------------|
| 0 | 0 | 0/1 | 1/0 (no change) |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

(b) Characteristic table

 


(c) Timing diagram

→ Time

[Figure 5.4 from the textbook]

 
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |


(b) Characteristic table

 

 (c) Timing diagram

For a brief moment the latch goes through the undesirable state $Q_a=0$ and $Q_b=0$.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |


(b) Characteristic table

 

 (c) Timing diagram

But these zeros loop around ...


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |


(b) Characteristic table

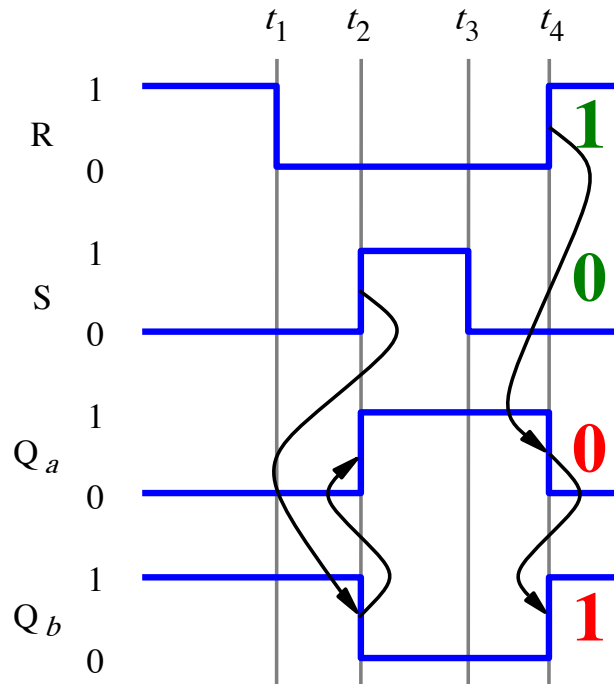

 (c) Timing diagram

... and set it to $Q_a=0$ and $Q_b=1$.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q _a | Q _b | |
|---|---|----------------|----------------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |


(b) Characteristic table

 

 (c) Timing diagram

The new values also loop around ...


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q_a | Q_b | |
|---|---|-------|-------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |


(b) Characteristic table

 

 (c) Timing diagram

... but they leave the outputs the same.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q_a | Q_b |
|---|---|-------|-----------------|
| 0 | 0 | 0/1 | 1/0 (no change) |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |


(b) Characteristic table

 

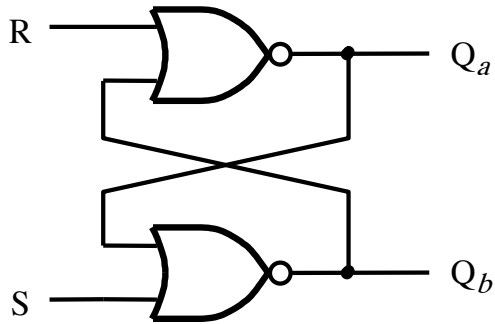(c) Timing diagram

[Figure 5.4 from the textbook]


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q_a | Q_b |
|---|---|-------|-----------------|
| 0 | 0 | 0/1 | 1/0 (no change) |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

(b) Characteristic table

 


(c) Timing diagram

→ Time

[Figure 5.4 from the textbook]

 
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

| S | R | Q_a | Q_b |
|---|---|-------|-----------------|
| 0 | 0 | 0/1 | 1/0 (no change) |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

(b) Characteristic table

 

A transition from $S=R=1$ to $S=R=0$ causes oscillations of the two output values Q_a and Q_b .


(c) Timing diagram

Time


[Figure 5.4 from the textbook]

Basic Latch with NAND Gates

 
Circuit for the Basic Latch with NAND Gates



Basic Latch (with NOR Gates)

 


Basic Latch (with NAND Gates)

 

Notice that in the NAND case the two inputs are swapped and negated.


The labels of the outputs are the same in both cases.

Basic Latch (with NOR Gates)

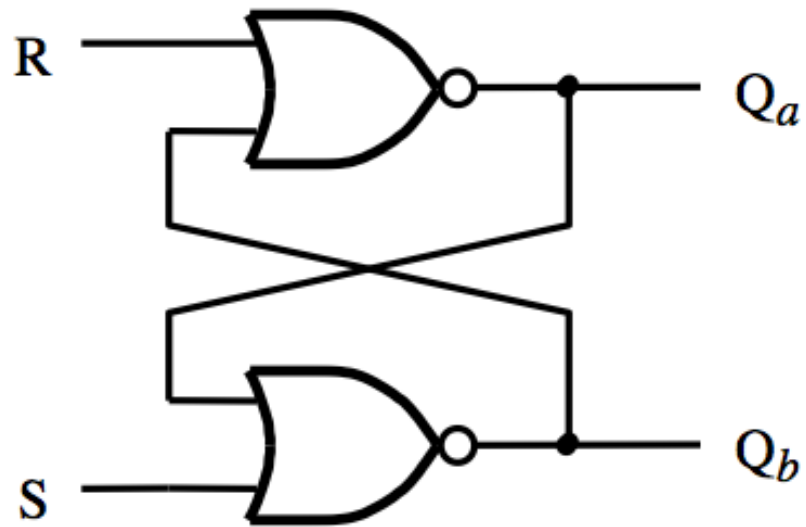


SR Latch

Basic Latch (with NAND Gates)

 

$\bar{S}\bar{R}$ Latch

Circuit and Characteristic Table

 

(a) Circuit


| \bar{S} | \bar{R} | Q_a | Q_b |
|-----------|-----------|-------|-----------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0/1 | 1/0 (no change) |

(b) Characteristic table (version 1)

| S | R | Q_a | Q_b |
|---|---|-------|-----------------|
| 0 | 0 | 0/1 | 1/0 (no change) |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 |

(c) Characteristic table (version 2)


NAND Gate

 

NAND Gate Truth table


| x_1 | x_2 | f |
|-------|-------|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Basic Latch (with NOR Gates)

 


| S | R | Q_a | Q_b | |
|---|---|-------|-------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 0 | 0 | |

Basic Latch (with NAND Gates)

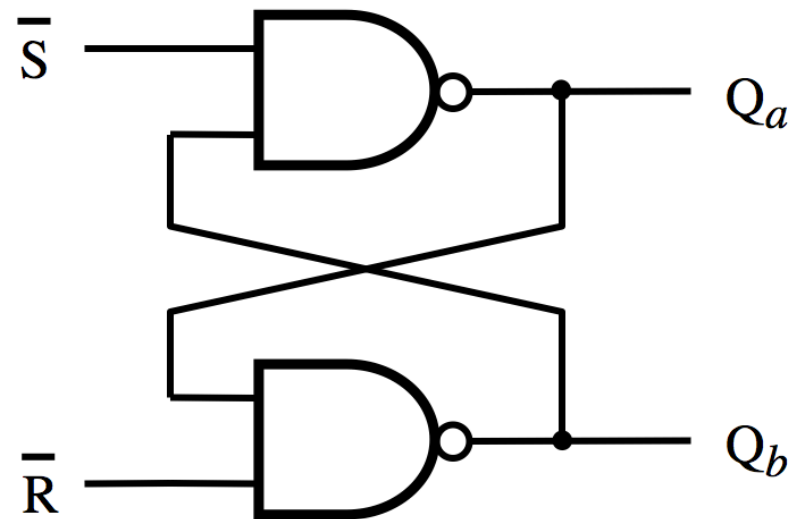


| S | R | Q_a | Q_b | |
|---|---|-------|-------|-------------|
| 0 | 0 | 0/1 | 1/0 | (no change) |
| 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 0 | |
| 1 | 1 | 1 | 1 | |

Basic Latch (with NOR Gates)

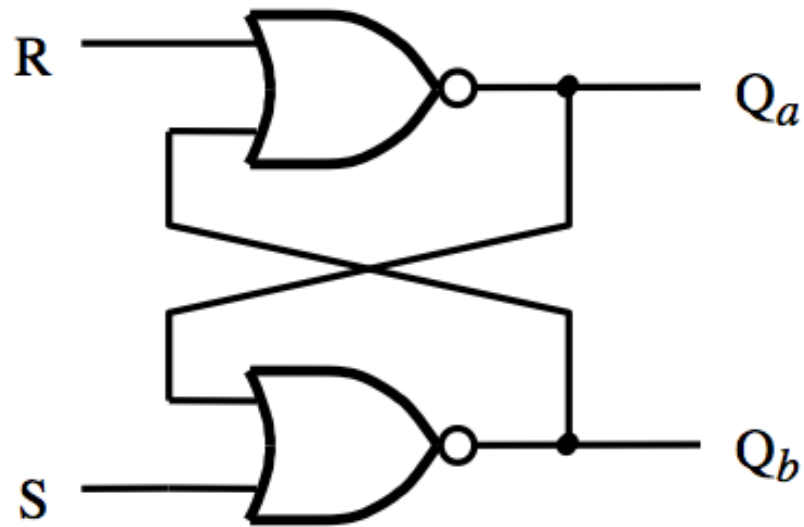


| S | R | Q_a | Q_b | |
|---|---|-------|-------|--------------------------|
| 0 | 0 | 0/1 | 1/0 | (no change) Latch |
| 0 | 1 | 0 | 1 | Reset |
| 1 | 0 | 1 | 0 | Set |
| 1 | 1 | 0 | 0 | Undesirable |

Basic Latch (with NAND Gates)

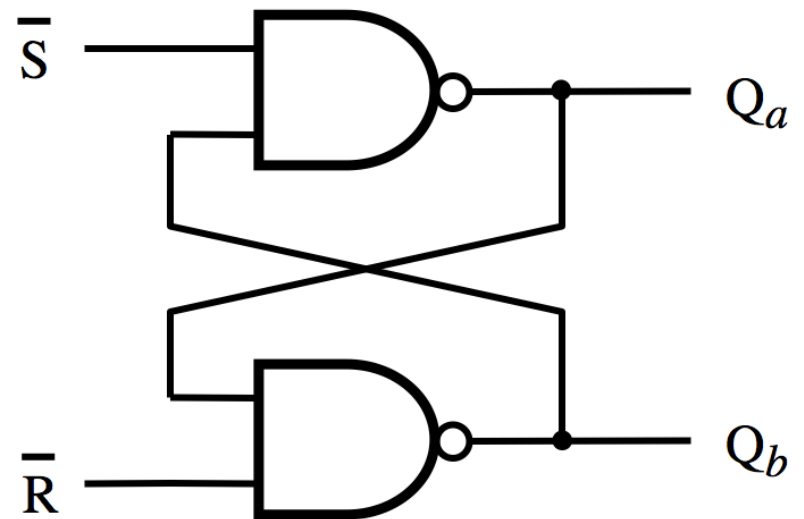


| S | R | Q_a | Q_b | |
|---|---|-------|-------|--------------------------|
| 0 | 0 | 0/1 | 1/0 | (no change) Latch |
| 0 | 1 | 0 | 1 | Reset |
| 1 | 0 | 1 | 0 | Set |
| 1 | 1 | 1 | 1 | Undesirable |

Basic Latch (with NOR Gates)

 

| S | R | Q_a | Q_b | |
|---|---|-------|-------|--------------------------|
| 0 | 0 | 0/1 | 1/0 | (no change) Latch |
| 0 | 1 | 0 | 1 | Reset |
| 1 | 0 | 1 | 0 | Set |
| 1 | 1 | 0 | 0 | Undesirable |

Basic Latch (with NAND Gates)

 

| S | R | Q_a | Q_b | |
|---|---|-------|-------|--------------------------|
| 0 | 0 | 0/1 | 1/0 | (no change) Latch |
| 0 | 1 | 0 | 1 | Reset |
| 1 | 0 | 1 | 0 | Set |
| 1 | 1 | 1 | 1 | Undesirable |

The two characteristic tables are the same
(except for the last row, which is the undesirable configuration).

Oscillations and Undesirable States


- **The basic latch with NAND gates also suffers from oscillation problems, similar to the basic latch implemented with NOR gates.**
- **Try to do this analysis on your own.**

Gated SR Latch

Motivation


- **The basic latch changes its state when the input signals change**
- **It is hard to control when these input signals will change and thus it is hard to know when the latch may change its state.**
- **We want to have something like an Enable input.**
- **In this case it is called the “Clock” input because it is desirable for the state changes to be synchronized.**

Circuit Diagram for the Gated SR Latch

 


[Figure 5.5a from the textbook]

Circuit Diagram for the Gated SR Latch

 


This is the “gate”
of the gated latch

Circuit Diagram for the Gated SR Latch

 



Notice that these are complements of each other

 Circuit Diagram and Characteristic Table for the Gated SR Latch





| Clk | S | R | Q(t + 1) |
|-----|---|---|------------------|
| 0 | x | x | Q(t) (no change) |
| 1 | 0 | 0 | Q(t) (no change) |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | x |

  Circuit Diagram and Graphical Symbol for the Gated SR Latch




Timing Diagram for the Gated SR Latch

  


[Figure 5.5c from the textbook]

Gated SR latch with NAND gates

 


Gated SR latch with NAND gates

 


In this case the “gate” is constructed using NAND gates! Not AND gates.

Gated SR latch with NAND gates

 


Also, notice that the positions of S and R are now swapped.

Gated SR latch with NAND gates

 


Finally, notice that when $\text{Clk}=1$ this turns into the basic latch with NAND gates, i.e., the $\bar{S}\bar{R}$ Latch.


Gated SR latch with NOR gates

 


Gated SR latch with NAND gates

 

Gated SR latch with NOR gates

 


Gated SR latch with NAND gates

 


Graphical symbols are the same

Gated SR latch with NOR gates

 

| Clk | S | R | $Q(t+1)$ |
|-----|---|---|--------------------|
| 0 | x | x | $Q(t)$ (no change) |
| 1 | 0 | 0 | $Q(t)$ (no change) |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | x (undesirable) |

Gated SR latch with NAND gates

 

| Clk | S | R | $Q(t+1)$ |
|-----|---|---|--------------------|
| 0 | x | x | $Q(t)$ (no change) |
| 1 | 0 | 0 | $Q(t)$ (no change) |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | x (undesirable) |


Characteristic tables are the same

Gated D Latch

Motivation


- **Dealing with two inputs (S and R) could be messy. For example, we may have to reset the latch before some operations in order to store a specific value but the reset may not be necessary depending on the current state of the latch.**
- **Why not have just one input and call it D.**
- **The D latch can be constructed using a simple modification of the SR latch.**

Circuit Diagram for the Gated D Latch

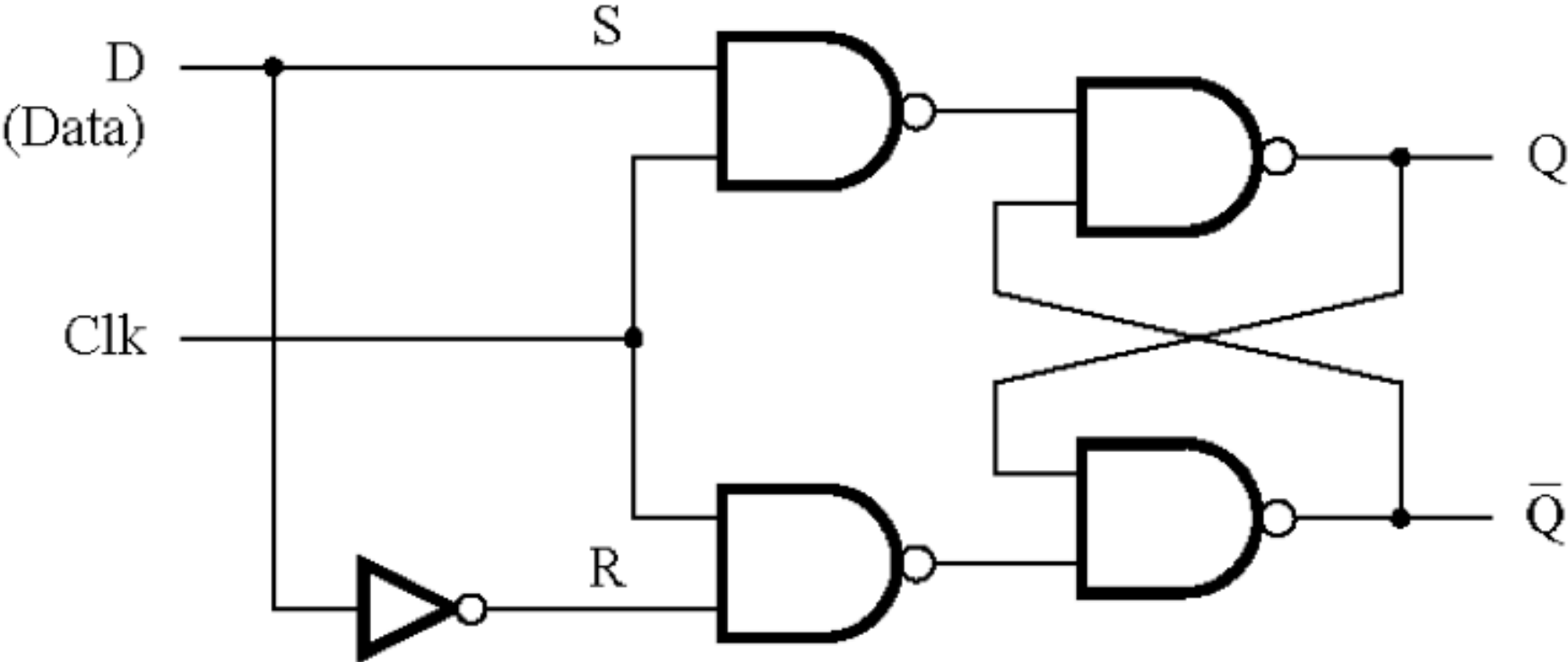


[Figure 5.7a from the textbook]

Circuit Diagram for the Gated D Latch

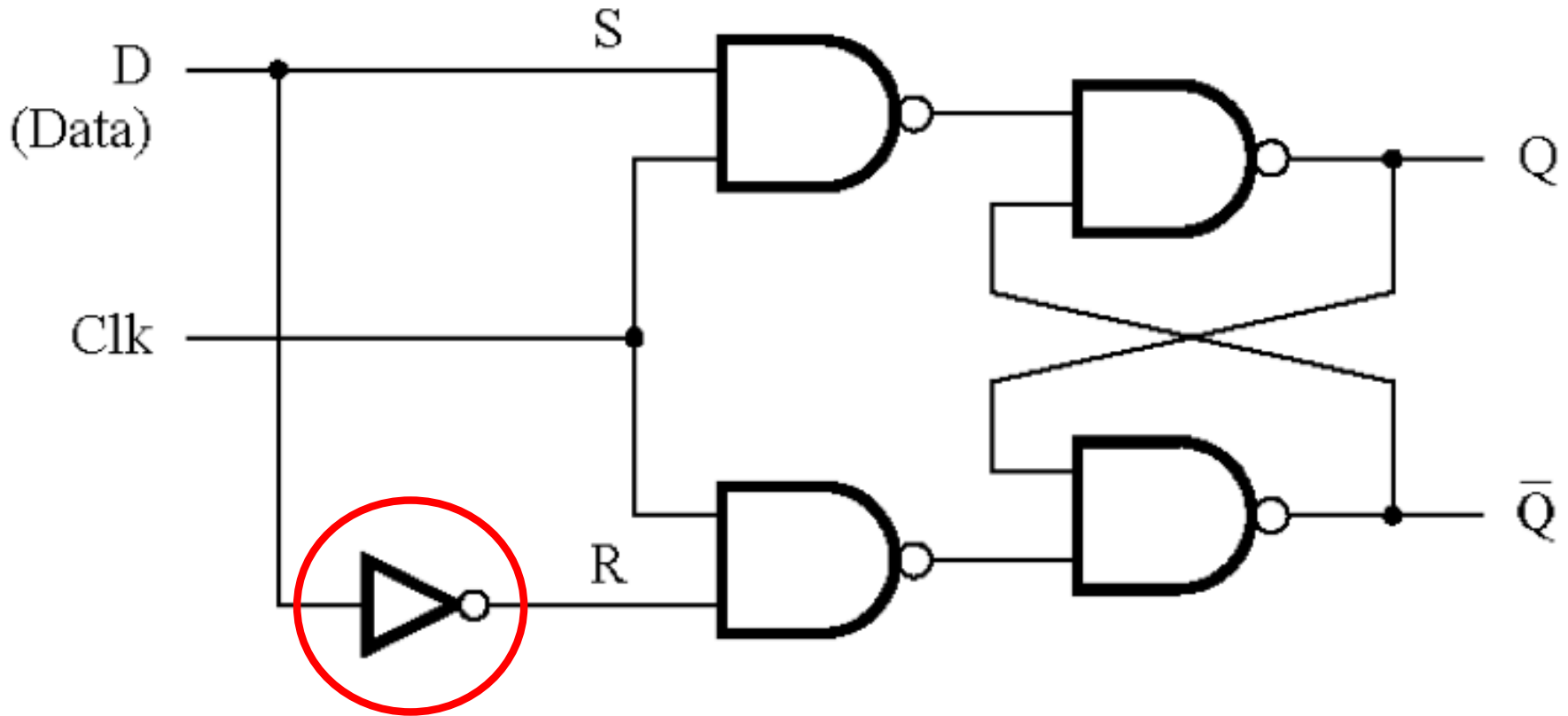


This is the only
new thing here.

Circuit Diagram for the Gated D Latch

 

[Figure 5.7a from the textbook]

Circuit Diagram for the Gated D Latch

 


| \bar{S} | \bar{R} | Q_a | Q_b |
|-----------|-----------|-------|-------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0/1 | 1/0 |

(no change)


[Figure 5.7a from the textbook]

Circuit Diagram for the Gated D Latch

 


[Figure 5.7a from the textbook]

Circuit Diagram for the Gated D Latch

 

[Figure 5.7a from the textbook]


Circuit Diagram for the Gated D Latch

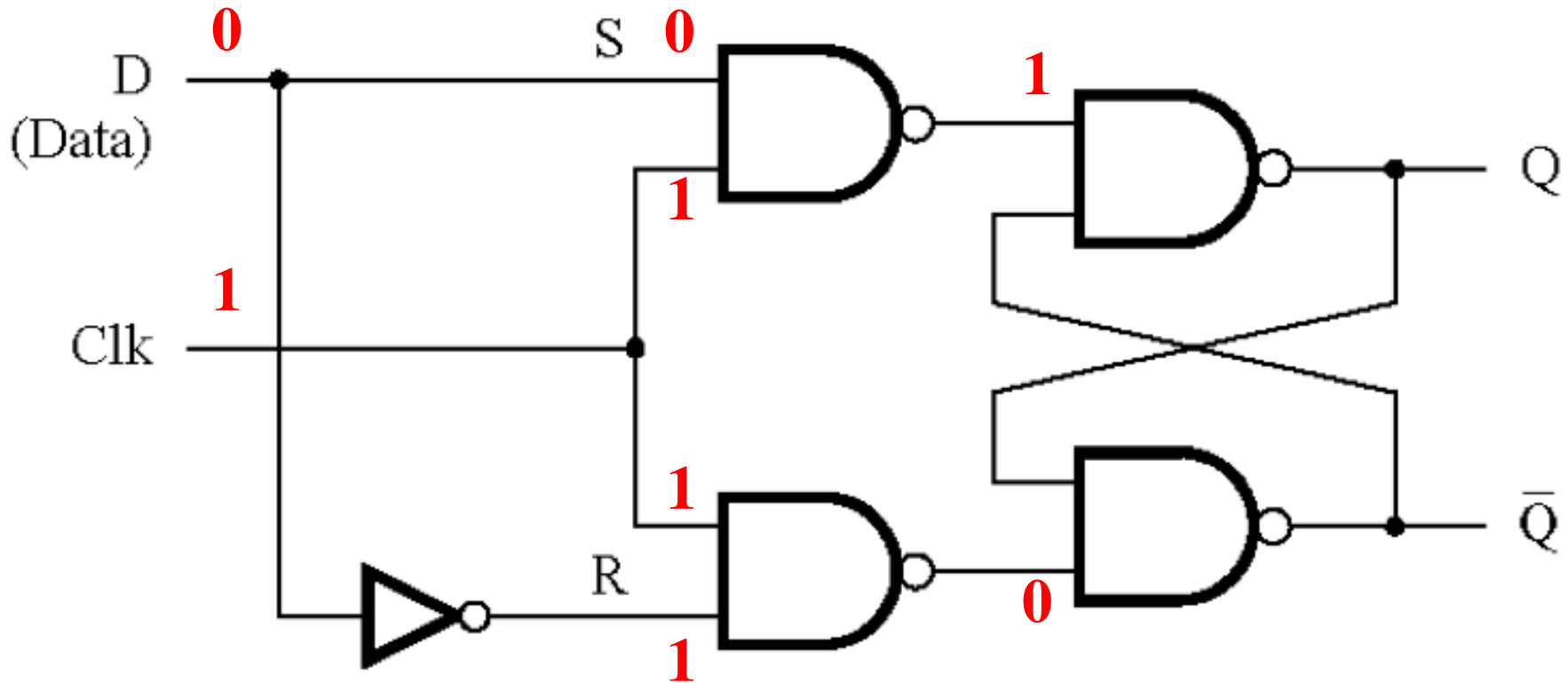

| \bar{S} | \bar{R} | Q_a | Q_b |
|-----------|-----------|-------|-----------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0/1 | 1/0 (no change) |

[Figure 5.7a from the textbook]


Circuit Diagram for the Gated D Latch

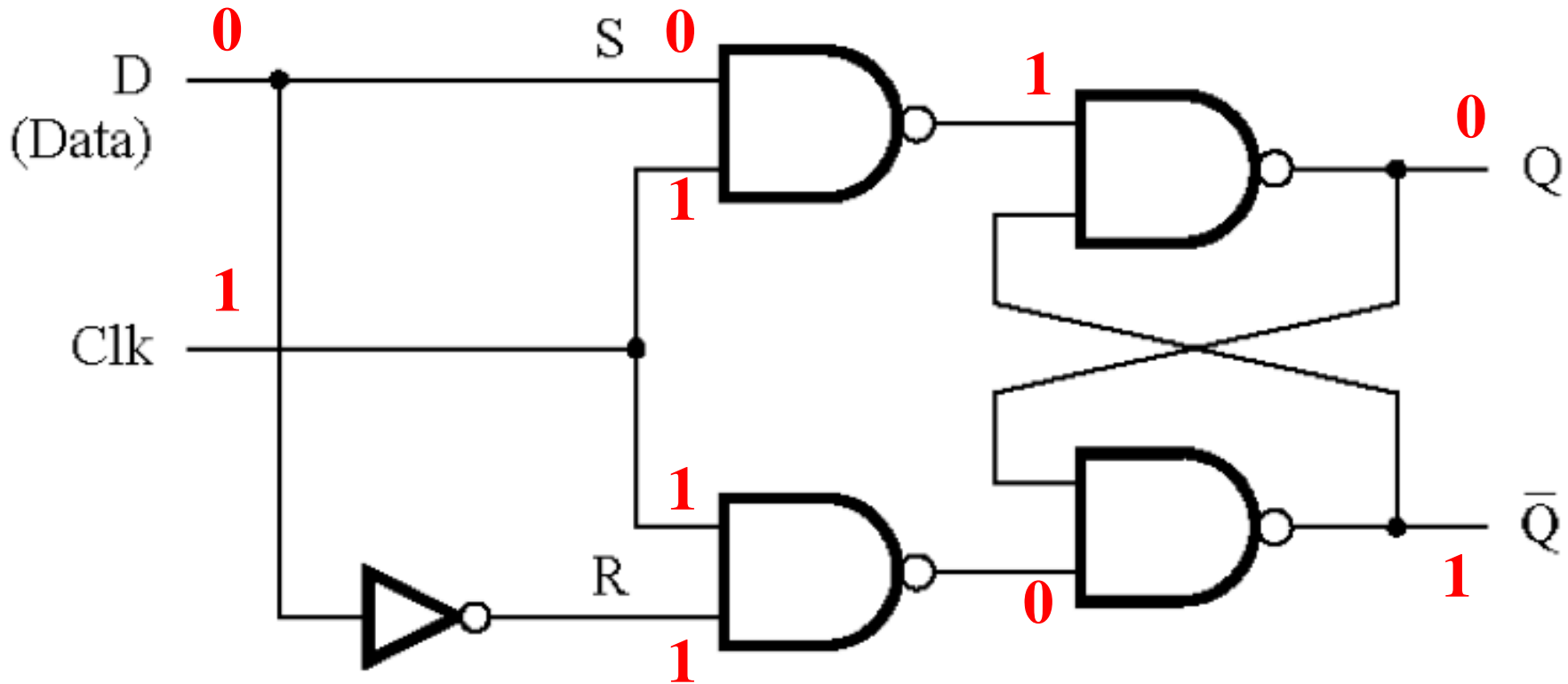

| \bar{S} | \bar{R} | Q_a | Q_b |
|-----------|-----------|-------|-----------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0/1 | 1/0 (no change) |

[Figure 5.7a from the textbook]


Circuit Diagram for the Gated D Latch

 

| \bar{S} | \bar{R} | Q_a | Q_b |
|-----------|-----------|-------|-----------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0/1 | 1/0 (no change) |

[Figure 5.7a from the textbook]

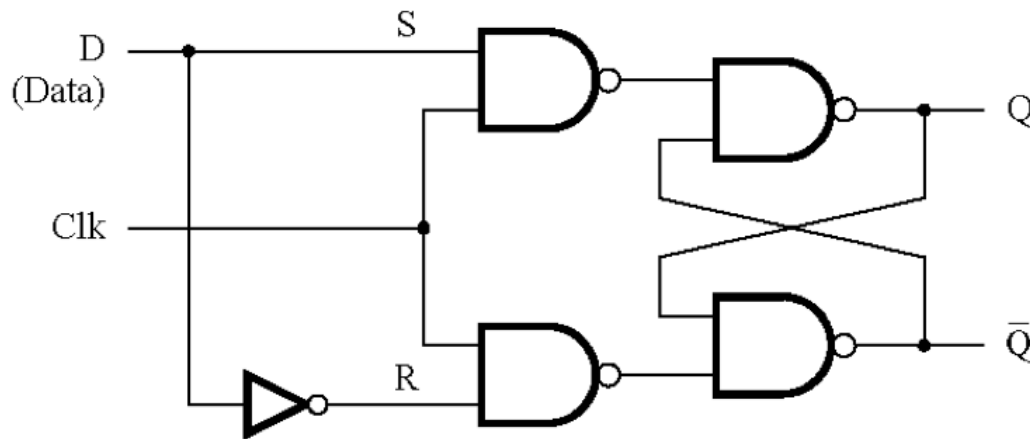
Circuit Diagram and Characteristic Table for the Gated D Latch



| Clk | D | $Q(t+1)$ |
|-----|---|----------|
| 0 | x | $Q(t)$ |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Note that it is now impossible to have $S=R=1$.


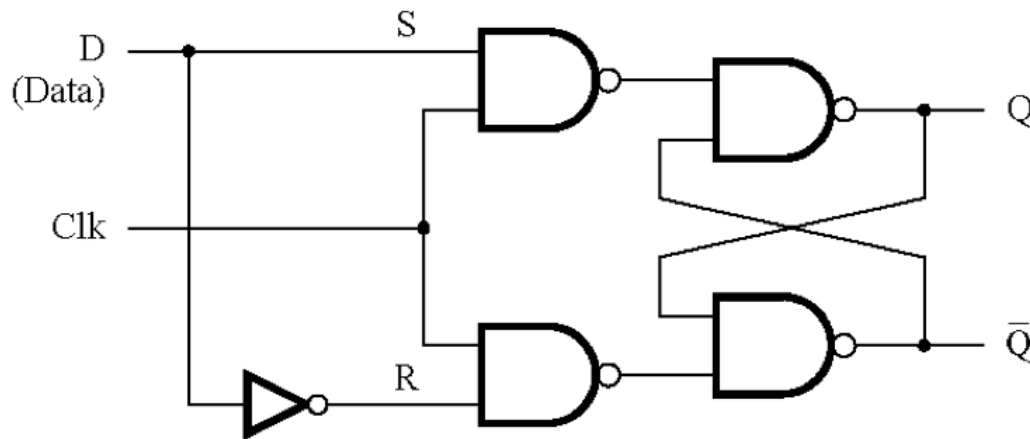
Circuit Diagram and Characteristic Table for the Gated D Latch





| Clk | D | $Q(t+1)$ |
|-----|---|----------|
| 0 | x | $Q(t)$ |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

When Clk=1 the output follows the D input.
When Clk=0 the output cannot be changed.

 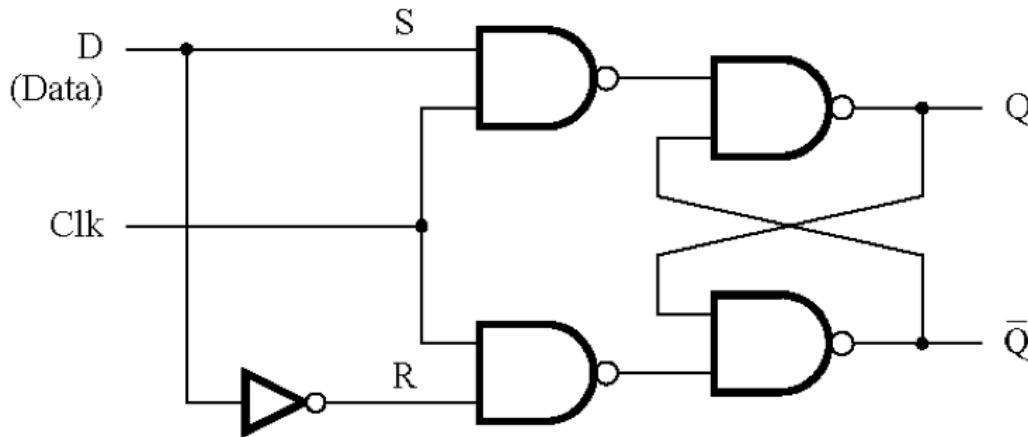Circuit Diagram and Graphical Symbol for the Gated D Latch




Timing Diagram for the Gated D Latch

 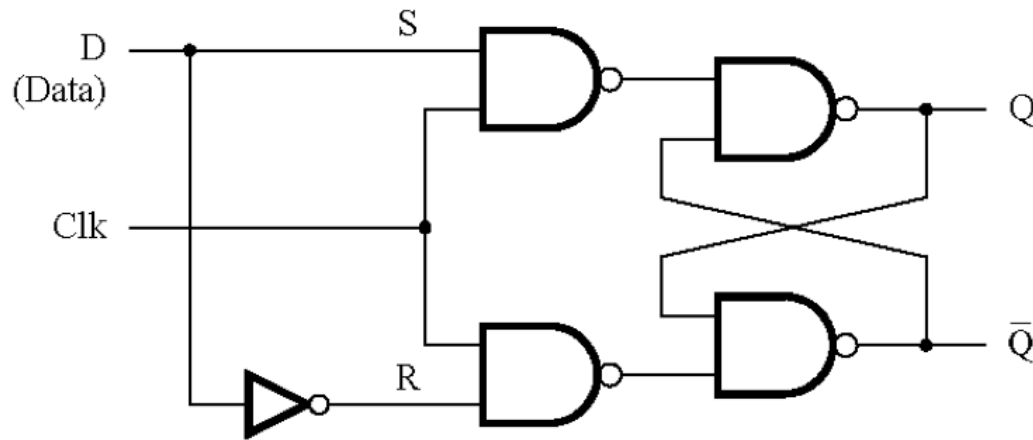


[Figure 5.7d from the textbook]

Timing Diagram for the Gated D Latch

 


Clk=0

the gate is closed

 


[Figure 5.7d from the textbook]

Timing Diagram for the Gated D Latch

 

Clk=0

the gate is closed

 


The output Q cannot *change* in these intervals.

Time →


[Figure 5.7d from the textbook]

Timing Diagram for the Gated D Latch

 


the gate is open

Clk=1

 


[Figure 5.7d from the textbook]

Timing Diagram for the Gated D Latch

 

Clk=1


the gate is open

 

The output Q is equal to D in these intervals.

[Figure 5.7d from the textbook]


Setup and hold times

 



Setup time (t_{su}) – the minimum time that the D signal must be stable prior to the the negative edge of the Clock signal.

Hold time (t_h) – the minimum time that the D signal must remain stable after the the negative edge of the Clock signal.

 Circuit Diagram for the Gated D Latch (with the latch implemented using NORs)




Circuit Diagram for the Gated D Latch (with the latch implemented using NORs)

  

[Figure 5.7a from the textbook]

[https://en.wikibooks.org/wiki/Digital_Circuits/Latches]

 
Circuit Diagram for the Gated D Latch (with the latch implemented using NORs)



The NOT gate is now in a different place.
Also, S and R are swapped.


Alternative Design for the Gated D Latch

Circuit Diagram for the Gated D Latch

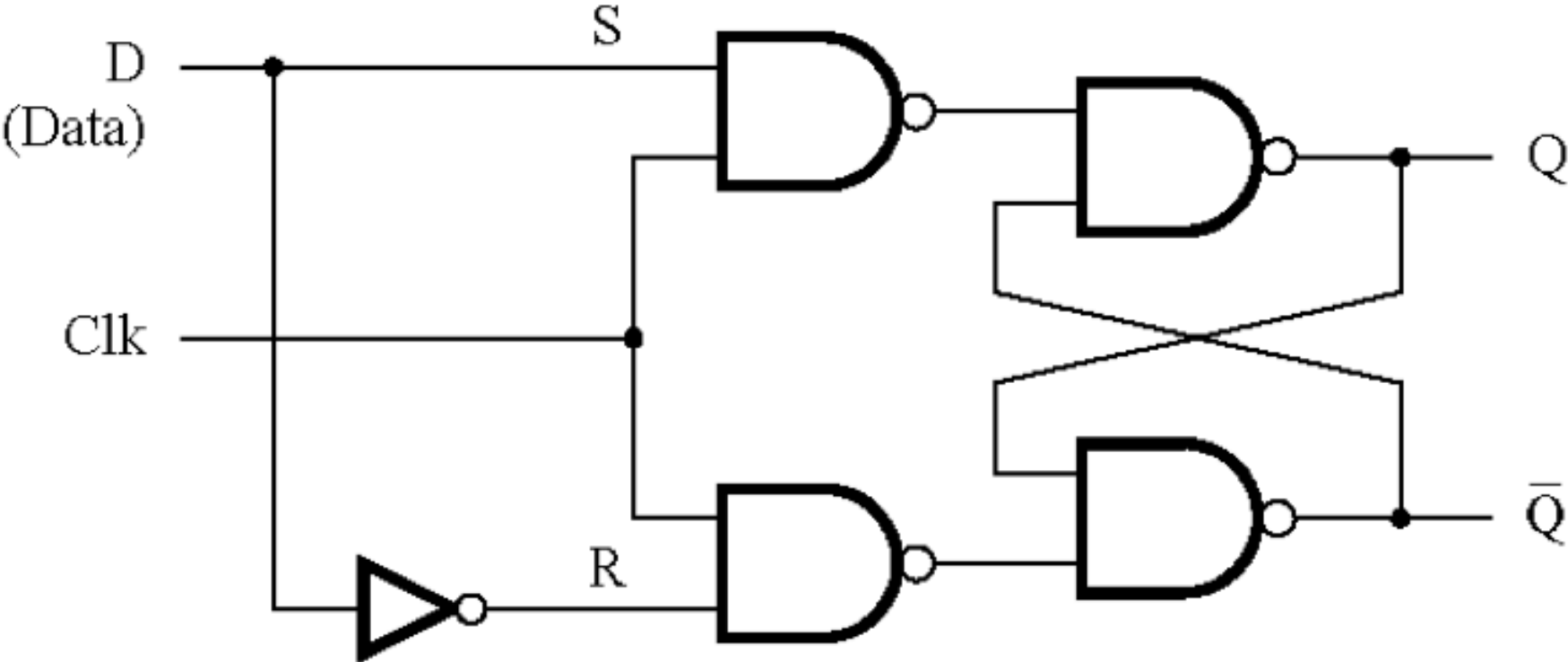

[Figure 5.7a from the textbook]


Gated D Latch: Alternative Design

 


Master-Slave D Flip-Flop

Constructing a Master-Slave D Flip-Flop From Two D Latches

Master Latch

 


Slave Latch

 

Constructing a Master-Slave D Flip-Flop From Two D Latches

Master Latch


Slave Latch

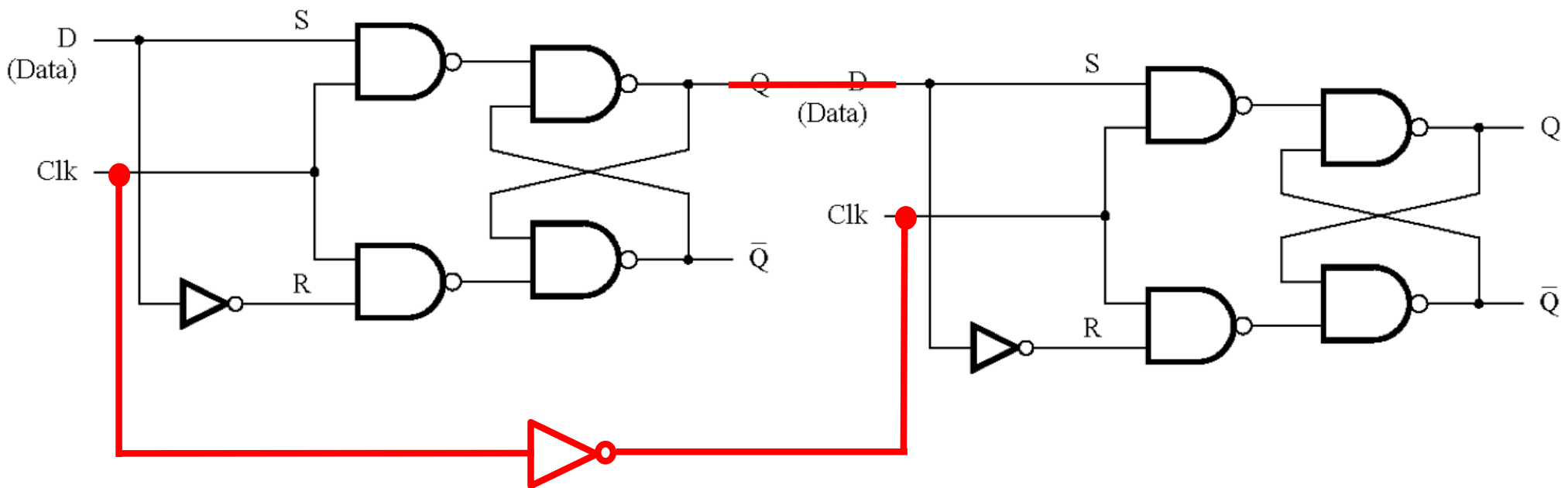


Constructing a Master-Slave D Flip-Flop From Two D Latches

Master Latch

Slave Latch

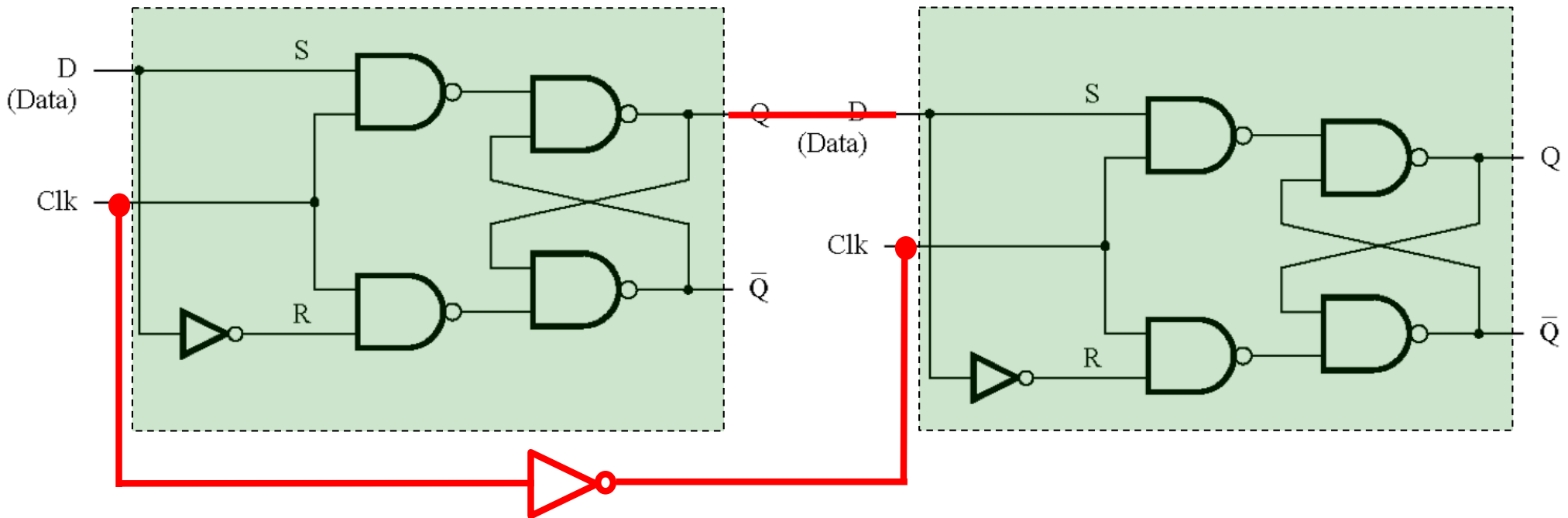


Constructing a Master-Slave D Flip-Flop From Two D Latches

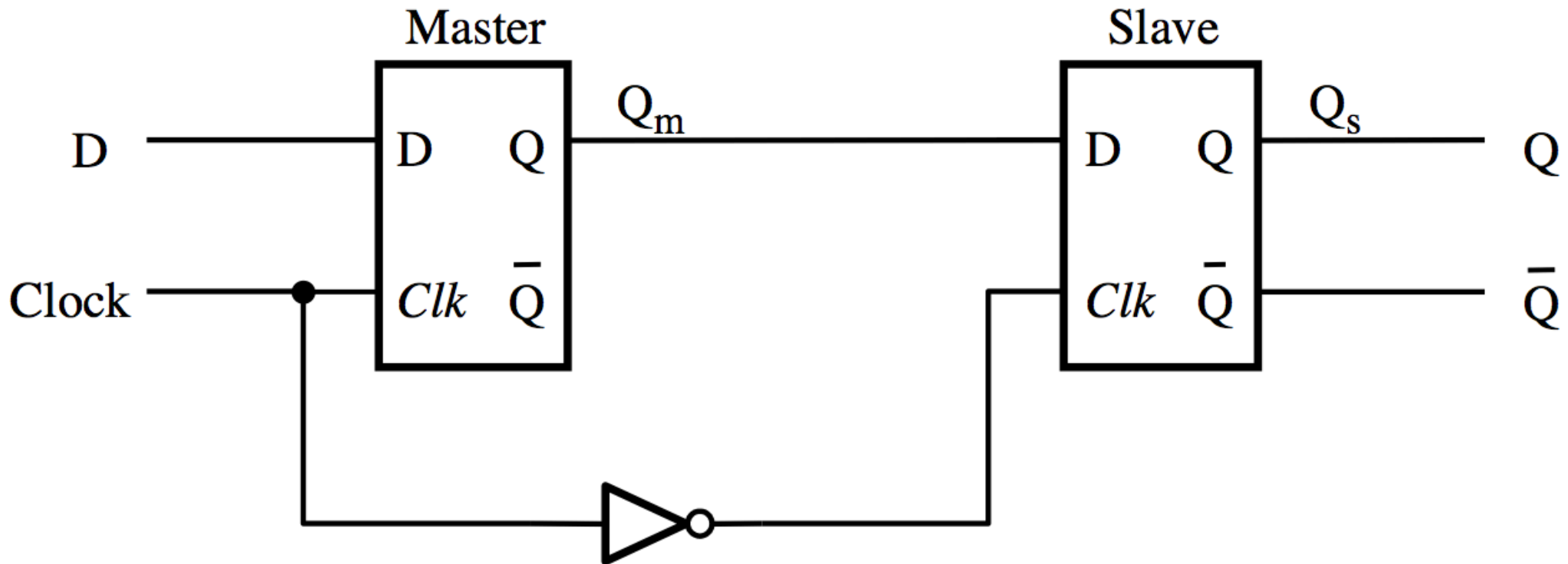


[Figure 5.9a from the textbook]

Clock is used for the D Flip-Flop

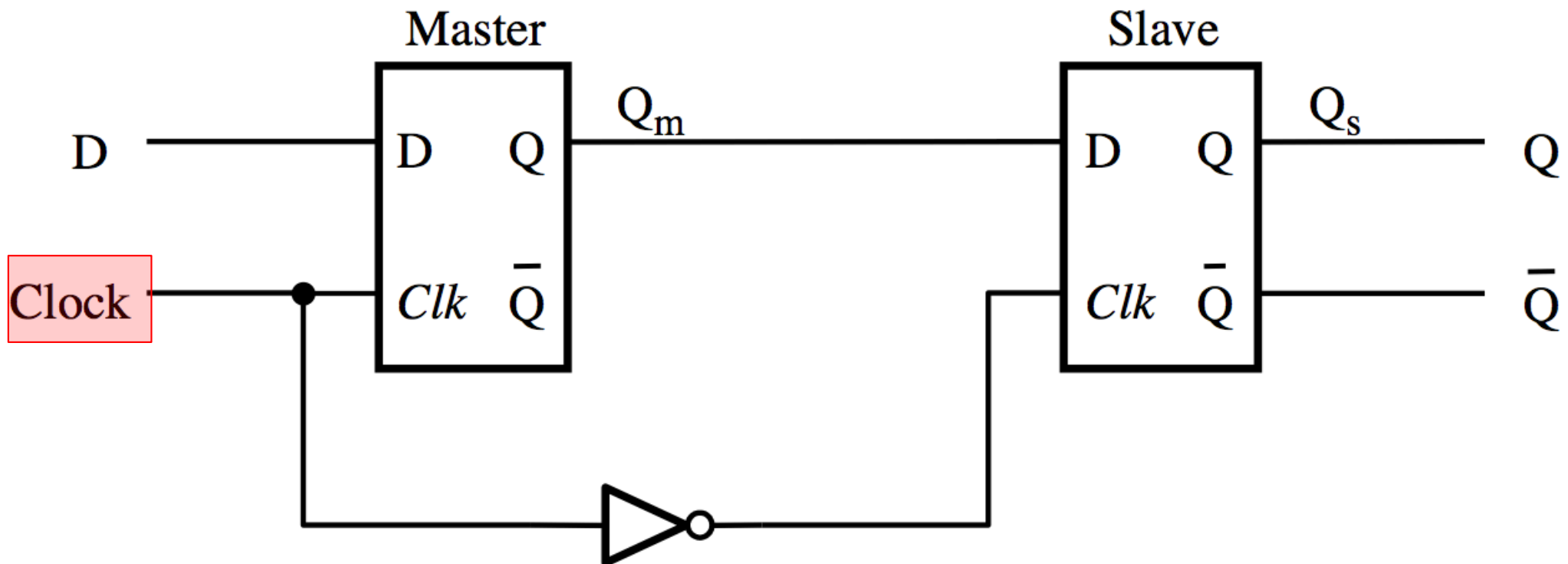

[Figure 5.9a from the textbook]

Clock is used for the D Flip-Flop, but Clk is used for each D Latch

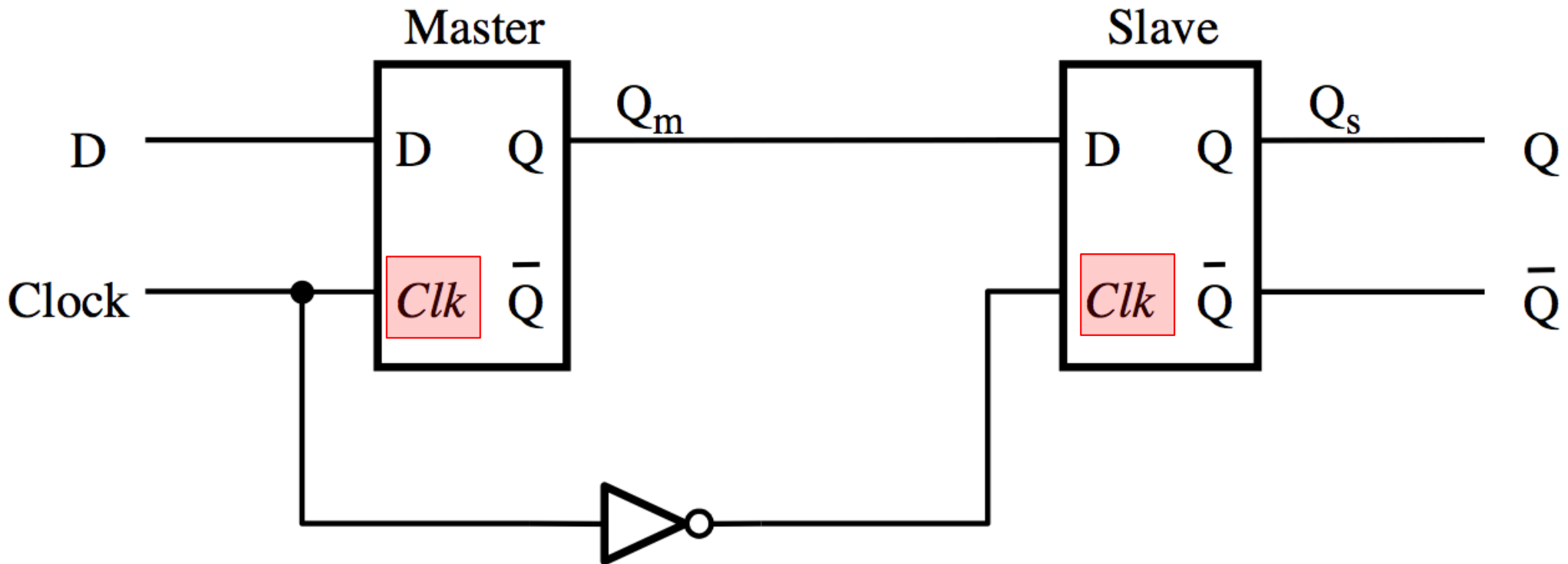


[Figure 5.9a from the textbook]


Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

Master Latch

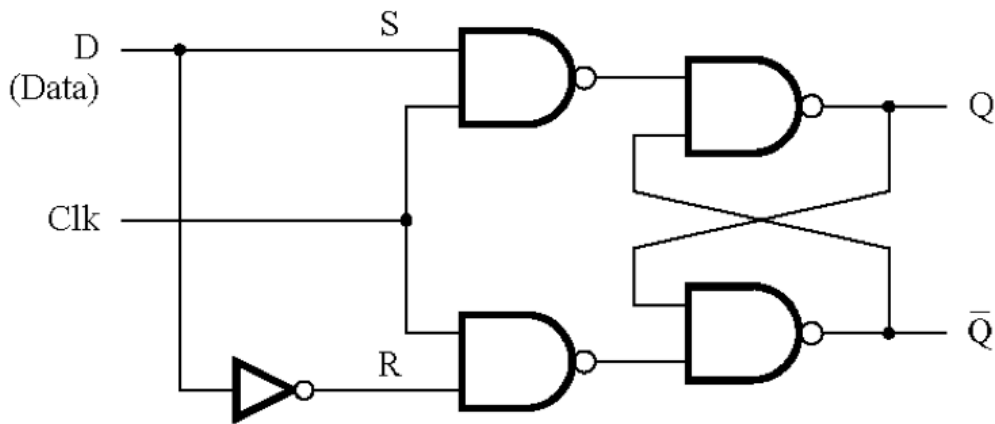


Slave Latch

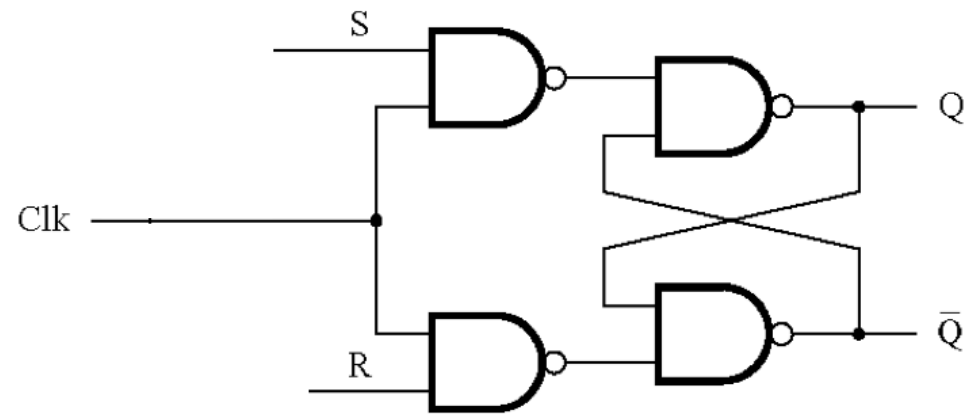

Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

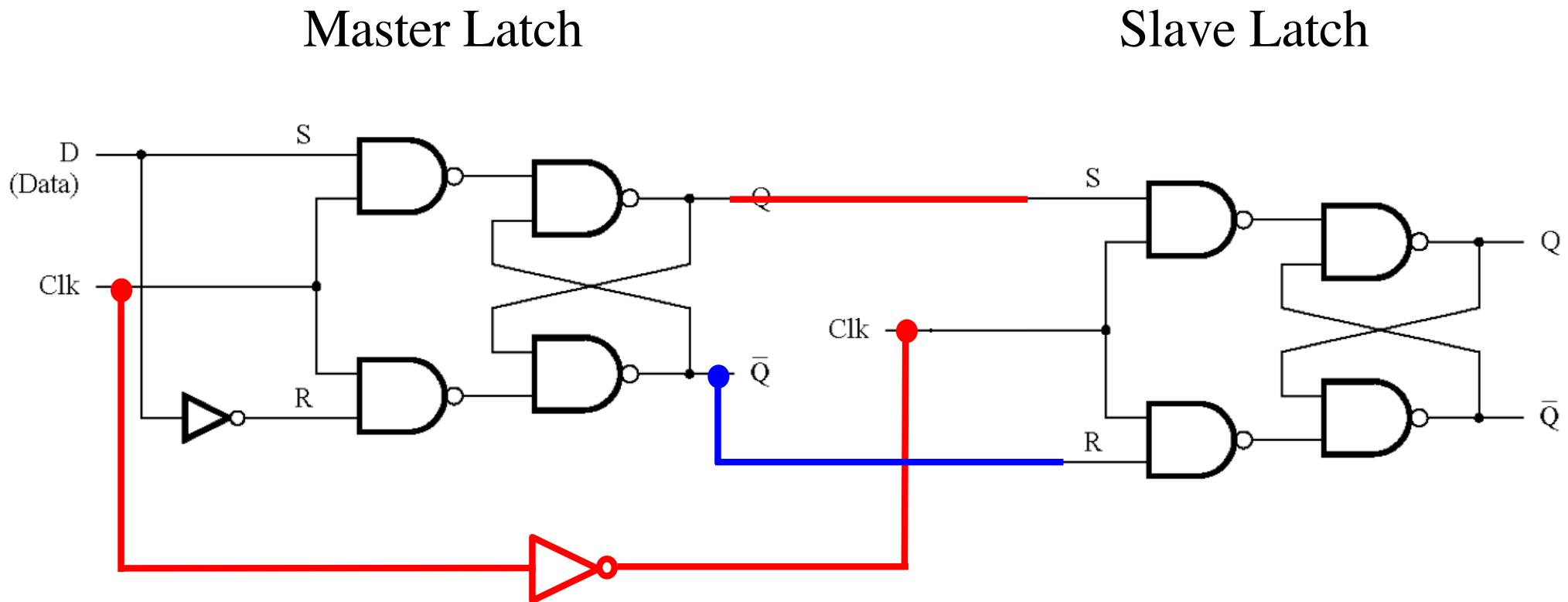

Flip-Flop



Latch



You need 2 latches to make a flip-flop




=



You need 2 latches to make a flip-flop

Master Latch


Slave Latch

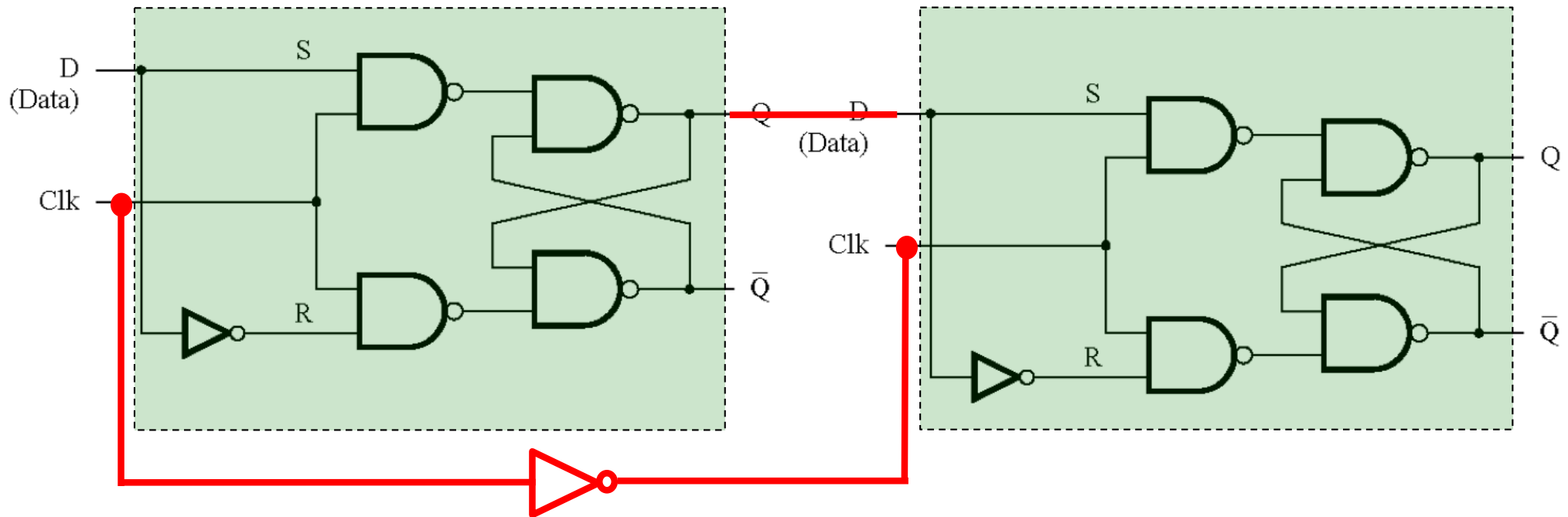

You need 2 latches to make a flip-flop

Master Latch

Slave Latch

 

You need 2 latches to make a flip-flop




Edge-Triggered D Flip-Flops

Motivation



In some cases we need to use a memory storage device that can change its state no more than once during each clock cycle.

Master-Slave D Flip-Flop

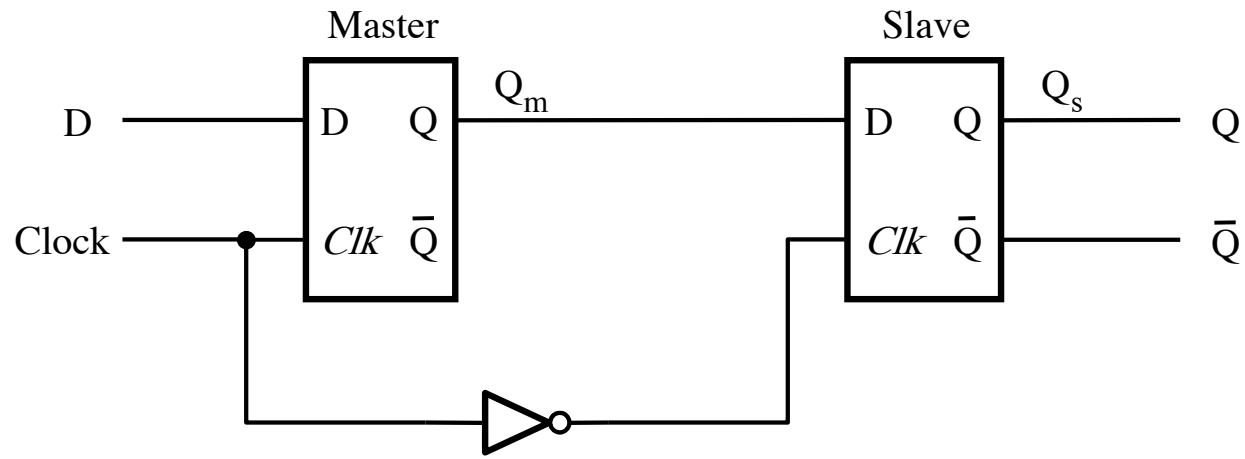


(a) Circuit

Timing Diagram for the Master-Slave D Flip-Flop

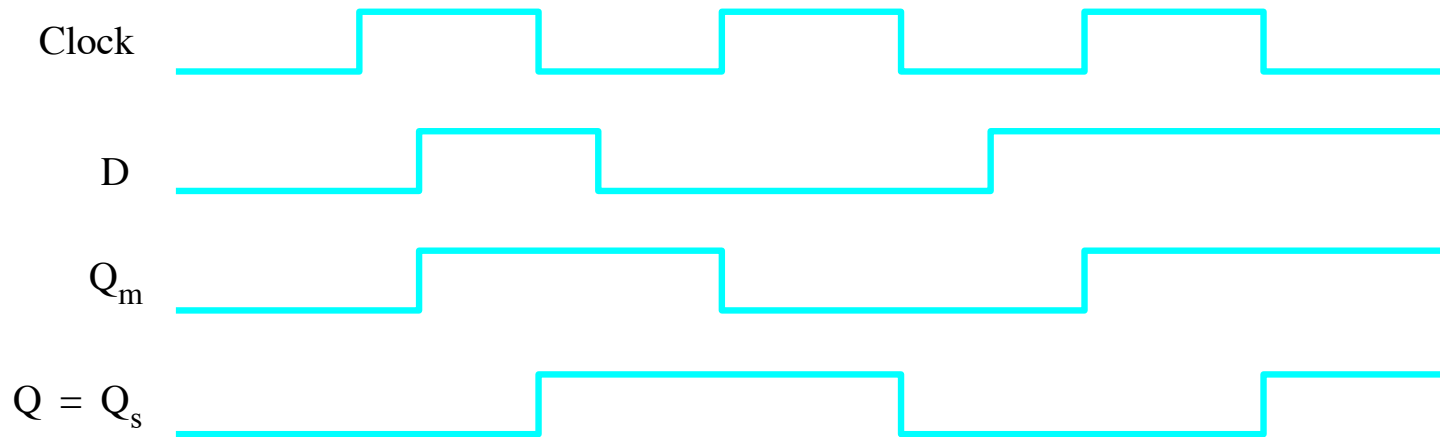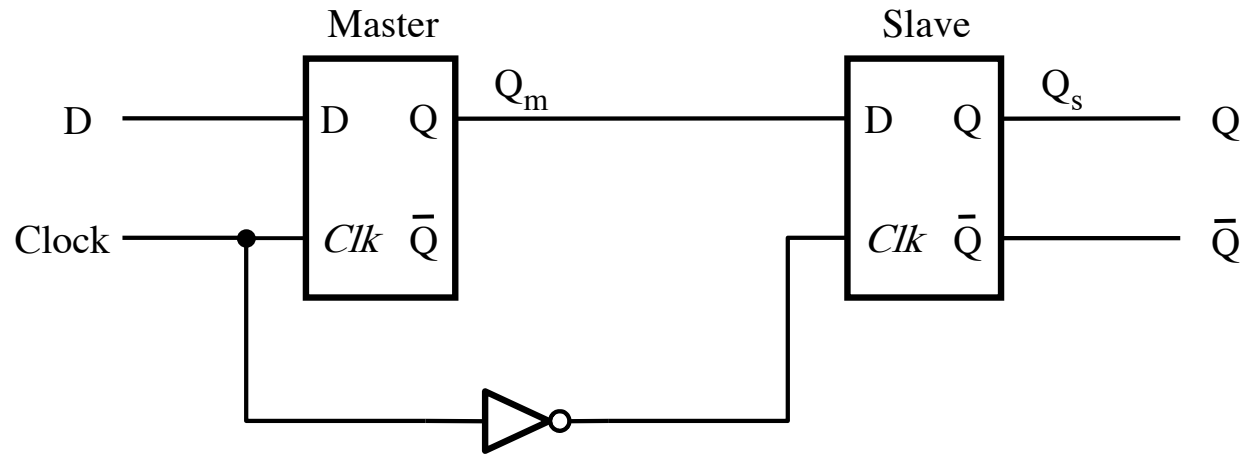


[Figure 5.9a,b from the textbook]

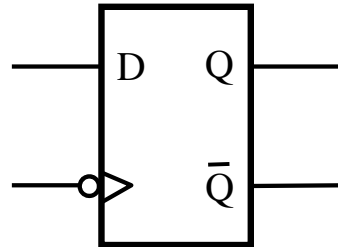Graphical Symbol for the Master-Slave D Flip-Flop



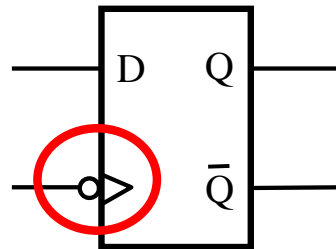
Graphical Symbol for the Master-Slave D Flip-Flop




The $>$ means that this is edge-triggered

The small circle means that it is the negative edge

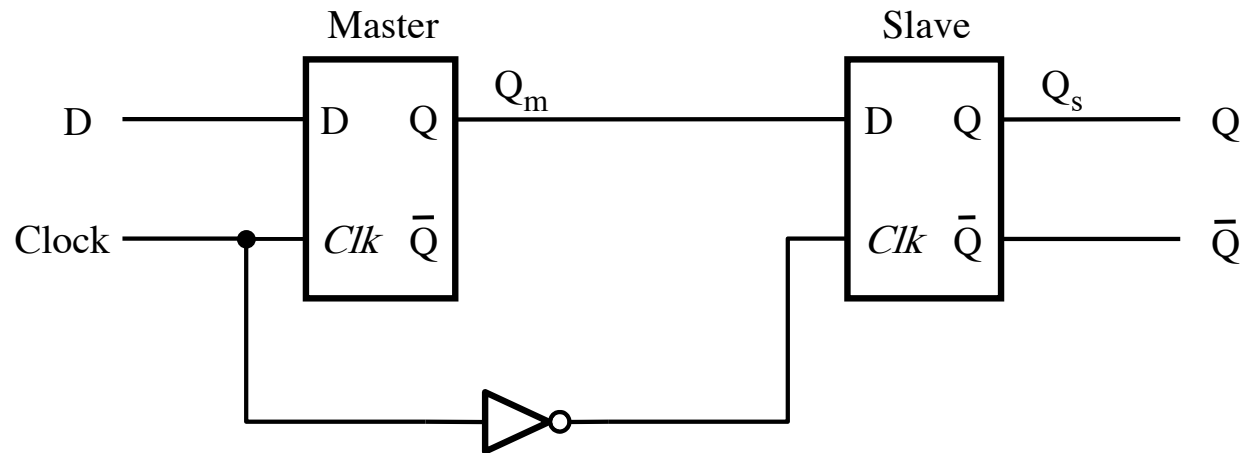
Negative-Edge-Triggered Master-Slave D Flip-Flop



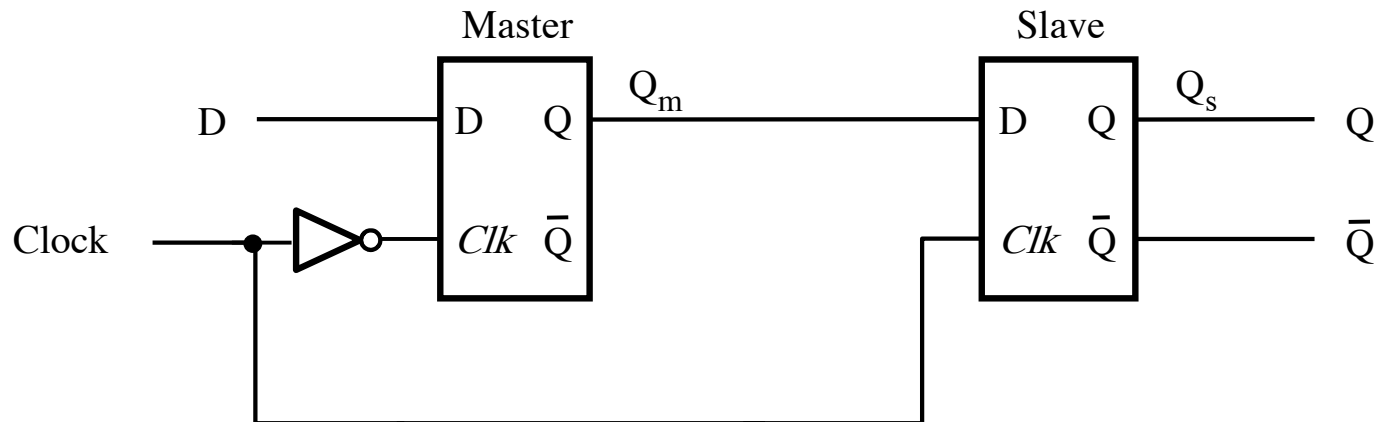
Positive-Edge-Triggered Master-Slave D Flip-Flop



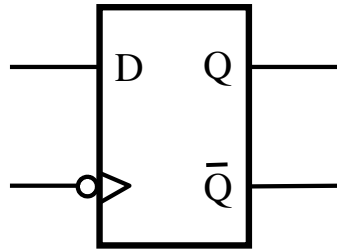Negative-Edge-Triggered Master-Slave D Flip-Flop




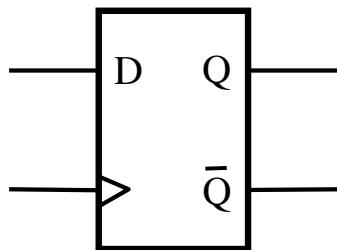Positive-Edge-Triggered Master-Slave D Flip-Flop




D Flip-Flop: A Double Door Analogy

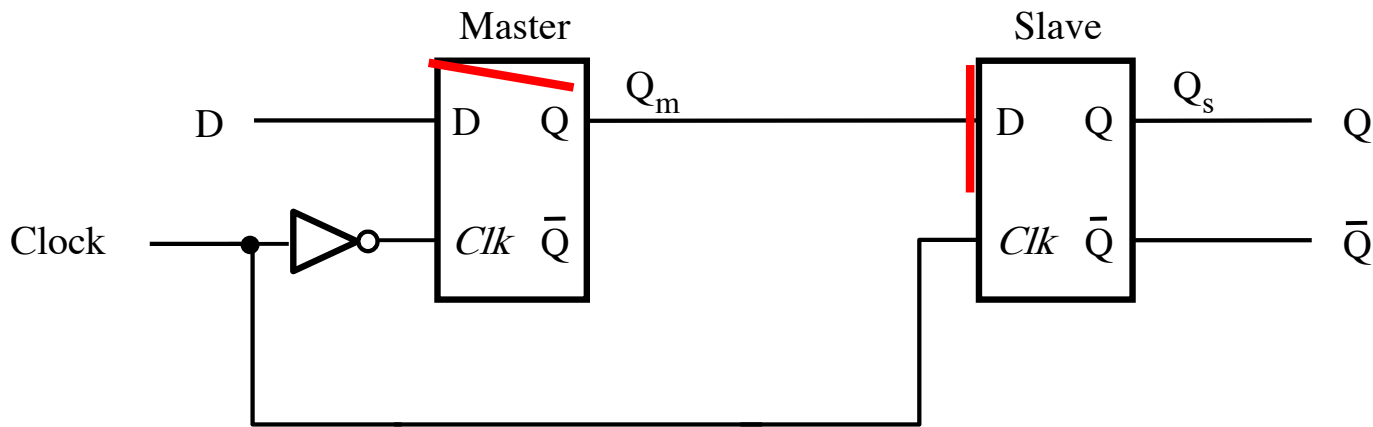
Positive-Edge-Triggered Master-Slave D Flip-Flop



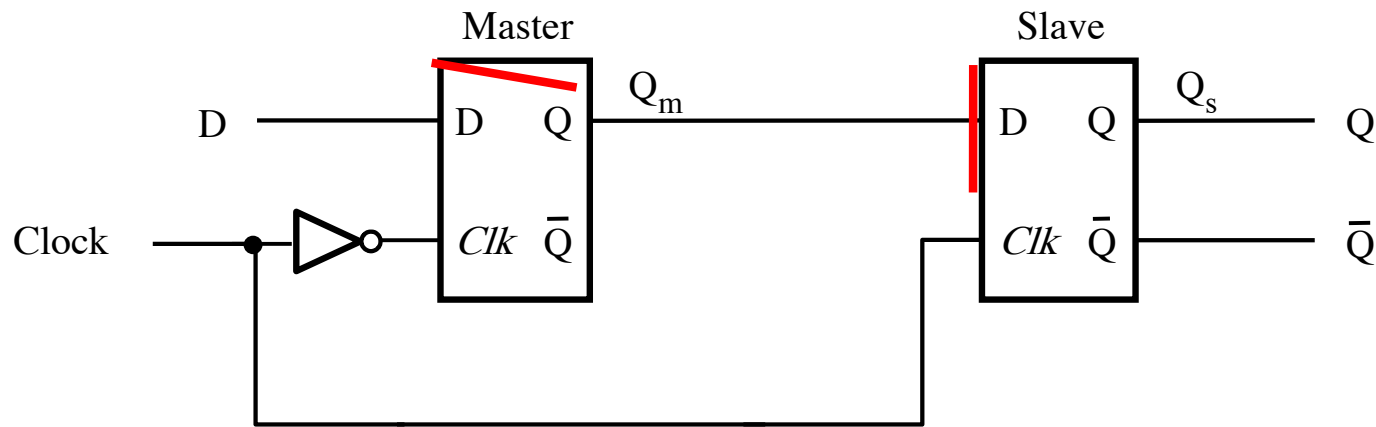
Positive-Edge-Triggered Master-Slave D Flip-Flop



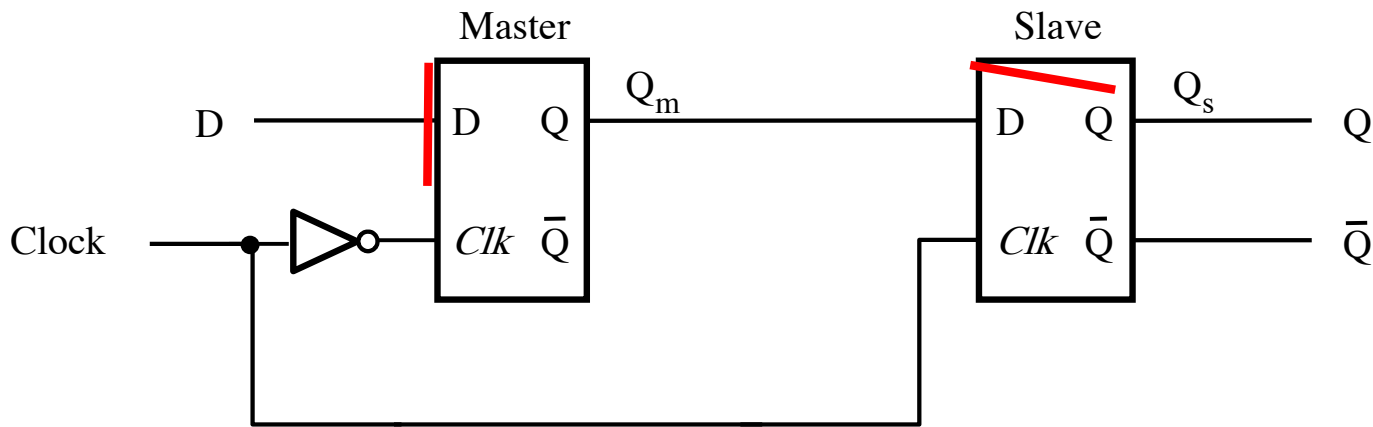
Positive-Edge-Triggered Master-Slave D Flip-Flop



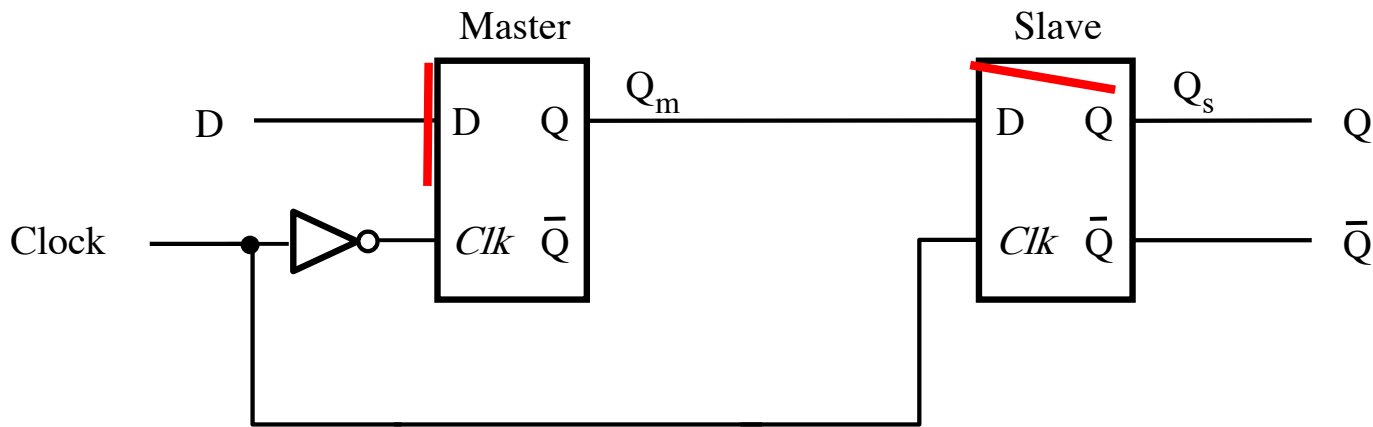
Positive-Edge-Triggered Master-Slave D Flip-Flop



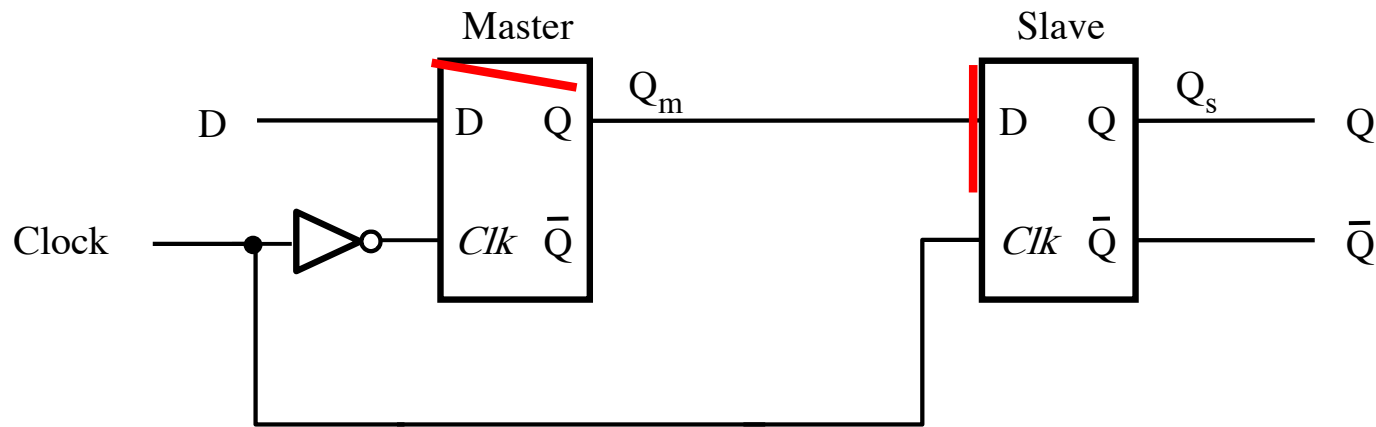
Positive-Edge-Triggered Master-Slave D Flip-Flop



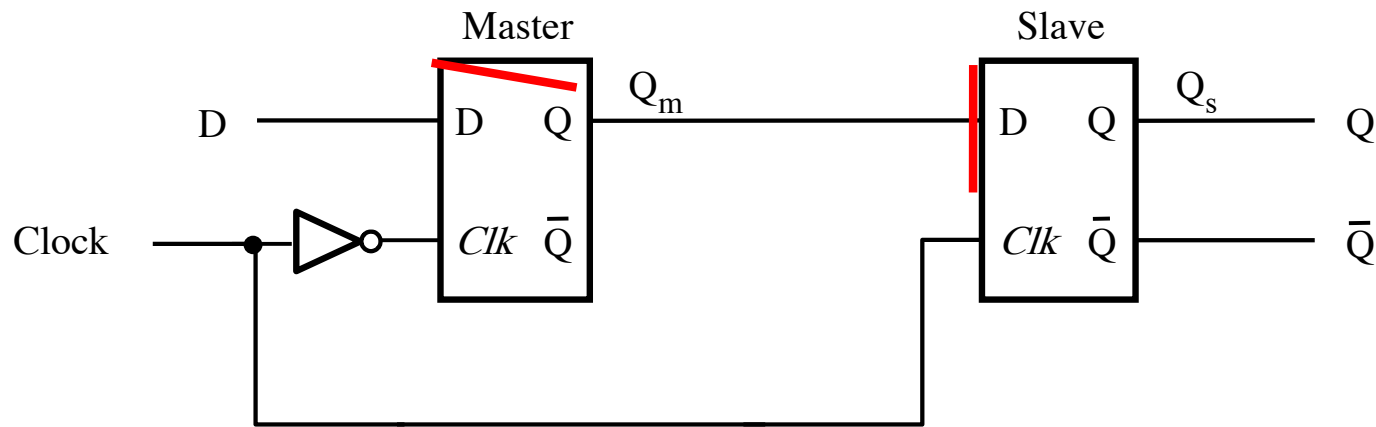
Positive-Edge-Triggered Master-Slave D Flip-Flop



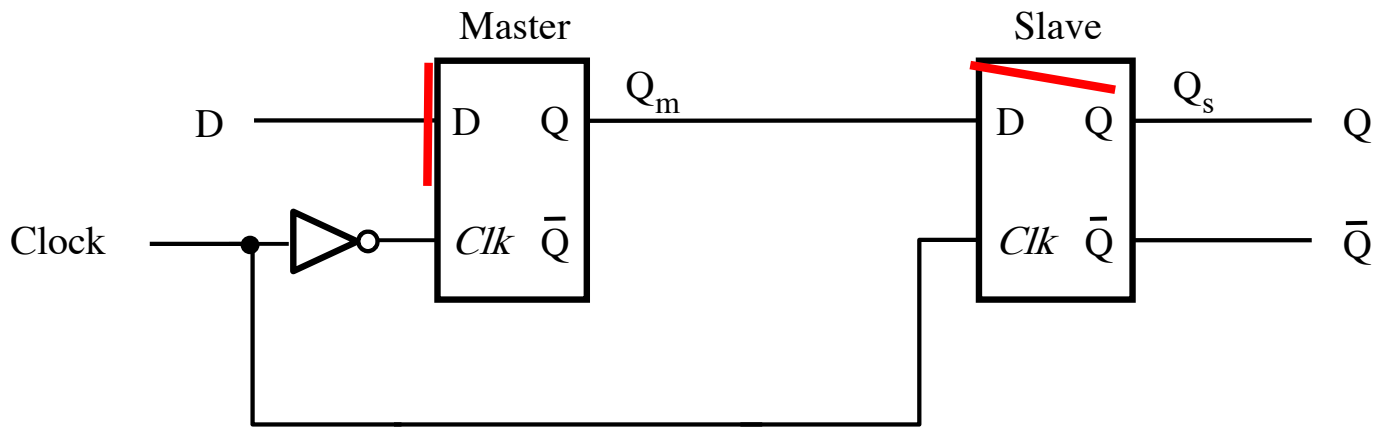
Positive-Edge-Triggered Master-Slave D Flip-Flop



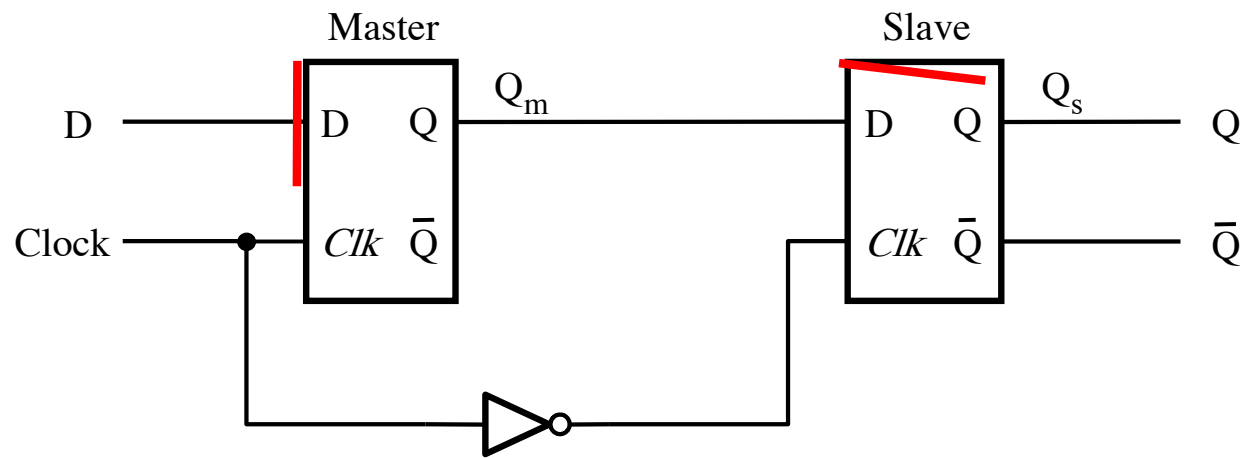
Negative-Edge-Triggered Master-Slave D Flip-Flop



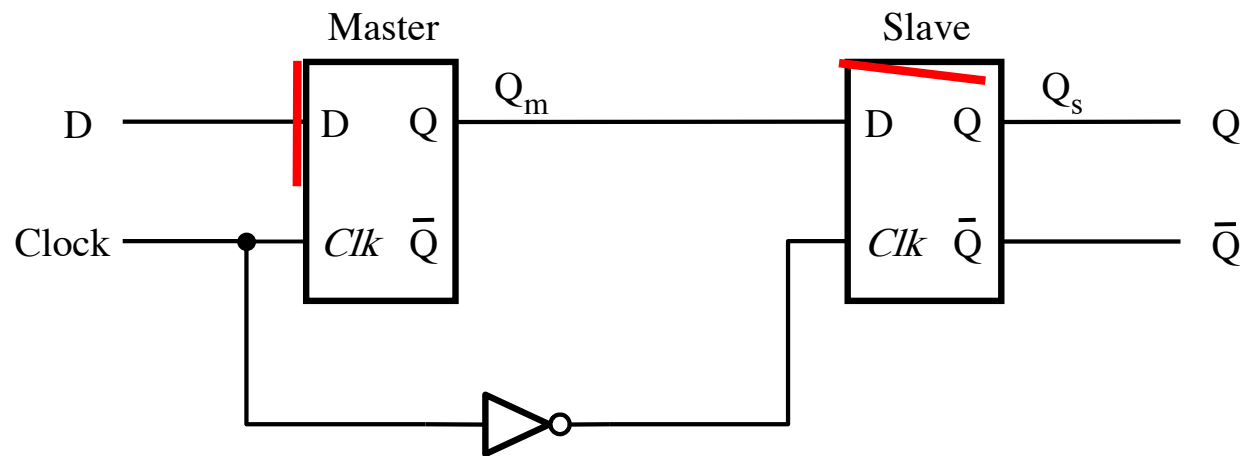
Negative-Edge-Triggered Master-Slave D Flip-Flop



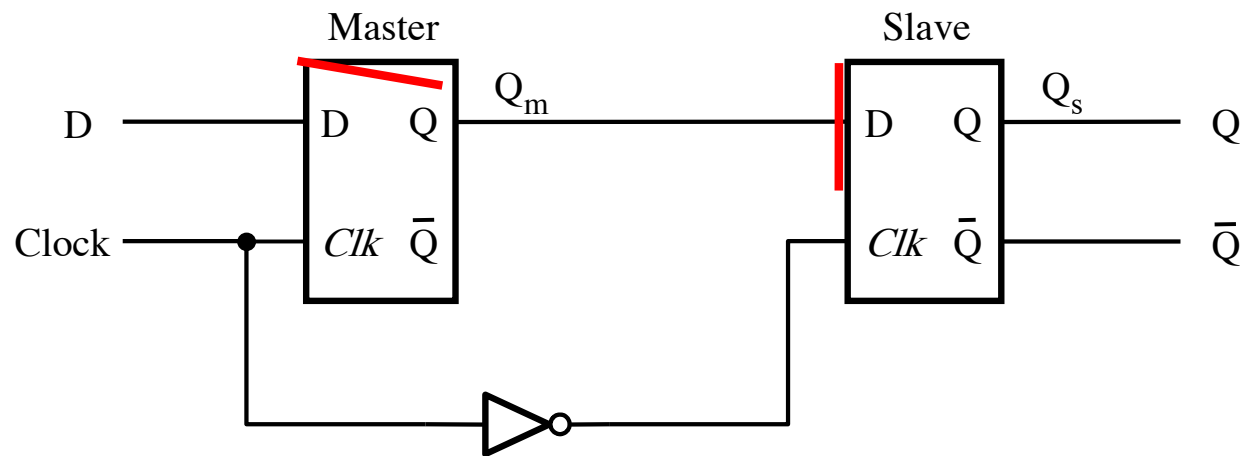
Negative-Edge-Triggered Master-Slave D Flip-Flop



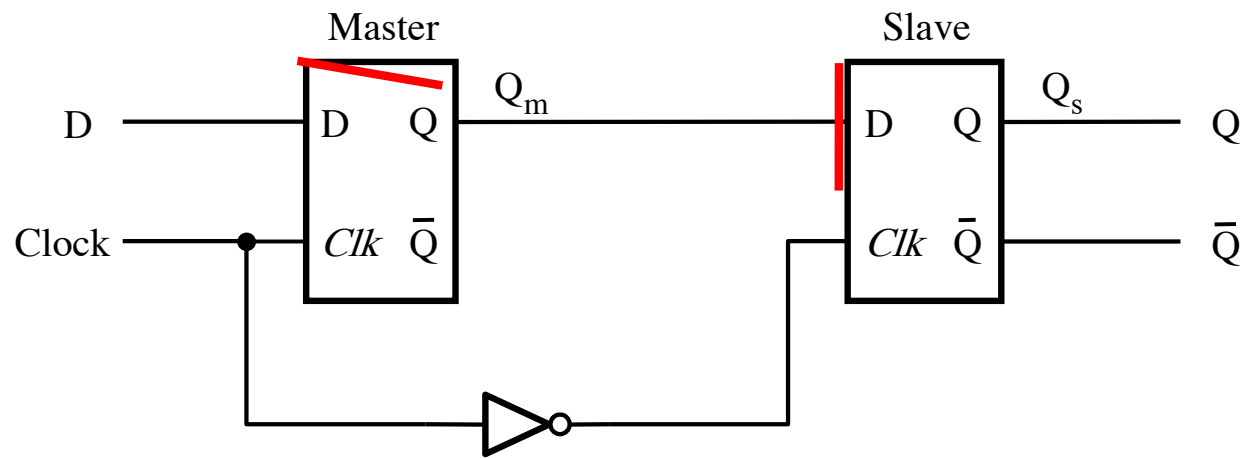
Negative-Edge-Triggered Master-Slave D Flip-Flop



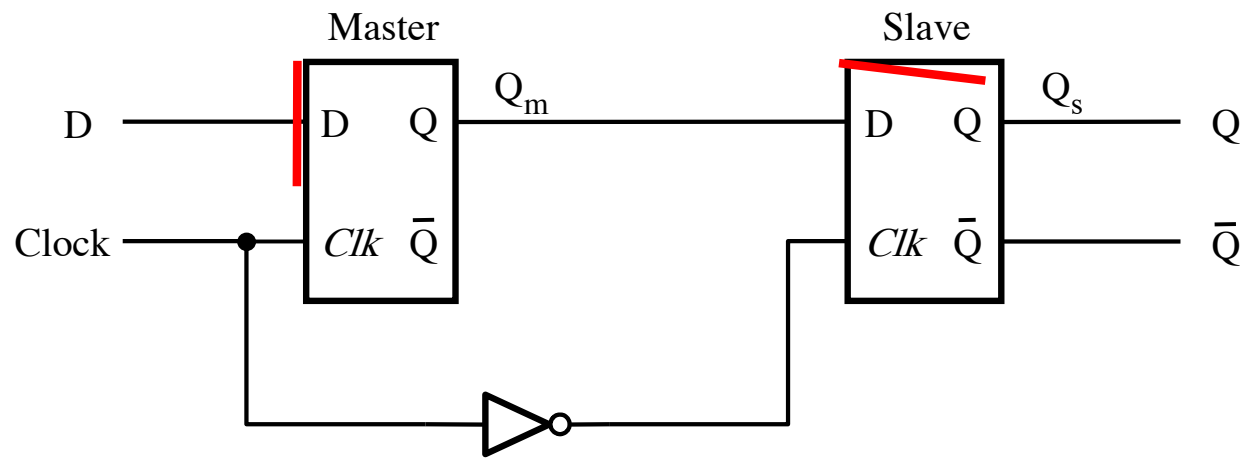
Negative-Edge-Triggered Master-Slave D Flip-Flop



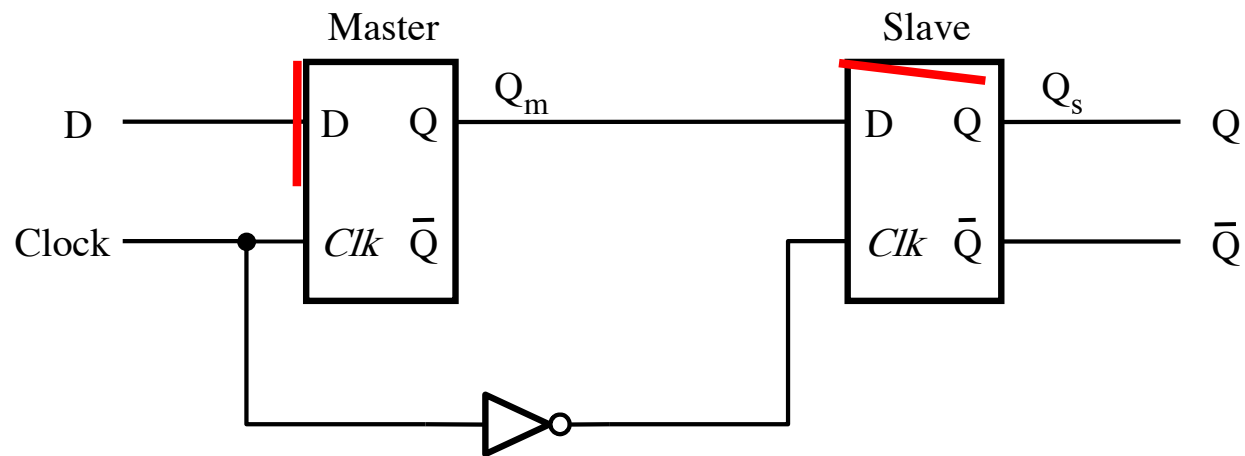Negative-Edge-Triggered Master-Slave D Flip-Flop





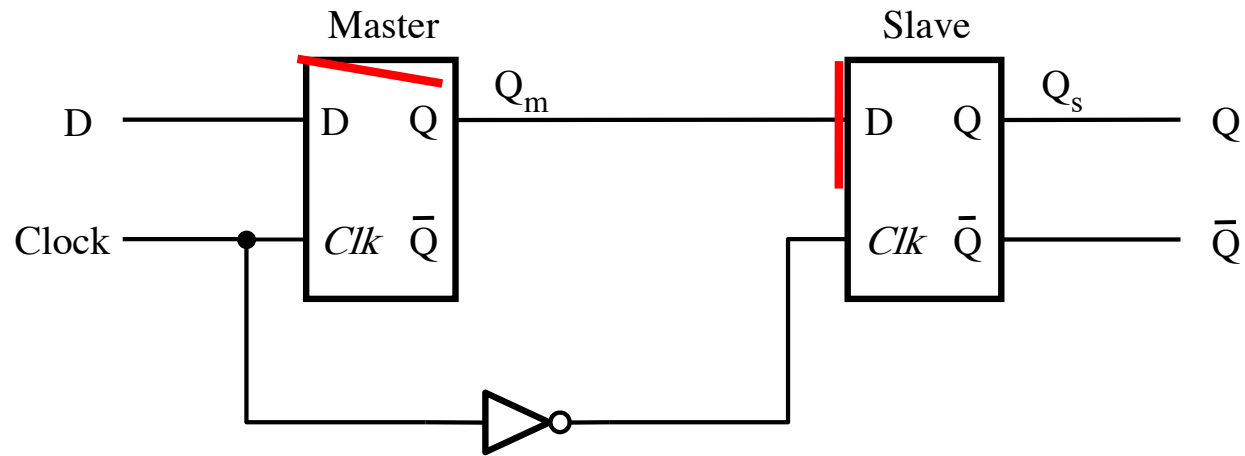Negative-Edge-Triggered Master-Slave D Flip-Flop




Level-Sensitive v.s. Edge-Triggered

 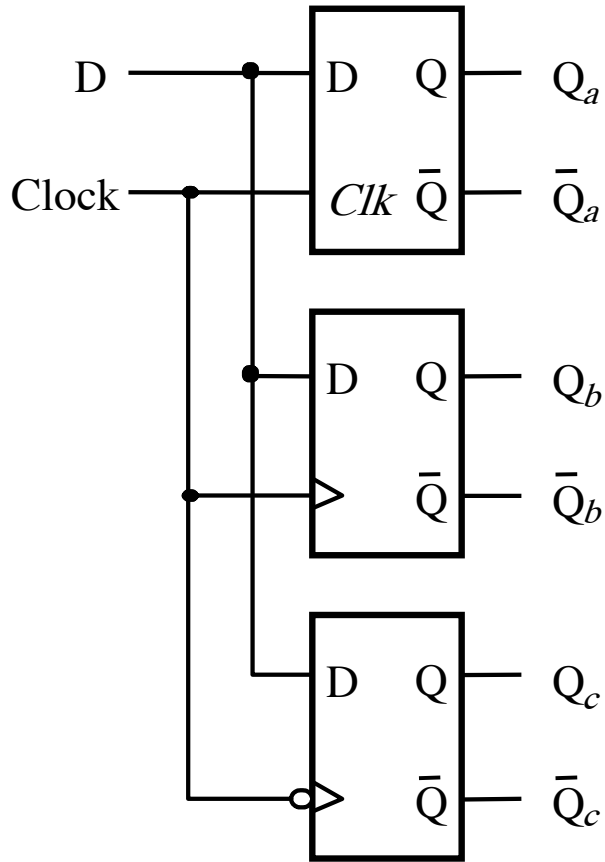
Comparison of level-sensitive and edge-triggered D storage elements



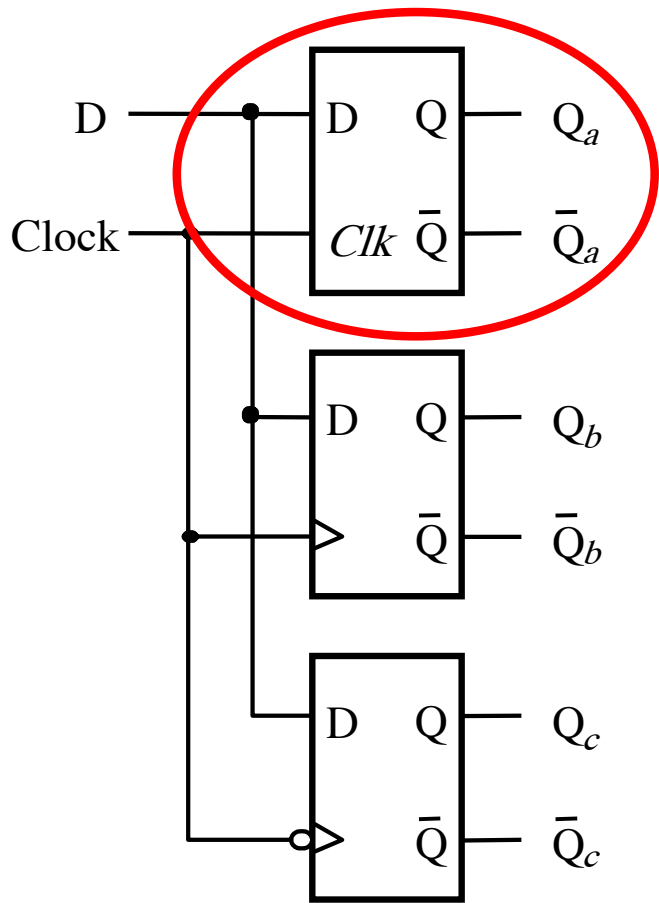
Comparison of level-sensitive and edge-triggered D storage elements



 
The D Latch is Level-Sensitive
(the output mirrors the D input when Clk=1)



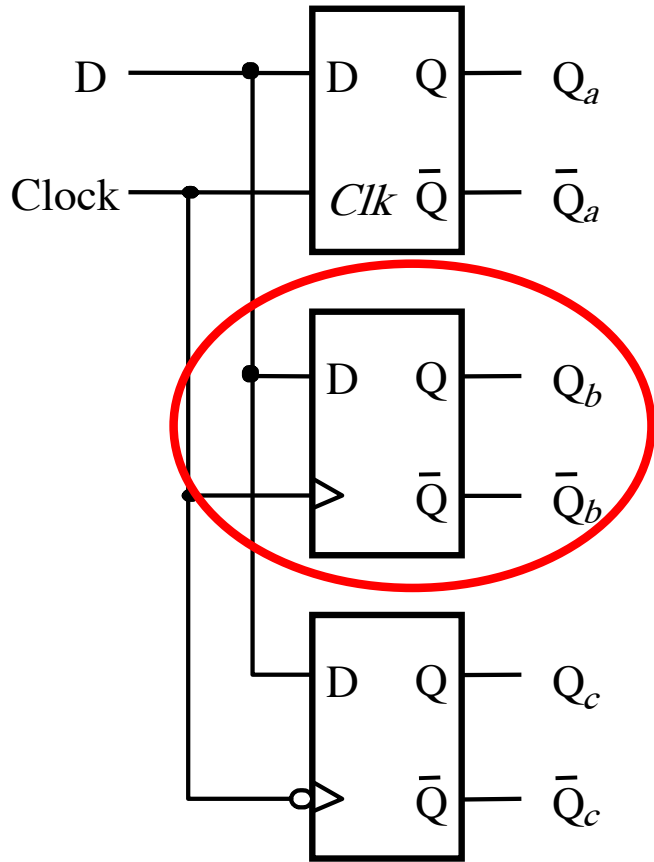
Comparison of level-sensitive and edge-triggered D storage elements



 
Positive-edge-triggered D Flip-Flop
(the output is equal to the value of D right at the positive edge of the clock signal)



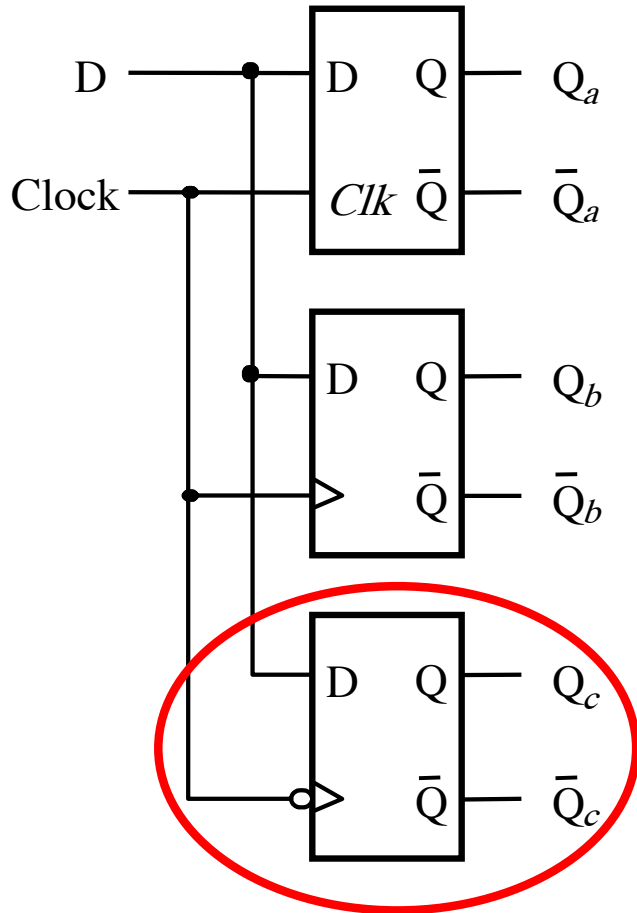Comparison of level-sensitive and edge-triggered D storage elements



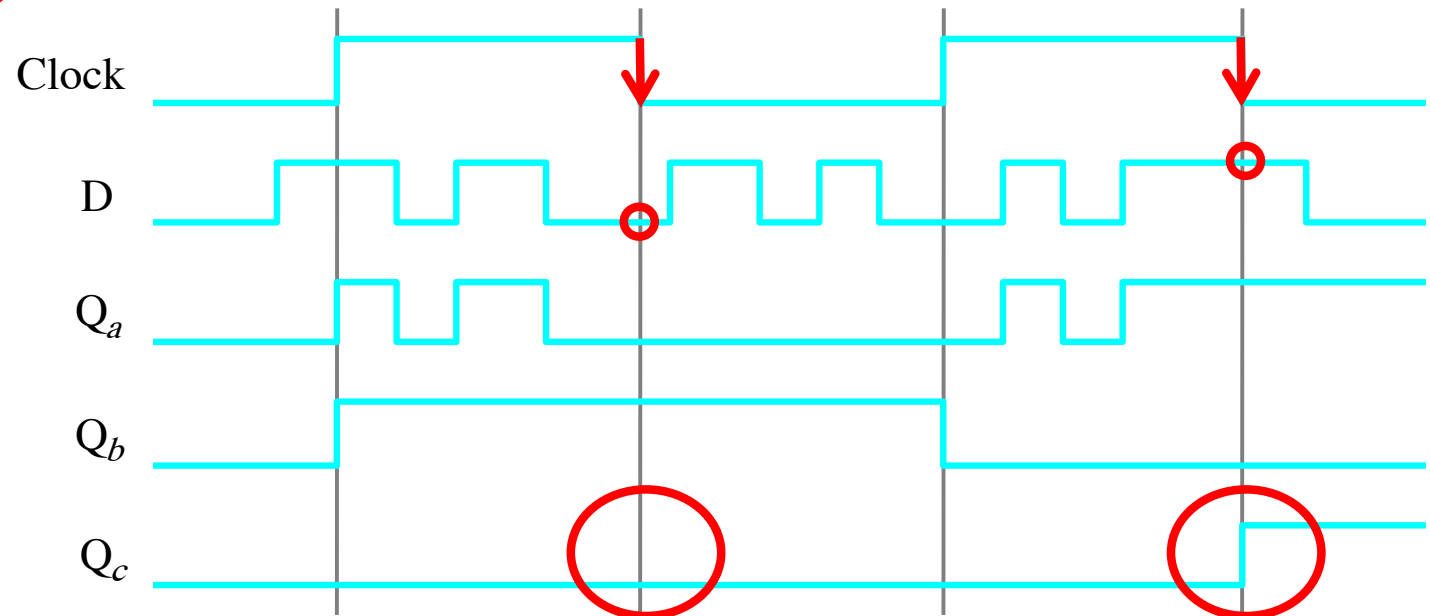
Negative-edge-triggered D Flip-Flop
(the output is equal to the value of D right at the negative edge of the clock signal)



Positive-edge-triggered D flip-flop with Clear and Preset

Positive-edge-triggered D flip-flop with Clear_n and Preset_n

 
Positive-edge-triggered D flip-flop with **Synchronous Clear**



 
(c) Adding a synchronous clear

The output Q can be cleared only on the positive clock edge.


The Complete Wiring Diagram for a Positive-Edge-Triggered D Flip-Flop




Adding an Asynchronous Clear

 


Adding an Asynchronous Preset

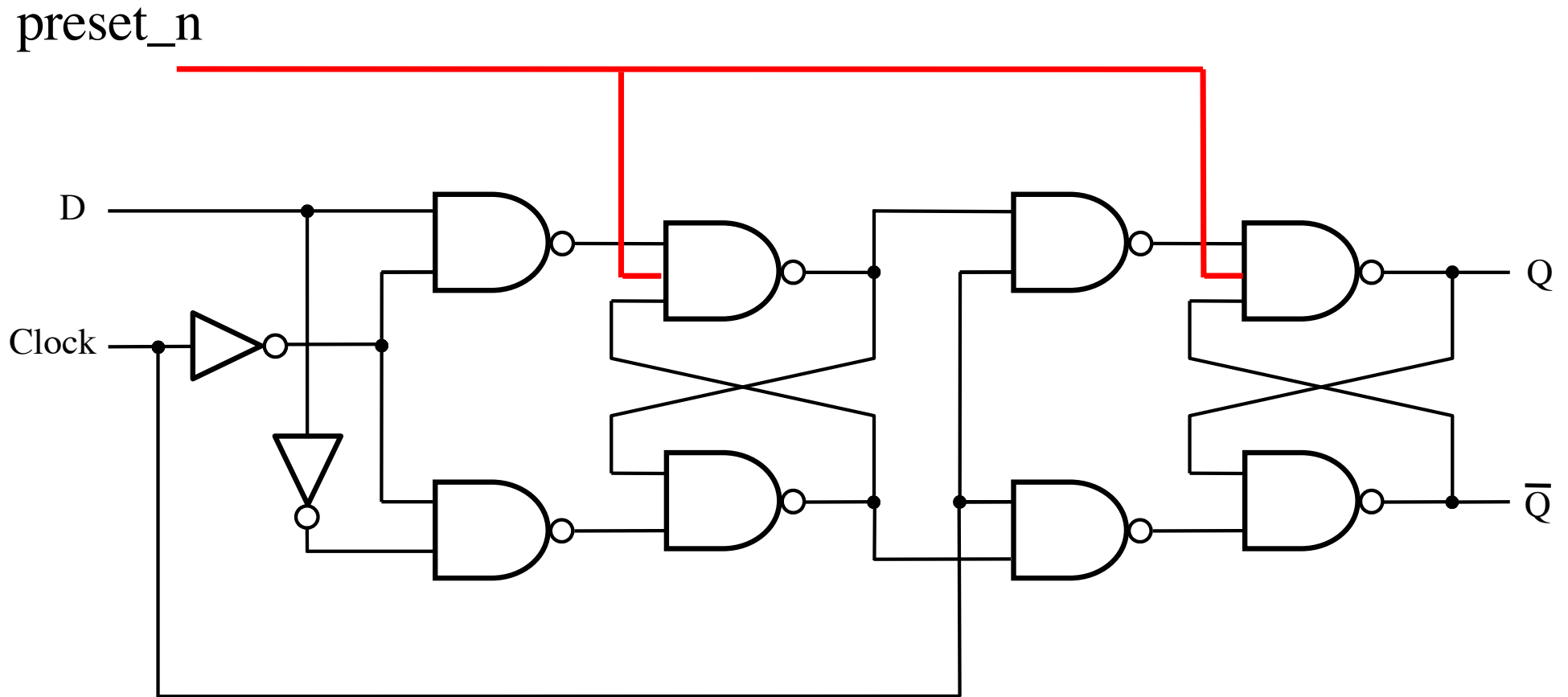

 Positive-Edge-Triggered D Flip-Flop with **Asynchronous** Clear and Preset




 Positive-edge-triggered D flip-flop with asynchronous Clear and Preset



 
(b) Graphical symbol

For normal operation both must be set to 1



 
(b) Graphical symbol

A zero on clear_n drives the output Q to zero



 (b) Graphical symbol


A zero on preset_n drives the output Q to one



(b) Graphical symbol


The output is indeterminate if both are zero

don't ever
use this one

 


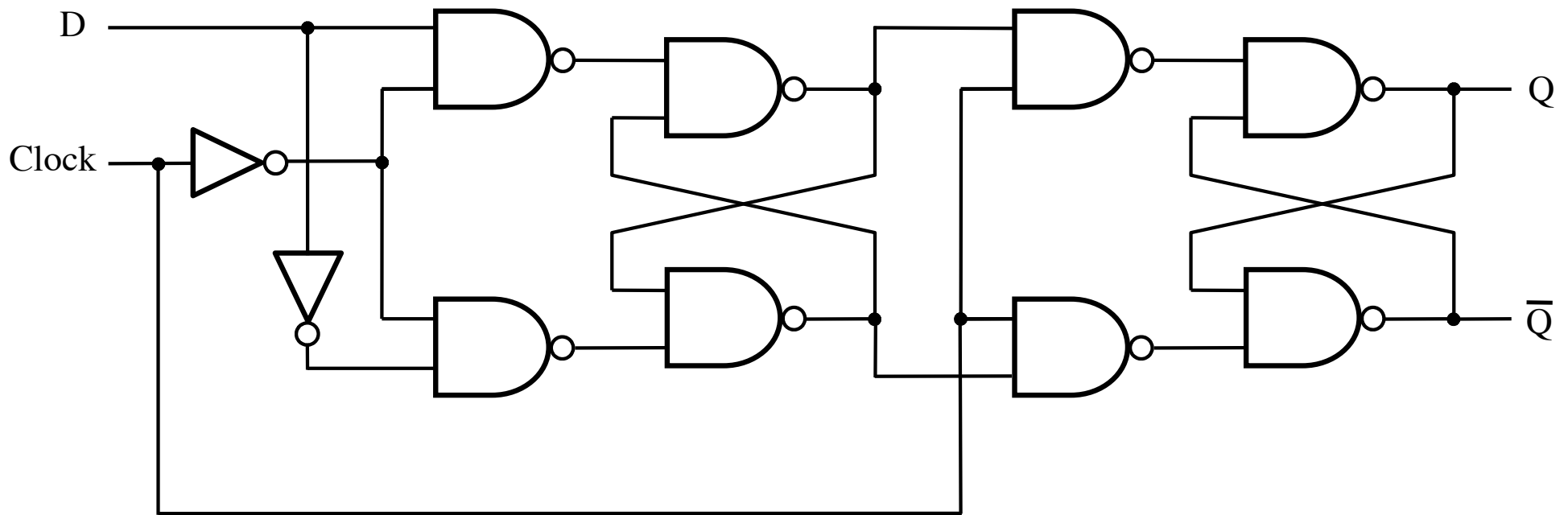(b) Graphical symbol


The Complete Wiring Diagram for a Positive-Edge-Triggered D Flip-Flop



 
The Complete Wiring Diagram for a **Negative**-Edge-Triggered D Flip-Flop



 
The Complete Wiring Diagram for a **Negative**-Edge-Triggered D Flip-Flop



 Negative-Edge-Triggered D flip-flop with asynchronous Clear and Preset




(a) Circuit

 


(b) Graphical symbol

[Figure 5.12 from the textbook]

Flip-Flop Timing Parameters

 

(a) D flip-flop with asynchronous clear

 


[Figure 5.14 from the textbook]


(b) Timing diagram

An alternative D Flip-Flop Design

A positive-edge-triggered D flip-flop

 


(a) Circuit

 

 
(b) Graphical symbol

A positive-edge-triggered D flip-flop

This circuit behaves like a positive-edge-triggered D flip-flop, but it uses only 6 NAND gates. Thus, it can be implemented with fewer transistors than the master-slave D flip-flop.




(a) Circuit

 

(b) Graphical symbol

Positive-edge-triggered D flip-flop with **asynchronous** Clear and Preset

 

[Figure 5.13a from the textbook]

Terminology

- **Basic Latch** – is a feedback connection of two NOR gates or two NAND gates, which can store one bit of information. It can be set using the S input and reset to 0 using the R input.
- **Gated Latch** – is a basic latch that includes input gating and a control input signal. The latch retains its existing state when the control input is equal to 0. Its state may be changed when the control signal is equal to 1.

Terminology

- **Two types of gated latches**
(the control input is the clock):
- **Gated SR Latch** – uses the S and R inputs to set the latch to 1 or reset it to 0.
- **Gated D Latch** – uses the D input to force the latch into a state that has the same logic value as the D input.

Terminology

- **Flip-Flop** – is a storage element that can have its output state changed only on the edge of the controlling clock signal.
- **Positive-edge triggered** – if the state changes when the clock signal goes from 0 to 1.
- **Negative-edge triggered** – if the state changes when the clock signal goes from 1 to 0.

Terminology

The word ***latch*** is mainly used for storage elements, while clocked devices are described as ***flip-flops***.

A **latch** is level-sensitive, whereas a **flip-flop** is edge-sensitive. That is, when a latch is enabled it becomes transparent, while a flip flop's output only changes on a single type of clock edge (positive going or negative going).

Questions?

THE END