
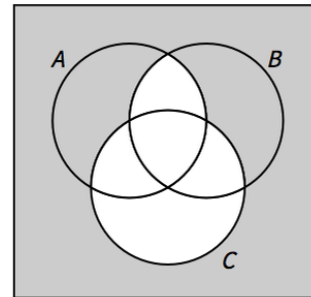
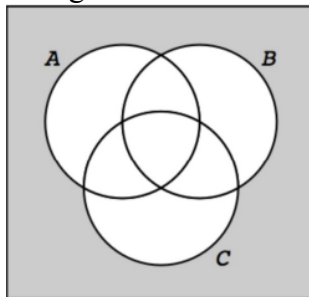


P1. (10 points)

- Convert BEEF₁₆ to binary.
- Convert BEEF₁₆ to quaternary (base 4).
- Convert BEEF₁₆ to octal.
- Convert BEEF₁₆ to decimal.
- Convert BEEF to dinner.

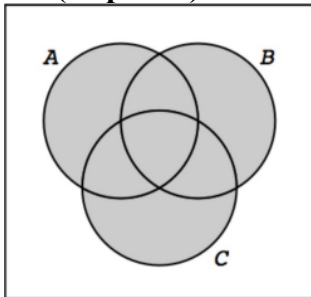P2. (25 points) For each Venn Diagram shown below:



- Draw the corresponding truth table.
- Draw the corresponding K-map.
- Write the minimized SOP expression.
- Write the minimized POS expression.

P3. (15 points) Given the logic expression:

$$F(X, Y, Z) = (X + \bar{X}\bar{Y})(X + Y + \bar{Z}) + \overline{(X + \bar{Y} + X\bar{Y})}(\bar{X}\bar{Y}Z)$$

- Use the theorems of Boolean algebra to simplify the formula given above into a minimum-cost expression.
- Draw the circuit diagram for the minimized F using only AND, OR, and NOT gates.
- Draw the circuit diagram for the simplified expression using only NOR gates.

P4. (15 points) Given the logic expression:

$$F(A, B, C, D) = \bar{A}(\bar{A} + C)\overline{(A\bar{B} + \bar{A}\bar{B} + \bar{C})}(B + \bar{B}C)$$

- Use the theorems of Boolean algebra to simplify the formula given above into a minimum-cost SOP expression.
- Draw the circuit diagram for the minimized F using only AND, OR, and NOT gates.
- Draw the circuit diagram using only NAND gates

P5. (15 points) Four Variable K-Maps.

- Draw the K-map for $F = \bar{a}\bar{b}\bar{c}d + \bar{a}c\bar{d} + a\bar{b}\bar{c} + \bar{a}c\bar{d}$.
- Draw another K-map to derive the minimum-cost SOP expression for F.
- Draw another K-map to derive the minimum-cost POS expression for F.

P6. (20 points) You stumble across an old manuscript containing the following page, but some ink stains are obscuring part of the content. Deduce the function $F(A, B, C)$ and write:


- the complete K-map
- the complete truth table
- the minimized POS expression
- the minimized SOP circuit diagram

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

(1) Truth Table

$F(A, B, C) = (A + \bar{B} + C)$

(2) Minimized POS Expression

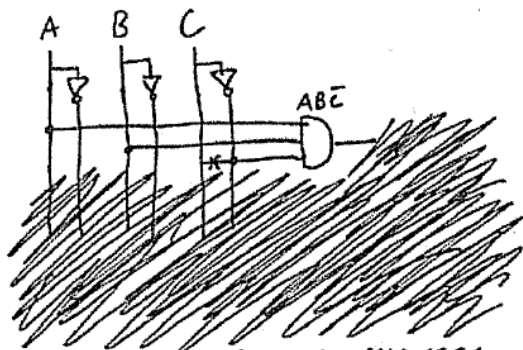

(3) Minimized SOP circuit

Representations of function $F(A, B, C)$