

# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**


# Mealy State Model

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*


# **Administrative Stuff**

- **Homework 10 is due on Wednesday Nov 8 @ 10 pm**
- **Homework 11 is due on Monday Nov 13 @ 10 pm**

 
# The general form of a synchronous sequential circuit



# Moore Type

 

# Mealy Type

 


# Sample Problem

**Implement a 11 detector. In other words, the output should be equal to 1 if two consecutive 1's have been detected on the input line.**


**The output should become 1 as soon as the second 1 is detected in the input.**

# **Moore Machine Implementation**




 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 

Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0




 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 

Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

# Inferring the States

 


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<i>w</i> :	0	1	0	1	1	0	1	1	1	0	1
<i>z</i> :	0	0	0	0	0	1	0	0	1	1	0

 

[ Figure 6.8 from the textbook ]


# The New and Improved Circuit Diagram

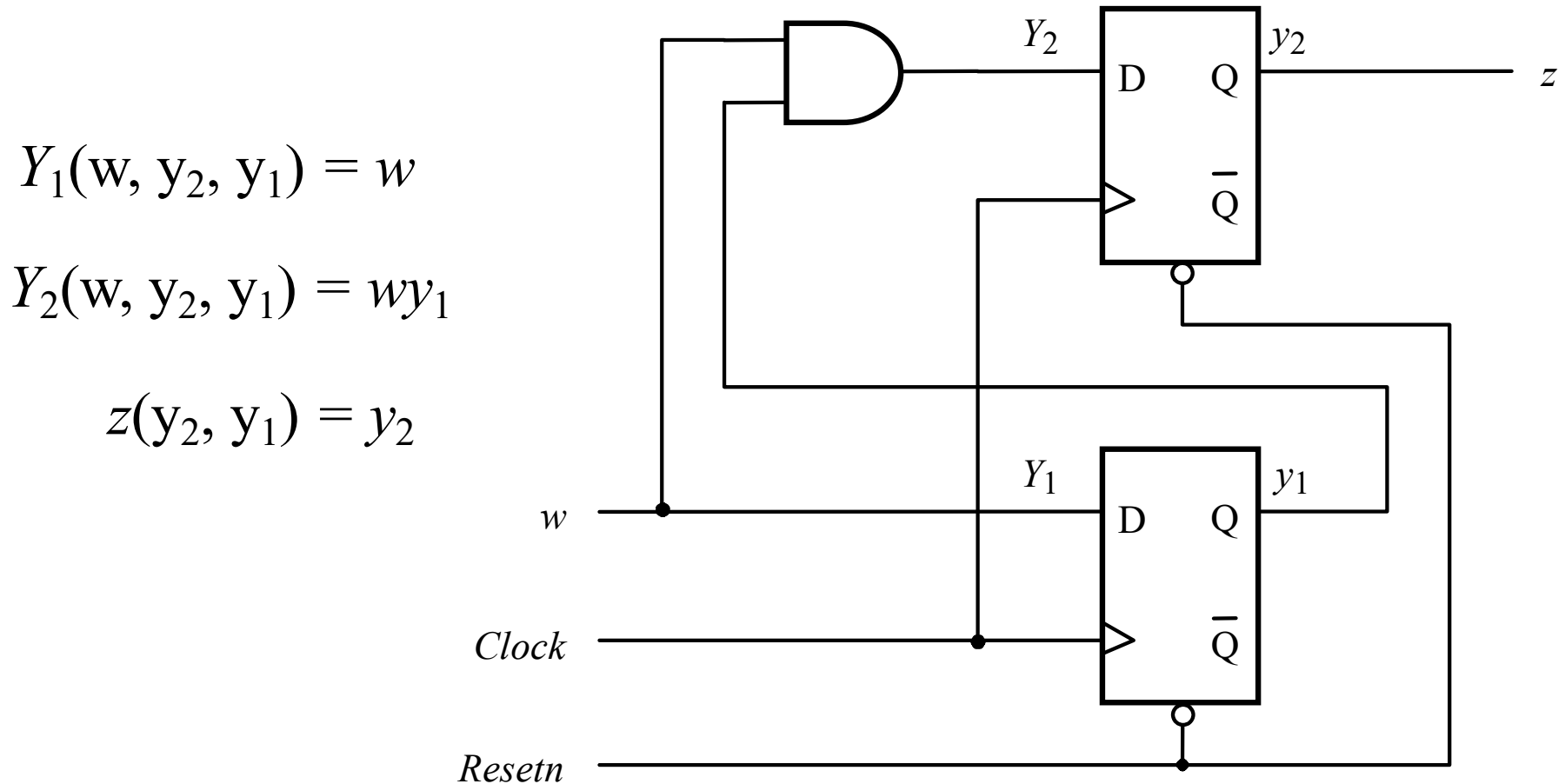




# **Mealy Machine Implementation**
 
# State diagram of an FSM that realizes the task




# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
input $w$ :	<input type="checkbox"/> 0	1	0	1	1	0	1	1	1	0	1
output $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 

# Let's Do a Simulation


Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 




# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 

# Let's Do a Simulation


Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 




# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 


# Let's Do a Simulation

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
<b>input</b> $w$ :	0	1	0	1	1	0	1	1	1	0	1
<b>output</b> $z$ :	0	0	0	0	1	0	0	1	1	0	0

 

 
# Now Let's Do the State Table for this FSM



Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A				
B				
 
# Now Let's Do the State Table for this FSM



Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

# The State Table for this FSM

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1



# Let's Do the State-assigned Table

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
$y$	$Y$	$Y$	$z$	$z$
A 0				
B 1				

# Let's Do the State-assigned Table

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	$y$	$Y$	$Y$	$z$	$z$
A	0	0	1	0	0
B	1	0	1	0	1

# The State-assigned Table

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	$y$	$Y$	$Y$	$z$	$z$
A	0	0	1	0	0
B	1	0	1	0	1

# The State-assigned Table


	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	$y$	$Y$	$Y$	$z$	$z$
A	0	0	1	0	0
B	1	0	1	0	1

$$Y = D = w \quad z = wy$$

# The State-assigned Table


	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	$y$	$Y$	$Y$	$z$	$z$
A	0	0	1	0	0
B	1	0	1	0	1

$$Y = D = w \quad z = wy$$

 

This assumes D flip-flop


# Circuit Implementation of the FSM

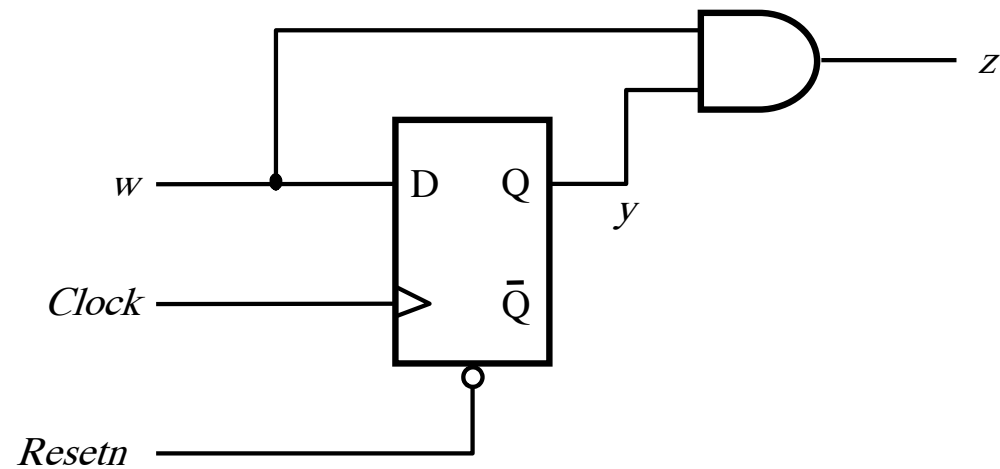


$$Y = D = w$$

$$z = wy$$

# Circuit & Timing Diagram

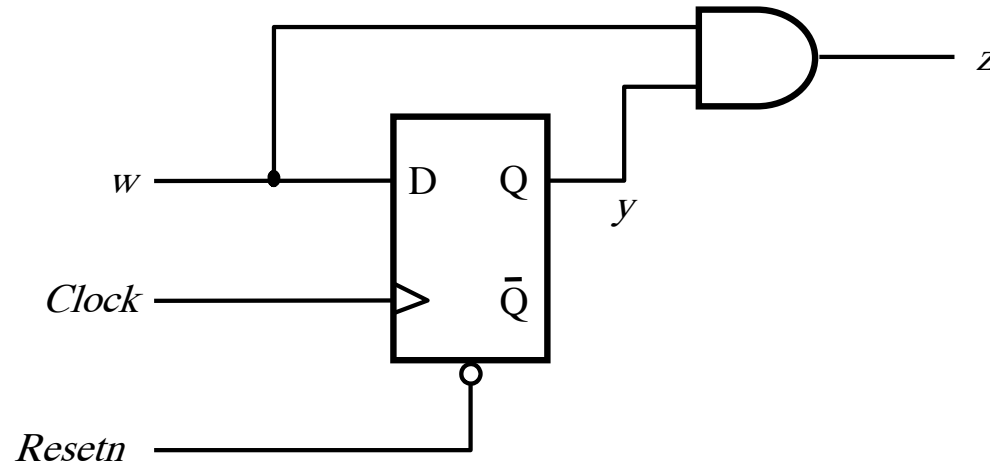

(a) Circuit

 


(b) Timing diagram

[ Figure 6.26 from the textbook ]

**What if we wanted the output signal to be delayed by 1 clock cycle?**




# Circuit Implementation of the Modified FSM

 

[ Figure 6.27a from the textbook ]
 
# Circuit Implementation of the Modified FSM




This flip-flop delays the output signal by one clock cycle

# We Have Seen This Diagram Before


$$Y_1(w, y_2, y_1) = w$$

$$Y_2(w, y_2, y_1) = wy_1$$


$$z(y_2, y_1) = y_2$$

 


# Circuit & Timing Diagram

 


(a) Circuit

 

 
# The general form of a synchronous sequential circuit




# Moore Type

 


# Mealy Type

 

# Moore


 


# Mealy


 





# Moore

  


# Mealy

  

# Mealy

 


# Moore

 


Notice that the output of the Moore machine is delayed by one clock cycle

**Mealy**

 

**Moore**

 

Notice that the output of the Moore machine is delayed by one clock cycle

## Mealy

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
input $w$ :	0	1	0	1	1	0	1	1	1	0	1
output $z$ :	0	0	0	0	1	0	0	1	1	0	0

## Moore


Clockcycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
input $w$ :	0	1	0	1	1	0	1	1	1	0	1
output $z$ :	0	0	0	0	0	1	0	0	1	1	0

**Questions?**

**More slides for  
the State Assignment Problem**


# **Example #2**

# Register Swap Controller

 




# Register Swap Controller

 


Design a Moore machine control circuit for swapping the contents of registers R1 and R2 by using R3 as a temporary.

# State Diagram

 


[ Figure 6.11 from the textbook ]

# Animated Register Swap

 


# Animated Register Swap

 


These are the original values of the 8-bit registers

# Animated Register Swap

 


**For clarity, only inputs that are equal to 1 will be shown.**


# Animated Register Swap

 

# Animated Register Swap

 


# Animated Register Swap

 





# Animated Register Swap

 


# Animated Register Swap

 


# Animated Register Swap

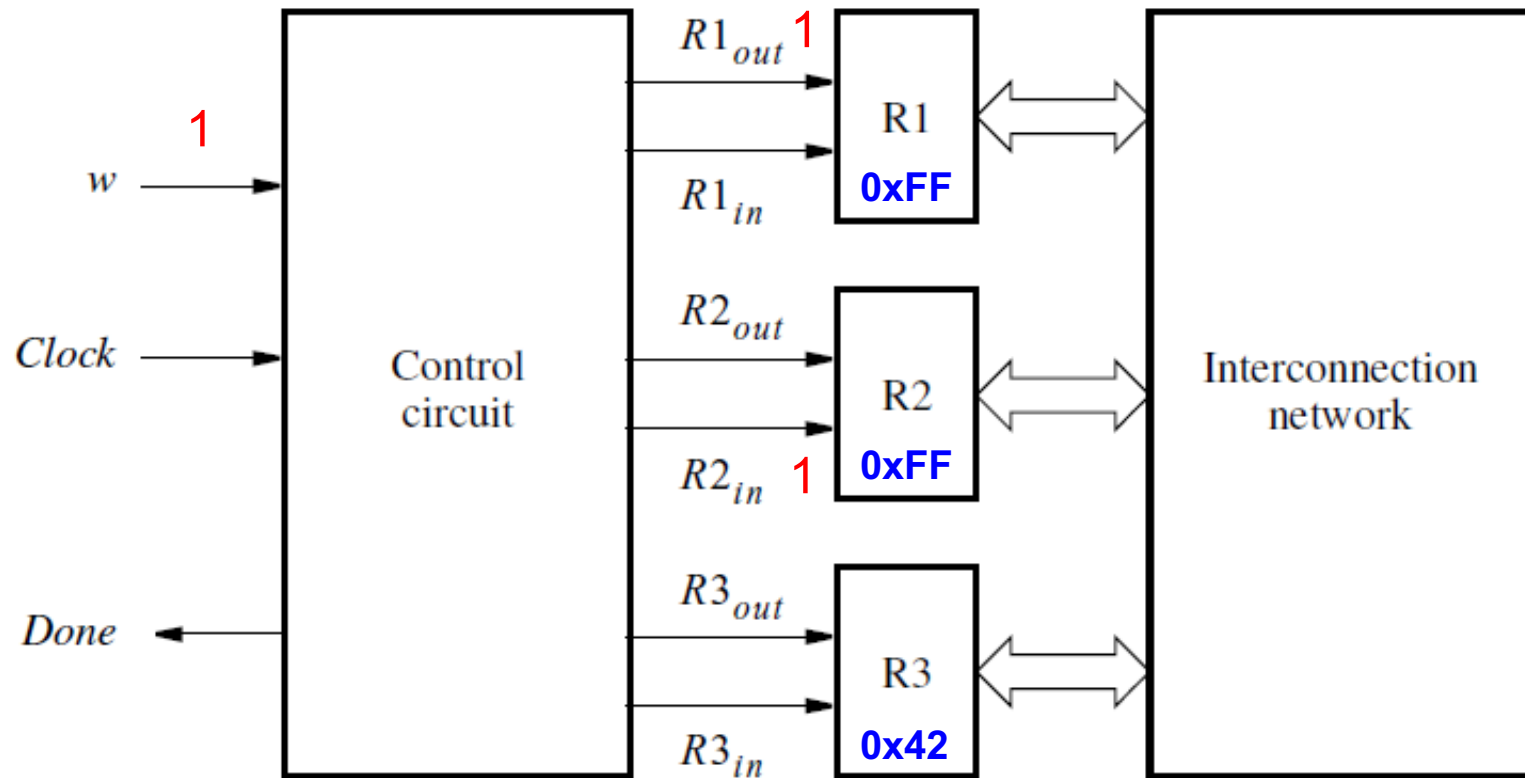


# Animated Register Swap

 


# Animated Register Swap

 


# Animated Register Swap

 

# Animated Register Swap

 

# State Diagram


 




[ Figure 6.11 from the textbook ]



  
# Some Questions

- **How many flip-flops are we going to use?**
- **How many logic expressions do we need to find?**



  



 

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

**As we saw before, we can expect that some state encodings will be better than others.**

**We will consider three encoding schemes.**

**Encoding #1:**  
**A=00, B=01, C=10, D=11**

**(Uses Two Flip-Flops)**

## State Table

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State-Assigned Table

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A										
B										
C										
D										



## State Table

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State Assigned Table

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	00									
B	01									
C	10									
D	11									

## State Table

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State Assigned Table

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	00	00	01							
B	01	10	10							
C	10	11	11							
D	11	00	00							

## State Table

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State Assigned Table

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
	$Y_2Y_1$	$Y_2Y_1$								
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Let's derive the next-state expressions.



	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0

Pay attention to the way the columns of the truth table are labeled.

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0

  

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0

$Y_1$



$w$	$y_2y_1$	00	01	11	10
0		0	0	0	1
1		1	0	0	1

$Y_2$

$w$	$y_2y_1$	00	01	11	10
0		0	1	0	1
1		0	1	0	1

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1


$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0

  




	Present state	Next state		Outputs						
		$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$							
A	00	00	01	0	0	0	0	0	0	0
B	01	10	10	0	0	1	0	0	1	0
C	10	11	11	1	0	0	1	0	0	0
D	11	00	00	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0

 

$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$

 

$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$
0	0			
0	1			
1	0			
1	1			

Let's derive the output expressions

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$
0	0			
0	1			
1	0			
1	1			

Let's derive the output expressions.

We need to derive only these 3 unique ones.

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$
0	0	0	0	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0


	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$
0	0	0	0	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

$$R1_{out} = R2_{in} = \overline{y_1} y_2$$

$$R1_{in} = R3_{out} = \text{Done} = y_1 y_2$$

 
$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$




	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$


$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$

 



	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

 






 


 

 

 

  

 

**Encoding #2:**  
**A=00, B=01, C=11, D=10**

**(Also Uses Two Flip-Flops)**

## State Table (same as before)

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State-Assigned Table

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A B C D										



## State Table (same as before)

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State-Assigned Table

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	00									
B	01									
C	11									
D	10									

## State Table (same as before)

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State-Assigned Table

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	00	00	01							
B	01	11	11							
C	11	10	10							
D	10	00	00							

## State Table (same as before)

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State-Assigned Table

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		



Let's derive the next-state expressions

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	0

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	0

  

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	0

$Y_1$



	$y_2y_1$	00	01	11	10
$w$					
0		0	1	0	0
1		1	1	0	0

$Y_2$

	$y_2y_1$	00	01	11	10
$w$					
0		0	1	1	0
1		0	1	1	0

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1


$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	0

  




	Present state	Next state		Outputs						
		$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$w$	$Y_2$	$Y_1$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	0

 

$$Y_1 = w\bar{y}_2 + y_1\bar{y}_2$$

 

$$Y_2 = y_1$$

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$							
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$
0	0			
0	1			
1	0			
1	1			

Let's derive the output expressions

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$							
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

$y_2$	$y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$
0	0			
0	1			
1	0			
1	1			

Let's derive the output expressions

Once again, we only need to derive these three unique ones.

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$							
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

	$y_2$	$y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$
A	0	0	0		
B	0	1	0		
D	1	0	0		
C	1	1	<b>1</b>		

**Note that C and D are swapped in the truth table due to the new state encoding that was chosen.**

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
	$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$							
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1

	$y_2$	$y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$
A	0	0	0	0	0
B	0	1	0	0	1
D	1	0	0	1	0
C	1	1	1	0	0

	Present state	Next state		Outputs						
		$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
	$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$							
A	00	00	0 1	0	0	0	0	0	0	0
B	01	11	1 1	0	0	1	0	0	1	0
C	11	10	1 0	1	0	0	1	0	0	0
D	10	00	0 0	0	1	0	0	1	0	1


	$y_2$	$y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$
A	0	0	0	0	0
B	0	1	0	0	1
D	1	0	0	1	0
C	1	1	1	0	0

$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = Done = \overline{y_1} y_2$$

$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$

# Let's Complete the Circuit Diagram

 

$$Y_1 = w \bar{y}_2 + y_1 \bar{y}_2$$


$$Y_2 = y_1$$

$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = Done = \bar{y}_1 y_2$$

$$R2_{out} = R3_{in} = y_1 \bar{y}_2$$

# Let's Complete the Circuit Diagram

 

$$Y_1 = w \overline{y_2} + y_1 \overline{y_2}$$

$$Y_2 = y_1$$


$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = Done = \overline{y_1} y_2$$

$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$



# Let's Complete the Circuit Diagram

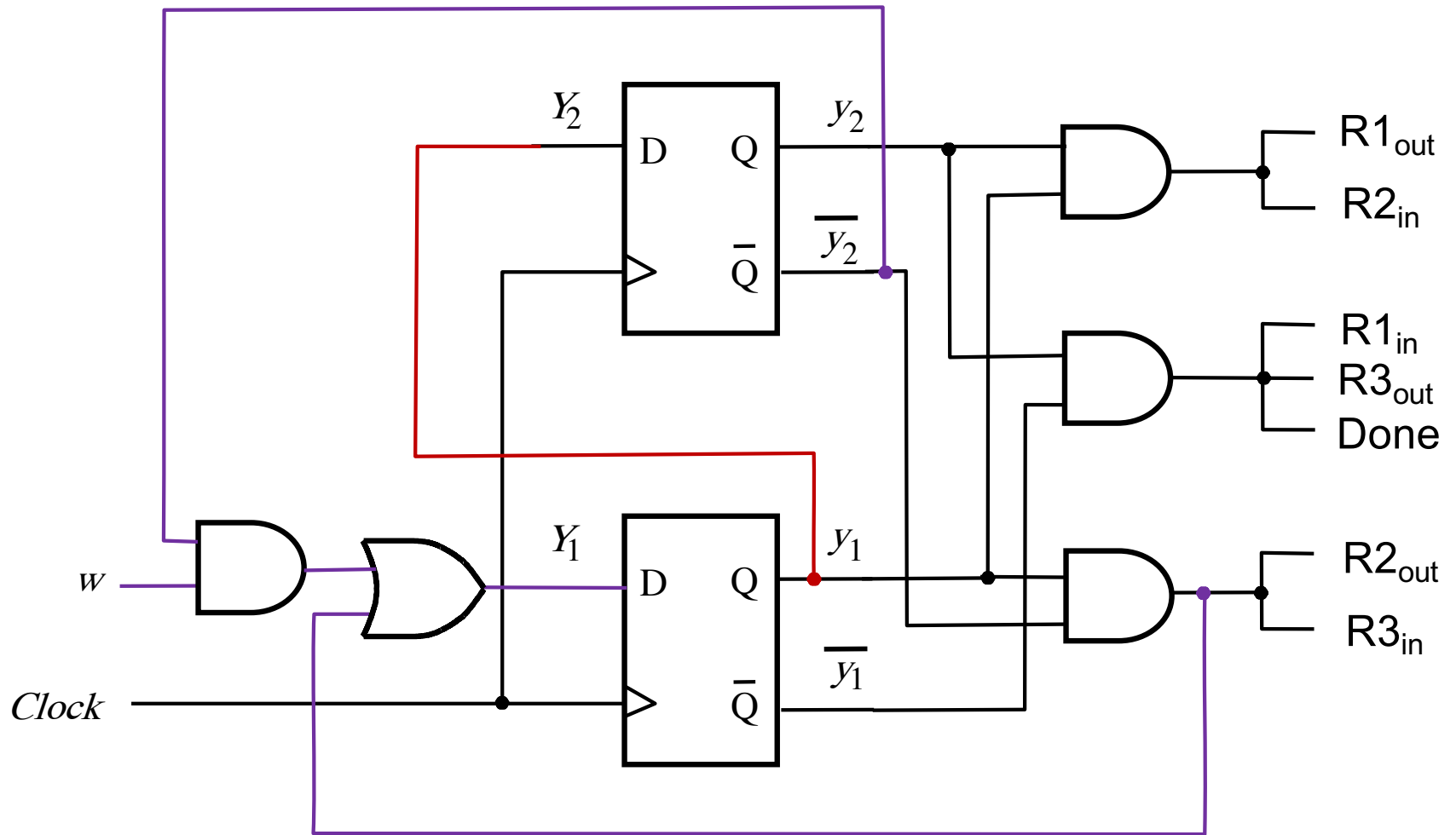

$$Y_1 = w \overline{y_2} + y_1 \overline{y_2}$$


$$Y_2 = y_1$$

$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = \text{Done} = \overline{y_1} y_2$$

$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$

# Let's Complete the Circuit Diagram

 

$$Y_1 = w \overline{y_2} + y_1 \overline{y_2}$$

$$Y_2 = y_1$$

$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = \text{Done} = \overline{y_1} y_2$$

$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$

## **Encoding #3:**


**A=0001, B=0010, C=0100, D=1000**

**(One-Hot Encoding – Uses Four Flip-Flops)**


# One-Hot State Encoding

- **So far, we have been encoding states in a way that minimizes the number of flip-flops.**
- **But sometimes we can decrease the complexity of our logic if we encode states more sparsely.**


# Encoding for State A

 


# Encoding for State B

 

# Encoding for State C

 

# Encoding for State D

 



# Register Swap Controller

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

# Register Swap Controller

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

**Let's use four flip-flops and the following one-hot state encoding scheme:**

**A = 0001**

**B = 0010**

**C = 0100**

**D = 1000**

## State Table (same as before)

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State-Assigned Table

Present State $y_4y_3y_2y_1$	Next State		Outputs						
	$w = 0$	$w = 1$							
	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A									
B									
C									
D									

## State Table (same as before)

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State-Assigned Table

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	0 001									
B	0 010									
C	0 100									
D	1 000									

## State Table (same as before)

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State-Assigned Table

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	0 001	0001	0010							
B	0 010	0100	0100							
C	0 100	1000	1000							
D	1 000	0001	0001							

## State Table (same as before)

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

## State-Assigned Table

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

# Let's Derive the Next-State Expressions

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

# Let's Derive the Next-State Expressions

- $Y_1(w, y_4, y_3, y_2, y_1)$

- $Y_2(w, y_4, y_3, y_2, y_1)$

- $Y_3(w, y_4, y_3, y_2, y_1)$

- $Y_4(w, y_4, y_3, y_2, y_1)$

We need to do four 5-variable K-maps!

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4 y_3 y_2 y_1$	$Y_4 Y_3 Y_2 Y_1$	$Y_4 Y_3 Y_2 Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	Done
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1



# Let's Derive the Next-State Expressions

- $Y_1(w, y_4, y_3, y_2, y_1) = \neg w y_1 + y_4$

- $Y_2(w, y_4, y_3, y_2, y_1) = w y_1$

- $Y_3(w, y_4, y_3, y_2, y_1) = y_2$

- $Y_4(w, y_4, y_3, y_2, y_1) = y_3$

Or we can be smarter than that 😊

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4 y_3 y_2 y_1$	$Y_4 Y_3 Y_2 Y_1$	$Y_4 Y_3 Y_2 Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	Done
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

# Let's Derive the Next-State Expressions

•  $Y_1(w, y_4, y_3, y_2, y_1) = \neg w y_1 + y_4$  (why?)

•  $Y_2(w, y_4, y_3, y_2, y_1) = w y_1$  (why?)

•  $Y_3(w, y_4, y_3, y_2, y_1) = y_2$  =1 only in B

•  $Y_4(w, y_4, y_3, y_2, y_1) = y_3$  =1 only in C

Or we can be smarter than that 😊

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4 y_3 y_2 y_1$	$Y_4 Y_3 Y_2 Y_1$	$Y_4 Y_3 Y_2 Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	Done
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

# Let's Derive the Output Expressions

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	R1 <sub>out</sub>	R1 <sub>in</sub>	R2 <sub>out</sub>	R2 <sub>in</sub>	R3 <sub>out</sub>	R3 <sub>in</sub>	<i>Done</i>
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

# Let's Derive the Output Expressions

- $R1_{out}(y_4, y_3, y_2, y_1)$
- $R1_{in}(y_4, y_3, y_2, y_1)$
- $R2_{out}(y_4, y_3, y_2, y_1)$
- $R2_{in}(y_4, y_3, y_2, y_1)$
- $R3_{out}(y_4, y_3, y_2, y_1)$
- $R3_{in}(y_4, y_3, y_2, y_1)$
- $Done(y_4, y_3, y_2, y_1)$

We need to do seven 4-variable K-maps!

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4 y_3 y_2 y_1$	$Y_4 Y_3 Y_2 Y_1$	$Y_4 Y_3 Y_2 Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

# Let's Derive the Output Expressions

- $R1_{out}(y_4, y_3, y_2, y_1) = y_3$  *equal to 1 only in State C*
- $R1_{in}(y_4, y_3, y_2, y_1) = y_4$  *equal to 1 only in State D*
- $R2_{out}(y_4, y_3, y_2, y_1) = y_2$  *equal to 1 only in State B*
- $R2_{in}(y_4, y_3, y_2, y_1) = y_3$  *equal to 1 only in State C*
- $R3_{out}(y_4, y_3, y_2, y_1) = y_4$  *equal to 1 only in State D*
- $R3_{in}(y_4, y_3, y_2, y_1) = y_2$  *equal to 1 only in State B*
- $Done(y_4, y_3, y_2, y_1) = y_4$  *equal to 1 only in State D*

Or we can be smarter than that by exploiting the one-hot encoded property

	Present State	Next State		Outputs						
		$w = 0$	$w = 1$							
	$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	<b>1</b>	0	0	<b>1</b>	0
C	0 100	1000	1000	<b>1</b>	0	0	<b>1</b>	0	0	0
D	1 000	0001	0001	0	<b>1</b>	0	0	<b>1</b>	0	<b>1</b>

# Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = \text{Done} = y_4$$


$$R2_{out} = R3_{in} = y_2$$

$$Y_1 = \bar{w} y_1 + y_4$$

$$Y_2 = w y_1$$

$$Y_3 = y_2$$

$$Y_4 = y_3$$

 

# Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$


$$R2_{out} = R3_{in} = y_2$$

$$Y_1 = \bar{w} y_1 + y_4$$

$$Y_2 = w y_1$$

$$Y_3 = y_2$$

$$Y_4 = y_3$$

 


# Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$

$$R2_{out} = R3_{in} = y_2$$

 

$$Y_1 = \bar{w} y_1 + y_4$$

$$Y_2 = w y_1$$

$$Y_3 = y_2$$

$$Y_4 = y_3$$

$w$  \_\_\_\_\_

*Clock* \_\_\_\_\_




# Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$

$$R2_{out} = R3_{in} = y_2$$

 

$$Y_1 = \bar{w} y_1 + y_4$$

$$Y_2 = w y_1$$

$$Y_3 = y_2$$


$$Y_4 = y_3$$

# Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$

$$R2_{out} = R3_{in} = y_2$$

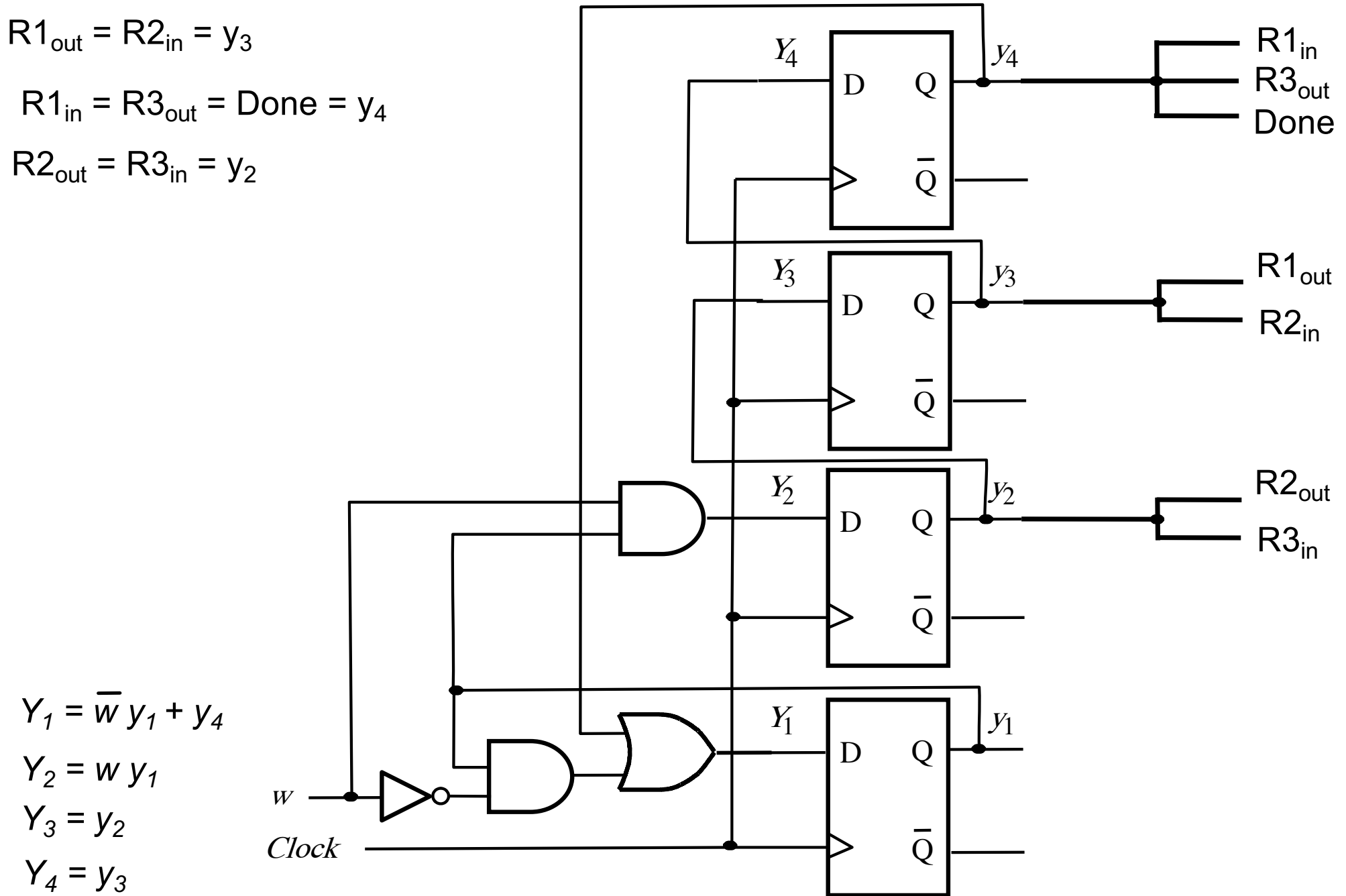


## **Encoding #4:**

**A=0001, B=0010, C=0100, D=1000**


**(same as before, but shows an alternative implementation with a 4-bit ring counter)**

# Exploit the Structure of the FSM

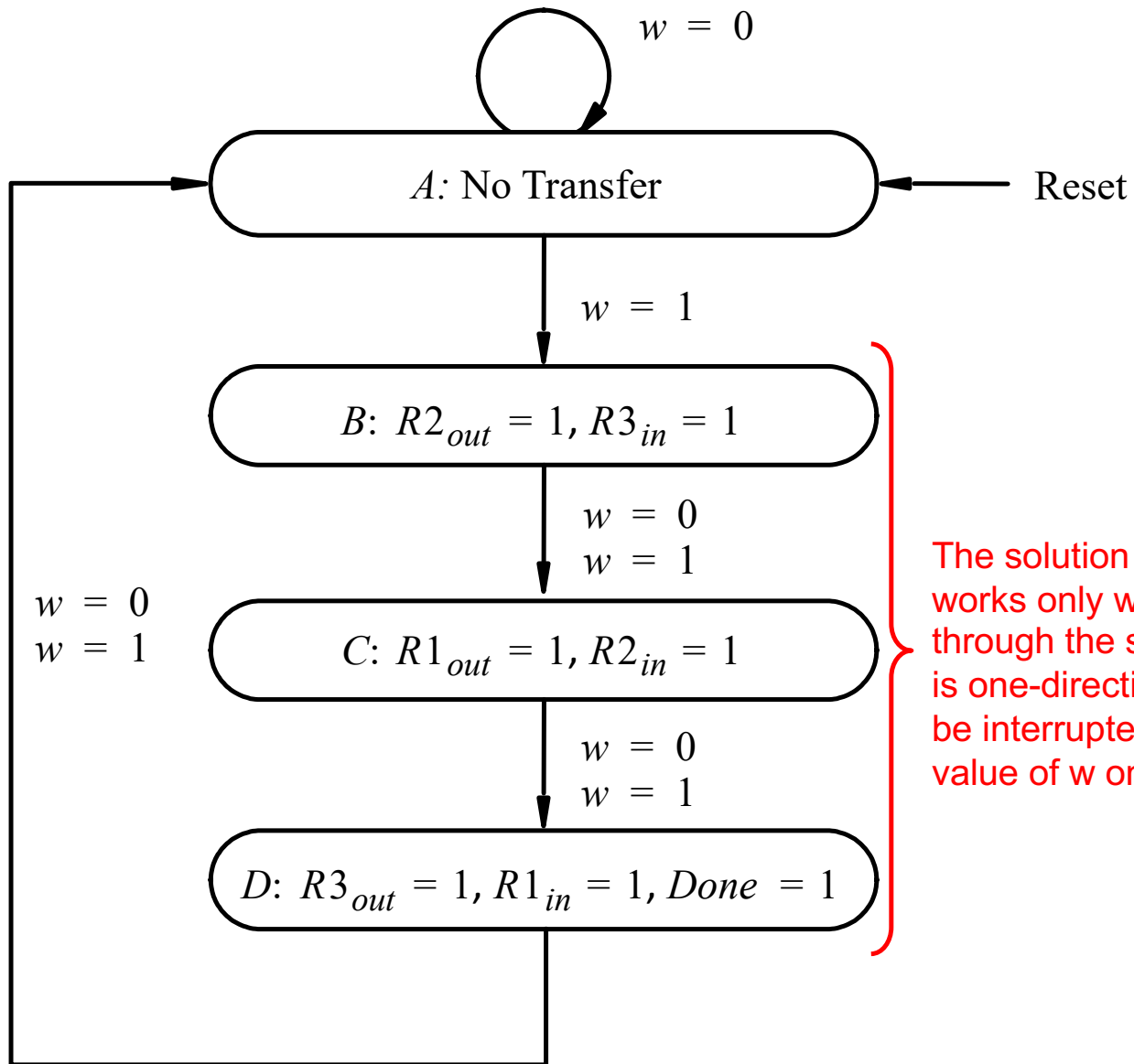

The solution with the ring counter works only when the traversal through the states of the FSM is one-directional and cannot be interrupted by the value of  $w$  once it has started.
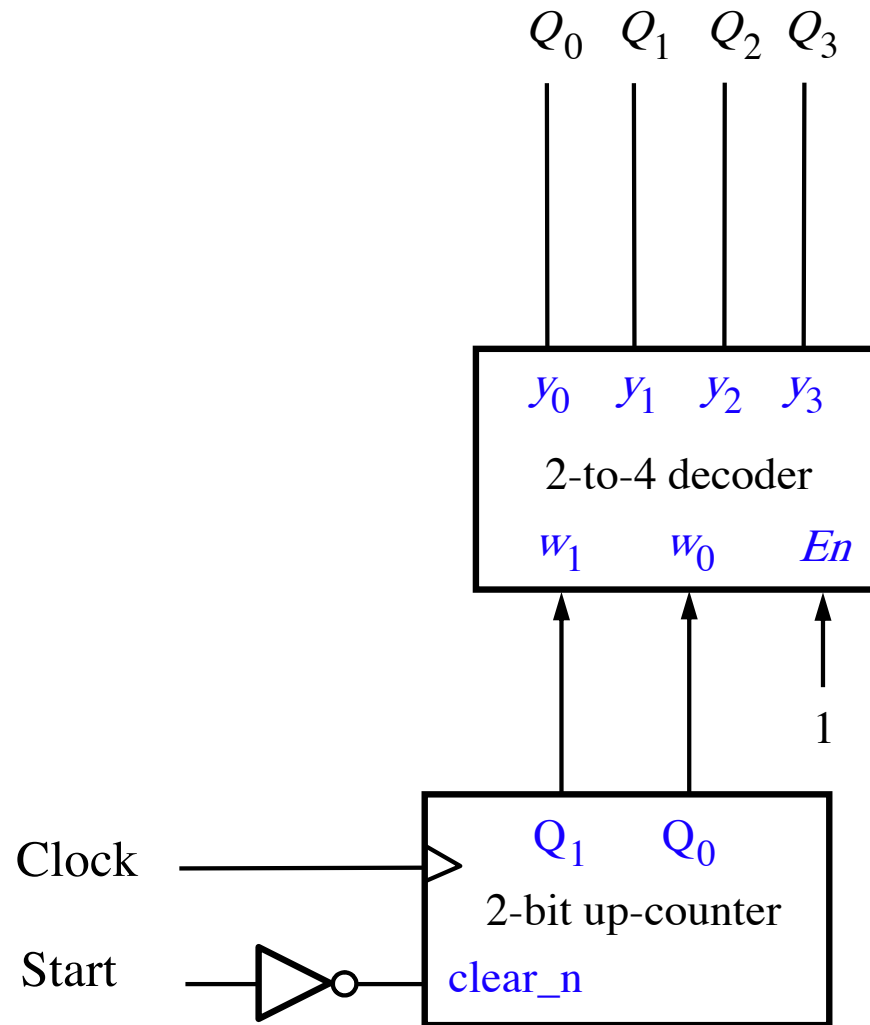
# Alternative version of a 4-bit ring counter





# Alternative version of a 4-bit ring counter

Switch to 1-based indexing of the outputs →

$Q_1$   $Q_2$   $Q_3$   $Q_4$


Switch to 1-based indexing of the outputs →

  (this is done to be consistent with the previous example)




# Alternative version of a 4-bit ring counter

Also, omit these labels →

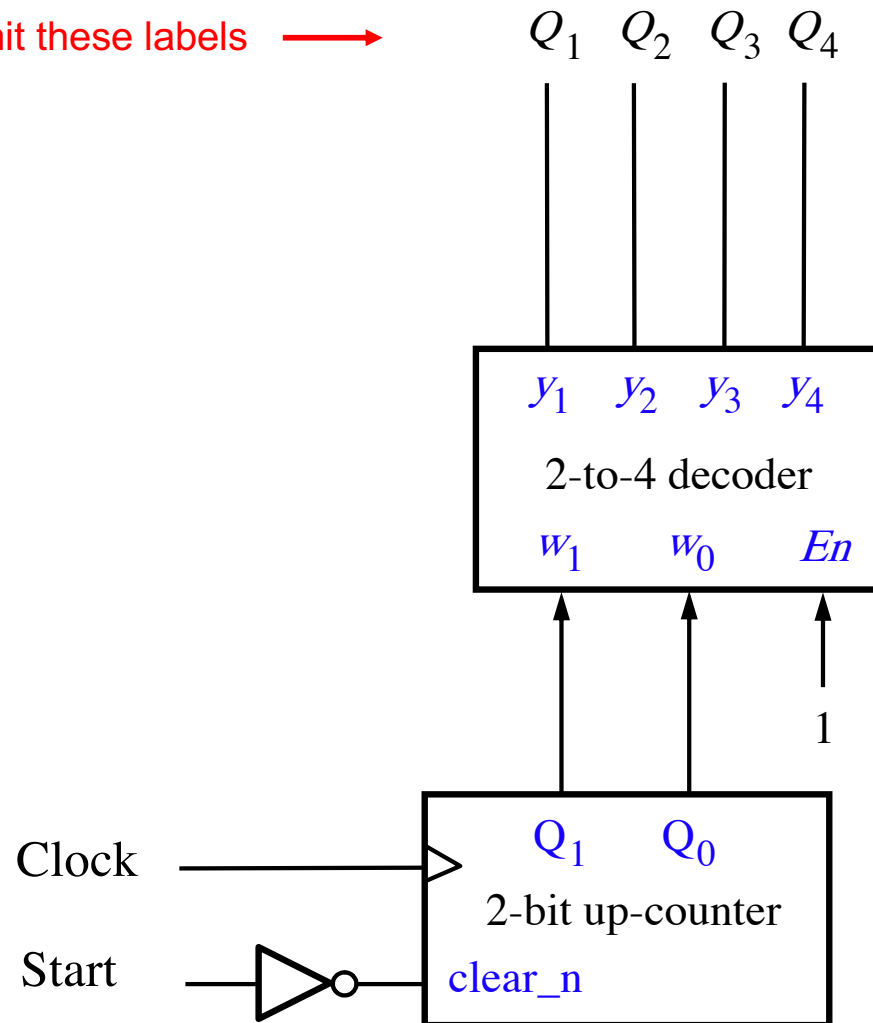

 
# Alternative version of a 4-bit ring counter






# 2-to-4 Decoder with Enable Input

 

[ Figure 4.14c from the textbook ]


# 2-to-4 Decoder with Enable Input

 

Switch to 1-based indexing of the outputs


(this is done to be consistent with the previous example)

# 2-to-4 Decoder with Enable Input

 


(always enabled in this example)
 
# Alternative version of a 4-bit ring counter







# Let's Complete the Circuit Diagram

 

# Let's Complete the Circuit Diagram

 


# Let's Complete the Circuit Diagram

 



# Let's Complete the Circuit Diagram

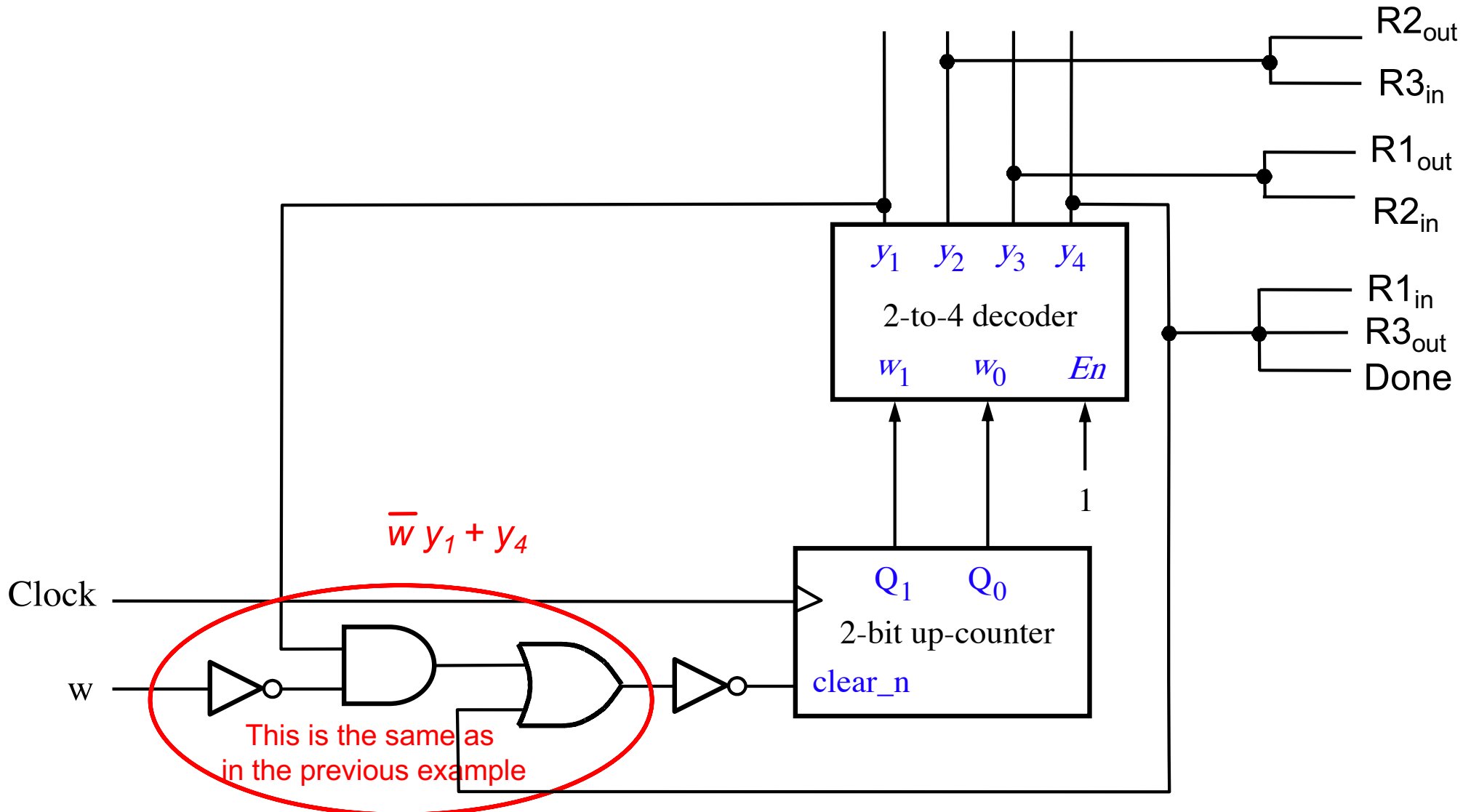

# The Solution for Encoding #3

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$


$$R2_{out} = R3_{in} = y_2$$

$$Y_1 = \bar{w} y_1 + y_4$$


$$Y_2 = w y_1$$

$$Y_3 = y_2$$


$$Y_4 = y_3$$

 


# How Does It Work?

 


# How Does It Work?

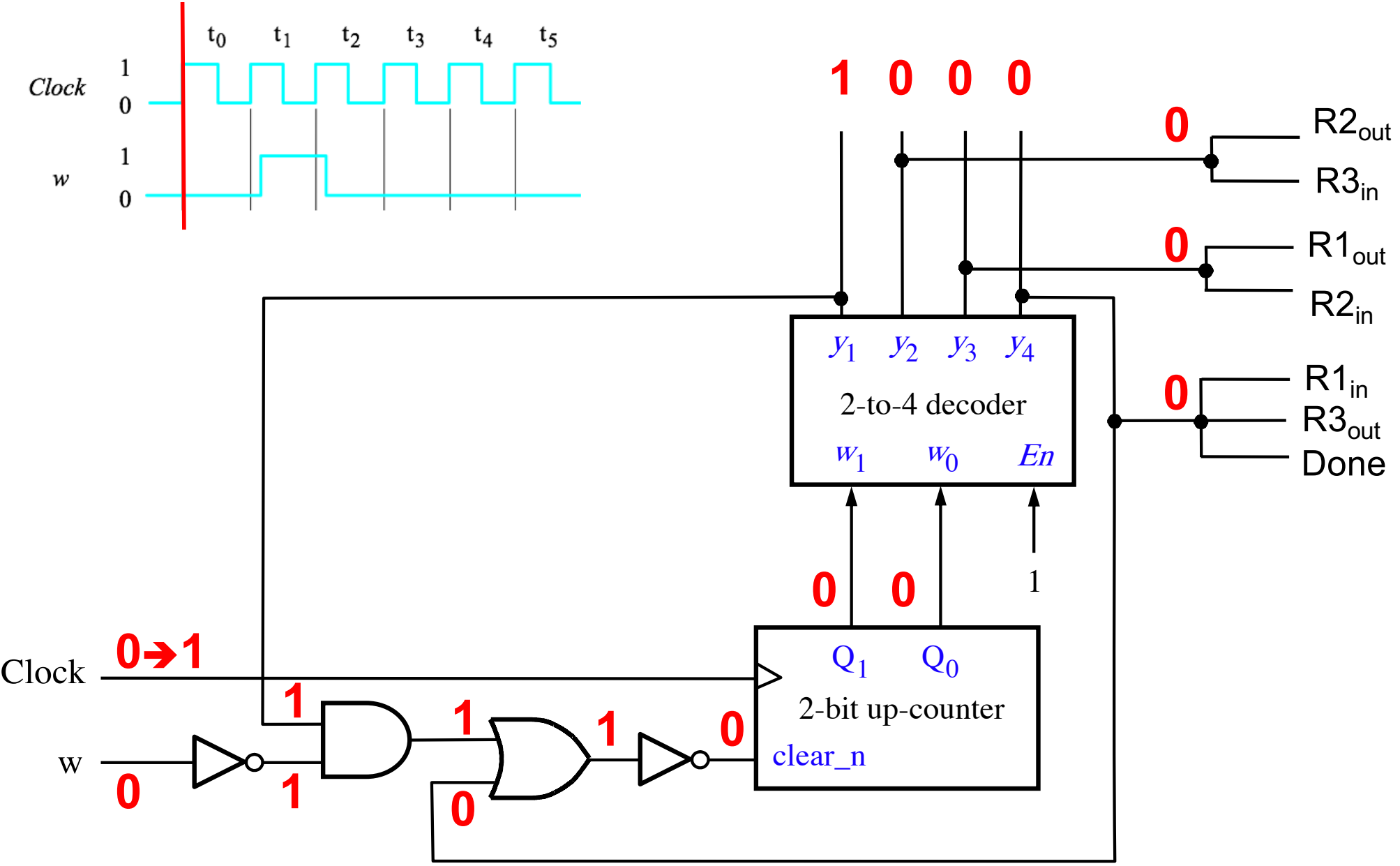


# How Does It Work?

 


# How Does It Work?

 

# How Does It Work?

 


# How Does It Work?

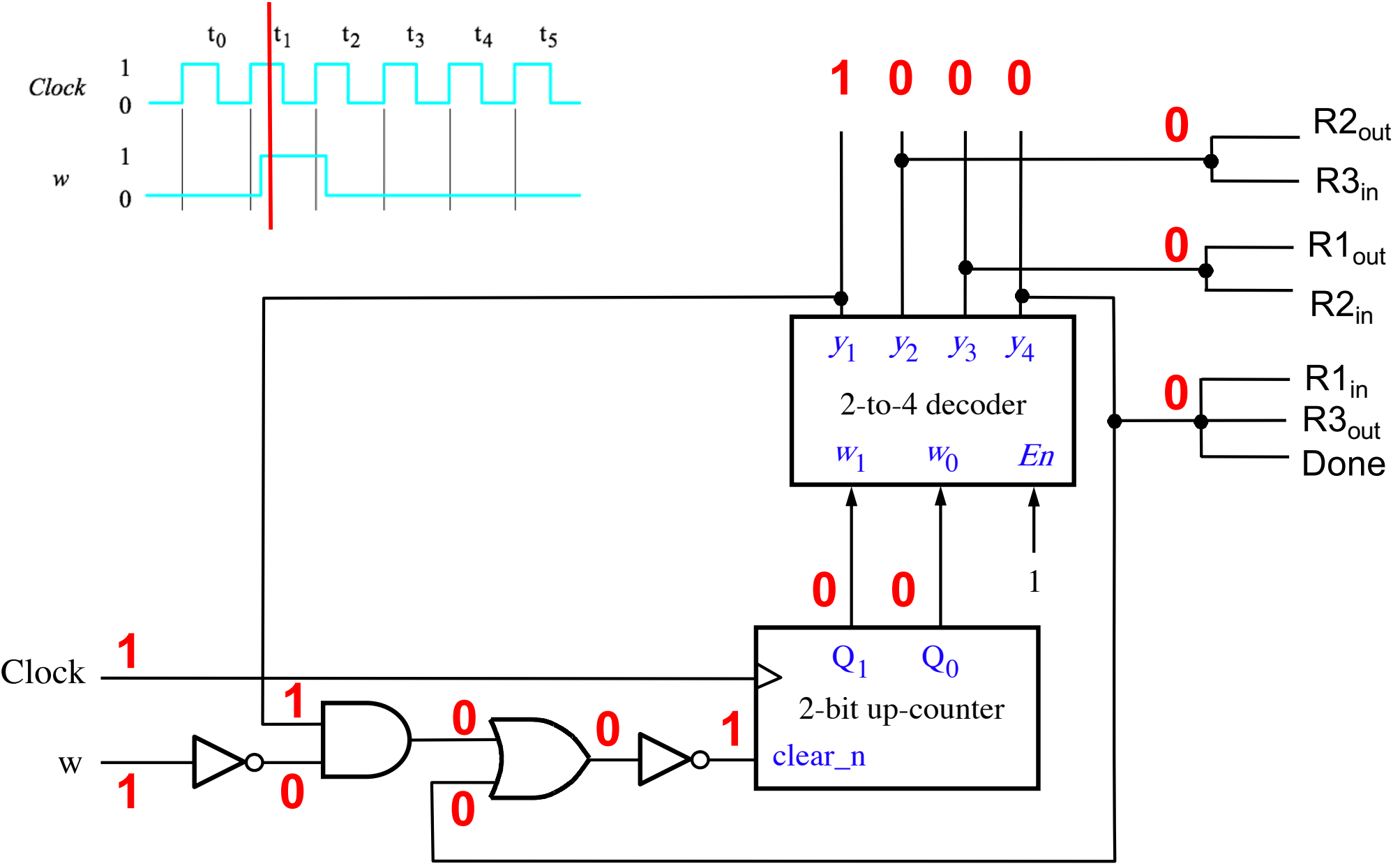





# How Does It Work?

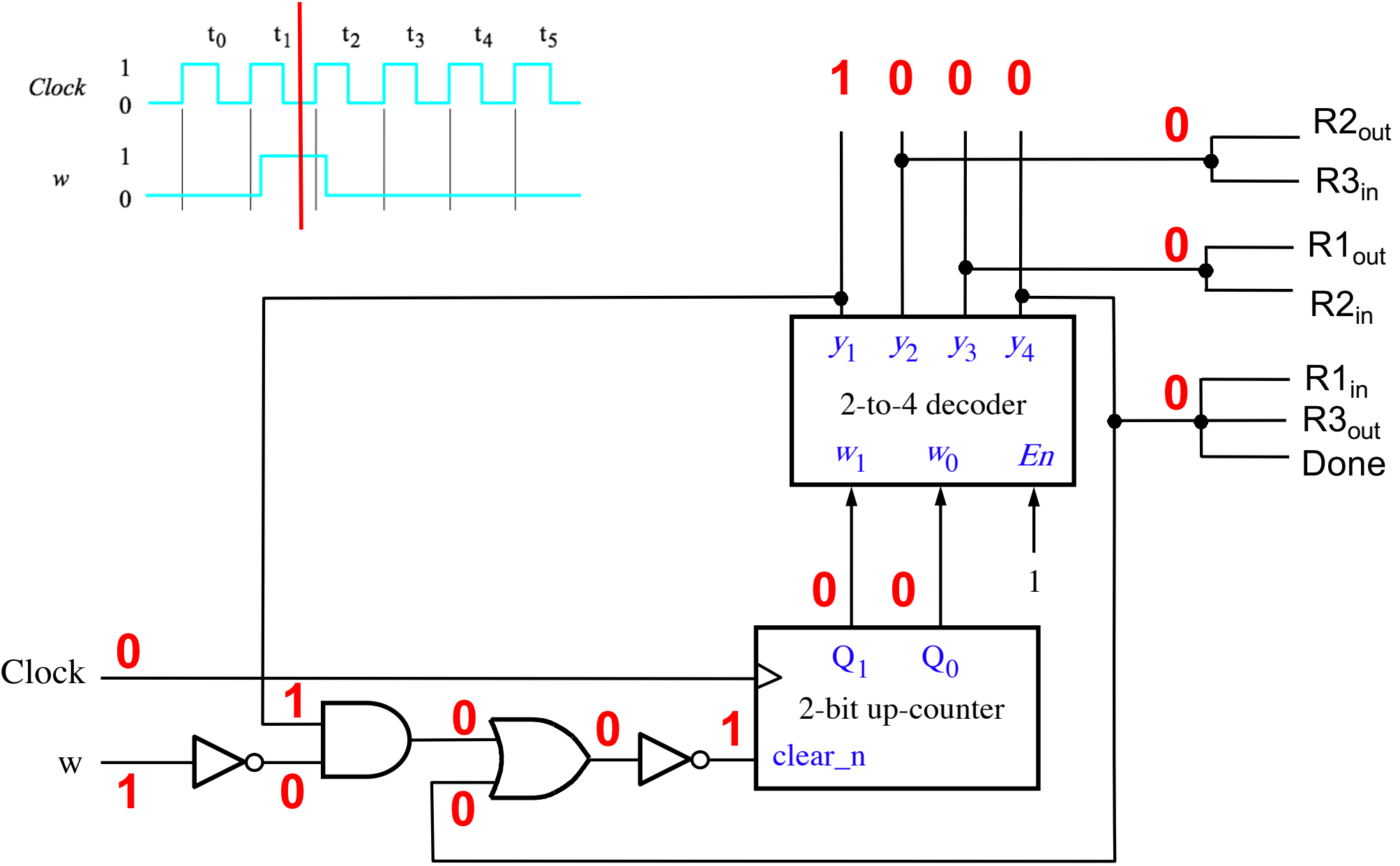


# How Does It Work?

 


# How Does It Work?

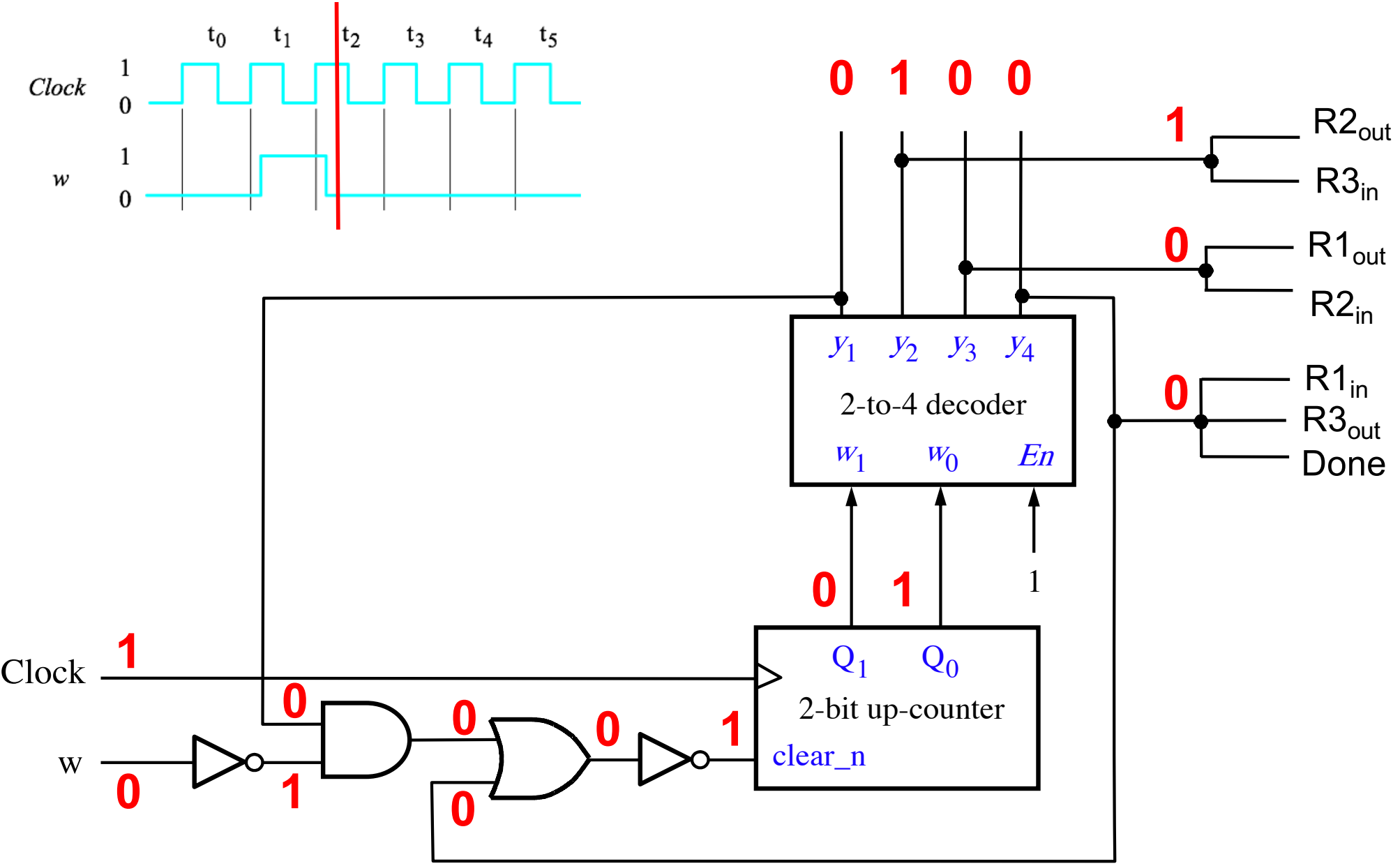


# How Does It Work?

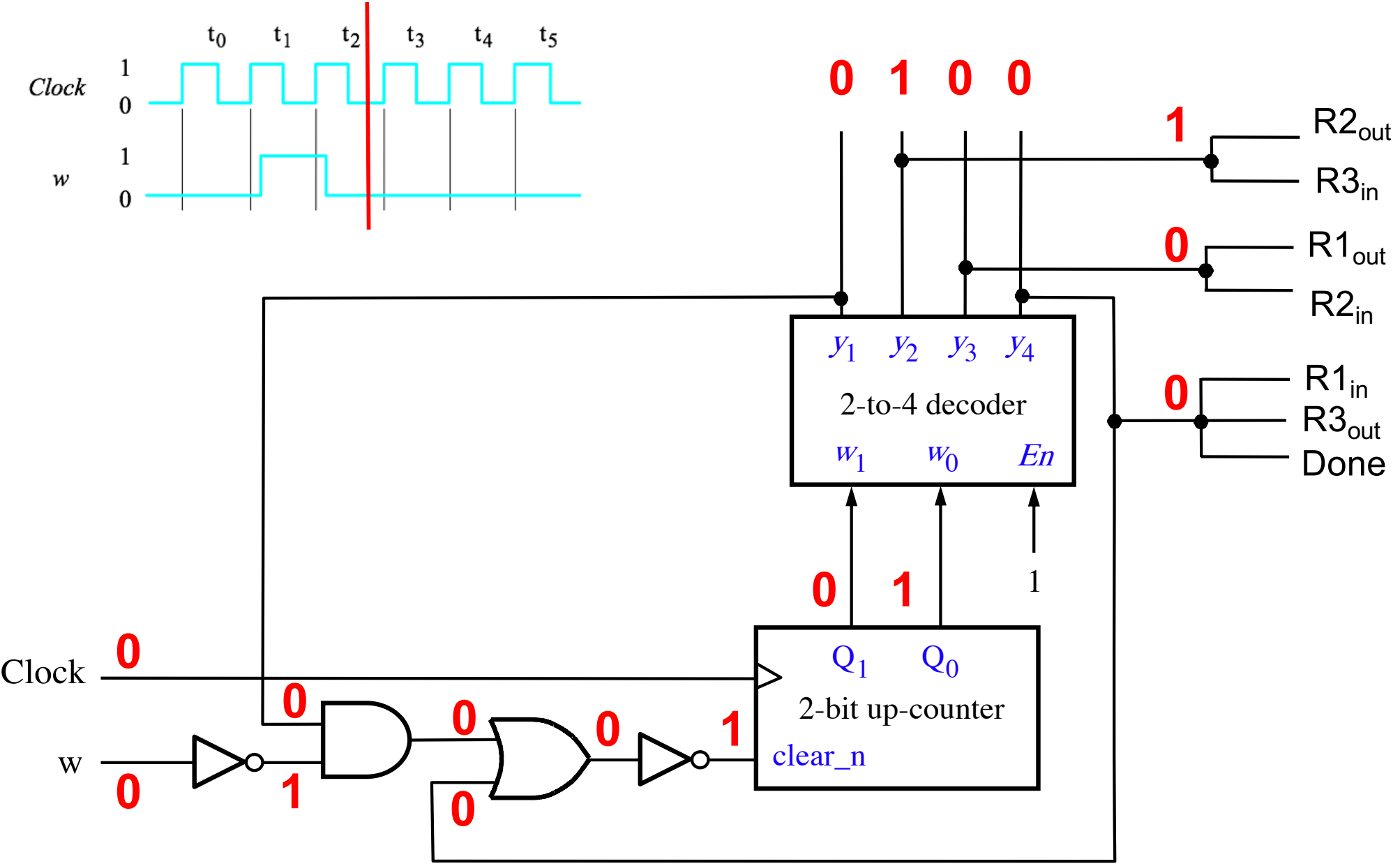


# How Does It Work?

 


# How Does It Work?

 

# How Does It Work?

 


# How Does It Work?

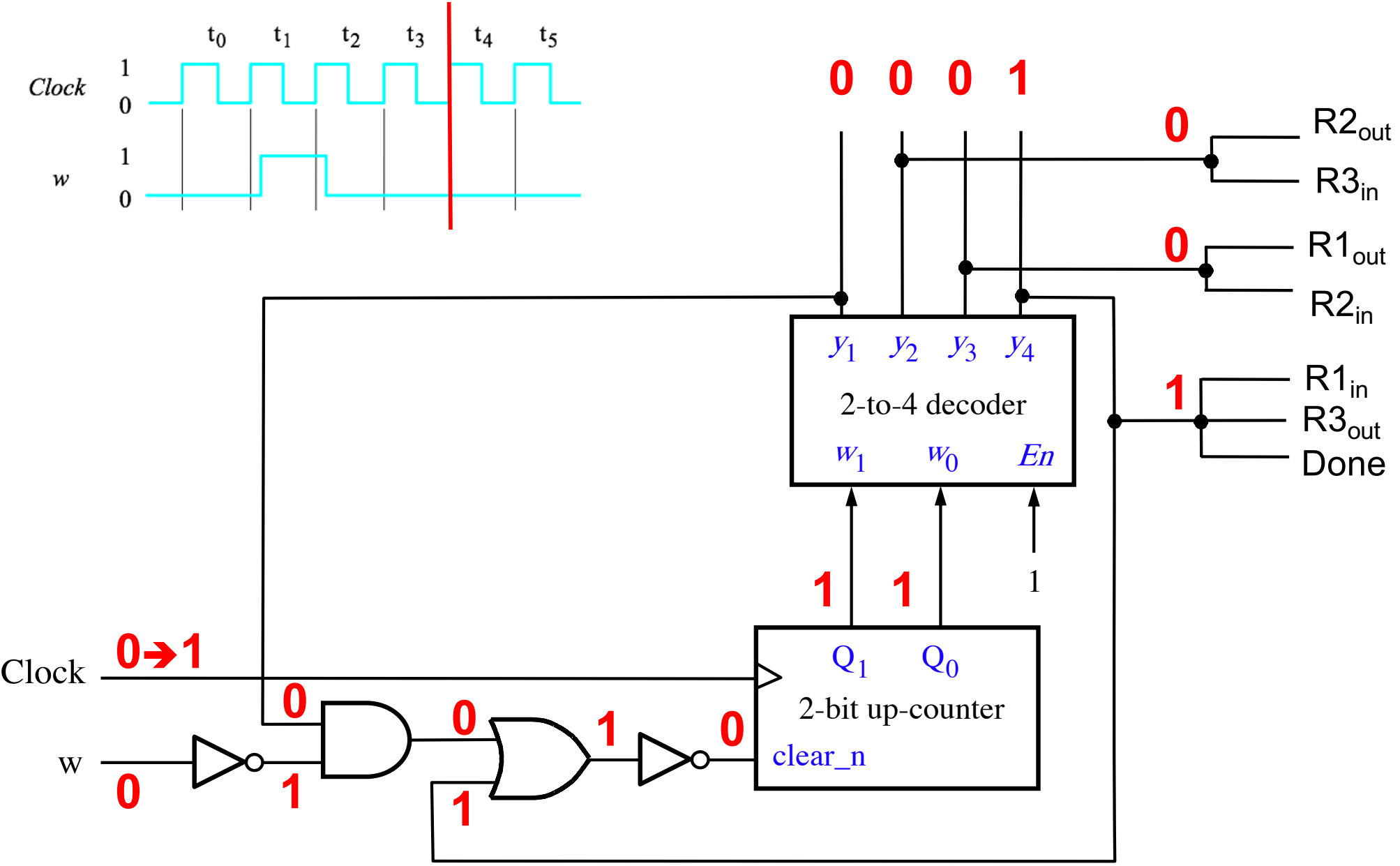





# How Does It Work?

 


# How Does It Work?

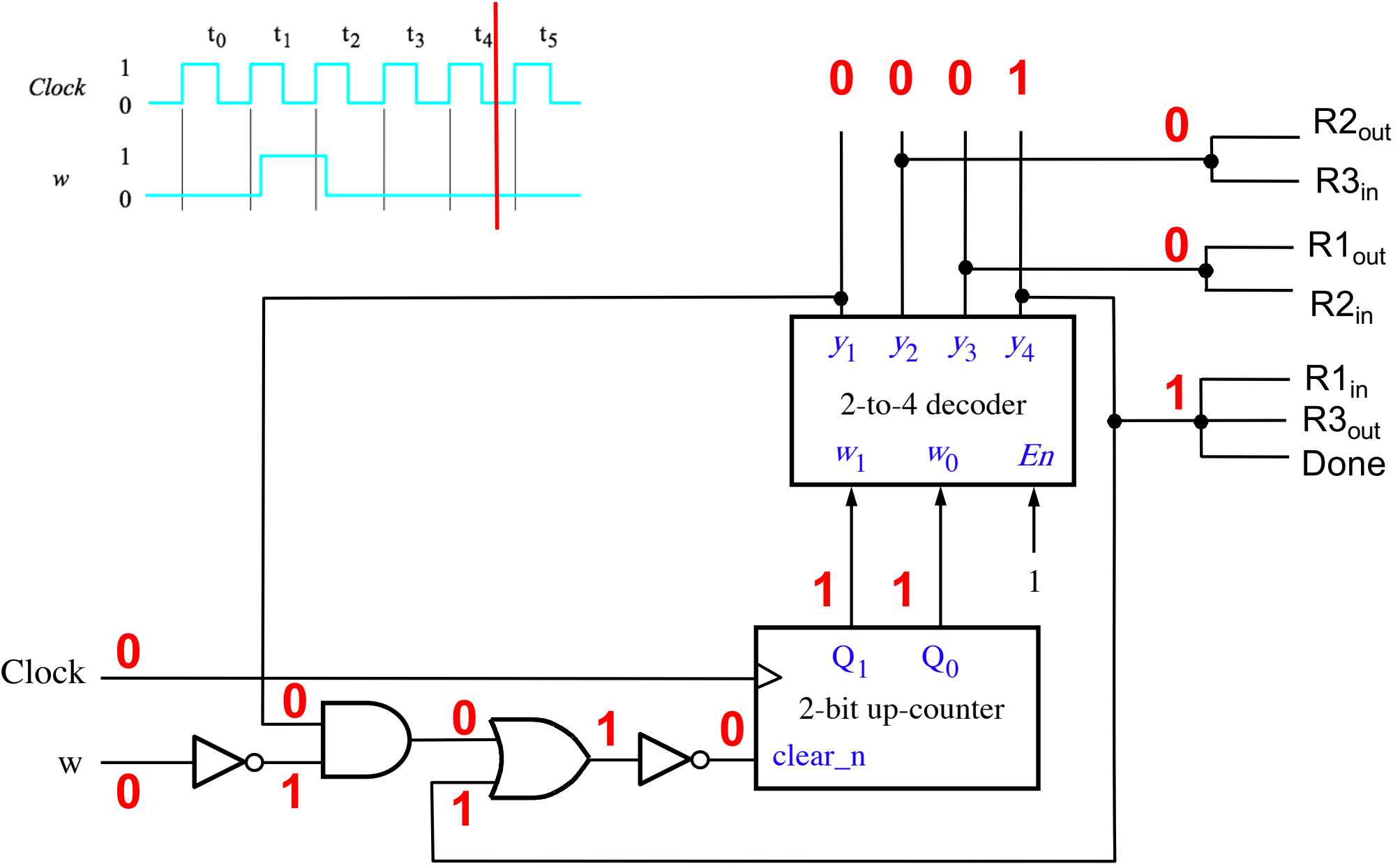

# How Does It Work?

 

# How Does It Work?

 

**Questions?**

**THE END**