

# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Logic Gates

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*

# Administrative Stuff

- HW1 is out. It is due on Wednesday Sep 4 @ 10pm.
- Submit it as a PDF upload on Canvas before the deadline.
- You can write the solutions on paper and then scan the pages to make **\*\*one\*\*** PDF file.
- **No late homeworks will be accepted.**
- Please write clearly on the first page:
  - your name
  - student ID
  - lab section number

# Labs Next Week

- Please download and read the lab assignment for next week before you go to your lab section.
- [https://www.ece.iastate.edu/~alexs/classes/2024\\_Fall\\_2810/labs/Lab\\_01/](https://www.ece.iastate.edu/~alexs/classes/2024_Fall_2810/labs/Lab_01/)
- You must **print and complete** the prelab **before** you go to the lab.
- The TAs will check your prelab answers at the **beginning of the recitation**. If you don't have it done you'll lose 20% of the lab grade for that lab.





---

# CprE 2810: Digital Logic (Fall 2024)

4:25 - 5:15 pm (Mondays, Wednesdays, and Fridays)

Hoover Hall, Room 2055

Instructor: [Alexander Stoytchev](#)

---

- [Syllabus](#)
- [Class Schedule \(Tentative\)](#)
- [Lecture Notes](#) (also in [PDF](#))
- [Labs](#)
- [Recitations](#)
  
- [Extra Readings](#)
  
- [Verilog Stuff](#)
- [Verilog Reference](#)
  
- [i281 CPU](#)
- [i281 CPU Simulator](#)

# CprE 2810: Digital Logic (Lab Assignments)

- [Lab 1](#)
- [Lab 2](#)
- [Lab 3](#)
- [Lab 4](#)
- [Lab 5](#)
- [Mini Project](#)
- [Lab 6](#)
- [Lab 7](#)
- [Lab 8](#)
- [Lab 9](#)
- [Lab 10](#)
- [Lab 11](#)
- [Lab 12](#)
- [Lab 13](#)
  
- [Remote Access Instructions](#)

# Index

Name	Last modified	Size
<a href="#">Parent Directory</a>		-
<a href="#">CPRE281_LAB01(Answer_Sheet).docx</a>	2021-08-27 14:02	26K
<a href="#">CPRE281_LAB01(Answer_Sheet).pdf</a>	2021-08-27 14:03	338K
<a href="#">CPRE281_LAB01.docx</a>	2021-08-27 14:04	1.9M
<a href="#">CPRE281_LAB01.pdf</a>	2021-08-27 14:04	1.4M
<a href="#">lab1.zip</a>	2021-08-27 13:56	5.4M



# Index

Name	Last modified	Size
<a href="#">Parent Directory</a>		-
<a href="#">CPRE281_LAB01(Answer_Sheet).docx</a>	2021-08-27 14:02	26K
<a href="#">CPRE281_LAB01(Answer_Sheet).pdf</a>	2021-08-27 14:03	338K
<a href="#">CPRE281_LAB01.docx</a>	2021-08-27 14:04	1.9M
<a href="#">CPRE281_LAB01.pdf</a>	2021-08-27 14:04	1.4M
<a href="#">lab1.zip</a>	2021-08-27 13:56	5.4M

READ one of these at home.

This is the lab assignment.

# Index

Name	Last modified	Size
<a href="#">Parent Directory</a>		-
<a href="#">CPRE281_LAB01(Answer_Sheet).docx</a>	2021-08-27 14:02	26K
<a href="#">CPRE281_LAB01(Answer_Sheet).pdf</a>	2021-08-27 14:03	338K
<a href="#">CPRE281_LAB01.docx</a>	2021-08-27 14:04	1.9M
<a href="#">CPRE281_LAB01.pdf</a>	2021-08-27 14:04	1.4M
<a href="#">lab1.zip</a>	2021-08-27 13:56	5.4M

During the lab next week,  
download this ZIP file and  
follow the instructions.

# Index

Name	Last modified	Size
<a href="#">Parent Directory</a>		-
<a href="#">CPRE281_LAB01(Answer_Sheet).docx</a>	2021-08-27 14:02	26K
<a href="#">CPRE281_LAB01(Answer_Sheet).pdf</a>	2021-08-27 14:03	338K
<a href="#">CPRE281_LAB01.docx</a>	2021-08-27 14:04	1.9M
<a href="#">CPRE281_LAB01.pdf</a>	2021-08-27 14:04	1.4M
<a href="#">lab1.zip</a>	2021-08-27 13:56	5.4M

Print this file,  
complete the prelab,  
and bring it with you  
to the lab.

# Index

Name	Last modified	Size
<a href="#">Parent Directory</a>		-
<a href="#">CPRE281_LAB01(Answer_Sheet).docx</a>	2021-08-27 14:02	26K
<a href="#">CPRE281_LAB01(Answer_Sheet).pdf</a>	2021-08-27 14:03	338K
<a href="#">CPRE281_LAB01.docx</a>	2021-08-27 14:04	1.9M
<a href="#">CPRE281_LAB01.pdf</a>	2021-08-27 14:04	1.4M
<a href="#">lab1.zip</a>	2021-08-27 13:56	5.4M

This is the same,  
but in Word format.

Name and Student ID: \_\_\_\_\_ Lab Section: \_\_\_\_\_

Date: \_\_\_\_\_

**PRELAB:**

**Q1.** Fill in the Truth Table below for an AND gate:

A	B	C
0	0	
0	1	
1	0	
1	1	

**Q2.** What does the .bdf file extension stand for?

**Q3.** What is the name of the FPGA on the DE2-115 board?

TA Initials: \_\_\_\_\_

**LAB:**

**2.0 Fill in the Truth Table for *lab1step1*:**

A	B	C
0	0	
0	1	
1	0	
1	1	

Logic Expression: \_\_\_\_\_

This is the prelab  
for lab #1.

Quartus Simulation TA Initials: \_\_\_\_\_ Questa ModelSim TA Initials: \_\_\_\_\_

**4.0 Fill in the Truth Table for *lab1step2*:**

W	X	Y	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Logic Expression: \_\_\_\_\_

TA Initials: \_\_\_\_\_

**4.0 Fill in the Truth Table for *lab1step3*:**

A	B	C	F

Logic Expression: \_\_\_\_\_

TA Initials: \_\_\_\_\_

# CprE 2810: Digital Logic (Lab Assignments)

- [Lab 1](#)
- [Lab 2](#)
- [Lab 3](#)
- [Lab 4](#)
- [Lab 5](#)
- [Mini Project](#)
- [Lab 6](#)
- [Lab 7](#)
- [Lab 8](#)
- [Lab 9](#)
- [Lab 10](#)
- [Lab 11](#)
- [Lab 12](#)
- [Lab 13](#)
- [Remote Access Instructions](#)





# Lab Safety

**This class has a substantial hands-on laboratory section. Students will be using expensive, sensitive, and potentially hazardous equipment. Safety in the lab is a number one priority for students and instructors and to ensure a safe laboratory experience, a brief safety presentation will be given during the first lab session. It is mandatory that all students attend this presentation. Moreover, it is expected that students follow any and all posted safety guidelines. All students must sign the [lab safety form](#) (posted in the syllabus).**

**For reference, a copy of the University Laboratory Safety Manual can be found at:**

**[www.ehs.iastate.edu/sites/default/files/uploads/publications/manuals/labsm.pdf](http://www.ehs.iastate.edu/sites/default/files/uploads/publications/manuals/labsm.pdf)**

**See also the [safety page of the ECpE Department](#):**


**<http://www.ece.iastate.edu/the-department/safety/>**



# A Binary Switch




(a) Two states of a switch

 


(b) Symbol for a switch

# A Light Controlled by a Switch

 


(a) Simple connection to a battery


# A Light Controlled by a Switch

 

# A Light Controlled by a Switch

 

# A Light Controlled by a Switch

 


(b) Using a ground connection as the return path


**Logic AND with Switches**  
**(series connection of the switches)**




# AND Circuit

 


# AND Circuit

 

# AND Circuit

 


# AND Circuit

 


# **Logic OR with Switches**

**(parallel connection of the switches)**


# OR Circuit

 

# OR Circuit

 


# OR Circuit

 




# OR Circuit

 


# **Logic NOT with a Switch (an inverting circuit)**


# NOT Circuit

 


# NOT Circuit

 


# The Three Basic Logic Gates

 

NOT gate

 


AND gate

 


OR gate

# Truth Table for NOT

 


$x$	$\bar{x}$
0	1
1	0

# Truth Table for AND

 

$x_1$	$x_2$	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

# Truth Table for OR

 

$x_1$	$x_2$	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1




# Truth Tables for AND and OR

$x_1$	$x_2$	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1


AND

OR

# Logic Gates with n Inputs

 

AND gate

 


OR gate

# Truth Table for 3-input AND and OR

$x_1$	$x_2$	$x_3$	$x_1 \cdot x_2 \cdot x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


[ Figure 2.7 from the textbook ]

# A series-parallel connection of the switches

 



[ Figure 2.4 from the textbook ]

# Example of a Logic Circuit Implemented with Logic Gates

 


[ Figure 2.8 from the textbook ]

# Example of a Logic Circuit Implemented with Logic Gates

  


[ Figure 2.8 from the textbook ]

# Circuit Analysis

 

(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$


# Circuit Analysis

 

(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$




# Circuit Analysis

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

# Circuit Analysis

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

# Circuit Analysis

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

# Circuit Analysis

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

# Circuit Analysis

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

# Circuit Analysis

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

# Circuit Analysis

 

(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$


# Circuit Analysis

 

(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$




# Circuit Analysis

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

# Circuit Analysis

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$
 
# Circuit Analysis with Sequential Inputs




(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$
 
# Circuit Analysis with Sequential Inputs



(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

 
# Circuit Analysis with Sequential Inputs




(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

[ Figure 2.10 from the textbook ]
 
# Circuit Analysis with Sequential Inputs




(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

 


[ Figure 2.10 from the textbook ]
 
# Circuit Analysis with Sequential Inputs




(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

 


[ Figure 2.10 from the textbook ]
 
# Circuit Analysis with Sequential Inputs




(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

 


[ Figure 2.10 from the textbook ]


 
# Circuit Analysis with Sequential Inputs




(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

 


[ Figure 2.10 from the textbook ]
 
# Circuit Analysis with Sequential Inputs




(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

 

[ Figure 2.10 from the textbook ]

# Timing Diagram

 


[ Figure 2.10 from the textbook ]

# Truth Table for this Logic Circuit

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1


[ Figure 2.10 from the textbook ]
 
# Truth Table for $f = \overline{x_1} + x_1 x_2$




$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1
 
# Truth Table for $f = \overline{x_1} + x_1 x_2$




$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1
 
# Truth Table for $f = \overline{x_1} + x_1 x_2$



$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

 
# Truth Table for $f = \overline{x_1} + x_1 x_2$



$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1



 
# Truth Table for $f = \overline{x_1} + x_1 x_2$



$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

 
# Truth Table for $f = \overline{x_1} + x_1 x_2$



$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1




# Functionally Equivalent Circuits

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$

# Functionally Equivalent Circuits

 

 (a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$




(d) Network that implements  $g = \bar{x}_1 + x_2$




# **Logic XOR with Switches**

# XOR Circuit

 





# XOR Circuit

 


# XOR Circuit

 

# XOR Circuit

 

# The XOR Logic Gate

 


(a) Two switches that control a light

$x$	$y$	$L$
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table


# The XOR Logic Gate

 

(a) Two switches that control a light

$x$	$y$	$L$
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table

 


(c) Logic network




(d) XOR gate symbol

# XOR Analysis

 


[ Figure 2.11c from the textbook ]

## XOR Analysis (x=0, y=0)

 


## XOR Analysis (x=0, y=0)

 





## XOR Analysis (x=0, y=0)

 


## XOR Analysis (x=0, y=0)

 

## XOR Analysis (x=0, y=0)

 


# XOR Analysis

 


[ Figure 2.11c from the textbook ]

## XOR Analysis (x=0, y=1)

 


# XOR Analysis

 


[ Figure 2.11c from the textbook ]

## XOR Analysis (x=1, y=0)

 


# XOR Analysis

 

[ Figure 2.11c from the textbook ]



## XOR Analysis (x=1, y=1)

 

# Truth Table for XOR



$x$	$y$	$L$
0	0	0
0	1	1
1	0	1
1	1	0

# Truth Table for XOR



$x$	$y$	$L$
0	0	0
0	1	1
1	0	1
1	1	0

The output is 1 only if the two inputs are different.



# Addition of Binary Numbers

$a$	0	0	1	1
$+b$	$+0$	$+1$	$+0$	$+1$
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
$s_1 s_0$	0 0	0 1	0 1	1 0

[ Figure 2.12 from the textbook ]

# Addition of Binary Numbers

$$\begin{array}{r} a \\ + b \\ \hline s_1 s_0 \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 0 \end{array}$$

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

[ Figure 2.12 from the textbook ]

# Addition of Binary Numbers

<i>a</i>	0	0	1	1
<u>+ <i>b</i></u>	<u>+ 0</u>	<u>+ 1</u>	<u>+ 0</u>	<u>+ 1</u>
<i>s</i> <sub>1</sub> <i>s</i> <sub>0</sub>	0 0	0 1	0 1	1 0

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$a$	0	0	1	1
$+b$	$+0$	$+1$	$+0$	$+1$
$\hline$	$\hline$	$\hline$	$\hline$	$\hline$
$s_1 s_0$	0 0	0 1	0 1	1 0

$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



# Addition of Binary Numbers

$$\begin{array}{r} a \\ + b \\ \hline s_1 s_0 \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 0 \end{array}$$

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$a$	0	0	1	1
$+b$	$+0$	$+1$	$+0$	$+1$
$s_1 s_0$	0 0	0 1	0 1	1 0

$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$a$	0	0	1	1
$+b$	$+0$	$+1$	$+0$	$+1$
$s_1 s_0$	0 0	0 1	0 1	1 0

$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$a$	0	0	1	1
$+b$	<u>+0</u>	<u>+1</u>	<u>+0</u>	<u>+1</u>
$s_1 s_0$	0 0	0 1	0 1	1 0

$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$$\begin{array}{r} a \\ + b \\ \hline s_1 s_0 \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 0 \end{array}$$

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$$\begin{array}{r} a \\ + b \\ \hline s_1 s_0 \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 0 \end{array}$$

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$a$	0	0	1	1
$+b$	<u>+0</u>	<u>+1</u>	<u>+0</u>	<u>+1</u>
$s_1 s_0$	0 0	0 1	0 1	1 0

$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$$\begin{array}{r} a \\ + b \\ \hline s_1 \ s_0 \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 \ 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 \ 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 \ 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 \ 0 \end{array}$$

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



# Addition of Binary Numbers

$$\begin{array}{r} a \\ + b \\ \hline s_1 s_0 \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 0 \end{array}$$

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$$\begin{array}{r} a \\ + b \\ \hline s_1 s_0 \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 0 \end{array}$$

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

?

<i>a</i>	<i>b</i>		<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0		0	0
0	1		0	1
1	0		0	1
1	1		1	0

# Addition of Binary Numbers

AND

<i>a</i>	<i>b</i>		<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0		0	0
0	1		0	1
1	0		0	1
1	1		1	0

# Addition of Binary Numbers

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

?

<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

XOR


<i>a</i>	<i>b</i>	<i>s</i> <sub>1</sub>	<i>s</i> <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



# Addition of Binary Numbers


$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

 

$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Addition of Binary Numbers

 


$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0




The following examples came from this book



 


[ Platt 2009 ]

 

[ Platt 2009 ]



 

[ Platt 2009 ]



**Questions?**

**THE END**