

CprE 2810: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Incompletely Specified Functions & Multiple-Output Circuits

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW4 is due on Monday Sep 23 @ 10 pm**
- **It is posted on the class web page**
- **I also sent you an e-mail with the link.**

Administrative Stuff

- **HW5 is due on Monday Sep 30 @ 10 pm**
- **It is posted on the class web page**
- **I also sent you an e-mail with the link.**

TA Office Hours

- **Hanif Lashari: Mondays 2:10 – 3:10pm**
- **Le Zhang: Wednesdays 11 am – 1pm**
- **Himani Kohli: Thursdays 9 – 10 am**

Go to the Transformative Learning Area (TLA) on the first floor in Coover Hall. Look for a sign that says “CprE 2810 TA.”

Administrative Stuff

- **Midterm Exam #1**
- **When: Friday Sep 27.**
- **What: Chapter 1 and Chapter 2 plus number systems**
- **The exam will be closed book but open notes
(you can bring up to 3 pages of handwritten notes).**
- **It will be in this room.**
- **Sample exams are posted on the class web page.**

Topics for the Midterm Exam

- **Binary Numbers**
- **Octal Numbers**
- **Hexadecimal Numbers**
- **Conversion between the different number systems**
- **Truth Tables**
- **Boolean Algebra**
- **Logic Gates**
- **Circuit Synthesis with AND, OR, NOT**
- **Circuit Synthesis with NAND, NOR**
- **Converting an AND/OR/NOT circuit to NAND circuit**
- **Converting an AND/OR/NOT circuit to NOR circuit**
- **SOP and POS expressions**

Topics for the Midterm Exam

- Mapping a Circuit to Verilog code
- Mapping Verilog code to a circuit

- Multiplexers
- Venn Diagrams
- K-maps for 2, 3, and 4 variables

- Minimization of Boolean expressions using theorems
- Minimization of Boolean expressions with K-maps

- Incompletely specified functions (with don't cares)
- Functions with multiple outputs


- Something from Star Wars

One-Variable K-Map

One-Variable K-map

x_1	f
0	m_0
1	m_1

(a) Truth table

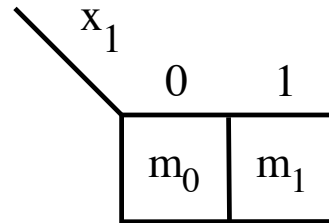


(b) Karnaugh map

One-Variable K-map

x_1	f
0	1
1	0

(a) Truth table

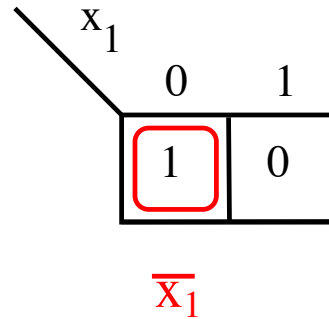


(b) Karnaugh map

Two-Variable K-Map

Two-Variable K-map

x_1	x_2	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

(a) Truth table

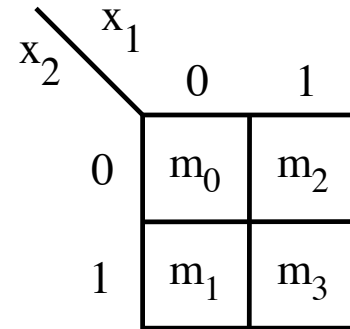

(b) Karnaugh map

These are all valid groupings

	x_1	0	1
x_2	0	1	0
	1	0	0

$$\bar{x}_1 \bar{x}_2$$

	x_1	0	1
x_2	0	0	0
	1	1	0

$$\bar{x}_1 x_2$$

	x_1	0	1
x_2	0	0	1
	1	0	0

$$x_1 \bar{x}_2$$

	x_1	0	1
x_2	0	0	0
	1	0	1

$$x_1 x_2$$

These are all valid groupings

	x_1	0	1
x_2	0	1	0
	1	1	0

\bar{x}_1

	x_1	0	1
x_2	0	0	1
	1	0	1

x_1

	x_1	0	1
x_2	0	1	1
	1	0	0

\bar{x}_2

	x_1	0	1
x_2	0	0	0
	1	1	1

x_2

This one is valid too

A Karnaugh map for two variables, x_1 and x_2 . The map is a 2x2 grid. The columns are labeled x_1 with values 0 and 1. The rows are labeled x_2 with values 0 and 1. All four cells in the grid contain the value 1. A red rounded rectangle is drawn around the entire 2x2 grid, indicating that all minterms are included in the function.

$x_2 \backslash x_1$	0	1
0	1	1
1	1	1


In this case the result is the constant function 1.

Why are these two not valid?

$x_2 \backslash x_1$	0	1
0	1	0
1	0	1

$x_2 \backslash x_1$	0	1
0	0	1
1	1	0

Minimization Example with a two-variable K-map

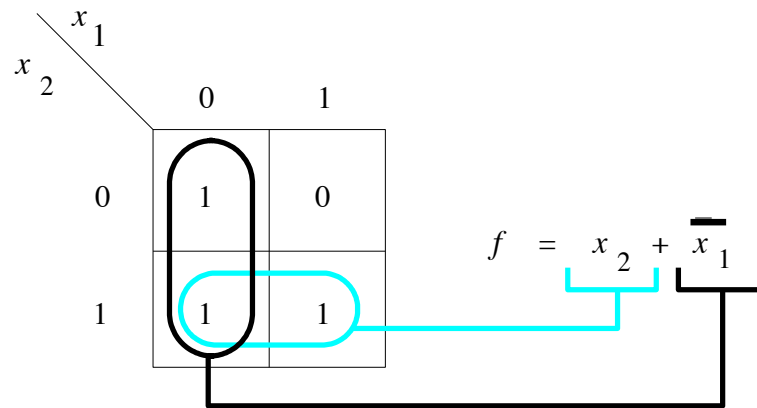

[Figure 2.50 from the textbook]

Three-Variable K-Map

Three-Variable K-map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map

Location of three-variable minterms

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map


Notice the placement of

- **Variables**
- **Binary pair values**
- **Minterms**

Adjacency Rules

$x_3 \backslash x_1x_2$	00	01	11	10
0	m_0	m_2	m_6	m_4
1	m_1	m_3	m_7	m_5

adjacent
columns

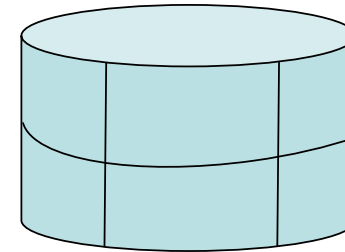


As if the K-map were
drawn on a cylinder

Adjacency Rules

$x_3 \backslash x_1x_2$	00	01	11	10
0	m_0	m_2	m_6	m_4
1	m_1	m_3	m_7	m_5


adjacent
columns

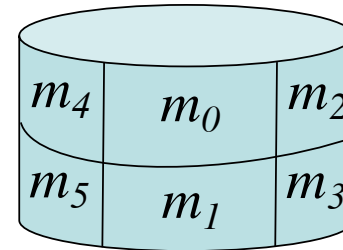


As if the K-map were
drawn on a cylinder

Some **Invalid** Groupings

		x_1x_2			
		00	01	11	10
x_3	0	0	1	0	0
	1	0	0	1	0

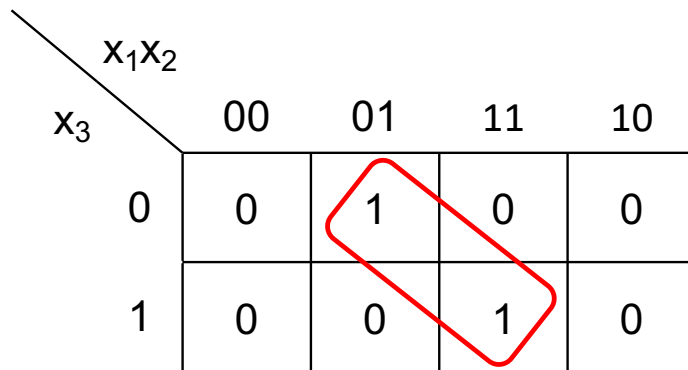A Karnaugh map for three variables x1, x2, and x3. The columns are labeled x1x2 with values 00, 01, 11, 10. The rows are labeled x3 with values 0 and 1. The map contains 1s at (x3=0, x1x2=01) and (x3=1, x1x2=11). A red rounded rectangle is drawn diagonally, enclosing the two 1s. This represents an invalid grouping because the two 1s do not share a common variable.

		x_1x_2			
		00	01	11	10
x_3	0	0	0	1	0
	1	0	1	0	0

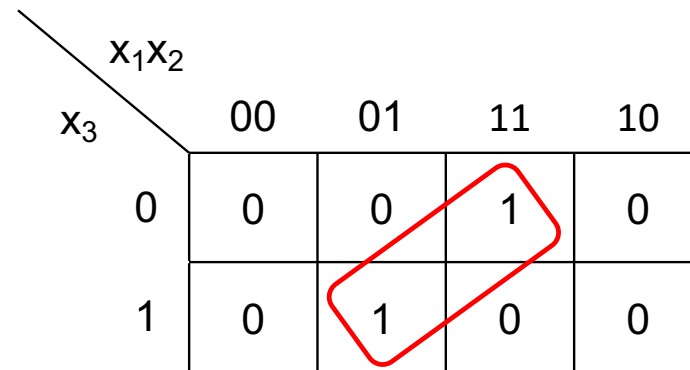A Karnaugh map for three variables x1, x2, and x3. The columns are labeled x1x2 with values 00, 01, 11, 10. The rows are labeled x3 with values 0 and 1. The map contains 1s at (x3=0, x1x2=11) and (x3=1, x1x2=01). A red rounded rectangle is drawn diagonally, enclosing the two 1s. This represents an invalid grouping because the two 1s do not share a common variable.

Can't group diagonally.

Some **Invalid** Groupings

		x_1x_2			
		00	01	11	10
x_3	0	1	1	1	0
	1	0	0	0	0

		x_1x_2			
		00	01	11	10
x_3	0	0	0	0	0
	1	0	1	1	1

Can't group three in a row.
Each side must be a power of 2.


Some **Invalid** Groupings

		x_1x_2			
		00	01	11	10
x_3	0	1	0	1	1
	1	0	0	0	0


		x_1x_2			
		00	01	11	10
x_3	0	0	0	1	0
	1	0	1	1	0

Can't group zeros and ones together.

Three-Variable K-map

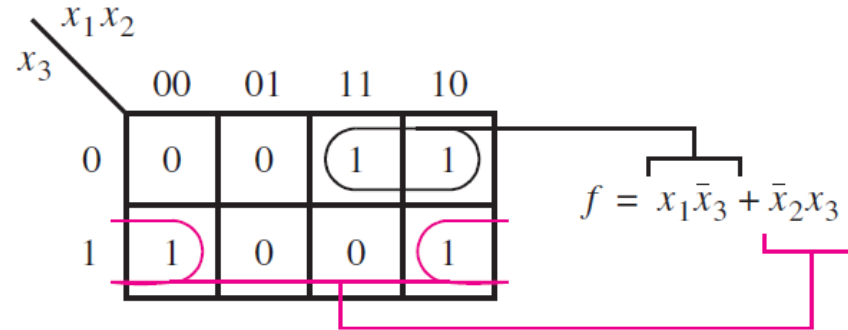

(a) The function of Figure 2.23

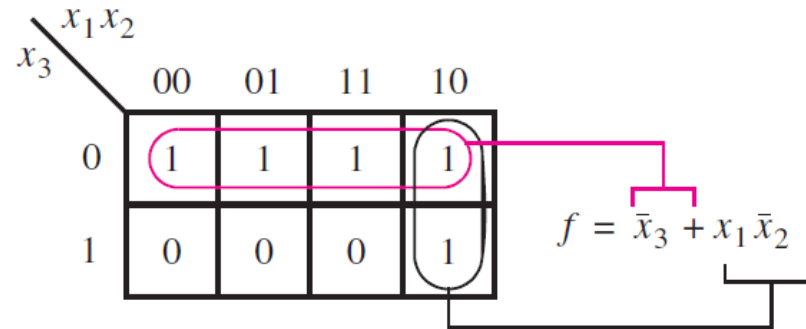

(b) The function of Figure 2.48

From Boolean Expression to K-map

From Boolean Expression to K-map

$$F = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}BC$$

		AB			
		00	01	11	10
C	0	m ₀	m ₂	m ₆	m ₄
	1	m ₁	m ₃	m ₇	m ₅

From Boolean Expression to K-map

$$F = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}BC$$

		AB			
		00	01	11	10
C	0				
	1				

From Boolean Expression to K-map

$$F = \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{A}BC$$

		AB			
		00	01	11	10
C	0	1	1		
	1				

From Boolean Expression to K-map

$$F = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}BC$$

		AB			
		00	01	11	10
C	0	1	1		
	1				

From Boolean Expression to K-map

$$F = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}BC$$

		AB			
		00	01	11	10
C	0	1	1		
	1	1			

From Boolean Expression to K-map

$$F = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}BC$$

		AB			
		00	01	11	10
C	0	1	1		
	1	1			

From Boolean Expression to K-map

$$F = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}BC$$

		AB			
		00	01	11	10
C	0	1	1		
	1	1	1		

From Boolean Expression to K-map

$$F = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}BC$$

		AB			
		00	01	11	10
C	0	1	1	0	0
	1	1	1	0	0

The Karnaugh map shows the function F for three variables A, B, and C. The rows represent C (0 and 1) and the columns represent AB (00, 01, 11, 10). The values in the cells are 1, 1, 0, 0 for C=0 and 1, 1, 0, 0 for C=1. Three groups are highlighted: a red group covering the top row (C=0), a blue group covering the first column (AB=00), and a green group covering the second column (AB=01).

From Boolean Expression to K-map

$$F = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}BC$$

		AB			
		00	01	11	10
C	0	1	1	0	0
	1	1	1	0	0

\bar{A}

From Boolean Expression to K-map

$$F = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}BC = \bar{A}$$

		AB			
		00	01	11	10
C	0	1	1	0	0
	1	1	1	0	0

\bar{A}

Different Ways to Draw the K-map

Two Different Ways to Draw the K-map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map

		$x_2 x_3$			
		00	01	11	10
x_1	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Another Way to Draw 3-variable K-map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map

		x_1	
		0	1
$x_2 x_3$	00	m_0	m_4
	01	m_1	m_5
	11	m_3	m_7
	10	m_2	m_6

There are 4 different versions!

		x_1x_2			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

		x_2x_3			
		00	01	11	10
x_1	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

		x_3	
		0	1
x_1x_2	00	m_0	m_1
	01	m_2	m_3
	11	m_6	m_7
	10	m_4	m_5

		x_1	
		0	1
x_2x_3	00	m_0	m_4
	01	m_1	m_5
	11	m_3	m_7
	10	m_2	m_6

**Why is it OK to combine
a group of four ones?**

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

x_2 \ $s x_1$	00	01	11	10
0	m_0	m_2	m_6	m_4
1	m_1	m_3	m_7	m_5

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

$x_2 \backslash s x_1$	00	01	11	10
0	000	010	110	100
1	001	011	111	101

Gray Code & K-map

	s	x_1	x_2
m_0	0	0	0
m_1	0	0	1
m_2	0	1	0
m_3	0	1	1
m_4	1	0	0
m_5	1	0	1
m_6	1	1	0
m_7	1	1	1

$x_2 \backslash s x_1$	00	01	11	10
0	000	010	110	100
1	001	011	111	101

These four neighbors
differ in the FIRST and LAST bit

They are similar in their MIDDLE bit

**The K-Map theory uses the
combining theorems of Boolean algebra**

$$**14a. \quad x \cdot y + x \cdot \bar{y} = x**$$

$$**14b. \quad (x + y) \cdot (x + \bar{y}) = x**$$

The K-Map theory uses the combining theorems of Boolean algebra

optimization by 1's

$$14a. \quad \mathbf{x \cdot y + x \cdot \bar{y} = x}$$

$$14b. \quad \mathbf{(x + y) \cdot (x + \bar{y}) = x}$$

**The K-Map theory uses the
combining theorems of Boolean algebra**

$$14a. \quad \mathbf{x \cdot y + x \cdot \bar{y} = x}$$

$$14b. \quad \mathbf{(x + y) \cdot (x + \bar{y}) = x}$$

optimization by 0's

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

Theorem 14a is behind the K-Map theory.
But that theorem is just for two variables.
Why is this grouping of four ones possible?

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \bar{x} y \bar{z} + x y \bar{z} + \bar{x} y z + x y z$$

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \underbrace{\bar{x} y \bar{z} + x y \bar{z}}_{(\bar{x} y + x y) \bar{z}} + \underbrace{\bar{x} y z + x y z}_{(\bar{x} y + x y) z}$$

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = (\bar{x}y + xy)\bar{z} + (\bar{x}y + xy)z$$

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \underbrace{(\bar{x}y + xy)}_{y\bar{z} \text{ (by 14a)}} \bar{z} + \underbrace{(\bar{x}y + xy)}_{yz \text{ (by 14a)}} z$$

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = y \bar{z} + y z$$

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \underbrace{y \bar{z} + y z}_{y \text{ (by 14a)}}$$

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = y$$

Why can we group these four ones?

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

Answer: We can combine them because Theorem 14a is applied three times, not just once.

Alternative Derivation

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

Alternative Derivation

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \bar{x} y \bar{z} + x y \bar{z} + \bar{x} y z + x y z$$

Alternative Derivation

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \bar{x} y \bar{z} + \bar{x} y z + x y \bar{z} + x y z$$

Alternative Derivation

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \underbrace{\bar{x} y \bar{z} + \bar{x} y z}_{\bar{x} (y \bar{z} + y z)} + \underbrace{x y \bar{z} + x y z}_{x (y \bar{z} + y z)}$$

Alternative Derivation

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \bar{x} (y \bar{z} + y z) + x (y \bar{z} + y z)$$

Alternative Derivation

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \underbrace{\bar{x} (y \bar{z} + y z)}_{\bar{x} y \text{ (by 14a)}} + \underbrace{x (y \bar{z} + y z)}_{x y \text{ (by 14a)}}$$

Alternative Derivation

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = \bar{x}y + xy$$

Alternative Derivation

		x y			
	z	00	01	11	10
0		0	1	1	0
1		0	1	1	0

$$f = \underbrace{\bar{x}y + xy}_{y \text{ (by 14a)}}$$

Alternative Derivation

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

$$f = y$$


Alternative Derivation

		x y			
		00	01	11	10
z	0	0	1	1	0
	1	0	1	1	0

Answer: We can combine them because Theorem 14a is applied three times, not just once.

Four-Variable K-Map


A four-variable Karnaugh map

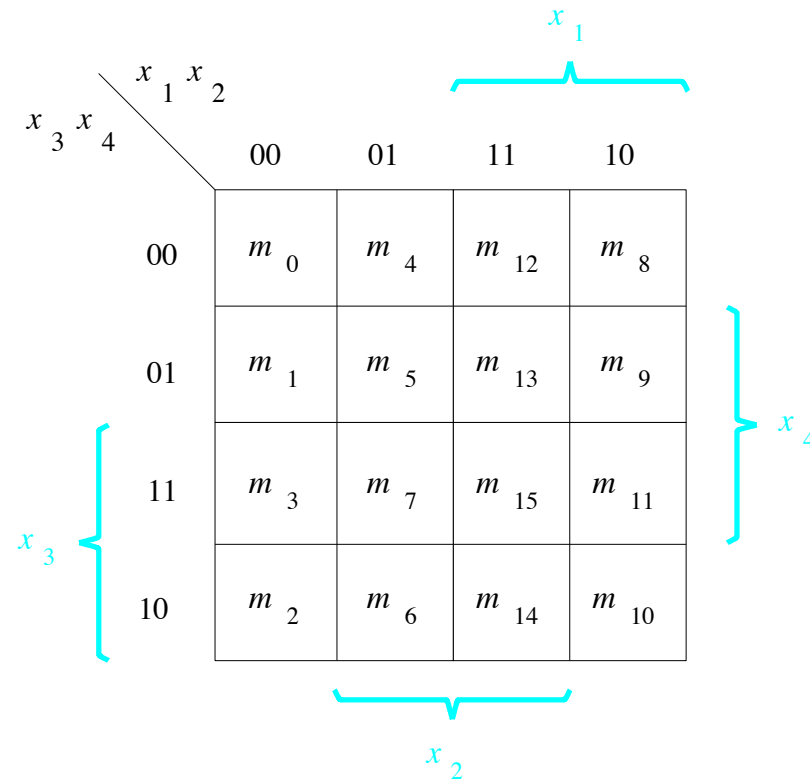

[Figure 2.53 from the textbook]


A four-variable Karnaugh map

x1	x2	x3	x4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

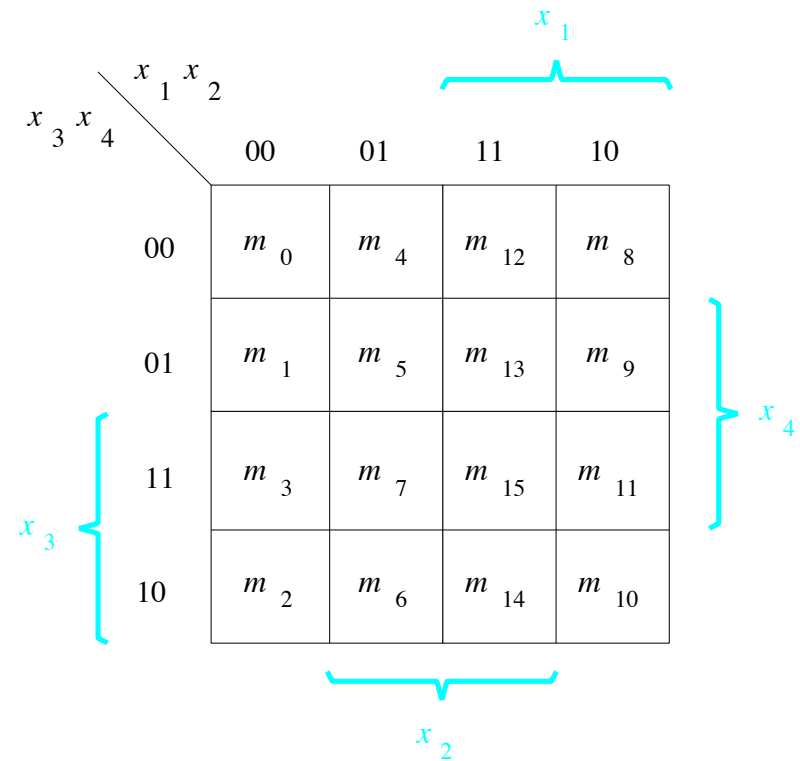


Gray Code & K-map

x1	x2	x3	x4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15


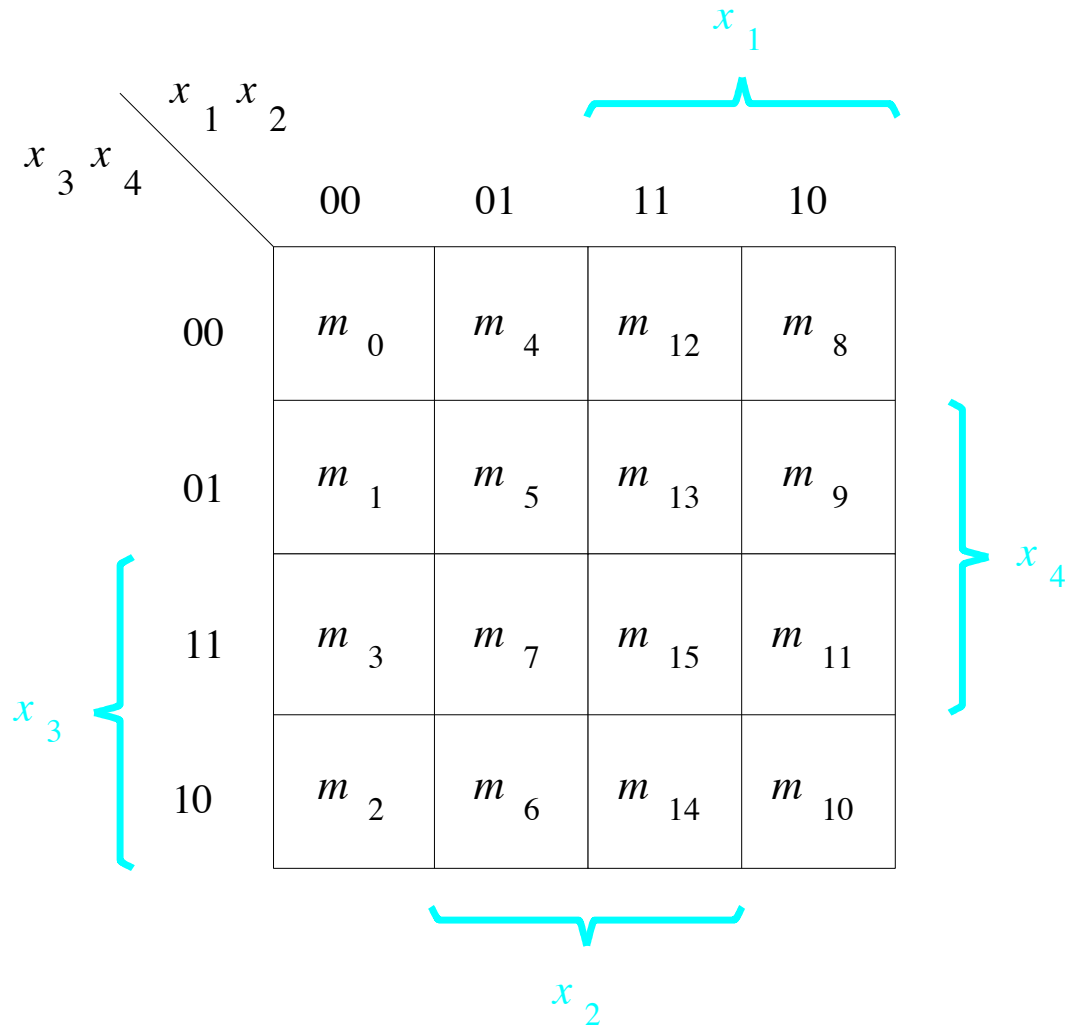


Gray Code & K-map



x1	x2	x3	x4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
<hr/>				
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
<hr/>				
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
<hr/>				
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

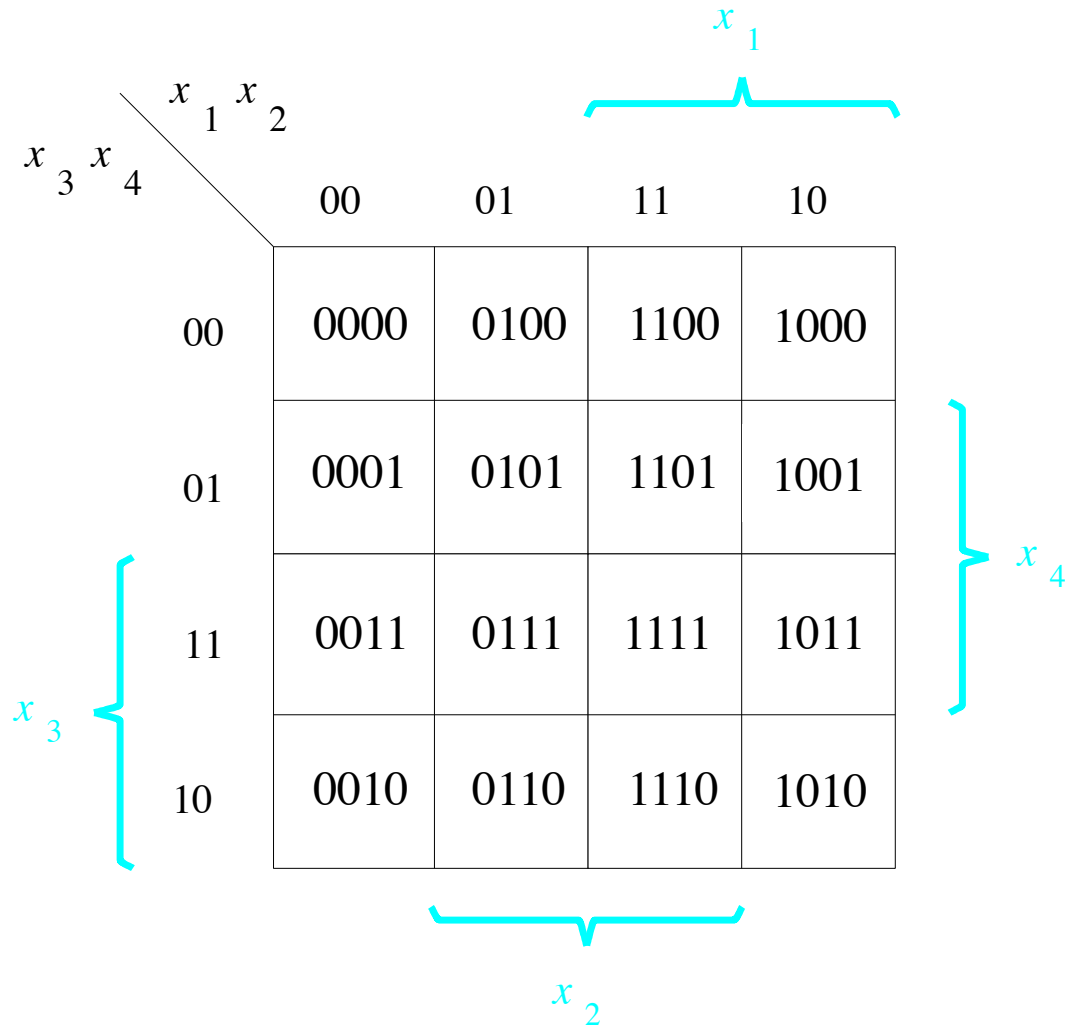

Adjacency Rules

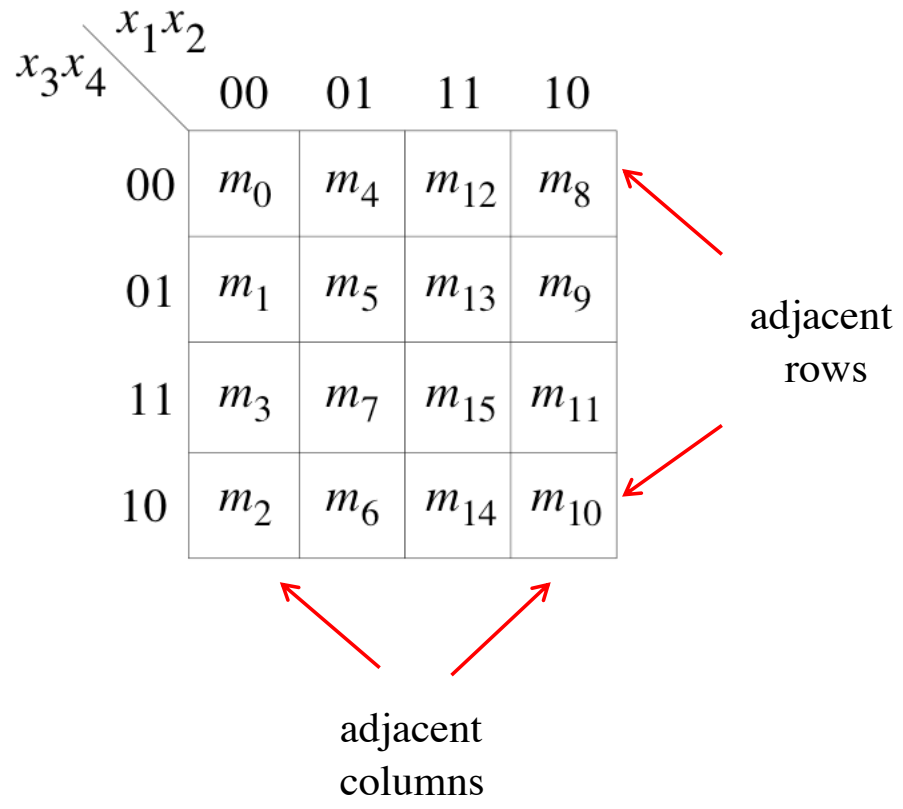
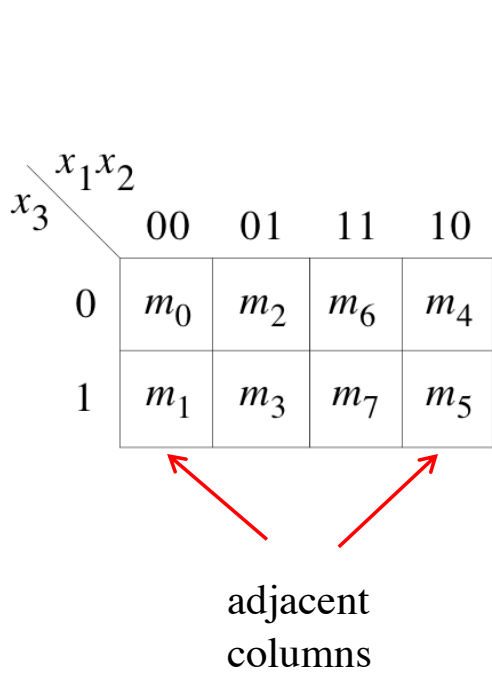


Adjacency Rules

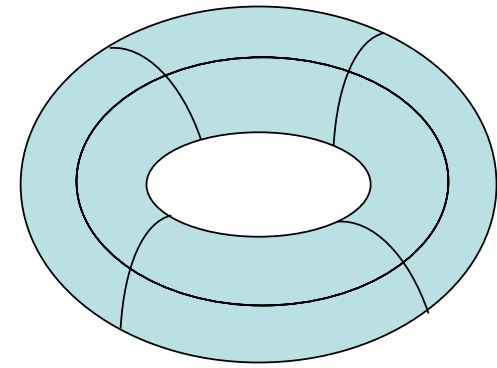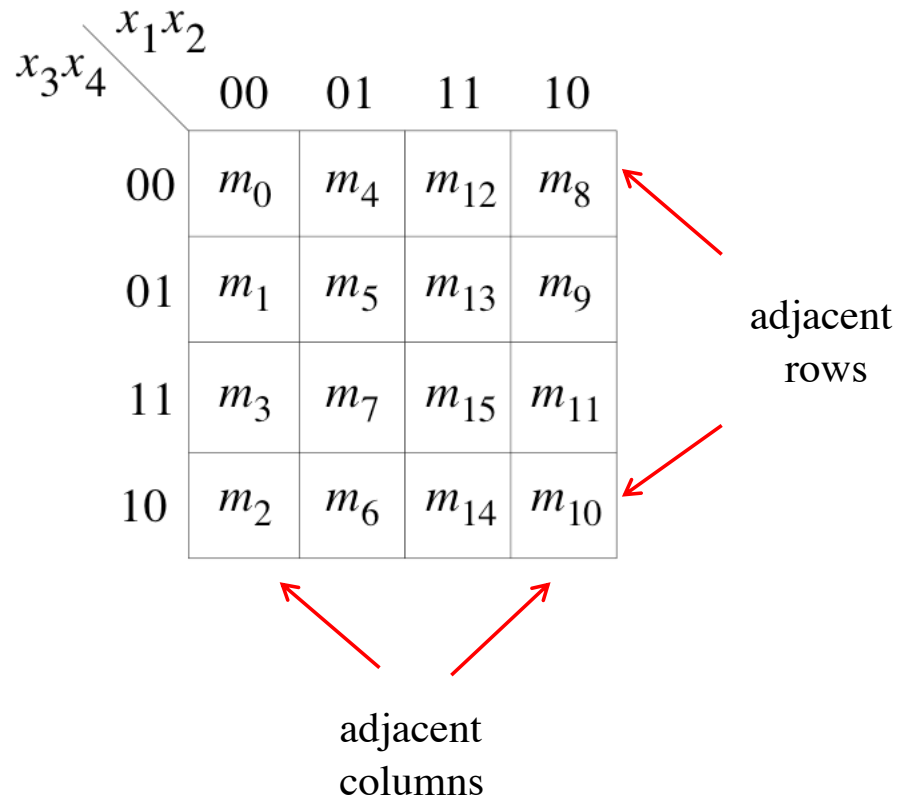



As if the K-map were drawn on a torus

Adjacency Rules

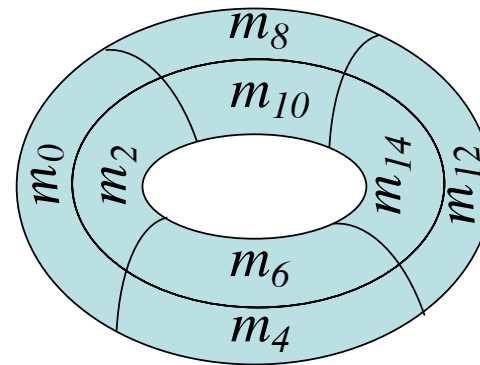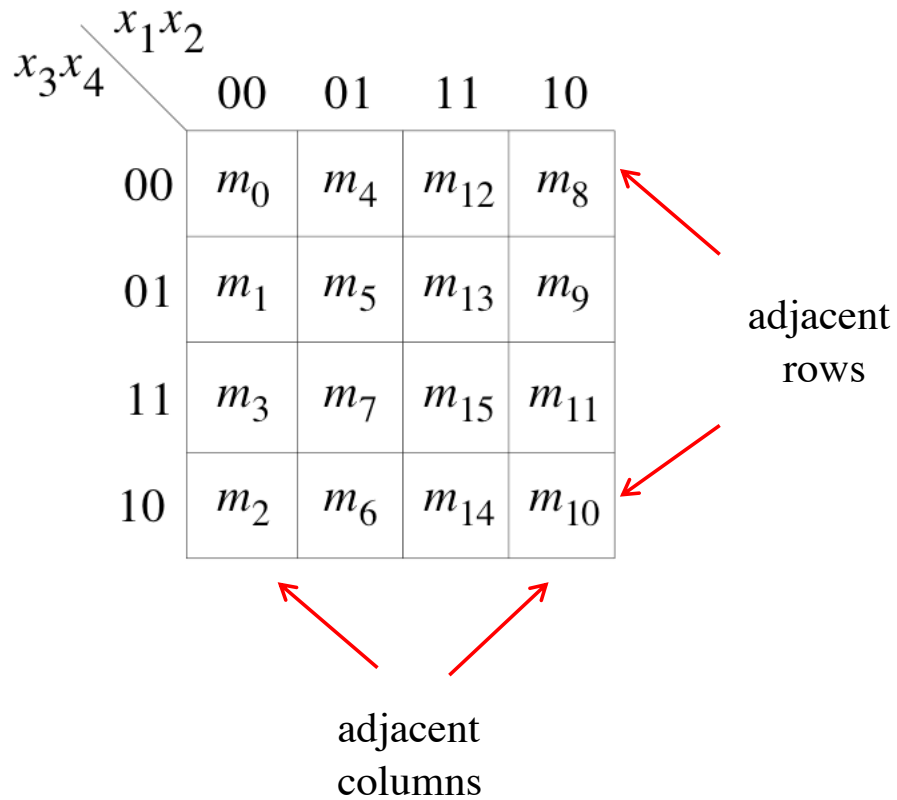


As if the K-map were drawn on a torus

Adjacency Rules

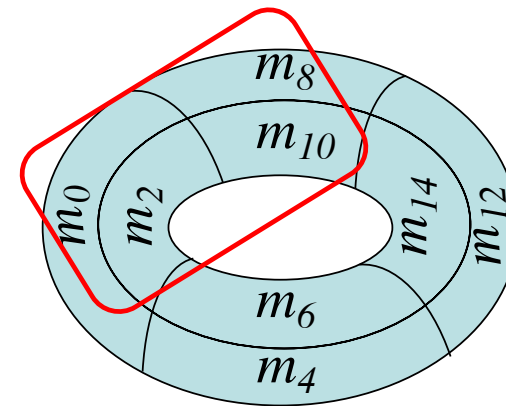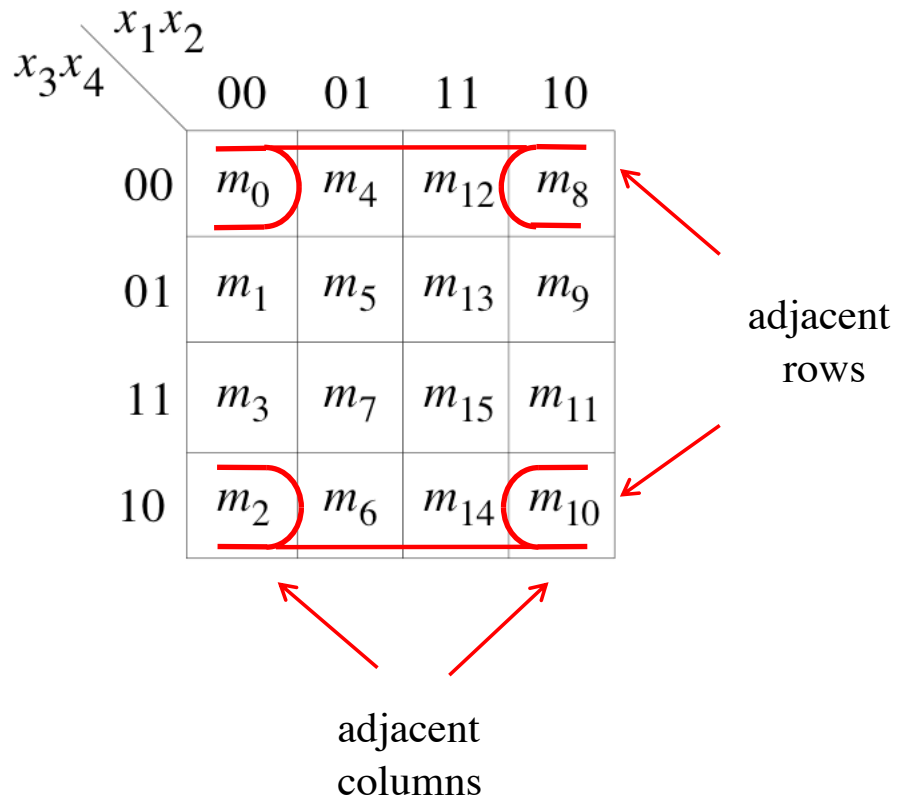


As if the K-map were drawn on a torus

Example of a four-variable Karnaugh map

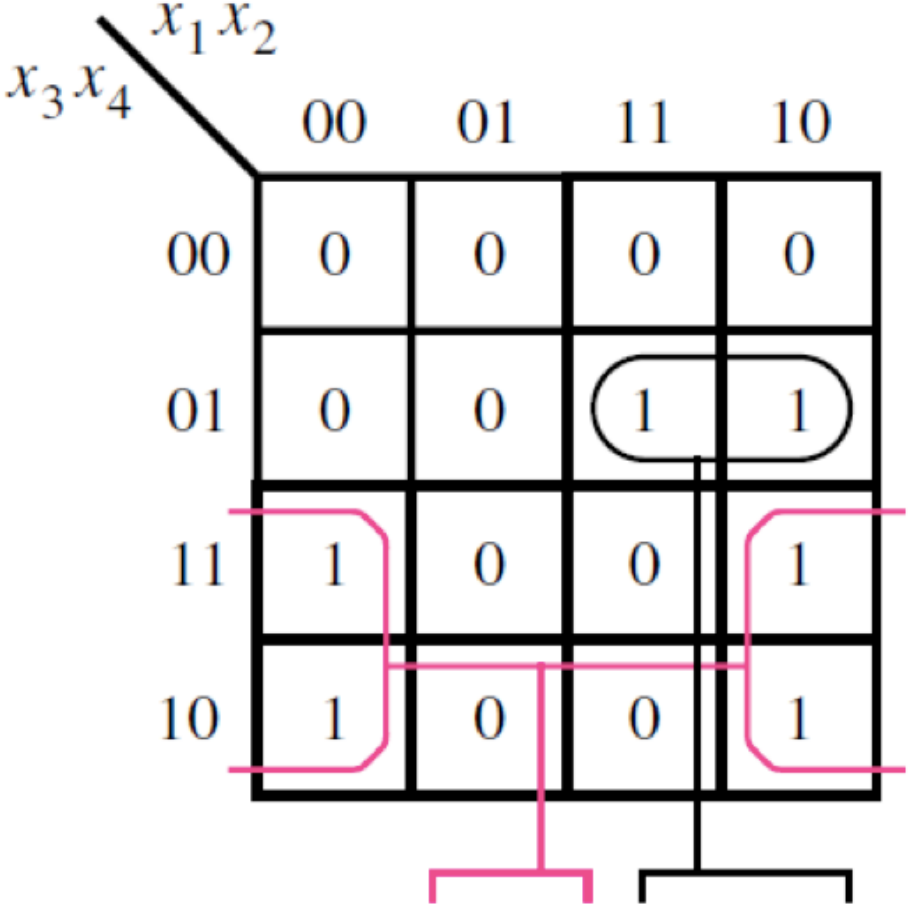


[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

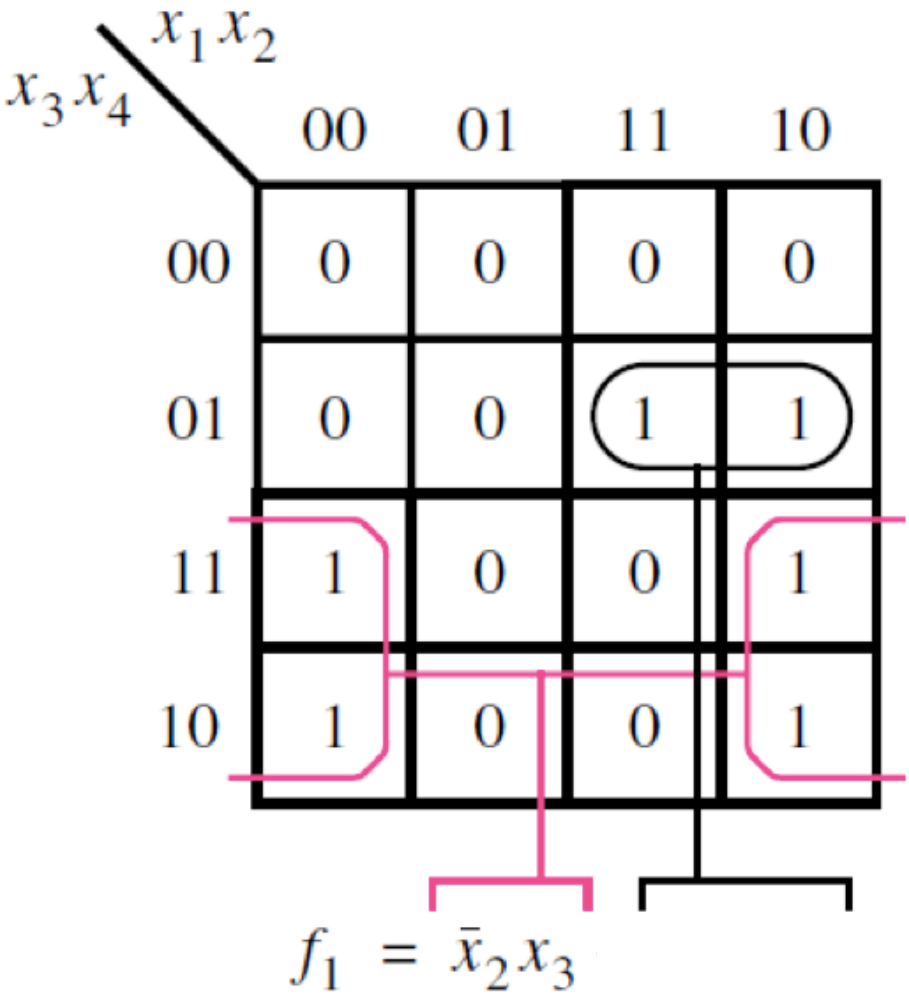


[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

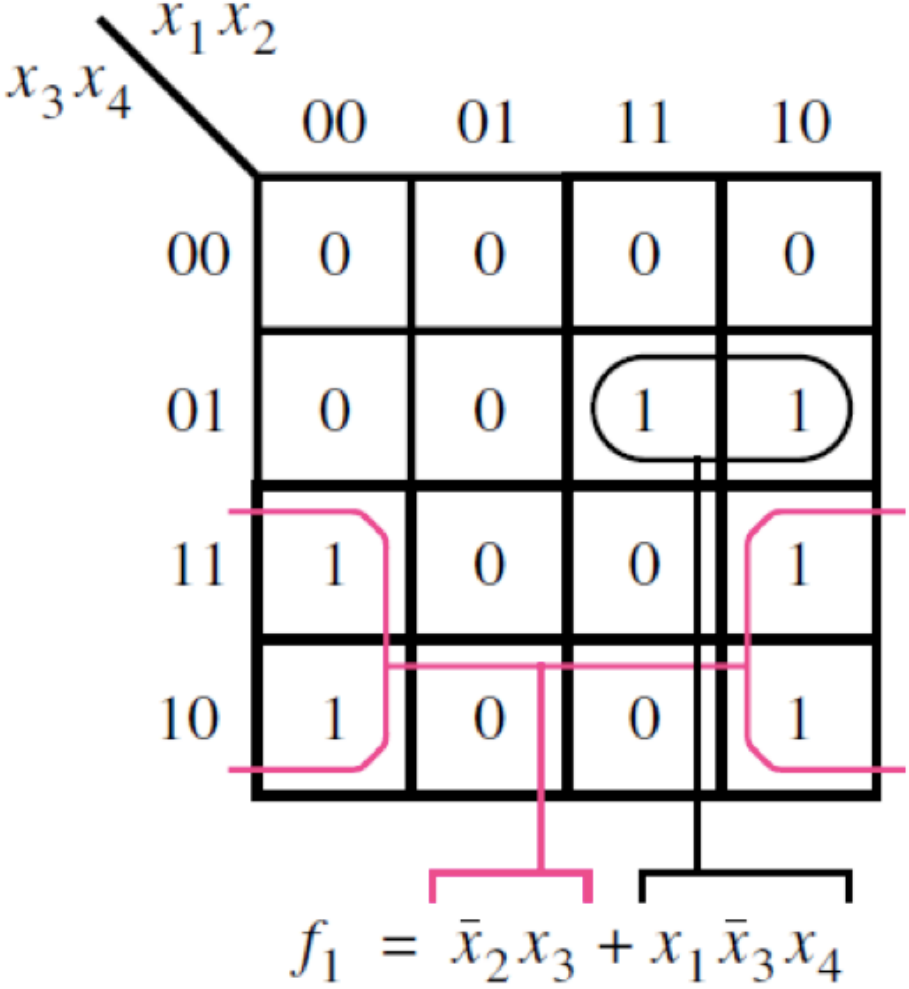


[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

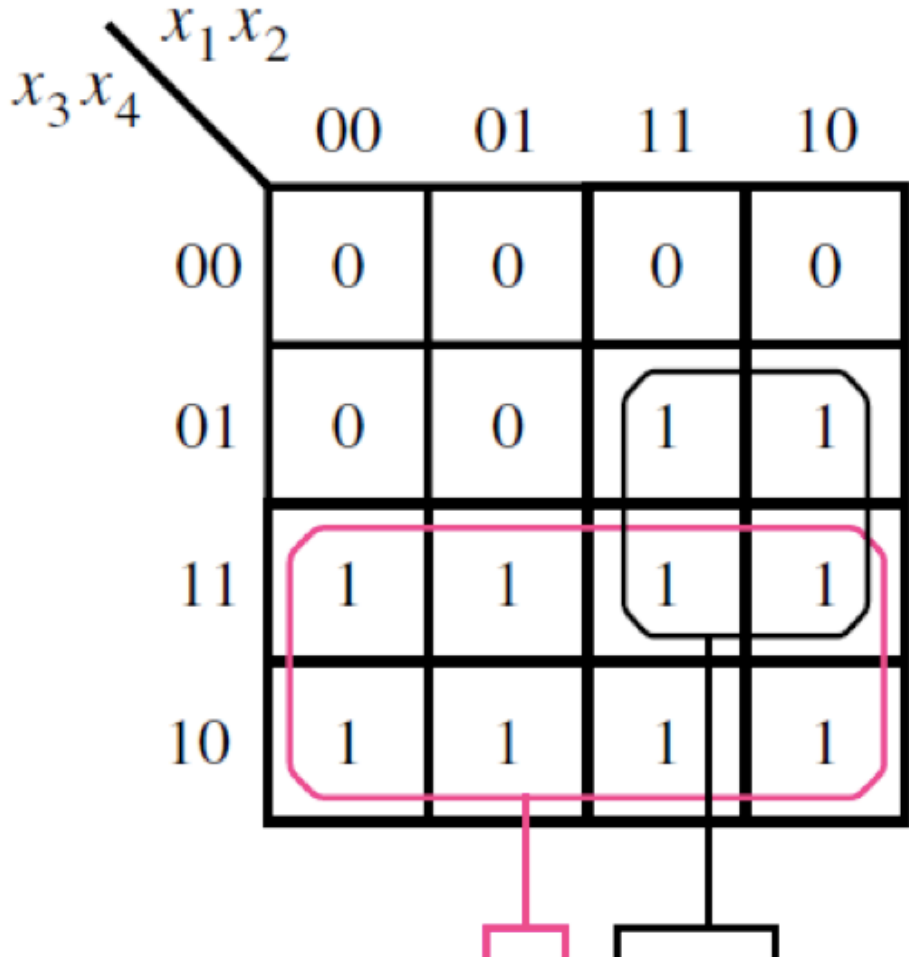


[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

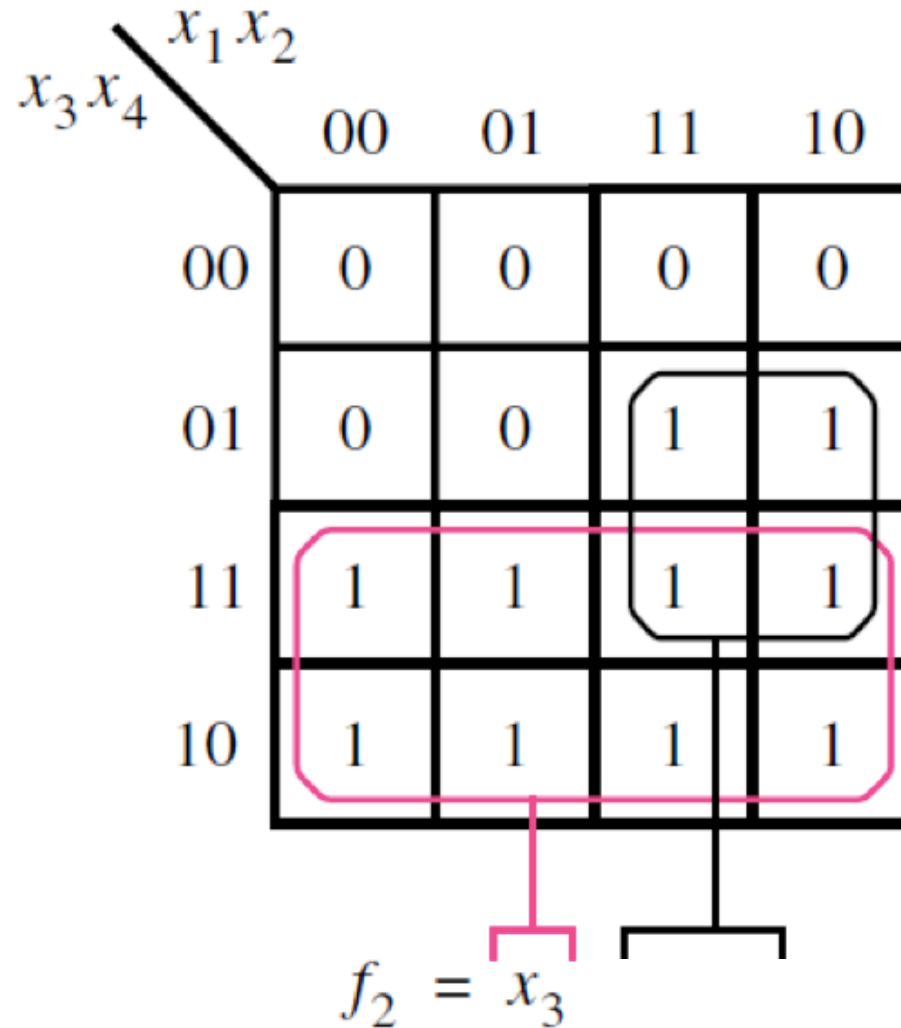





[Figure 2.54 from the textbook]

Example of a four-variable Karnaugh map

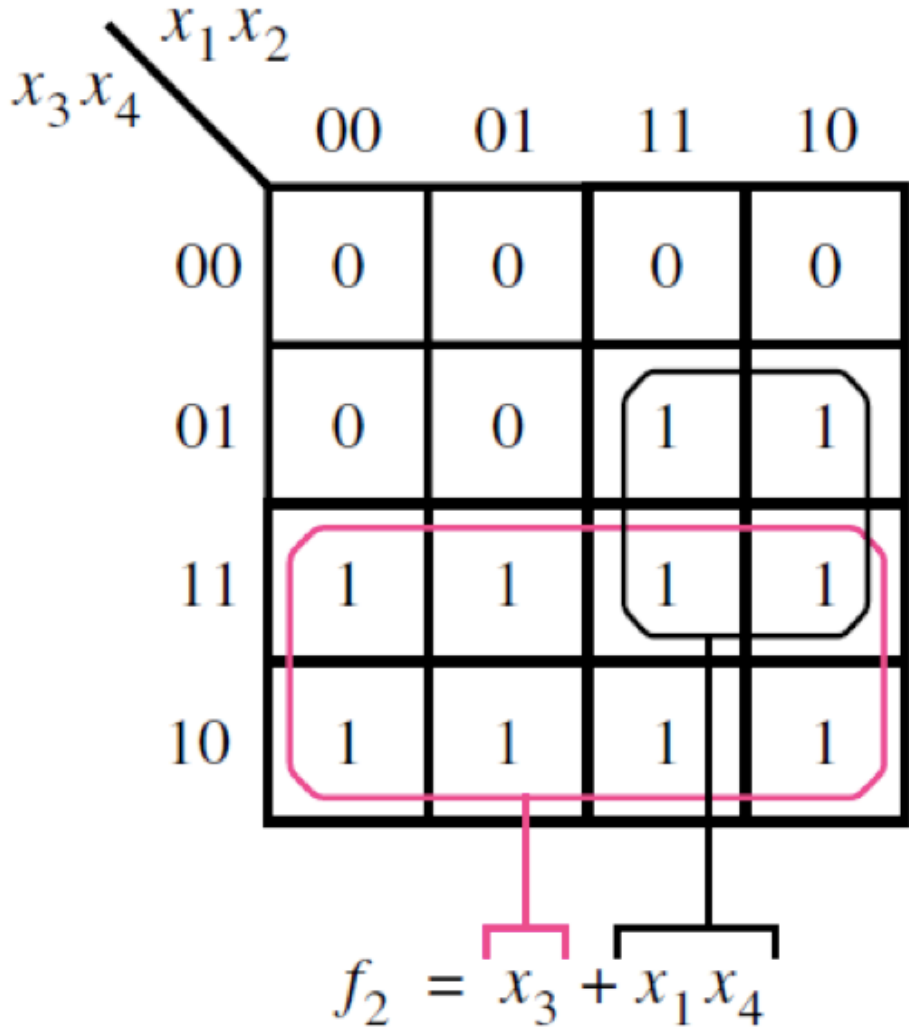

[Figure 2.54 from the textbook]


Other Four-Variable K-map Examples

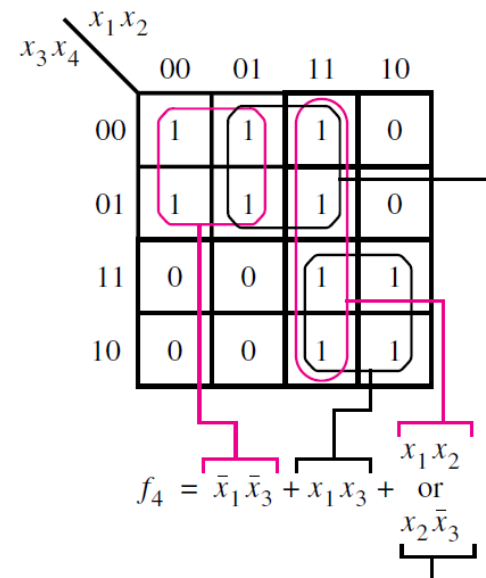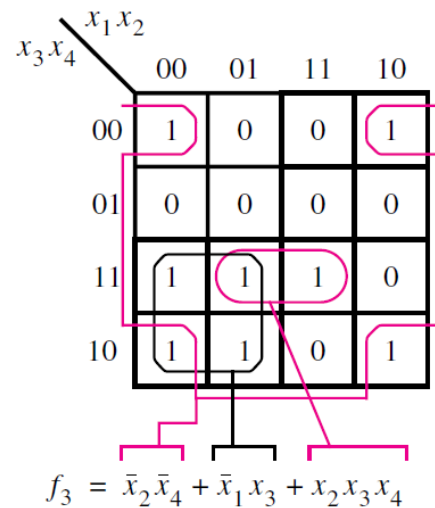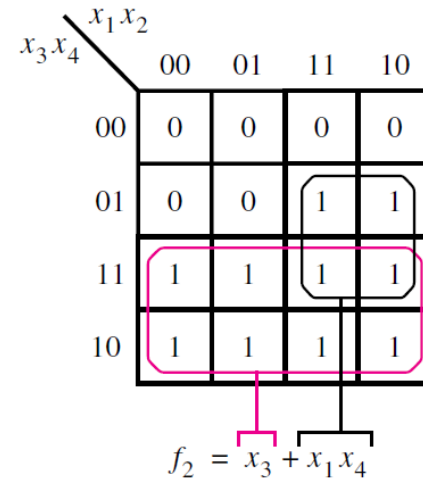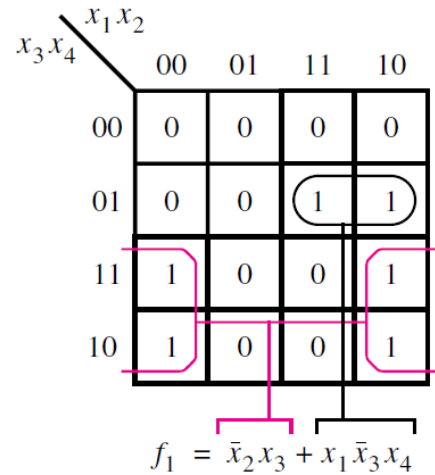

[Figure 2.54 from the textbook]


POS Minimization

POS minimization of $f(x_1, x_2, x_3) = \prod M(4, 5, 6)$

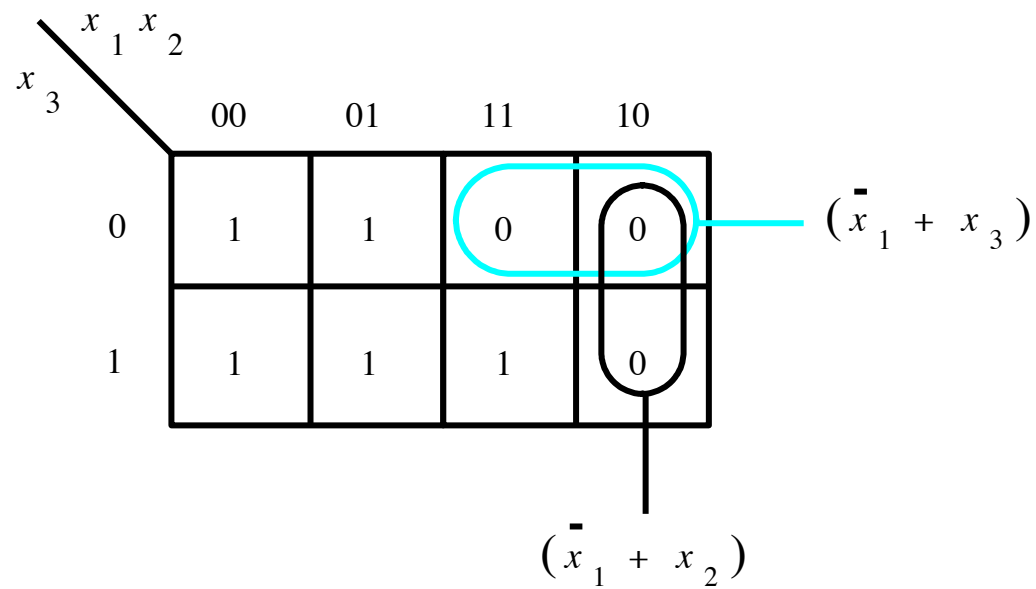

[Figure 2.60 from the textbook]

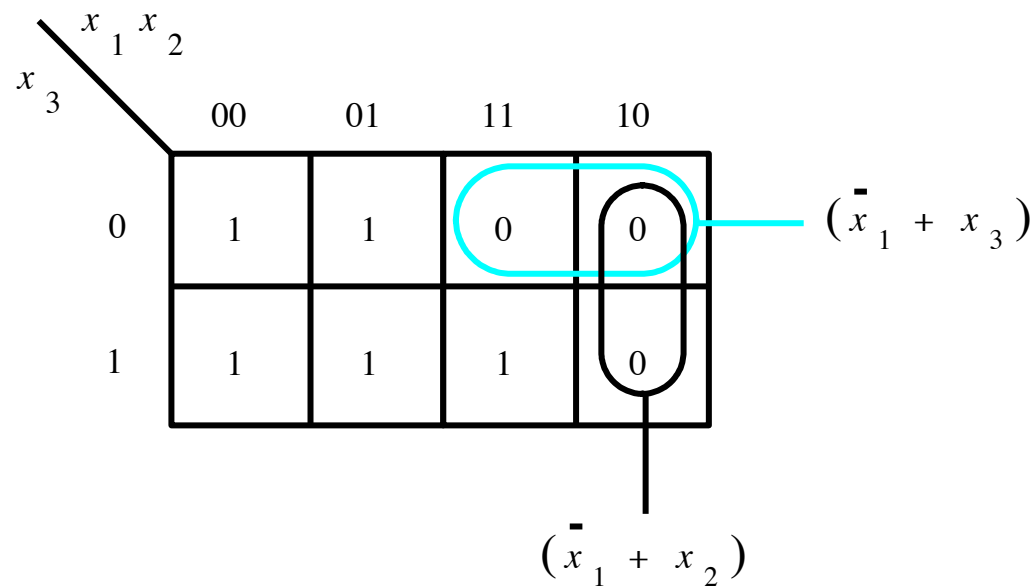
POS minimization of $f(x_1, x_2, x_3) = \prod M(4, 5, 6)$



$$f(x_1, x_2, x_3) = (\bar{x}_1 + x_3)(\bar{x}_1 + x_2)$$


[Figure 2.60 from the textbook]

POS minimization of $f(x_1, \dots, x_4) = \prod M(0, 1, 4, 8, 9, 12, 15)$

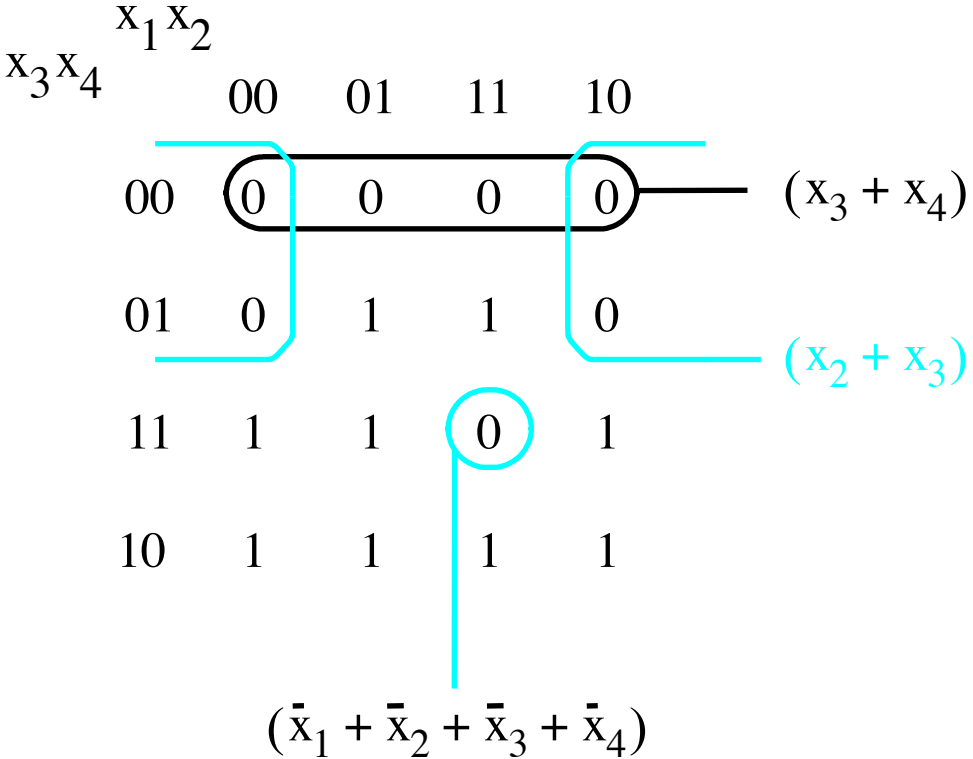

[Figure 2.61 from the textbook]

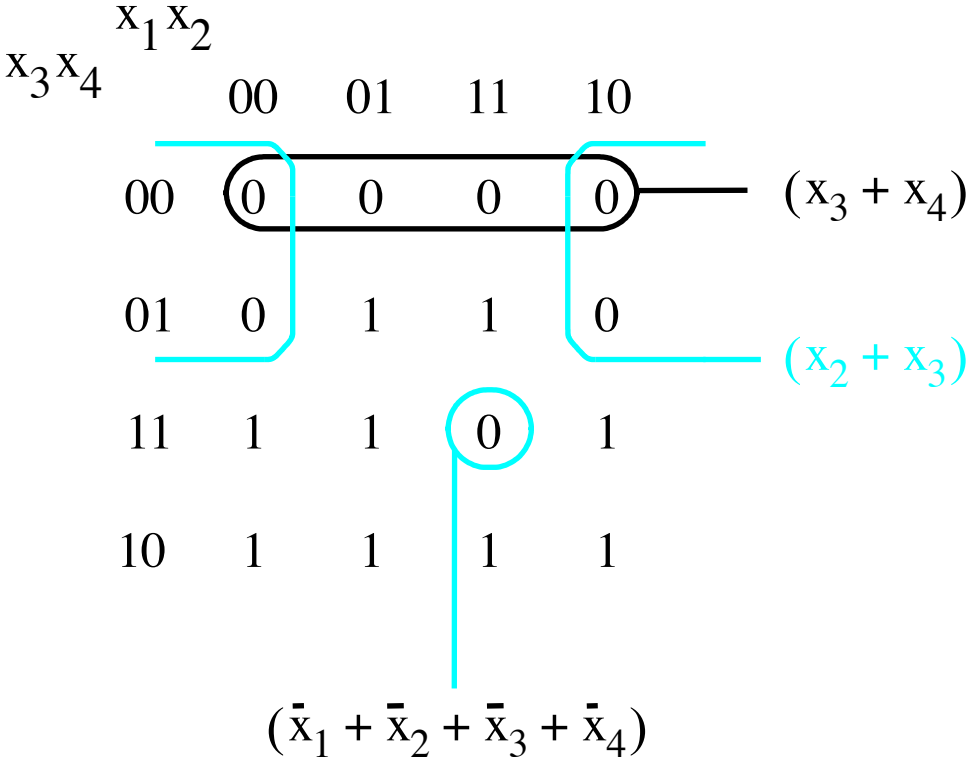POS minimization of $f(x_1, \dots, x_4) = \prod M(0, 1, 4, 8, 9, 12, 15)$



$$f(x_1, x_2, x_3, x_4) = (x_3 + x_4)(x_2 + x_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4)$$


[Figure 2.61 from the textbook]

**Example:
Incompletely Specified Function**

Three Ways to Specify the Function

$$f(x_1, x_2, x_3, x_4) = \Sigma m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

x_1	x_2	x_3	x_4	f
0	0	0	0	m_0
0	0	0	1	m_1
0	0	1	0	m_2
0	0	1	1	m_3
0	1	0	0	m_4
0	1	0	1	m_5
0	1	1	0	m_6
0	1	1	1	m_7
1	0	0	0	m_8
1	0	0	1	m_9
1	0	1	0	m_{10}
1	0	1	1	m_{11}
1	1	0	0	m_{12}
1	1	0	1	m_{13}
1	1	1	0	m_{14}
1	1	1	1	m_{15}

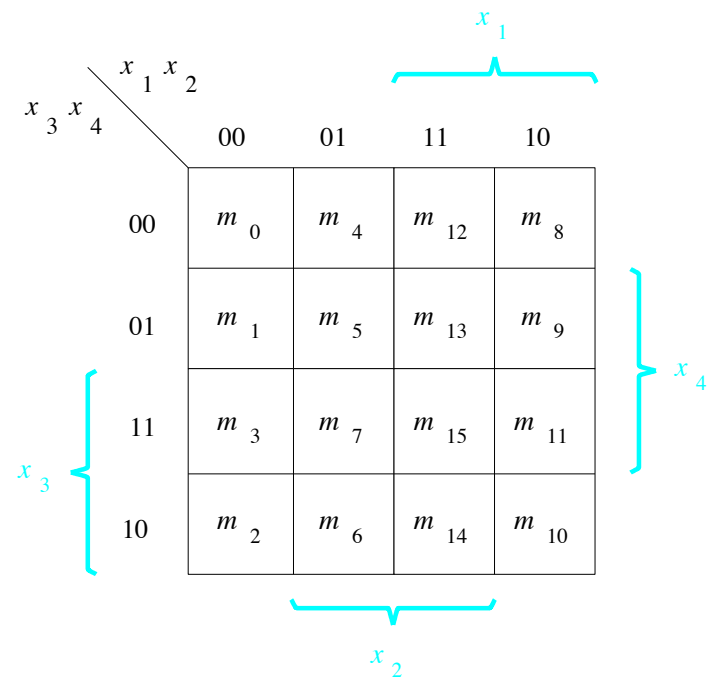

Three Ways to Specify the Function

$$f(x_1, x_2, x_3, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

x_1	x_2	x_3	x_4	f	
0	0	0	0	m_0	0
0	0	0	1	m_1	0
0	0	1	0	m_2	1
0	0	1	1	m_3	0
0	1	0	0	m_4	1
0	1	0	1	m_5	1
0	1	1	0	m_6	1
0	1	1	1	m_7	1
1	0	0	0	m_8	0
1	0	0	1	m_9	0
1	0	1	0	m_{10}	1
1	0	1	1	m_{11}	0
1	1	0	0	m_{12}	d
1	1	0	1	m_{13}	d
1	1	1	0	m_{14}	d
1	1	1	1	m_{15}	d

		$x_1 x_2$			
		00	01	11	10
$x_3 x_4$	00	0	1	d	0
	01	0	1	d	0
	11	0	0	d	0
	10	1	1	d	1


SOP implementation

A 4x4 Karnaugh map for variables x_1, x_2, x_3, x_4 . The columns are labeled $x_1 x_2$ with values 00, 01, 11, 10. The rows are labeled $x_3 x_4$ with values 00, 01, 11, 10. The map contains 1s at (01, 00), (01, 01), and (10, 00), (10, 01), (10, 10). Don't care terms (d) are at (11, 00), (11, 01), and (11, 10). Two prime implicants are circled in cyan: a vertical one covering (01, 00) and (01, 01) labeled $x_2 \bar{x}_3$, and a horizontal one covering (10, 00), (10, 01), (10, 10) labeled $x_3 \bar{x}_4$.

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00	0	1	d	0
01	0	1	d	0
11	0	0	d	0
10	1	1	d	1

(a) SOP implementation


POS implementation

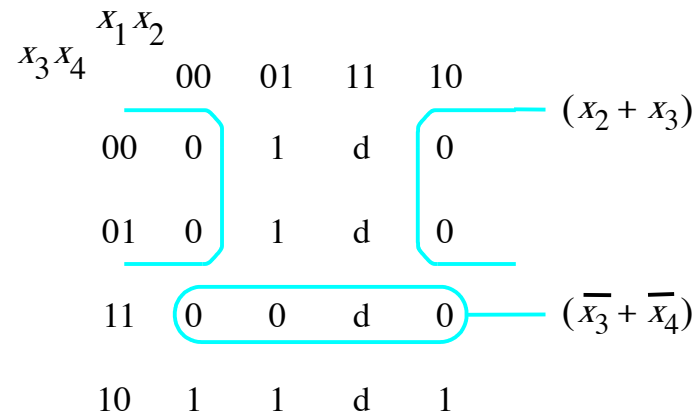

(b) POS implementation


Example:
A circuit with multiple outputs

Seven-Segment Indicator

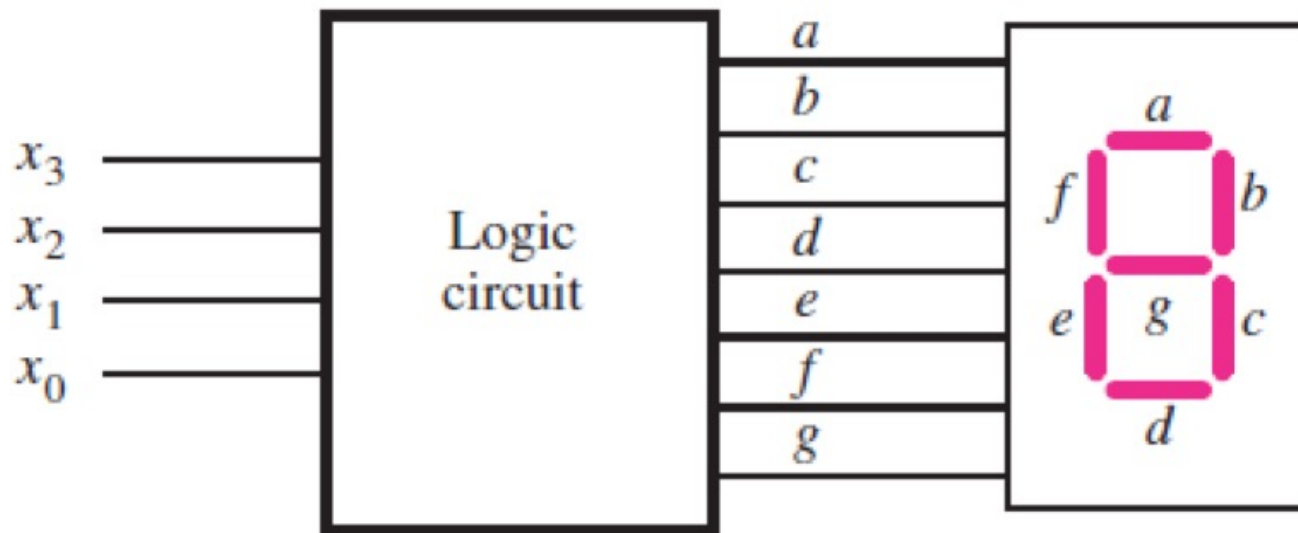

(a) Logic circuit and 7-segment display

Seven-Segment Indicator

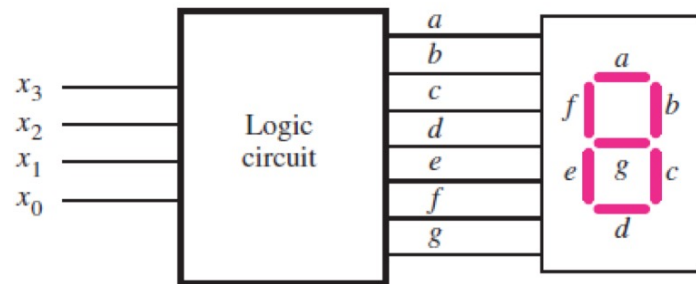

(a) Logic circuit and 7-segment display

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

(b) Truth table

Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
10	1	0	1	0							
11	1	0	1	1							
12	1	1	0	0							
13	1	1	0	1							
14	1	1	1	0							
15	1	1	1	1							

Seven-Segment Indicator



	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0000-1000	0	0	0	0	1	1	1	1	1	1	0
	0	0	0	1	0	1	1	0	0	0	0
	0	0	1	0	1	1	0	1	1	0	1
	0	0	1	1	1	1	1	1	0	0	1
	0	1	0	0	0	1	1	0	0	1	1
	0	1	0	1	1	0	1	1	0	1	1
	0	1	1	0	1	0	1	1	1	1	1
	0	1	1	1	1	1	1	0	0	0	0
	1	0	0	0	1	1	1	1	1	1	1
	1	0	0	1	1	1	1	1	0	1	1
	1	0	1	0	d	d	d	d	d	d	d
	1	0	1	1	d	d	d	d	d	d	d
	1	1	0	0	d	d	d	d	d	d	d
	1	1	0	1	d	d	d	d	d	d	d
	1	1	1	0	d	d	d	d	d	d	d
	1	1	1	1	d	d	d	d	d	d	d

Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	d	d	d	d	d	d	d
1011	1	0	1	1	d	d	d	d	d	d	d
1100	1	1	0	0	d	d	d	d	d	d	d
1101	1	1	0	1	d	d	d	d	d	d	d
1110	1	1	1	0	d	d	d	d	d	d	d
1111	1	1	1	1	d	d	d	d	d	d	d



Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	d	d	d	d	d	d	d
1011	1	0	1	1	d	d	d	d	d	d	d
1100	1	1	0	0	d	d	d	d	d	d	d
1101	1	1	0	1	d	d	d	d	d	d	d
1110	1	1	1	0	d	d	d	d	d	d	d
1111	1	1	1	1	d	d	d	d	d	d	d

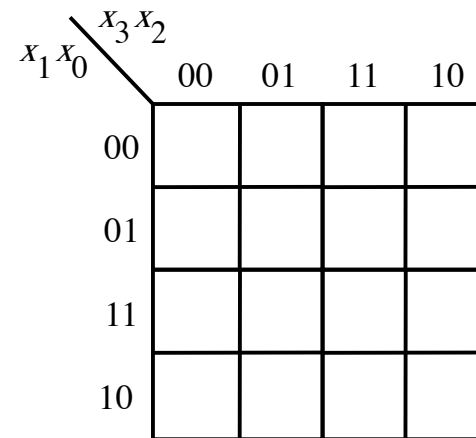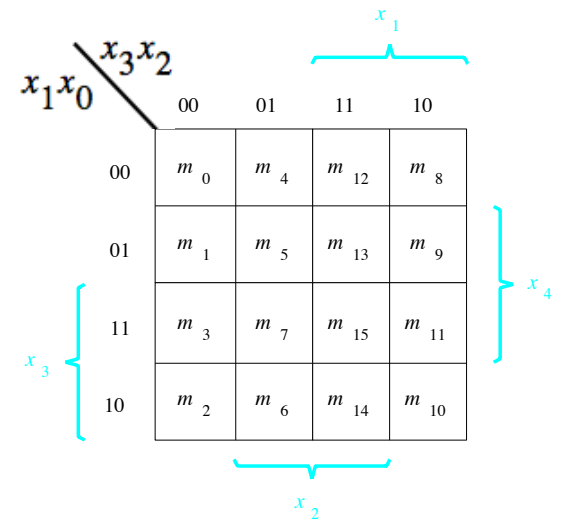

Seven-Segment Indicator



	x_3	x_2	x_1	x_0	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	d	d	d	d	d	d	d
1011	1	0	1	1	d	d	d	d	d	d	d
1100	1	1	0	0	d	d	d	d	d	d	d
1101	1	1	0	1	d	d	d	d	d	d	d
1110	1	1	1	0	d	d	d	d	d	d	d
1111	1	1	1	1	d	d	d	d	d	d	d

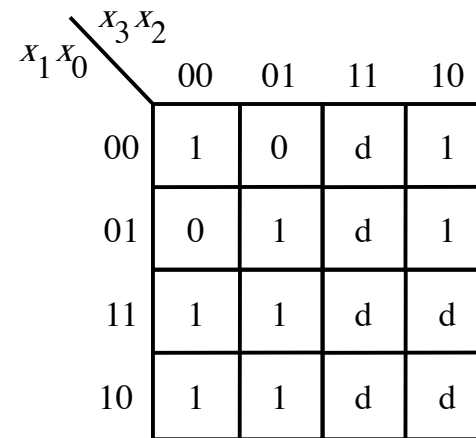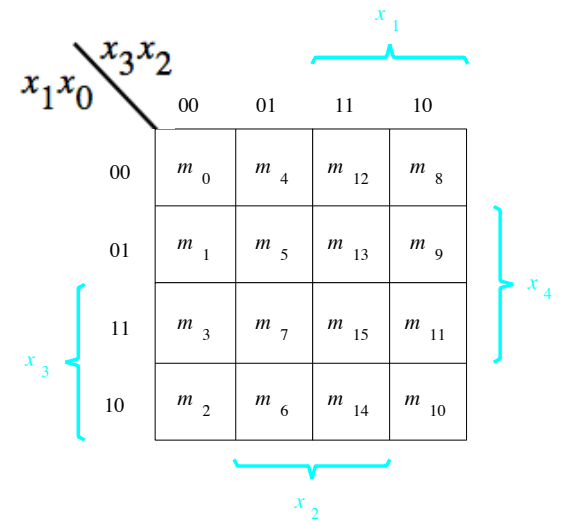

Seven-Segment Indicator



x_3	x_2	x_1	x_0	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	d	d	d	d	d	d	d
1	0	1	1	d	d	d	d	d	d	d
1	1	0	0	d	d	d	d	d	d	d
1	1	0	1	d	d	d	d	d	d	d
1	1	1	0	d	d	d	d	d	d	d
1	1	1	1	d	d	d	d	d	d	d

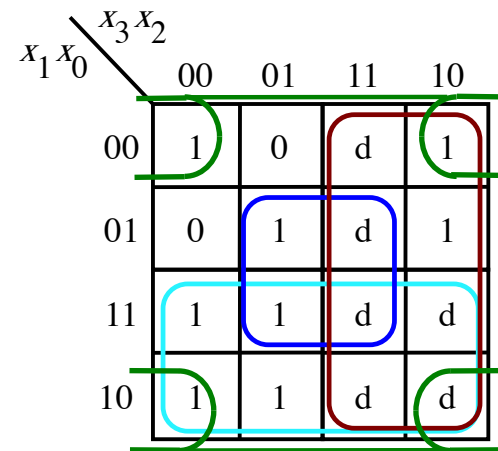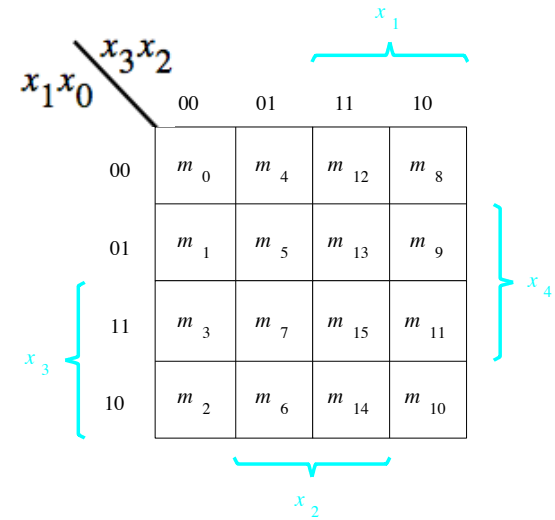0000 0001 0010 0011 0100 0101 0110 0111 1000 1001



Seven-Segment Indicator

x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	d	d	d	d	d	d
1	0	1	1	1	d	d	d	d	d	d
1	1	0	0	1	d	d	d	d	d	d
1	1	0	1	1	d	d	d	d	d	d
1	1	1	0	1	d	d	d	d	d	d
1	1	1	1	1	d	d	d	d	d	d

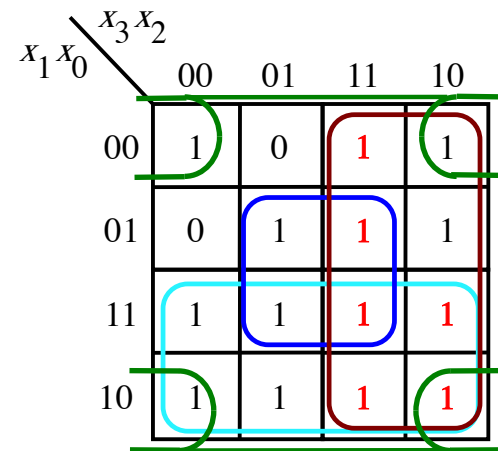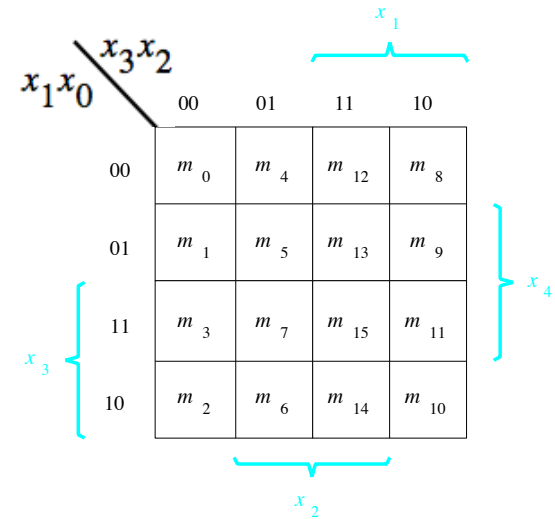



In this case all d's were treated as 1's.

Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	1	d	d	d	d	d	d
1011	1	0	1	1	1	d	d	d	d	d	d
1100	1	1	0	0	1	d	d	d	d	d	d
1101	1	1	0	1	1	d	d	d	d	d	d
1110	1	1	1	0	1	d	d	d	d	d	d
1111	1	1	1	1	1	d	d	d	d	d	d



Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	1	d	d	d	d	d	d
1011	1	0	1	1	1	d	d	d	d	d	d
1100	1	1	0	0	1	d	d	d	d	d	d
1101	1	1	0	1	1	d	d	d	d	d	d
1110	1	1	1	0	1	d	d	d	d	d	d
1111	1	1	1	1	1	d	d	d	d	d	d

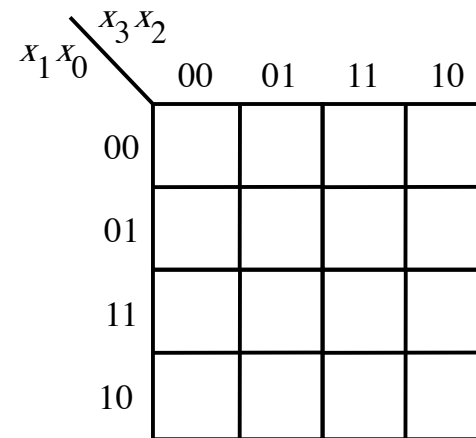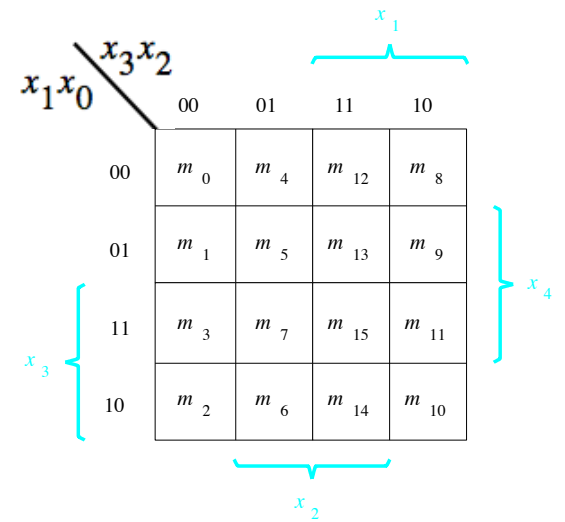



Seven-Segment Indicator

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	1	d	d	d	d	d	d
1011	1	0	1	1	1	d	d	d	d	d	d
1100	1	1	0	0	1	d	d	d	d	d	d
1101	1	1	0	1	1	d	d	d	d	d	d
1110	1	1	1	0	1	d	d	d	d	d	d
1111	1	1	1	1	1	d	d	d	d	d	d

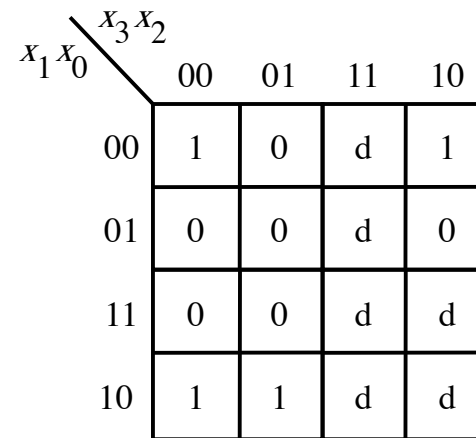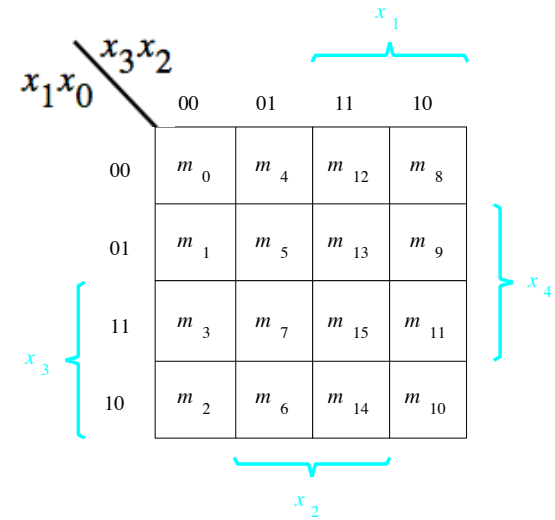

Seven-Segment Indicator


	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	1	d	d	d	d	d	d
1011	1	0	1	1	1	d	d	d	d	d	d
1100	1	1	0	0	1	d	d	d	d	d	d
1101	1	1	0	1	1	d	d	d	d	d	d
1110	1	1	1	0	1	d	d	d	d	d	d
1111	1	1	1	1	1	d	d	d	d	d	d

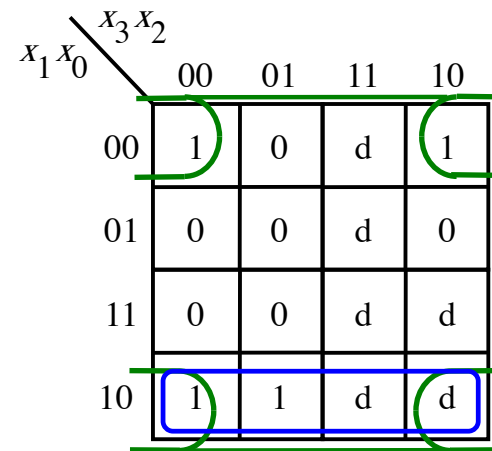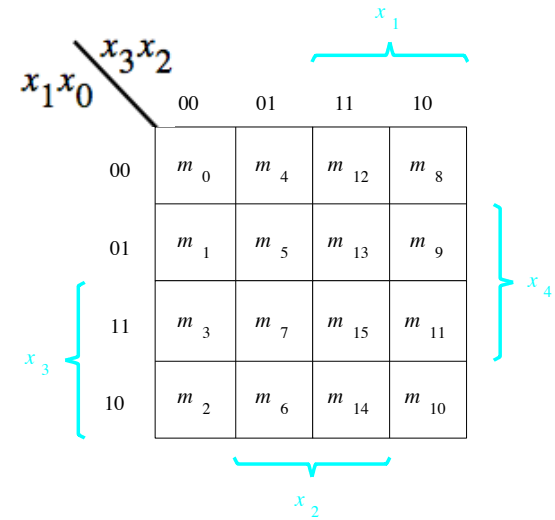

Seven-Segment Indicator


	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

(b) Truth table

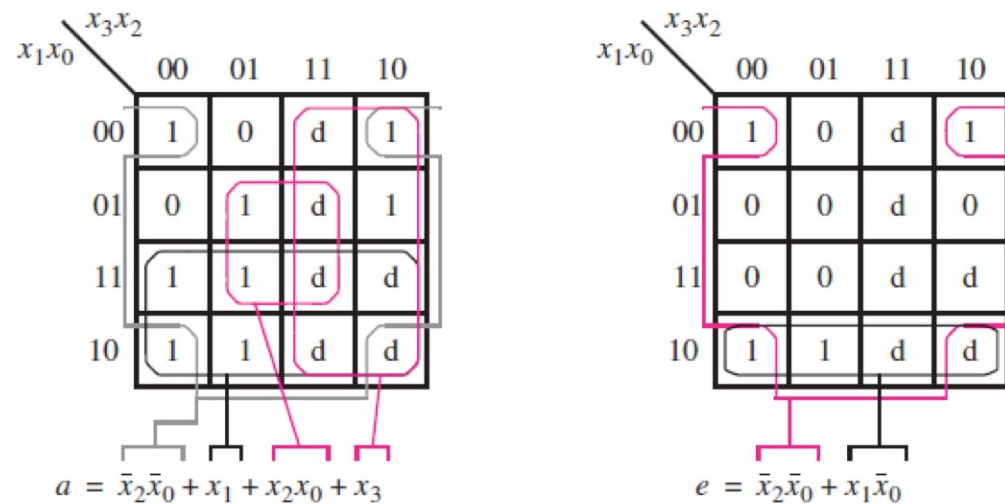


(c) The Karnaugh maps for outputs a and e .

Another Example

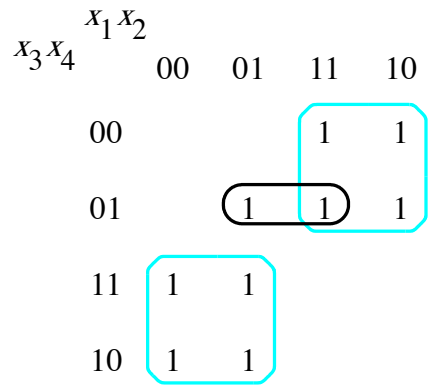

(a) Function f_1

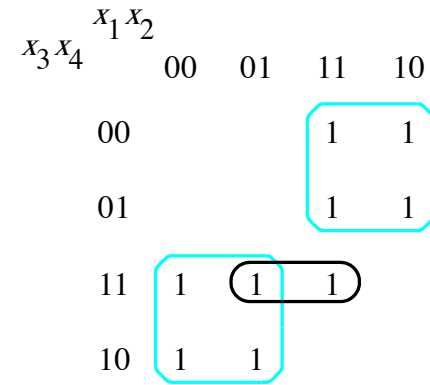

(b) Function f_2

$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function f_1

$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01			1	1
11	1	1		
10	1	1		

(b) Function f_2


$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function f_1

$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01			1	1
11	1	1		
10	1	1		

(b) Function f_2

$\bar{x}_1 x_3$

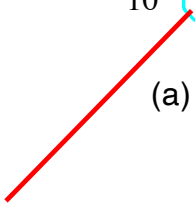

$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function f_1

$$\overline{X_1} X_3$$

$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01			1	1
11	1	1		
10	1	1		

(b) Function f_2

$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function f_1

$$\overline{X_1} X_3$$

$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01			1	1
11	1	1		
10	1	1		

(b) Function f_2

$$\overline{X_1} X_3$$

$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		


(a) Function f_1

$$\overline{X_1} X_3$$


$x_3 x_4$	$x_1 x_2$			
	00	01	11	10
00			1	1
01			1	1
11	1	1		
10	1	1		



(b) Function f_2


$$\overline{X_1} X_3$$



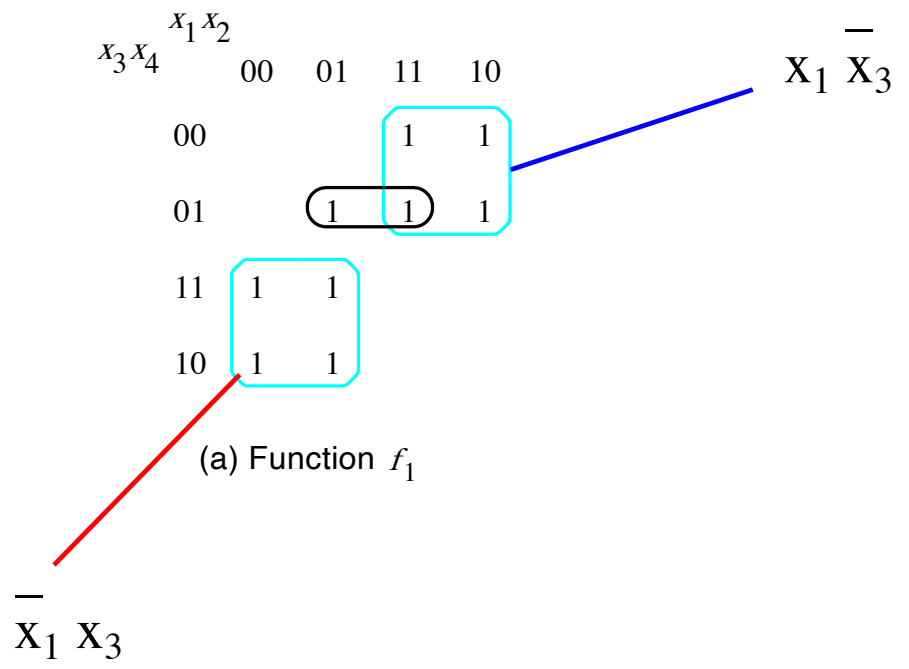


$X_1 \bar{X}_3$


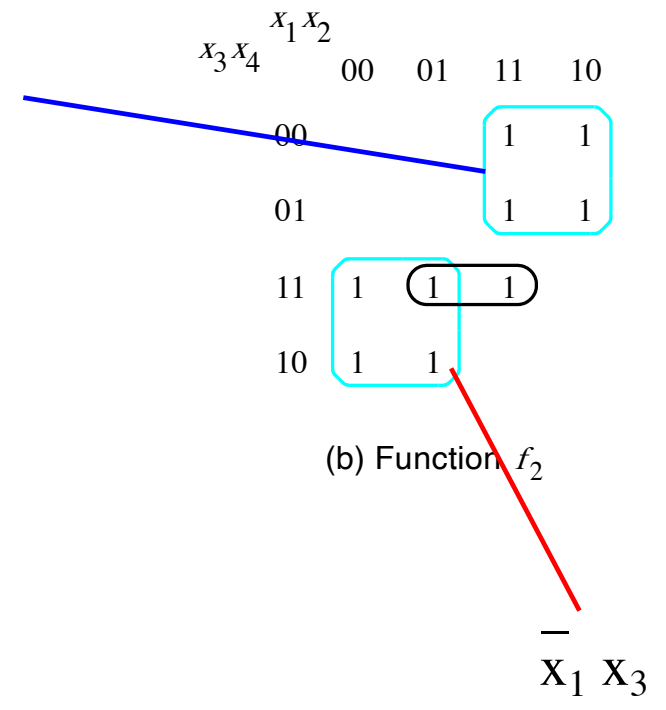


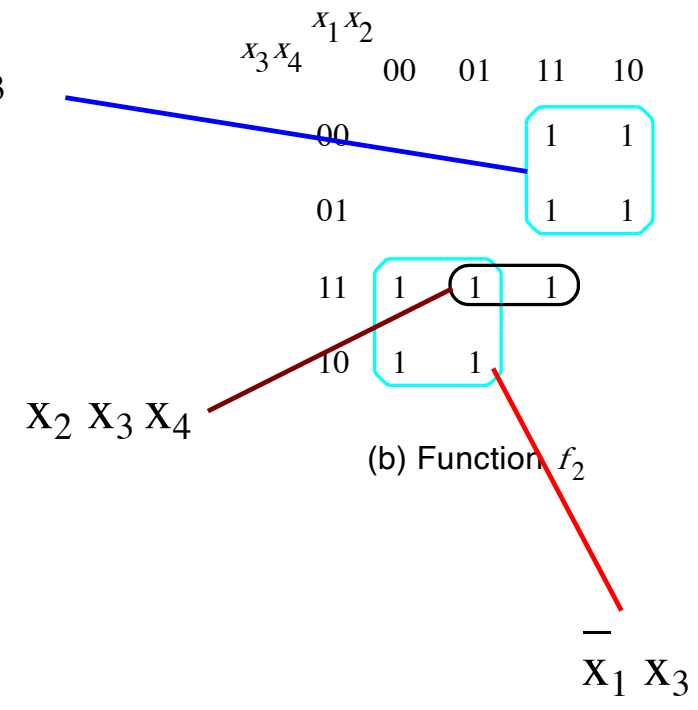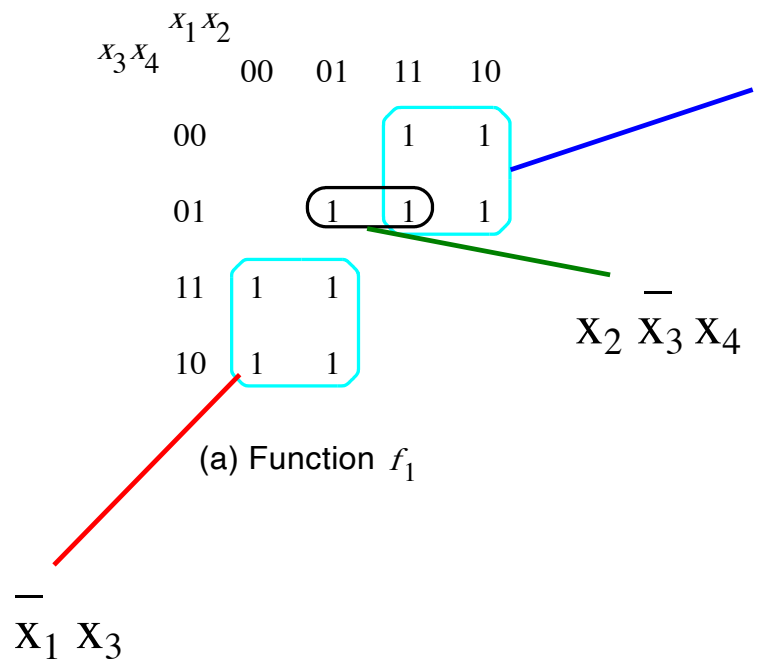


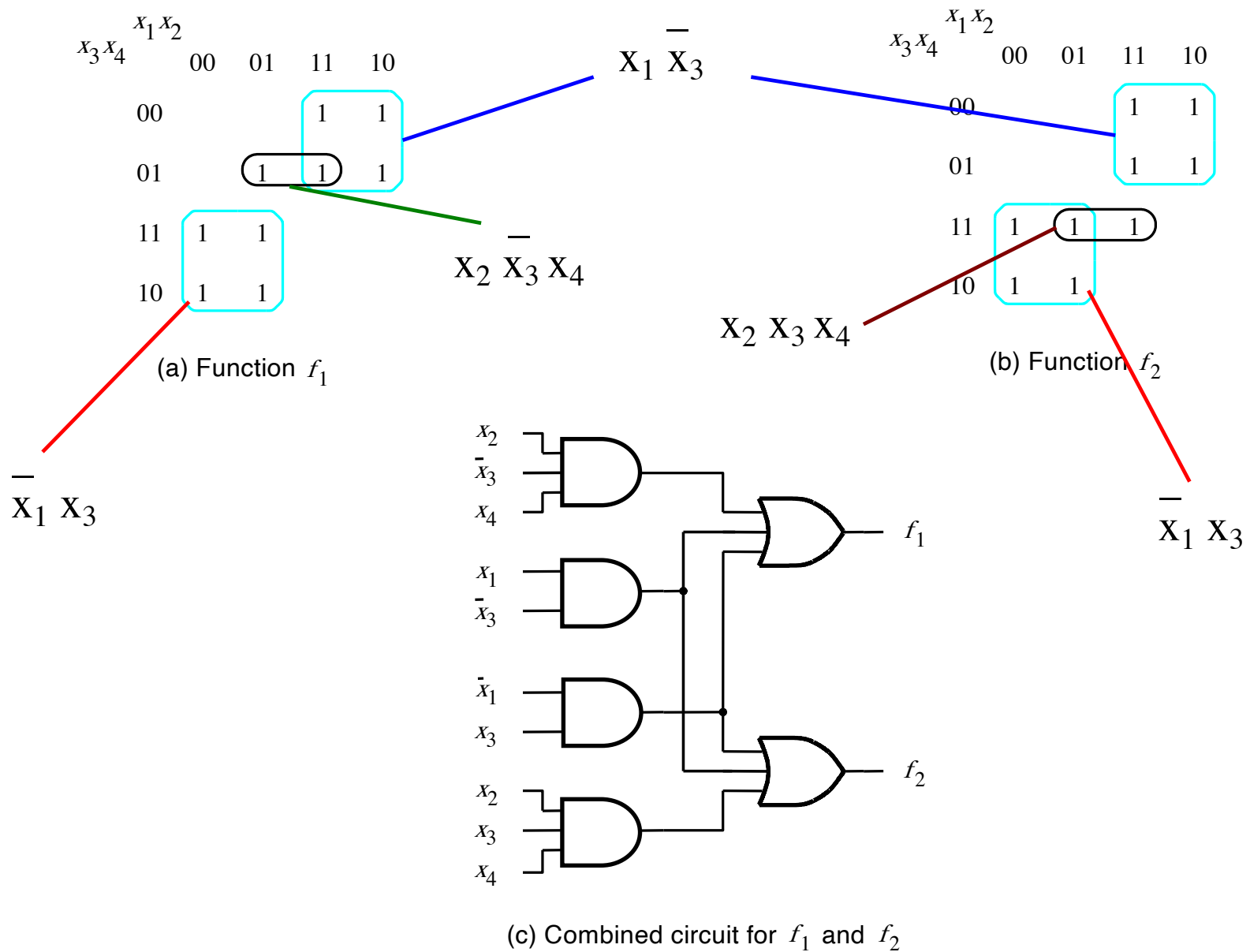


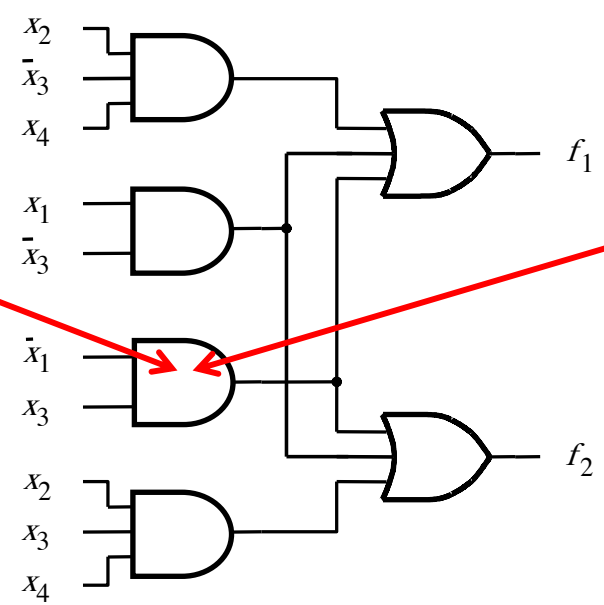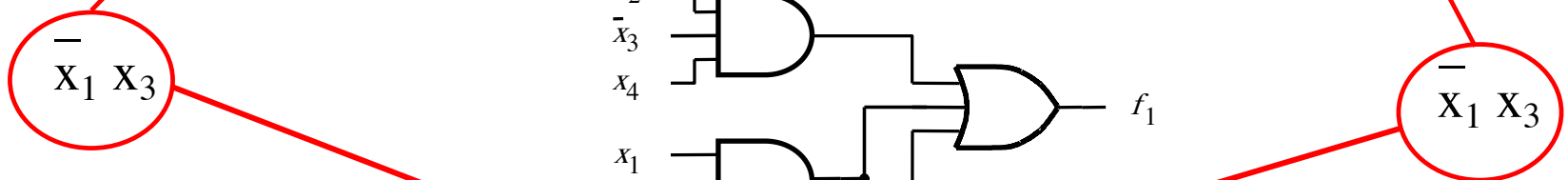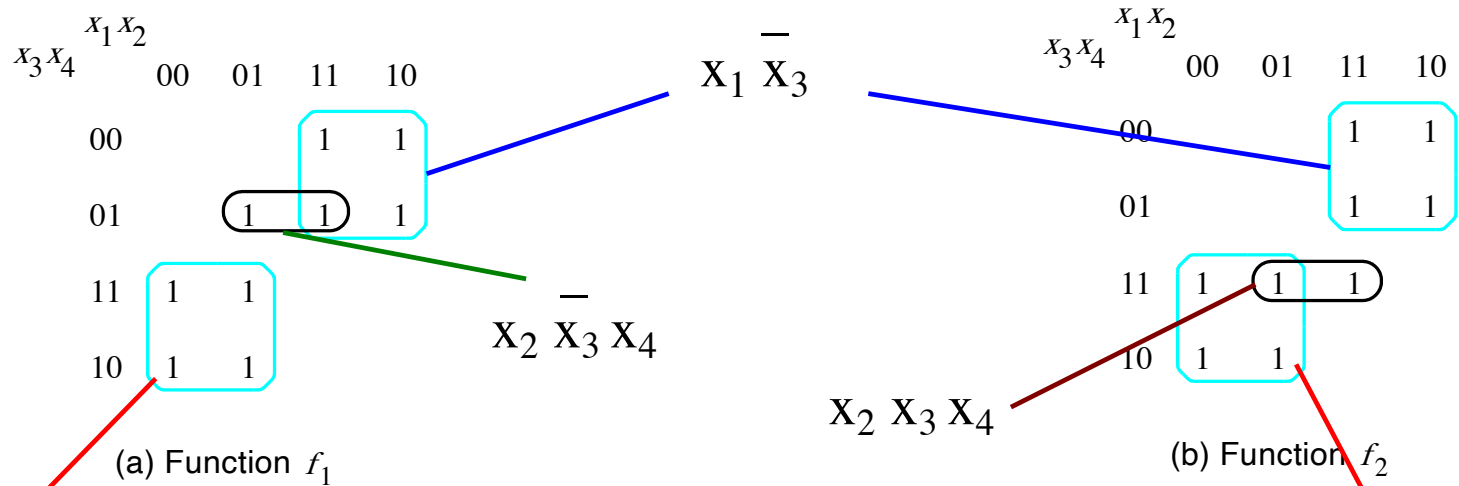



(c) Combined circuit for f_1 and f_2

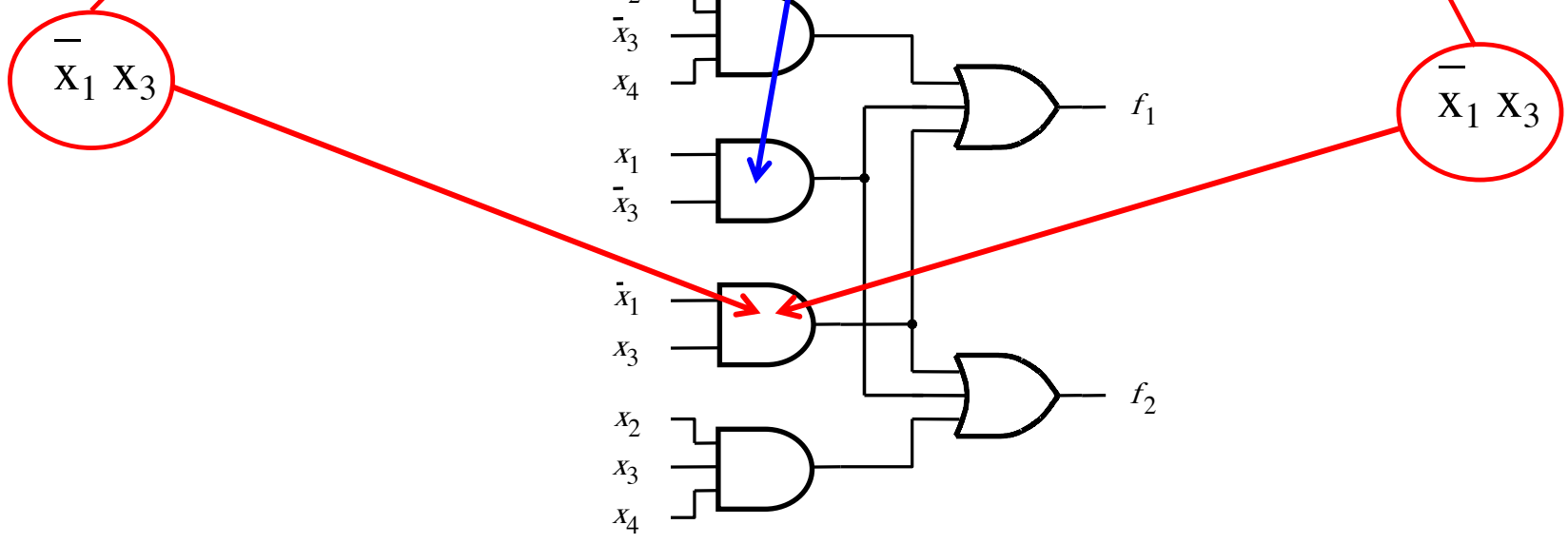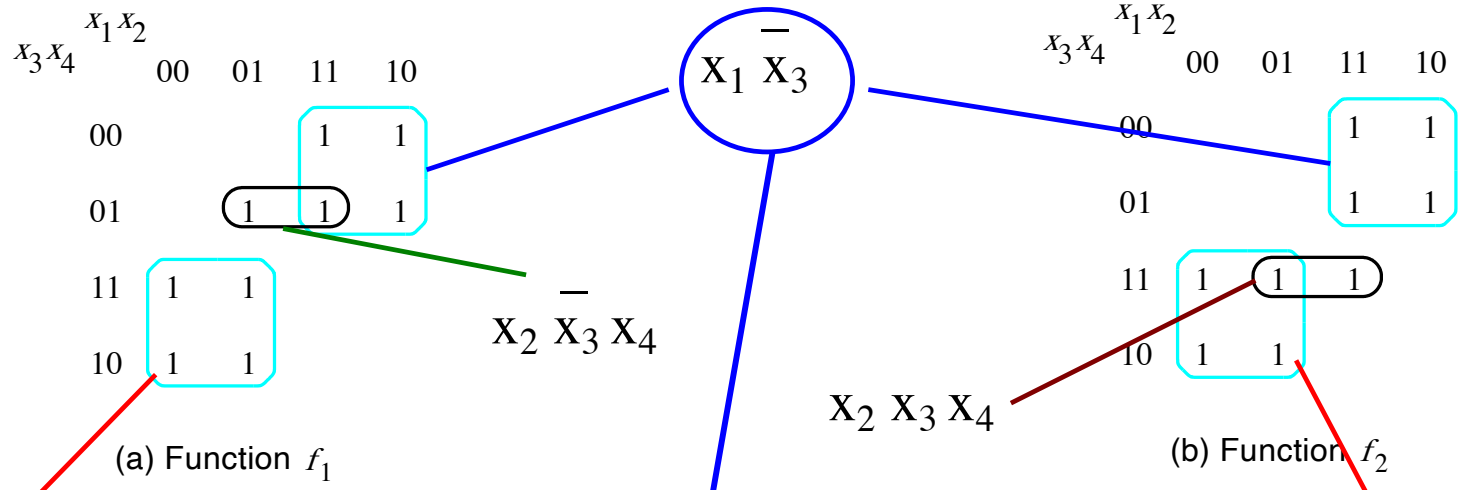

(c) Combined circuit for f_1 and f_2

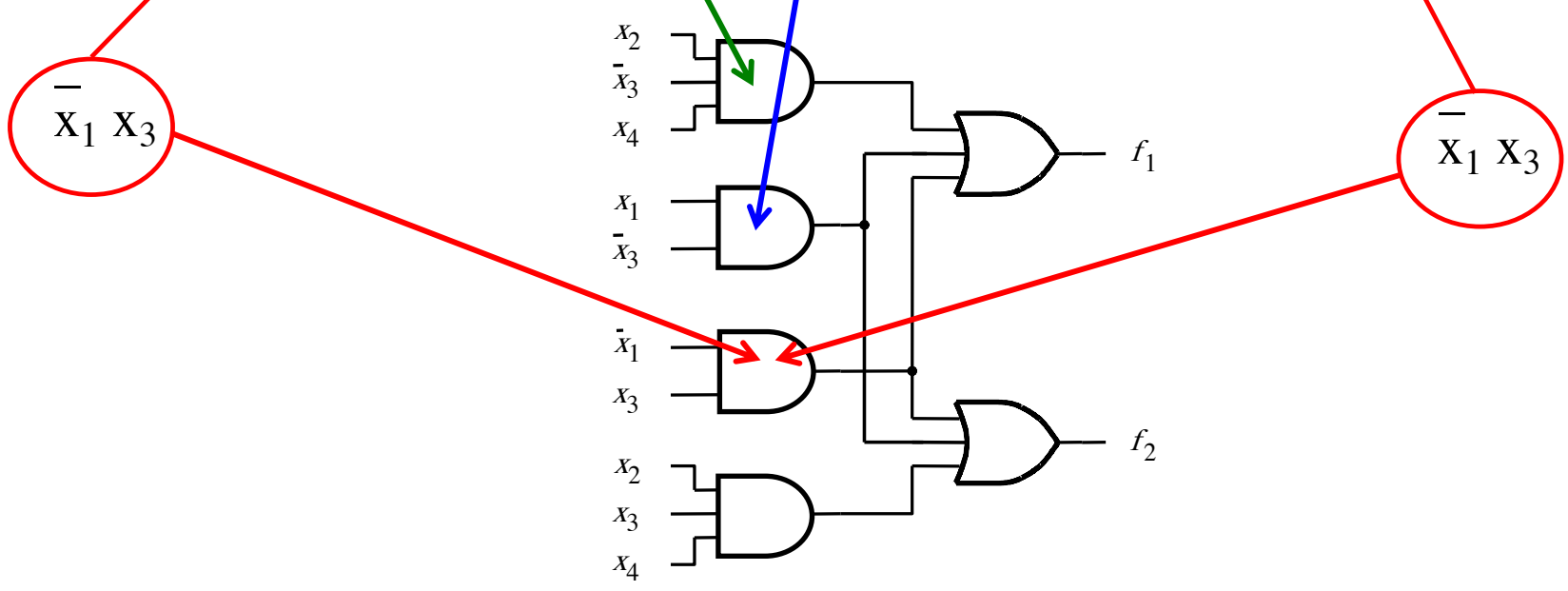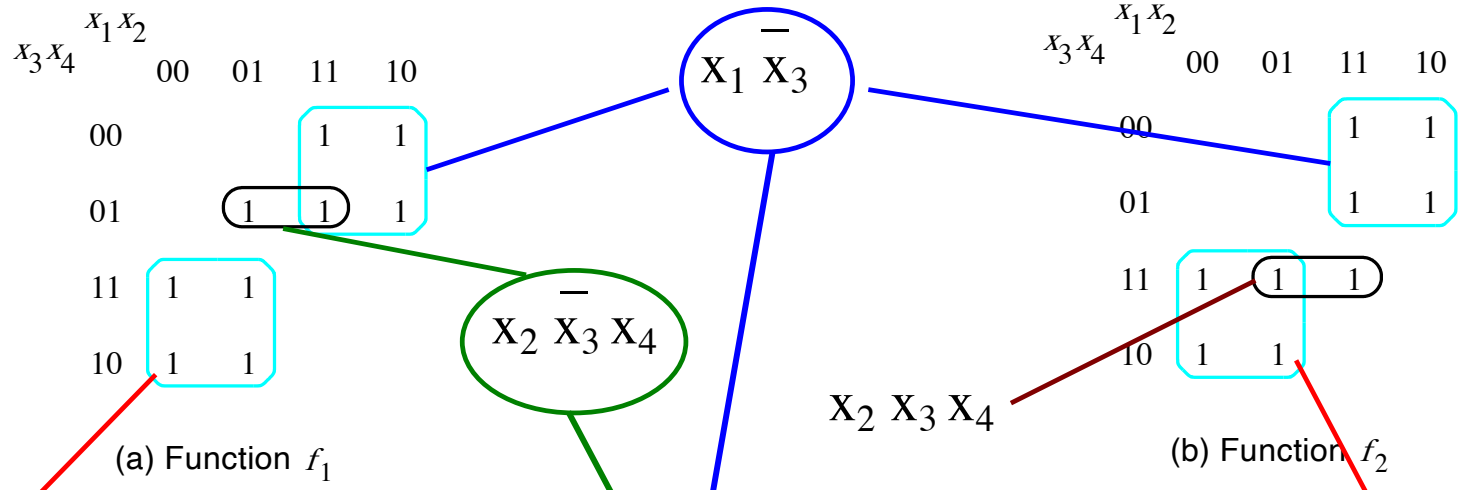

(c) Combined circuit for f_1 and f_2

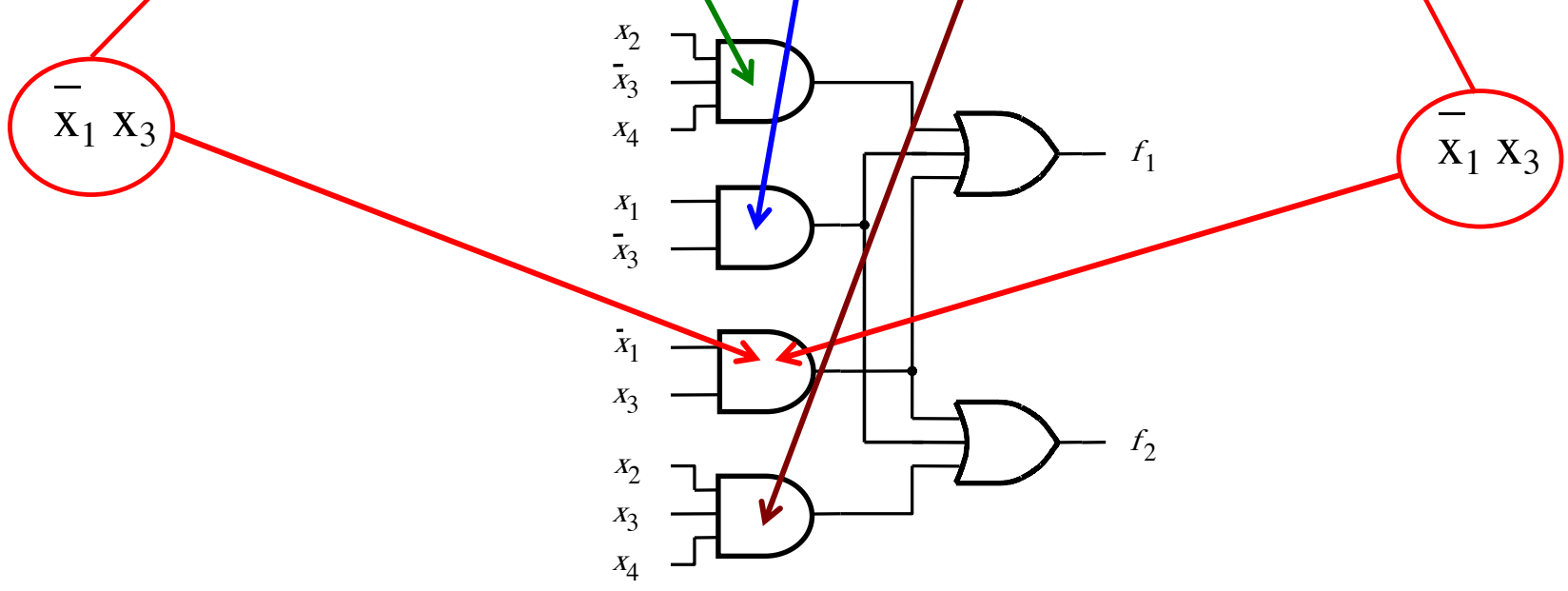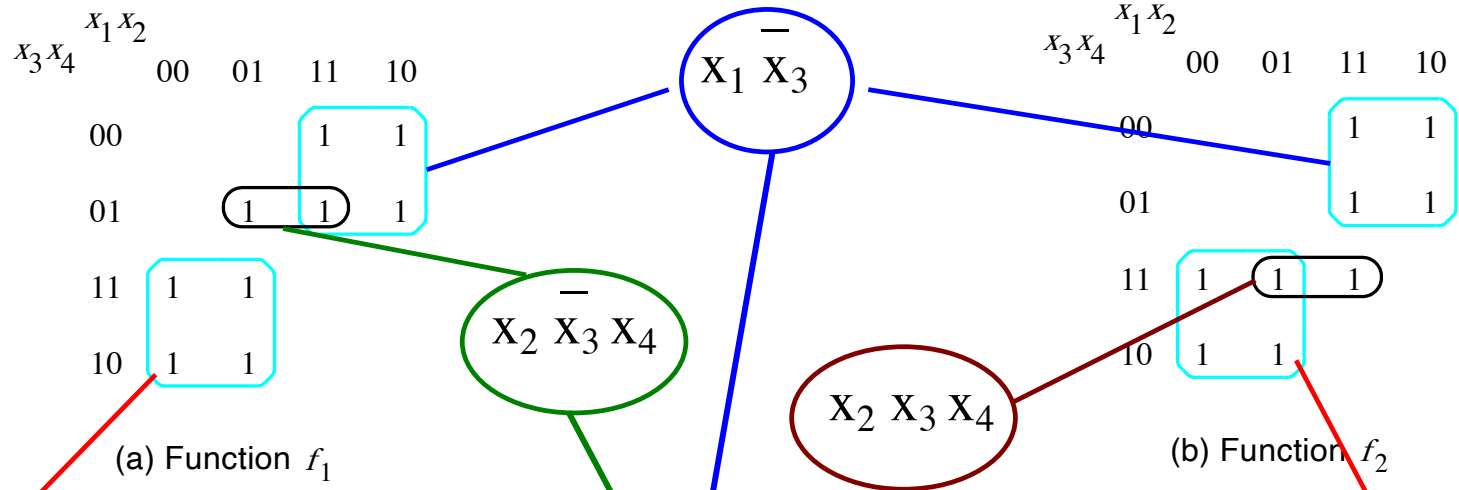


(c) Combined circuit for f_1 and f_2

x_3x_4	x_1x_2			
	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function f_1

x_3x_4	x_1x_2			
	00	01	11	10
00			1	1
01			1	1
11	1	1		
10	1	1		

(b) Function f_2

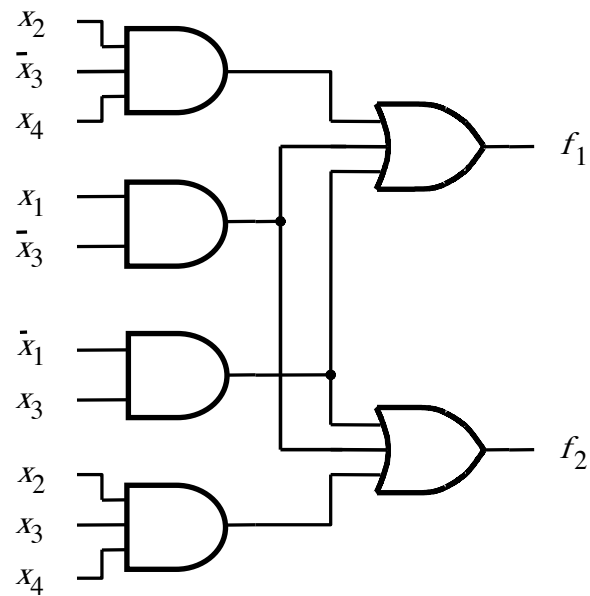

(c) Combined circuit for f_1 and f_2

[Figure 2.64 from the textbook]

Individual vs Joint Optimization


Individual Optimization

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00				
01	1	1	1	
11	1	1	1	
10		1		


(a) Optimal realization of f_3

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00				
01	1		1	1
11	1		1	1
10		1		

(b) Optimal realization of f_4

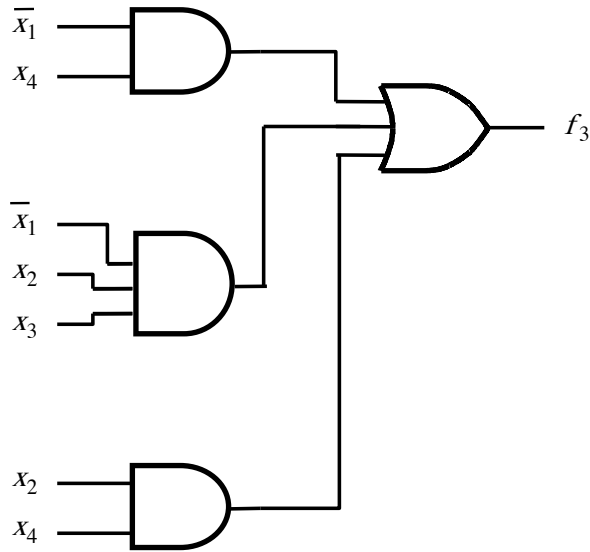


Circuit only for f_3

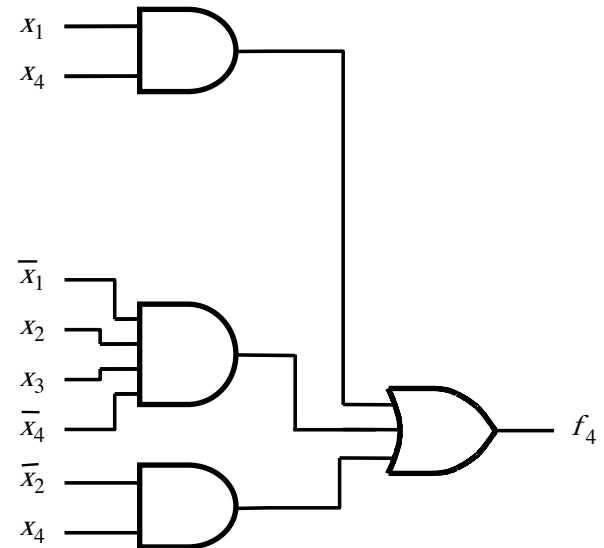


Circuit only for f_4


Individual Optimization

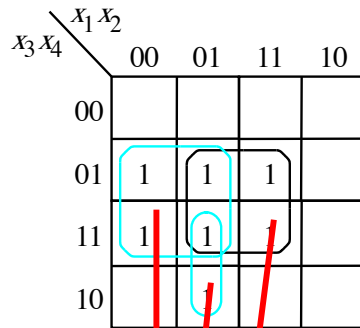


(a) Optimal realization of f_3

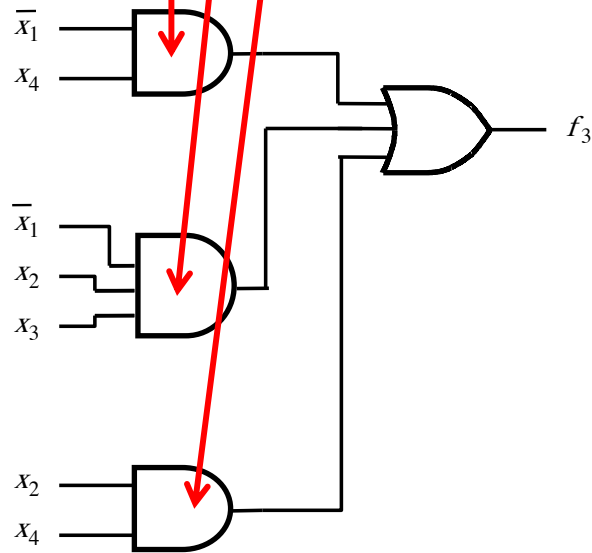

Circuit only for f_3

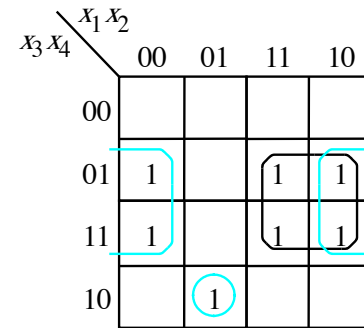

(b) Optimal realization of f_4

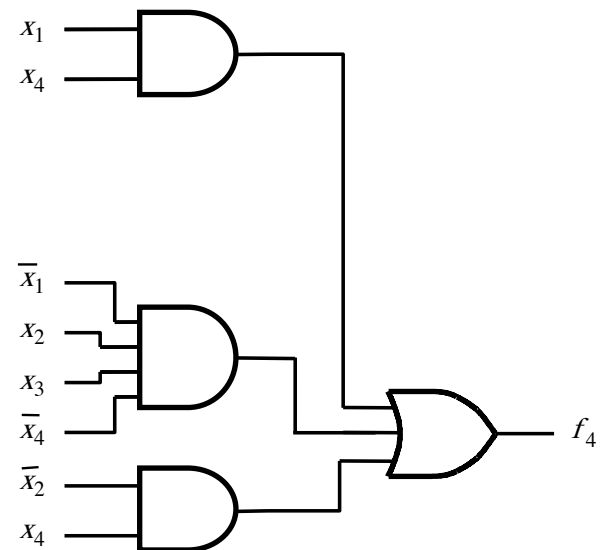


Circuit only for f_4

Individual Optimization

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00				
01	1	1	1	
11	1	1	1	
10		1		


(a) Optimal realization of f_3

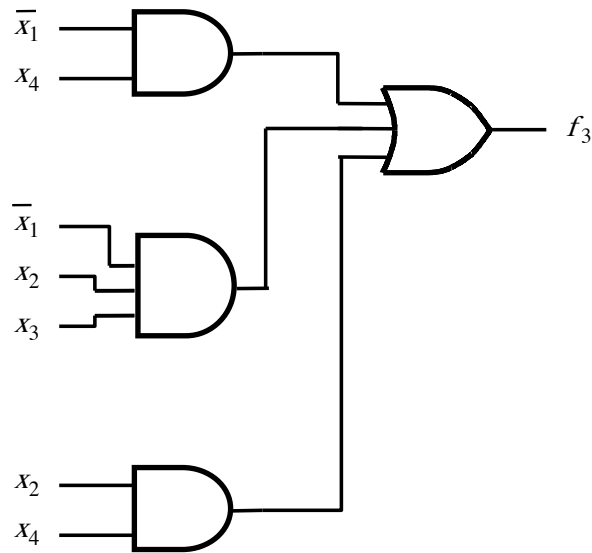

Circuit only for f_3

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00				
01	1		1	1
11	1		1	1
10		1		

(b) Optimal realization of f_4

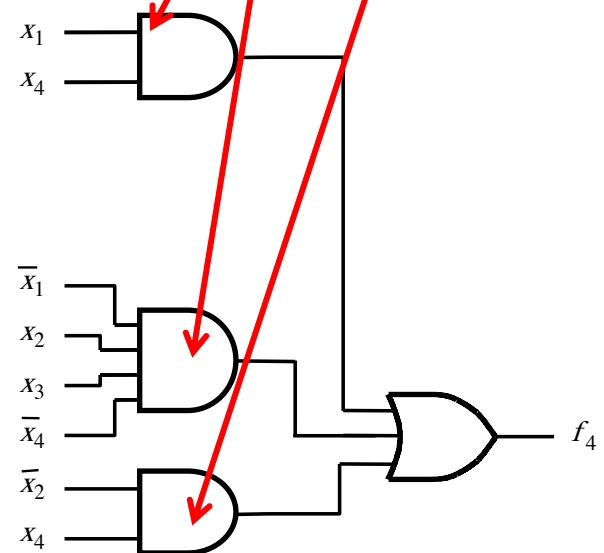

Circuit only for f_4


Individual Optimization

	$x_1 x_2$			
$x_3 x_4$	00	01	11	10
00				
01	1	1	1	
11	1	1	1	
10		1		

(a) Optimal realization of f_3


	$x_1 x_2$			
$x_3 x_4$	00	01	11	10
00				
01	1		1	1
11	1		1	1
10		1		

(b) Optimal realization of f_4

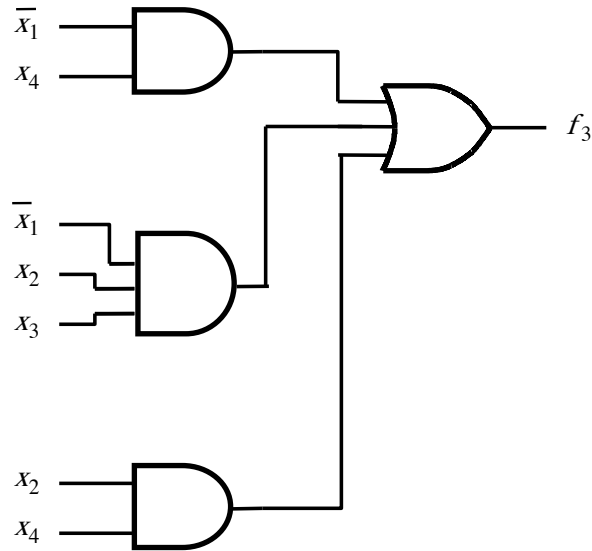

cost = 14

Circuit only for f_3

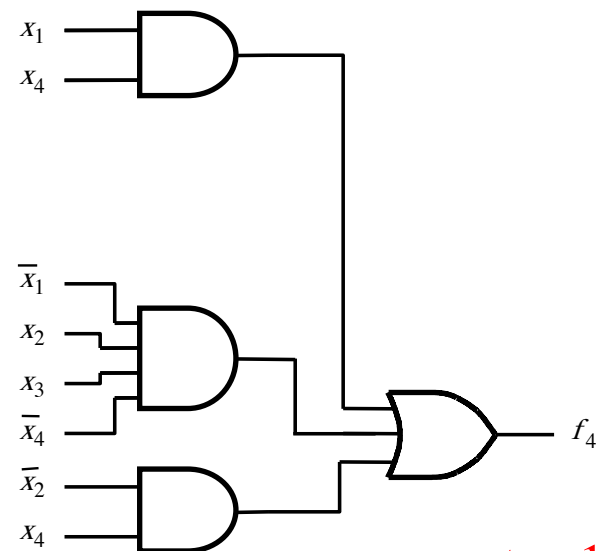

cost = 15

Circuit only for f_4


Individual Optimization

	$x_1 x_2$			
$x_3 x_4$	00	01	11	10
00				
01	1	1	1	
11	1	1	1	
10		1		

(a) Optimal realization of f_3


	$x_1 x_2$			
$x_3 x_4$	00	01	11	10
00				
01	1		1	1
11	1		1	1
10		1		

(b) Optimal realization of f_4

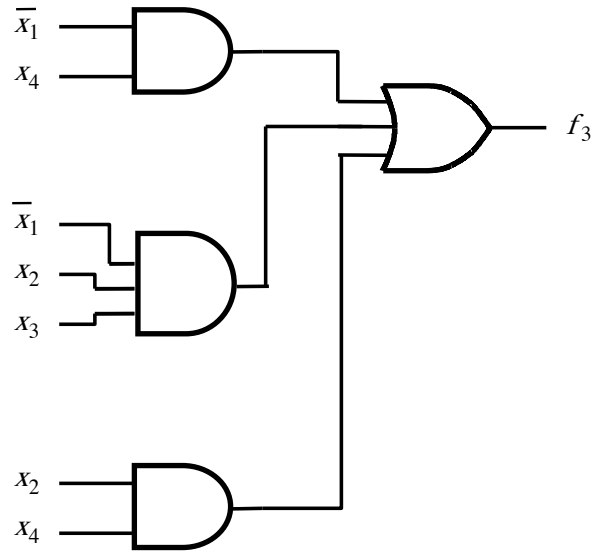

cost = 14

Circuit only for f_3

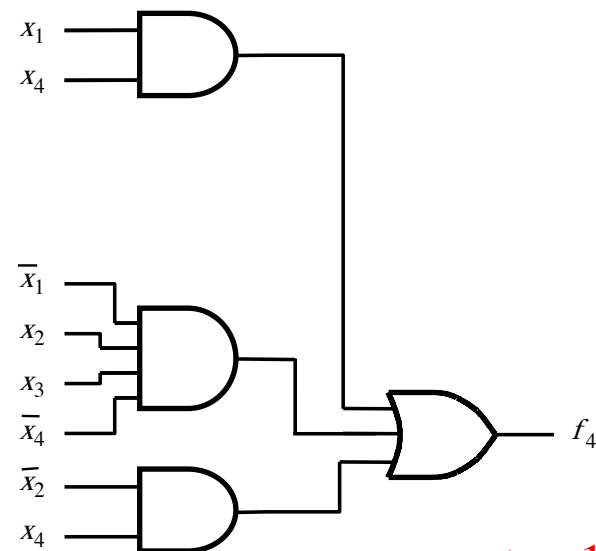


cost = 15

Circuit only for f_4


TOTAL cost: 29

Individual vs Joint Optimization

Individual

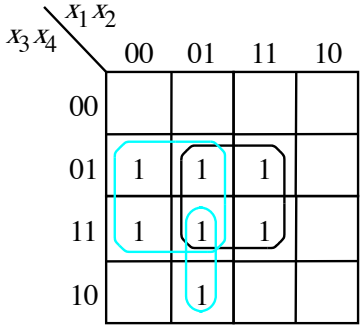


(a) Optimal realization of f_3

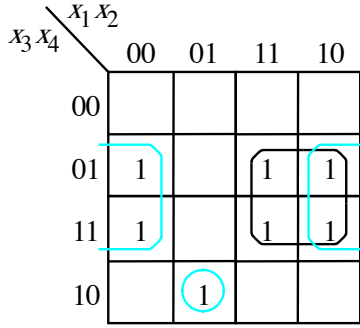

(b) Optimal realization of f_4


Joint

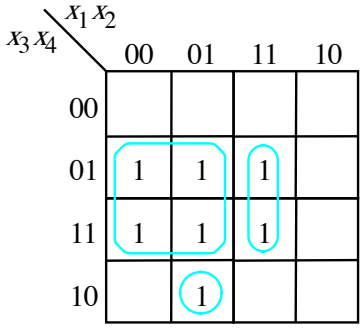


(c) Optimal realization of f_3 and f_4 together

[Figure 2.65 from the textbook]

Joint Optimization

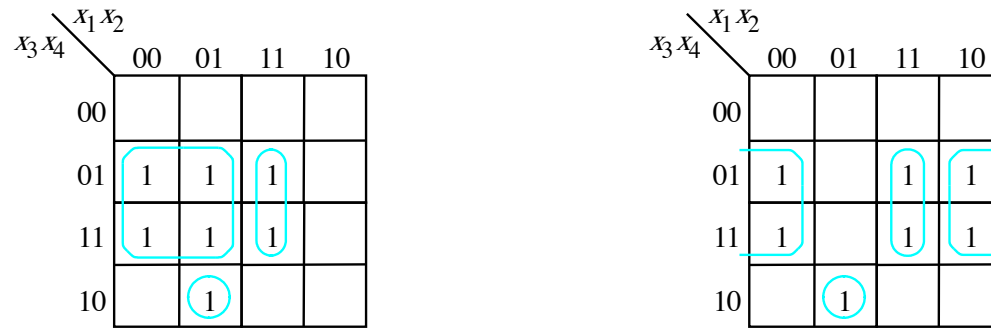


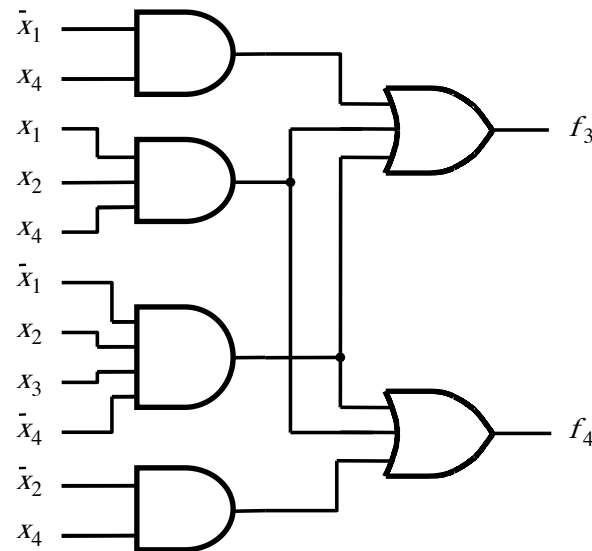(c) Optimal realization of f_3 and f_4 together




(d) Combined circuit for f_3 and f_4

Joint Optimization

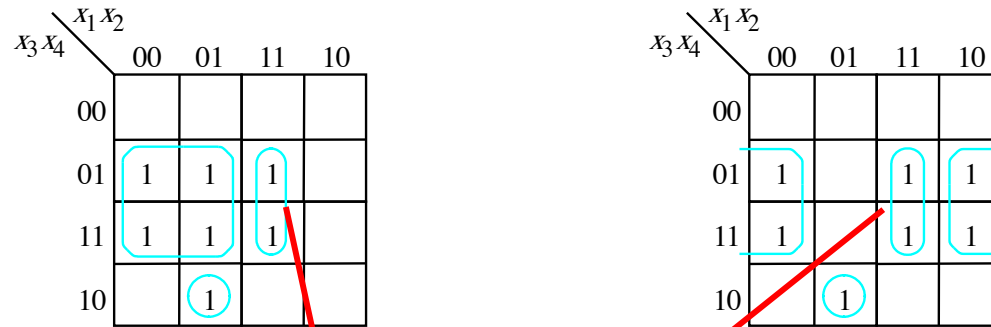

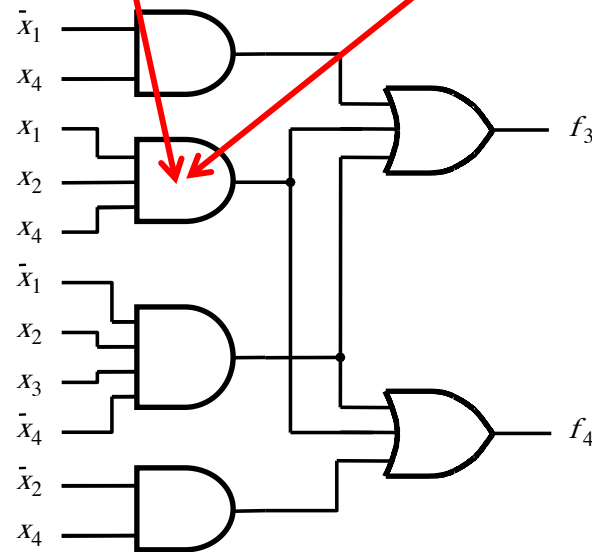
(c) Optimal realization of f_3 and f_4 together




shared gate

(d) Combined circuit for f_3 and f_4

Joint Optimization

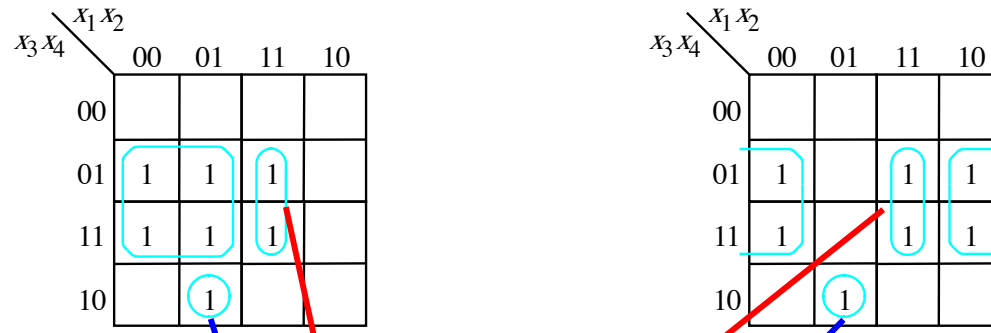

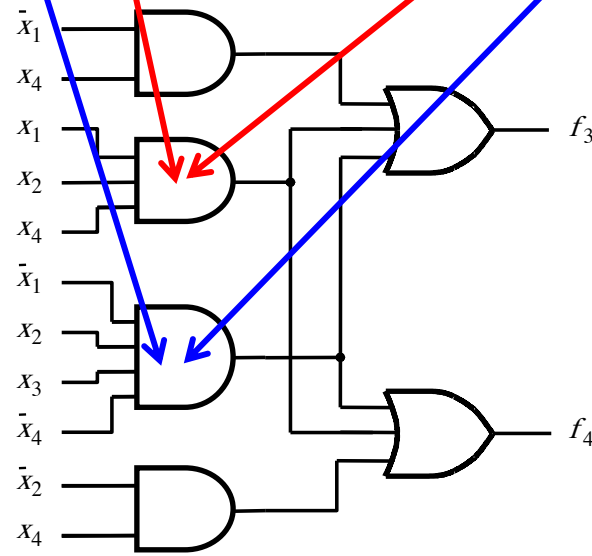
(c) Optimal realization of f_3 and f_4 together




another shared gate

(d) Combined circuit for f_3 and f_4

Joint Optimization

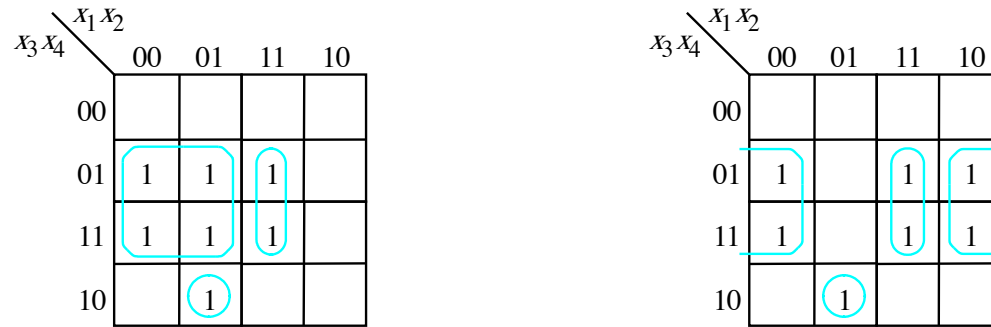

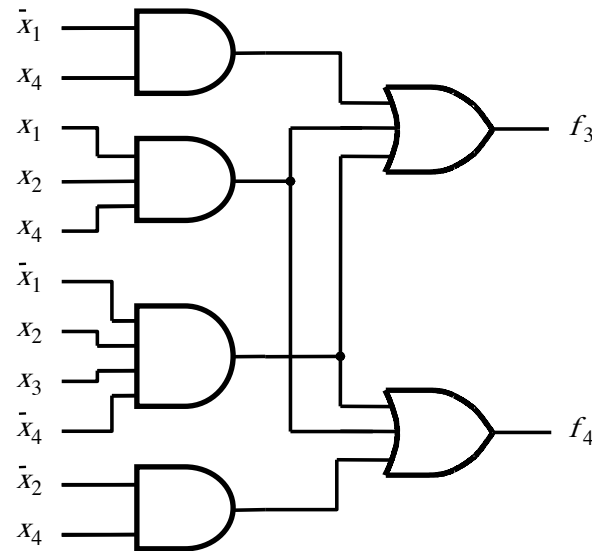(c) Optimal realization of f_3 and f_4 together



(d) Combined circuit for f_3 and f_4

cost = 23

Questions?

THE END