


CprE / ComS 583 Reconfigurable Computing

Prof. Joseph Zambreno
Department of Electrical and Computer Engineering
Iowa State University

Lecture #3 – FPGA Basics

Quick Points

 - HW #1 is out
 - Due Thursday, September 7 (12pm)
 - Submission via WebCT
- Possible strategies



August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.2

Recap

- FPGAs – spatial computation
- CPU – temporal computation
- FPGAs are by their nature more computationally “dense” than CPU
 - In terms of number of computations / time / area
 - Can be quantitatively measured and compared
- Capacity, cost, ease of programming still important issues
- Numerous challenges to reconfiguration

August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.3

Outline

- Recap
- FPGA Taxonomy
- Lookup Tables and Digital Logic
- Interconnect / Routing Structures
- FPGA Architectural Issues

August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.4


FPGA Taxonomy

- *Programming technology* – how is the FPGA programmed? Where does it store configuration bits?
 - SRAM
 - Anti-fuse
 - EPROM
 - Flash memory (EEPROM)
- *Logic cell architecture* – what is the granularity of configurable component? Tradeoff between complexity and versatility
 - Transistors
 - Gates
 - PAL/PLAs
 - LUTs
 - CPUs
- *Interconnect architecture* – how do the logic cells communicate?
 - Tiled
 - Hierarchical
 - Local

August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.5

Anti-Fuse Technology

 - Dielectric that prevents current flow
- Applying a voltage melts the dielectric




- One time programmable – not really *reconfigurable* computing

August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.6

●●● Anti-Fuse Technology (cont.)

 
- Negligible programming overhead
- Fast routing
- Nonvolatile (hold data after power off)
- High level of security:
 - No bitstream can be intercepted in the field
 - Need a Scanning Electron Microscope (SEM) to figure out the anti-fuse states



August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.7 © Actel

●●● E(E)PROM Technology


- To program a transistor, a voltage differential between the access/floating gates accelerates electrons from the source fast enough to travel across the insulator to the floating gate
- Electrons prevent the access gate from closing
- EPROM – Erasable Programmable Read-Only Memory
 - Nonvolatile
 - Can be erased using UV light
- EEPROM – Electrically Erasable Programmable Read-Only Memory
 - Removes the electrons by reversing the voltage differential
 - Limited number of erases possible
 - Precursor to Flash technology

 

August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.8

●●● Flash / EEPROM Devices

 
- Migrated from early PLD technology
- Traditionally based on AND/OR architecture
- High ratio of logic-to-registers
- Future of Flash devices?
 - Logic elements (LUTs and flip flops)
 - Segmented routing
 - Low logic to register ratio



August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.9

●●● SRAM Technology

 - SRAM – Static Random Access Memory
- SRAM cells are larger (6 transistors) than anti-fuse or EEPROM
 - Slower
 - Less computational power per λ^2
- SRAM bits can be programmed many times



August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.10

●●● Which Devices to Study?




- SRAM – ~95%, Flash/Anti-fuse – ~5%

August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.11

●●● Lookup Tables (LUTs)

 - What is a Lookup Table (LUT)?
 - In most generic terms, a pre-loaded memory



```
int table[256] = {1,7,8,9,...14};
int Q, addr;
...
Q = table[addr];
```

- Great way of implementing some function without calculation – a **cheat sheet**


Q7: What is the answer to life, the universe, and everything?



Answer Key
.
.
.
A(Q7) = 42

August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.12

LUTs and Digital Logic

 

- Each k -LUT operates on k one-bit inputs
- Output is one data bit
- Can perform any Boolean function of k inputs

August 29, 2006

CprE 583 – Reconfigurable Computing

Lect-03.13

LUTs and Digital Logic (cont.)

- k inputs $\rightarrow 2^k$ possible input values
- k -LUT corresponds to $2^k \times 1$ bit memory
- How many different functions?
 - Two-input (A_1, A_2) case
 - $F(A_1, A_2) = \{0, A_1 \text{ nor } A_2, \bar{A}_1 \text{ and } A_2, \bar{A}_1, A_1 \text{ and } \bar{A}_2, \bar{A}_2, A_1 \text{ xor } A_2, A_1 \text{ nand } A_2, A_1 \text{ and } A_2, A_1 \text{ xnor } A_2, \bar{A}_2, \bar{A}_1 \text{ or } A_2, A_1, A_1 \text{ or } \bar{A}_2, A_1 \text{ or } A_2, 1\} = 16$ different possibilities
- What to store in the LUT?

A_1	A_2	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

August 29, 2006

CprE 583 – Reconfigurable Computing

Lect-03.14

LUTs and Digital Logic

- $F(\text{input})$ can be 0 or 1 independently for each of the 2^k bits
 - 2^{2^k} possible functions
 - Not all patterns are unique ($k!$ permutations of the inputs)
 - Approximately $2^{2^k} / k!$ unique functions

A_1	A_2	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

- Is this efficient?
- How to select k value?

August 29, 2006


CprE 583 – Reconfigurable Computing

Lect-03.15

LUT Mapping

- How many gates in a 2-LUT + flip-flop?

A_1	A_2	f
0	0	x_0
0	1	x_1
1	0	x_2
1	1	x_3

 

August 29, 2006


CprE 583 – Reconfigurable Computing

Lect-03.16

LUT Mapping (cont.)

- Implement the following logic function with k -LUTs, for $k=\{2, 3, 4\}$:
 
$$F = A_0 A_1 A_3 + A_1 A_2 \bar{A}_3 + \bar{A}_0 \bar{A}_1 \bar{A}_2$$



August 29, 2006

CprE 583 – Reconfigurable Computing

Lect-03.17

Logic Block Granularity

- Each k -LUT requires 2^k configuration bits:
 - The 2-LUT implementation requires $2^2 \times 7 = 28$ bits
 - The 3-LUT needs $2^3 \times 3 = 24$ bits
 - The 4-LUT needs just $2^4 \times 1 = 16$ bits
- Using configuration bits as area measure (area cost), the 4-LUT implementation achieves minimum logic area


August 29, 2006

CprE 583 – Reconfigurable Computing

Lect-03.18

Interconnect

 
- Problem:
 - Thousands of operators producing results
 - Each taking as outputs the results of other bit operators
 - Initial assumptions – have to connect them all *simultaneously*



August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.19

Interconnect Design Issues

 - *Flexibility* – route anything (within reason?)
 - Bisection bandwidth
 - Simultaneous routes
- *Area*
 - Bisection bandwidth
 - Switches
- *Delay (and Power)*
 - Switches in path
 - Wire length
- *Routability* – difficulty of finding a route



August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.20


General Routing Architecture

- A *wire segment* is a wire unbroken by programmable switches
 - Typically one switch is attached to each end of a wire segment
- A *track* is a sequence of one or more wire segments in a line
- A routing channel is a group of parallel tracks
- A *connection block* provides connectivity from the inputs and outputs of a logic block to the wire segments in the channels

August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.21

Attempt 1 – Crossbar

 
- Any operator may want to take as input the output of any other operator
- Let n be the number of LUTs, and l the length of wire
 - Delay:
 - Parasitic loads = kn
 - Switches/path = l
 - Wire length = $O(kn)$
 - Delay = $O(kn)$
 - Area:
 - Bisection BW = n
 - Switches = kn^2
 - Area = $O(n^2)$




August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.22

Attempt 2 – Mesh

 - Put connected components together
- Transitive fan-in grows faster than the close sites:




 - Let w be the channel width
 - Delay:
 - Switches/path = l
 - Wire length = $O(l)$
 - Best Delay = $O(w)$
 - Worst Delay = $O(n^2/w)$
 - Area:
 - Bisection BW = $wn^{2/3}$
 - Switches = $O(nw^2)$
 - Area = $O(nw^2)$



August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.23

Segmentation

 


- Segmentation distribution: how many of each length?
- Longer length
 - Better performance?
 - Reduced routability?

August 29, 2006 CprE 583 – Reconfigurable Computing Lect-03.24

●●● Interconnect Area/Delay

 - Interconnect area = $\sim 10x$ configuration memory = $\sim 100x$ logic
- The interconnect constitutes $\sim 90\%$ of the total area and 70-80% of the total delay
- See [Deh96A] for details




August 29, 2006

CprE 583 - Reconfigurable Computing

Lect-03.25

●●● Architectural Issues [AhmRos04A]

 - What values of N , I , and K minimize the following parameters?
 - Area
 - Delay
 - Area-delay product
- Assumptions
 - All routing wires length 4
 - Fully populated IMUX
 - Wiring is half pass transistor, half tri-state
 - 180 nm
 - Routing performed with $W_{\min} + 30\%$ tracks



August 29, 2006

CprE 583 - Reconfigurable Computing

Lect-03.26

●●● Summary

- Three basic types of FPGA devices
 - Antifuse
 - EEPROM
 - SRAM
- Key issues for SRAM FPGA are logic cluster, connection box, and switch box.
- Most tasks have structure, which can be exploited by LUT arrays with programmable interconnect (FPGAs)
- Cannot afford full interconnect, or make all interconnects local

August 29, 2006

CprE 583 - Reconfigurable Computing

Lect-03.27