

CprE / ComS 583
Reconfigurable Computing


Prof. Joseph Zambreno
 Department of Electrical and Computer Engineering
 Iowa State University

Lecture #16 – Introduction to VHDL I


Quick Points


- Midterm was a semi-success
 - Right time estimate, wrong planet (Pluto?)
 - Everyone did OK
- HW #3 extended to Thursday, 10/18 (12:00pm)
- Resources for the next couple of weeks
 - Sundar Rajan, *Essential VHDL: RTL Synthesis Done Right*, 1997.
 - Will add some VHDL links to CprE 583 web page sometime this week

October 16, 2006 CprE 583 – Reconfigurable Computing Lect-16.2


VHDL


- VHDL is a language for describing digital hardware used by industry worldwide
- **VHDL** is an acronym for **V**HSIC (**V**ery **H**igh **S**peed **I**ntegrated **C**ircuit) **H**ardware **D**escription **L**anguage
- Developed in the early '80s
- Three versions in common use: VHDL-87, VHDL-93, VHDL-01


October 16, 2006 CprE 583 – Reconfigurable Computing Lect-16.3


VHDL v. Verilog


VHDL	Verilog
Government Developed	Commercially Developed
Ada based	C based
Strongly Type Cast	Mildly Type Cast
Difficult to learn	Easier to Learn
More Powerful	Less Powerful

October 16, 2006 CprE 583 – Reconfigurable Computing Lect-16.4


VHDL for Synthesis

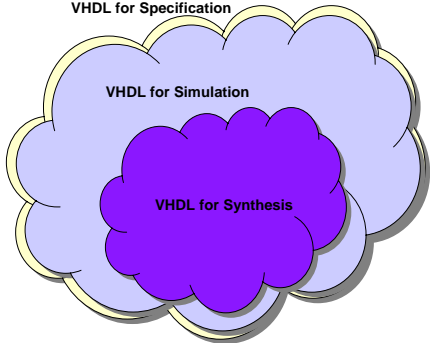

October 16, 2006 CprE 583 – Reconfigurable Computing Lect-16.5


Outline

- Introduction
- VHDL Fundamentals
- Design Entities
- Libraries
- Logic, Wires, and Buses
- VHDL Design Styles
- Introductory Testbenches

October 16, 2006 CprE 583 – Reconfigurable Computing Lect-16.6

Naming and Labeling

- VHDL is not case sensitive

Example:

Names or labels
databus
Databus
DataBus
DATABUS
 are all equivalent

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.7

Naming and Labeling (cont.)

General rules of thumb (according to VHDL-87)

- All names should start with an alphabet character (a-z or A-Z)
- Use only alphabet characters (a-z or A-Z) digits (0-9) and underscore (_)
- Do not use any punctuation or reserved characters within a name (!, ?, ., &, +, -, etc.)
- Do not use two or more consecutive underscore characters (__) within a name (e.g., Sel__A is invalid)
- All names and labels in a given entity and architecture must be unique

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.8

Free Format

- VHDL is a “free format” language
 No formatting conventions, such as spacing or indentation imposed by VHDL compilers. Space and carriage return treated the same way.

Example:

```
if (a=b) then
or
if (a=b) then
or
if (a =
b) then
are all equivalent
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.9

Comments

- Comments in VHDL are indicated with a “double dash”, i.e., “--”
 - Comment indicator can be placed anywhere in the line
 - Any text that follows in the same line is treated as a comment
 - Carriage return terminates a comment
 - No method for commenting a block extending over a couple of lines

Examples:


```
-- main subcircuit
Data_in <= Data_bus; -- reading data from the input FIFO
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.10

Design Entity

 

Design Entity - most basic building block of a design

One *entity* can have many different *architectures*


October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.11

Entity Declaration

 - Entity Declaration* describes the interface of the component, i.e. the *input* and *output* ports



October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.12

Entity Declaration (cont.)

```

ENTITY entity_name IS
  PORT (
    port_name : signal_mode signal_type;
    port_name : signal_mode signal_type;
    .....
    port_name : signal_mode signal_type);
END entity_name;

```

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.13

Architecture

- Describes an implementation of a design entity
- Architecture example:

```

ARCHITECTURE model OF nand_gate IS
  BEGIN
    z <= a NAND b;
  END model;

```

- Simplified syntax:

```

ARCHITECTURE architecture_name OF entity_name IS
  [ declarations ]
  BEGIN
    code
  END architecture_name;

```

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.14

Entity Declaration and Architecture

nand_gate.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_gate IS
  PORT(
    a : IN STD_LOGIC;
    b : IN STD_LOGIC;
    z : OUT STD_LOGIC);
END nand_gate;

ARCHITECTURE model OF nand_gate IS
  BEGIN
    z <= a NAND b;
  END model;


```

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.15

Port Modes

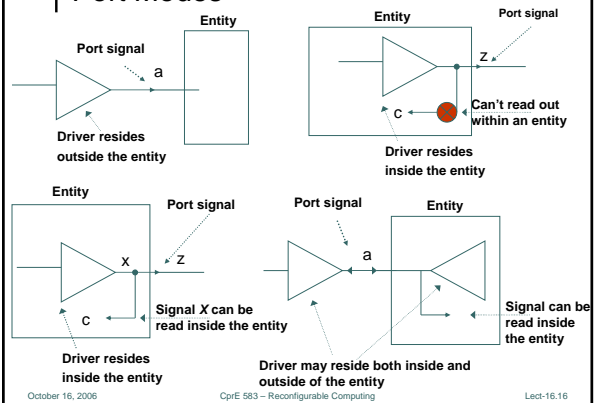

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.16

Port Modes (cont.)

- The *Port Mode* of the interface describes the direction in which data travels with respect to the *component*
 - In:** Data comes in this port and can only be read within the entity. It can appear only on the **right side** of a signal or variable assignment
 - Out:** The value of an output port can only be updated within the entity. It can only appear on the **left side** of a signal assignment
 - Inout:** The value of a bi-directional port can be read and updated within the entity model. It can appear on **both sides** of a signal assignment
 - Buffer:** Used for a signal that is an output from an entity. The value of the signal can be used inside the entity, which means that in an assignment statement the signal can appear on the left and right sides of the <= operator

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.17

Library Declarations

IEEE Library declaration

Use all definitions from the package std_logic_1164

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_gate IS
  PORT(
    a : IN STD_LOGIC;
    b : IN STD_LOGIC;
    z : OUT STD_LOGIC);
END nand_gate;

ARCHITECTURE model OF nand_gate IS
  BEGIN
    z <= a NAND b;
  END model;

```

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.18

Library Declarations (cont.)


```
LIBRARY library_name;
USE library_name.pkg_name.pkg_parts;
```

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.19

Library Components

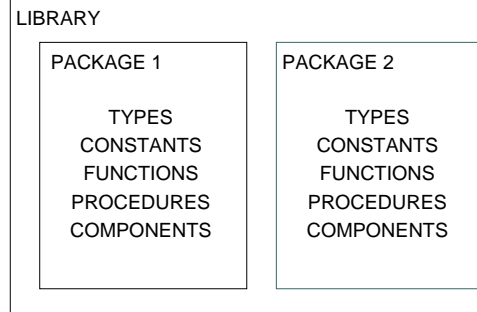

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.20

Common Libraries

- IEEE
 - Specifies multi-level logic system, including STD_LOGIC, and STD_LOGIC_VECTOR data types
 - Needs to be explicitly declared
- STD
 - Specifies pre-defined data types (BIT, BOOLEAN, INTEGER, REAL, SIGNED, UNSIGNED, etc.), arithmetic operations, basic type conversion functions, basic text i/o functions, etc.
 - Visible by default
- WORK
 - Current designs after compilation
 - Visible by default

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.21

STD_LOGIC Demystified

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_gate IS
  PORT(
    a : IN STD_LOGIC;
    b : IN STD_LOGIC;
    z : OUT STD_LOGIC);
END nand_gate;

ARCHITECTURE model OF nand_gate IS
BEGIN
  z <= a NAND b;
END model;
```

Hmm?

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.22

STD_LOGIC Demystified (cont.)

Value	Meaning
'X'	Forcing (Strong driven) Unknown
'0'	Forcing (Strong driven) 0
'1'	Forcing (Strong driven) 1
'Z'	High Impedance
'W'	Weak (Weakly driven) Unknown
'L'	Weak (Weakly driven) 0. Models a pull down.
'H'	Weak (Weakly driven) 1. Models a pull up.
'-'	Don't Care

October 16, 2006

CprE 583 - Reconfigurable Computing

Lect-16.23

Resolving Logic Levels

	X	0	1	Z	W	L	H	-
X	X	X	X	X	X	X	X	X
0	X	0	X	0	0	0	0	X
1	X	X	1	1	1	1	1	X
Z	X	0	1	Z	W	L	H	X
W	X	0	1	W	W	W	W	X
L	X	0	1	L	W	L	W	X
H	X	0	1	H	W	W	H	X
-	X	X	X	X	X	X	X	X


October 16, 2006

CprE 583 - Reconfigurable Computing


Lect-16.24

Wires and Buses

- SIGNAL a : STD_LOGIC;

 

 - SIGNAL b : STD_LOGIC_VECTOR(7 DOWNTO 0);



October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.25

Standard Logic Vectors

```
SIGNAL a: STD_LOGIC;
SIGNAL b: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL c: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL d: STD_LOGIC_VECTOR(7 DOWNTO 0);
SIGNAL e: STD_LOGIC_VECTOR(15 DOWNTO 0);
SIGNAL f: STD_LOGIC_VECTOR(8 DOWNTO 0);

a <= '1';
b <= "0000";           -- Binary base assumed by default
c <= B"0000";         -- Binary base explicitly specified
d <= "0110_0111";    -- To increase readability
e <= X"AF67";         -- Hexadecimal base
f <= O"723";          -- Octal base
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.26

Vectors and Concatenation

```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL c, d, e: STD_LOGIC_VECTOR(7 DOWNTO 0);

a <= "0000";
b <= "1111";
c <= a & b;           -- c = "00001111"

d <= '0' & "0001111"; -- d <= "00001111"


e <= '0' & '0' & '0' & '0' & '1' & '1' &
    '1' & '1';       -- e <= "00001111"
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.27

VHDL Design Styles

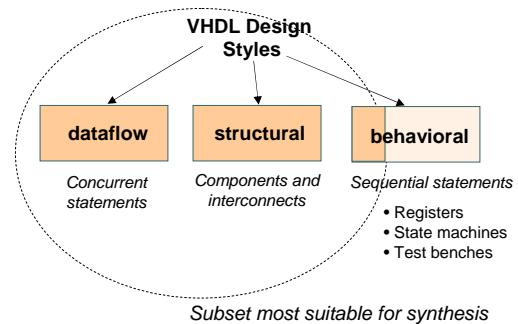

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.28

XOR3 Example



```
ENTITY xor3 IS
  PORT (
    A : IN STD_LOGIC;
    B : IN STD_LOGIC;
    C : IN STD_LOGIC;
    Result : OUT STD_LOGIC);
end xor3;
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.29

Dataflow Descriptions

- Describes how data moves through the system and the various processing steps
- Dataflow uses series of concurrent statements to realize logic
 - Concurrent statements are evaluated at the same time
 - Order of these statements doesn't matter
- Dataflow is most useful style when series of Boolean equations can represent a logic

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.30

XOR3 Example (cont.)

```

ARCHITECTURE dataflow OF xor3 IS
SIGNAL U1_out: STD_LOGIC;
BEGIN
    U1_out <= A XOR B;
    Result <= U1_out XOR C;
END dataflow;
    
```



Structural Description

- Structural design is the simplest to understand
 - Closest to schematic capture
 - Utilizes simple building blocks to compose logic functions
- Components are interconnected in a hierarchical manner
- Structural descriptions may connect simple gates or complex, abstract components
- Structural style is useful when expressing a design that is naturally composed of sub-blocks

XOR3 Example (cont.)

```

ARCHITECTURE structural OF xor3 IS
SIGNAL U1_OUT: STD_LOGIC;
COMPONENT xor2 IS
    PORT (
        I1 : IN STD_LOGIC;
        I2 : IN STD_LOGIC;
        Y : OUT STD_LOGIC;
    );
END COMPONENT;
BEGIN
    U1: xor2 PORT MAP (I1 => A,
                       I2 => B,
                       Y => U1_OUT);
    U2: xor2 PORT MAP (I1 => U1_OUT,
                       I2 => C,
                       Y => Result);
END structural;
    
```



Component and Instantiation

- Named association connectivity (recommended)
- Positional association connectivity (not recommended)

```

COMPONENT xor2 IS
    PORT(
        I1 : IN STD_LOGIC;
        I2 : IN STD_LOGIC;
        Y : OUT STD_LOGIC
    );
END COMPONENT;
U1: xor2 PORT MAP (I1 => A,
                   I2 => B,
                   Y => U1_OUT);
    
```

```

COMPONENT xor2 IS
    PORT(
        I1 : IN STD_LOGIC;
        I2 : IN STD_LOGIC;
        Y : OUT STD_LOGIC
    );
END COMPONENT;
U1: xor2 PORT MAP (A, B, U1_OUT);
    
```


Behavioral Description

- Accurately models what happens on the inputs and outputs of the black box
- Uses PROCESS statements in VHDL

```

ARCHITECTURE behavioral OF xor3 IS
BEGIN
    xor3_behave: PROCESS (A,B,C)
    BEGIN
        IF ((A XOR B XOR C) = '1') THEN
            Result <= '1';
        ELSE
            Result <= '0';
        END IF;
    END PROCESS xor3_behave;
END behavioral;
    
```

Testbenches

 

Testbench Definition

- *Testbench* applies stimuli (drives the inputs) to the Design Under Test (DUT) and (optionally) verifies expected outputs
- The results can be viewed in a waveform window or written to a file
- Since *Testbench* is written in VHDL, it is not restricted to a single simulation tool (portability)
- The same *Testbench* can be easily adapted to test different implementations (i.e. different *architectures*) of the same design

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.37

Testbench Anatomy

```

ENTITY tb IS
    --TB entity has no ports
END tb;

ARCHITECTURE arch_tb OF tb IS
    --Local signals and constants
    COMPONENT TestComp --All DUT component declarations
        PORT ( );
    END COMPONENT;
-----
BEGIN
    testSequence: PROCESS -- Input stimuli
    END PROCESS;
    DUT:TestComp PORT MAP(); -- Instantiations of DUTs
END arch_tb;
    
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.38

Testbench for XOR3

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY xor3_tb IS
END xor3_tb;

ARCHITECTURE xor3_tb_architecture OF xor3_tb IS
COMPONENT xor3
PORT(
    A : IN STD_LOGIC;
    B : IN STD_LOGIC;
    C : IN STD_LOGIC;
    Result : OUT STD_LOGIC );
END COMPONENT;

-- Stimulus signals - mapped to the input and inout ports of tested entity
SIGNAL test_vector: STD_LOGIC_VECTOR(2 DOWNTO 0);
SIGNAL test_result : STD_LOGIC;
    
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.39

Testbench for XOR3 (cont.)

```

BEGIN
UUT : xor3
    PORT MAP (
        A => test_vector(0),
        B => test_vector(1),
        C => test_vector(2),
        Result => test_result);

Testing: PROCESS
BEGIN
    test_vector <= "000";
    WAIT FOR 10 ns;
    test_vector <= "001";
    WAIT FOR 10 ns;
    test_vector <= "100";
    WAIT FOR 10 ns;
    test_vector <= "101";
    WAIT FOR 10 ns;
    test_vector <= "110";
    WAIT FOR 10 ns;
    test_vector <= "111";
    WAIT FOR 10 ns;
END PROCESS;
END xor3_tb_architecture;
    
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.40

What is a Process?

A process is a sequence of instructions referred to as sequential statements

- A process can be given a unique name using an optional LABEL
- This is followed by the keyword PROCESS
- The keyword BEGIN is used to indicate the start of the process
- All statements within the process are executed **SEQUENTIALLY**. Hence, order of statements is important
- A process must end with the keywords END PROCESS

```

Testing: PROCESS
BEGIN
    test_vector<="00";
    WAIT FOR 10 ns;
    test_vector<="01";
    WAIT FOR 10 ns;
    test_vector<="10";
    WAIT FOR 10 ns;
    test_vector<="11";
    WAIT FOR 10 ns;
END PROCESS;
    
```

The keyword PROCESS

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.41

Process Execution

- The execution of statements continues sequentially till the last statement in the process
- After execution of the last statement, the control is again passed to the beginning of the process

```

Testing: PROCESS
BEGIN
    test_vector<="00";
    WAIT FOR 10 ns;
    test_vector<="01";
    WAIT FOR 10 ns;
    test_vector<="10";
    WAIT FOR 10 ns;
    test_vector<="11";
    WAIT FOR 10 ns;
END PROCESS;
    
```

Order of execution

Program control is passed to the first statement after BEGIN

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.42

••• | WAIT Statements

- The last statement in the PROCESS is a **WAIT** instead of WAIT FOR 10 ns
- This will cause the PROCESS to **suspend indefinitely** when the WAIT statement is executed
- This form of WAIT can be used in a process included in a testbench when all possible combinations of inputs have been tested or a non-periodical signal has to be generated

```
Testing: PROCESS
BEGIN
  test_vector<="00";
  WAIT FOR 10 ns;
  test_vector<="01";
  WAIT FOR 10 ns;
  test_vector<="10";
  WAIT FOR 10 ns;
  test_vector<="11";
  WAIT;
END PROCESS;
```

Order of execution ↓

Program execution stops here


October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.43

••• | WAIT FOR vs. WAIT

 WAIT FOR: waveform will keep repeating itself forever



WAIT: waveform will keep its state after the last wait instruction.



October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.44

••• | Loop Statement

- Loop Statement

```
FOR i IN range LOOP
  statements
END LOOP;
```

- Repeats a Section of VHDL Code
 - Example: process every element in an array in the same way

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.45

••• | Loop Statement Example

```
Testing: PROCESS
BEGIN
  test_vector<="000";
  FOR i IN 0 TO 7 LOOP
    WAIT FOR 10 ns;
    test_vector<=test_vector+"001";
  END LOOP;
END PROCESS;
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.46

••• | Loop Statement Example (cont.)

```
Testing: PROCESS
BEGIN
  test_ab<="00";
  test_sel<="00";
  FOR i IN 0 TO 3 LOOP
    FOR j IN 0 TO 3 LOOP
      WAIT FOR 10 ns;
      test_ab<=test_ab+"01";
    END LOOP;
    test_sel<=test_sel+"01";
  END LOOP;
END PROCESS;
```

October 16, 2006

CprE 583 – Reconfigurable Computing

Lect-16.47