

# CprE / ComS 583 Reconfigurable Computing

Prof. Joseph Zambreno  
Department of Electrical and Computer Engineering  
Iowa State University

Lecture #17 – Introduction to VHDL II

## Quick Points

- Midterm course evaluation form available on WebCT
- HW #4 – VHDL for synthesis
  - Due Thursday, November 2 (12:00pm)
  - Work with your project group

October 18, 2006 CprE 583 – Reconfigurable Computing Lect-17.2

## Recap – PROCESS Block

- List of signals to which the process is sensitive
- Whenever there is an event on any of the signals in the sensitivity list, the process fires
- Every time the process fires, it will run in its entirety
- WAIT statements are NOT allowed in a processes with sensitivity list

label: process (sensitivity list)  
 declaration part  
 begin  
 statement part  
 end process;

October 18, 2006 CprE 583 – Reconfigurable Computing Lect-17.3

## Processes in VHDL

- Processes describe sequential behavior
- Processes in VHDL are very powerful statements
  - Allow to define an arbitrary behavior that may be difficult to represent by a real circuit
  - Not every process can be synthesized
- Use processes with caution in the code to be synthesized
- Use processes freely in testbenches

October 18, 2006 CprE 583 – Reconfigurable Computing Lect-17.4

## Mixed Style Modeling

The diagram illustrates a process block with the following components:

- Ports:** Two 'in' ports on the left, two 'out' ports on the left, and one 'inout' port on the left.
- Process:** A central box containing the code:
 

```
Process (clk)
if clk'Event and
clk='1' then
Count <= Count + 1;
end if;
end process;
```
- Components:** Two boxes labeled 'Component' on the right, connected to the process.
- Signal:** A line labeled 'Signal' connects the process to the components.
- Dataflow Expression:** The expression `X <= (Y = '1') and (Z = "110")` is shown below the process.

October 18, 2006 CprE 583 – Reconfigurable Computing Lect-17.5

## Design Exercise

- Create the entity declaration for some component of your final project
  - Names, ports, signal types
  - Just the structure

```
ENTITY entity_name IS
PORT (
port_name : signal_mode signal_type;
port_name : signal_mode signal_type;
.....
port_name : signal_mode signal_type);
END entity_name;
```

October 18, 2006 CprE 583 – Reconfigurable Computing Lect-17.6

## Outline

- Recap
- Dataflow Style
  - Logic Gates
  - Decoders / Encoders
  - Arithmetic Functions
- A Structural Example
- Behavioral Style
  - Registers
  - Counters

October 18, 2006

CprE 583 – Reconfigurable Computing

Lect-17.7

## Dataflow VHDL

- All concurrent statements
- Major instructions:
  - Concurrent signal assignment ( $\leftarrow$ )
  - Conditional concurrent signal assignment (when-else)
  - Selected concurrent signal assignment (with-select-when)
  - Generate scheme for equations (for-generate)

October 18, 2006

CprE 583 – Reconfigurable Computing

Lect-17.8

## Dataflow Example – Full Adder

```
ENTITY fulladd IS
  PORT ( x   : IN     STD_LOGIC ;
         y   : IN     STD_LOGIC ;
         cin : IN     STD_LOGIC ;
         s   : OUT    STD_LOGIC ;
         cout : OUT   STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE dataflow OF fulladd IS
BEGIN
  s <= x XOR y XOR cin ;
  cout <= (x AND y) OR (cin AND x) OR (cin AND y) ;
END dataflow ;
```

October 18, 2006

CprE 583 – Reconfigurable Computing

Lect-17.9

## Logical Operators

- AND, OR, NAND, NOR, XOR, NOT, XNOR
- Only NOT has order of precedence
- Otherwise, no implied precedence
- Example:  $y = ab + cd$ 
  - $y <= a \text{ AND } b \text{ OR } c \text{ AND } d$ ; -- Equivalent to
  - $y <= ((a \text{ AND } b) \text{ OR } c) \text{ AND } d$ ; -- Equivalent to
  - $y = (ab + cd)$

October 18, 2006

CprE 583 – Reconfigurable Computing

Lect-17.10

## Arithmetic Operators

- For basic arithmetic operators on `std_logic` types, use the IEEE libraries
- Standard addition, subtraction, multiplication

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all; -- or std_logic_signed.all
```

```
signal A : STD_LOGIC_VECTOR(3 downto 0);
signal B : STD_LOGIC_VECTOR(3 downto 0);
signal C : STD_LOGIC_VECTOR(3 downto 0);
.....
C <= A + B;
```

October 18, 2006

CprE 583 – Reconfigurable Computing

Lect-17.11

## 16-bit Addition

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY adder16 IS
  PORT ( Cin      : IN     STD_LOGIC ;
         X, Y     : IN     STD_LOGIC_VECTOR(15 DOWNT0 0) ;
         S        : OUT    STD_LOGIC_VECTOR(15 DOWNT0 0) ;
         Cout     : OUT    STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE Dataflow OF adder16 IS
  SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNT0 0) ;
BEGIN
  Sum <= ('0' & X) + Y + Cin ;
  S <= Sum(15 DOWNT0 0) ;
  Cout <= Sum(16) ;
END Dataflow ;
```

October 18, 2006


CprE 583 – Reconfigurable Computing

Lect-17.12

## Conditional Signal Assignment
 
### When - Else

```
target_signal <= value1 when condition1 else
                value2 when condition2 else
                . . .
                valueN-1 when conditionN-1 else
                valueN;
```



October 18, 2006

CprE 583 - Reconfigurable Computing

Lect-17.13

## 2:1 Multiplexer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT (w0, w1, s : IN  STD_LOGIC ;
          f : OUT STD_LOGIC) ;
END mux2to1 ;
```

```
ARCHITECTURE dataflow OF mux2to1 IS
BEGIN
    f <= w0 WHEN s = '0' ELSE w1 ;
END dataflow ;
```

October 18, 2006

CprE 583 - Reconfigurable Computing

Lect-17.14

## Priority Encoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY priority IS
    PORT (w : IN  STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y : OUT STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT STD_LOGIC) ;
END priority ;
```

```
ARCHITECTURE dataflow OF priority IS
BEGIN
    y <= "11" WHEN w(3) = '1' ELSE
        "10" WHEN w(2) = '1' ELSE
        "01" WHEN w(1) = '1' ELSE
        "00" ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END dataflow ;
```

October 18, 2006


CprE 583 - Reconfigurable Computing

Lect-17.15

## Selected Signal Assignment
 
### With - Select - When

```
with choice_expression select
target_signal <= expression1 when choices_1,
                expression2 when choices_2,
                . . .
                expressionN when choices_N;
```



October 18, 2006

CprE 583 - Reconfigurable Computing

Lect-17.16

## 4:1 Multiplexer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY mux4to1 IS
    PORT (w0, w1, w2, w3 : IN  STD_LOGIC ;
          s : IN  STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          f : OUT STD_LOGIC) ;
END mux4to1 ;
```

```
ARCHITECTURE dataflow OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN "00",
          w1 WHEN "01",
          w2 WHEN "10",
          w3 WHEN OTHERS ;
END dataflow ;
```

October 18, 2006

CprE 583 - Reconfigurable Computing

Lect-17.17

## Generate Statements

- A way to simplify a pattern of concurrent statements
- Can't do regular FOR...LOOP in dataflow

### For - Generate

```
label: FOR identifier IN range GENERATE
    BEGIN
        {Concurrent Statements}
    END GENERATE;
```

October 18, 2006

CprE 583 - Reconfigurable Computing

Lect-17.18

### Parity Example

```

ARCHITECTURE parity_dataflow OF parity IS
SIGNAL xor_out: STD_LOGIC_VECTOR (7 DOWNTO 0);
BEGIN
  xor_out(0) <= parity_in(0);
  G2: FOR i IN 0 TO 6 GENERATE
    xor_out(i+1) <= xor_out(i) XOR parity_in(i+1);
  end generate G2;
  parity_out <= xor_out(7);
END parity_dataflow;

```

October 18, 2006      CprE 583 – Reconfigurable Computing      Lect-17.19

### Structural Mapping Example

October 18, 2006      CprE 583 – Reconfigurable Computing      Lect-17.20

### Structural Mapping Example (cont.)

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority_resolver IS
  PORT (r : IN STD_LOGIC_VECTOR(5 DOWNTO 0) ;
        s : IN STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        z : OUT STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END priority_resolver;

ARCHITECTURE structural OF priority_resolver IS

SIGNAL p : STD_LOGIC_VECTOR (3 DOWNTO 0) ;
SIGNAL q : STD_LOGIC_VECTOR (1 DOWNTO 0) ;
SIGNAL ena : STD_LOGIC ;


```

October 18, 2006      CprE 583 – Reconfigurable Computing      Lect-17.21

### Structural Mapping Example (cont.)

```

COMPONENT mux2to1
  PORT (w0, w1, s : IN STD_LOGIC ;
        f : OUT STD_LOGIC ) ;
END COMPONENT ;

COMPONENT priority
  PORT (w : IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;
        y : OUT STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        z : OUT STD_LOGIC ) ;
END COMPONENT ;

COMPONENT dec2to4
  PORT (w : IN STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        En : IN STD_LOGIC ;
        y : OUT STD_LOGIC_VECTOR(0 TO 3) ) ;
END COMPONENT ;

```

October 18, 2006      CprE 583 – Reconfigurable Computing      Lect-17.22

### Structural Mapping Example (cont.)

```

BEGIN
  u1: mux2to1 PORT MAP (w0 => r(0) ,
                       w1 => r(1) ,
                       s => s(0) ,
                       f => p(0));

  p(1) <= r(2);
  p(1) <= r(3);
  u2: mux2to1 PORT MAP (w0 => r(4) ,
                       w1 => r(5) ,
                       s => s(1) ,
                       f => p(3));

  u3: priority PORT MAP (w => p ,
                       y => q ,
                       z => ena);

  u4: dec2to4 PORT MAP (w => q ,
                       En => ena ,
                       y => z);

END structural;

```

October 18, 2006      CprE 583 – Reconfigurable Computing      Lect-17.23

### Behavioral Latch

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
  PORT (D, Clock : IN STD_LOGIC ;
        Q : OUT STD_LOGIC ) ;
END latch ;

ARCHITECTURE Behavior OF latch IS
BEGIN
  PROCESS ( D, Clock )
  BEGIN
    IF Clock = '1' THEN
      Q <= D ;
    END IF ;
  END PROCESS ;
END Behavior;

```

Clock	D	Q(t+1)
0	-	Q(t)
1	0	0
1	1	1


October 18, 2006      CprE 583 – Reconfigurable Computing      Lect-17.24

## Behavioral Flip Flop

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY flipflop IS
    PORT ( D, Clock : IN STD_LOGIC ;
          Q          : OUT STD_LOGIC );
END flipflop ;
```
 
```
ARCHITECTURE Behavior_1 OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior_1 ;
```



Truth table

Clk	D	Q(t+1)
↑	0	0
↑	1	1
0	-	Q(t)
1	-	Q(t)

October 18, 2006


CprE 583 - Reconfigurable Computing

Lect-17.25
 
## N-bit Register with Reset

```
ENTITY regn IS
    GENERIC ( N : INTEGER := 16 ) ;
    PORT ( D          : IN STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
          Resetn, Clock : IN STD_LOGIC ;
          Q          : OUT STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
END regn ;
```

```
ARCHITECTURE Behavior OF regn IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= (OTHERS => '0') ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



October 18, 2006


CprE 583 - Reconfigurable Computing

Lect-17.26
 
## 4-bit Up-Counter with Reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
```

```
ENTITY upcount IS
    PORT ( Clock, Resetn, Enable : IN STD_LOGIC ;
          Q : OUT STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END upcount ;
```




October 18, 2006

CprE 583 - Reconfigurable Computing

Lect-17.27
 
## 4-bit Up-Counter with Reset (cont.)

```
ARCHITECTURE Behavior OF upcount IS
    SIGNAL Count : STD_LOGIC_VECTOR(3 DOWNTO 0) ;
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Count <= "0000" ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF Enable = '1' THEN
                Count <= Count + 1 ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;
```




October 18, 2006

CprE 583 - Reconfigurable Computing

Lect-17.28

## Shift Register With Parallel Load

 

October 18, 2006


CprE 583 - Reconfigurable Computing

Lect-17.29
 
## Shift Register With Load (cont.)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY shift4 IS
    PORT ( D          : IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Enable : IN STD_LOGIC ;
          Load   : IN STD_LOGIC ;
          Sin    : IN STD_LOGIC ;
          Clock  : IN STD_LOGIC ;
          Q      : BUFFER STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END shift4 ;
```



October 18, 2006

CprE 583 - Reconfigurable Computing

Lect-17.30

## Shift Register With Load (cont.)

ARCHITECTURE Behavior\_1 OF shift4 IS

BEGIN

PROCESS (Clock)

BEGIN

IF Clock'EVENT AND Clock = '1' THEN

IF Load = '1' THEN

Q <= D;

ELSIF Enable = '1' THEN

Q(0) <= Q(1);

Q(1) <= Q(2);

Q(2) <= Q(3);


Q(3) <= Sin;

END IF;

END IF;

END PROCESS;

END Behavior\_1;

 

October 18, 2006

CprE 583 - Reconfigurable Computing

Lect-17.31